
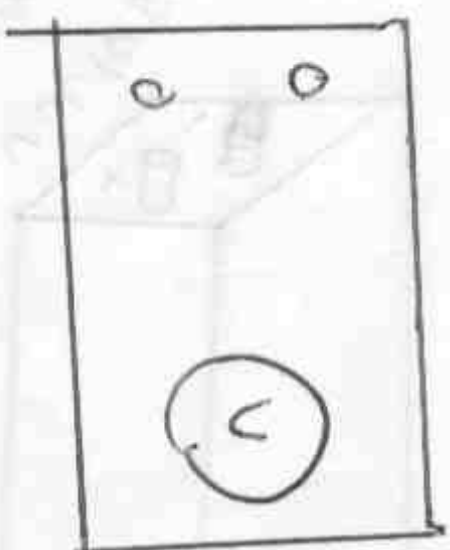


③ / ⑦ Three terminals regulator.

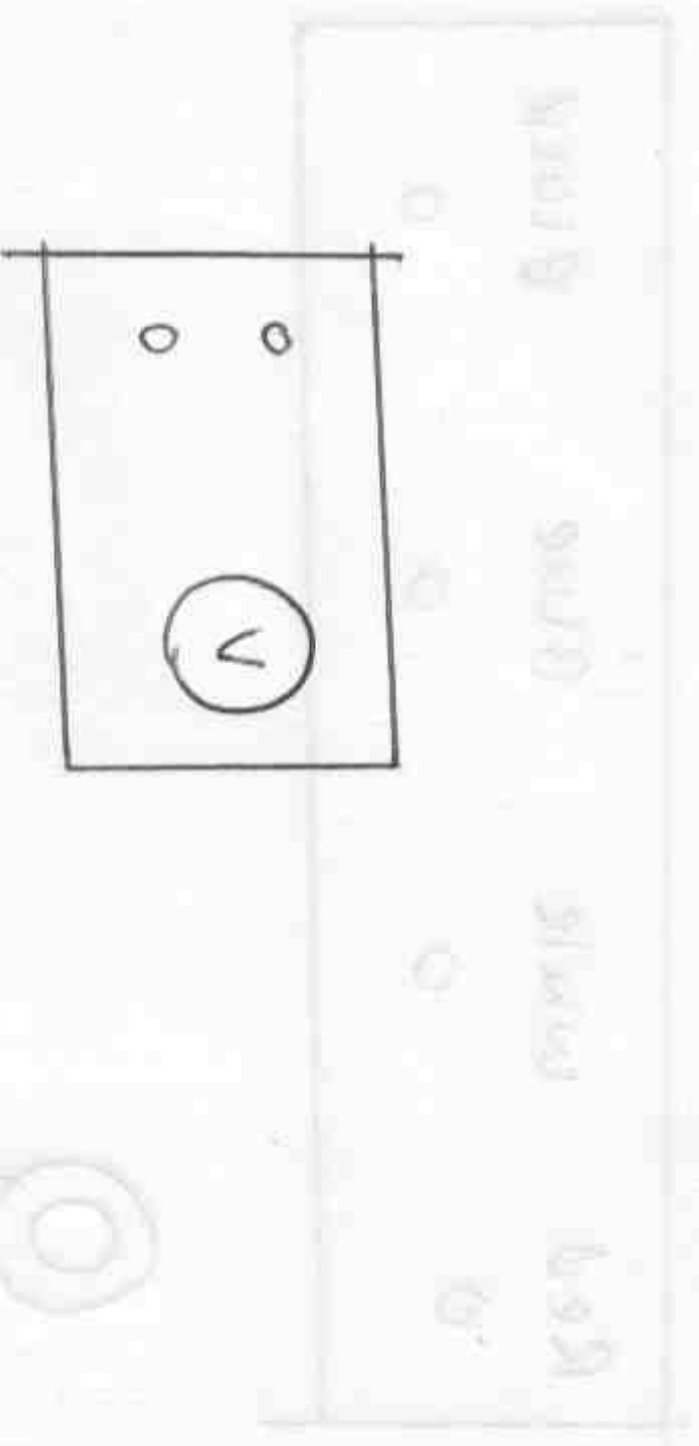

resistor and diode ⑧ / ⑨