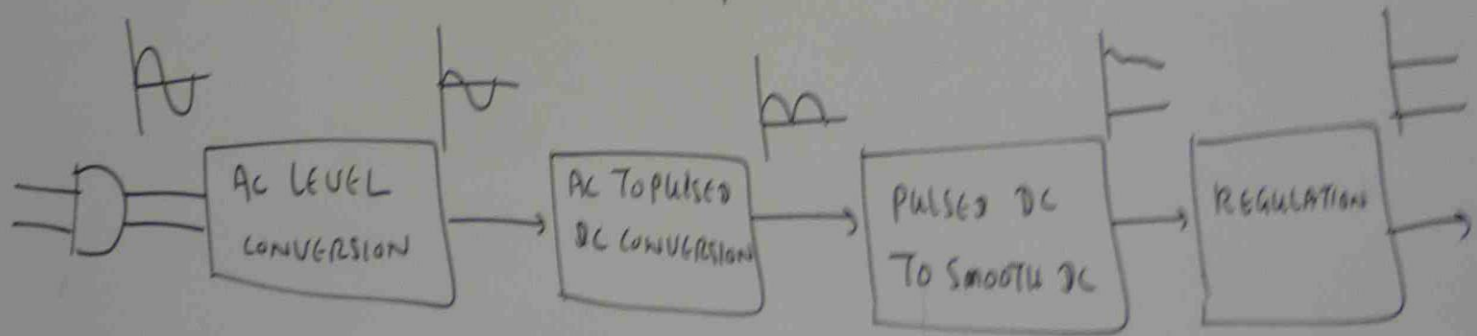




POWER SUPPLIES

MOST ELECTRONIC EQUIPMENTS REQUIRES SOME FORM OF DC POWER TO OPERATE. IF THIS EQUIPMENT IS TO BE OPERATED FROM A STANDARD AC OUTLET, THEN A DC POWER SUPPLY IS NEEDED. A POWER SUPPLY TAKES ELECTRICAL POWER FROM A DISTRIBUTION SYSTEM AND CONVERTS IT TO THE DESIRED FORM OF POWER.



BLOCK DIAGRAM OF A REGULATED POWER SUPPLY

SINGLE PHASE HALF WAVE RECTIFIER

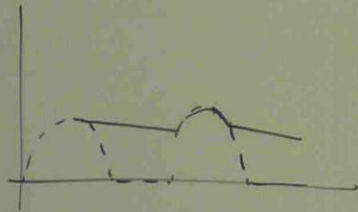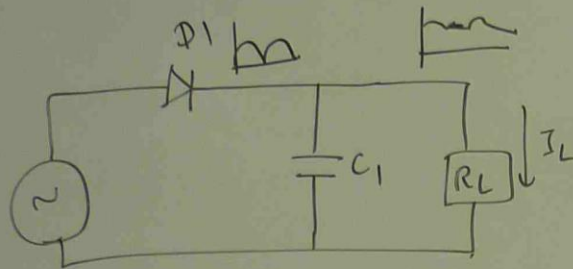


C_1 - FILTER CAPACITOR


HALF WAVE RECTIFIER WITH FILTER CAPACITOR.

FULL WAVE RECTIFIER

THE BRIDGE RECTIFIER

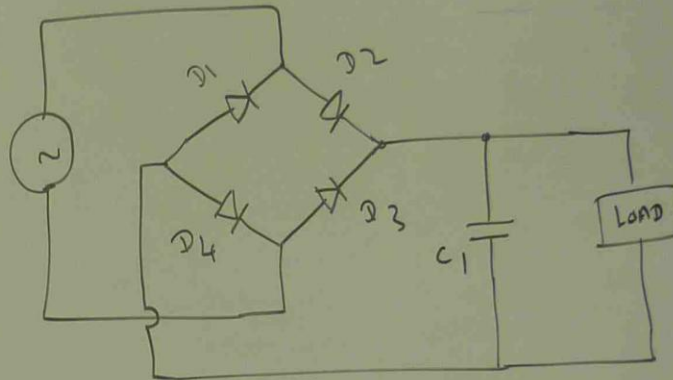

THE CENTRE - TAPPED FULL WAVE RECTIFIER

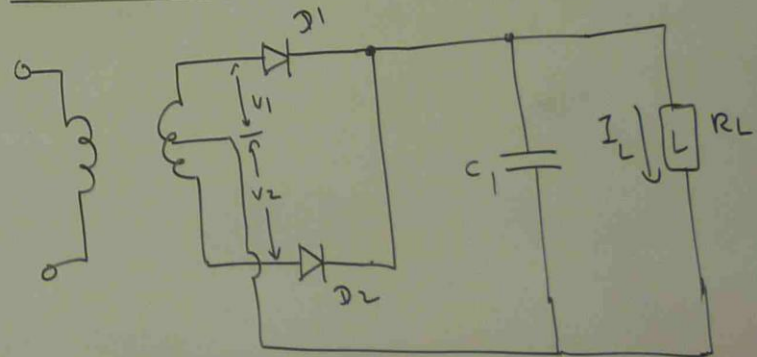

CENTRE TAPPED TRANSFORMER, FULL WAVE RECTIFIER

CALCULATING THE SIZE OF FILTER CAPACITOR

$$V_{dc} = V_r f_r R_L C$$


V_{dc} - DC OUTPUT VOLTAGE

V_r - P-P RIPPLE VOLTAGE

f_r - RIPPLE FREQUENCY

C - CAPACITANCE

R_L - LOAD SEEN BY CAPACITOR.

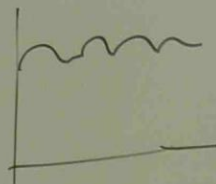

$$V_r = 40 \times \frac{2}{100} = 0.8V$$

$$V_{dc} = V_r f_r R_L C$$

$$40 = 0.8 \times 100 \times 160 \times C$$

$$C = \frac{40}{0.8 \times 100 \times 160}$$

$$C = 312.5 \mu F$$

pb CALCULATE THE LOAD RESISTANCE AND CAPACITOR SIZE OF A FULL WAVE RECTIFIER THAT SUPPLIES 40V DC WITH 2% RIPPLE VOLTAGE AT 250mA TO A RESISTIVE LOAD. ASSUME THE RECTIFIER CIRCUIT IS SUPPLIED WITH 50Hz AC. (RIPPLE FREQ = 100Hz)

$$R_L = \frac{V_L}{I} = \frac{40}{250 \times 10^{-3}} = 160 \Omega$$


POWER SUPPLIES - PART (2)

VOLTAGE REGULATION

THE PURPOSE OF VOLTAGE REGULATION IS TO MAINTAIN A CONSTANT VOLTAGE ACROSS A LOAD REGARDLESS OF ANY CHANGE IN LOAD CONDITION (OR) SUPPLY VOLTAGE.

THE MAIN TYPES OF REGULATION ARE SERIES, SHUNT AND SWITCHING.


ZENER DIODE - VOLTAGE REFERENCE DIODE.

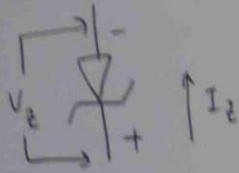

THE OUTPUT VOLTAGE ACROSS THE LOAD R_L EQUALS


THE ZENER VOLTAGE V_Z .

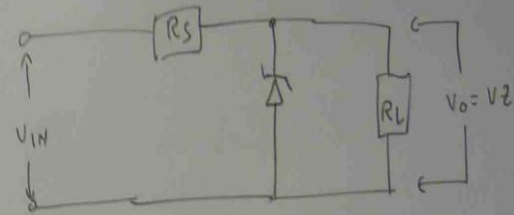THE OUTPUT VOLTAGE IS KEPT CONSTANT DESPITE CHANGES IN V_{IN} AND I_L .



BASIC SERIES ZENER REGULATOR


SERIES TRANSISTOR REGULATOR

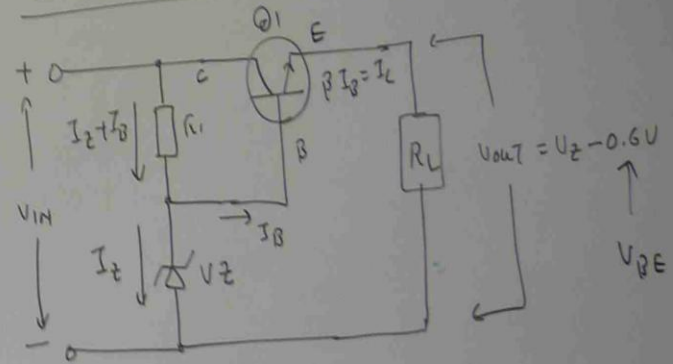

$V_{BE} = 0.6V$ SILICON TRANSISTOR

$V_{BE} = 0.2V$ - GERMANIUM TRANSISTOR

REGULATORS WITH FEEDBACK

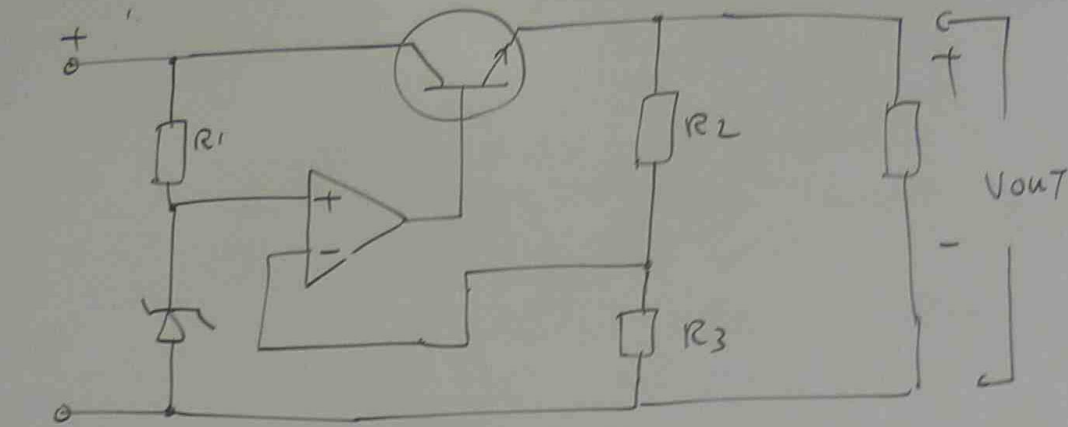

SERIES REGULATOR WITH FEEDBACK


$$V_{out} = \left(\frac{R_2}{R_3} + 1 \right) \times V_{REF}$$

$$\text{WHERE } V_{REF} = V_Z$$

$$P_d = \text{DISSIPATED POWER} = (V_{in} - V_{out}) \times I_L$$


pb FOR THE CIRCUIT IN FIGURE, CALCULATE

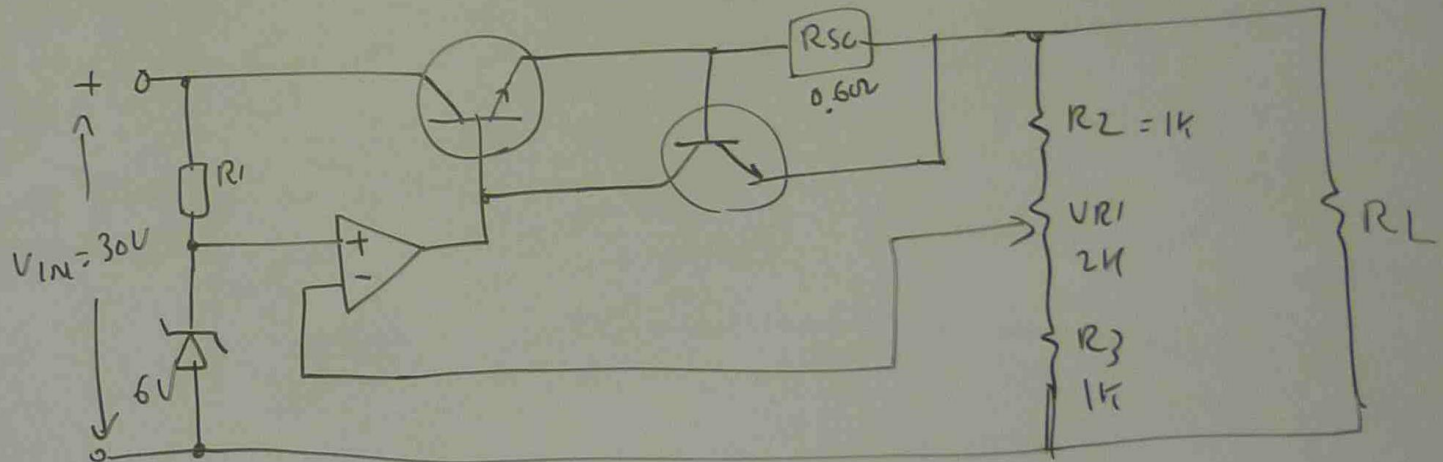- THE MAXIMUM AND MINIMUM OUTPUT VOLTAGES
- THE CURRENT THAT WILL FLOW IF OUTPUT IS SHORT CIRCUITED
- THE POWER DISSIPATED BY Q_1 IF THE OUTPUT IS SHORT CIRCUITED



pb FOR THE CIRCUIT IN FIGURE, CALCULATE

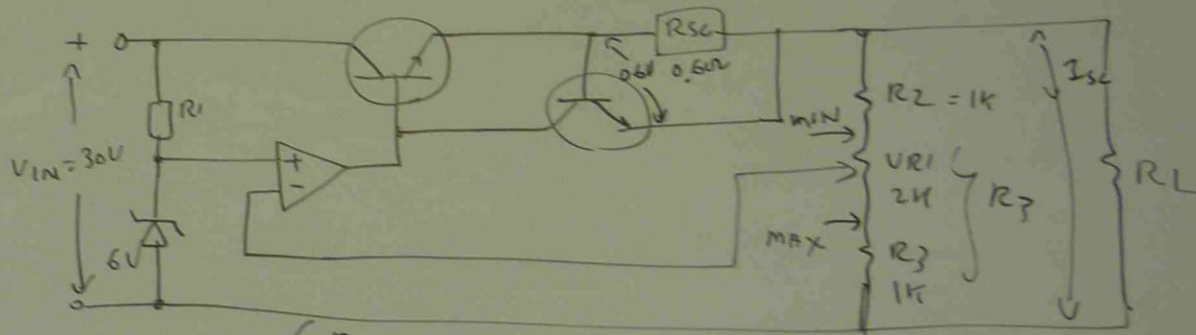- THE MAXIMUM AND MINIMUM OUTPUT VOLTAGES
- THE CURRENT THAT WILL FLOW IF OUTPUT IS SHORT CIRCUITED
- THE POWER DISSIPATED BY Q_1 IF THE OUTPUT IS SHORT CIRCUITED



$$(a) V_{out} = \left(\frac{R_2}{R_3} + 1 \right) V_{Ref}$$

$$V_{out} = \left(\frac{1}{3} + 1 \right) \times 6 = (1.33) \times 6 = 8V$$

$$V_{out} = \left(\frac{3}{1} + 1 \right) \times 6 = 4 \times 6 = 24V$$

$$(b) I_{sc} = \frac{0.6}{R_{sc}} = \frac{0.6}{0.6\Omega} = 1A$$

$$(c) P_d = (V_{IN} - V_{out}) \times I_L$$

$$= (30 - 0) \times 1 = 30W$$

TRANSISTOR CONNECTIONS

The TO-92 dilemma

The TO-92 package is very common, but has at least six variations on the lead connections and has numerous lead forms. Transistor data books vary in their method of referring to the particular variation of the package, and some data books even leave out the variation altogether, and just state that the transistor is in a TO-92 package. A little like giving your address as 'Australia'.

The package is used for transistors, FETs, SCRs and other devices including regulator ICs, PUTs, UJTs etc. Each





pinout variation is usually shown with the terminals marked for both transistors and FETs, although not all variations have pinouts for both devices.

One variation is known as the standard, but it is not the most common variation. Some transistors come in two variations - for example, the BC182B has a totally different lead configuration to the BC182L, even though both are in a TO-92 package. We have even found variations referred to in data manuals that don't exist, that is, no drawing

showing the lead connections could be found in the manual.

Obviously there is a slight(?) possibility of confusion - perhaps our summary below will help. Each variation that we could find is shown in two ways; as viewed from the bottom and as seen when mounted on a PCB. Next to each drawing is a listing of some transistor types that apply to that variation. We have not included FET example types, although the FET pinouts are included where applicable.

Voltage regulators

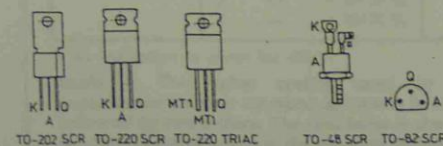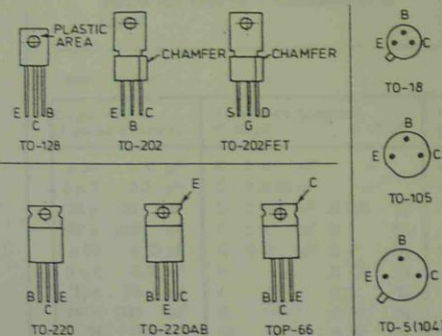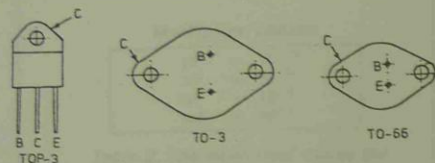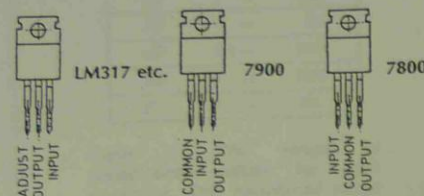

TO-92



Variation 1

Also called variation 71, 96 etc.
Includes the following transistor types:
MPS6542, '6543, '6546, '6547.
MPSH10, '11, '19, '20, '24, '30.
PE3100, BF233.



Variation 2

Also called variation 72, 92 etc.
Known as the 'standard'.
2N3641, '3642, '3643, '3903, '3904.
2N3905, '3906, '4400, '4403, '5401.
BC170, '171, '172, '173, '174, '317.



Variation 3

Also called variation 74, 94 etc.
TIP31, '32, '110, '117.
BC182L, '183L, '213L, '214L, '257.
BC258, '259, '635, '636, '639, '640.
2N3702, '2926.



Variation 4

Also called variation 77, 97 etc.
The most common type.
BC237B, '307B, '327, '328, '337.
BC338, '415, '485, '546, '547.
BC548, '549, '556, '557, '558.
BC559, '560, BF936, '324.



Variation 5


Also called variation 76.
2SC710. Mainly used for FETs.



Variation 6

Also called variation 98.
BF194, '195, '196, '197, '198, '199.
BF237, '238, '240, '241, '254, '255.
BF450, '451.

TO-72

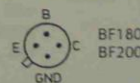

BF180
BF200



BF115
BF167
BF173
BF184
BF185

CAPACITOR CODES

This reference sheet is intended to help readers who have problems converting between multipliers for capacitors. It includes the standard we use in the magazine, (conforms to metric standard, by the way), and shows when to use the nanofarad or the millifarad instead of the venerable microfarad.

Although a very difficult area to summarise, due to the number of standards being used, the data sheet also includes information on how to interpret manufacturer's capacitor value codes. The standard used by Philips is reproduced below.

Multiplier ranges

pF	1 →	820
nF	1 →	82
uF	0.1 →	820
mF	1 →	820
F	1 →	inf.

Table 1. The range of capacitance values for each multiplier. The nanofarad range has the least number of values.

Multiplier values

pF	=	10^{-12}
nF	=	10^{-9}
uF	=	10^{-6}
mF	=	10^{-3}

Table 2. The numerical values for each multiplier. For example, micro (u) means 1 millionth of a farad.

The multiplier

Table 1 shows the range of capacitance values that apply to each multiplier. For example, the value of 1nF is OK, but 100nF is outside the range — instead use the next multiplier and express the value as 0.1uF. Table 2 simply shows the actual value the multiplier represents. For example, the millifarad (mF) is one thousandth of a farad (F).

Table 3 is a conversion table between all the multipliers. For example, a 2.2nF capacitor could also be a 2200pF capacitor or a 0.0022uF capacitor.

Value codes

Capacitor value coding varies, and we include that used by Philips as a guide. Note the use of the multiplier in place of the decimal point. For example, 8.2pF would be written as 8p2.

Another way of expressing a value of a capacitor is to print the first two digits followed by a multiplier digit. This way, 47nF, would be expressed as 473, perhaps followed with a letter representing tolerance. To convert the number to a value, write the first two digits, followed by the number of zeros expressed by the third digit. The value obtained is in pF, which can then be converted to nF or uF using Table 3.

10^{-12} 10^{-9}		Conversions 10^{-3}			
pF	nF	10^{-6} uF	mF	F	
100	0.1	0.0001	—	—	
820	0.82	0.00082	—	—	
1,000	1	0.001	—	—	
8,200	8.2	0.0082	—	—	
10,000	10	0.01	—	—	
82,000	82	0.082	—	—	
100,000	100	0.1	0.0001	—	
—	820	0.82	0.00082	—	
—	1,000	1	0.001	—	
—	8,200	8.2	0.0082	—	
—	10,000	10	0.01	—	
—	82,000	82	0.082	—	
—	100,000	100	0.1	0.0001	
—	—	820	0.82	0.00082	
—	—	1,000	1	0.001	
—	—	8,200	8.2	0.0082	
—	—	10,000	10	0.01	
—	—	82,000	82	0.082	
—	—	100,000	100	0.1	
—	—	—	820	0.82	
—	—	—	1000	1	

Table 3. Conversion reference table. This table should allow conversion between multipliers for most given capacitor values. Numerical values for each decade are from 1 to 8.2.

DC Power Dissipation: 400mW at 50°C Ambient
(Derate 3.2mW/°C above 50°C)


DC Power Dissipation: 1Watt @ 50°C Ambient (Derate 6.67mW/°C above 50°C)

This range will dissipate up to 3W @ 75°C with 10mm lead length as heatsink.


Three Terminal Regulators

	Polarity	Case	V _{OUT} min typ max	I _{OUT} (nom)	Dropout Voltage
05	positive	TO-92	4.8 5 5.2	100mA	1.7
62	positive	TO-92	5.95 6.2 6.45	100mA	1.7
09	positive	TO-92	8.64 9 9.36	100mA	1.7
12	positive	TO-92	11.5 12 12.5	100mA	1.7
15	positive	TO-92	14.4 15 15.6	100mA	1.7
5	positive	TO-220	4.8 5 5.2	1A	2
9	positive	TO-220	5.75 6.0 6.25	1A	2
3	positive	TO-220	8.64 9 9.36	1A	2
2	positive	TO-220	11.5 12 12.5	1A	2
5	positive	TO-220	14.4 15 15.6	1A	2
4	positive	TO-220	4.8 5 5.2	1A	1.1
2	negative	TO-220	-11.5 -12 -12.5	1A	1.1
3	negative	TO-220	-14.4 -15 -15.6	1A	1.1
17K	positive	TO-3	adj. 1.2 to 37	1.5Amin	
17T	positive	TO-220	adj. 1.2 to 37	1.5Amin	
50K	positive	TO-3	adj. 1.2 to 33	3A	
50T	positive	TO-220	adj. 1.2 to 33	3A	
05	positive	TO-3	4.85 5 5.25	5A	2.5

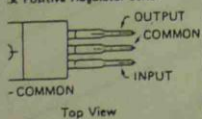
Connections TO-220 Package
xx Positive Regulator Series



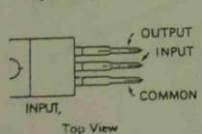
Connections TO-220 Package
xx Negative Regulator Series



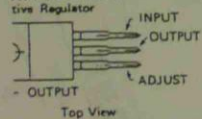Connections TO-220 Package
1771 and LM350T
Tive Regulator



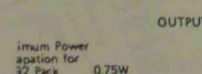Connection TO-92 Package
xx Positive Regulator Series



336 Reference Diodes

	LM336-2.5	LM336-5.0
Fwd Current (mA)	10	10
Rated Ref Voltage	2.44-2.54	4.9-5.1

Voltage Regulators

These voltage regulators almost make power supply building unnecessary since they require only a filtered DC voltage input, they are essentially indestructible (if used within manufacturer's specs.) because of internal current limiting and thermal shutdown should a short occur. They are ideally suited to local, on board regulation simplifying power supply distribution systems. Excellent for TTL and project supplies. With the advent of microprocessors and microcomputers, these regulators have been used extensively in power supplies for such systems. This type of use typifies their versatility and reliability. Another area of supply regulation use is with analogue operational amplifiers. These circuits usually call for both + and - complementary rail voltages. These three terminal devices ideally suit such requirements.

The addition of protection diodes, as shown in the 317/350 application circuit, is recommended if there is any possibility of the regulator input or output being shorted to ground. These may also be necessary if significant (>1uF) capacitance is connected between ground and either the common or output terminals of the regulator.

Increase the Output Voltage of a 3 Terminal Voltage Regulator


Regulators like the 7805 and the 7905 can give higher output if two additional resistors are configured into the circuit as shown below.

$$R1 = V_R / 0.02 \quad R2 = V_B / 0.025$$

Where V_R is the normal regulated voltage from the IC and V_B is the amount by which the regulator has to be boosted above V_R . Some examples are given below:

V _{OUT}	Regulator	R1	R2
6	5V	220	39
9	5V	220	150
13.8	12V	560	68
18	15V	680	120

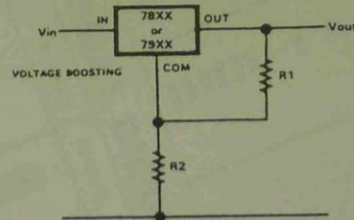To make a variable regulator, use a potentiometer as R2.




Increasing the Output Current of the Regulator

By adding a PNP power transistor to a positive regulator, the output current can be increased above the normal rating of the regulator itself. The circuit shown below can be expected to deliver in excess of 4A with the pass transistor mounted on a heatsink. The same conditions can also be implemented with a negative regulator, the difference being the polarities of components, the pass transistor in this case would be an NPN type such as a 2N3055.


Typical Power Supply Using a 3 Terminal Regulator

Output: 5V @ 1A

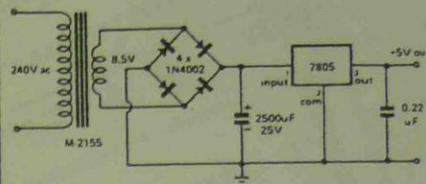The same basic circuit can be used with other regulators of different voltages, only the input ac voltage has to be changed to accommodate the requirement of that regulator. eg. If an output of 12V was the requirement, a 7812 IC could be used with an ac input voltage of 15V.



LM317 or LM350 Series

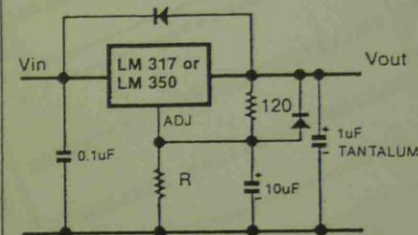

1. Choose Resistor R as follows:
 $R = (96 \times V_{out}) - 120$
Where R is in ohms and V_{out} is in volts
2. V_{in} should be at least 2.5 volts greater than V_{out} .
3. Capacitor voltage ratings must be chosen appropriately.
4. The protection diodes shown will be necessary if the input or output of the regulator is shorted to ground. 1 amp types should be adequate.

LM334 Adjustable Current Source

Operating Voltage	1-30
Max Power Dissipation	200mW
Voltage Sensitivity	0.1%/V
Temperature Sensitivity	+0.33%/°C

$$I = 68mV / R_{set}$$

FETS

FETS	Case	BVGSS		VGS(OFF)		IDSS(mA)		VGS	Yfs(umhos)		Ptot	Use/Comments
		V @	IG(uA)	Min	Max @ VDS	ID(nA)	Max @ VDS		Min	Max @ VDS	mW	
BF245B	TO-92 Var 1	60	1	0.5	8	15	10	6	15	15	0	N/CH Junction Audio to H.F.
BF981	SOT-103	±6	±10	2.5	8	10	20uA	4	25	10	0	N/CH Dual Gate MOS. VHF Amp
BFW10	TO-72(25)	30	1					8	20	15	0	N/CH Junction Audio to H.F.
BFW11	TO-72(25)	30	1					4	10	15	0	N/CH Junction Audio to H.F.
BFW61	TO-72(25)	25	1					2	20	15	0	N/CH Junction Audio to H.F.
MEM831	W-25	±6	±10		4	15	200uA	5	30	15	0	N/CH Dual Gate MOS. VHF Amp
MFE131	TO-72(2)	±6	±10		4	15	200uA	3	30	15	0	N/CH Junction — VHF
MPF102	TO-92(72)	25	1	0.5	8	15	2	2	20	15	0	N/CH Junction — Audio Sw.
MPF103	TO-92(72)	25	1		6	15	1	1	9	15	0	N/CH Junction — Audio Sw.
MPF104	TO-92(72)	25	1		7	15	1	4	16	15	0	N/CH Junction — Audio Sw.
MPF105	TO-92(72)	25	1		8	15	10	4	10	15	0	N/CH Junction — RF
MPF106	TO-92(72)	25	1	0.5	4	15	10	5	30	15	0	N/CH Dual Gate MOS. VHF Amp
MPF121	206(B)	±6	±10		4	15	200uA	3	30	15	0	N/CH Dual Gate MOS. VHF Amp
MPF131	262	±6	±10		4	15	200uA	12	30	15	0	P/CH Junction — Audio Sw.
2N4342	TO-92(72)	25	10	0.5	6	15	100	1	5	15	0	N/CH VHF/UHF Mixer
2N4360	TO-92(72)	30	1	1.5	6	10	10	1	5	15	0	N/CH Junction — Audio Sw.
2N5245	TO-92(72)	30	1	0.5	6	15	10	2	6	15	0	N/CH Junction — Audio Sw.
2N5457	TO-92(72)	25	1	1	7	15	10	1	5	15	0	N/CH Junction — VHF
2N5458	TO-92(72)	25	1	2	8	15	10	1	5	15	0	N/CH Junction — VHF
2N5459	TO-92(72)	25	1	0.3	3	15	10	4	10	15	0	N/CH Junction — VHF
2N5464	TO-92(72)	25	1	0.5	4	15	10	8	20	15	0	N/CH Dual Gate MOS. VHF Amp
2N5485	TO-92(72)	25	1	2	6	15	10	25	15	0	0	N/CH UHF GaAs Dual Gate
2N5486	TO-72(2)	±6	±10		4	15	100uA	20	45	5	0	N/CH Dual Gate MOS. VHF Amp
3SK40	2-6F1A	±5	±10	-2.5	4	5	100uA	35	15	0	0	N/CH Dual Gate MOS. VHF Amp
3SK121	TO-72(2)	±6	±10	-2	8	15	200uA					
40673	TO-72(2)	±6	±10		8	15	200uA					

POWER FETS

TYPE	CASE	Ptot	Vds(max)	Id(max)	Vgs(off)	Gfs	Ciss	Rds	Comment
		(W)	(V)	(A)	min	max	(pF)	(ohms)	
BUZ71	TO220	40	50	14	-	-	-	0.1	Nch Power MOSFET
VN10K	TO92	1	60	1	.3	1.5	100K	48	Nch DMOS FET
VN46AF	TO202F	12.5	40	2	.8	2	150K	50	Nch VMOS FET
VN66AF	TO202F	12.5	60	2	.8	2	-	-	Nch VMOS FET
VN86AF	TO202F	12.5	80	2	.8	2	-	-	Nch VMOS FET
VN88AF	TO202F	12.5	80	2	.8	2	-	-	Nch VMOS FET
2SJ48	TO3	100	120	7	-.15	1.45	1M	900	Pch Power MOSFET
2SJ49	TO3	100	140	7	-.15	1.45	1M	900	Pch Power MOSFET
2SJ50	TO3	100	160	7	-.15	1.45	1M	900	Pch Power MOSFET
2SK133	TO3	100	120	7	-.15	1.45	1M	600	Nch Power MOSFET
2SK134	TO3	100	140	7	-.15	1.45	1M	600	Nch Power MOSFET
2SK135	TO3	100	160	7	-.15	1.45	1M	600	Nch Power MOSFET

SMALL SIGNAL DIODES


TYPE	CASE	VR	IF (mA)	Cd (pF)	VF @	IF (mA)	IR (uA)	@ VR	Trr (nS)	Use/Comparable Types
Germanium										
AA119	DO-7	30	100	1.2	2.2	10	150	30	70	AM/FM Detection Point Contact
OA47	DO-7	30	110	3.5	0.45	10	450	20		Gold Bonded G.P. Switching
OA90	DO-7	20	45		1.5	10	180	75		G.P. Point Contact OA70, OA80
OA91	DO-7	80	50		1.3	5	200	10		G.P. Point Contact OA71, 79, 81
DSOA91	DO-7	50	30	1	1.5	10	110	0.75		G.P. OA91, 1N60
DSOA91	DO-7	90	50							G.P. Point Contact
Silicon										
BA100	DO-7	60	90	25	0.96	10	10	60		G.P. — Alloyed
BA102	DO-7	80	100	20-45	Cd Ratio 1.4 @	4/10 V/VV				Variable Capacitance
BA114	DO-7	20	100	<2	0.7	1	0.1	15	4	Blas Stabilizer
BA234/4	DO-35	20	100	2	0.75	5	0.1	75		High Speed Silicon Sw.
BAW62	SOD-27	75	200	20-25 @ 4V	Cd Ratio >> 1.3		0.05	28		Varicap — replaces BA102
BB119	DO-35	15	120	12 @ 3V	Cd Ratio 5.2		0.05	10		UHF Sw.
BB122	DO-35	30	120	500-620 @ 0.5V	Cd Ratio > 22.5		0.1	150		AM Dual Varicap
BB212	TO-92	12	150	25	0.96	10	0.1	50		Small Signal — Alloyed
OA200	DO-7	50	160	25	0.96	10	0.1	150		Small Signal — Alloyed
OA202	DO-7	150	160	25	0.96	10	0.1	150		Small Signal Sw. 1N4148
1N914A	DO-35	75	200	4	1	100	0.025	20	4	G.P. Silicon Sw. 1N4148
1N4148	DO-35	75	200	4	1	100	0.025	20	4	Schottky (Hot Carrier) UHF
1N4448	DO-35	75	300	4	1	100	0.2	50	0.1	Detector, Mixer Switch
5082-2800	DO-7	70	15	2	0.41	1				

RECTIFIERS

TYPE	MAT	VR	IF(A)	VF	@	IF(A)	IR(uA)	@ VR	USE
BYX21/200/R	S	75	25	1.2		25	1.1mA	75	Automobile H. Duty Press fit.
BYX68/300	S	300	10	1.4		10	200	300	Power Rectifier Stud Mount
DSS404	S	200	3	1.1		3	5	200	G.P. Rectifier
EM4005	S	50	1	1.1		1	5	50	G.P. Rectifier
EM401	S	100	1	1.1		1	5	400	G.P. Rectifier
EM404	S	400	1	1.1		1	5	1000	G.P. Rectifier
EM410	S	1000	1	1.1		1	5	1000	G.P. Stud Mount
MR110	S	100	10						G.P. Stud Mount
MR410	S	400	10						G.P. Rectifier
MRS108	S	1000	3	1.1		3	5	1000	Heavy Duty Automobile Press fit.
IN3452/R	S	100	25	1.7		18	1mA	200	Heavy Duty Automobile Press fit.
IN3485/R	S	200	25	1.7		18	1mA	50	G.P. Rectifier
IN4001	S	50	1	1.1		1	5	100	G.P. Rectifier
IN4002	S	100	1	1.1		1	5	400	G.P. Rectifier
IN4004	S	400	1	1.1		1	5	1000	G.P. Rectifier
IN4007	S	1000	1	1.1		1	0.2	1000	G.P. Rectifier
BY229-400	S	400	7	1.85		20	5	400	SMPS tr=450nS
1N4936	S	400	1	1		1	0.2	200	SMPS tr=200nS
IN5059(A14B)	S	200	2.5	1.25		2.5	0.2	400	Transient Protected (Controlled Avalanche).
IN5060(A14D)	S	400	2.5	1.25		2.5	0.2	200	Transient Protected (Controlled Avalanche).
IN5061(A14M)	S	600	2.5	1.25		2.5	0.2	600	Transient Protected (Controlled Avalanche).
IN5062(A14N)	S	800	2.5	1.25		2.5	0.5	800	Transient Protected (Controlled Avalanche).
IN5404	S	400	3	1.1		3	5	1000	G.P. Rectifier
IN5408	S	1000	3	1.1		3	5	1000	G.P. Rectifier
IN5624	S	200	5	1.1		5	5	200	Transient Protected (Controlled Avalanche).

INPUT
OUTPUT

SIGNAL
SOURCE

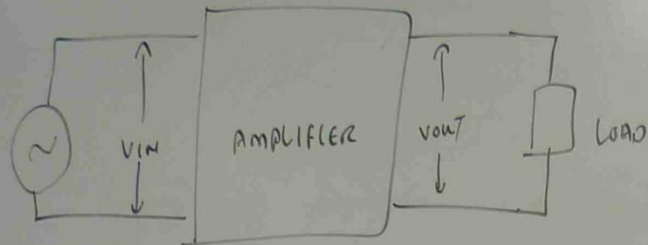

INPUT AND OUTPUT CONNECTION TO
AMPLIFIER.

GAIN

AN AMPLIFIER CAN PRODUCE A GAIN IN THE
SIGNAL VOLTAGE, CURRENT AND POWER

$$A_v = \frac{V_{out}}{V_{in}}$$

A_v = VOLTAGE GAIN

V_{in} = INPUT VOLTAGE

V_{out} = OUTPUT VOLTAGE

$$A_i = \frac{I_{out}}{I_{in}}$$

$$A_p = \frac{P_{out}}{P_{in}}$$

AV

GAIN IN d.B (DECIBEL) UNIT

POWER GAIN IN dB

$$dB = 10 \log \frac{P_{out}}{P_{in}}$$

VOLTAGE GAIN IN dB

$$dB = 20 \log \frac{V_{out}}{V_{in}}$$

CURRENT GAIN IN dB

$$dB = 20 \log \frac{I_{out}}{I_{in}}$$

ph

AN AMPLIFIER DEVELOPS 10W FOR AN INPUT POWER OF 1mW
CALCULATE THE POWER GAIN OF AMPLIFIER IN dB.

$$\begin{aligned} \text{dB} &= 10 \log \frac{P_{\text{OUT}}}{P_{\text{IN}}} = 10 \log \frac{10}{1 \times 10^{-3}} = 10 \log 10 \times 10^3 \\ &= 10 \log 10^4 = 10 \times 4 \log 10 = 40 \text{ dB} \end{aligned}$$

ph



AN AMPLIFIER FED WITH 50mV SIGNAL PRODUCES A 2V
OUT PUT. CALCULATE THE GAIN.

$$A_v = \frac{V_{\text{OUT}}}{V_{\text{IN}}} = \frac{2}{50 \times 10^{-3}} = \frac{2000}{50} = 40$$


BIPOLAR JUNCTION TRANSISTORS


BJT- BIPOlar JUNCTION TRANSISTOR

NPN PNP

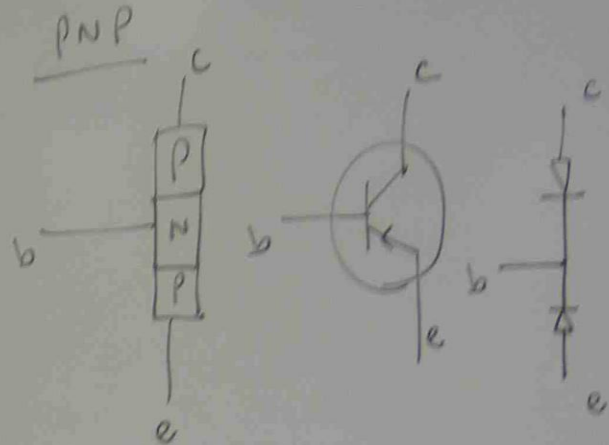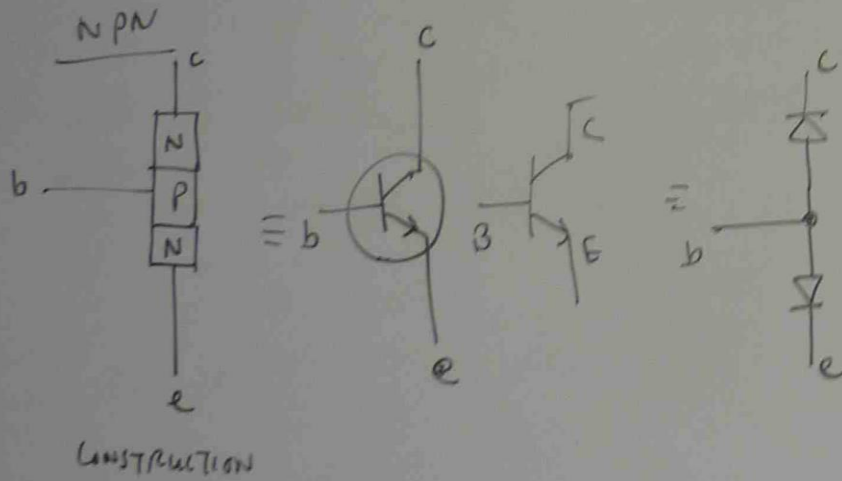

TRANSISTOR OPERATION


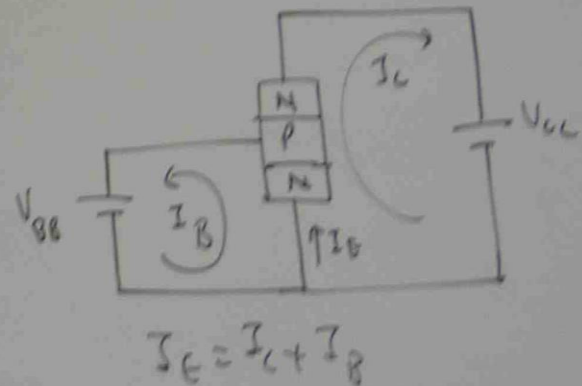


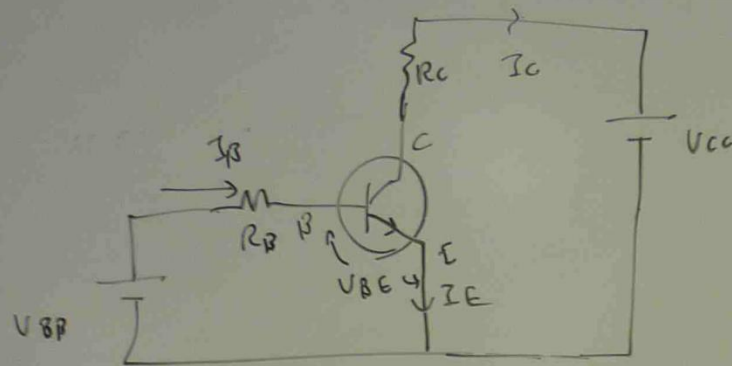


$$\alpha = \frac{I_C}{I_E}$$

$$\beta = \frac{I_C}{I_B}$$


TRANSISTOR BIASING DIAGRAM

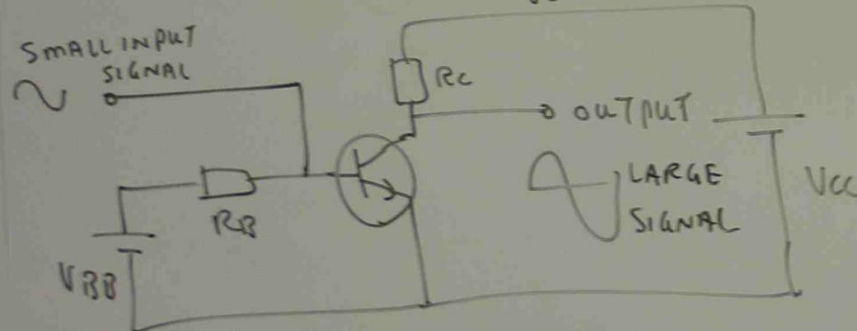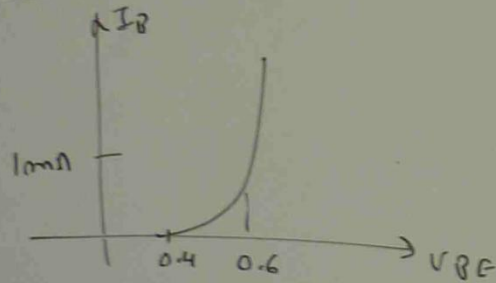

DARLINGTON PAIR

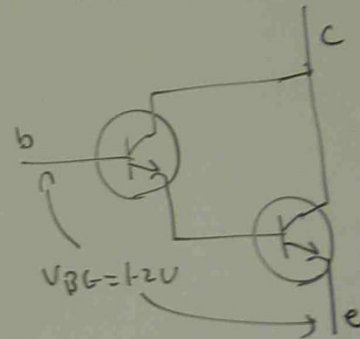

NPN DARLINGTON PAIR

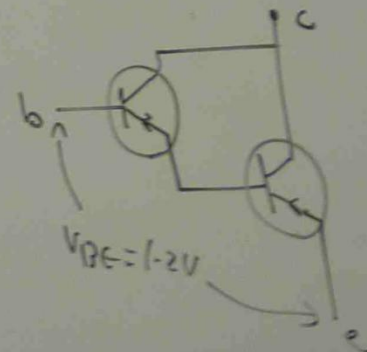

PNP DARLINGTON PAIR

CLASS A

- THIS TYPE OF AMPLIFIER PRODUCES AN OUTPUT OVER THE FULL CYCLE 360° OF INPUT CYCLE

CLASS B

PRODUCE AN OUTPUT FOR ONLY $\frac{1}{2}$ OF INPUT CYCLE 180°



CLASS A B

THIS TYPE COMPARE BETWEEN CLASS A & B

CLASS C

THE TRANSISTOR CONDUCTS FOR LESS THAN 180° OF INPUT WAVE FORM.

TRANSISTOR BIASING CIRCUITS

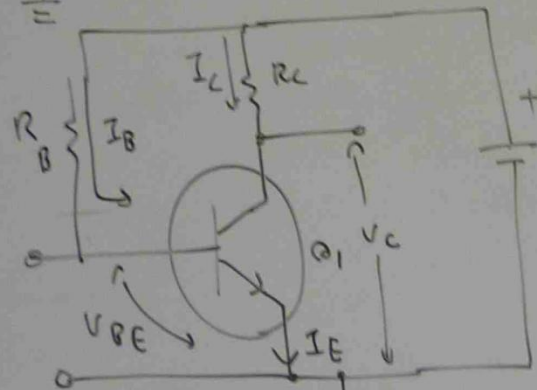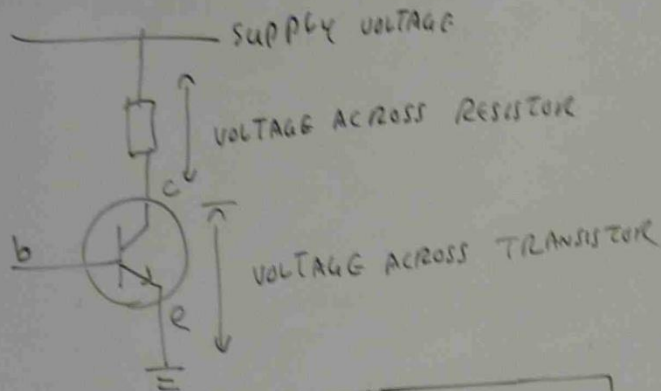

V_{CB} - VOLTAGE AT COLLECTOR
RESPECT TO BASE

V_{BE} - VOLTAGE AT BASE RESPECT TO
EMITTER

V_{RE} - VOLTAGE
ACROSS
EMITTER
RESISTOR

V_{RB} - VOLTAGE
ACROSS
BASE RESISTOR

V_{CC} - SUPPLY
VOLTAGE

V_{RC} - VOLTAGE ACROSS
COLLECTOR RESISTOR

V_{BE} - VOLTAGE ACROSS
BASE RESPECT TO
EMITTER

I_C - COLLECTOR CURRENT

I_B - BASE CURRENT

I_E - EMITTER CURRENT.

$$I_B = \frac{V_C - 0.6}{R_B}$$

$$I_C = \beta I_B$$


$$I_E = I_C$$

$$V_E = 0 \text{ V}$$

$$V_B = 0.6 \text{ V}$$

$$V_C = V_{CC} - I_C R_C$$

MULTI STAGE AMPLIFIERS

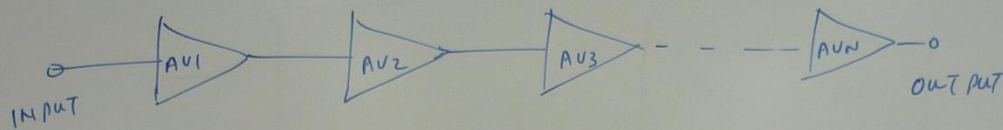

$$A_{VT} = A_{V1} \times A_{V2} \times A_{V3} \times \dots \times A_{VN}$$

$$A_V (dB) = 20 \log A_V$$

$$A_{VT} (dB) = A_{V1} (dB_1) + A_{V2} (dB_2) + A_{V3} (dB_3) + \dots + A_{VN} (dB_N)$$


CASADING — HIGHER GAIN
HIGH INPUT RESISTANCE, LOW OUTPUT RESISTANCE

COUPL

- RESIST
- DIRECT
- TRANS
- TUNE
- IN

Rc cou

C1

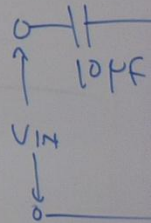


OUT


COUPLING METHODS

- RESISTANCE - CAPACITANCE (RC) COUPLING
- DIRECT COUPLING - (DC COUPLING)
- TRANSFORMER COUPLING
- TUNED TRANSFORMER COUPLING
- INDUCTANCE - CAPACITANCE COUPLING (LC COUPLING)

RC COUPLING FOR CE AMPLIFIER

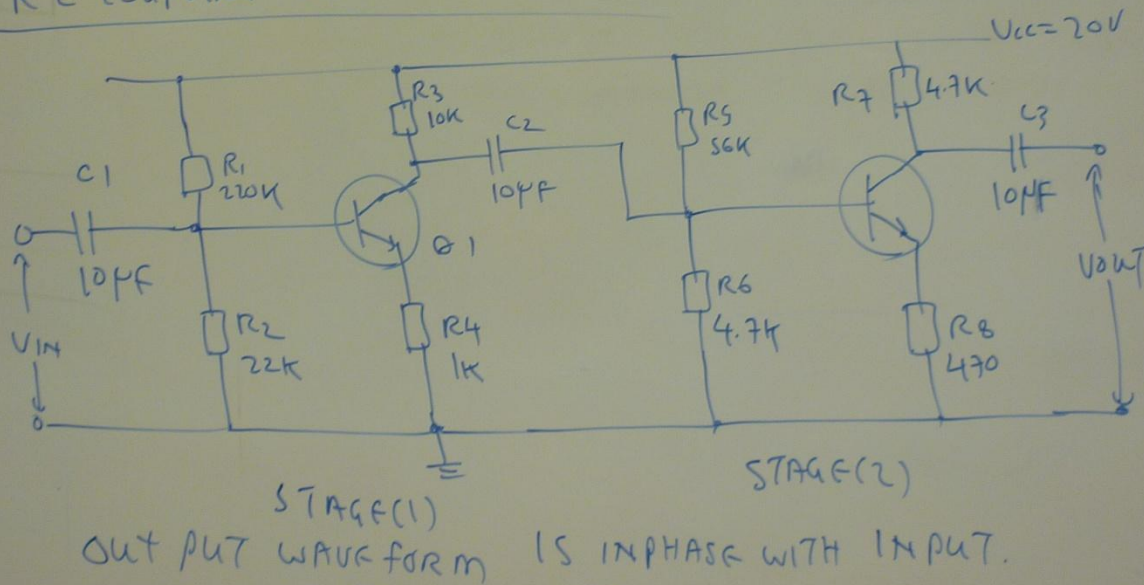

DIRECT COUPLING

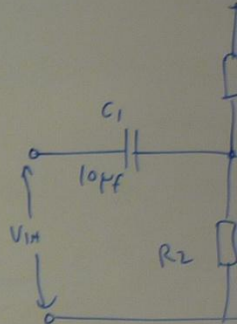


- NO BIASING
- HIGHER INPUT
- HIGHER GAIN

Pb For ABO
(a) V_{B1} (b)
(f) V_{E2}


RC) COUPLING
(NG)

NG
coupling (LC coupling)
AMPLIFIER

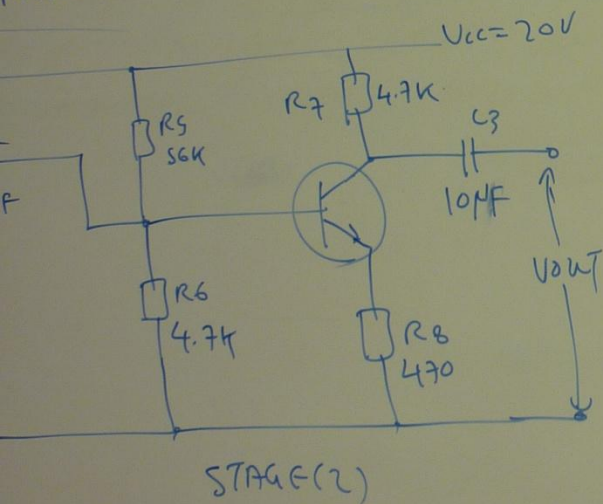

IS INPHASE WITH INPUT.

DIRECT COUPLED AMPLIFIER

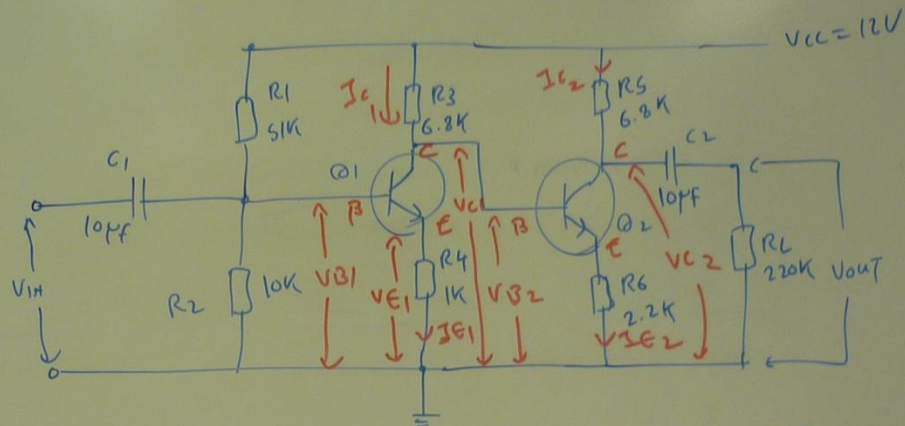

- NO BIASING CAPACITOR FOR SECOND STAGE
- HIGHER INPUT IMPEDANCE
- HIGHER GAIN.

pb) FOR ABOVE AMPLIFIER, CALCULATE

- (a) V_{B1} (b) V_{E1} (c) I_{E1} (d) I_{C1} (e) V_{C1}
(f) V_{E2} (g) I_{E2} (h) V_{C2}

$$V_{B1} = V_{CC} \times \frac{R_2}{R_1 + R_2}$$

$$= 12 \times \frac{10}{51 + 10}$$

$$= 1.96$$

$$V_{E1} = V_{B1} - V_{BE1}$$

$$= 1.96 - 0.7$$


$$V_{C1} = V_{CC} - I_{C1} R_{C1}$$

$$I_{C1} = I_{E1} = \frac{V_{E1}}{R_{E1}}$$

$$V_{C1} = V_{CC} - I_{C1} R_{C1}$$

$$= 12 - 1.96 \times \frac{6.8}{10}$$

$$= 3.84$$

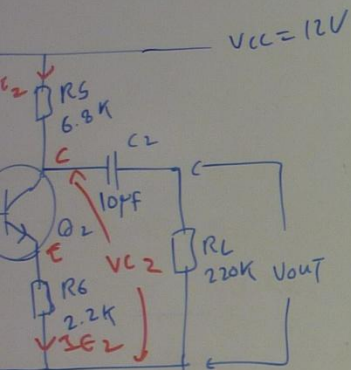

SECOND STAGE

CALCULATE

a) I_{C1} (e) V_{C1}

V_{C2}

$$V_{B1} = V_{CC} \times \frac{R_2}{R_1 + R_2}$$

$$= 12V \times \frac{10}{10 + 51}$$

$$= 1.96V$$

$$V_{E1} = V_{B1} - V_{BE}$$

$$= 1.96 - 0.6 = 1.36V$$

$$V_{C1} = V_{CC} - I_{C1} R_3$$

$$I_{C1} = I_{E1} = \frac{V_{E1}}{R_4}$$

$$= \frac{1.36}{1k}$$

$$\approx 1.36mA$$

$$V_{C1} = V_{CC} - I_{C1} R_3$$

$$= 12 - 1.36 \times 10^{-3} \times 6.8 \times 10^3$$

$$= 3.84V$$

$$V_{C1} = V_{B2}$$

$$V_{E2} = V_{B2} - V_{BE}$$

$$= 3.84 - 0.6$$

$$= 3.24V$$

$$I_{E2} = \frac{V_{E2}}{R_6}$$

$$= \frac{3.24}{2.2k}$$

$$= 1.6mA$$


$$I_{E2} = I_{C2} = 1.6mA$$

$$V_{C2} = V_{CC} - I_{C2} \times R_5$$

$$= 12 - 1.6 \times 10^{-3} \times 6.8 \times 10^3$$

$$\approx 2.4V$$

FEED BACK

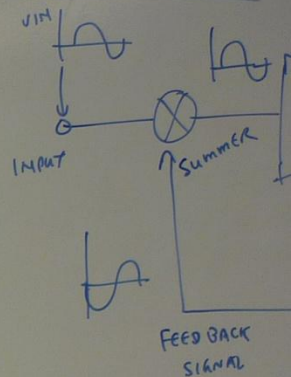

ADVANTAGES OF N

- REDUCED BUT S
- INCREASED INPUT
- REDUCED OUTPUT
- LESS NOISE IN
- LESS DISTORTION
- WIDER FREQUENCY

DC FEED BACK

- DC VOLTAGE S


$$V_{C1} = V_{B2}$$

$$\begin{aligned} V_{E2} &= V_{B2} - V_{BE} \\ &= 3.84 - 0.6 \\ &= 3.24 \text{ V} \end{aligned}$$

$$\begin{aligned} I_{E2} &= \frac{V_{E2}}{R_6} \\ &= \frac{3.24}{2.2 \text{ K}} \\ &= 1.6 \text{ mA} \end{aligned}$$

$$I_{E2} = I_{C2} = 1.6 \text{ mA}$$
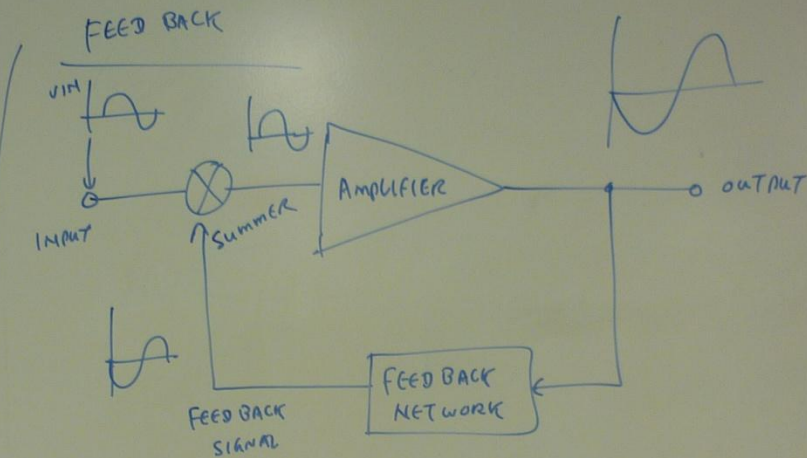
$$\begin{aligned} V_{C2} &= V_{CC} - I_{C2} \times R_5 \\ &= 12 - 1.6 \times 10^{-3} \times 6.8 \times 10^3 \\ &\approx 2.4 \text{ V} \end{aligned}$$




ADVANTAGES OF NEGATIVE FEED BACK

- REDUCED BUT STABILISED GAIN
- INCREASED INPUT RESISTANCE
- REDUCED OUTPUT RESISTANCE
- LESS NOISE IN OUTPUT SIGNAL
- LESS DISTORTION IN OUTPUT SIGNAL
- WIDER FREQUENCY RESPONSE.


DC FEED BACK

- DC VOLTAGE STABILIZING

AC FEED BACK

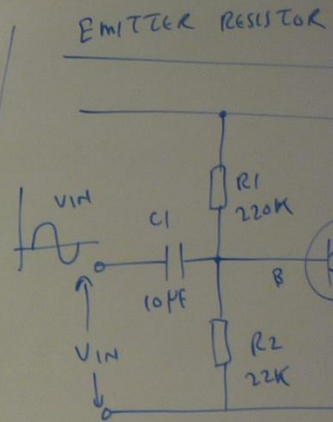


CURRENT DERIVATION

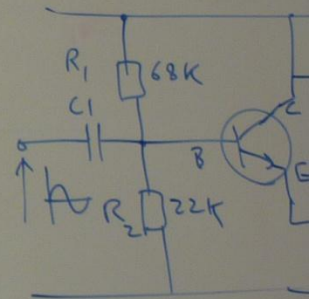

DC & AC FEEDBACK

R_5 - LOAD FOR
RESISTANCE FOR

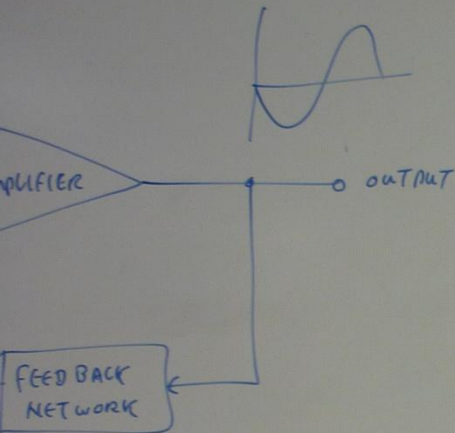


ACTIVE FEEDBACK

REDUCED GAIN
INCREASED RESISTANCE
INCREASED RESISTANCE
INPUT SIGNAL
WITH OUTPUT SIGNAL
RESPONSE.

STABILIZING

AC FEEDBACK


EMITTER RESISTOR AS FEED BACK

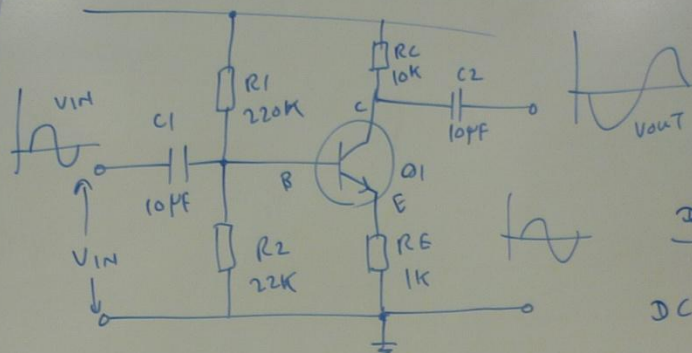

CURRENT DERIVED FEED BACK.

DC FEEDBACK


DC STABILITY CAN BE
ACHIEVED

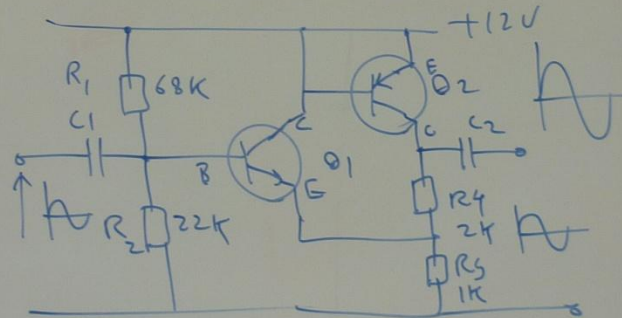

DC & AC FEEDBACK.

R_L - LOAD FOR Q_2 , EMITTER FEEDBACK
RESISTANCE FOR Q_1 .

VOLTAGE DERIVED FEED BACK

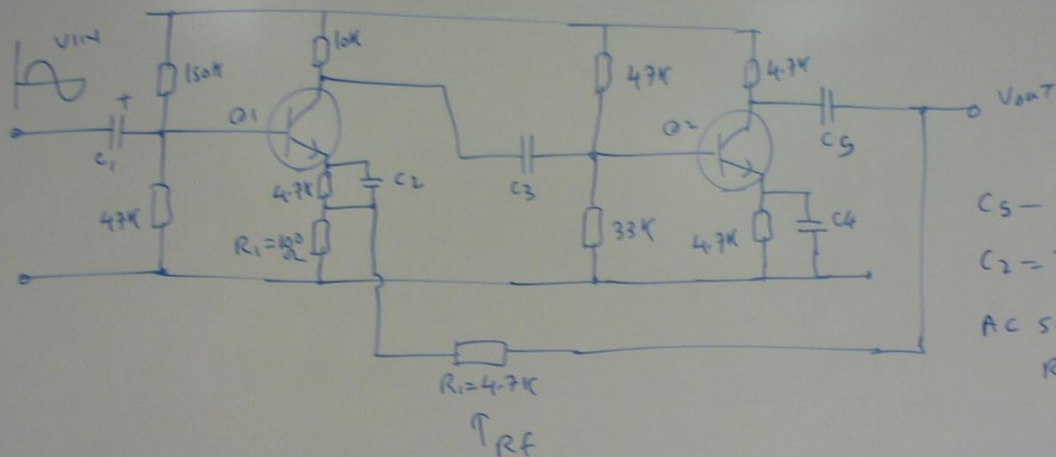


C_3 - DC ISOLATION
 C_2 - BY PASS
 AC SIGNAL ACROSS R_1

FEED BACK GAIN $A_{Vf} = \frac{R_f}{R_1} + 1$

BENEFIT OF VOLTAGE FEED BACK

- LOWER THE CIRCUIT GAIN AND STABILIZE IT
- INCREASE THE INPUT RESISTANCE
- DECREASE THE OUTPUT RESISTANCE
- PROVIDE ALL BENEFITS OF NEGATIVE FEED BACK.


AC FEED BACK

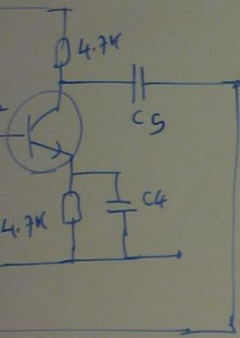

C_5 - DC ISOLATION
 C_2 - BY PASS
 AC SIGNAL ACROSS
 R_1



AC FEED BACK
 AC FEED BACK.

EXAMPLES OF AC & DC FEED BACK

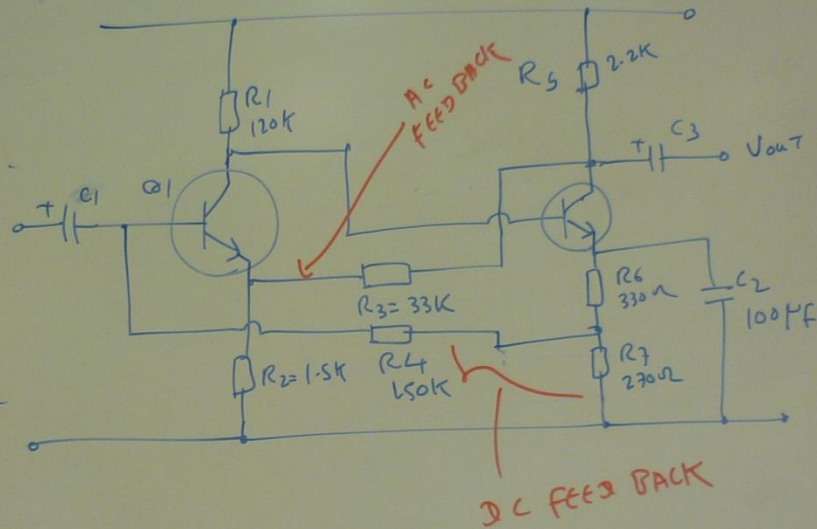

DC FEED BACK


EMITTER RESISTOR AS FEEDBACK

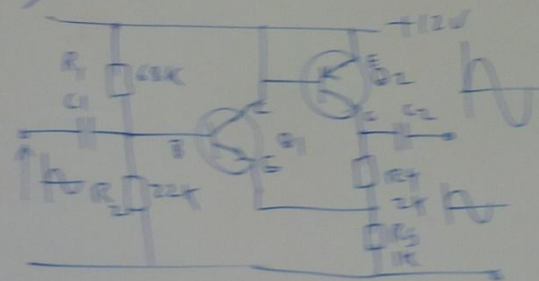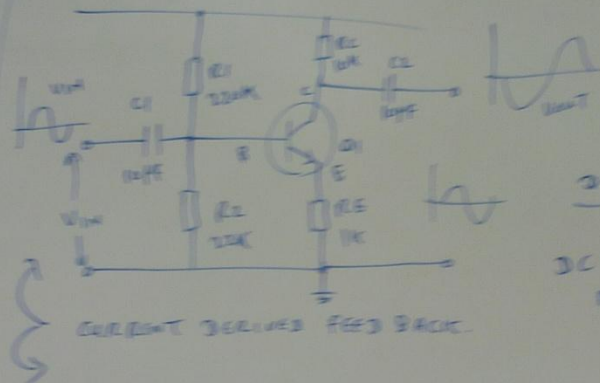

DC & AC FEEDBACK.

R_4 - loads for Q_2 , Emitter Feedback Resistance for Q_1 .

VOLTAGE DERIVED FEED BACK

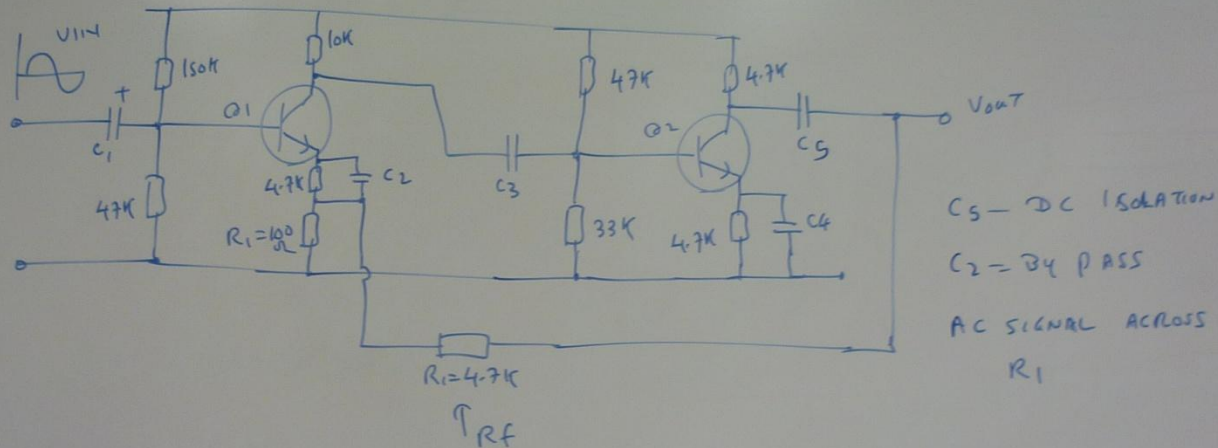


FEED BACK GAIN $A_{Vf} = \frac{R_f}{R_1} + 1$

BENEFIT OF VOLTAGE FEED BACK

- LOWER THE CIRCUIT GAIN AND STABILIZE IT
- INCREASE THE INPUT RESISTANCE
- DECREASE THE OUTPUT RESISTANCE
- PROVIDE ALL BENEFITS OF NEGATIVE FEED BACK.

AC FEED BACK

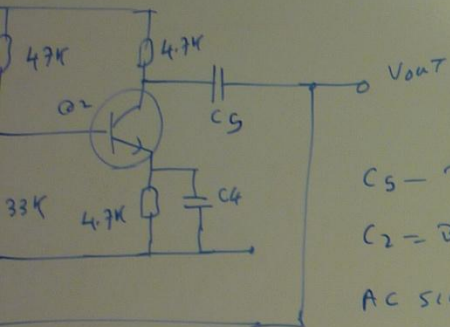


C_5 - DC ISOLATION
 C_2 - BY PASS
 AC SIGNAL ACROSS
 R_1

+1
 STABILIZE IT
 CE
 TANCE
 GATIVE FEED BACK.

AC FEED BACK


EXAMPLES OF AC & DC FEED BACK

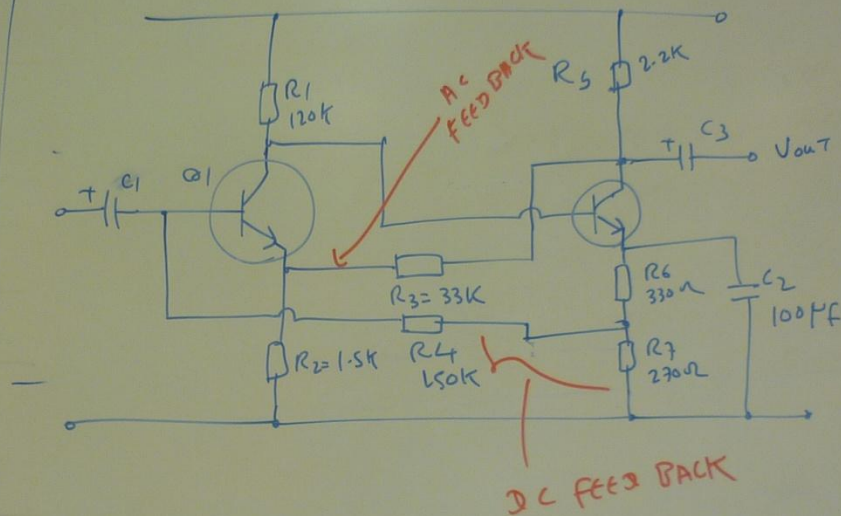

FIELD EFFECT
 BJT - TRANSISTOR
 FET - TRANSISTOR -


FET

J FET

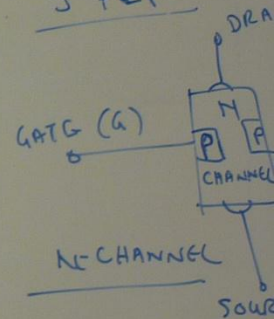

N C

AC FEED BACK

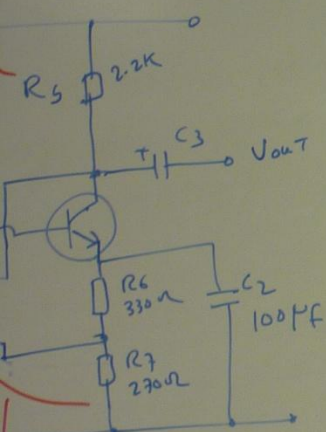


DC FEED BACK



FIELD EFFECT TRANSISTORS

BJT-TRANSISTOR - THE JUNCTION IS OPERATED WITH REVERSE BIAS



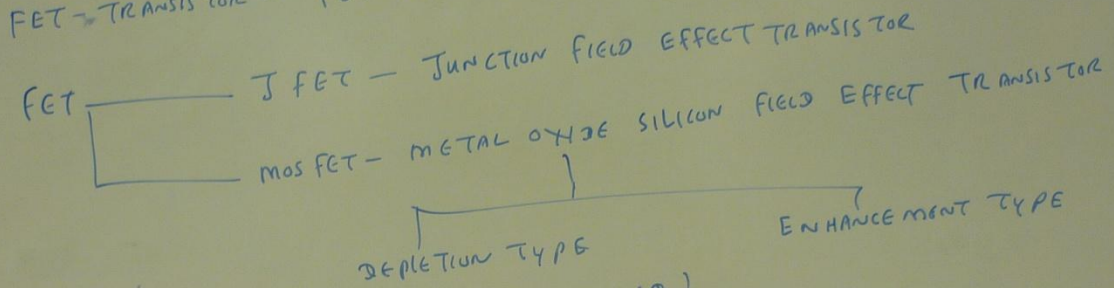
FET-TRANSISTOR - FET IS A VOLTAGE OPERATED DEVICE



J FET

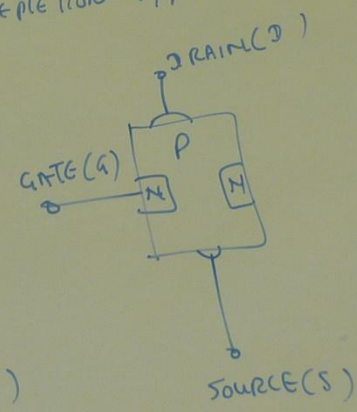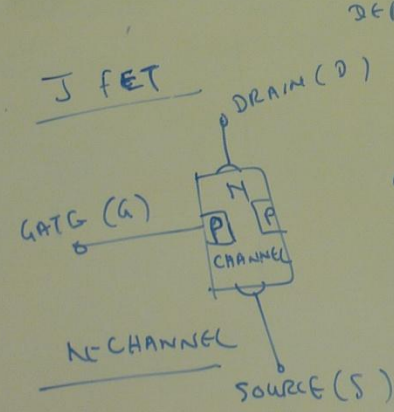

P-CHANNEL

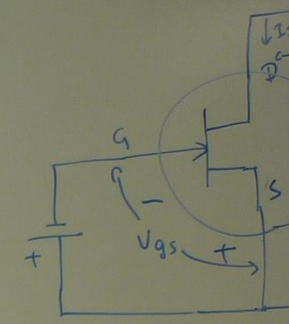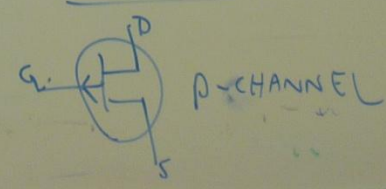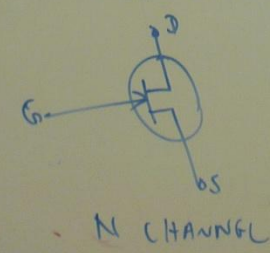

THE HIGHER THE V_{GS}
GREATER THE I_{DS}
THE HIGHER THE
THE CURRENT
TO SOURCE TO

WHEN $V_{GS} = 0$

$I_{DSS} - I_{DS}$


V_{GS} $V_{GS OFF}$

IS OPERATED WITH REVERSE BIAS
TAGED OPERATED DEVICE.



W FIELD EFFECT TRANSISTOR

OXIDE SILICON FIELD EFFECT TRANSISTOR

TYPE
ENHANCEMENT TYPE

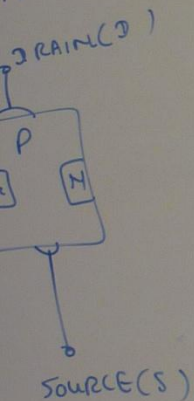


CHANNEL

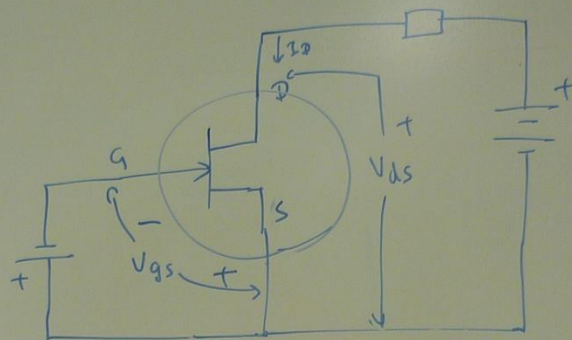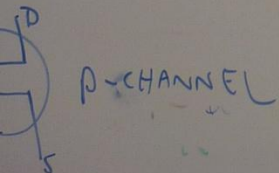


THE HIGHER THE VALUE OF V_{GS} , THE
GREATER THE DEPTH OF THE FIELD AND
THE HIGHER THE RESISTANCE OFFERED TO
THE CURRENT FLOWING FROM DRAIN
TO SOURCE TERMINAL.

WHEN V_{GS} IS ZERO $\rightarrow$ CURRENT FLOWS

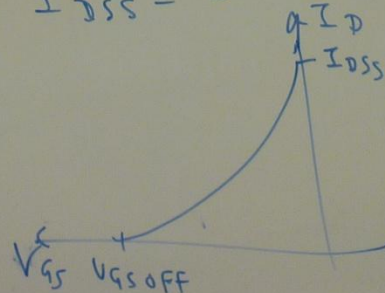I_{DSS} - DRAIN CURRENT FLOWS WHEN $V_{GS}=0$



& DC FEED BACK

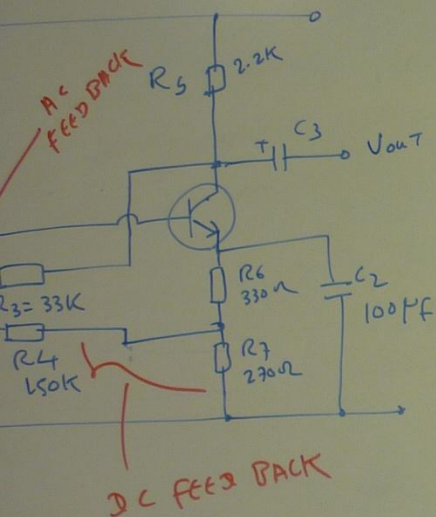

FIELD EFFECT TRANSISTORS

BJT-TRANSISTOR - THE JUNCTION IS OPERATED WITH REVERSE BIAS

FET-TRANSISTOR - FET IS A VOLTAGE OPERATED DEVICE


FET JFET - JUNCTION FIELD EFFECT TRANSISTOR

MOSFET - METAL OXIDE SILICON FIELD EFFECT TRANSISTOR

DEPLETION TYPE


ENHANCEMENT TYPE

JFET

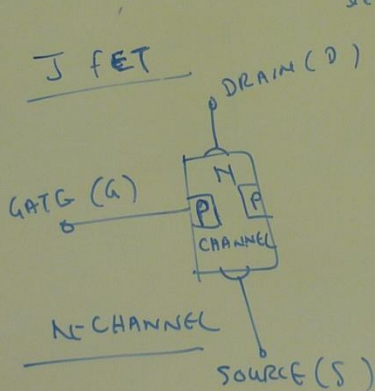


N-CHANNEL

SOURCE (S)

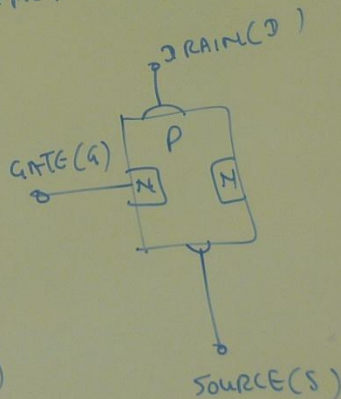


SOURCE (S)


P-CHANNEL

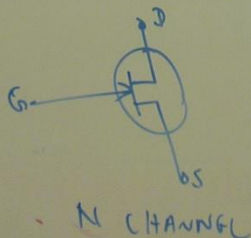

N CHANNEL

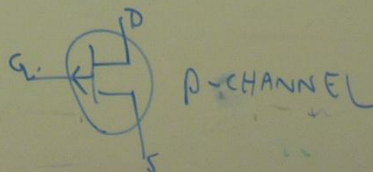

P-CHANNEL

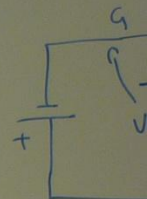

THE H
GREATER
THE H
THE
TO SO

WHEN

I_{DS}

$-V_{GS}$
 V_{GS} V_{GS}

IS OPERATED WITH REVERSE BIAS
VOLTAGE OPERATED DEVICE.


ION FIELD EFFECT TRANSISTOR

OXIDE SILICON FIELD EFFECT TRANSISTOR

TYPE



ENHANCEMENT TYPE

DRAIN(D)

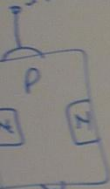

SOURCE(S)


CHANNEL

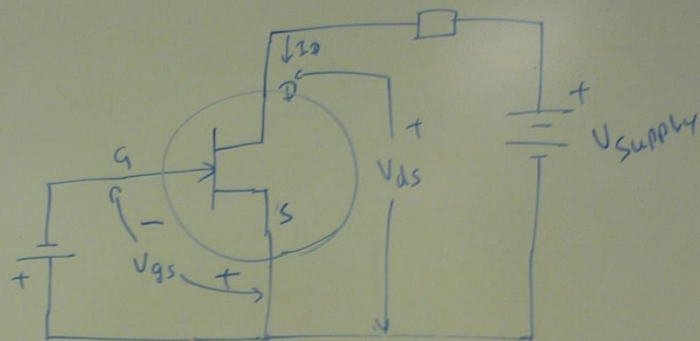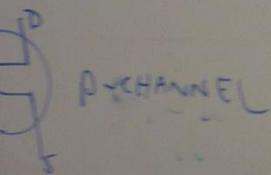

THE HIGHER THE VALUE OF V_{gs} , THE
GREATER THE DEPTH OF THE FIELD AND
THE HIGHER THE RESISTANCE OFFERED TO
THE CURRENT FLOWING FROM DRAIN
TO SOURCE TERMINAL.

WHEN V_{gs} IS ZERO $\rightarrow$ CURRENT FLOWS

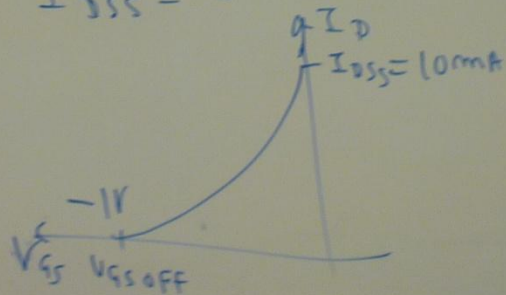I_{DSS} - DRAIN CURRENT FLOWS WHEN $V_{gs}=0$




DC CONDITION OF

$$V_{ds} = \frac{1}{2} V_{supply}$$

V_{gs} - REVERSED B

I_d

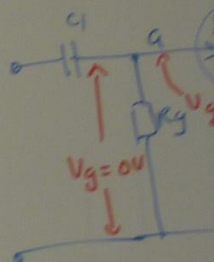

ph FOR THE A
 $V_{gs} = -1V$

(a) THE V

(b) R_d

(c) MULT

+
V_{supply}


g_s, THE
AND
ERED TO
DRAIN
CURRENT FLOWS

WITEN V_{gs}=0

DC CONDITION OF JFET

$$V_{ds} = \frac{1}{2} V_{supply}$$

V_{gs} - REVERSED BIAS

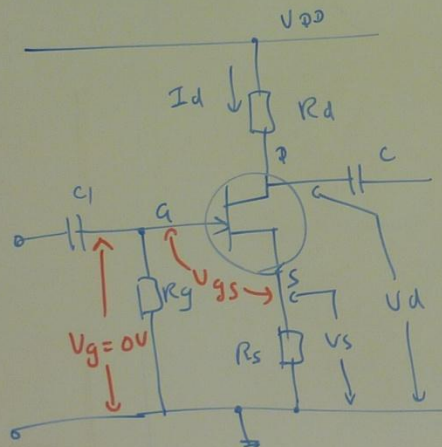

$$I_D = \frac{I_{DSS}}{2}$$

$$V_{gs} = -I_D R_S$$

$$R_S = \frac{V_{gs}}{I_D}$$

$$g_m = \frac{I_D}{V_{gs}}$$

$$V_D = V_{DD} - I_D R_D$$

$$R_g = 1 \text{ M}\Omega \text{ (OR) LESS}$$

(FOR JFET)

$$(a) I_D = \frac{I_{DSS}}{2} =$$

$$R_S = \frac{V_{gs}}{I_D} =$$

$$(b) V_D = V_{DD} - I_D R_D$$

$$I_D R_D = V_{DD} - V_D$$

$$R_D = \frac{V_{DD} - V_D}{I_D}$$

$$= \frac{10}{10} = 1 \text{ k}\Omega$$

$$= 10$$

$$=$$

pb

FOR THE ABOVE CIRCUIT DIAGRAM, V_{DD} = 10V,

V_{gs} = -1V I_{DSS} = 10mA CALCULATE

(a) THE VALUE OF R_S TO CORRECTLY BIAS THE CIRCUIT

(b) R_D

(c) MUTUAL CONDUCTANCE g_m (amp/volt)

$$(c) g_m = \frac{I_D}{V_{gs}}$$

$$I_D = \frac{I_{DSS}}{2}$$

$$V_{GS} = -I_D R_S$$

$$R_S = \frac{V_{GS}}{R_D} \quad g_m = \frac{I_D}{V_{GS}}$$

$$V_D = V_{DD} - I_D R_D$$

$$R_G = 1 \text{ M}\Omega \text{ (or) } \infty$$

(For JFET)

DIAGRAM, $V_{DD} = 10 \text{ V}$,

10 mA CALCULATE

TO CORRECTLY BIAS THE CIRCUIT

WCE g_m (amp/volt)

$$(a) I_D = \frac{I_{DSS}}{2} = \frac{10 \text{ mA}}{2} = 5 \text{ mA}$$

$$R_S = \frac{V_{GS}}{I_D} = \frac{1}{5 \text{ mA}} = 0.2 \times 10^3 \Omega = 200 \Omega$$

$$(b) V_D = V_{DD} - I_D R_D$$

$$I_D R_D = \frac{V_{DD} - V_D}{V_{DD} - V_D}$$

$$R_D = \frac{I_D}{V_{DD} - V_D}$$

$$= \frac{10 - \frac{V_{DD}}{2}}{5 \text{ mA}}$$

$$= \frac{10 - \frac{10}{2}}{5 \times 10^{-3}}$$

$$= \frac{5}{5 \times 10^{-3}} = 1 \text{ k}\Omega$$

$$(c) g_m = \frac{I_D}{V_{GS}} = \frac{5 \text{ mA}}{1 \text{ V}} = 5 \text{ mA/V}$$

$$(a) I_D = \frac{I_{DSS}}{2} = \frac{10 \text{ mA}}{2} = 5 \text{ mA}$$

$$R_S = \frac{V_{GS}}{I_D} = \frac{1}{5 \text{ mA}} = 0.2 \times 10^3 \Omega = 200 \Omega$$

$$(b) V_D = V_{DD} - I_D R_D$$

$$I_D R_D = V_{DD} - V_D$$

$$R_D = \frac{V_{DD} - V_D}{I_D}$$

$$= \frac{10 - \frac{V_{DD}}{2}}{5 \text{ mA}}$$

$$= \frac{10 - \frac{10}{2}}{5 \times 10^{-3}}$$

$$= \frac{5}{5 \times 10^{-3}} = 1 \text{ k}\Omega$$

$$(c) g_m = \frac{I_D}{V_{GS}} = \frac{5 \text{ mA}}{1 \text{ V}} = 5 \text{ mA/V}$$

MOSFET


THE MOSFET IS SIMILAR CONSTRUCTION TO JFET EXCEPT A VERY THIN LAYER OF SILICON OXIDE IS PLACED BETWEEN GATE AND CHANNEL

DE-MOSFET - DEPLETION ENHANCEMENT MODE


DESIGNED TO OPERATE WITH GATE-SOURCE VOLTAGE REVERSED BIAS

E-MOSFET - ENHANCEMENT MODE MOSFET -


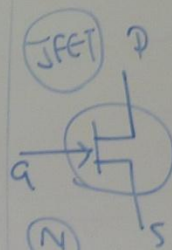
DESIGNED TO OPERATE GATE-SOURCE VOLTAGE FORWARD BIAS.





(N) TYPE

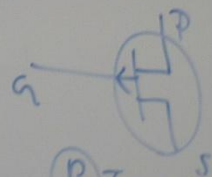

(P) TYPE

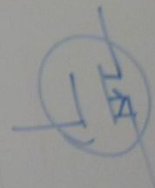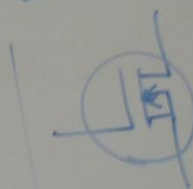

DE-MOSFET

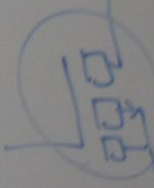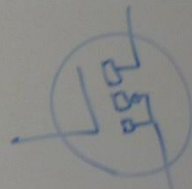

E-MOSFET

N-CHANNEL

P-CHANNEL

J-FET AMPLIFIER

THE J FET AMPLIFIER IS SIMPLER THAN BJT . IT USES LESS COMPONENT AND VOLTAGE OPERATED.


THE GATE-SOURCE VOLTAGE OF FET CONTROLS ITS DRAIN CURRENT
(IN BJT- BASE CURRENT CONTROLS COLLECTOR CURRENT)

- INPUT IMPEDANCE OF FET IS HIGHER THAN BJT

CD - common DRAIN , CS - common SOURCE .

J FET	—	BJT
CD		CE
CS	—	EMITTER FOLLOWER

J FET - CS

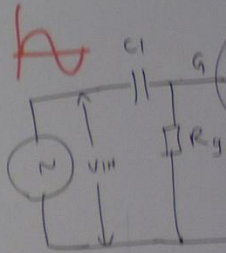


AC CONDITION

$V_{in} \uparrow$
 $V_S \text{ CONST}$
 $I_d \uparrow$
 $V_d \downarrow$
 i.e. OUT PO

AMPLER THAN BJT . IT USES LESS
 ET CONTROLS ITS DRAIN CURRENT
 S COLLECTOR CURRENT)
 ER THAN BJT
 COMMON SOURCE .

JFET - CS AMPLIFIER

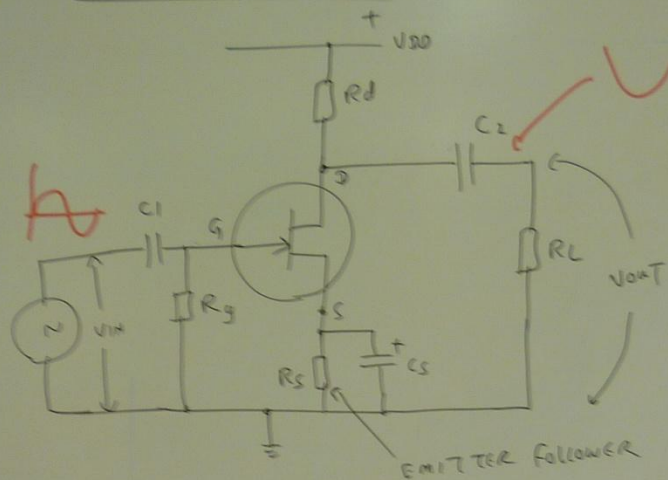

OUT PUT IS 180°
 OUT OF PHASE WITH
 INPUT.

AC CONDITION

$$V_{IN} \uparrow \rightarrow V_G \uparrow$$

V_S CONSTANT

$$I_D \uparrow$$

$$V_D \downarrow$$

i.e. OUT PUT DECREASES.

INCREASE IN INPUT CAUSES
 DECREASES IN OUT PUT
 (180° OPPOSITE)

$$A_V = \frac{g_m}{1 + \dots}$$

$$g_m = \text{TRANS}$$

$$R_D = \text{VALUE}$$

$$R_L = \text{VALUE}$$


$$R_S = \text{VALUE}$$

$$A_V = g_m (R_D \parallel R_L)$$

$$A_V = g_m R_D$$

$$r_{in} = R_G$$

$$r_{out} = R_D$$

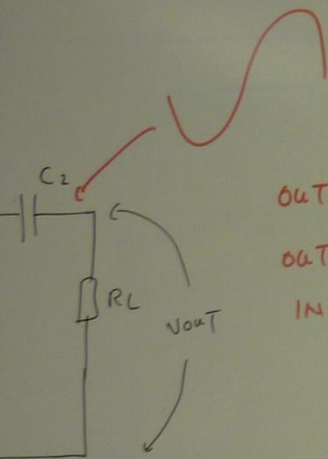

OUT PUT IS 180°
OUT OF PHASE WITH
INPUT.

CMOS FOLLOWER

INCREASE IN INPUT CAUSES
DECREASES IN OUT PUT
(180° OPPOSITE)

$$A_v = \frac{g_m (R_d \parallel R_L)}{1 + g_m R_s}$$

g_m = MUTUAL CONDUCTANCE Amp/VOLT

R_d = VALUE OF DRAIN RESISTOR

R_L = VALUE OF LOAD RESISTOR

R_s = VALUE OF UNBYPASSED SOURCE RESISTOR.

$$A_v = g_m (R_d \parallel R_L) \quad (R_s \text{ IS BYPASSED})$$

$$A_v = g_m R_d$$

(R_s IS BYPASSED, NO LOAD RESISTOR
CONNECTED)

$$r_{in} = R_g$$

$$r_{out} = R_d$$

J-FET Amplifier

THE J FET AMPLIFIER IS SIMPLER THAN BJT. IT USES LESS COMPONENT AND VOLTAGE OPERATED.


THE GATE-SOURCE VOLTAGE OF FET CONTROLS ITS DRAIN CURRENT
(IN BJT - BASE CURRENT CONTROLS COLLECTOR CURRENT)

- INPUT IMPEDANCE OF FET IS HIGHER THAN BJT

CD - COMMON DRAIN , CS - COMMON SOURCE .

J FET	—	BJT
CD		CE
CS	—	EMITTER FOLLOWER

J FET - CS

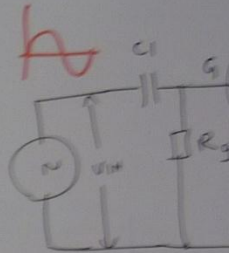

AC CONDITION

$V_{in} \uparrow$

V_S CONSTANT

$I_d \uparrow$

$V_d \downarrow$

i. OUT PUT

AMPLIFIER

SIMPLER THAN BJT. IT USES LESS
ATED.


FET CONTROLS ITS DRAIN CURRENT
CONTROLS COLLECTOR CURRENT)

HIGHER THAN BJT
COMMON SOURCE.

BJT
CE

EMITTER
FOLLOWER

JFET - CS AMPLIFIER

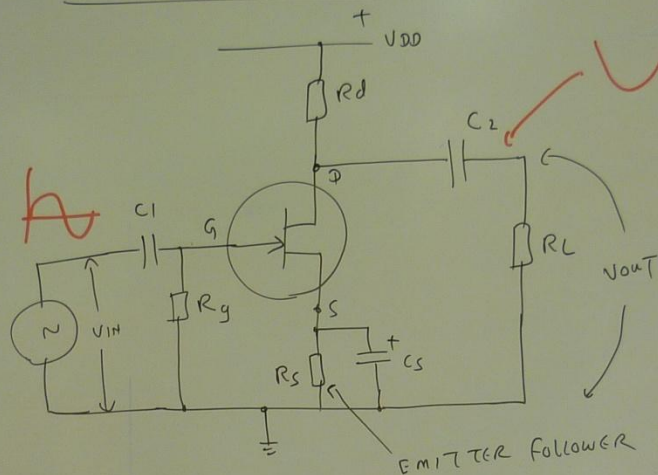

OUT PUT IS 180°
OUT OF PHASE WITH
INPUT.

AC CONDITION

$$V_{IN} \uparrow \rightarrow V_G \uparrow$$

V_S CONSTANT

$$I_D \uparrow$$

$$V_D \downarrow$$

∴ OUT PUT DECREASES.

INCREASE IN INPUT CAUSES
DECREASES IN OUT PUT
(180° OPPOSITE)

$$A_V =$$

$$g_m = m$$

$$R_D = V_A$$

$$R_L = U_A$$


$$R_S = U$$

$$A_V = g_m (R_D \parallel R_L)$$

$$A_V = g_m R_D$$

$$r_{in} = R_G$$

$$r_{out} = R_S$$

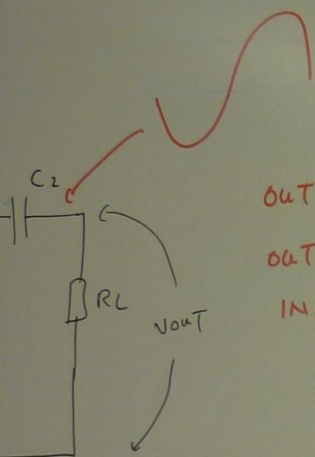

OUT PUT IS 180°
OUT OF PHASE WITH
INPUT.

CMR FOLLOWER

INCREASE IN INPUT CAUSES
DECREASES IN OUT PUT

(180° OPPOSITE)

$$A_v = \frac{g_m (R_d \parallel R_L)}{1 + g_m R_s}$$

g_m = MUTUAL CONDUCTANCE AMP/VOLT

R_d = VALUE OF DRAIN RESISTOR

R_L = VALUE OF LOAD RESISTOR

R_s = VALUE OF UNBYPASSED SOURCE RESISTOR.

$$A_v = g_m (R_d \parallel R_L) \quad (R_s \text{ IS BYPASSED})$$

$$A_v = g_m R_d$$

(R_s IS BYPASSED, NO LOAD RESISTOR
CONNECTED)

$$r_{in} = R_g$$

$$r_{out} = R_d$$

ph

FOR THE

CALCULA

(a)

(b)

(c)

(d)

ph

For THE GIVEN JFET CIRCUIT, $g_m = 3 \text{ mA/V}$


CALCULATE

(a) VOLTAGE GAIN OF THE CIRCUIT

(b) INPUT RESISTANCE

(c) OUTPUT RESISTANCE

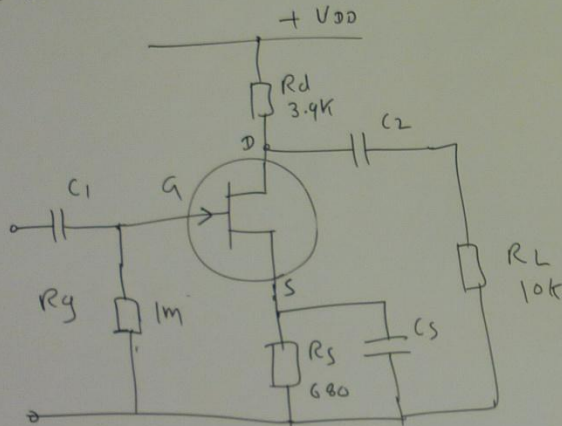(d) VOLTAGE GAIN IF BY PASS CAPACITOR IS REMOVED



$$R_d || R_L = \frac{R_d R_L}{R_d + R_L}$$

$$\begin{aligned} (a) A_v &= \frac{g_m (R_d || R_L)}{1 + g_m R_S} \\ &= \frac{g_m \times \frac{R_d R_L}{R_d + R_L}}{1 + g_m R_S} \\ &= \frac{3 \times 10^{-3} \times \frac{3.9 \times 10}{3.9 + 10}}{1 + 3 \times 10^{-3} \times 680} \\ &= 2.76 \end{aligned}$$

$$(b) r_{in} = r_g = 1 \text{ M}\Omega$$

$$(c) r_{out} = R_d = 3.9 \text{ K}\Omega$$

$$\begin{aligned} (d) A_v &= g_m (R_d || R_L) \\ &= 3 \times 10^{-3} \left(\frac{3.9 \times 10}{3.9 + 10} \right) = 8.4 \end{aligned}$$

$$= 3 \text{ mA/V}$$

IS REMOVED

RL
10k


$$\begin{aligned} (a) A_v &= \frac{g_m (R_d \parallel R_L)}{1 + g_m R_S} \\ &= \frac{g_m \times \frac{R_d R_L}{R_d + R_L}}{1 + g_m R_S} \\ &= \frac{3 \times 10^{-3} \times \frac{3.9 \times 10}{3.9 + 10}}{1 + 3 \times 10^{-3} \times 680} \\ &= 2.76 \end{aligned}$$

$$(b) r_{in} = r_g = 1 \text{ M}\Omega$$

$$(c) r_{out} = R_d = 3.9 \text{ k}\Omega$$

$$\begin{aligned} (d) A_v &= g_m (R_d \parallel R_L) \\ &= 3 \times 10^{-3} \left(\frac{3.9 \times 10}{3.9 + 10} \right) = 8.4 \end{aligned}$$

COMMON DRAIN JFET AMPLIFIER

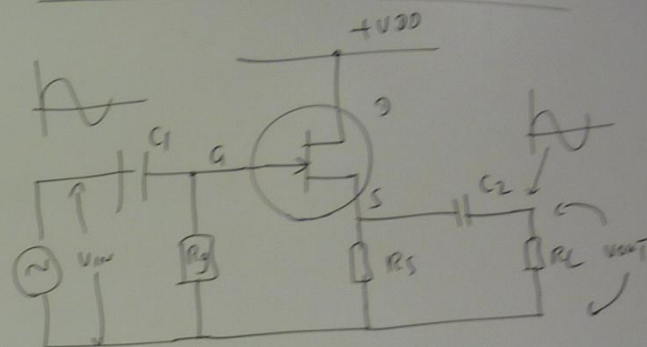

- HIGH INPUT RESISTANCE
- LOW OUTPUT RESISTANCE
- VOLTAGE GAIN ≈ 1

- APPLICATION
TO CHARGE
CAPACITOR

$$A_v = \frac{g_m (R_S \parallel R_L)}{1 + g_m R_S}$$

pb

$$r_{in} = R_g$$

$$r_{out} = \frac{R_S}{1 + g_m R_S}$$


FOR THE

(a)

(b)

(c)

JFET Amplifier

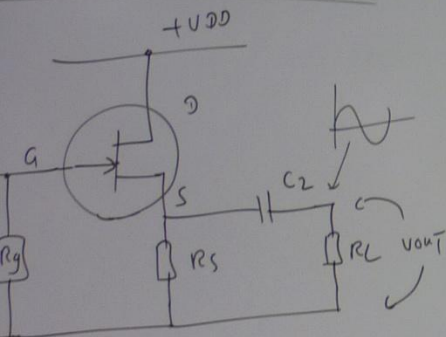

PUT RESISTANCE
PUT RESISTANCE
GAIN ≈ 1

$$\frac{g_m (R_s \parallel R_L)}{1 + g_m R_s}$$


$$= \frac{R_g}{R_s}$$

$$= \frac{R_s}{1 + g_m R_s}$$

APPLICATION


TOUCH SCREEN TECHNOLOGY
COMPUTER TOUCH SWITCH

pb

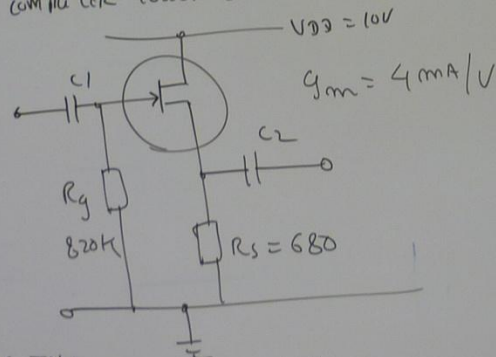

FOR THE GIVEN CIRCUIT, CALCULATE

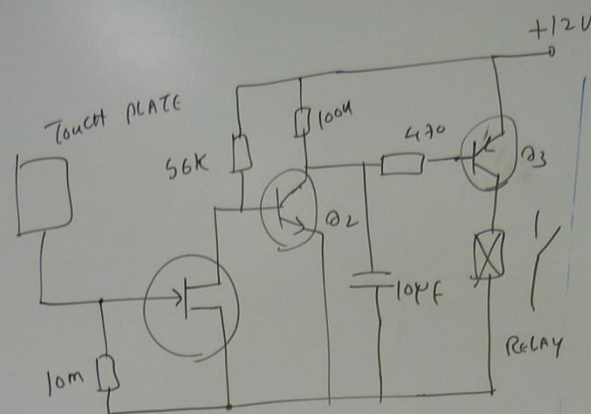- VOLTAGE GAIN
- INPUT RESISTANCE
- OUTPUT RESISTANCE



$$(a) A_v \approx 1$$

$$(b) r_{in} = R_g = 820K$$

$$(c) r_{out} = \frac{R_s}{1 + g_m R_s}$$


$$= \frac{680}{1 + 4 \times 10^{-3} \times 680}$$

$$= 182 \Omega$$

POWER OUTPUT STAGE (PART-1)

FIRST AND INTERMEDIATE STAGE AMPLIFIERS CAN NOT HANDLE THE LARGE POWER. THE OUTPUT STAGE REQUIRES THE POWER AMPLIFIER. THE OUTPUT STAGE MAY BE SERVO MOTOR (OR) INDICATING DEVICES (OR) SPEAKER.

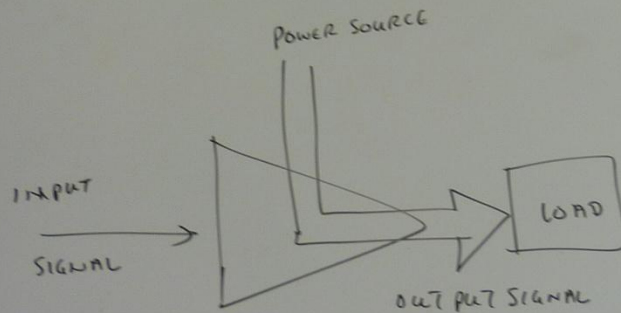OUTPUT STAGE USUALLY HAS UNITY VOLTAGE GAIN



THE BASIC REQUIREMENTS FOR ANY POWER OUTPUT STAGE ARE


- HIGH EFFICIENCY
- LOW DISTORTION
- LOW OUTPUT IMPEDANCE

OUTPUT STAGE AMPLIFIERS

- (1) CLASS (A)
- (2) CLASS (B)
- (3) CLASS (A+B)

CLASS (A)

- OUTPUT DEVIATION

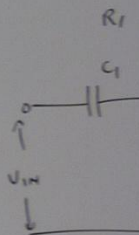


COM
CLA

CLASS (A)

- MAXIMUM
- MAXIMUM
- LOW DISTORTION
- HIGH
- OUTPUT

CLASS (A) Amplifier

— output device conducts for 360°

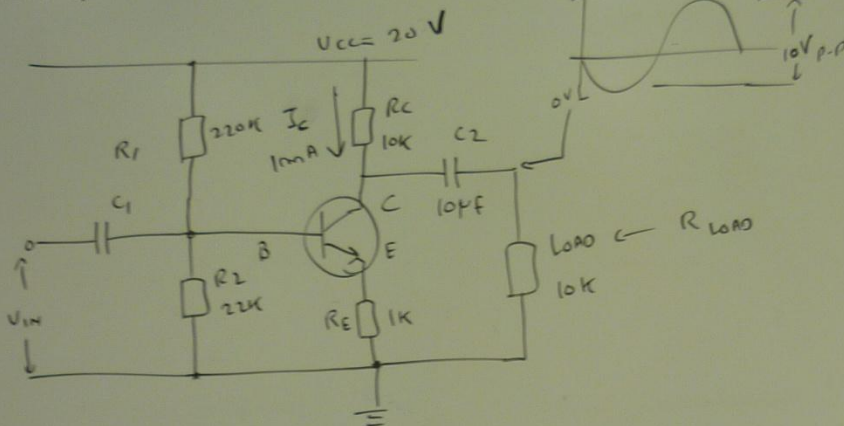

COMMON EMITTER RC COUPLED
CLASS (A) AMPLIFIER

CLASS (A) AMPLIFIER CHARACTERISTICS

- MAXIMUM EFFICIENCY 25% FOR RC COUPLED TYPE
- MAXIMUM EFFICIENCY 50% FOR TRANSFORMER COUPLED TYPE
- LOW DISTORTION THAN CLASS (B)
- HIGH QUIESCENT CURRENT
- OUTPUT DEVICE CONDUCTS FOR 360° OF INPUT SIGNAL

$$P_{in} = V_{CC} \times I_C$$

$$V_{O-rms} = \frac{V_{O-P-P}}{2\sqrt{2}}$$


$$P_{out} = \frac{(V_{O-rms})^2}{R_{LOAD}}$$

$$\% \eta = \frac{P_{out}}{P_{in}} \times 100$$

Pb CALCULATE (a) P_{in} (b) P_{out}
(c) V_{O-rms} (d) EFFICIENCY OF
ABOVE CLASS (A) AMPLIFIER

$$P_{in} = V_{CC} \times I_C = 20 \times 1\text{mA} = 20\text{mW}$$
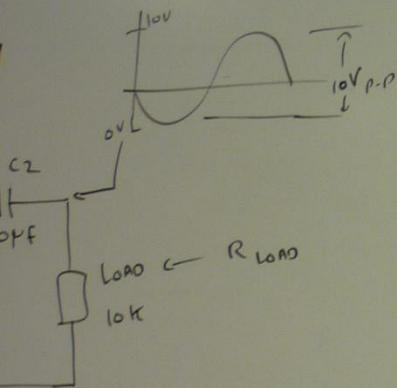
$$V_{O-rms} = \frac{V_{O-P-P}}{2\sqrt{2}} = \frac{10}{2 \times 1.4142} = 3.53\text{V}$$



$$P_{IN} = V_{CC} \times I_C$$

$$V_{O-rms} = \frac{V_{O-P-P}}{2\sqrt{2}}$$

$$P_{OUT} = \frac{(V_{O-rms})^2}{R_{LOAD}}$$

$$\% \eta = \frac{P_{OUT}}{P_{IN}} \times 100$$

Pb CALCULATE (a) P_{IN} (b) P_{OUT}
(c) V_{O-rms} (d) EFFICIENCY OF
ABOVE CLASS(A) AMPLIFIER

$$P_{IN} = V_{CC} \times I_C = 20 \times 1\text{mA} = 20\text{mW}$$

$$V_{O-rms} = \frac{V_{O-P-P}}{2\sqrt{2}} = \frac{10}{2 \times 1.4142} = 3.53\text{V}$$

$$P_{OUT} = \frac{(V_{O-rms})^2}{R_{LOAD}}$$

$$= \frac{(3.53)^2}{10\text{k}} = 1.25\text{mW}$$

$$\% \eta = \frac{P_{OUT}}{P_{IN}} \times 100$$

$$= \frac{1.25}{20} \times 100 = 6.25\%$$

Pb CALCULATE THE INPUT POWER
REQUIRED FOR AN INDUSTRIAL SOUND
SYSTEM WITH AN EFFICIENCY OF
20% THAT HAS AN OUTPUT POWER
OF 50kW.

$$\% \eta = \frac{P_{OUT}}{P_{IN}} \times 100$$

$$20 = \frac{50}{P_{IN}} \times 100 \rightarrow P_{IN} = \frac{50 \times 100}{20} = 250\text{ kW}$$

$$\eta = \frac{P_{OUT}}{P_{IN}} \times 100$$

$$P_{IN} = V_{CC} \times I_C$$

$$V_{rms} = \frac{V_{O\ p-p}}{2\sqrt{2}}$$

$$P_{OUT} = \frac{(V_{O-rms})^2}{R_{LOAD}}$$

$$\% \eta = \frac{P_{OUT}}{P_{IN}} \times 100$$

CALCULATE (a) P_{IN} (b) P_{OUT}
 V_{O-rms} (c) EFFICIENCY OF
 A CLASS (A) AMPLIFIER

$$V_{CC} \times I_C = 20 \times 1\text{mA} = 20\text{mW}$$

$$V_{rms} = \frac{V_{O\ p-p}}{2\sqrt{2}} = \frac{10}{2 \times 1.4142} = 3.53\text{V}$$

$$P_{OUT} = \frac{(V_{O-rms})^2}{R_{LOAD}} = \frac{(3.53)^2}{10\text{k}} = 1.25\text{mW}$$

$$\% \eta = \frac{P_{OUT}}{P_{IN}} \times 100 = \frac{1.25}{20} \times 100 = 6.25\%$$

Pb CALCULATE THE INPUT POWER
 REQUIRED FOR AN INDUSTRIAL SOUND
 SYSTEM WITH AN EFFICIENCY OF
 20% THAT HAS AN OUTPUT POWER
 OF 50kW.

$$\% \eta = \frac{P_{OUT}}{P_{IN}} \times 100$$

$$20 = \frac{50}{P_{IN}} \times 100 \rightarrow P_{IN} = \frac{50 \times 100}{20} = 250\text{kW}$$


$$I = \frac{P_{IN}}{V} = \frac{250\text{kW}}{240} = \frac{250 \times 10^3}{240} = 1041.67\text{A}$$

CLASS (A)

POWER OUTPUT STAGE (PART-1)

FIRST AND INTERMEDIATE STAGE AMPLIFIERS CAN NOT HANDLE THE LARGE POWER. THE OUTPUT STAGE REQUIRES THE POWER AMPLIFIER. THE OUTPUT STAGE MAY BE SERVO MOTOR (OR) INDICATING DEVICES (OR) SPEAKER.

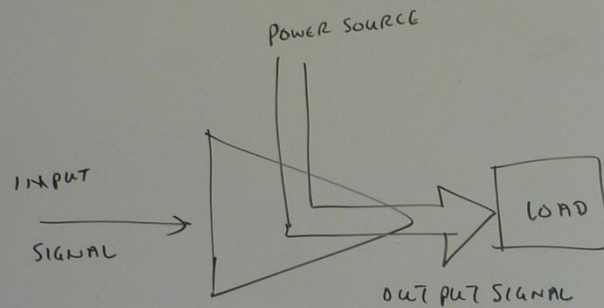OUTPUT STAGE USUALLY HAS UNITY VOLTAGE GAIN



THE BASIC REQUIREMENTS FOR ANY POWER OUTPUT STAGE ARE


- HIGH EFFICIENCY
- LOW DISTORTION
- LOW OUTPUT IMPEDANCE

OUTPUT STAGE AMPLIFIERS

- (1) CLASS (A)
- (2) CLASS (B)
- (3) CLASS (A+B)

CLASS (A) AMPLIFIER

- OUTPUT DEVICE

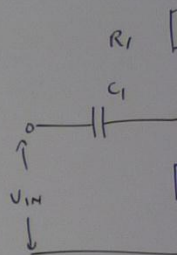


COMMON
CLASS

CLASS (A) AMPLIFIER

- MAXIMUM
- MAXIMUM
- LOW DIST
- HIGH Q
- OUTPUT

CLASS (A) Amplifier

— OUTPUT DEVICE CONDUCTS FOR 360°

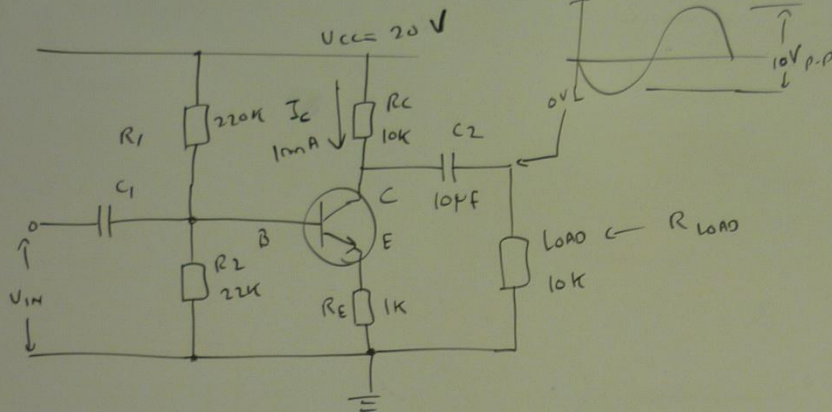

COMMON EMITTER RC COUPLED
CLASS (A) AMPLIFIER

CLASS (A) AMPLIFIER CHARACTERISTICS

- MAXIMUM EFFICIENCY 25% FOR RC COUPLED TYPE
- MAXIMUM EFFICIENCY 50% FOR TRANSFORMER COUPLED TYPE
- LOW DISTORTION THAN CLASS (B)
- HIGH QUIESCENT CURRENT
- OUTPUT DEVICE CONDUCTS FOR 360° OF INPUT SIGNAL

$$P_{IN} = V_{CC} \times I_C$$

$$V_{O-rms} = \frac{V_{O-P-P}}{2\sqrt{2}}$$

$$P_{OUT} = \frac{(V_{O-rms})^2}{R_{LOAD}}$$

$$\% \eta = \frac{P_{OUT}}{P_{IN}} \times 100$$

Pb CALCULATE (a) P_{IN} (b) P_{OUT}
(c) V_{O-rms} (d) EFFICIENCY OF
ABOVE CLASS (A) AMPLIFIER

$$P_{IN} = V_{CC} \times I_C = 20 \times 1\text{mA} = 20\text{mW}$$

$$V_{O-rms} = \frac{V_{O-P-P}}{2\sqrt{2}} = \frac{10}{2 \times 1.4142} = 3.53\text{V}$$

$$P_{OUT} = \frac{V_{O-rms}^2}{R_{LOAD}}$$

$$= \frac{(3.53)^2}{10k}$$

$$\% \eta = \frac{P_{OUT}}{P_{IN}} \times 100$$

$$= \frac{1.19}{20} \times 100$$

Pb CALCULATE
REQUIRED
SYSTEM WITH
20% THAT
OF SOLW.

$$\% \eta =$$

$$20 = \frac{50}{P_{IN}}$$

$$V_{cc} \times I_c$$

$$= \frac{V_{o \text{ p-p}}}{2\sqrt{2}}$$

$$\frac{(V_{o-rms})^2}{R_{LOAD}}$$

$$\frac{P_{OUT}}{P_{IN}} \times 100$$

Q1. Calculate (a) P_{IN} (b) P_{OUT} (c) Efficiency of CLASS (A) AMPLIFIER

$$I_c = 20 \times 1 \text{ mA} = 20 \text{ mA}$$

$$\frac{V_{o \text{ p-p}}}{2\sqrt{2}} = \frac{10}{2 \times 1.4142}$$

$$= 3.53 \text{ V}$$

$$P_{OUT} = \frac{(V_{o-rms})^2}{R_{LOAD}}$$

$$= \frac{(3.53)^2}{10 \text{ k}} = 1.25 \text{ mW}$$

$$\% \eta = \frac{P_{OUT}}{P_{IN}} \times 100$$

$$= \frac{1.25}{20} \times 100 = 6.25\%$$

Pb Calculate the input power required for an industrial sound system with an efficiency of 20% that has an output power of 50 kW.

$$\% \eta = \frac{P_{OUT}}{P_{IN}} \times 100$$

$$20 = \frac{50}{P_{IN}} \times 100 \rightarrow P_{IN} = \frac{50 \times 100}{20} = 250 \text{ kW}$$

$$I = \frac{P_{IN}}{V} = \frac{250 \text{ kW}}{240}$$

$$= \frac{250 \times 10^3}{240}$$

$$= 1041.67 \text{ A}$$

GENERAL FEATURES OF CLASS (B) AMPLIFIER


- MAXIMUM EFFICIENCY - 78.5%
- HIGH DISTORTION (COMPARED TO CLASS (A))
- LOWER POWER DISSIPATION BY THE OUTPUT DEVICES
- TWO OUTPUT DEVICES NEEDED

BOTH CONDUCT FOR 180°.

- VOLTAGE GAIN (A_V) = UNITY

POWER GAIN (A_P) = CURRENT GAINS OF TRANSISTOR

CLASS (B) POWER

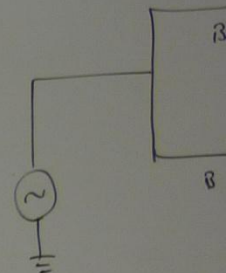

- CLASS (B) AMPLIFIER OF TWO OUTPUT
- Q_1 CONDUCTS FOR THE INPUT SIGNAL
- Q_2 CONDUCTS FOR THE INPUT SIGNAL
- THE OUTPUT SIGNAL IS BOTH TRANSISTORS

Q_1 CONDUCTS FOR 180°
 Q_2 OFF

1.25 mW

6.25%

$$I = \frac{P_{IM}}{V} = \frac{250 \text{ kW}}{240} = \frac{250 \times 10^3}{240} = 1041.67 \text{ A}$$

GENERAL FEATURES OF CLASS (B) AMPLIFIER

- MAXIMUM EFFICIENCY - 78.5%
- HIGH DISTORTION (COMPARED TO CLASS (A))
- LOWER POWER DISSIPATION BY THE OUTPUT DEVICES
- TWO OUTPUT DEVICES NEEDED


BOTH CONDUCT FOR 180°

- VOLTAGE GAIN (A_V) = UNITY

POWER GAIN (A_P) = CURRENT GAINS OF TRANSISTOR

$$P_{IM} = \frac{50 \times 100}{20} = 250 \text{ W}$$

CLASS (B) POWER OUTPUT STAGE



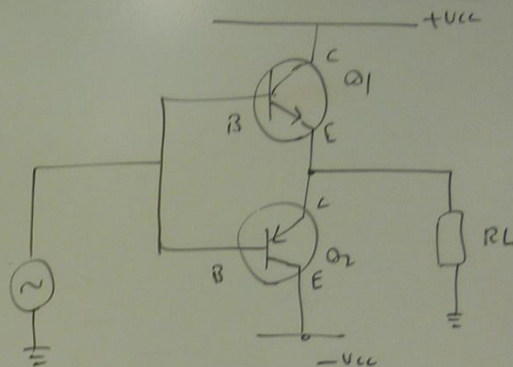


- CLASS (B) AMPLIFIER REQUIRES A MINIMUM OF TWO OUTPUT DEVICES
- Q_1 CONDUCTS FOR THE POSITIVE HALF OF THE INPUT SIGNAL
- Q_2 CONDUCTS FOR THE NEGATIVE HALF.
- THE OUTPUT SIGNAL IS PRODUCED BY BOTH TRANSISTORS.


Q_1 CONDUCTS - Q_2 OFF

Q_1 OFF - Q_2 CONDUCT

DUAL POLARITY POWER SUPPLY

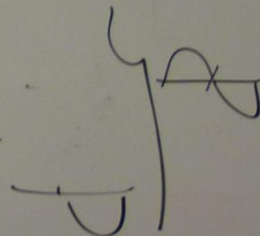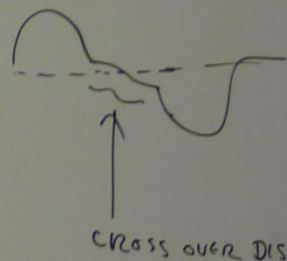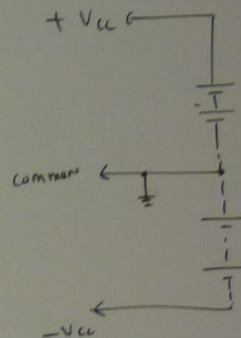

(B) POWER OUTPUT STAGE

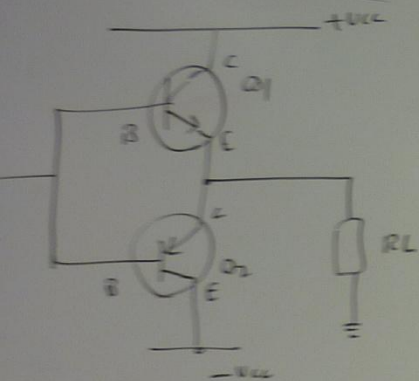

AMPLIFIER REQUIRES A MINIMUM
OUTPUT DEVICES

FOR THE POSITIVE HALF OF
INPUT SIGNAL


CONDUCTS FOR THE NEGATIVE HALF.

OUTPUT SIGNAL IS PRODUCED BY
TRANSISTORS.

CONDUCTS - Q2 off

off - Q2 conducts

DUAL POLARITY POWER SUPPLY

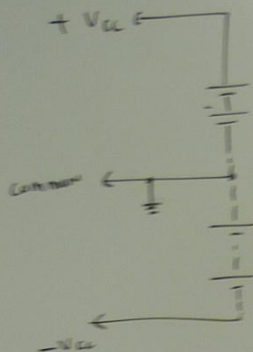

CROSS OVER DISTORTION


POWER OUTPUT EQUATIONS

$$P_{OUT} = \frac{(V_{O-RMS})^2}{R_{LOAD}}$$

$$P_{OUT} = \frac{\left(\frac{V_{O-P-P}}{2\sqrt{2}}\right)^2}{R_{LOAD}}$$

$$P_{OUT} = \frac{(V_{O-P-P})^2}{8 R_{LOAD}}$$

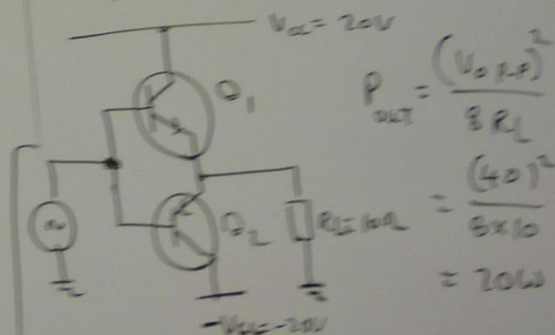P3 CALCULATE THE MAXIMUM OUTPUT
POWER FOR THE GIVEN CIRCUIT



$$P_{OUT} = \frac{(V_{O-P-P})^2}{8 R_L}$$

$$= \frac{(40)^2}{8 \times 10}$$

$$= 20W$$

$$I = \frac{P_{in}}{V} = \frac{250 \text{ kW}}{240} = \frac{250 \times 10^3}{240} = 1041.67 \text{ A}$$

GENERAL FEATURES OF CLASS (B) AMPLIFIER


- MAXIMUM EFFICIENCY - 78.5%
- HIGH DISTORTION (COMPARED TO CLASS (A))
- LOWER POWER DISSIPATION BY THE OUTPUT DEVICES
- TWO OUTPUT DEVICES NEEDED

BOTH CONDUCT FOR 180°

- VOLTAGE GAIN (A_V) = UNITY



POWER GAIN (A_P) = CURRENT GAINS OF TRANSISTOR

CLASS (B) POWER OUTPUT STAGE

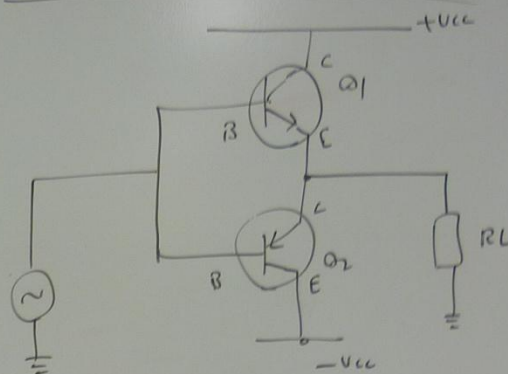


- CLASS (B) AMPLIFIER REQUIRES A MINIMUM OF TWO OUTPUT DEVICES
- Q_1 CONDUCTS FOR THE POSITIVE HALF OF THE INPUT SIGNAL
- Q_2 CONDUCTS FOR THE NEGATIVE HALF.
- THE OUTPUT SIGNAL IS PRODUCED BY BOTH TRANSISTORS.

DUAL POLARITY POWER SUPPLY

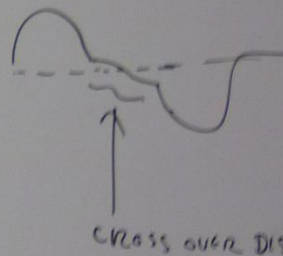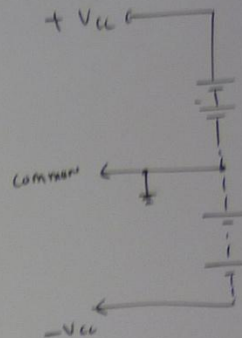

 Q_1 CONDUCTS - Q_2 OFF


Q_1 OFF - Q_2 CONDUCT

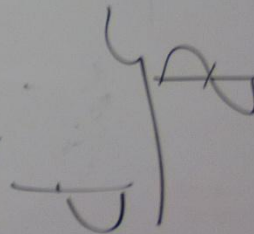

UT POWER
TRIAL SOUND
CIENCY OF
UT PUT POWER


$$I_{IN} = \frac{50 \times 100}{20} = 250 \text{ mA}$$

(B) POWER OUTPUT STAGE

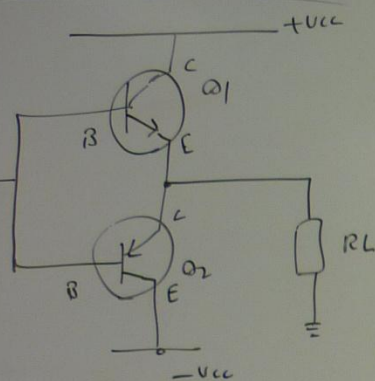


B) AMPLIFIER REQUIRES A MINIMUM OUTPUT DEVICES
 CONDUCTS FOR THE POSITIVE HALF OF INPUT SIGNAL
 CONDUCTS FOR THE NEGATIVE HALF.
 INPUT SIGNAL IS PRODUCED BY TRANSISTORS.

CONDUCTS - Q₂ OFF
 OFF - Q₂ CONDUCT

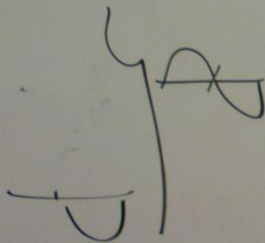

DUAL POLARITY POWER SUPPLY

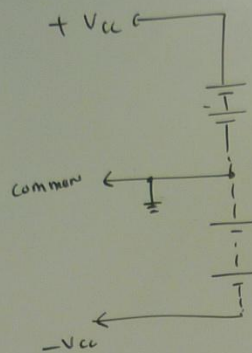

CROSS OVER DISTORTION


POWER OUTPUT EQUATION

$$P_{out} = \frac{(V_{o-rms})^2}{R_{load}}$$

$$P_{out} = \frac{\left(\frac{V_{o-p-p}}{2\sqrt{2}}\right)^2}{R_{load}}$$

$$P_{out} = \frac{(V_{o-p-p})^2}{8 R_{load}}$$

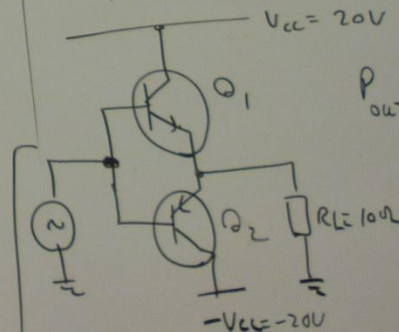pb CALCULATE THE MAXIMUM OUTPUT POWER FOR THE GIVEN CIRCUIT




$$P_{out} = \frac{(V_{o-p-p})^2}{8 R_L}$$

$$= \frac{(40)^2}{8 \times 10}$$

$$= 20W$$

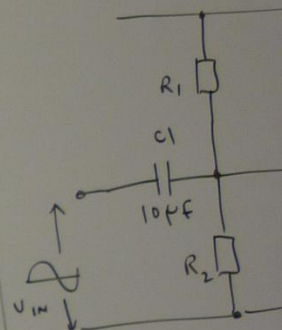pb FOR THE GIVEN
 (a) STATE THE OPT
 (b) CALCULATE THE
 (c) CALCULATE TH
 (d) STATE THE



$$V_c(RMS) = \frac{V}{\sqrt{2}}$$

$$V_c(max) = \sqrt{2} V_c(RMS)$$

$$P_{out} = \frac{(V_o)^2}{R}$$

$$I_c = \frac{V_{cc} - V_c}{R_c}$$


POWER OUTPUT EQUATION

$$P_{OUT} = \frac{(V_{O-RMS})^2}{R_{LOAD}}$$

$$= \frac{\left(\frac{V_{O-P-P}}{2.52}\right)^2}{R_{LOAD}}$$

$$= \frac{(V_{O-P-P})^2}{8 R_{LOAD}}$$

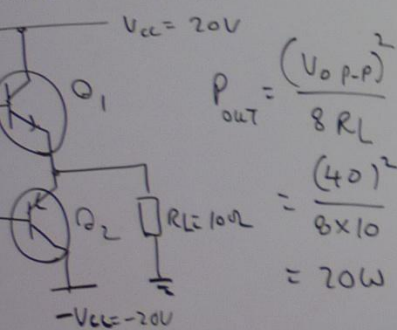CALCULATE THE MAXIMUM OUTPUT POWER FOR THE GIVEN CIRCUIT



$$P_{OUT} = \frac{(V_{O-P-P})^2}{8 R_L}$$

$$= \frac{(40)^2}{8 \times 10}$$

$$= 20W$$


pb FOR THE GIVEN CIRCUIT

(a) STATE THE OPTIMUM VALUE OF COLLECTOR VOLTAGE

(b) CALCULATE THE MAXIMUM OUTPUT POWER

(c) CALCULATE THE POWER BEING DISSIPATED BY Q1 WHEN THE INPUT SIGNAL IS ZERO

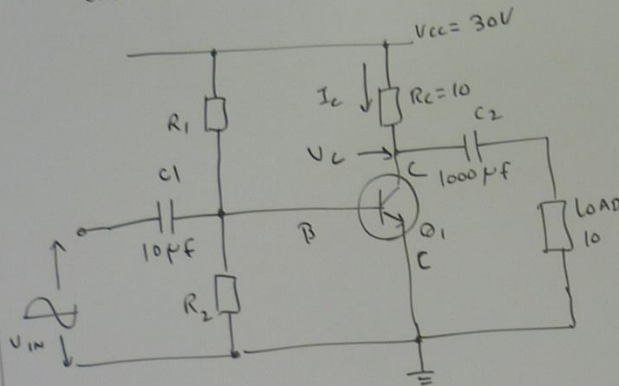(d) STATE THE MAXIMUM EFFICIENCY THE CIRCUIT CAN ACHIEVE.



$$V_{C(RMS)} = \frac{V_{CC}}{2} = \frac{30}{2} = 15V$$

$$V_{C(MAX)} = \sqrt{2} V_{C(RMS)} = \sqrt{2} \times 15 = 21.2V$$


$$P_{OUT} = \frac{(V_{O-RMS})^2}{R_{LOAD}} = \frac{15^2}{10} = 22.5W$$

$$I_{CQ} = \frac{V_{CC} - V_{CE}}{R_C} = \frac{30 - 15}{10} = 1.5A$$

$$P_{IN} = V_{CC} \times I_{CQ} = 30 \times 1.5 = 45W$$

$$\eta = \frac{P_{OUT}}{P_{IN}} \times 100 = \frac{22.5}{45} = 50\%$$

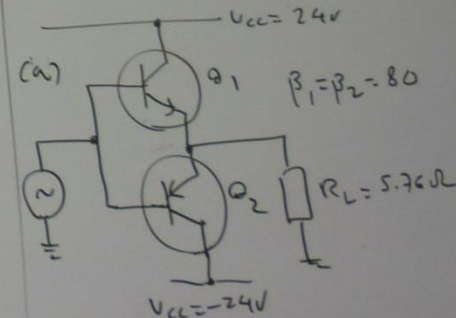pb FOR THE GIVEN CIRCUIT, CALCULATE
(a) THE THEORETICAL MAXIMUM OUTPUT POWER
(b) THE POWER GAIN OF THE CIRCUIT.



$$P_{O} = \frac{(V_{O-P-P})^2}{8 R_L} = \frac{(2 \times 24)^2}{8 \times 5.76}$$


$$= 50W$$

$$A_p = \beta_1 = \beta_2$$

$$A_p = 80$$

POWER OUTPUT STAGE (PART-2)


CLASS (AB) AMPLIFIER

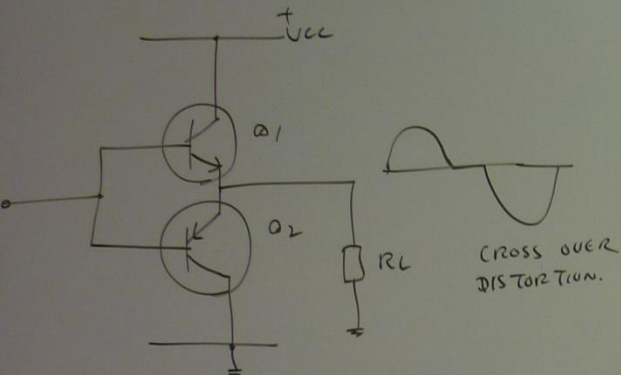

TO ELIMINATE THE CROSS OVER DISTORTION, FORWARD BIAS OF 0.6V NEEDS TO BE APPLIED TO BOTH TRANSISTORS.

CLASS (B) + 0.6V FORWARD BIAS TO ELIMINATE CROSS OVER DISTORTION = CLASS AB AMPLIFIER

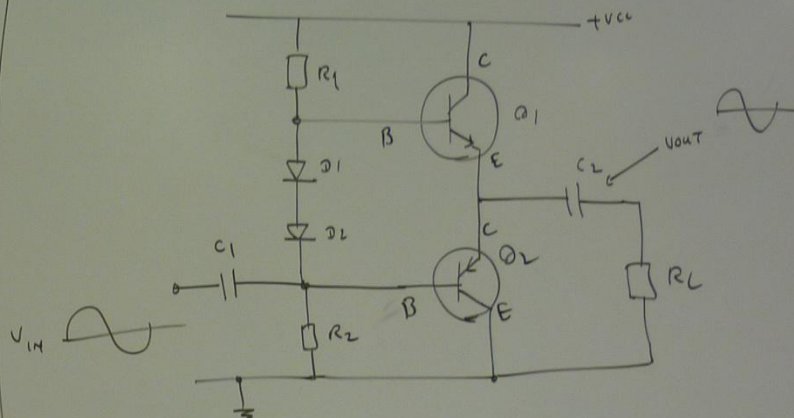
THE BASIC CLASS AB COMPLEMENTARY SYMMETRY AMPLIFIER



CHARACTERISTICS

- maximum efficiency = 78.5%
- EACH TRANSISTOR CONDUCTS FOR EXACTLY 180° OF THE INPUT SIGNAL
- THE CROSS OVER DISTORTION IS ELIMINATED
- THE FORWARD BIAS FOR THE TRANSISTOR IS SUPPLIED BY THE INPUT SIGNAL

DC CONDITION

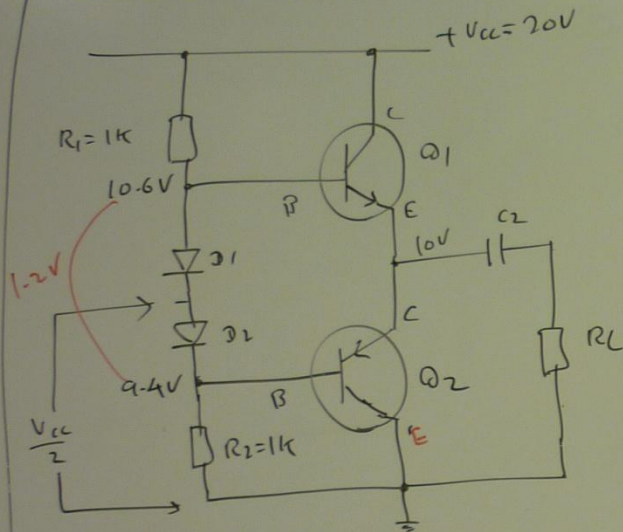

- R_1 must be equal to R_2
- THE DIODES ARE USED TO ENSURE THAT THERE IS A DIFFERENCE OF 1.2V BETWEEN THE VOLTAGES AT THE BASES OF Q_1 AND Q_2
- BOTH TRANSISTOR HAVE A FORWARD BIAS OF 0.6V ACROSS THEIR BASE-EMITTER JUNCTION

LIMITATION


EMITTER VOLTAGE MUST ALWAYS BE LESS 0.6V THAN BASE VOLTAGE.

BOOT STRAPPING

SOME TIME, IT WILL NOT FULLY FILL $V_E - V_B = 0.6V$ WHEN THE SIGNAL SWING IS HIGHER. THE CROSS OVER DISTORTION CAN HAPPEN AGAIN.


TO ELIMINATE THE CROSS OVER DISTORTION AT HIGH SIGNAL SWING, THE BOOTSTRAPPING CIRCUIT IS APPLIED.

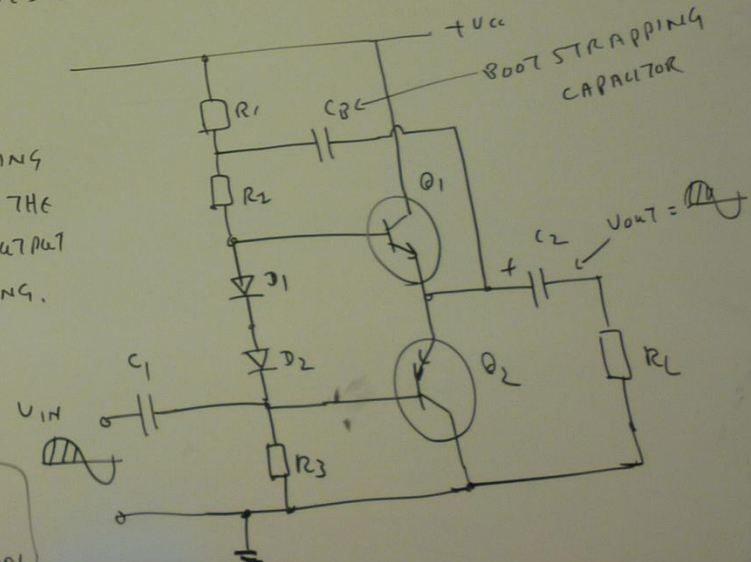APPLYING BOOTSTRAPPING TO OBTAIN THE GREATER OUTPUT SIGNAL SWING.



POWER OUTPUT STAGE (PART-2)


CLASS (AB) AMPLIFIER

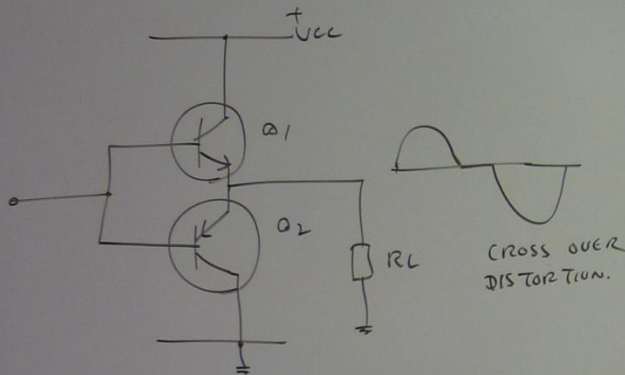

TO ELIMINATE THE CROSS OVER DISTORTION,
FORWARD BIAS OF 0.6V NEEDS TO BE
APPLIED TO BOTH TRANSISTORS.

CLASS (B) + 0.6V FORWARD
BIAS TO ELIMINATE CROSS OVER DISTORTION
= CLASS AB AMPLIFIER

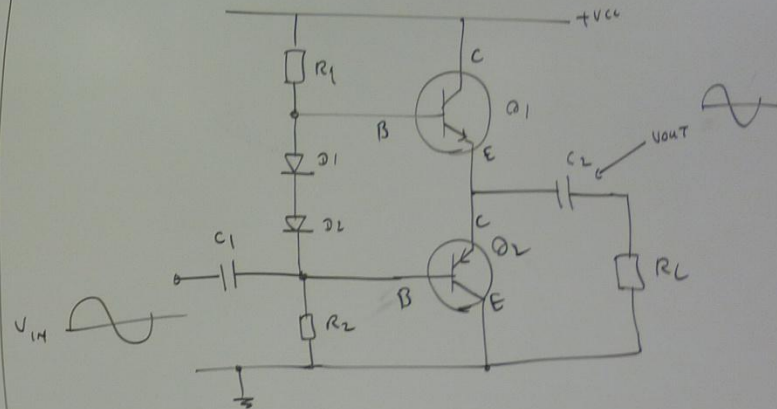THE BASIC CLASS AB COMPLEMENTARY SYMMETRY AMPLIFIER




CHARACTERISTICS

- MAXIMUM EFFICIENCY = 78.5%
- EACH TRANSISTOR CONDUCTS FOR EXACTLY 180° OF THE INPUT SIGNAL
- THE CROSS OVER DISTORTION IS ELIMINATED
- THE FORWARD BIAS FOR THE TRANSISTOR IS SUPPLIED BY THE INPUT SIGNAL

amplifier

DC CONDITION

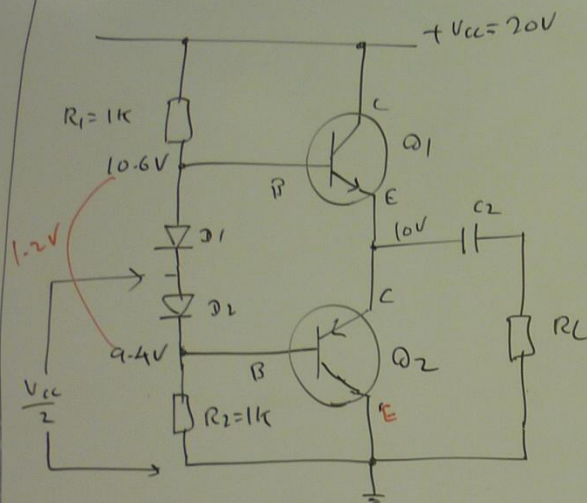

- R_1 must be equal to R_2
- THE DIODES ARE USED TO ENSURE THAT THERE IS A DIFFERENCE OF 1.2V BETWEEN THE VOLTAGES AT THE BASES OF Q_1 AND Q_2
- BOTH TRANSISTOR HAVE A FORWARD BIAS OF 0.6V ACROSS THEIR BASE-EMITTER JUNCTION

LIMITATION


EMITTER VOLTAGE MUST ALWAYS BE LESS 0.6V THAN BASE VOLTAGE.

BOOT STRAPPING

SOME TIME, IT WILL NOT FULL FILL $V_E - V_B = 0.6V$ WHEN THE SIGNAL SWING IS HIGHER. THE CROSS OVER DISTORTION CAN HAPPEN AGAIN.


TO ELIMINATE THE CROSS OVER DISTORTION AT HIGH SIGNAL SWING, THE BOOTSTRAPPING CIRCUIT IS APPLIED.

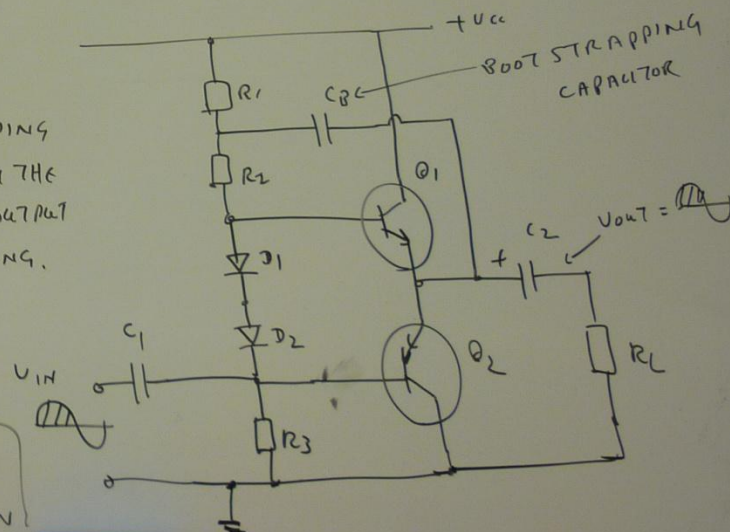APPLYING BOOTSTRAPPING TO OBTAIN THE GREATER OUTPUT SIGNAL SWING.




DARLINGTON OUTPUT TRANSISTORS

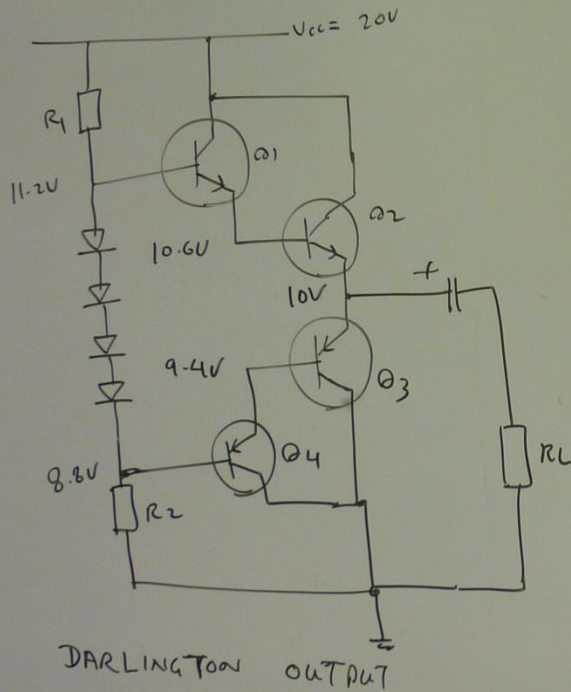TO INCREASE THE CURRENT GAIN OF THE OUTPUT TRANSISTORS, IT IS COMMON TO USE THE DARLINGTON PAIRS.



QUASI COMPLEMENTARY AMPLIFIER

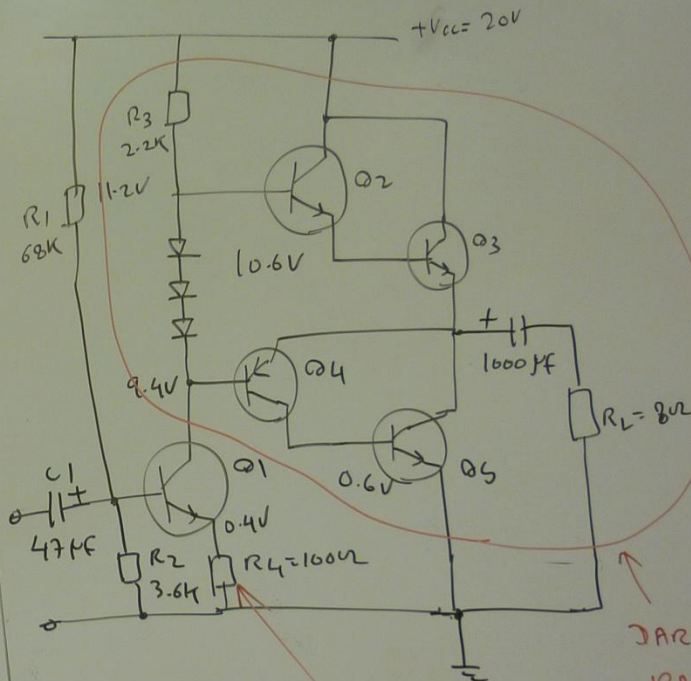


POWER AMPLIFIER WITH AMPLIFIER DRIVER STAGE

DRIVER STAGE

DARLINGTON PAIR
(TO INCREASE CURRENT GAIN)

QUASI COMPLEMENTARY AMPLIFIER

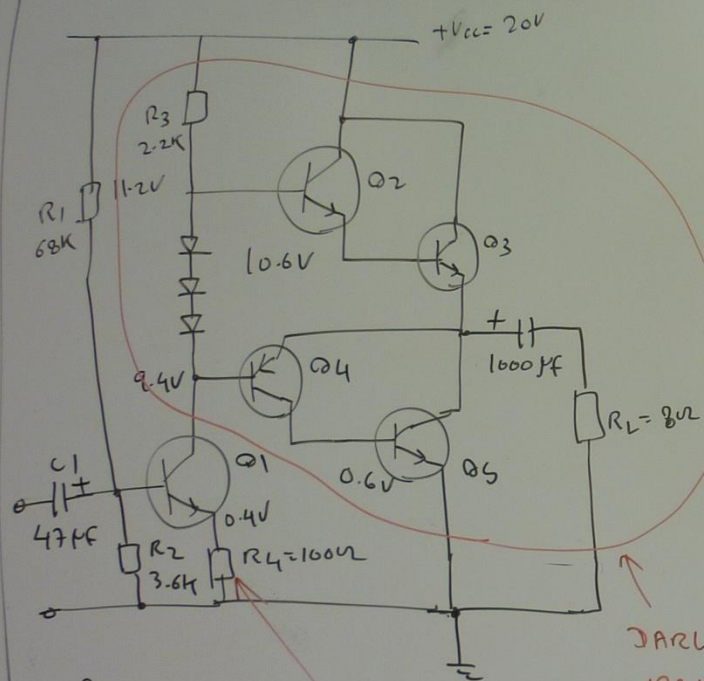

POWER AMPLIFIER WITH AMPLIFIER
DRIVER STAGE

DRIVER STAGE

DARLINGTON
PAIR
(TO INCREASE
CURRENT
GAIN)


POWER OUTPUT CALCULATION =

$$\frac{(V_{o \text{ p-p}})^2}{8 R_L}$$

Power Supplies PART (1)

MOST ELECTRONIC EQUIPMENTS REQUIRE SOME FORM OF DC POWER TO OPERATE.

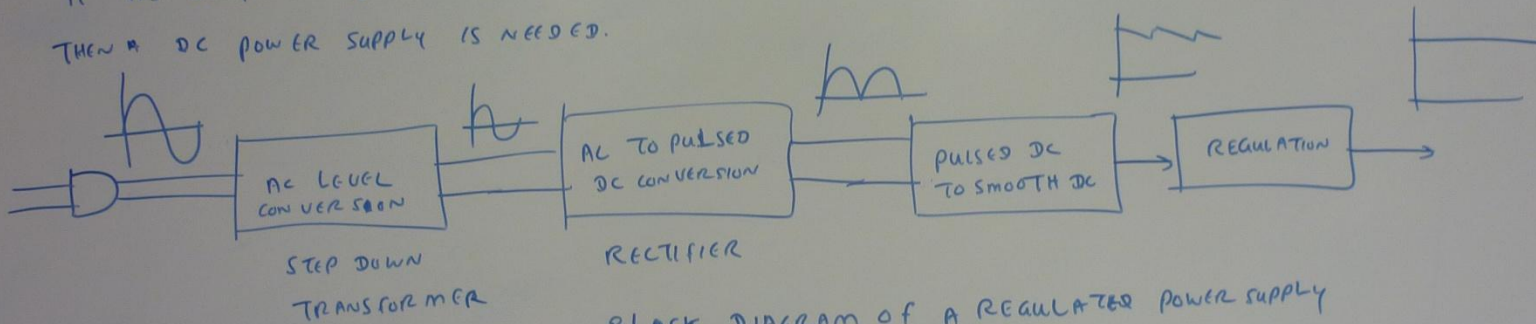IF THIS EQUIPMENT IS TO BE OPERATED FROM A STANDARD AC OUTLET THEN A DC POWER SUPPLY IS NEEDED.





BLOCK DIAGRAM OF A REGULATOR POWER SUPPLY



REGULATED power supply

- HALF WAVE RECTIFIER
- FULL WAVE RECTIFIER


HALF WAVE RECTIFIER

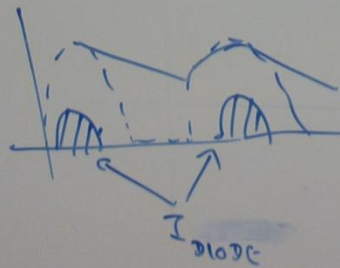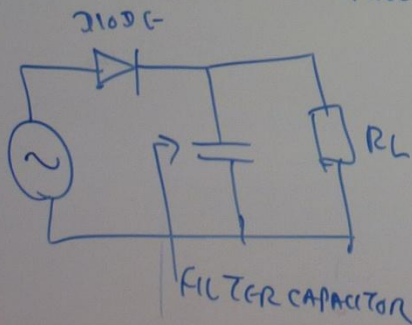

Fullwave Rectifier

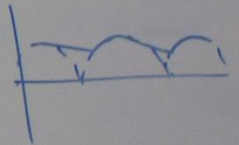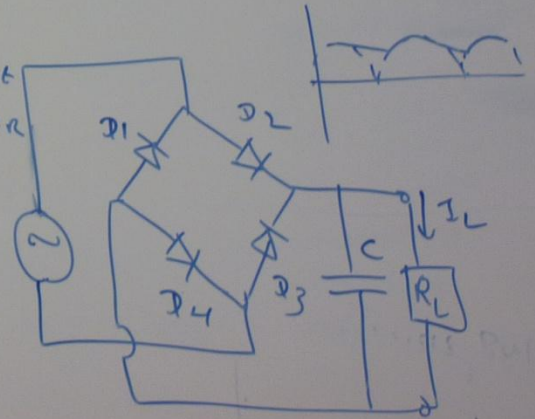

THE CENTRE TAPPED FULL WAVE RECTIFIER

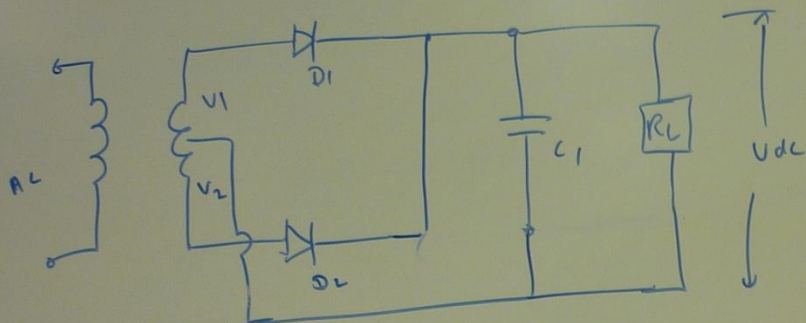

$$V_1 = V_2$$

$$V_{dc} = V_r \text{ for } R_L \text{ } C$$

V_{dc} = DC OUT PUT VOLTAGE

V_r = PEAK TO PEAK RIPPLE VOLTAGE

f_r = RIPPLE FREQUENCY

C = CAPACITANCE

R_L = LOAD SEEN BY CAPACITOR

P7) CALCULATE THE LOAD RESISTANCE AND CAPACITOR SIZE OF A FULL WAVE RECTIFIER THAT SUPPLIES A 40V DC WITH 2% RIPPLE VOLTAGE (PEAK TO PEAK) AT 250 mA TO A RESISTIVE LOAD. ASSUME THE RECTIFIER IS SUPPLIED WITH 50 Hz AC.

$$R_L = \frac{V_o}{I_L} = \frac{40}{250 \times 10^{-3}} = 160 \Omega$$

$$V_r = 2\% \times \text{DC VOLTAGE}$$

$$= \frac{2}{100} \times 40 = 0.8 \text{ V}$$

$$V_{dc} = V_r \text{ for } R_L \text{ } C$$

$$40 = 0.8 \times 100 \times 100 \times C$$

$$C = \frac{40}{0.8 \times 100 \times 100} = 3125 \times 10^{-6} \text{ F}$$

$$= 3125 \mu\text{F}$$

$$f_r = 2 f_{\text{supply}}$$

$$f_r = 2 \times 50$$

$$= 100 \text{ Hz}$$

CIRCUIT

1/2 wave
BRIDGE

C.T Full
wave

CIRCUIT	V_{dc}	RIPPLE FREQUENCY
$\frac{1}{2}$ wave	V_{max}	f_{supply}
BRIDGE	V_{max}	$2 f_{supply}$
C.T Full wave	V_{max}	$2 f_{supply}$


LOAD REGULATION

$$\% \text{ Load Regulation} = \frac{V_{dc}(\text{No Load}) - V_{dc}(\text{Full Load})}{V_{dc}(\text{Full Load})} \times 100$$

POWER SUPPLIES - PART (2)

THE PURPOSE OF VOLTAGE REGULATION IS TO MAINTAIN A CONSTANT VOLTAGE ACROSS A LOAD REGARDLESS OF ANY CHANGE IN LOAD CONDITION OR SUPPLY VOLTAGE.

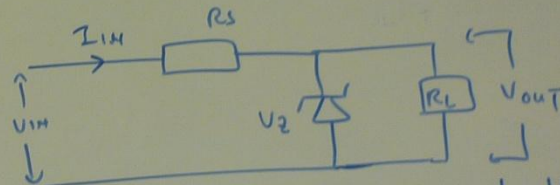THE BASIC REGULATING DEVICE IS ZENER DIODE.




THE OUTPUT VOLTAGE ACROSS LOAD L IS EQUAL TO ZENER VOLTAGE V_Z .

THE OUTPUT VOLTAGE IS KEPT CONSTANT DESPITE CHANGES IN V_{IN} AND I_L BECAUSE THE ZENER CURRENT VARIES TO CHANGE THE VOLTAGE ACROSS THE SERIES RESISTOR R_S TO COMPENSATE.

POWER SUPPLIES - PART (2)

THE PURPOSE OF VOLTAGE REGULATION IS TO MAINTAIN A CONSTANT VOLTAGE ACROSS A LOAD REGARDLESS OF ANY CHANGE IN LOAD CONDITION OR SUPPLY VOLTAGE.

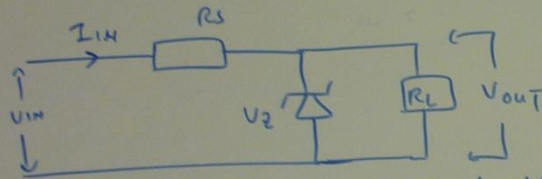
THE BASIC REGULATING DEVICE IS ZENER DIODE.



THE OUTPUT VOLTAGE ACROSS LOAD L IS EQUAL TO ZENER VOLTAGE V_Z .

THE OUTPUT VOLTAGE IS KEPT CONSTANT DESPITE CHANGES IN V_{IN} AND I_L BECAUSE THE ZENER CURRENT VARIES TO CHANGE THE VOLTAGE ACROSS THE SERIES RESISTOR R_S TO COMPENSATE.

SERIES TRANSISTOR REGULATOR

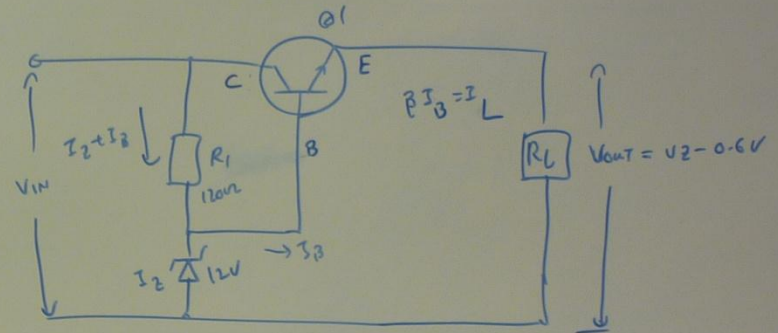


AN INCREASE IN THE LOAD CURRENT WILL CAUSE THE ZENER CURRENT TO REDUCE AS MORE BASE CURRENT IS REQUIRED BY THE TRANSISTOR.

IF THE INPUT VOLTAGE CHANGES, THE ZENER CURRENT WILL ALSO CHANGE, BUT THE ZENER VOLTAGE WILL REMAIN CONSTANT KEEPING THE OUTPUT CONSTANT.

THE INPUT VOLTAGE MUST BE HIGHER THAN REQUIRED OUTPUT VOLTAGE BY AT LEAST 2V.

SERIES TRANSISTOR REGULATOR

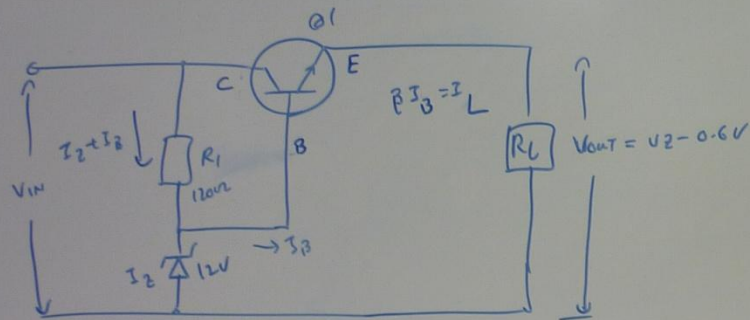


AN INCREASE IN THE LOAD CURRENT WILL CAUSE THE ZENER CURRENT TO REDUCE AS MORE BASE CURRENT IS REQUIRED BY THE TRANSISTOR.

IF THE INPUT VOLTAGE CHANGES, THE ZENER CURRENT WILL ALSO CHANGE, BUT THE ZENER VOLTAGE WILL REMAIN CONSTANT KEEPING THE OUTPUT CONSTANT.

THE INPUT VOLTAGE MUST BE HIGHER THAN REQUIRED OUTPUT VOLTAGE BY AT LEAST 2V.

REGULATOR WITH FEED BACK

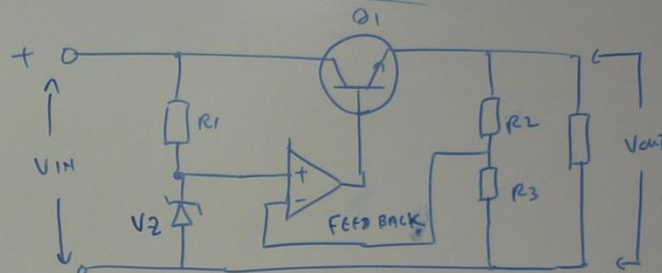



$$V_{OUT} = \left(\frac{R_2}{R_3} + 1 \right) \times V_{REF}$$

$$V_{REF} = V_Z$$

$$\text{POWER DISSIPATION } (P_d) = (V_{IN} - V_{OUT}) I_L$$


SERIES REGULATOR WITH CURRENT LIMITING

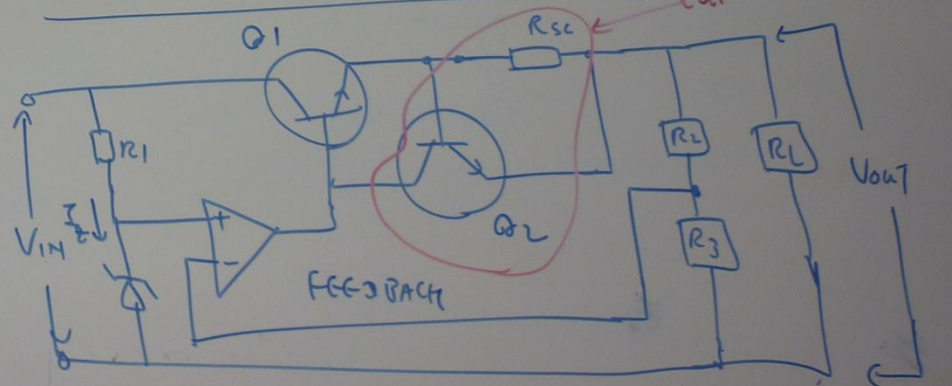

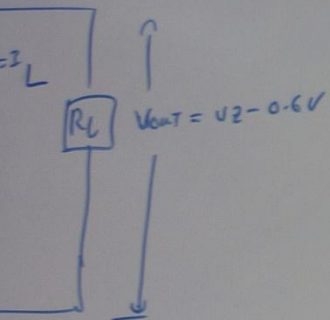

CURRENT WILL CAUSE
 AS MORE
 BY THE TRANSISTOR.
 ES, THE ZENER
 BUT THE ZENER
 CURRENT KEEPING
 HIGHER THAN
 BY AT LEAST 2V.

REGULATOR WITH FEED BACK

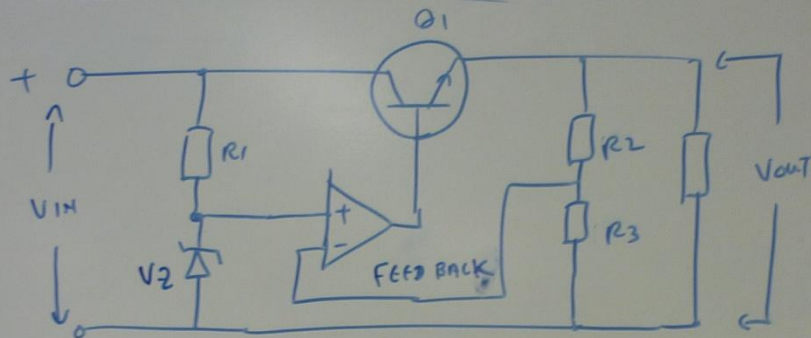


$$V_{out} = \left(\frac{R_2}{R_3} + 1 \right) \times V_{REF}$$

$$V_{REF} = V_z$$

$$\text{POWER DISSIPATION } (P_d) = (V_{in} - V_{out}) I_L$$


SERIES REGULATOR WITH CURRENT LIMITING

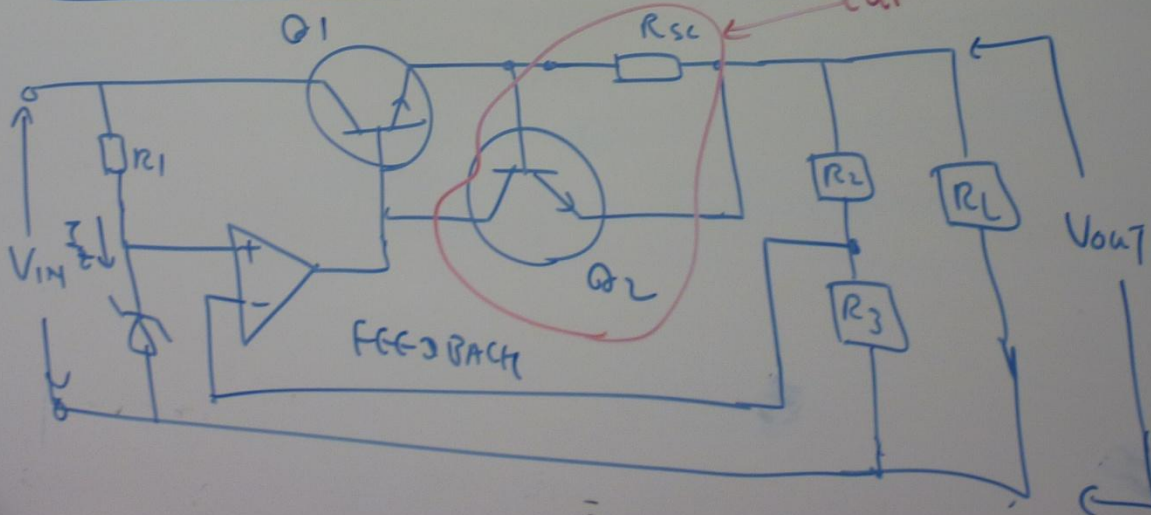

Ph

FOR THE GIVEN CIRCUIT, CALCULATE

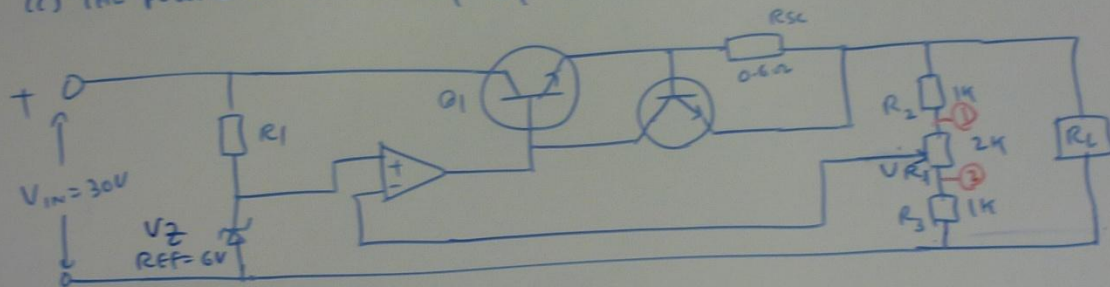- THE MAXIMUM AND MINIMUM OUTPUT VOLTAGES
- THE CURRENT THAT WILL FLOW IF THE OUTPUT IS SHORT CIRCUITED
- THE POWER DISSIPATED BY Q_1 IF THE OUTPUT IS SHORT CIRCUITED



$$V_{OUT} = \left(\frac{R_2}{R_3} + 1 \right) \times V_{REF}$$

$$V_{REF} = V_Z = 6V$$

V_{R1} AT POSITION ① $R_2 = 1k\Omega, R_3 = 3k\Omega$

$$V_{OUT} = \left(\frac{1}{3} + 1 \right) \times 6 = 8V$$

V_{R1} AT POSITION ② $R_2 = 3k\Omega, R_3 = 1k\Omega$

$$V_{OUT} = \left(\frac{3}{1} + 1 \right) \times 6 = 24V$$

$$I_{sc} = \frac{0.6}{R_{sc}}$$

$$= \frac{0.6}{0.6}$$

(MAXIMUM POWER)

$$P_d = (V_{IN} - 0)$$

$$= (30 - 0)$$

$$= 30W$$


THREE TERM
78XX,
LM317

ULATE

OUT VOLTAGES

IF THE OUT PUT IS SHORT CIRCUITED

IF THE OUT PUT IS SHORT CIRCUITED

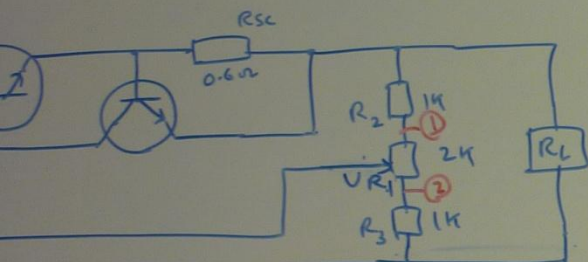

$\times V_{REF}$

$V_{REF} = V_Z = 6V$

$R_2 = 1k\Omega, R_3 = 3k\Omega$

$(+1) \times 6 = 8V$

$R_2 = 3k, R_3 = 1k$

$(+1) \times 6 = 24V$

$$I_{sc} = \frac{0.6}{R_{sc}}$$

$$= \frac{0.6}{0.6} = 1A$$

(MAXIMUM POWER DISSIPATION $\rightarrow$ OUT PUT SHORT CIRCUIT
 $V_{out} = 0, I_{sc} = I_L$)

$$P_d = (V_{in} - V_{out}) \times I_{sc}$$


$$= (30 - 0) \times 1$$

$$= 30W$$

THREE TERMINALS REGULATORS

78XX, 79XX, 78H05

LM317

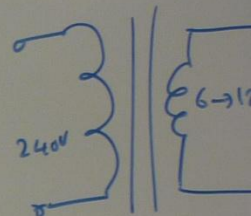

1 - IN PUT
2 - common
3 - OUT PUT

MAXIMUM P

IN PUT VO

OUT PUT

POWER DIS

$$I_{sc} = \frac{0.6}{R_{sc}}$$

$$= \frac{0.6}{0.6} = 1A$$

(MAXIMUM POWER DISSIPATION $\rightarrow$ OUT PUT SHORT CIRCUIT
 $V_{out} = 0, I_{sc} = I_L$)

$$P_d = (V_{in} - V_{out}) \times I_{sc}$$

$$= (30 - 0) \times 1$$


$$= 30W$$

THREE TERMINALS REGULATORS

78XX, 79XX, 78H05

LM317

5V POWER SUPPLY

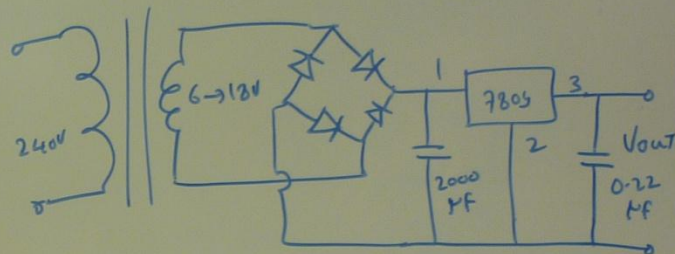

- 1 - INPUT
- 2 - common
- 3 - output

MAXIMUM RATINGS

INPUT VOLTAGE = 35V

OUTPUT CURRENT = 1A

POWER DISSIPATION - INTERNALLY LIMITED.

py CALCULATING
 SIZE OF A FULL
 40V DC WIT
 AT 250 mA
 RECTIFIER IS

$$R_L = -$$


$$V_r = 2$$

$$V_{dc} =$$

$$40 =$$

$$C =$$

POWER SUPPLY

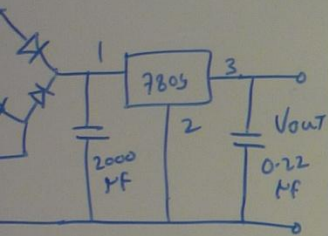

Q7) CALCULATE THE LOAD RESISTANCE AND CAPACITOR SIZE OF A FULL WAVE RECTIFIER THAT SUPPLIES A 40V DC WITH 2% RIPPLE VOLTAGE (PEAK TO PEAK) AT 250 mA TO A RESISTIVE LOAD. ASSUME THE RECTIFIER IS SUPPLIED WITH 50 Hz AC.

$$R_L = \frac{V_o}{I_L} = \frac{40}{250 \times 10^{-3}} = 160 \Omega$$

$$V_r = 2\% \times \text{DC VOLTAGE}$$

$$= \frac{2}{100} \times 40 = 0.8 \text{ V}$$

$$V_{DC} = V_r f_r R_L C$$

$$40 = 0.8 \times 100 \times 160 \times C$$

$$C = \frac{40}{0.8 \times 100 \times 160} = 3125 \times 10^{-6} \text{ F}$$

$$= 3125 \mu\text{F}$$

CIRCUIT	V_{DC}	RIPPLE FREQUENCY
$\frac{1}{2}$ WAVE	V_{max}	f_{supply}
BRIDGE	V_{max}	$2 f_{\text{supply}}$
C.T FULL WAVE	V_{max}	$2 f_{\text{supply}}$

LOAD REGULATION


$$\% \text{ LOAD REGULATION} = \frac{V_{DC}(\text{NO LOAD}) - V_{DC}(\text{FULL LOAD})}{V_{DC}(\text{FULL LOAD})} \times 100$$

$$f_r = 2 f_{\text{supply}}$$

$$f_r = 2 \times 50 = 100 \text{ Hz}$$

POWER AMPLIFIER CIRCUIT CALCULATIONS

pb ①

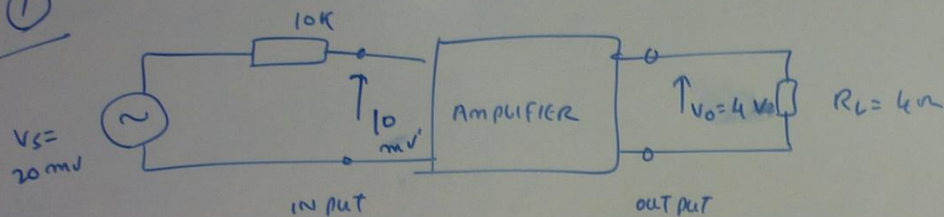

FIND (a) VOLTAGE GAIN (b) INPUT CURRENT

(c) OUTPUT CURRENT (d) CURRENT GAIN.

(e) OUTPUT POWER (f) POWER GAIN

(g) TRAN RESISTANCE (h) TRANS CONDUCTANCE.

$$(a) \text{ VOLTAGE GAIN (AV)} = \frac{V_o}{V_{in}} = \frac{4}{10 \times 10^{-3}} = \frac{4000}{10} = 400$$

$$(b) \text{ VOLTAGE DROP ACROSS } 10 \text{ k}\Omega \text{ RESISTOR} = 20 - 10 = 10 \text{ mV}$$

$$I = \frac{10 \text{ mV}}{10 \text{ k}} = \frac{10 \times 10^{-3}}{10 \times 10^3} = 1 \times 10^{-6} = 1 \mu\text{A}$$

$$(c) I_{out} = \frac{4 \text{ V}}{4 \Omega} = 1 \text{ A}$$

$$(d) \text{ CURRENT GAIN} = \frac{I_{out}}{I_{in}} = \frac{1}{1 \mu\text{A}} = \frac{1}{1 \times 10^{-6}} = \frac{10^6}{1} = 10^6$$

$$(e) P_{out} = V_{out} \times I_{out} = 4 \times 1 = 4 \text{ W}$$

$$(f) P_{in} = V_{in} \times I_{in} = 10 \times 10^{-3} \times 1 \times 10^{-6} = 10 \times 10^{-9} \text{ W}$$

$$P_{out} = 4 \text{ W}$$

$$(c) I_{out} = \frac{4V}{4\Omega} = 1A$$

$$(d) \text{ CURRENT GAIN} = \frac{I_{out}}{I_{in}} = \frac{1}{1 \times 10^{-6}} = 10^6$$

$$(e) P_{out} = V_{out} \times I_{out} = 4 \times 1 = 4W$$

$$(f) P_{in} = V_{in} \times I_{in} = 10 \times 10^{-3} \times 1 \times 10^{-6} = 10 \times 10^{-9} W$$

$$P_{out} = 4W$$


$$A_p = \frac{P_{out}}{P_{in}} = \frac{4}{10 \times 10^{-9}} = 4 \times 10^8$$


$$= 0.4 \times 10^9$$

$$= 4 \times 10^8$$

$$(g) \text{ TRAN RESISTANCE} = \frac{V_{out}}{I_{in}} = \frac{4}{1 \times 10^{-6}} = 4 \times 10^6 \Omega = 4M\Omega$$
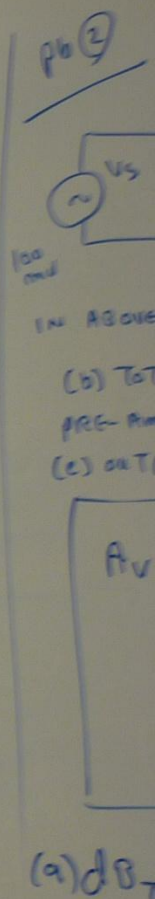
$$(h) \text{ TRAN CONDUCTANCE} = \frac{I_{out}}{V_{in}} = \frac{1}{10 \times 10^{-3}} = \frac{1}{10} = 0.1 S$$



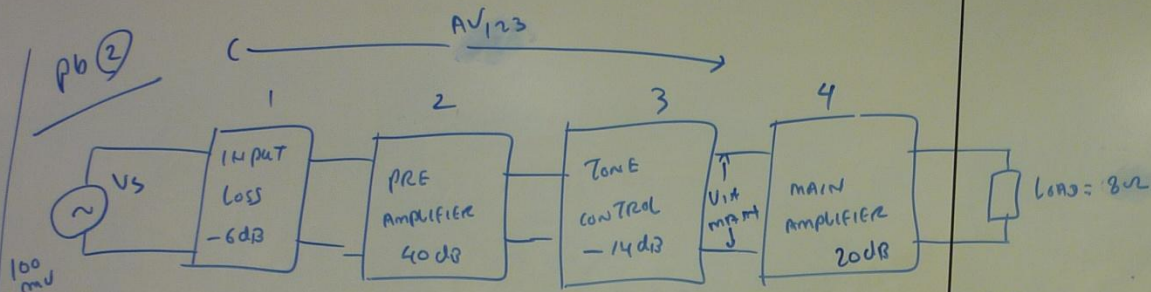

IN ABOVE CIRCUIT . FIND (a) TOTAL VOLTAGE GAIN IN dB
 (b) TOTAL VOLTAGE GAIN IN DIRECT RATIO (c) INPUT VOLTAGE OF PRE-AMPLIFIER (d) INPUT VOLTAGE OF MAIN AMPLIFIER
 (e) OUTPUT VOLTAGE OF AMPLIFIER

$$A_V(dB) = 20 \log_{10} \frac{V_2}{V_1}$$

$$\frac{V_2}{V_1} = 10^{\frac{A_V(dB)}{20}}$$

$$A_V = 10^{\frac{A_V(dB)}{20}}$$

$$dB_T = dB_1 + dB_2 + dB_3$$

$$A_{VT} = A_1 \times A_2 \times A_3$$

$$(a) dB_T = dB_1 + dB_2 + dB_3 + dB_4$$

$$= (-6) + (40) + (-14) + 20 = 40$$

$$(b) A_{VT} = A_{V1} \times A_{V2} \times A_{V3} \times A_{V4}$$

$$= 10^{\frac{A_{V1}(dB)}{20}} \times 10^{\frac{A_{V2}(dB)}{20}} \times 10^{\frac{A_{V3}(dB)}{20}} \times 10^{\frac{A_{V4}(dB)}{20}}$$

$$= 10^{\frac{-6}{20}} \times 10^{\frac{40}{20}} \times 10^{\frac{-14}{20}} \times 10^{\frac{20}{20}}$$

$$= 10^{-0.3} \times 10^2 \times 10^{-0.7} \times 10^1$$


$$= 10^{(-0.3) + 2 + (-0.7) + 1}$$

$$= 10^2 = 100$$

$$(1) A_{v123} = 10^{\frac{A_{V1}(dB)}{20}} \times 10^{\frac{A_{V2}(dB)}{20}} \times 10^{\frac{A_{V3}(dB)}{20}}$$

$$= 10^{-0.3} \times 10^2 \times 10^{-0.7}$$
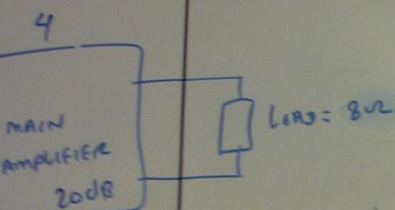
$$= 10^{(-0.3) + 2 + (-0.7)} = 10^1 = 10$$



dB
STAGE OF
FILTER

dB₃

AV₃

$$(b) A_{VT} = A_{V1} \times A_{V2} \times A_{V3} \times A_{V4}$$

$$= 10^{\frac{AV_1(dB)}{20}} \times 10^{\frac{AV_2(dB)}{20}} \times 10^{\frac{AV_3(dB)}{20}} \times 10^{\frac{AV_4(dB)}{20}}$$

$$= 10^{\frac{-6}{20}} \times 10^{\frac{40}{20}} \times 10^{\frac{-14}{20}} \times 10^{\frac{20}{20}}$$

$$= 10^{-0.3} \times 10^2 \times 10^{-0.7} \times 10^1$$

$$= 10^{(-0.3+2+(-0.7)+1)}$$

$$= 10^2 = 100$$

$$(c) A_{V_{123}} = 10^{\frac{AV_1(dB)}{20}} \times 10^{\frac{AV_2(dB)}{20}} \times 10^{\frac{AV_3(dB)}{20}}$$

$$= 10^{-0.3} \times 10^2 \times 10^{-0.7}$$

$$= 10^{(-0.3+2+(-0.7))} = 10^1 = 10$$

$$(d) V_{IN(MAIN)} = V_S \times A_{V_{123}}$$

$$= (100 \times 10^{-3}) \times 10$$

$$= 100 \times 10^{-3} \times 10$$

$$= 1V$$

$$(e) V_{OUT} = V_{IN(MAIN)} \times A_{V4}$$


$$= 1 \times 10^{\frac{AV_4(dB)}{20}}$$

$$= 1 \times 10^{\frac{20}{20}}$$



$$= 1 \times 10^1$$

$$= 10V$$

Pb(3)
FOR THE

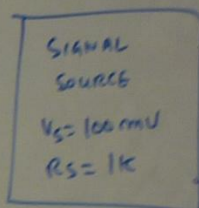

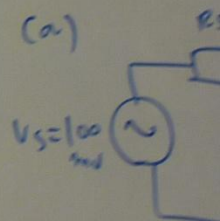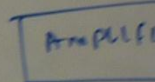- (a) DRAW THE EQ
(b) DETERMINE
(c) DETERMINE
(d) DETERMINE
TO ACHIEVE




$$\begin{aligned}
 (d) V_{IN(MAIN)} &= V_S \times A_{V_{123}} \\
 &= (100 \times 10^{-3}) \times 10 \\
 &= 100 \times 10^{-3} \times 10 \\
 &= 1V
 \end{aligned}$$



$$\begin{aligned}
 (e) V_{OUT} &= V_{IN(MAIN)} \times A_{V4} \\
 &= 1 \times 10^{\frac{20}{20}} \\
 &= 1 \times 10^1 \\
 &= 10V
 \end{aligned}$$

pb(3)

FOR THE AMPLIFIER CONNECTION BELOW

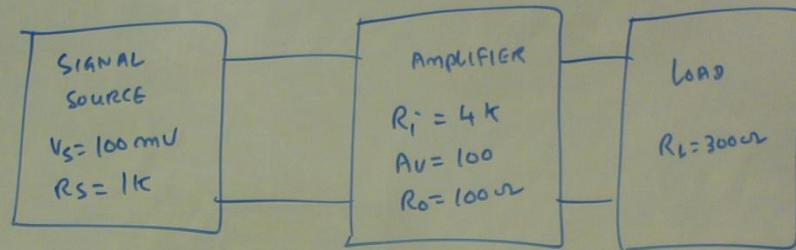

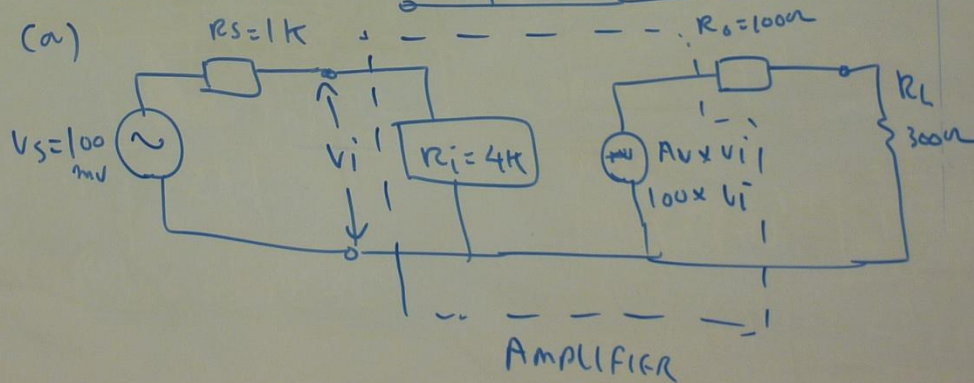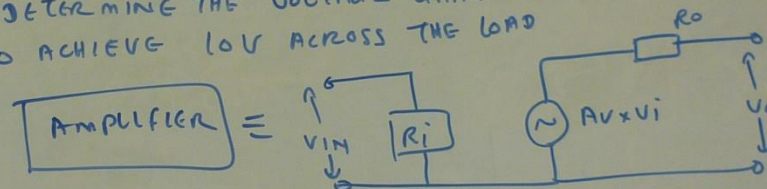- DRAW THE EQUIVALENT CIRCUIT
- DETERMINE THE INPUT VOLTAGE OF AMPLIFIER
- DETERMINE THE OUTPUT VOLTAGE OF AMPLIFIER
- DETERMINE THE VOLTAGE GAIN OF AMPLIFIER TO ACHIEVE 10V ACROSS THE LOAD



$$(b) V_i = V_S \times \frac{R_i}{R_S + R_i}$$


$$(c) V_{OUT} = A_V \times V_i$$

$$\begin{aligned}
 (d) V_{OUT} &= 10V \\
 V_{IN} &= 80mV
 \end{aligned}$$



$$A_V = \frac{V_{OUT}}{V_{IN}}$$

Pb(3)

FOR THE AMPLIFIER CONNECTION BELOW

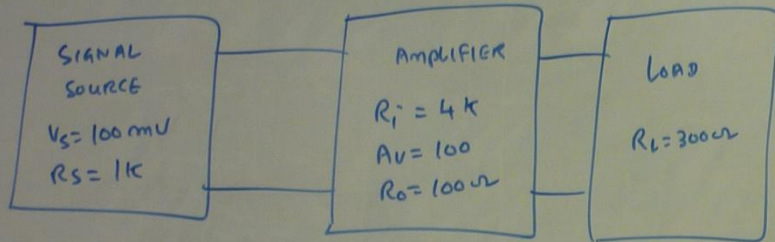

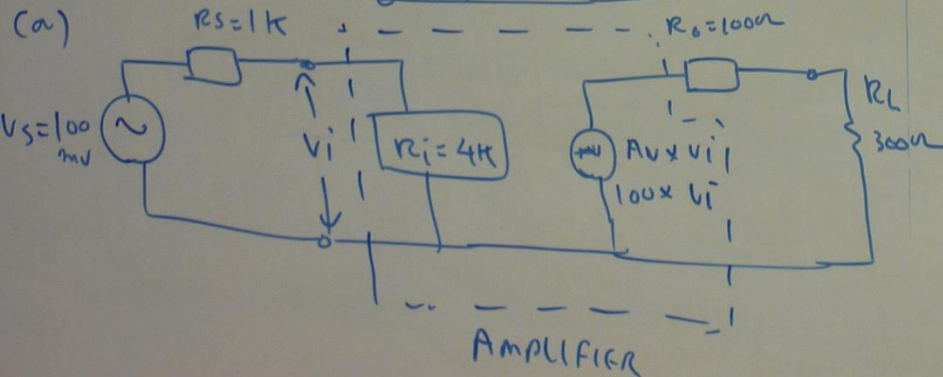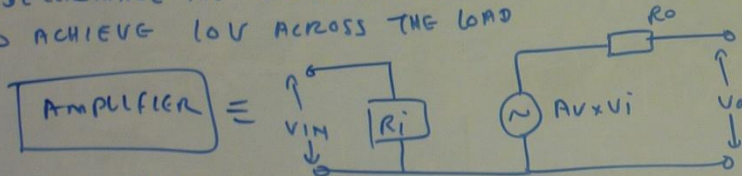- (a) DRAW THE EQUIVALENT CIRCUIT
 (b) DETERMINE THE INPUT VOLTAGE OF AMPLIFIER
 (c) DETERMINE THE OUTPUT VOLTAGE OF AMPLIFIER
 (d) DETERMINE THE VOLTAGE GAIN OF AMPLIFIER
 TO ACHIEVE 10V ACROSS THE LOAD



$$(b) V_i = V_s \times \frac{R_i}{R_s + R_i} = 100 \times \frac{4}{1+4} = \frac{100 \times 4}{5} = 80 \text{ mV}$$


$$(c) V_{out} = A_v \times V_i = 100 \times 80 \text{ mV} = 100 \times 80 \times 10^{-3} = 8 \text{ V}$$

$$(d) V_{out} = 10 \text{ V}$$

$$V_{in} = 80 \text{ mV}$$


$$A_v = \frac{V_{out}}{V_{in}} = \frac{10}{80 \times 10^{-3}} = \frac{1000}{80} = 12.5$$

6. AMPLIFIER CONNECTION BELOW

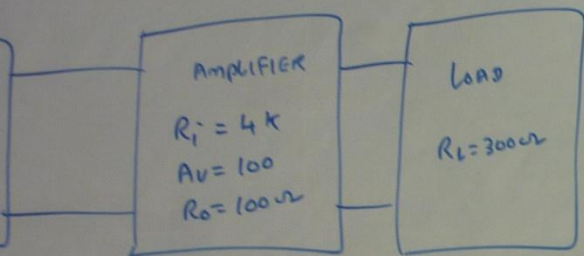

EQUIVALENT CIRCUIT

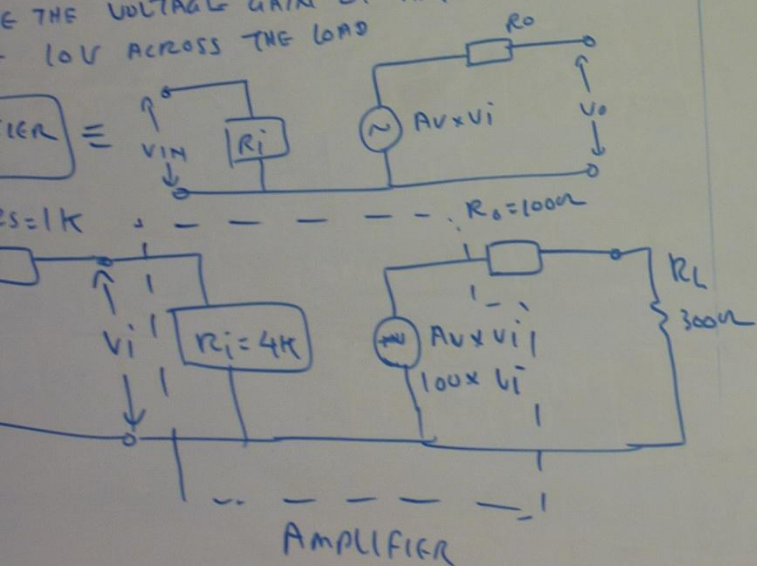THE INPUT VOLTAGE OF AMPLIFIER
THE OUTPUT VOLTAGE OF AMPLIFIER
THE VOLTAGE GAIN OF AMPLIFIER
10V ACROSS THE LOAD



$$(b) V_i = V_s \times \frac{R_i}{R_s + R_i} = 100 \times \frac{4}{1 + 4} = \frac{100 \times 4}{5} = 80 \text{ mV}$$


$$(c) V_{out} = A_v \times V_i = 100 \times 80 \text{ mV} = 100 \times 80 \times 10^{-3} = 8 \text{ V}$$

$$(d) V_{out} = 10 \text{ V}$$

$$V_{in} = 80 \text{ mV}$$


$$A_v = \frac{V_{out}}{V_{in}} = \frac{10}{80 \times 10^{-3}} = \frac{1000}{80} = 12.5$$

Pb 4

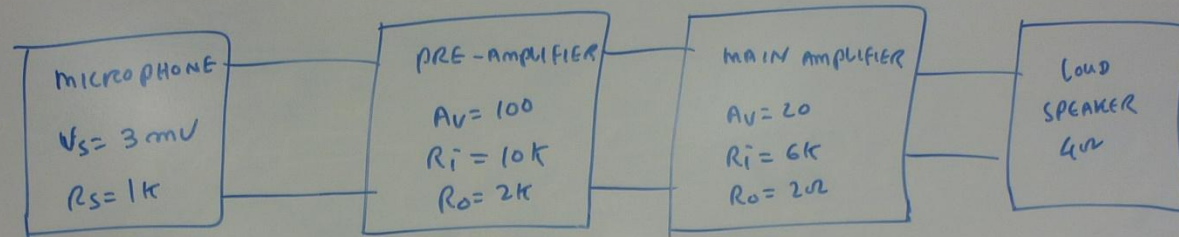

THE ABOVE DIAGRAM IS A MULTI STAGE AMPLIFIER

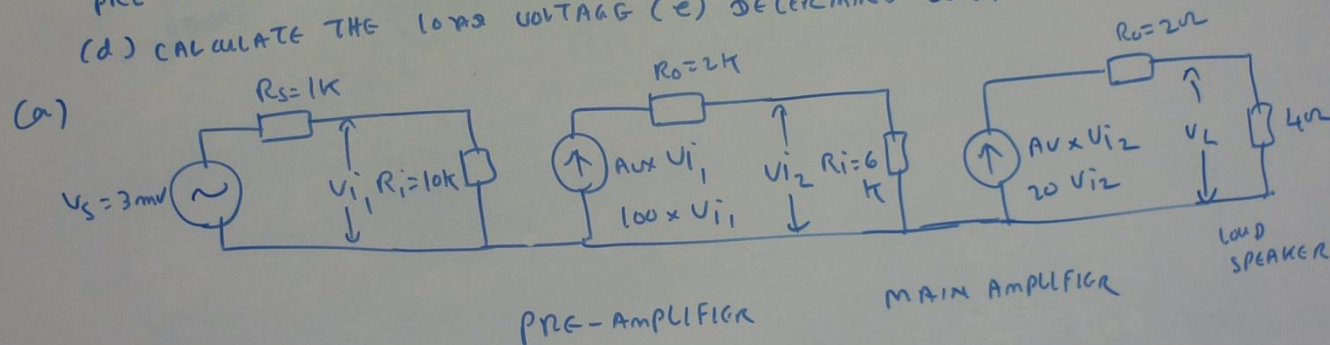- (a) DRAW AN EQUIVALENT CIRCUIT (b) CALCULATE THE INPUT VOLTAGE OF PRE-AMPLIFIER (c) CALCULATE THE INPUT VOLTAGE OF MAIN AMPLIFIER (d) CALCULATE THE LOAD VOLTAGE (e) DETERMINE OUTPUT POWER.




(b) $V_{i1} = ?$

$$V_{i1} = V_s \times \frac{R_i}{R_s + R_i} = 3\text{mV} \times \frac{10\text{k}}{(1+10)\text{k}} = 2.72\text{mV}$$

(c) $A_v \times V_{i1} = 2.72 \times 100 = 272\text{mV}$

LOAD
SPEAKER
4Ω

OF
R
2Ω

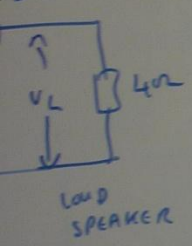

0.72 mV

$$V_{i2} = A_V \times V_{i1} \times \frac{R_i}{R_i + R_o}$$

$$= 272 \times \frac{6}{6+2}$$

$$= 204 \text{ mV}$$

$$(d) A_V \times V_{i2} = 20 \times 204 \text{ mV}$$

$$= 20 \times 0.204$$

$$= 4.08 \text{ V}$$

$$V_L = (A_V \times V_{i2}) \times \frac{R_L}{R_o + R_L}$$

$$= 4.08 \times \frac{4}{4+2}$$

$$= \frac{4.08 \times 4}{6} = \frac{16.32}{6}$$

$$= 2.7 \text{ V}$$

$$P_{out} = \frac{V_{out}^2}{R_L}$$

$$= \frac{(2.7)^2}{4}$$

$$= \frac{2.7 \times 2.7}{4}$$

$$= 1.8225 \text{ W}$$

MID BAND

pb 5

PLOT THE FREQUENCY RESPONSE FROM AN AMPLIFIER AND INDICATE

$$\text{VOLTAGE GAIN } A_V = \frac{V_o}{V_i}$$

$$\text{POWER AT LOAD} = \frac{V_o^2}{R}$$

FREQUENCY (Hz)	V _i (mV)	V _o (V)	VOLTAGE
10	100	1	100 × 10 ⁻³
20	100	1.96	1.96 × 10 ⁻³
40	100	3.71	3.71 × 10 ⁻³
100	100	7.07	7.07 × 10 ⁻³
200	100	8.94	8.94 × 10 ⁻³
400	100	9.28	9.28 × 10 ⁻³
1k	100	9.95	9.95 × 10 ⁻³
2k	100	10	10 × 10 ⁻³
4k	100	10	10 × 10 ⁻³
10k	100	9.95	9.95 × 10 ⁻³
20k	100	9.81	9.81 × 10 ⁻³

$$P_T = \frac{V_{out}^2}{R_L}$$

$$= \frac{(2.7)^2}{4}$$

$$= \frac{2.7 \times 2.7}{4}$$

$$= 1.8225 \text{ W}$$

pb 5 Plot the frequency response of the following data obtained from an amplifier and indicate mid band and half power points.

$$\text{VOLTAGE GAIN } A_V = \frac{V_o}{V_i}$$

$$\text{VOLTAGE GAIN (dB)} = 20 \log_{10} \frac{V_o}{V_i}$$

$$\text{POWER AT LOAD} = \frac{V_o^2}{R}$$

$$\text{POWER GAIN (dB)} = 10 \log \frac{\text{POWER AT LOAD}}{\text{BASE POWER}}$$

FREQUENCY (Hz)	V _i (mV)	V _o (V)	VOLTAGE GAIN	VOLTAGE GAIN (dB)	LOAD POWER (mW)	POWER GAIN (dB)
					10mW	(mW = 0dB)
10	100	1	$\frac{1}{100 \times 10^{-3}} = 10$	$20 \log_{10} \frac{1}{100 \times 10^{-3}} = 20$	$\frac{1^2}{10} = 0.1 \text{ W}$	$10 \log \frac{0.1}{1 \times 10^{-3}} = 10$
20	100	1.96	$\frac{1.96}{100 \times 10^{-3}} = 19.6$	$20 \log_{10} \frac{1.96}{100 \times 10^{-3}} = 25.8$	$\frac{1.96^2}{10} = 0.384 \text{ W}$	$10 \log \frac{0.384}{1 \times 10^{-3}} = 15.3$
40	100	3.71	37.1	31.3	1.376	31.3
100	100	7.07	70.7	36.9	4.99	36.9
200	100	8.94	89.4	39	7.94	39.02
400	100	9.28	92.8	39.3	8.61	39.35
1k	100	9.95	99.5	39.5	9.9	39.45
2k	100	10	100	40	10	40
4k	100	10	100	40	10	40
10k	100	9.95	99.5	39.9	9.9	39.95
20k	100	9.81	98.1	39.8	9.62	39.83

MID BAND

HALF

MID

$$\frac{V_{out}^2}{R_L}$$

$$\frac{(2.7)^2}{4}$$

$$\frac{2.7 \times 2.7}{4}$$

$$1.8225 W$$

pb 5

PLOT THE FREQUENCY RESPONSE OF THE FOLLOWING DATA OBTAINED FROM AN AMPLIFIER AND INDICATE MID BAND AND HALF POWER POINT.

$$VOLTAGE GAIN A_V = \frac{V_o}{V_i}$$

$$VOLTAGE GAIN (dB) = 20 \log \frac{V_o}{V_i}$$

$$POWER AT LOAD = \frac{V_o^2}{R}$$

$$POWER GAIN (dB) = 10 \log \frac{POWER AT LOAD}{BASE POWER}$$

FREQUENCY (Hz)	V _i (mV)	V _o (V)	VOLTAGE GAIN	VOLTAGE GAIN (dB)	LOAD POWER (W)	POWER GAIN (dB)
10	100	1	$\frac{1}{100 \times 10^{-3}} = 10$	$20 \log \frac{1}{100 \times 10^{-3}} = 20$	$\frac{1^2}{10} = 0.1 W$	$10 \log \frac{0.1}{1 \times 10^{-3}} = 10$
20	100	1.96	$\frac{1.96}{100 \times 10^{-3}} = 19.6$	$20 \log \frac{1.96}{100 \times 10^{-3}} = 25.8$	$\frac{1.96^2}{10} = 0.384 W$	$10 \log \frac{0.384}{1 \times 10^{-3}} = 15.3$
40	100	3.71	37.1	31.3	1.376	31.3
100	100	7.07	70.7	36.9	4.99	36.9
200	100	8.94	89.4	39	7.94	39.02
400	100	9.28	92.8	39.3	8.61	39.35
1k	100	9.95	99.5	39.5	9.9	39.95
2k	100	10	100	40	10	40
4k	100	10	100	40	10	40
10k	100	9.95	99.5	39.9	9.9	39.95
20k	100	9.81	98.1	39.8	9.62	39.85

MID BAND

HALF POWER POINT

MID BAND

FREQUENCY

40k

100k

200k

400k

1M

$\text{GAIN (dB)} = 20 \log \left(\frac{V_o}{V_i} \right)$
 $\text{mW} = 0.43$
 $\frac{0.1}{1 \times 10^3} = 10$
 $\frac{0.384}{1 \times 10^3} = 15.3$

31.3
36.9

39.02

39.35

39.95

40
40

39.95


39.83

FREQUENCY (Hz)	V_i (mV)	V_o (V)	VOLTAGE GAIN	VOLTAGE GAIN (dB)	LOAD POWER POWER	POWER GAIN (dB)
40k	100	9.28	92.8	39.8	8.61	39.35
100k	100	7.07	70.7	36.9	4.99	36.9
200k	100	4.47	44.7	33	1.99	32.9
400k	100	2.43	24.3	27.7	0.59	27.7
1M	100	1	10	20	0.1	10

HALF POWER
POINT (2)

HALF POWER
POINT (1)

MID BAND

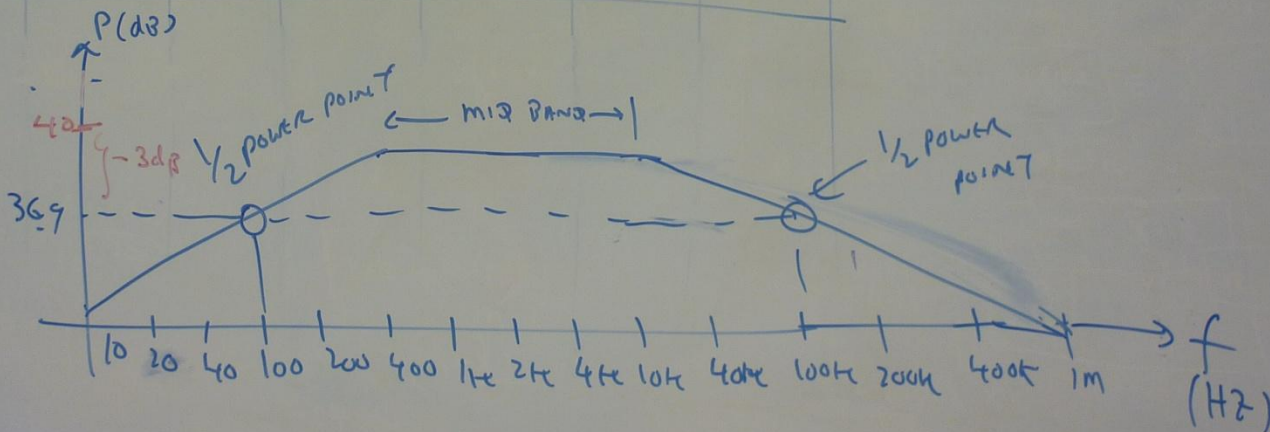

pb 6

AN
AN
Em
FR

pn 7

pb ⑥

AN AUDIO SIGNAL GENERATOR WHOSE SOURCE RESISTANCE IS $600\ \Omega$ IS CONNECTED TO AN AMPLIFIER WHICH HAS A $3\ \text{k}\Omega$ INPUT RESISTANCE. A $1\ \mu\text{F}$ COUPLING CAPACITOR IS EMPLOYED THE SIGNAL SOURCE AND THE AMPLIFIER. DETERMINE THE LOWER HALF POWER FREQUENCY.

$$f_{L-3dB} = \frac{1}{2\pi (R_S + R_i) C}$$

(frequency)

R_S = SOURCE RESISTANCE, R_i = INPUT RESISTANCE OF AMPLIFIER, C = COUPLING CAPACITOR

$$f_{L-3dB} = \frac{1}{2 \times 3.1416 \times (600 + 3 \times 10^3) \times 1 \times 10^{-6}} = 44.2\ \text{Hz}$$

pb ⑦



AN AMPLIFIER HAS AN INPUT IMPEDANCE $10\ \text{k}\Omega$. CALCULATE THE VALUE OF COUPLING CAPACITOR REQUIRES FOR $40\ \text{Hz}$ LOWER -3dB FREQUENCY. SOURCE RESISTANCE = $600\ \Omega$

$$40 = \frac{1}{2 \times 3.1416 (600 + 1000) C}$$

$$C = \frac{1}{2 \times 3.1416 \times 40 \times 1600} = 2.486\ \mu\text{F}$$

f
(Hz)

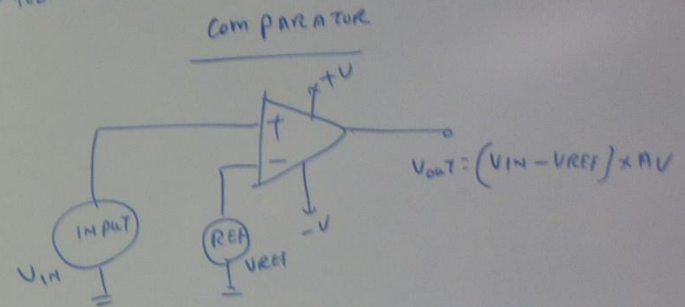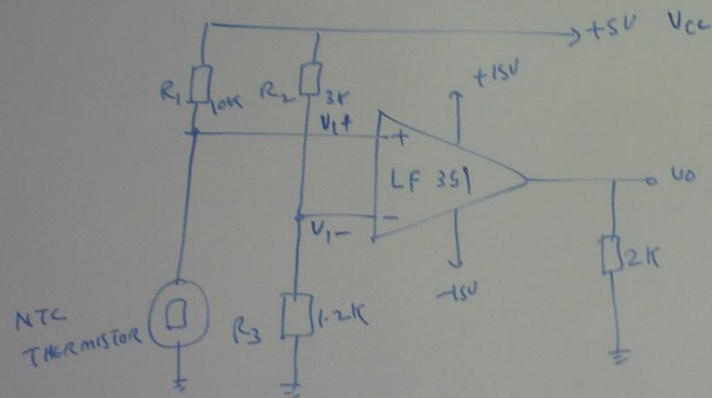Pb → AN NTC (NEGATIVE TEMPERATURE COEFFICIENT) THERMISTOR IS EMPLOYED TO CONTROL THE TEMPERATURE AS SHOWN BELOW



$$R_t = R_0(1 + \alpha \Delta t)$$

TEMPERATURE (°C)	20	25	30	35	40	45	50	55	60	65	70	75	80
R (kΩ) (R _{NTC})	9.5	8.2	6.8	5.7	4.9	4.3	3.7	3.3	3	2.7	2.5	2.3	2.2
V ₁₊	2.436	2.252	2.02	1.81	1.64	1.5	1.35	1.24	1.15	1.06	1	0.93	0.9

DRAW V₁₊ GRAPH

$$V_{I(+)} = V_{CC} \times \frac{R_{NTC}}{R_1 + R_{NTC}}$$


$$V_{I(-)} = V_{CC} \times \frac{R_3}{R_2 + R_3}$$

IF $R_{NTC} = 9.5 k\Omega$
 $R_1 = 10 k$

$$V_{I(+)} = \frac{9.5}{10 + 9.5} \times 5 = 2.435$$

IF $R_{NTC} = 8.2 k\Omega$
 $R_1 = 10 k$
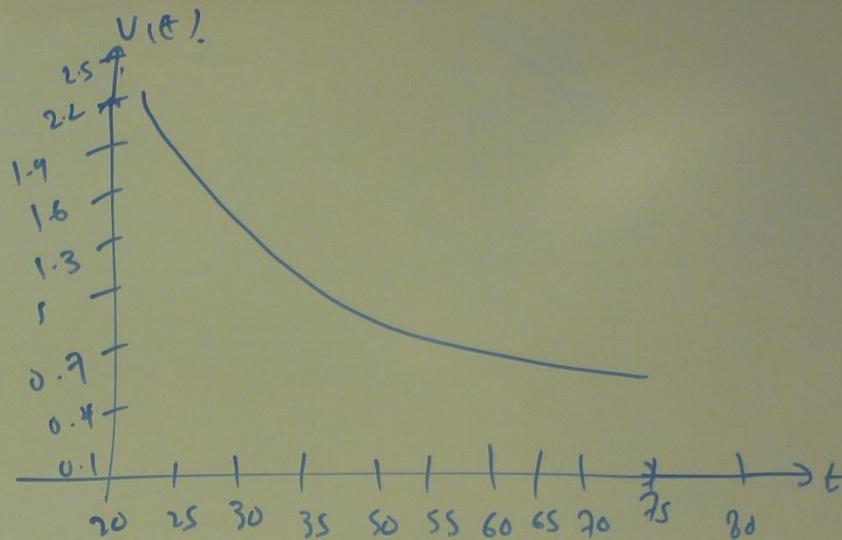
$$V_{I(+)} = \frac{8.2}{10 + 8.2} \times 5 = 2.252 \Omega$$



IN ABOVE PROBLEM

(i) CALCULATE INPUT VOLTAGE

$V_{I(-)}$

(ii) DETERMINE THE TRANSITION TEMPERATURE

(iii) DETERMINE THE VALUE OF R_3 FOR $70^\circ C$ TRANSITION TEMPERATURE

(iv) SHOW A RELAY INTERFACE CIRCUIT TO THE OUTPUT TERMINAL TO OPERATE A 240V HEATING ELEMENT.

$$V_{i(+)} = V_{cc} \times \frac{R_{NTC}}{R_1 + R_{NTC}}$$


$$V_{i(-)} = V_{cc} \times \frac{R_3}{R_2 + R_3}$$

IF $R_{NTC} = 9.5 k\Omega$
 $R_1 = 10 k$

$$V_{i(+)} = \frac{9.5}{10 + 9.5} \times 5 = 2.435$$

IF $R_{NTC} = 8.2 k\Omega$
 $R_1 = 10 k$
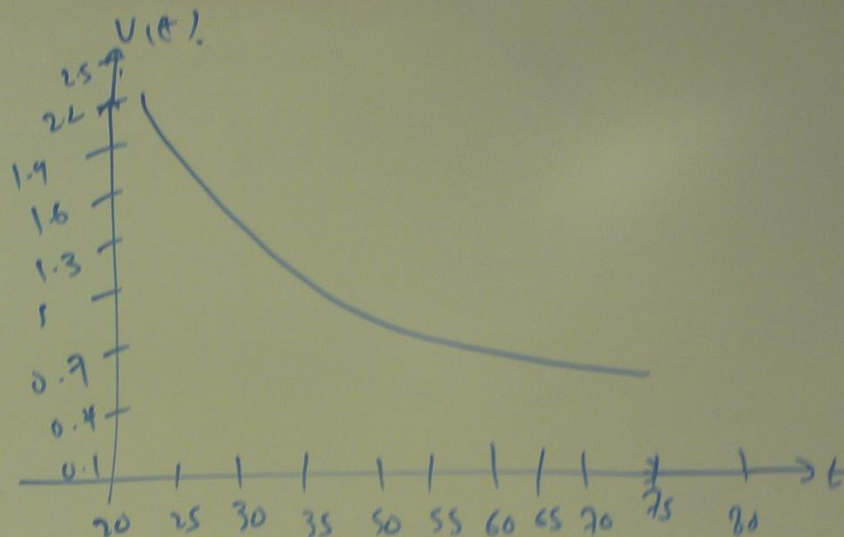
$$V_{i(+)} = \frac{8.2}{10 + 8.2} \times 5 = 2.252$$



IN ABOVE PROBLEM

(i) CALCULATE INVERTING INPUT VOLTAGE

$$V_{i(-)}$$

(ii) DETERMINE THE TRANSITION TEMPERATURE

(iii) DETERMINE THE VALUE OF R_3 FOR $70^\circ C$ TRANSITION TEMPERATURE

(iv) SHOW A RELAY INTERFACE CIRCUIT TO THE OUTPUT TERMINAL TO OPERATE A 240V HEATING ELEMENT.

$$(k) \quad V_1(-) = V_{cc} \times \frac{R_3}{R_3 + R_2}$$

$$(i) \quad = 5 \times \frac{1.2}{1.2 + 3}$$

$$= 1.043 \text{ V}$$

$$\text{AT } 50^\circ\text{C}, \quad V_1(+) < V_1(-)$$

1.35V 1.43V

(ii) 50°C IS TRANSITION TEMPERATURE

FOR 70°C TEMPERATURE TO
BECOME TRANSITION TEMPERATURE

$V_1(-)$ MUST BE AT LEAST 1V

$$V_1(-) = V_{cc} \times \frac{R_3}{R_2 + R_3}$$


$$1 = 5 \times \frac{R_3}{R_3 + 3}$$

$$1 = \frac{5R_3}{R_3 + 3}$$



$$R_3 + 3 = 5R_3$$

$$4R_3 = 3$$

$$R_3 = 0.75 \text{ k}\Omega$$

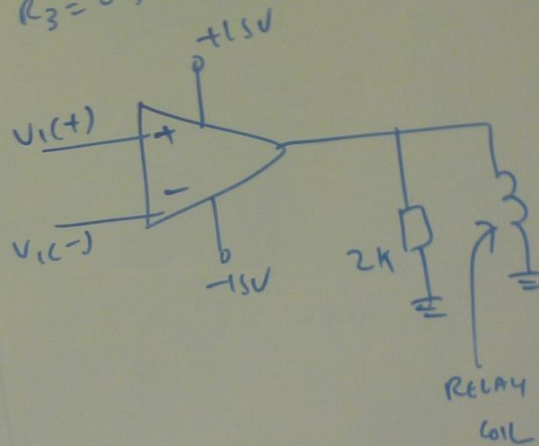

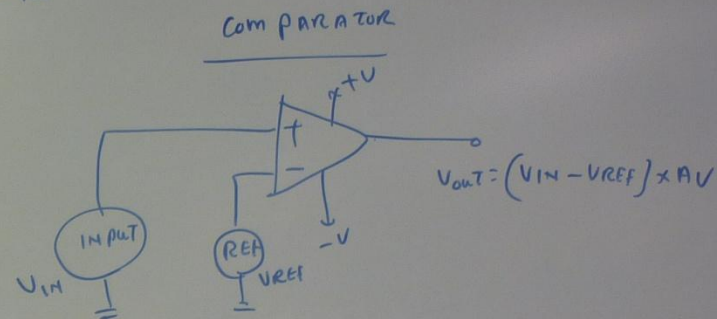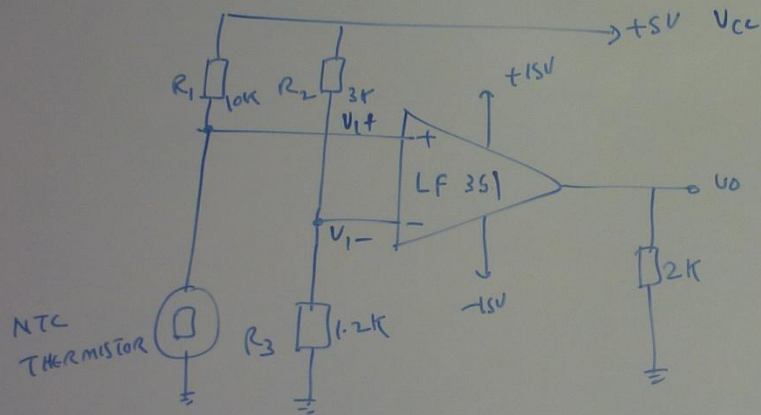pb AN NTC (NEGATIVE TEMPERATURE COEFFICIENT) THERMISTOR IS EMPLOYED TO CONTROL THE TEMPERATURE AS SHOWN BELOW



$$R_t = R_0(1 + \alpha \Delta T)$$

TEMPERATURE (°C)	20	25	30	35	40	45	50	55	60	65	70	75	80
R (kΩ) (R _{NTC})	9.5	8.2	6.8	5.7	4.9	4.3	3.7	3.3	3	2.7	2.5	2.3	2.2
V ₁₊	2.436	2.252	2.02	1.81	1.64	1.5	1.35	1.24	1.15	1.06	1	0.93	0.9

DRAW V₁₊ GRAPH

$$V_{in} - V_{REF} \times AV$$

$$V_{I(+)} = V_{CC} \times \frac{R_{NTC}}{R_1 + R_{NTC}}$$


$$V_{I(-)} = V_{CC} \times \frac{R_3}{R_2 + R_3}$$

IF $R_{NTC} = 9.5 k\Omega$
 $R_1 = 10 k\Omega$

$$V_{I(+)} = \frac{9.5}{10 + 9.5} \times 5 = 2.435$$

IF $R_{NTC} = 8.2 k\Omega$
 $R_1 = 10 k\Omega$
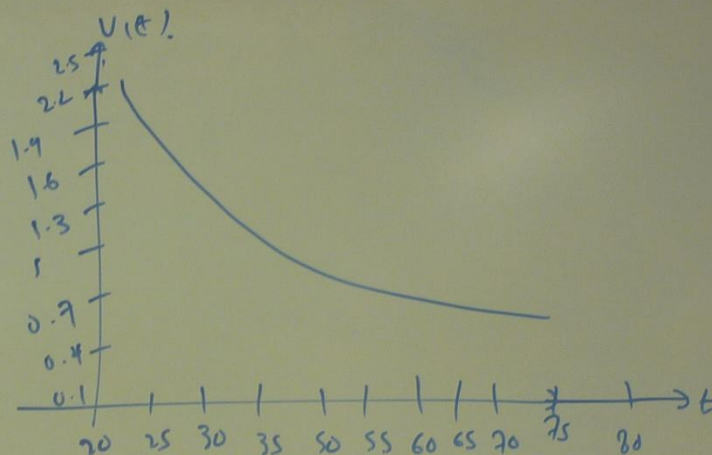
$$V_{I(+)} = \frac{8.2}{10 + 8.2} \times 5 = 2.252$$



IN ABOVE PROBLEM

(i) CALCULATE INVERTING INPUT VOLTAGE

$$V_{I(-)}$$

(ii) DETERMINE THE TRANSITION TEMPERATURE

(iii) DETERMINE THE VALUE OF R_3 FOR $70^\circ C$ TRANSITION TEMPERATURE

(iv) SHOW A RELAY INTERFACE CIRCUIT TO THE OUTPUT TERMINAL TO OPERATE A 240V HEATING ELEMENT.

(b) V
 (i)

AT SO

(ii) so c

(iii)

$$\begin{aligned}
 (b) \quad V_1(-) &= V_{cc} \times \frac{R_3}{R_2 + R_3} \\
 (i) \quad &= 5 \times \frac{1.2}{1.2 + 3} \\
 &= 1.043 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 \text{AT } 50^\circ\text{C}, V_1(+)<V_1(-) \\
 1.35\text{V} \quad 1.43\text{V}
 \end{aligned}$$

(ii) 50°C IS TRANSITION TEMPERATURE

(iii) FOR 70°C TEMPERATURE TO
BECOME TRANSITION TEMPERATURE
 $V_1(-)$ MUST BE AT LEAST 1V


$$\begin{aligned}
 V_1(-) &= V_{cc} \times \frac{R_3}{R_2 + R_3} \\
 1 &= 5 \times \frac{R_3}{R_3 + 3}
 \end{aligned}$$


$$1 = \frac{5R_3}{R_3 + 3}$$

$$R_3 + 3 = 5R_3$$

$$4R_3 = 3$$


$$R_3 = 0.75 \text{ k}\Omega$$

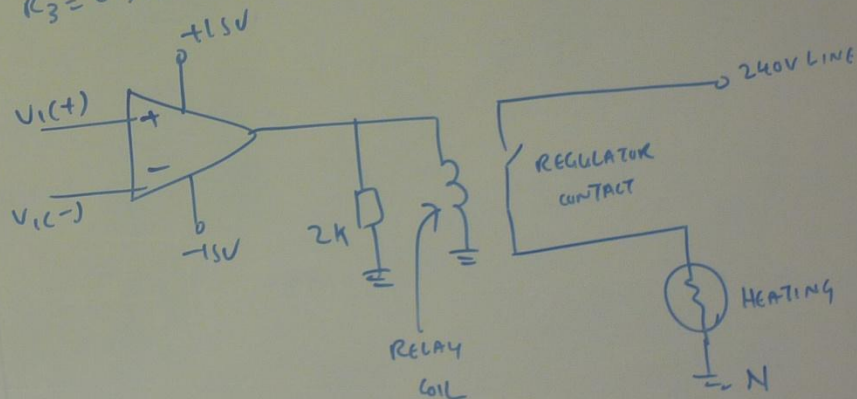

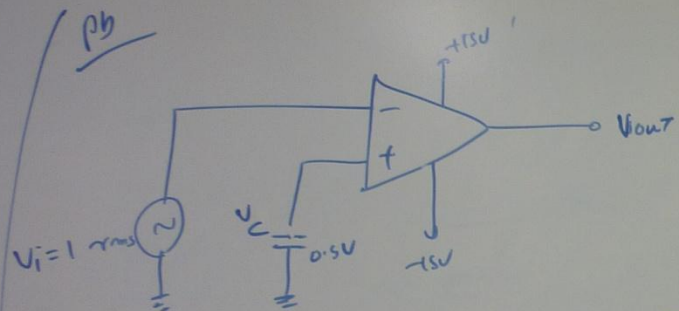

DRAW BOTH INPUT AND OUTPUT WAVE FORMS
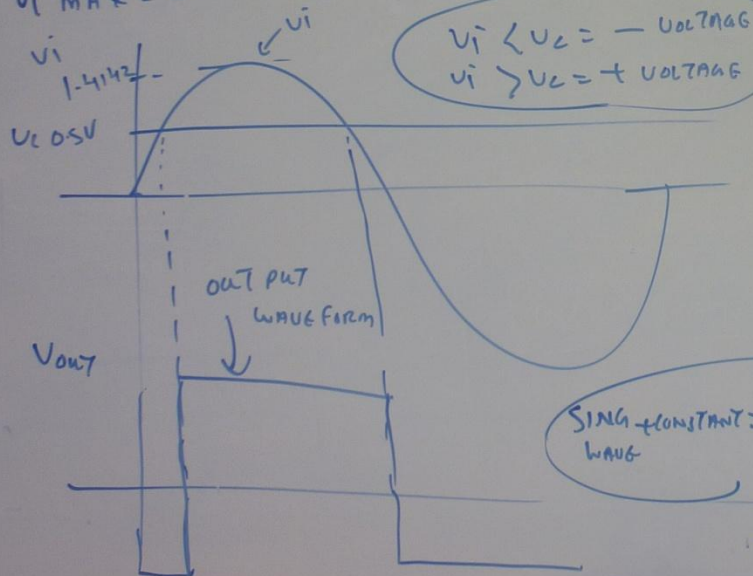
$$V_{i \text{ MAX}} = \sqrt{2} V_{i \text{ rms}} = 1.4142 \times 1 = 1.4142 \text{ V}$$





$$V_i < V_c = - \text{VOLTAGE}$$

$$V_i > V_c = + \text{VOLTAGE}$$


SING + CONSTANT $\Rightarrow$ SQUARE WAVE

BASIC PWM CIRCUIT

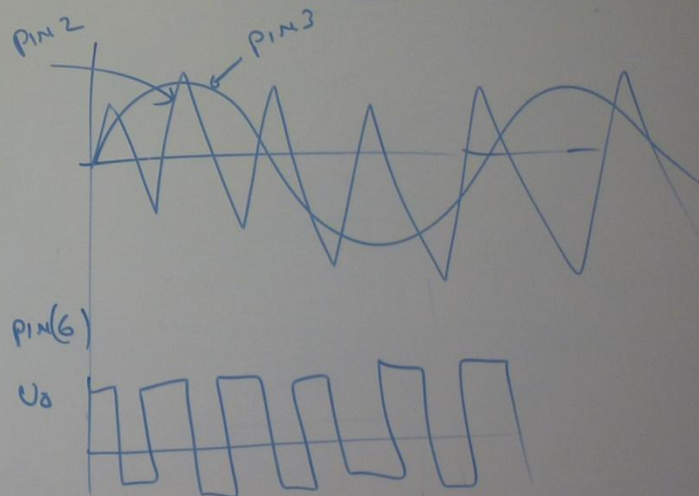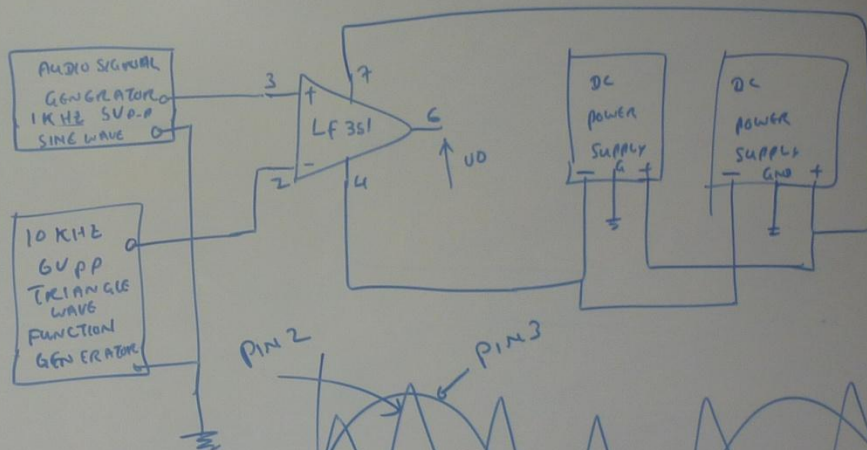

ph

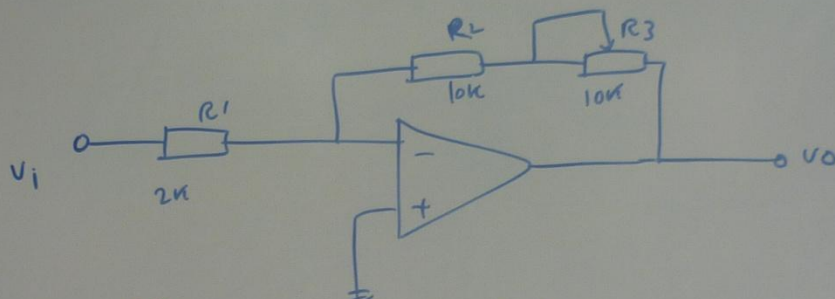FOR THE AMPLIFIER CIRCUIT SHOWN BELOW, DETERMINE MINIMUM VOLTAGE GAIN AND MAXIMUM VOLTAGE GAIN.




$$A_v = -\frac{R_f}{R_i} = -\frac{(R_2 + R_3)}{R_1}$$

$$\text{MAX } R_3 = 10k \rightarrow A_v = -\frac{(10+10)}{2} = -10$$

$$\text{MIN } R_3 = 0 \rightarrow A_v = -\frac{(10+0)}{2} = -5$$

ph

FOR THE CIRCUIT THE CURRENT

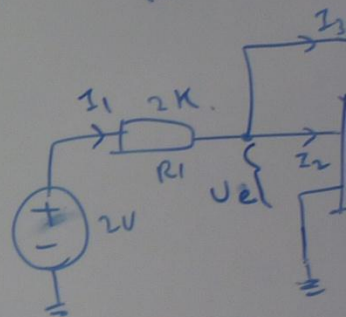

$$I_1 = \frac{V_{in}}{R_1} = \frac{2}{2}$$

$$I_2 = 0$$


$$\therefore I_1 = I_3 = 1$$

$$V_{Ref} = I_3$$

$$= 1$$

$$= 1$$

BELOW, DETERMINE
M JUTAGE GAIN.

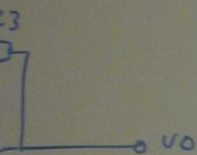


$$\frac{v_o}{v_i} = -10$$

$$\frac{v_o}{v_i} = -5$$

pn For THE CIRCUIT SHOWN BELOW FIND

THE CURRENT $I_1 \sim I_5$

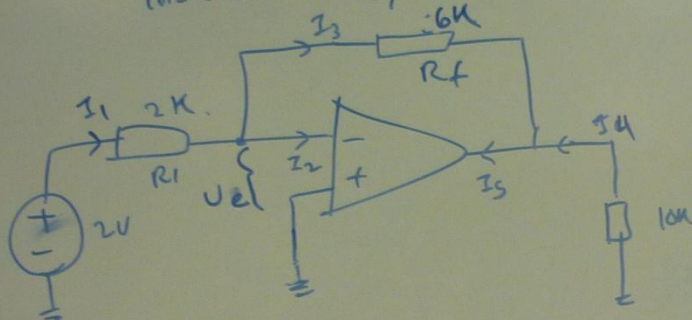

$$I_1 = \frac{V_{in}}{R_1} = \frac{2}{2K} = 1 \text{ mA}$$

$$I_2 = 0$$

$$\therefore I_1 = I_3 = 1 \text{ mA}$$

$$\begin{aligned} V_{Ref} &= I_3 \times R_f \\ &= 1 \text{ mA} \times 6K \\ &= 6V \end{aligned}$$


$$V_o = V_c - V_{Ref}$$

$$= 0 - 6 = -6V$$



$$\begin{aligned} I_4 &= \frac{V_{out}}{R_4} = \frac{-6}{10} \\ &= -0.6 \text{ mA} \end{aligned}$$

$$\begin{aligned} I_5 &= I_3 + I_4 \\ &= 1 + (-0.6) \\ &= 0.4 \text{ mA} \end{aligned}$$

$$\begin{aligned} I_1 \sim I_5 &= 1 - 0.4 \\ &= 0.6 \text{ mA} \end{aligned}$$

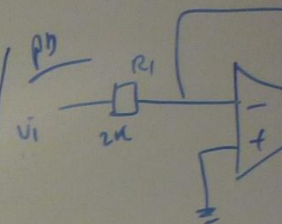

DETERMINE IN

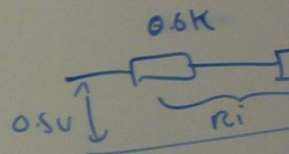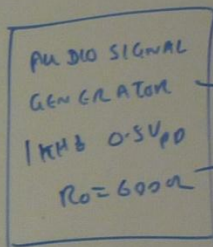

$$R_i = 0$$


$$V_o = V_c - V_{ref}$$

$$= 0 - 6 = -6 \text{ V}$$


$$I_4 = \frac{V_{out}}{R_4} = \frac{-6}{10} \\ \approx -0.6 \text{ mA}$$

$$I_5 = I_3 + I_4 \\ = 1 + (-0.6) \\ \approx 0.4 \text{ mA}$$

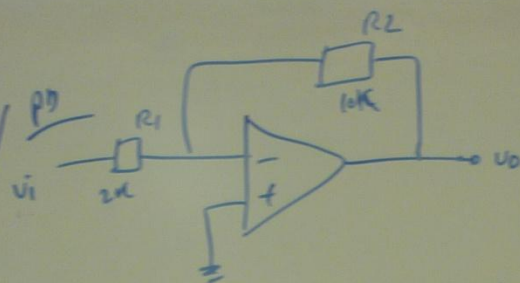
$$I_1 \sim I_5 = 1 - 0.4 \\ \approx 0.6 \text{ mA}$$



DETERMINING IN PUT RESISTANCE

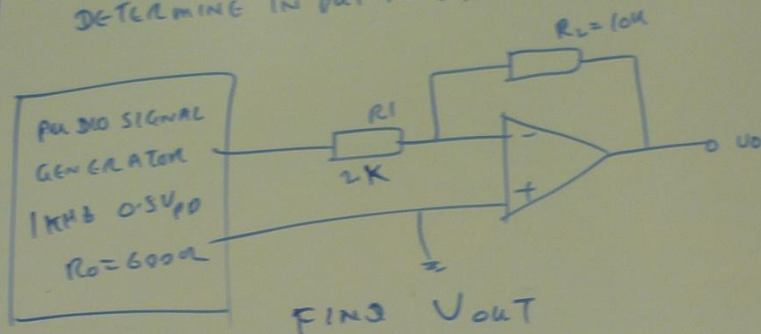

FIND V_{out}

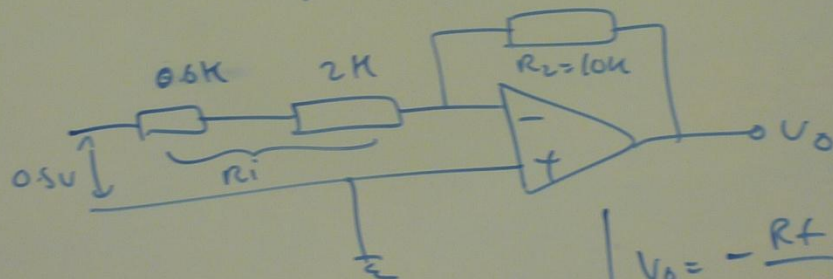

$$R_i = 0.6 + 2 = 2.6 \text{ k}$$

$$V_o = -\frac{R_f}{R_i} \times V_{in} \\ = -\frac{10}{2.6} \times 0.5 \\ \approx -1.92 \text{ V}$$

$$R_{in} = R_1 = 2 \text{ k}$$


(b)
(i)

AT

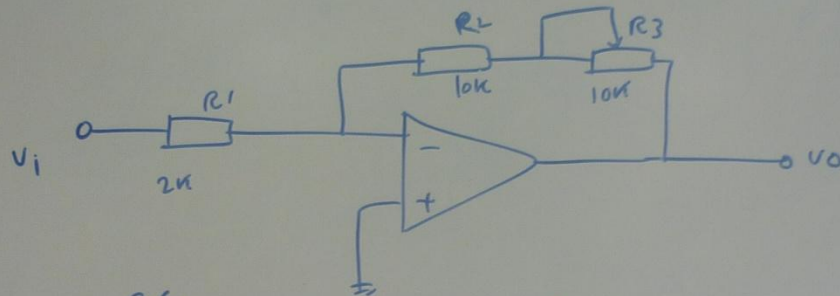(ii) so

(iii)

pb FOR THE AMPLIFIER CIRCUIT SHOWN BELOW, DETERMINE MINIMUM VOLTAGE GAIN AND MAXIMUM VOLTAGE GAIN.




$$A_v = -\frac{R_f}{R_i} = -\frac{(R_2 + R_3)}{R_1}$$

$$\text{MAX } R_3 = 10k \rightarrow A_v = -\frac{(10+10)}{2} = -10$$

$$\text{MIN } R_3 = 0 \rightarrow A_v = -\frac{(10+0)}{2} = -5$$

pb FOR THE CIR
THE CURRENT

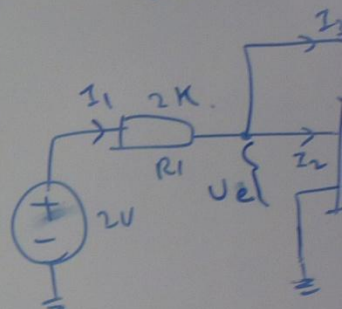

$$I_1 = \frac{V_{in}}{R_1} = \frac{2}{2}$$

$$I_2 = 0$$


$$\therefore I_1 = I_3 = 1$$

$$V_{Ref} = I_3$$

$$= 10$$

$$= 6$$

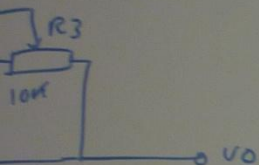Q.1) BELOW, DETERMINE
MAXIMUM VOLTAGE GAIN.




$$\frac{10+10}{2} = -10$$

$$\frac{10+10}{2} = -5$$

Q.2) FOR THE CIRCUIT SHOWN BELOW FIND

THE CURRENT $I_1 \sim I_5$

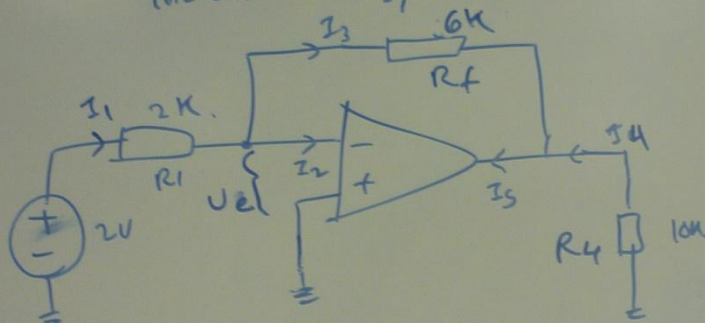

$$I_1 = \frac{V_{in}}{R_1} = \frac{2}{2K} = 1mA$$

$$I_2 = 0$$

$$\therefore I_1 = I_3 = 1mA$$

$$V_{Ref} = I_3 \times R_f$$

$$= 1mA \times 6K$$

$$= 6V$$

$$V_o = V_e - V_{Ref}$$

$$= 0 - 6 = -6V$$

$$I_4 = \frac{V_{out}}{R_4} = \frac{-6}{10}$$

$$= -0.6mA$$


$$I_5 = I_3 + I_4$$

$$= 1 + (-0.6)$$

$$= 0.4mA$$


$$I_1 \sim I_5 = 1 - 0.4$$

$$= 0.6mA$$

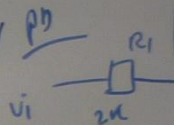

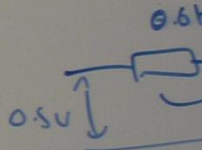Q.3) DETERMINE

AUDIO SIGNAL
GENERATOR
1KHz 0.5V_{pp}
 $R_o = 600\Omega$




$$V_o = V_c - V_{ref}$$

$$= 0 - 6 = -6 \text{ V}$$

$$I_4 = \frac{V_{out}}{R_4} = \frac{-6}{10} = -0.6 \text{ mA}$$


$$I_5 = I_3 + I_4 = 1 + (-0.6) = 0.4 \text{ mA}$$
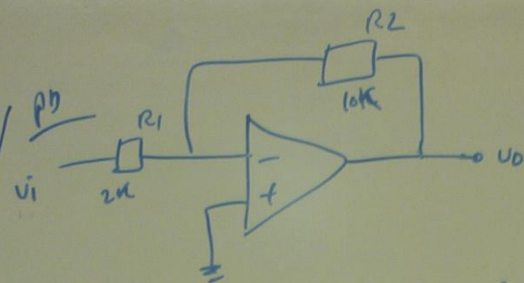
$$I_1 \sim I_5 = 1 - 0.4 = 0.6 \text{ mA}$$




DETERMINING IN PUT RESISTANCE

$$R_{in} = R_1 = 2 \text{ k}$$

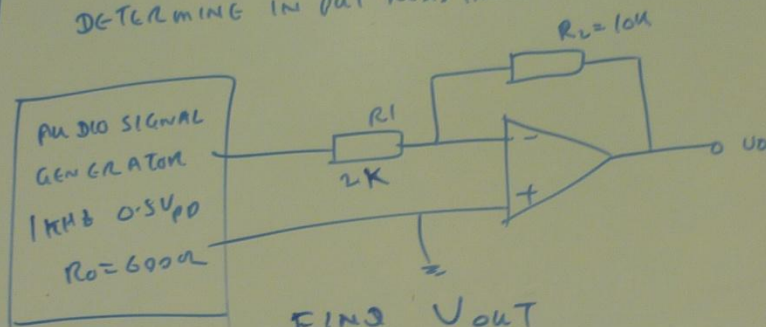

FIND V_{out}

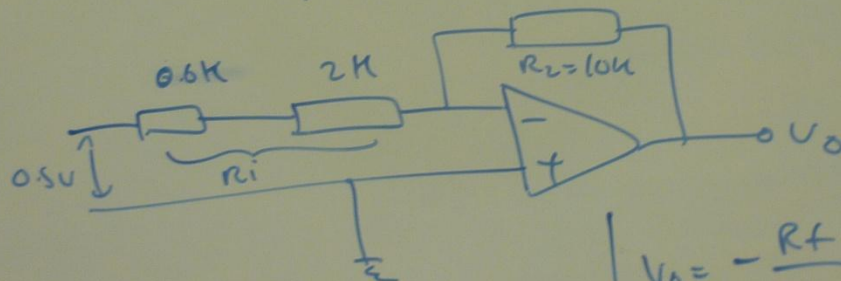


$$R_i = 0.6 + 2 = 2.6 \text{ k}$$

$$V_o = -\frac{R_f}{R_i} \times V_{in} = -\frac{10}{2.6} \times 0.5 = -1.92 \text{ V}$$


pb

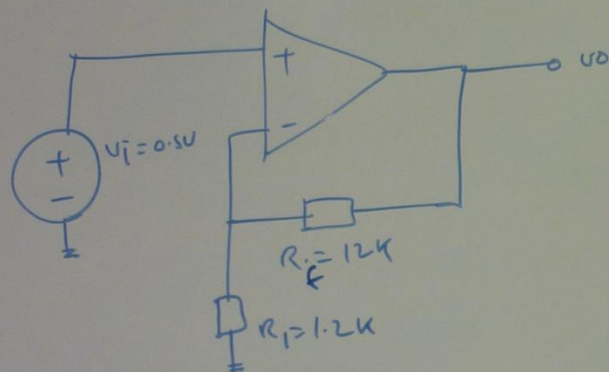FOR THE GIVEN CIRCUIT, CALCULATE
OUT PUT VOLTAGE



$$\begin{aligned}
 V_o &= \left[1 + \frac{R_f}{R_i} \right] V_i \\
 &= \left[1 + \frac{12}{1} \right] \times 0.5 \\
 &= [13] \times 0.5 \\
 &= 6.5V
 \end{aligned}$$

pb

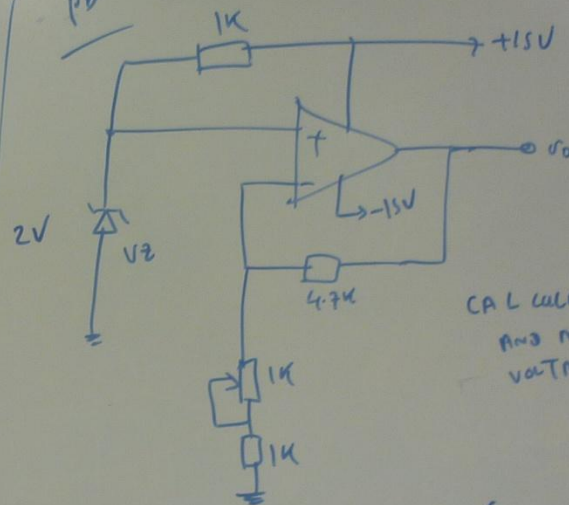

CALCULATE MAXIMUM
AND MINIMUM OUT PUT
VOLTAGES

$$V_o = (V_{IN} - V_z) \left(1 + \frac{R_f}{R_i} \right)$$

$$\frac{R_i = 1k}{V_o = (15 - 2) \left(1 + \frac{4.7}{1} \right) = 39V}$$

$$\frac{R_i = 2k}{V_o = (15 - 2) \left(1 + \frac{4.7}{2} \right) = 65V}$$

pb

$V_i = 1 \text{ rms}$

OR

$V_i \text{ max}$

V_i


1.414

$V_o \text{ rms}$

V_{out}

pb

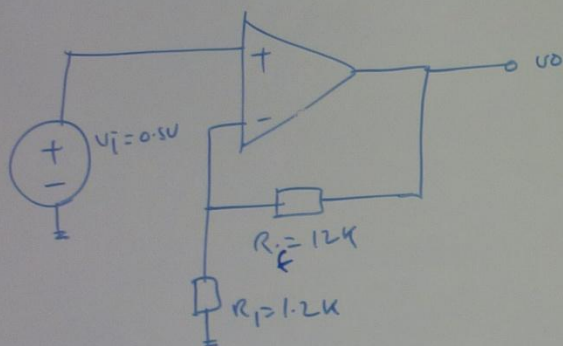FOR THE GIVEN CIRCUIT, CALCULATE
OUT PUT VOLTAGE




$$V_o = \left[1 + \frac{R_f}{R_i} \right] V_i$$

$$= \left[1 + \frac{12}{1} \right] \times 0.5$$

$$= [13] \times 0.5$$

$$= 6.5V$$

pb

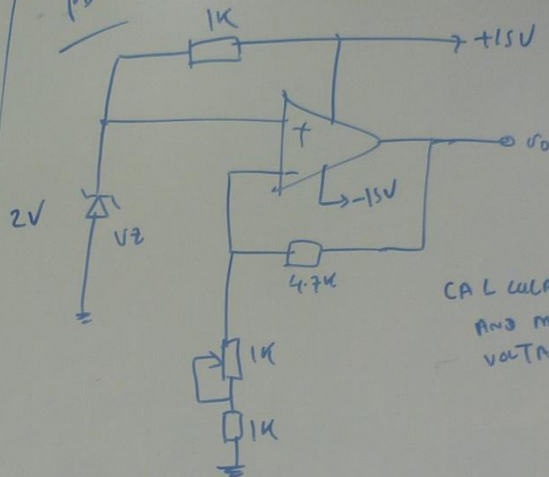

CALCULATE MAXIMUM
AND MINIMUM OUT PUT
VOLTAGES

$$V_o = (V_{IN} - V_z) \left(1 + \frac{R_f}{R_i} \right)$$

$$\frac{R_i = 1k}{R_f = 2k}$$

$$V_o = (15 - 2) \left(1 + \frac{4.7}{1} \right) = 39V$$

$$\frac{R_i = 2k}{R_f = 4.7k}$$

$$V_o = (15 - 2) \left(1 + \frac{4.7}{2} \right) = 65V$$

pb

