





D.C. DRIVE



LOAD

Excitation Volt

+ 89V

Operating Volt 30V

Maximum 70V




START



A.C. DRIVE



STOP

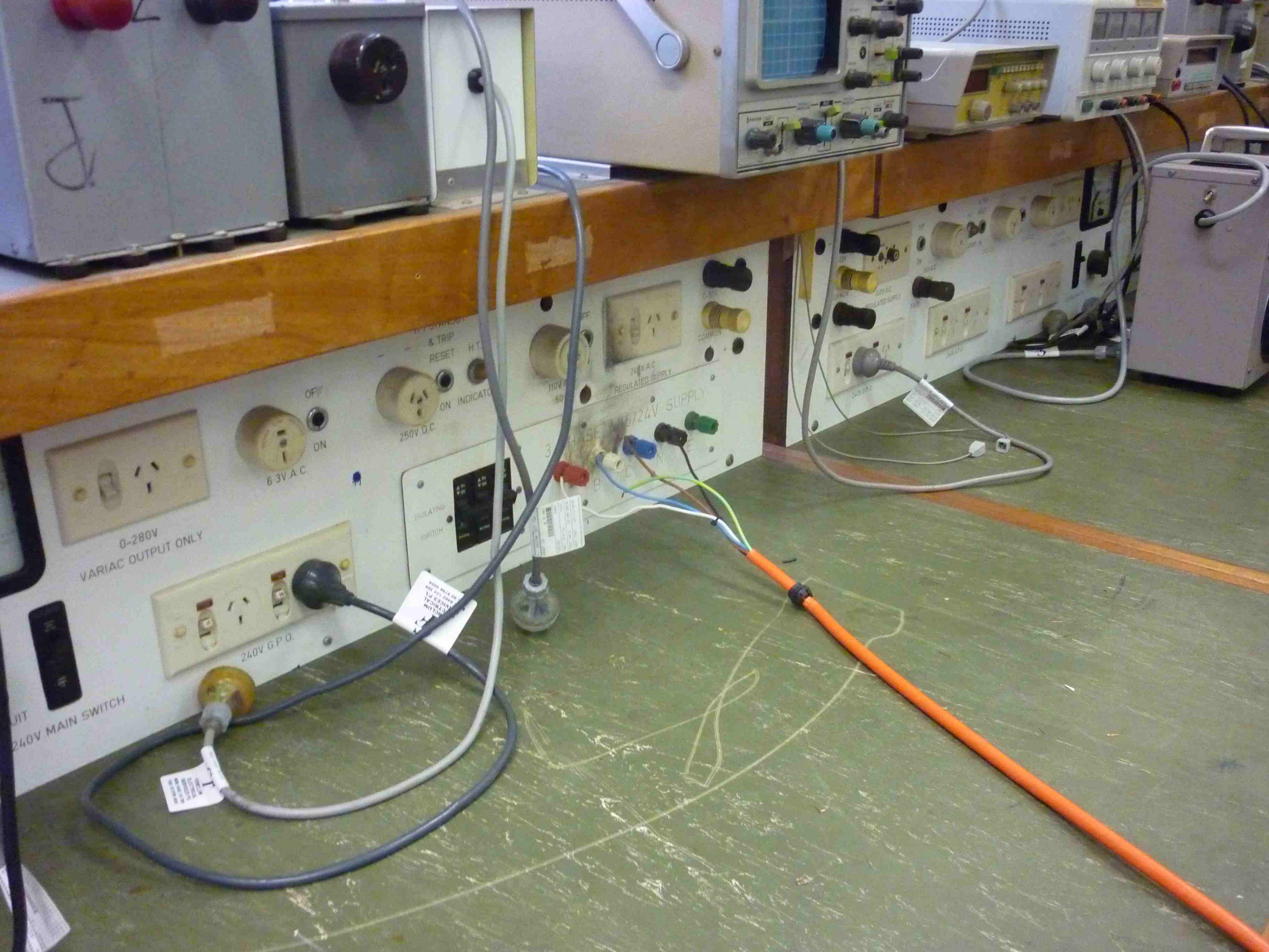






D. C. DRIVE

LOAD






DC GENERATOR CHARACTERISTICS TEST

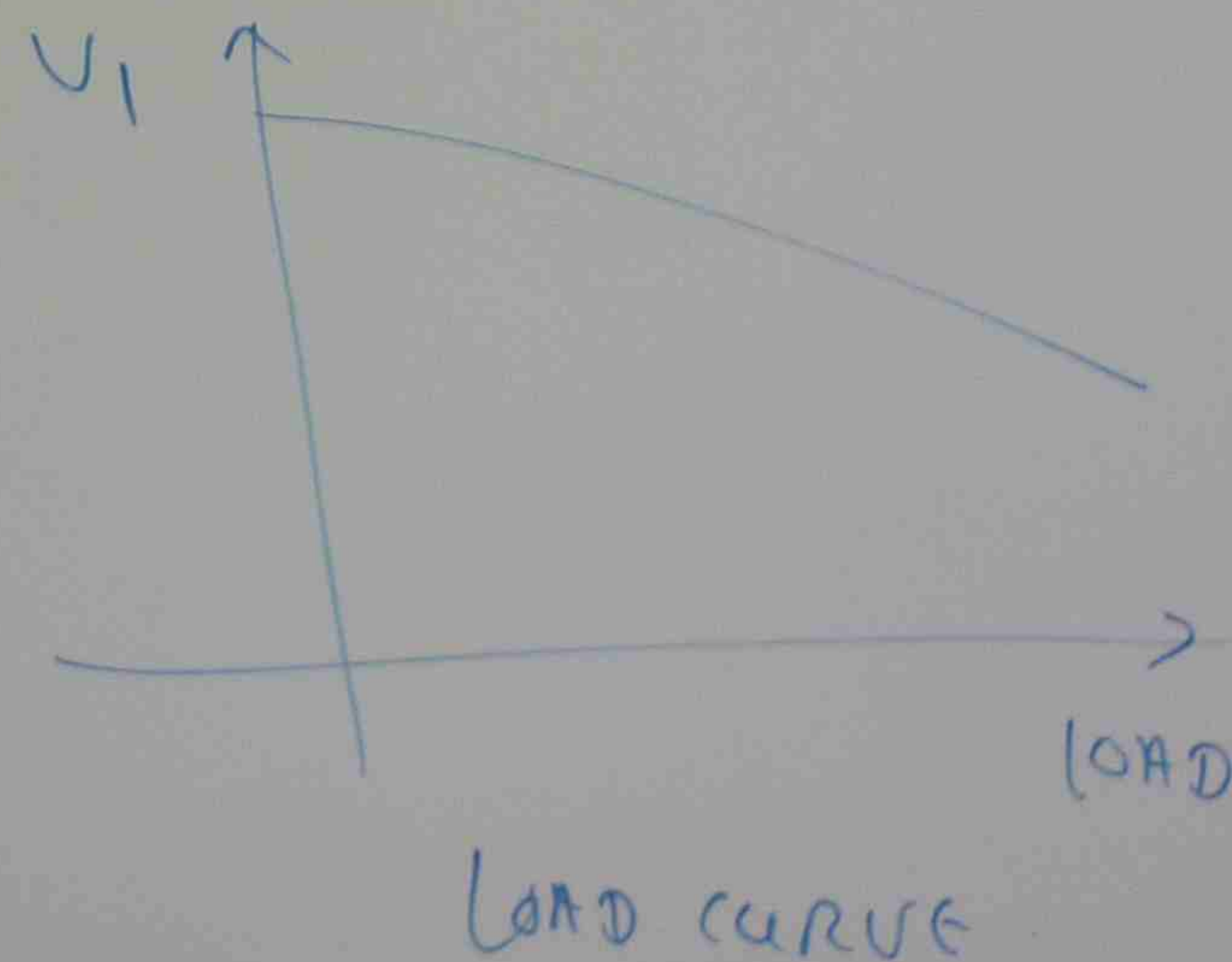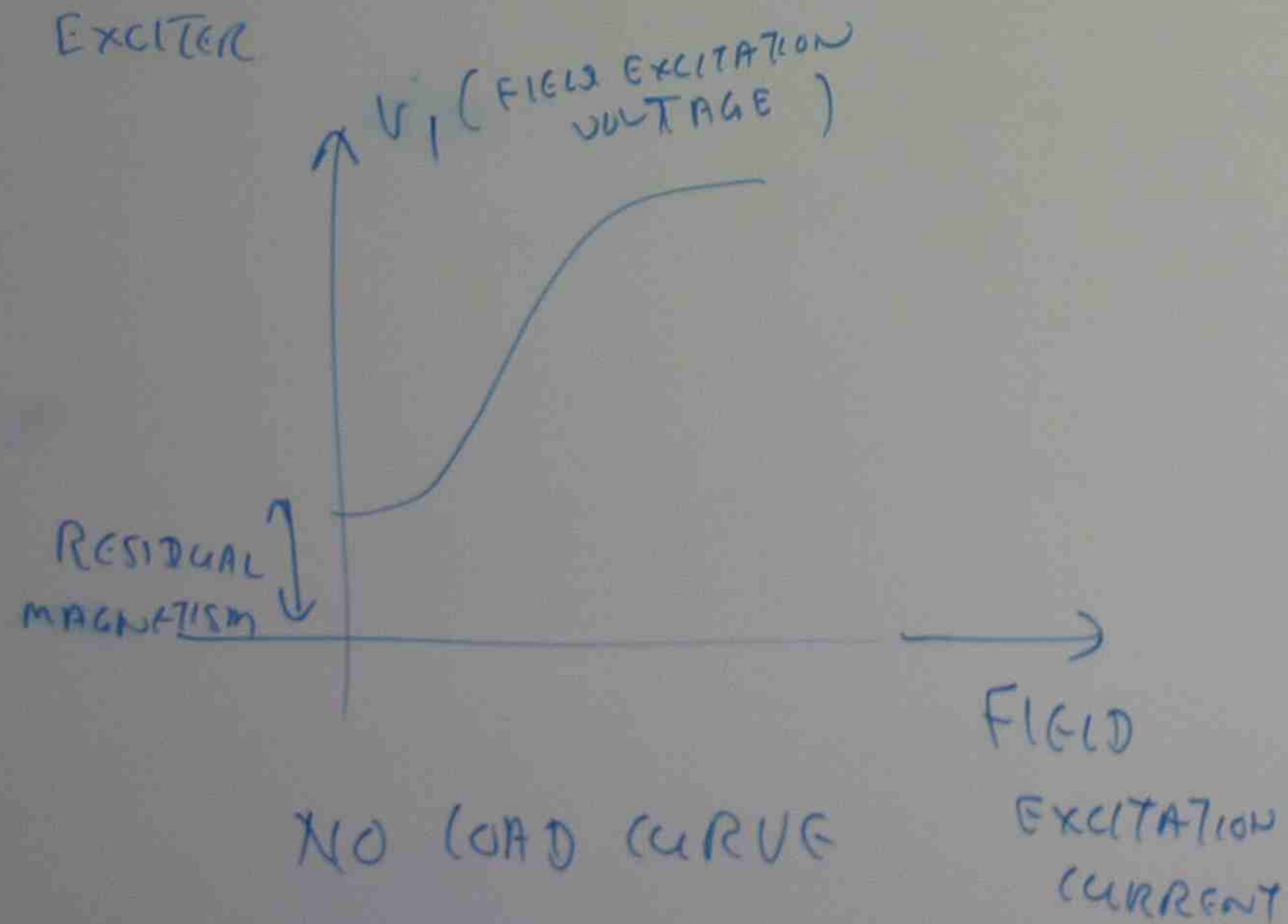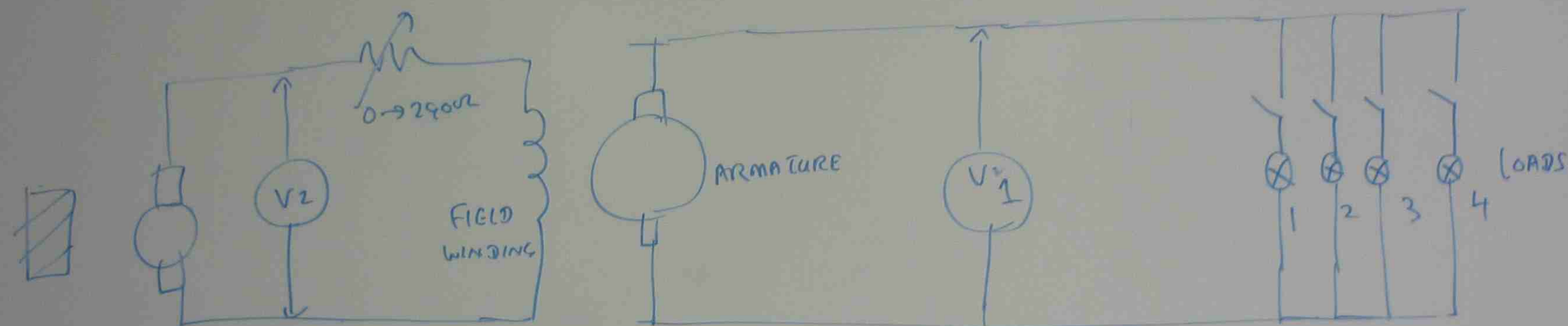

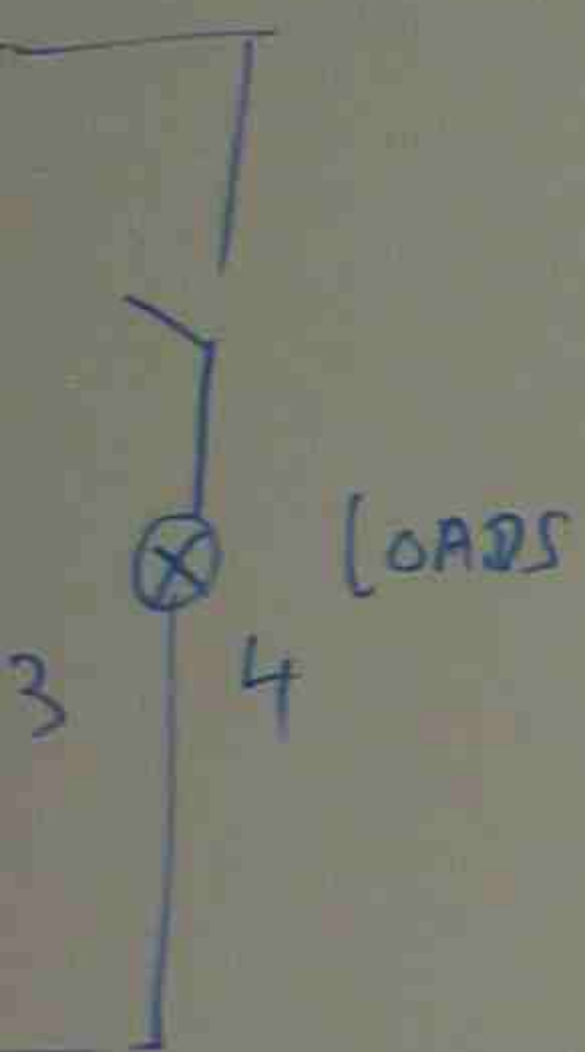- (1) CON
- (2) OF
- (3) NOT
- (4) ON
- (5) -




- ① CONNECT THE GIVEN CIRCUIT
- ② OFF THE FIELD EXCITATION SWITCH
- ③ NOTE THE TERMINAL VOLTAGE PRODUCED BY RESIDUAL MAGNETISM
- ④ ON THE FIELD EXCITATION SWITCH
- ⑤ REDUCE FIELD RESISTANCE AND NOTE TERMINAL VOLTAGE


FIELD RESISTANCE	$I_f = \frac{V_2}{\text{RESISTANCE}}$	V_1
Full 290 Ω		
$\frac{9}{10} \times 290$		
$\frac{8}{10} \times 290$		
$\frac{7}{10} \times 290$		
$\frac{6}{10} \times 290$		
$\frac{5}{10} \times 290$		
$\frac{4}{10} \times 290$		
$\frac{3}{10} \times 290$		

	V_1
$\frac{2}{10} \times 290$	
$\frac{1}{10} \times 290$	

PLOT FIELD CURRENT
VS TERMINAL
VOLTAGE

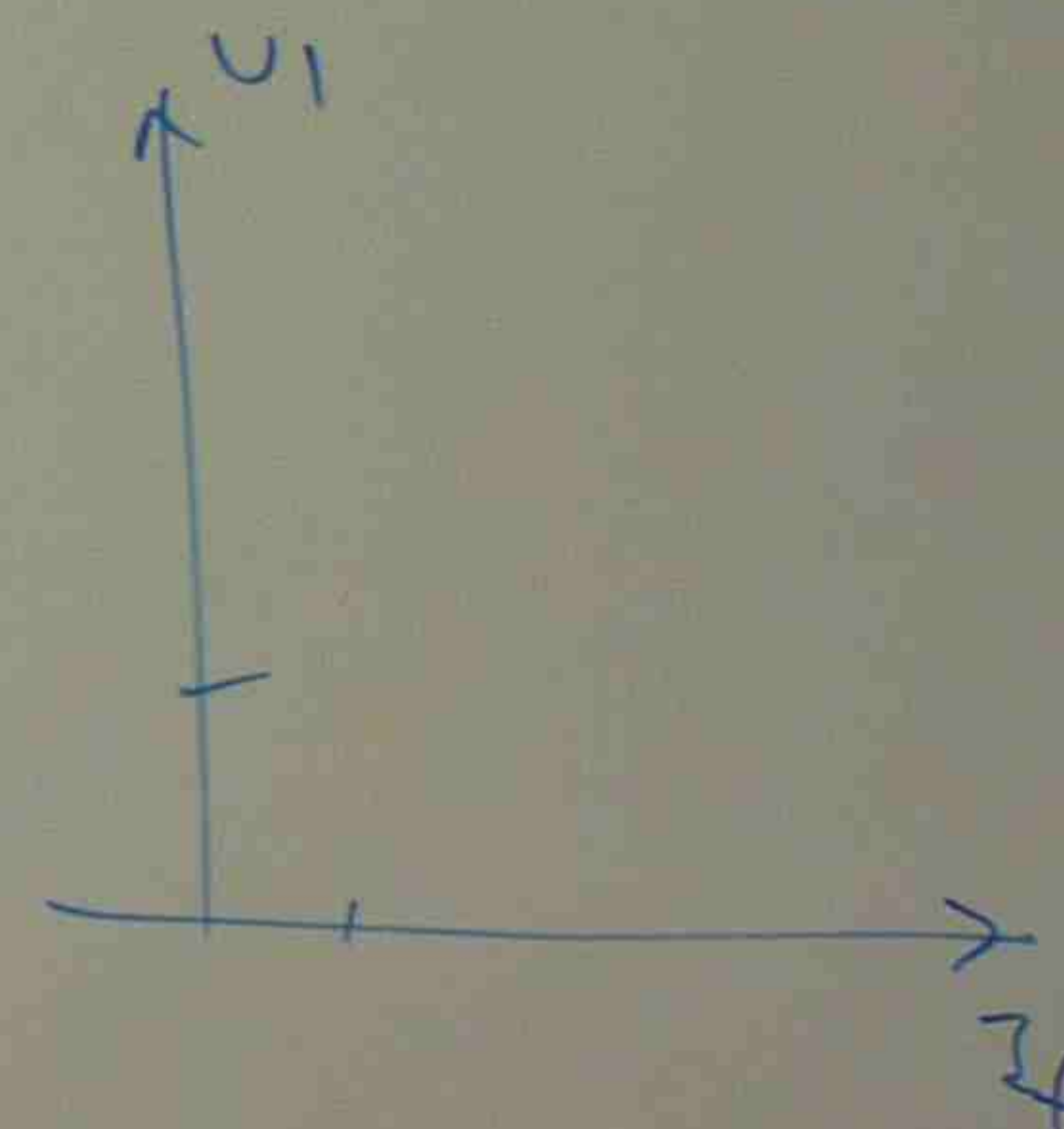

Plot FIELD CURRENT
VS TERMINAL
VOLTAGE

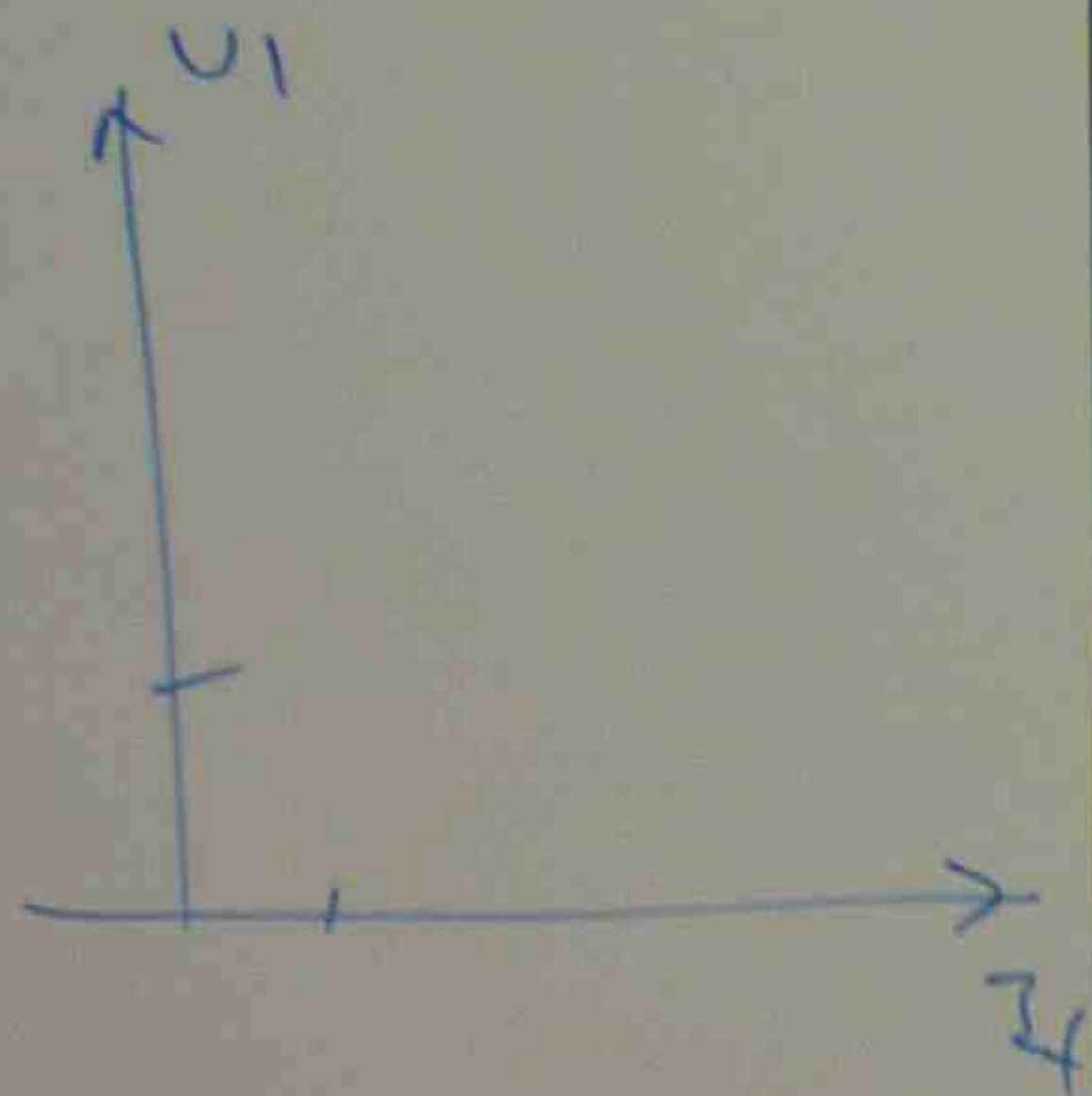

⑥ REDUCE TERMINAL VOLTAGE TO 30V




⑦ INCREASE THE LOADS AND NOTE TERMINAL VOLTAGE, FILL THE TABLE

LOAD LAMP	U_1
1	
2	
3	
4	

Plot LOAD VS TERMINAL VOLTAGE




DC GENERATOR CHARACTERISTICS TEST

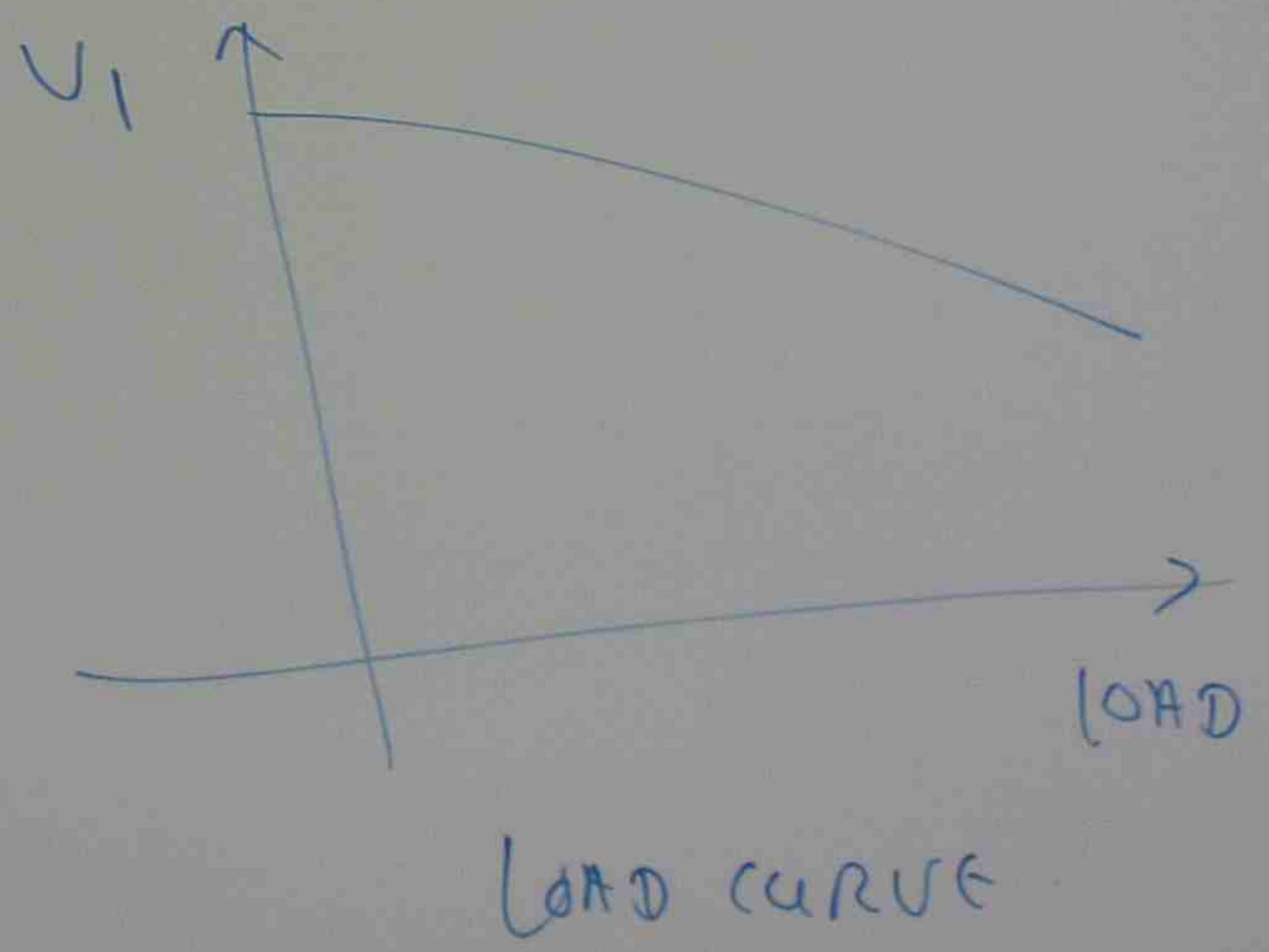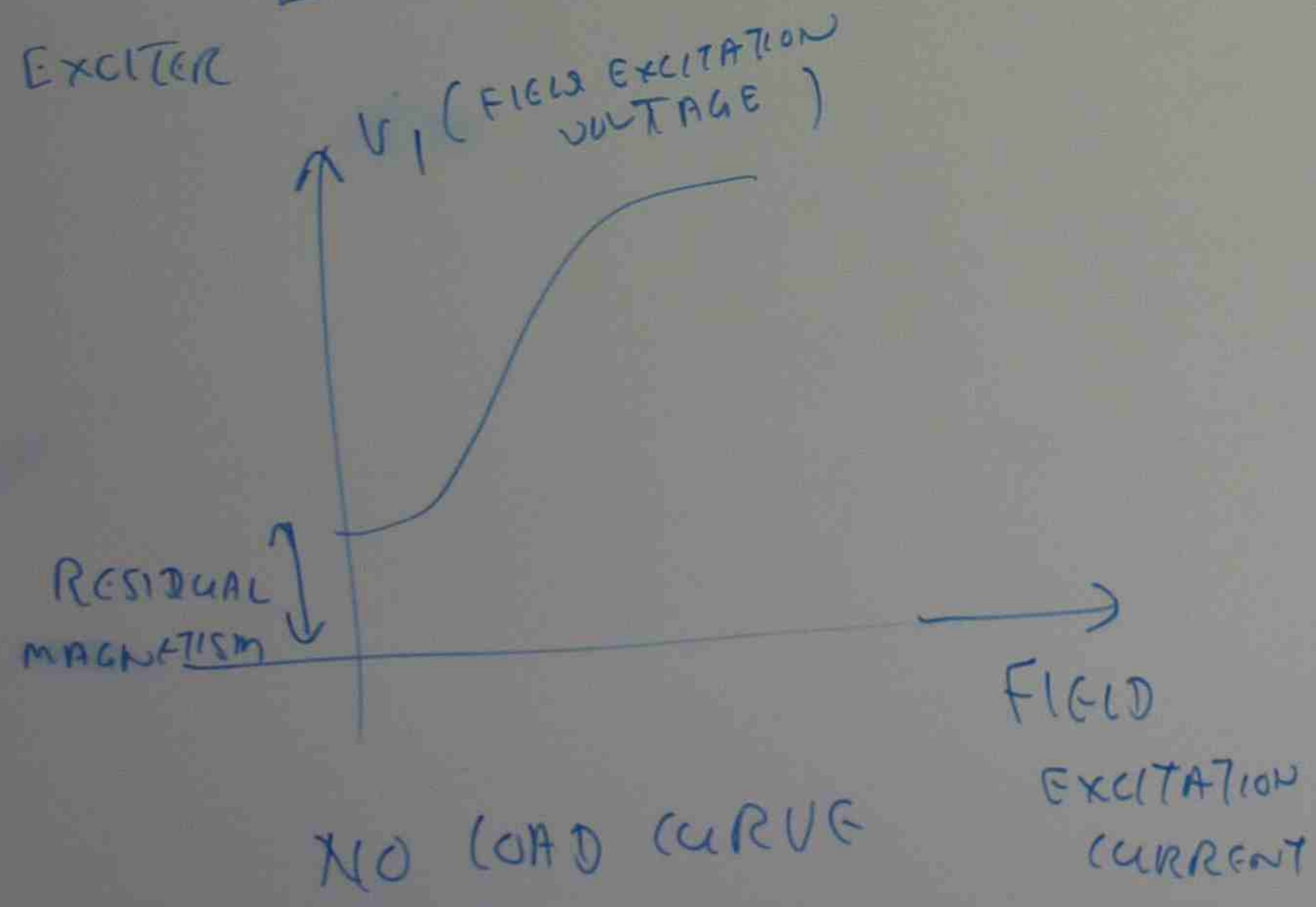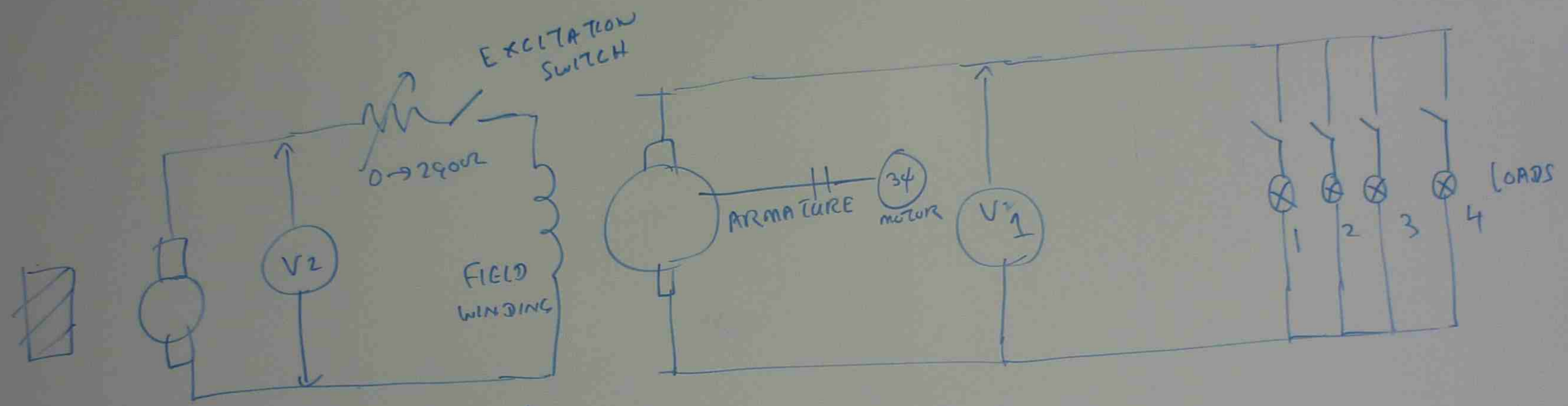

- ① CONNECT
- ② OFF THE
- ③ NOTE THE
- ④ ON THE
- ⑤ REDU

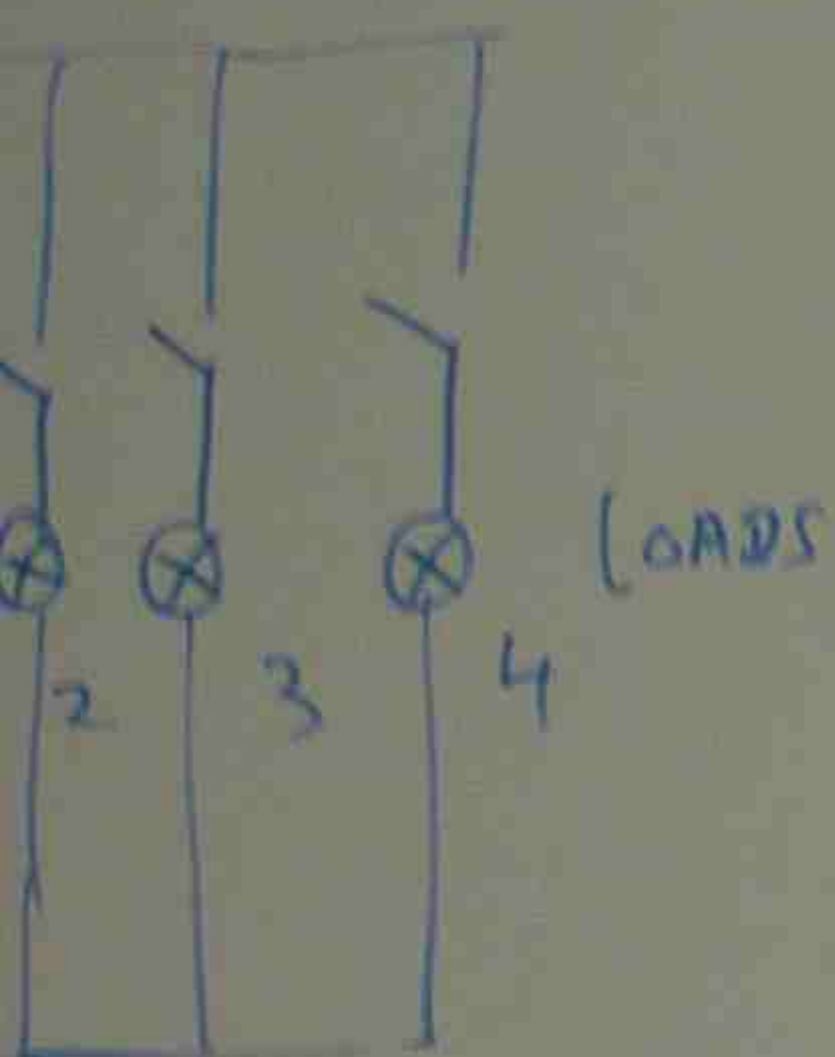FIELD
Full
$\frac{9}{10}$
$\frac{8}{10}$
$\frac{7}{10}$
$\frac{6}{10}$
$\frac{5}{10}$
$\frac{4}{10}$
$\frac{3}{10}$
$\frac{2}{10}$
$\frac{1}{10}$




- ① CONNECT THE GIVEN CIRCUIT
- ② OFF THE FIELD EXCITATION SWITCH
- ③ NOTE THE TERMINAL VOLTAGE PRODUCED BY RESIDUAL MAGNETISM
- ④ ON THE FIELD EXCITATION SWITCH
- ⑤ - REDUCE FIELD RESISTANCE AND NOTE TERMINAL VOLTAGE

FIELD RESISTANCE	$I_f = \frac{V_2}{\text{RESISTANCE}}$	V_1
FULL 290Ω + 10Ω		
$\frac{9}{10} \times 290 + 10\Omega$		
$\frac{8}{10} \times 290 + 10\Omega$		
$\frac{7}{10} \times 290 + 10\Omega$		
$\frac{6}{10} \times 290 + 10\Omega$		
$\frac{5}{10} \times 290 + 10\Omega$		
$\frac{4}{10} \times 290 + 10\Omega$		
$\frac{3}{10} \times 290 + 10\Omega$		




	V_1
$\frac{2}{10} \times 290 + 10\Omega$	
$\frac{1}{10} \times 290 + 10\Omega$	
100	

PLOT FIELD CURRENT

V_2 TERMINAL VOLTAGE

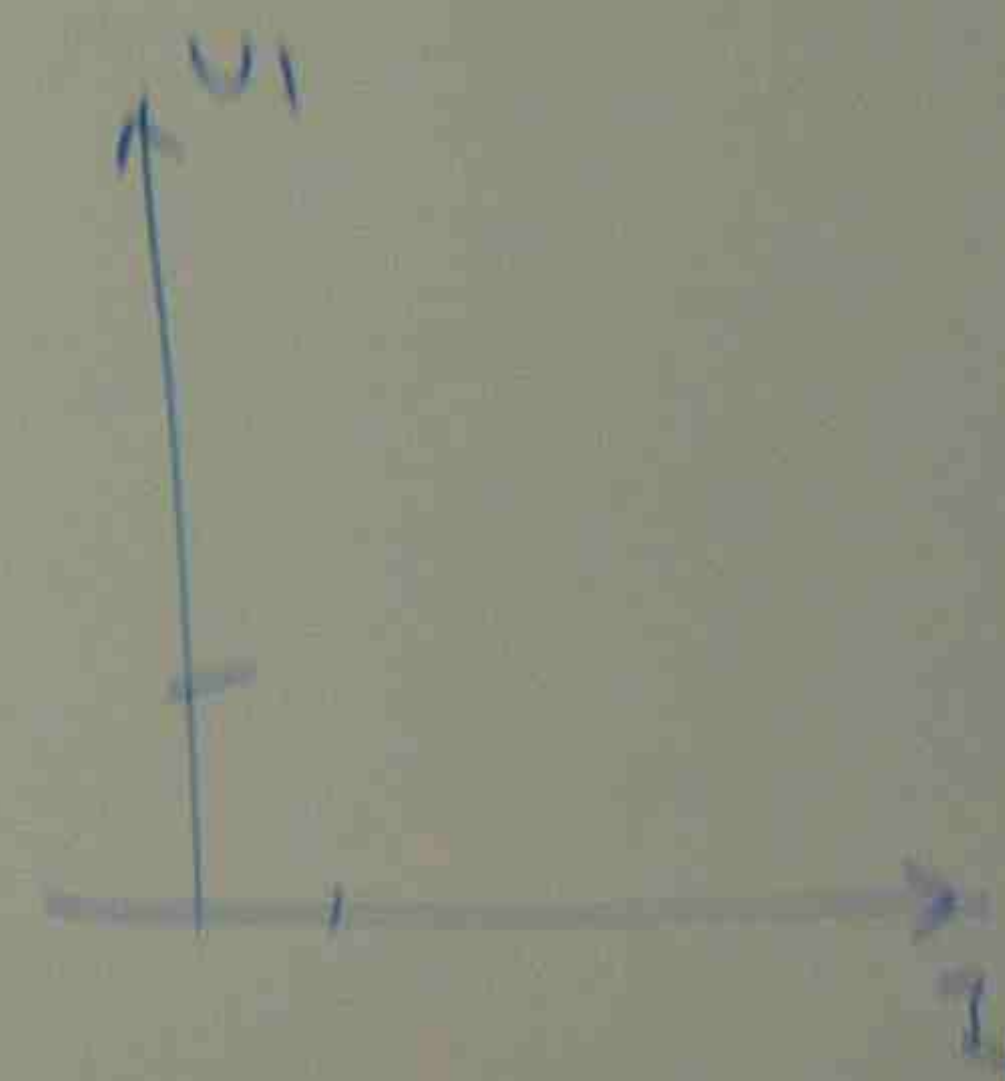


DC GENERATOR CHARACTERISTICS TEST

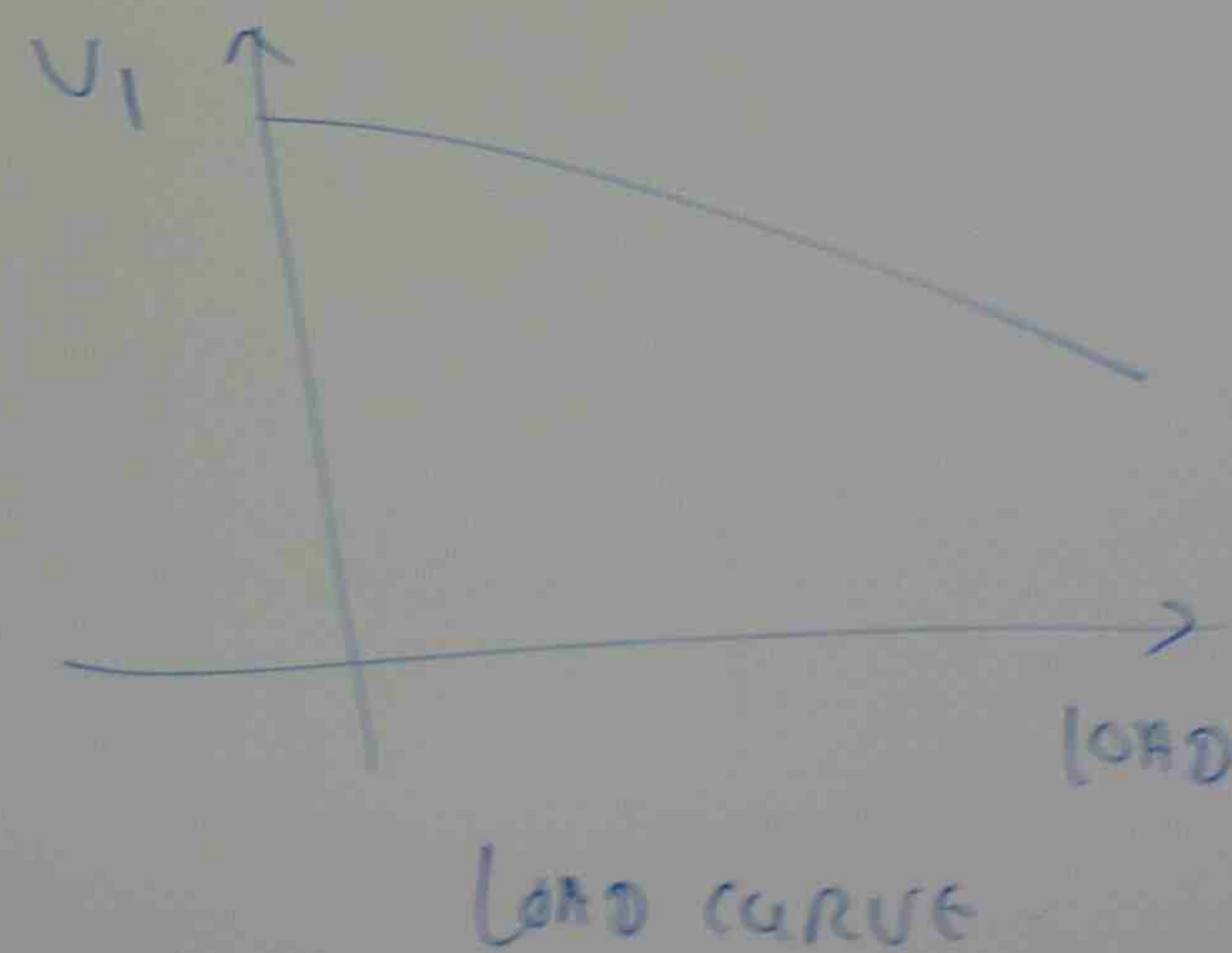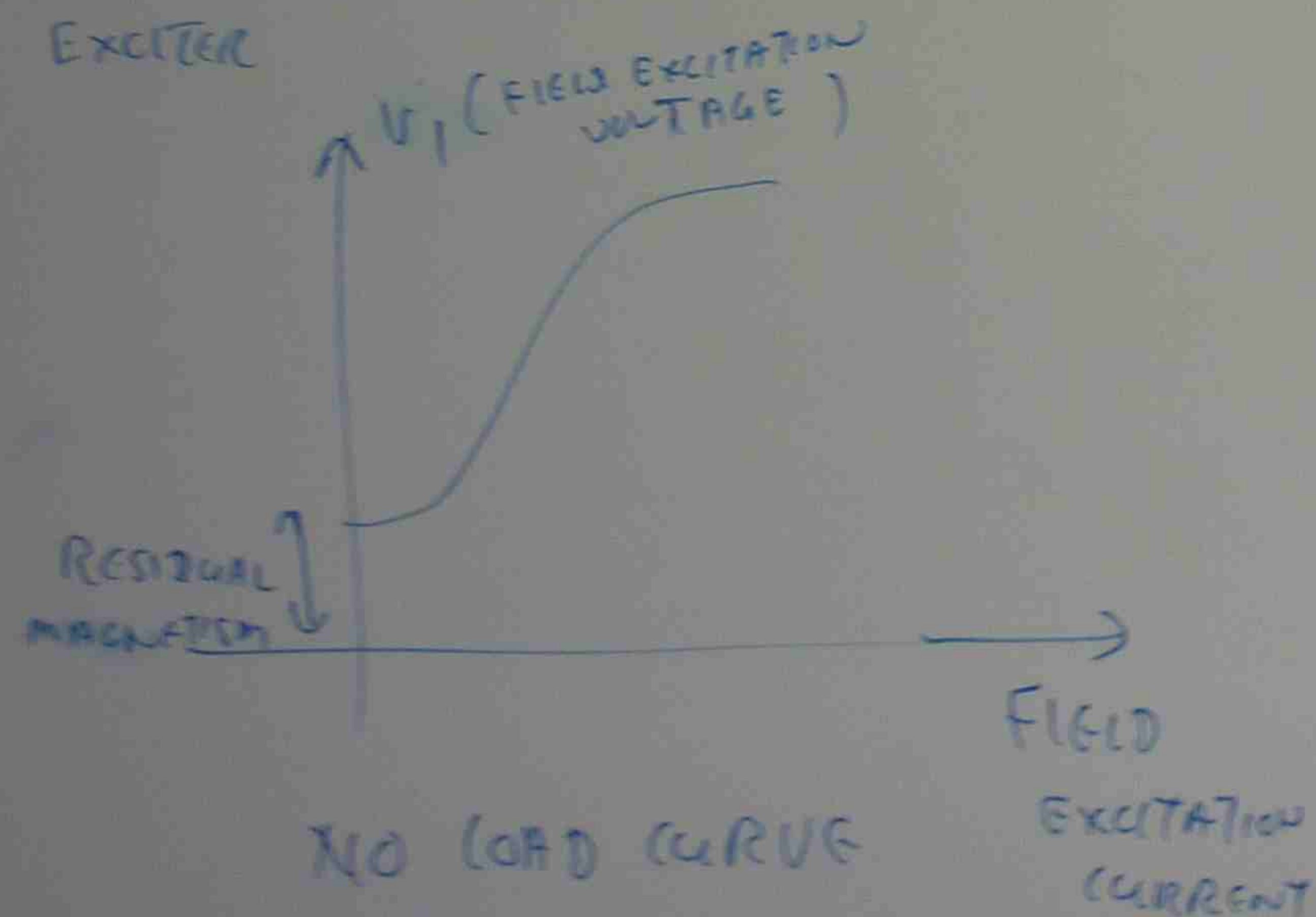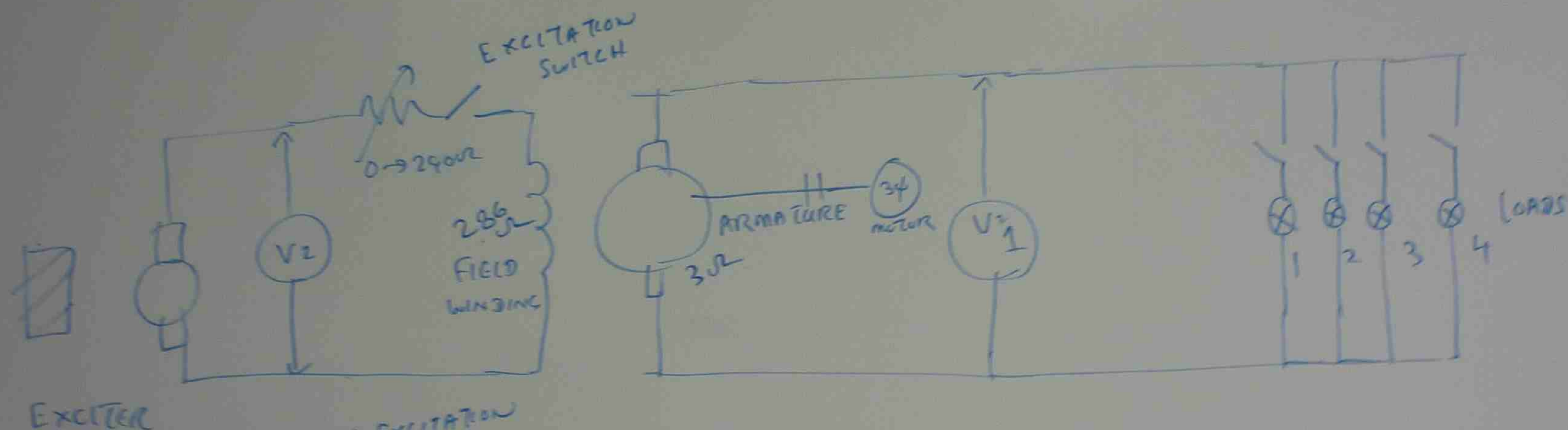

- ① CONNECT
- ② OFF THE
- ③ NOTE THE
- ④ ON THE
- ⑤ - READ

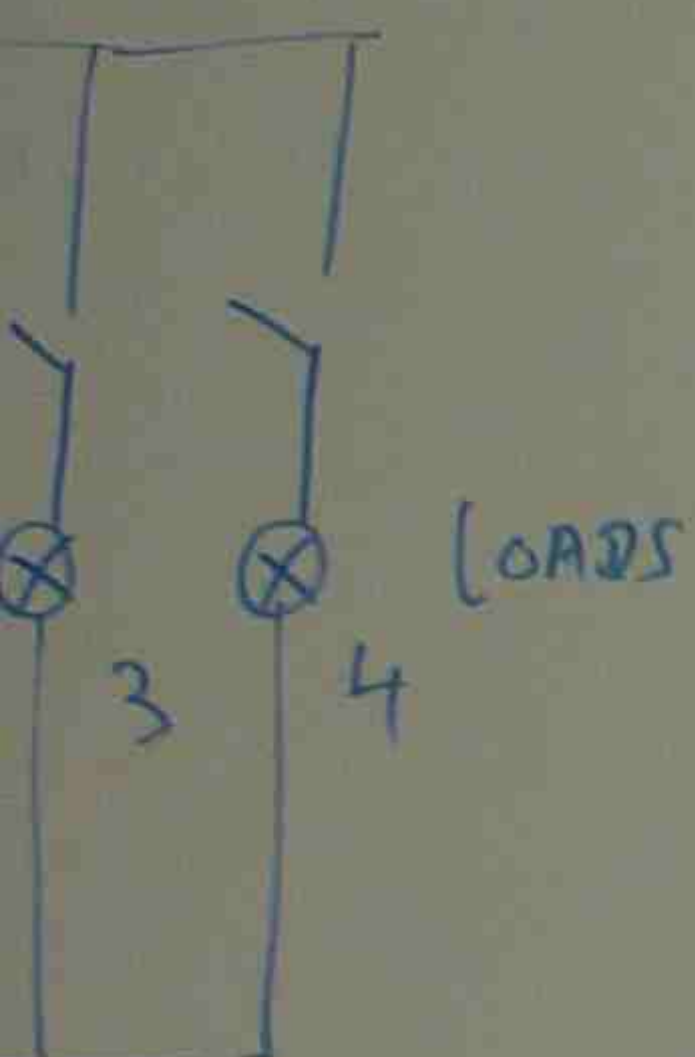FIELD
FULL
9/10
8/10
7/10
6/10
5/10
4/10
3/10




- ① CONNECT THE GIVEN CIRCUIT
- ② OFF THE FIELD EXCITATION SWITCH
- ③ NOTE THE TERMINAL VOLTAGE PRODUCED BY RESIDUAL MAGNETISM
- ④ ON THE FIELD EXCITATION SWITCH
- ⑤ - REDUCE FIELD RESISTANCE AND NOTE TERMINAL VOLTAGE

FIELD RESISTANCE	$I_f = \frac{V_2}{\text{RESISTANCE}}$	V_1
Full 290Ω + 286		
$\frac{9}{10} \times 290 + 286$		
$\frac{8}{10} \times 290 + 286$		
$\frac{7}{10} \times 290 + 286$		
$\frac{6}{10} \times 290 + 286$		
$\frac{5}{10} \times 290 + 286$		
$\frac{4}{10} \times 290 + 286$		
$\frac{3}{10} \times 290 + 286$		

	V_1
$\frac{2}{10} \times 290 + 286$	
$\frac{1}{10} \times 290 + 286$	
286	

PLOT FIELD CURRENT
VS TERMINAL
VOLTAGE

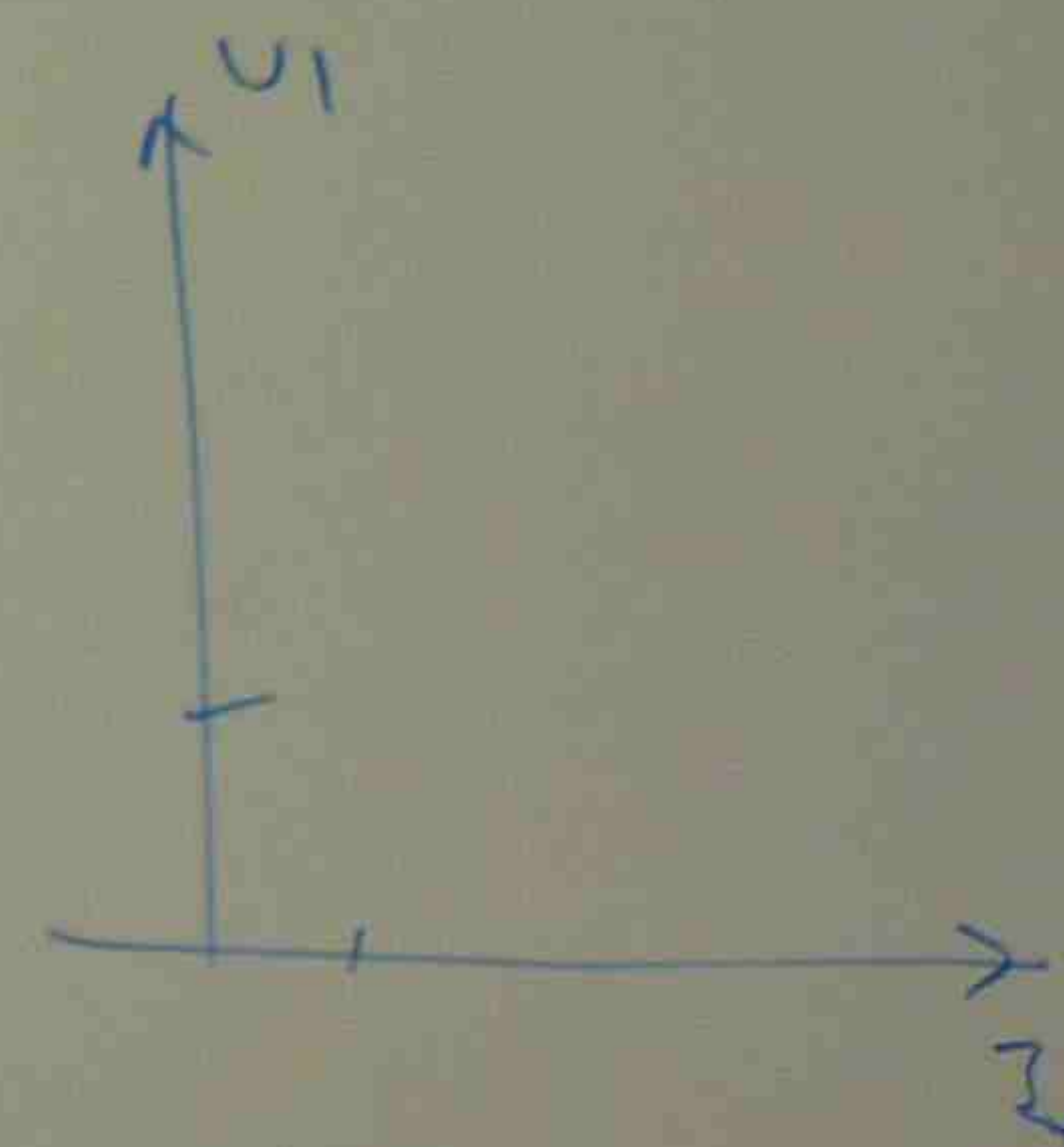

REVISION (1)

Q1 MOTOR PARTICULARS : SHUNT MOTOR 3.75 kW, 230V
18 amp, 1750 RPM. $R_a = 0.3 \Omega$ BRUSH DROP

2V ON LOAD

CALCULATE (a) FULL LOAD TORQUE

(b) INITIAL RUSH OF ARMATURE CURRENT AND
CORRESPONDING MOMENTARY MAXIMUM TORQUE
AT THE INSTANT THE FIELD RHEOSTAT RESISTANCE
IS INCREASED TO REDUCE THE FIELD FLUX TO
0.96 OF ORIGINAL VALUE

(c) FINAL ARMATURE CURRENT, SPEED AND
POWER ASSUMING TORQUE IS AS IN (a)

(1)



3.75 kW

(a)

$$P = \frac{2}{\text{POWER}}$$

$$T = \frac{60}{2T}$$

$$= \frac{6}{2}$$


$$= 3$$

W, 230V
drop

CURRENT AND
MUM TORQUE
STAT RESISTANCE
FLUX TO

PEED AND
IS AS IN (a)

(1)

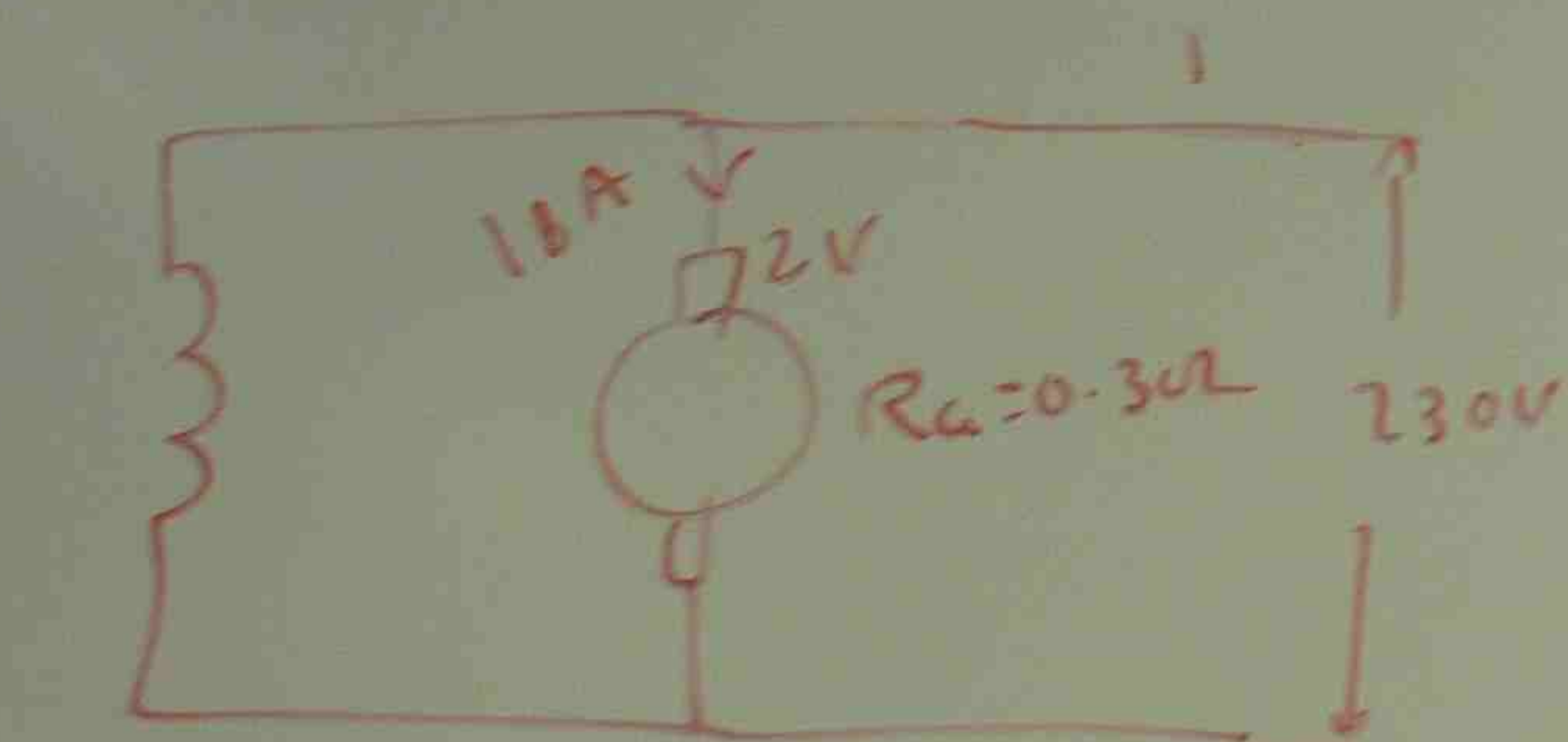

3.75 kW

(a)

$$P = \frac{2\pi NT}{60}$$

power

$$T = \frac{60 P}{2\pi N}$$

$$= \frac{60 \times 3750}{2 \times 3.1416 \times 1750}$$

$$= 20.4 \text{ N-m}$$

(b)

$$N_{FL} = \frac{V_t - \text{Brush drop} - I_a R_a}{K \phi_a}$$

$$N_{FL} = \frac{230 - 2 - 18 \times 0.3}{K \phi_a}$$

$$1750 = \frac{222.6}{K \phi_a}$$

$$K \phi_a = \frac{222.6}{1750} = 0.1273$$

96% reduction

$$K \phi_b = 0.96 K \phi_a = 0.96 \times 0.1273$$

$$N_{FL} = \frac{V_t - \text{BRUSH DROP} - I_a R_a}{K \phi_a}$$

$$N_{FL} = \frac{230 - 2 - 18 \times 0.3}{K \phi_a}$$

$$= \frac{222.6}{K \phi_a}$$

$$= \frac{222.6}{1750} = 0.1273$$

action

$$K \phi_a = 0.96 \times 0.1273$$

$$K \phi_b = \frac{V_t - \text{BRUSH DROP} - I_{a2} R_a}{N_{FL}}$$

$$0.96 \times 0.1273 = \frac{230 - 2 - I_{a2} \times 0.3}{1750}$$

$$I_{a2} = 46.7 \text{ Amp.}$$

$$\frac{T_2}{T_1} = \frac{K \phi_b I_{a2}}{K \phi_a I_{a1}}$$

$$\frac{T_2}{20.4} = \frac{0.96 \times 46.7}{18}$$

$$T_2 = \frac{20.4 \times 0.96 \times 46.7}{18} = 50.56 \text{ N-m}$$

$$\% \Delta T = \frac{50.56 - 20.4}{20.4} \times 100 = 150\%$$

$$\% \Delta I = 46.7$$

$$(c) \quad N =$$

$$K \phi_b = \frac{V_t - \text{BRUSH DROP} - I_{a2} R_a}{N_{FL}}$$

$$0.96 \times 0.1273 = \frac{230 - 2 - I_{a2} \times 0.3}{1750}$$

$$I_{a2} = 46.7 \text{ Amp.}$$

$$\frac{T_2}{T_1} = \frac{K \phi_b I_{a2}}{K \phi_a I_{a1}}$$

$$\frac{T_2}{20.4} = \frac{0.96 \times 46.7}{18}$$

$$T_2 = \frac{20.4 \times 0.96 \times 46.7}{18} = 50.56 \text{ N-m}$$

$$\Delta T = \frac{50.56 - 20.4}{20.4} \times 100 = 150\%$$

$$\% \Delta S = \frac{46.7 - 18}{18} \times 100 = 160\%$$

(c)

$$N = \frac{V_t - \text{BRUSH DROP} - I_{a2} R_a}{K \phi_b}$$

$$= \frac{230 - 2 - 46.7 \times 0.3}{0.96 \times 0.1273}$$

$$= 1751 \text{ rpm}$$

(2) A 7.5 kW
RESISTANCE

(a) IF NO

86%.

CALCULATION

PLACED IN

NEW SPEED,

IN RESPECT

(a)

R_{sh}
62.2Ω



60%

brush drop - $I_a R_a$

46

46.7×0.3


12.73

rpm

(2) A 7.46 kW, 230V, 1750 RPM SHUNT MOTOR ARMATURE RESISTANCE 0.35Ω HAS A SHUNT FIELD RESISTANCE 62.2Ω .

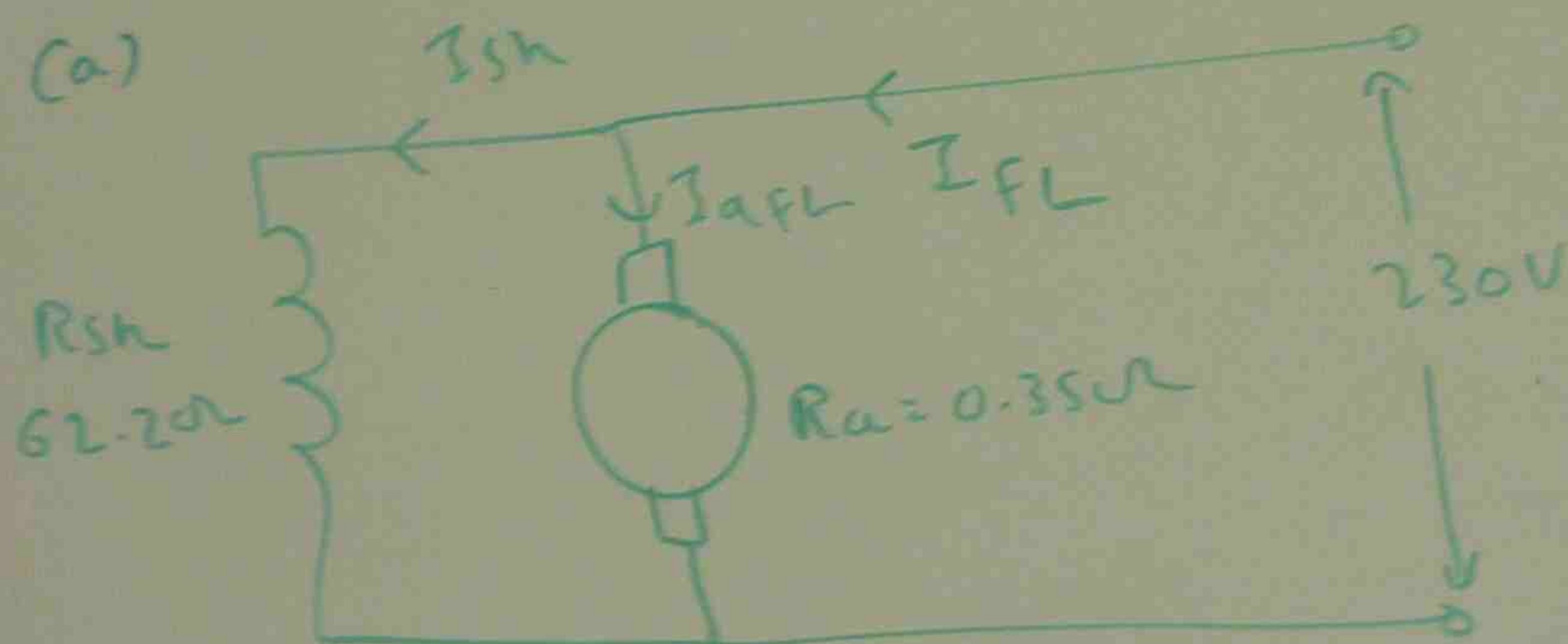(a) IF NO LOAD CURRENT IS 7.7 AMP AND FULL LOAD EFFICIENCY 86% BRUSH DROP 3V AT FULL LOAD, 1VOLT AT NO LOAD

CALCULATE % SPEED REGULATION (b) A 2.65Ω RESISTANCE IS PLACED IN SERIES WITH THE ARMATURE CIRCUIT, CALCULATE THE NEW SPEED, % REGULATION AND POWER LOSS IN SERIES RESISTANCE IN RESPECT TO TOTAL POWER INPUT AT FULL LOAD



Full Load

$$\text{Full Load Input Power} = \frac{7460}{0.86}$$

$$I_{FL} = \frac{7460}{0.86 \times 230} = 37.7 \text{ Amp}$$

$$I_{sh} = \frac{230}{62.2} = 3.7 \text{ Amp}$$

$$I_{aFL} = I_{FL} - I_{sh} = 37.7 - 3.7 = 34 \text{ Amp}$$

$$I_N = 3.7 \text{ A}$$

$$I_{sh} = 3.7 \text{ A}$$

$$I_{aFL} = 34 \text{ A}$$

$$N = \frac{V_t - E_b}{k \phi}$$

$$N_{FL} = \frac{230}{k \phi}$$

$$N_{NL} = \frac{230}{k \phi}$$

% Speed Reg

DC SHUNT MOTOR ARMATURE
RESISTANCE 62.2Ω

AND FULL LOAD EFFICIENCY

AT FULL LOAD, 1 VOLT AT NO LOAD

A 2.65Ω RESISTANCE IS

IN CIRCUIT, CALCULATE THE

POWER LOSS IN SERIES RESISTANCE

AT FULL LOAD

Full Load

$$\text{Full Load Input Power} = \frac{7460}{0.86}$$

$$I_{FL} = \frac{7460}{0.86 \times 230}$$

$$= 37.7 \text{ Amp}$$

$$= 3.7 \text{ Amp}$$

$$I_{sh} = 37.7 - 3.7 = 34 \text{ Amp}$$

$$I_N = 3.7 \text{ Amp}$$

$$I_{sh} = 3.7 \text{ Amp}$$

$$I_{an} = 37.7 - 3.7 = 34 \text{ Amp}$$

$$N = \frac{V_t - \text{BRUSH DROP} - I_a R_a}{K \phi}$$

$$N_{FL} = \frac{230 - 3 - 34 \times 0.35}{K \phi} = \frac{215.1}{K \phi} \rightarrow 1750 \text{ rpm}$$

$$N_{NL} = \frac{230 - 1 - 4 \times 0.35}{K \phi} = \frac{227.6}{K \phi}$$

$$\% \text{ SPEED REG} = \frac{N_{NL} - N_{FL}}{N_{NL}} \times 100$$

$$= \frac{\frac{227.6}{K \phi} - \frac{215.1}{K \phi}}{\frac{227.6}{K \phi}} \times 100 = 5.49\%$$

$$N_{FL2} = \frac{V_t - \text{BRUSH DROP} - I_a R_a}{K \phi}$$

$$= \frac{230 - 3 - 34 \times 0.35}{K \phi}$$

$$N_{FL2} = \frac{230 - 3 - 34 \times 0.35}{K \phi}$$

$$N_{FL2} = \frac{230 - 3 - 34 \times 0.35}{K \phi}$$

$$\% \text{ SPEED REG} =$$

POWER LOSS IN
RESISTANCE



$$I_N = 7.7 \text{ Amp}$$

$$I_{sh} = 3.7 \text{ Amp}$$

$$= 7.7 - 3.7 = 4 \text{ Amp}$$

$$= \frac{V_t - \text{BRUSH DROP} - I_a R_a}{K \phi}$$

$$= \frac{230 - 3 - 34 \times 0.35}{K \phi} = \frac{215.1}{K \phi} \rightarrow 1750 \text{ rpm}$$

$$= \frac{230 - 1 - 4 \times 0.35}{K \phi} = \frac{227.6}{K \phi}$$

$$\% \text{ REG} = \frac{N_{NL} - N_{FL}}{N_{NL}} \times 100$$

$$= \frac{\frac{227.6}{K \phi} - \frac{215.1}{K \phi}}{\frac{227.6}{K \phi}} \times 100 = 5.49\%$$

$$N_{FL2} = \frac{V_t - \text{BRUSH DROP} - I_a R_a}{K \phi}$$

$$= \frac{230 - 3 - 34 \times (2.65 + 0.35)}{K \phi}$$

$$N_{FL2} = \frac{230 - 3 - 34 \times 3}{K \phi} = \frac{125}{K \phi}$$

$$N_{FL2} = \frac{125}{\frac{215.1}{1750}} = \frac{1750 \times 125}{215.1}$$

$$= 1016 \text{ rpm}$$

$$\% \text{ SPEED REG} = \frac{1750 - 1016}{1750} \times 100 = 41.9\%$$

$$\text{POWER LOSS IN SERIES RESISTOR} = I_a^2 R_{se} = 34^2 \times 2.65 = 3063.4 \text{ W}$$



$$\% \text{ power loss} = \frac{3063.4}{7460} \times 100 = 41\%$$

$$\times 100 = 160\%$$

$$t - \text{BRUSH DROP} - I_a R_a$$

$$k \phi_b$$


$$- 2 - 4.67 \times 0.3$$

$$0.96 \times 0.1273$$

$$- 51 \text{ rpm}$$

(2) A 7.46 kW, 230V, 1750 RPM SHUNT MOTOR ARMATURE RESISTANCE 0.35Ω HAS A SHUNT FIELD RESISTANCE 62.2Ω .

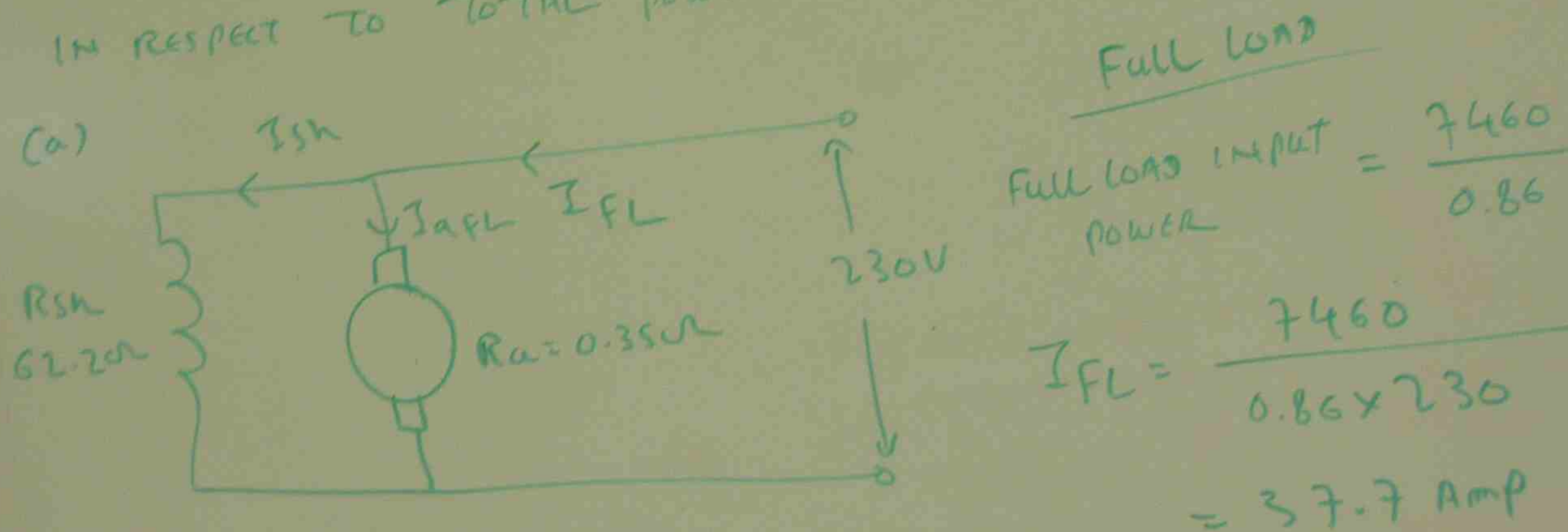(a) IF NO LOAD CURRENT IS 3.7 AMP AND FULL LOAD EFFICIENCY 86%. BRUSH DROP 3V AT FULL LOAD, 1 VOLT AT NO LOAD CALCULATE % SPEED REGULATION (b) A 2.65Ω RESISTANCE IS PLACED IN SERIES WITH THE ARMATURE CIRCUIT, CALCULATE THE NEW SPEED, % REGULATION AND POWER LOSS IN SERIES RESISTANCE IN RESPECT TO TOTAL POWER INPUT AT FULL LOAD



$$I_{sh} = \frac{230}{62.2} = 3.7 \text{ Amp}$$

$$I_{a FL} = I_{FL} - I_{sh} = 37.7 - 3.7 = 34 \text{ Amp}$$

$$I_N = 3.7 \text{ Amp}$$

$$I_{sh} = 3.7 \text{ Amp}$$

$$I_{a N} = 37.7 - 3.7 = 34 \text{ Amp}$$

$$N = \frac{V_t - \text{BRUSH}}{k \phi}$$

$$N_{FL} = \frac{230 - 3}{k}$$

$$N_{NL} = \frac{230 - 1}{k}$$

$$\% \text{ SPEED REG} =$$

1750 RPM SHUNT MOTOR ARMATURE
SHUNT FIELD RESISTANCE 62.2 Ω .
IS 3.7 AMP AND FULL LOAD EFFICIENCY
AT FULL LOAD, 1 VOLT AT NO LOAD
LATION (b) A 2.65 Ω RESISTANCE IS
ARMATURE CIRCUIT, CALCULATE THE
AND POWER LOSS IN SERIES RESISTANCE
POWER INPUT AT FULL LOAD

Full Load

Full Load Input = $\frac{7460}{0.86}$

$I_{FL} = \frac{7460}{0.86 \times 230}$

$= 37.7 \text{ Amp}$

$\frac{230}{62.2} = 3.7 \text{ Amp}$

$I_{FL} = I_{FL} - I_{sh} = 37.7 - 3.7 = 34 \text{ Amp}$

$I_N = 3.7 \text{ Amp}$

$I_{sh} = 3.7 \text{ Amp}$

$I_{an} = 37.7 - 3.7 = 34 \text{ Amp}$

$N = \frac{V_t - \text{Brush Drop} - I_a R_a}{K \phi}$

$N_{FL} = \frac{230 - 3 - 34 \times 0.35}{K \phi} = \frac{215.1}{K \phi} \rightarrow 1750 \text{ rpm}$

$N_{NL} = \frac{230 - 1 - 4 \times 0.35}{K \phi} = \frac{227.6}{K \phi}$

% Speed Reg = $\frac{N_{NL} - N_{FL}}{N_{NL}} \times 100$

$= \frac{\frac{227.6}{K \phi} - \frac{215.1}{K \phi}}{\frac{227.6}{K \phi}} \times 100 = 5.49\%$

$N_{FL2} = \frac{V_t - \text{Brush Drop}}{K \phi}$

$= \frac{230 - 3 - 34 \times 0.35}{K \phi}$

$N_{FL2} = \frac{230 - 3 - 34 \times 0.35}{K \phi}$

$N_{FL2} = \frac{125}{\frac{215.1}{1750}}$

% Speed Reg = $\frac{1750 - 1}{1750}$

Power loss in series resistor



% Power

$$I_N = 7.7 \text{ A}$$

$$I_{sh} = 3.7 \text{ A}$$

$$I_{an} = 7.7 - 3.7 = 4 \text{ A}$$

$$N = \frac{V_t - \text{BRUSH DROP} - I_a R_a}{k\phi}$$

$$k\phi = \frac{215.1}{1750}$$

$$N_{FL} = \frac{230 - 3 - 34 \times 0.35}{k\phi} = \frac{215.1}{k\phi} \rightarrow 1750 \text{ rpm}$$

$$N_{NL} = \frac{230 - 1 - 4 \times 0.35}{k\phi} = \frac{227.6}{k\phi}$$

$$\begin{aligned} \% \text{ SPEED REG} &= \frac{N_{NL} - N_{FL}}{N_{NL}} \times 100 \\ &= \frac{\frac{227.6}{k\phi} - \frac{215.1}{k\phi}}{\frac{227.6}{k\phi}} \times 100 = 5.49\% \end{aligned}$$

$$N_{FL2} = \frac{V_t - \text{BRUSH DROP} - I_a R_{a2}}{k\phi}$$

$$= \frac{230 - 3 - 34 \times (2.65 + 0.35)}{k\phi}$$

$$N_{FL2} = \frac{230 - 3 - 34 \times 3}{k\phi} = \frac{125}{k\phi}$$

$$N_{FL2} = \frac{125}{\frac{215.1}{1750}} = \frac{1750 \times 125}{215.1}$$

$$= 1016 \text{ RPM}$$

$$\% \text{ SPEED REG} = \frac{1750 - 1016}{1750} \times 100 = 41.97\%$$

$$\begin{aligned} \text{POWER LOSS IN SERIES RESISTOR} &= I_a^2 R_{se} = 34^2 \times 2.65 \\ &= 3063.4 \text{ W} \end{aligned}$$



$$\begin{aligned} \% \text{ POWER LOSS} &= \frac{3063.4}{7460} \times 100 \\ &= 41\% \end{aligned}$$

③ A 4 pole wave wound armature operating in a field of flux 0.01 weber is wound with 360 armature conductors. Determine the expression of Torque as a function of speed if $V_t = 250V$, $R_a = 0.1\Omega$

$$T = \frac{k_t \phi V_t}{R_a} - \frac{k_e k_t \phi^2}{R_a} \text{ N}$$

$$k_t = \frac{pZ}{2\pi a}$$

$$a = 2 \text{ m}$$

Simple wave

$$k_t = \frac{4 \times 360}{2 \times 3.1416 \times 2}$$

$$m = 1$$

$$a = 2 \times 1 = 2$$

$$= 114.5$$

$$k_e = \frac{pZ}{60a} = \frac{4 \times 360}{60 \times 2} = 12$$

$$T = 114.5$$

$$T = 2$$

A WAVE WOUND ARMATURE OPERATING IN A FIELD
 OF 0.01 WEBER IS WOUND WITH 360 ARMATURE
 DETERMINE THE EXPRESSION OF TORQUE AS A
 FUNCTION OF SPEED IF $V_f = 250V$, $R_a = 0.1\Omega$

$$\frac{\phi}{R_a} = \frac{k_e k_t \phi^2}{R_a} \quad N$$

$$k_t = \frac{pZ}{2\pi a}$$

$$k_t = \frac{4 \times 360}{2 \times 3.1416 \times 2} = 114.5$$

$$k_e = \frac{pZ}{60a} = \frac{4 \times 360}{60 \times 2} = 12$$

$$a = 2 \text{ m}$$

Simple wave

$$m = 1$$

$$a = 2 \times 1 = 2$$

$$T = \frac{114.5 \times 0.01 \times 250}{0.1} - \frac{12 \times 114.5 \times (0.01)^2}{0.1} \quad N$$

$$T = 2860 - 1.38 \quad N$$

- ③ A 4 pole wave wound armature operating in a field of flux 0.01 weber is wound with 360 armature conductors. Determine the expression of torque as a function of speed if $V_f = 250V$, $R_a = 0.1\Omega$

$$T = \frac{k_t \phi V_t}{R_a} - \frac{k_e k_t \phi^2}{R_a} \text{ N}$$

$$k_t = \frac{p z}{2\pi a}$$

$$a = 2 \text{ m}$$

Simple wave

$$k_t = \frac{4 \times 360}{2 \times 3.1416 \times 2} = 114.5$$

$$m = 1$$

$$a = 2 \times 1 = 2$$

$$k_e = \frac{p z}{60 a} = \frac{4 \times 360}{60 \times 2} = 12$$

$$T = \frac{114.5 \times 250}{0.1}$$

$$T = 2860$$

④ THE M
EQUATION

FOR LONG CI
CII

CALCULA

$$(i) \quad T =$$

$$T =$$

$$2860 -$$

$$2860$$

$$N = \frac{2}{-}$$

A COIL WOUND ARMATURE OPERATING IN A FIELD OF WEBER IS WOUND WITH 360 ARMATURE
 DETERMINE THE EXPRESSION OF TORQUE AS A
 SPEED IF $V_f = 250V$, $R_a = 0.1\Omega$

$$T = \frac{k_e k_t \Phi^2}{R_a} \text{ N}$$

$a = 2 \text{ m}$
 Simple wave
 $m = 1$
 $a = 2 \times 1 = 2$

$$\frac{4 \times 360}{60 \times 2} = 12$$

$$T = \frac{114.5 \times 0.01 \times 250}{0.1} - \frac{12 \times 114.5 \times (0.01)^2}{0.1} \text{ N}$$

$$T = 2860 - 1.38 \text{ N}$$

④ THE MOTOR HAS THE FOLLOWING CHARACTERISTICS
 EQUATION $T = 2860 - 1.38 \text{ N}$

FOR LOAD (i) $T = 50 + 1.25 \text{ N}$

(ii) $T = 50 + 6.25 \times 10^{-4} \text{ N}^2$

CALCULATE SPEED.

(i) $T = 2860 - 1.38 \text{ N}$

$$T = 50 + 1.25 \text{ N}$$

$$2860 - 1.38 \text{ N} = 50 + 1.25 \text{ N}$$

$$2860 - 50 = (1.38 + 1.25) \text{ N}$$

$$N = \frac{2810}{2.63} = 1068 \text{ rpm}$$

(ii) $T = 2$
 $T =$

$$2860 - 1.38 \text{ N} =$$

$$6.25 \times 10^{-4} \text{ N}^2$$

$$X = \frac{-B \pm}{A}$$

$$= \frac{-(1.38)}{1}$$

$$= \frac{-1.38}{1}$$

$$= \frac{-1.38}{1}$$

$$\frac{114.5 \times 0.01 \times 250}{0.1} - \frac{12 \times 114.5 \times (0.01)^2}{0.1} \text{ N}$$

$$2860 - 1.38 \text{ N}$$

MOTOR HAS THE FOLLOWING CHARACTERISTICS

$$T = 2860 - 1.38 \text{ N}$$

$$(i) T = 50 + 1.25 \text{ N}$$

$$(ii) T = 50 + 6.25 \times 10^{-4} \text{ N}^2$$

CALCULATE SPEED.

$$T = 2860 - 1.38 \text{ N}$$

$$T = 50 + 1.25 \text{ N}$$

$$2860 - 1.38 \text{ N} = 50 + 1.25 \text{ N}$$

$$2860 - 50 = (1.38 + 1.25) \text{ N}$$

$$\frac{2810}{2.63} = 1068 \text{ RPM}$$

$$(ii) T = 2860 - 1.38 \text{ N}$$

$$T = 50 + 6.25 \times 10^{-4} \text{ N}^2$$

$$2860 - 1.38 \text{ N} = 50 + 6.25 \times 10^{-4} \text{ N}^2$$

$$6.25 \times 10^{-4} \text{ N}^2 + 1.38 \text{ N} - 2810 = 0$$

$$A x^2 + B x + C = 0$$

$$x = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$

$$= \frac{-(1.38) \pm \sqrt{(1.38)^2 - 4 \times 6.25 \times 10^{-4} \times (-2810)}}{2 \times 6.25 \times 10^{-4}}$$

$$= \frac{-1.38 \pm \sqrt{1.9044 + 7.025}}{12.5 \times 10^{-4}}$$


$$= \frac{-1.38 \pm 2.92}{12.5 \times 10^{-4}} = \frac{-1.38 + 2.92}{12.5 \times 10^{-4}}$$

$$\frac{1.6}{12.5 \times 10^{-4}} = 1280 \text{ RPM}$$

(5) THE RESISTANCE OF A 240 V DC MOTOR ASSUMING THAT THE CURRENT AT FULL LOAD IS 200% OF THE FULL LOAD CURRENT AND THE FULL LOAD SPEED IS 1280 RPM DETERMINE (a) THE ARMATURE CIRCUIT RESISTANCE (b) THE NUMBER OF STAGES IN THE STARTER EACH STAGE



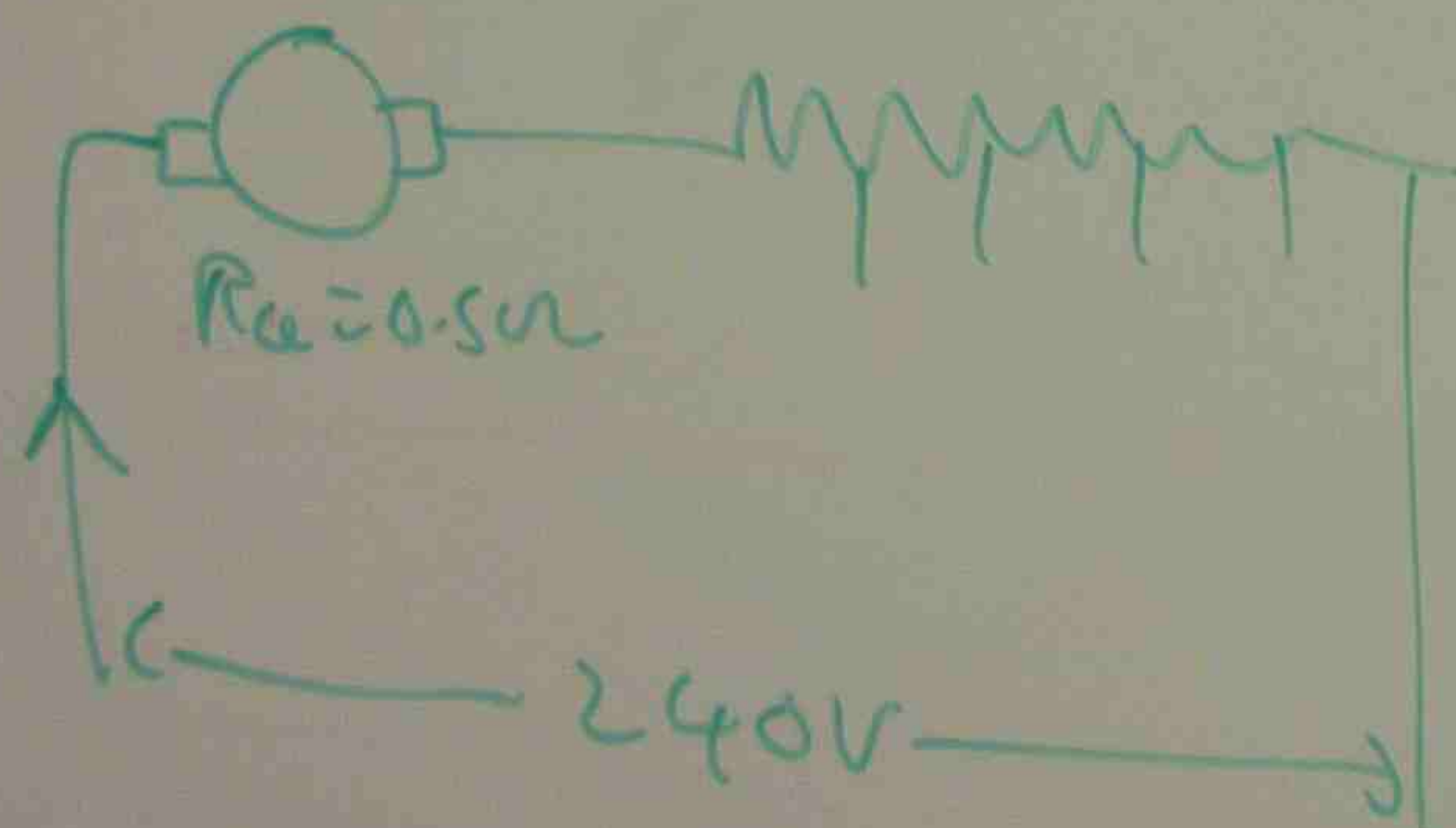- 9) THE RESISTANCE OF AN ARMATURE OF A 240 V DC SHUNT MOTOR IS 0.5Ω . ASSUMING THAT IT IS REQUIRED THAT THE CURRENT AT STARTING BE LIMITED TO 200% OF THE FULL LOAD CURRENT AND THE FULL LOAD CURRENT IS 15 amp DETERMINE (a) TOTAL RESISTANCE OF THE ARMATURE CIRCUIT AT STARTING (b) THE NUMBER OF STUDS ON THE STARTER (c) THE RESISTANCE BETWEEN EACH STUD.



$$I_s = 200\% I_{FL} \\ = 2 \times 15 = 30 \text{ A}$$

$$(a) R_1 = \frac{V_t}{I_s} = \frac{240}{30} = 8 \Omega$$

$$\left(\frac{I_s}{I_R} \right)^n = \frac{R_1}{R_a}$$

$$\left(\frac{30}{15} \right)^n = \frac{8}{0.5}$$

$$2^n = 16$$

$$2^n = 2^4$$

$$n = 4$$

$$(b) \text{ NO. OF STUDS} = n + 1 = 4 + 1 = 5$$

$$R_2 = R_1 \times \frac{20}{5}$$

$$= 8 \times \frac{20}{5} = 4 \Omega$$

$$R_3 = R_2 \times \frac{20}{5}$$

$$= 4 \times \frac{20}{5} = 2 \Omega$$

$$R_4 = R_3 \times \frac{20}{5}$$

$$= 2 \times \frac{20}{5} = 1 \Omega$$

$$R_5 = R_4 \times \frac{20}{5}$$

$$= 1 \times \frac{20}{5} = 0.5 \Omega$$

$$R_1 = R_1 - R_2 = 8 - 4 = 4 \Omega$$

$$R_2 = R_2 - R_3 = 4 - 2 = 2 \Omega$$

$$R_3 = R_3 - R_4 = 2 - 1 = 1 \Omega$$

$$R_4 = R_4 - R_5 = 1 - 0.5 = 0.5 \Omega$$

$$R_{total} = 4 + 1 + 0.5$$