
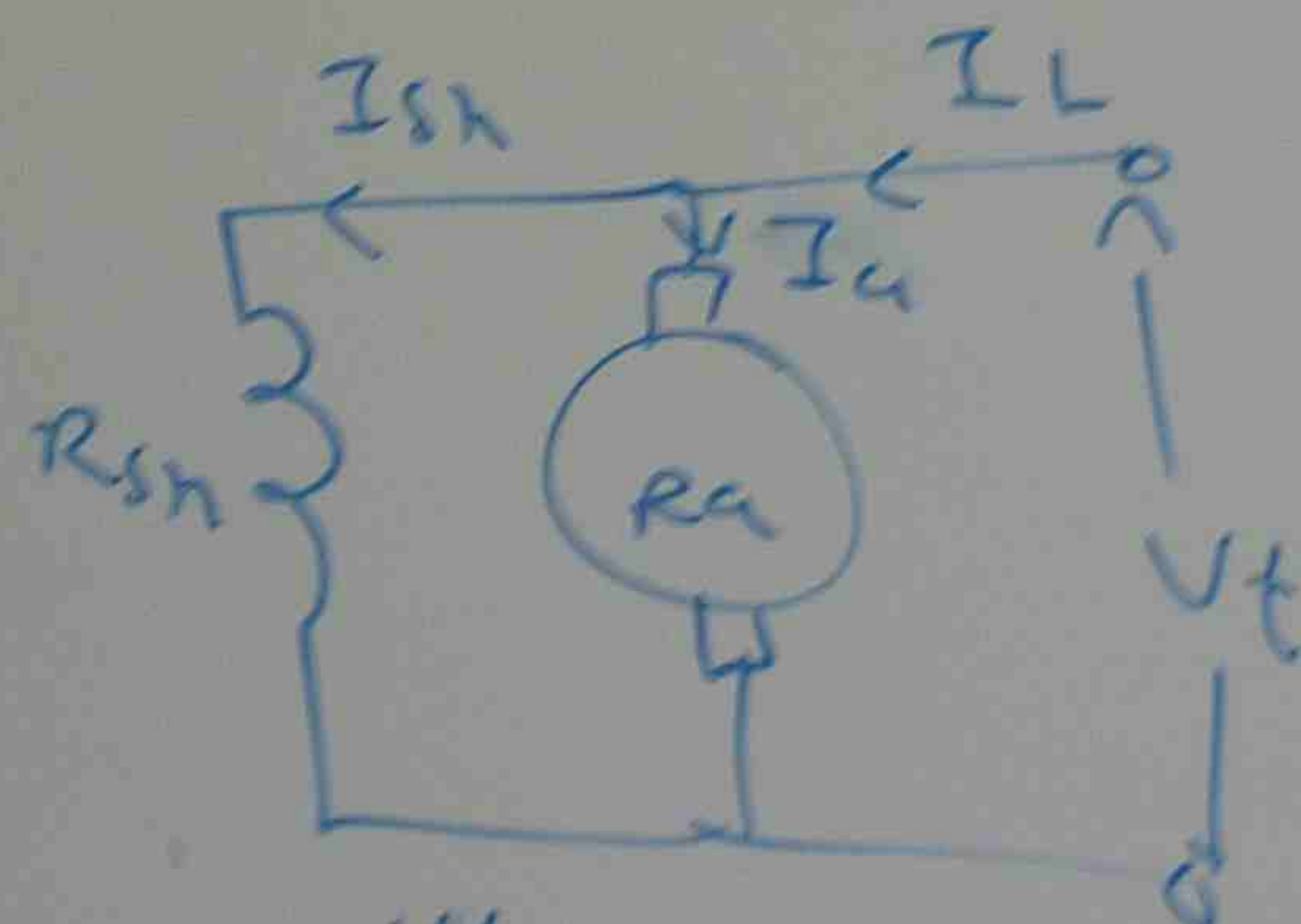


MAXIMUM EFFICIENCY

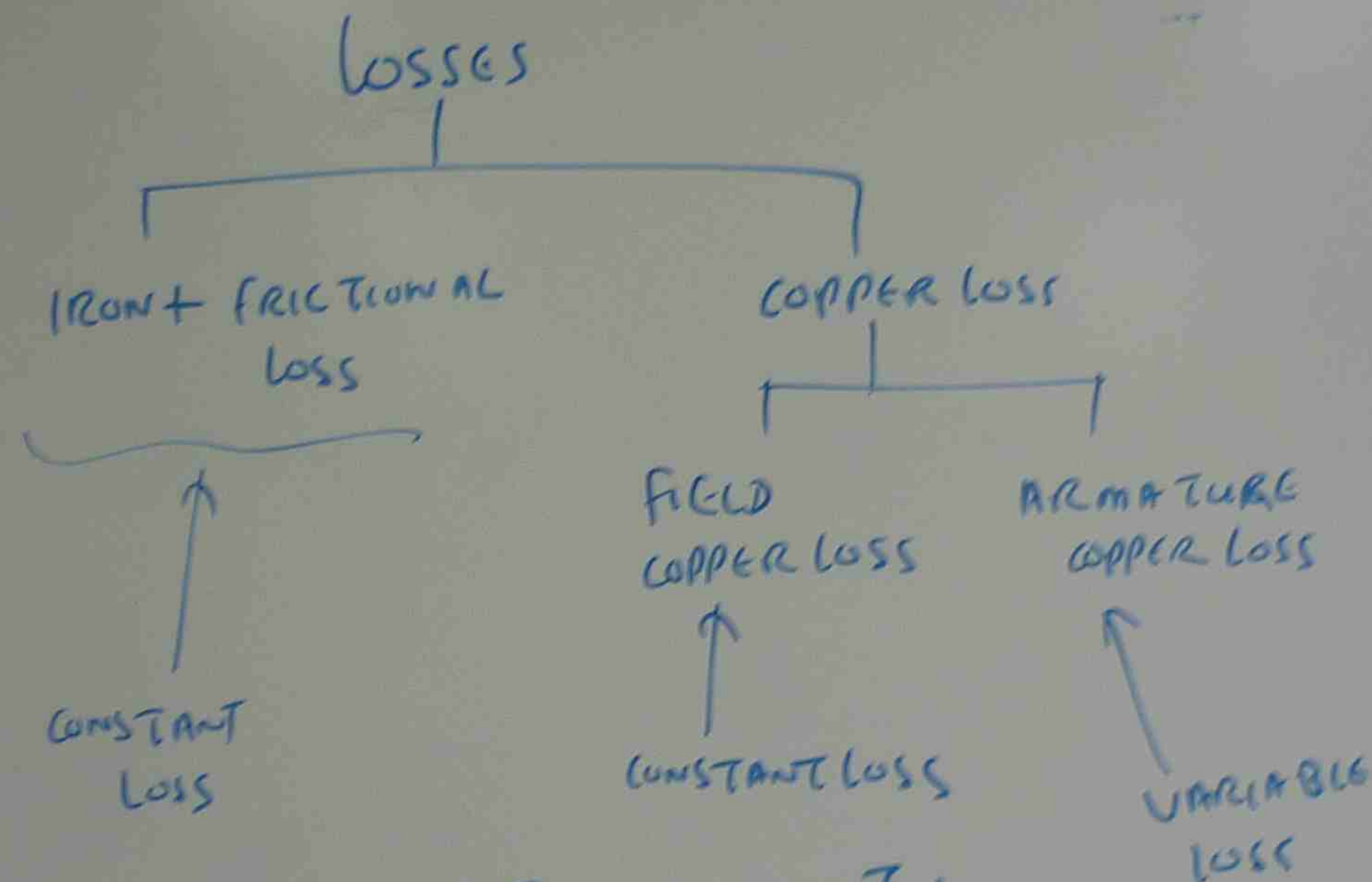

$$I_{sh} = \frac{V_t}{R_{sh}}$$

SO LONG AS V_t IS CONSTANT

I_{sh} IS CONSTANT & $I_{sh}^2 R_{sh}$

IS CONSTANT.

I_a DEPENDS ON

CONSTANT LOSSES

VARIABLE LOSSES

MAXIMUM EFF

IS EQUAL TO


SHUNT MAG

$V_t R_{sh}$

CONST

TOTAL LOSS

cy

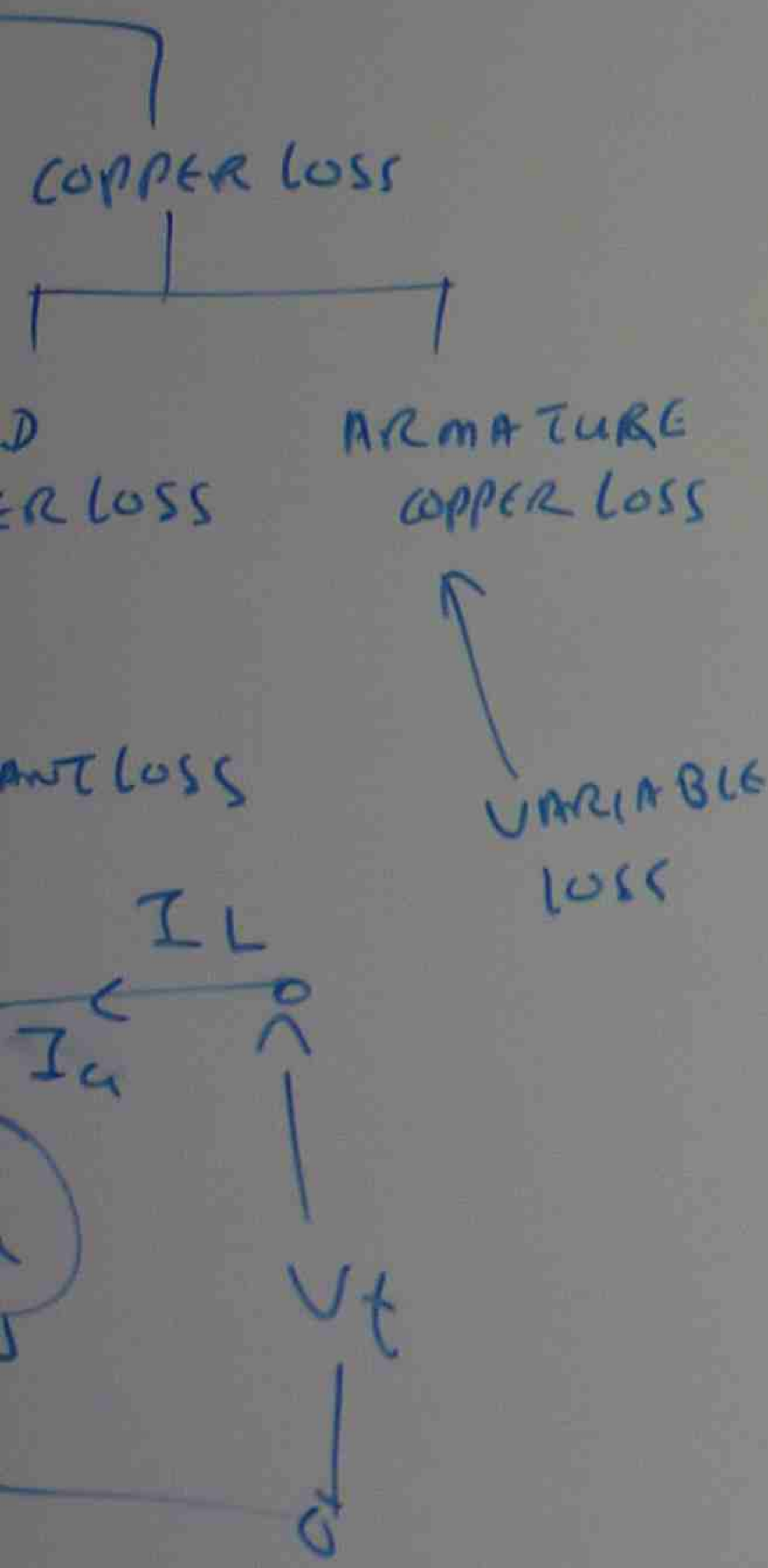

I_a DEPENDS ON LOAD CONDITION

CONSTANT LOSSES = IRON + FRICTIONAL LOSSES + SHUNT FIELD COPPER LOSS

VARIABLE LOSSES = ARMATURE COPPER LOSS + SERIES FIELD COPPER LOSS

MAXIMUM EFFICIENCY OCCURS WHEN CONSTANT LOSS IS EQUAL TO VARIABLE LOSS.

SHUNT MACHINE

VARIABLE LOSS = $I_a^2 R_a$

CONSTANT LOSS = VARIABLE LOSS = $I_a^2 R_a$

TOTAL LOSSES = VARIABLE LOSS + CONSTANT LOSS
 $= I_a^2 R_a + I_a^2 R_a = 2 I_a^2 R_a$

SO LONG AS V_t IS CONSTANT
 I_{sh} IS CONSTANT & $I_{sh}^2 R_{sh}$ IS CONSTANT.

MAXIMUM EFFICIENCY

Ex A 60 KW
 RESISTANCE OF
 EFFICIENCY 91
 (a) TOTAL LOSS
 (b) STRAY POWER

$$\text{MAXIMUM EFFICIENCY} = \frac{\text{OUT PUT POWER}}{\text{IN PUT POWER}} \times 100$$

$$= \frac{\text{OUT PUT POWER}}{\text{OUTPUT POWER} + \text{TOTAL LOSSES}} \times 100$$

$$\eta_{\max} = \frac{V_t I_L}{V_t I_L + 2 I_a^2 R_a} \times 100$$

Ex A 60 KW, 250 V SHUNT GENERATOR HAS AN ARMATURE CIRCUIT RESISTANCE OF 0.05Ω , FIELD RESISTANCE OF 50Ω AND A MAXIMUM EFFICIENCY 91%. CALCULATE

- (a) TOTAL LOAD FOR WHICH THE EFFICIENCY IS APPROXIMATELY A MAXIMUM
 (b) STRAY POWER LOSS

$$\eta_{\max} = \frac{V_t I_L}{V_t I_L + 2 I_a^2 R_a} \times 100$$

$$91 = \frac{V_t I_L}{V_t I_L + 2 I_a^2 R_a} \times 100$$

SHUNT FIELD
COPPER LOSS

ARMATURE FIELD
COPPER LOSS

CONSTANT LOSS

$$W = I_a^2 R_a$$

CONSTANT LOSS

$$= 2 I_a^2 R_a$$

$$R_{sh} = 50 \Omega$$


$$91 =$$

$$I_a = I$$

$$I_s$$

$$I_a$$

$$0.4$$

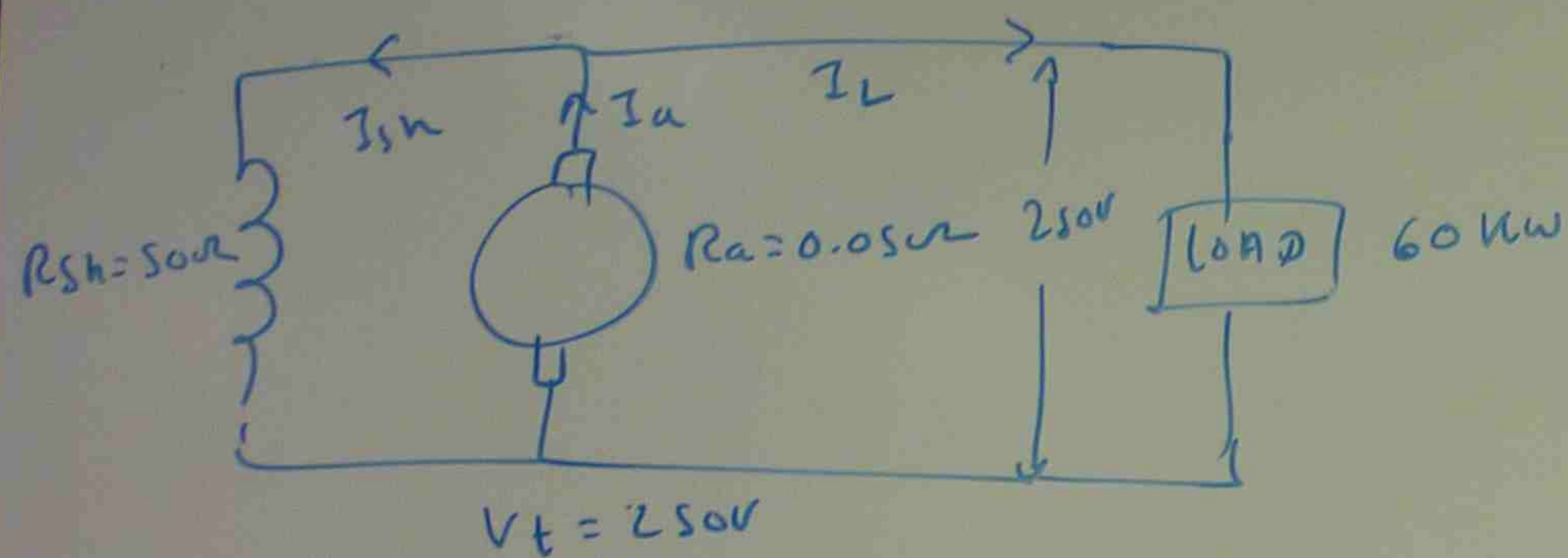

$$\eta = \frac{250 I_L}{250 I_L + 2 I_a^2 \times 0.05} \times 100$$

$$I_a = I_L + I_{sh}$$

$$I_{sh} = \frac{V_t}{R_{sh}} = \frac{250}{50} = 5 \text{ Amp}$$

$$I_a = I_L + 5$$

$$0.91 = \frac{250 I_L}{250 I_L + 2 \times (I_L + 5)^2 \times 0.05}$$

$$0.91 = \frac{250 I_L}{250 I_L + 0.1 (I_L^2 + 10 I_L + 25)}$$

$$0.91 = \frac{250 I_L}{250 I_L + 0.1 I_L^2 + I_L + 2.5}$$

$$0.91 (250 I_L + 0.1 I_L^2 + I_L + 2.5) = 250 I_L$$

$$227.5 I_L + 0.091 I_L^2 + 0.91 I_L + 2.275 = 250 I_L$$

$$0.091 I_L^2 - 21.59 I_L + 2.275 = 0$$

$$A x^2 + B x + C = 0$$

$$x = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$

$$I_L = \frac{-(-21.59) \pm \sqrt{(-21.59)^2 - 4 \times 0.091 \times 2.275}}{2 \times 0.091}$$

$$= 247.2 \text{ Amp.}$$

$$\frac{I_L + 5}{I_L + 5} = \frac{I_L^2 + 5 I_L}{5 I_L + 25}$$

$$1(I_L^2 + 10I_L + 25)$$

$$\frac{\begin{array}{r} I_L + 5 \\ I_L + 5 \\ \hline I_L^2 + 5I_L \\ 5I_L + 25 \\ \hline I_L^2 + 10I_L + 25 \end{array}}$$

$$I_L^2 + I_L + 2.5$$

$$I_L^2 + I_L + 2.5 = 250 I_L$$

$$0.91 I_L^2 + 0.91 I_L + 2.275 = 250 I_L$$

$$0.91 I_L + 2.275 = 0$$

$$x + c = 0$$

$$= \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$

$$\frac{-2.275 \pm \sqrt{(-2.275)^2 - 4 \times 0.91 \times 2.275}}{2 \times 0.91}$$

2 Amp.

$$\text{STRAY loss} = I_a^2 R_a - V_t \times I_{\text{field}}$$

$$I_a = I_L + I_{sh} = 247.2 + 5 = 252.2 \text{ Amp}$$

$$I_{\text{field}} = I_{sh} = 5 \text{ Amp}$$

$$\text{STRAY loss} = I_a^2 R_a - V_t I_{sh}$$

$$= (252.2)^2 \times 0.05 - 250 \times 5$$

$$= 1800 \text{ WATT.}$$

$$\text{STRAY LOSS} = I_a^2 R_a - V_t \times I_{\text{field}}$$

$$I_a = I_b + I_{sh} = 247.2 + 5 = 252.2 \text{ Amp}$$

$$I_{\text{field}} = I_{sh} = 5 \text{ amp}$$

$$\begin{aligned} \text{STRAY LOSS} &= I_a^2 R_a - V_t I_{sh} \\ &= (252.2)^2 \times 0.05 - 250 \times 5 \\ &= 1800 \text{ WATT} \end{aligned}$$

MACHINE TEMPERATURE RISE

MACHINE TEMPERATURE RISE CAN BE MEASURED

- By
- (a) THERMOMETER
 - (b) EMBEDDED THERMOCOUPLE (OR) THERMISTOR
 - (c) COMPUTATION FROM HOT AND COLD RESISTANCE

$$\frac{R_F}{R_{RT}} = \frac{234.5 + T_F}{234.5 + T_{RT}}$$

R_F = FINAL RESISTANCE

R_{RT} = RESISTANCE AT ROOM TEMPERATURE

T_F = FINAL TEMPERATURE

T_{RT} = ROOM TEMPERATURE (25°C)

Ex

THE RESISTANCE OF AN ARMATURE WINDING AT 25°C WAS FOUND TO BE 0.26Ω . AFTER A HEAT RUN, IT BECOMES 0.296Ω .

CALCULATE TEMPERATURE RISE OF THE WINDING.

$$T_{RT} = 25^{\circ}\text{C}, \quad R_{RT} = 0.26\Omega$$
$$R_F = 0.296\Omega$$
$$T_F = ?$$

$$\frac{R_F}{R_{RT}} = \frac{234.5 + T_F}{234.5 + T_{RT}}$$

$$\frac{0.296}{0.26} = \frac{234.5 + T_F}{234.5 + 25}$$

$$\frac{0.296}{0.26} (234.5 + 25) - 234.5 = T_F$$

$$T_F = 61^{\circ}\text{C}$$

$$\text{TEMPERATURE RISE} = T_F - T_{RT} = 61 - 25 = 36^{\circ}\text{C}$$

ANALY

ROTATION

- (a) B
- (b) W
- (c) B
- (d) H
- (e) -

HYSTERESIS

- DEPENDS ON

- FREQUENCY

- FLUX

- MASS

WINDING AT 25°C WAS FOUND TO
IT BECOMES 0.296Ω .
THE WINDING.

0.26Ω

0.296Ω

$s = T_f$

G/c

$G/25 = 360$

ANALYSIS OF POWER LOSSES IN DC MACHINE

ROTATIONAL LOSSES

- (a) BEARING FRICTION
- (b) WIND FRICTION
- (c) BRUSH FRICTION ————— DEPENDS ON KIND OF BRUSH
- (d) HYSTERESIS
- (e) IRON EDDY CURRENT LOSSES

HYSTERESIS LOSS

- DEPENDS ON QUALITY OF IRON
- FREQUENCY OF AC CURRENT

$$f = \frac{P \times N}{120} \text{ Hz}$$

- FLUX DENSITY IN ARMATURE CORE
- MASS OF IRON

$$P_h = K$$

$$K_h = c$$

$$f = f$$

$$B = m$$

$$m =$$

EDDY CURRENT



DC MACHINE

DEPENDS ON KIND OF BRUSH

ASSES

IRE CORE

$$P_h = K_h f B^{\frac{1.6}{m}} \text{ WATT}$$


K_h = CONSTANT DEPENDING ON MATERIAL & UNIT USED

f = FREQUENCY (Hz)


B = MAXIMUM FLUX DENSITY (T)

m = MASS OF CORE (kg)

EDDY CURRENT PATHS IN SOLID CORE

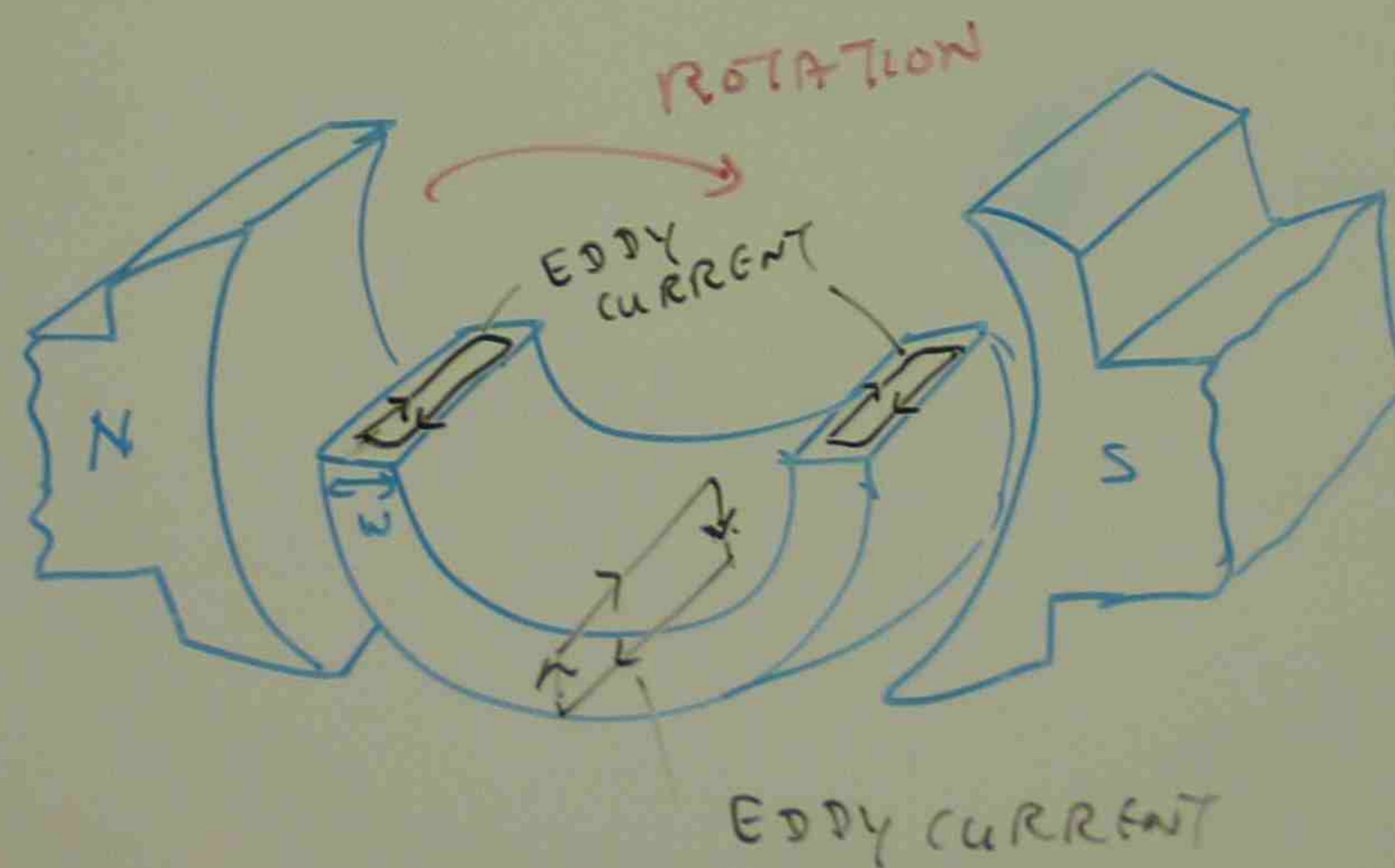

Eddy cur

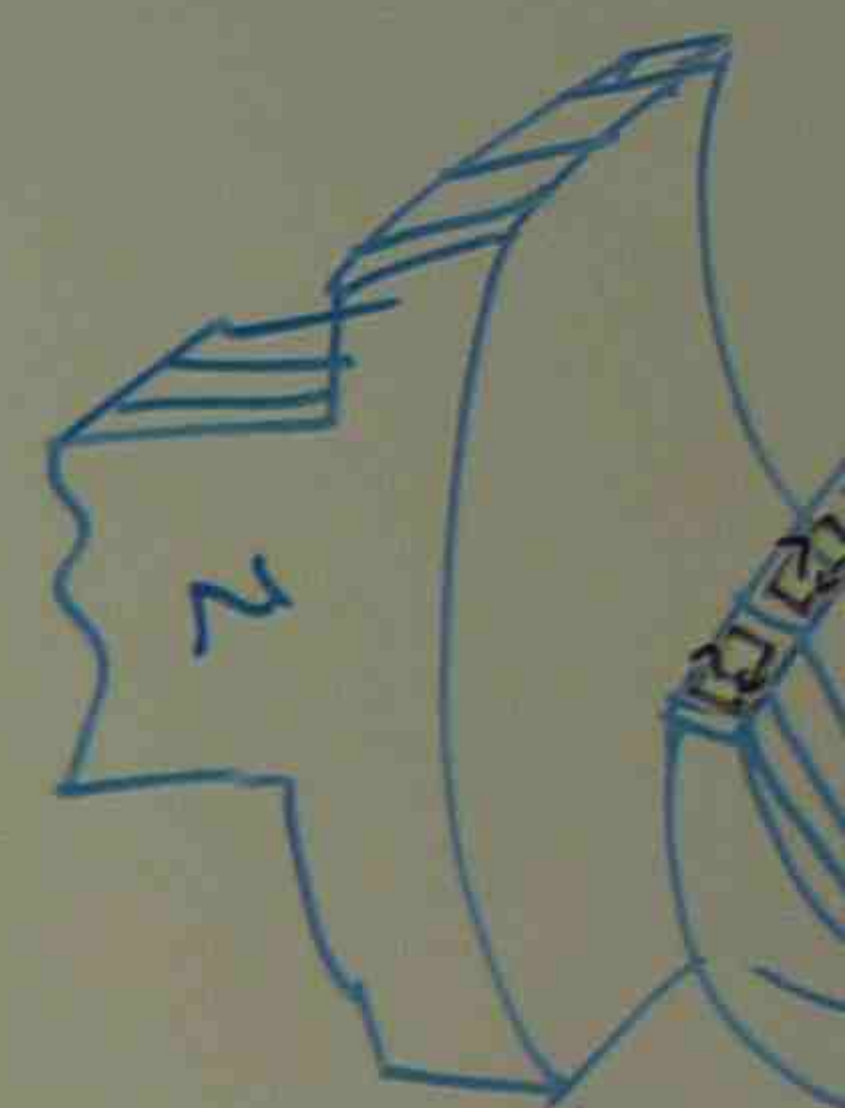

THE EDDY

- FREQUENCY

(OR) FLUX

- THE THICKNESS

LAMINATIONS

- THE FLUX DENSITY

- THE VOLUME

WATT

ON MATERIAL & UNIT USED

Hz)

Density (T)


(kg)

SOLID CORE



CURRENT

EDDY CURRENT PATHS IN LAMINATION

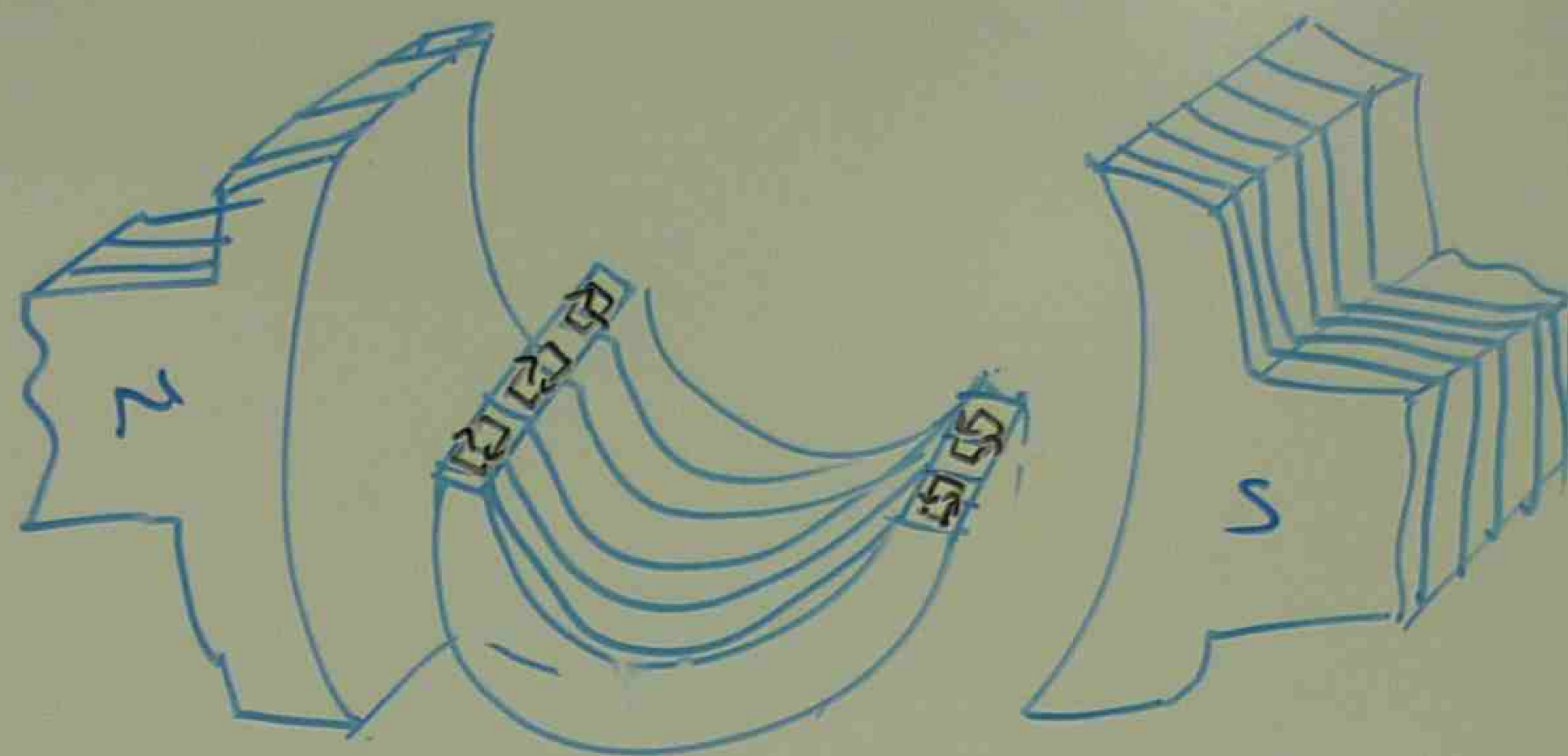

THE EDDY CURRENT LOSS DEPENDS ON

- FREQUENCY OF THE ALTERNATING CURRENT (OR) FLUX IN ARMATURE CORE
- THE THICKNESS OF THE ARMATURE CORE LAMINATION
- THE FLUX DENSITY IN THE CORE
- THE VOLUME OF THE IRON.

$$P_E = K_e$$

P_E = EDDY CURRENT LOSS

K_e = CONSTANT

THE IRON

THE FACTOR


f = FREQUENCY

t = THICKNESS

B = MAXIMUM FLUX DENSITY

V = VOLUME OF IRON

PATHS IN LAMINATION

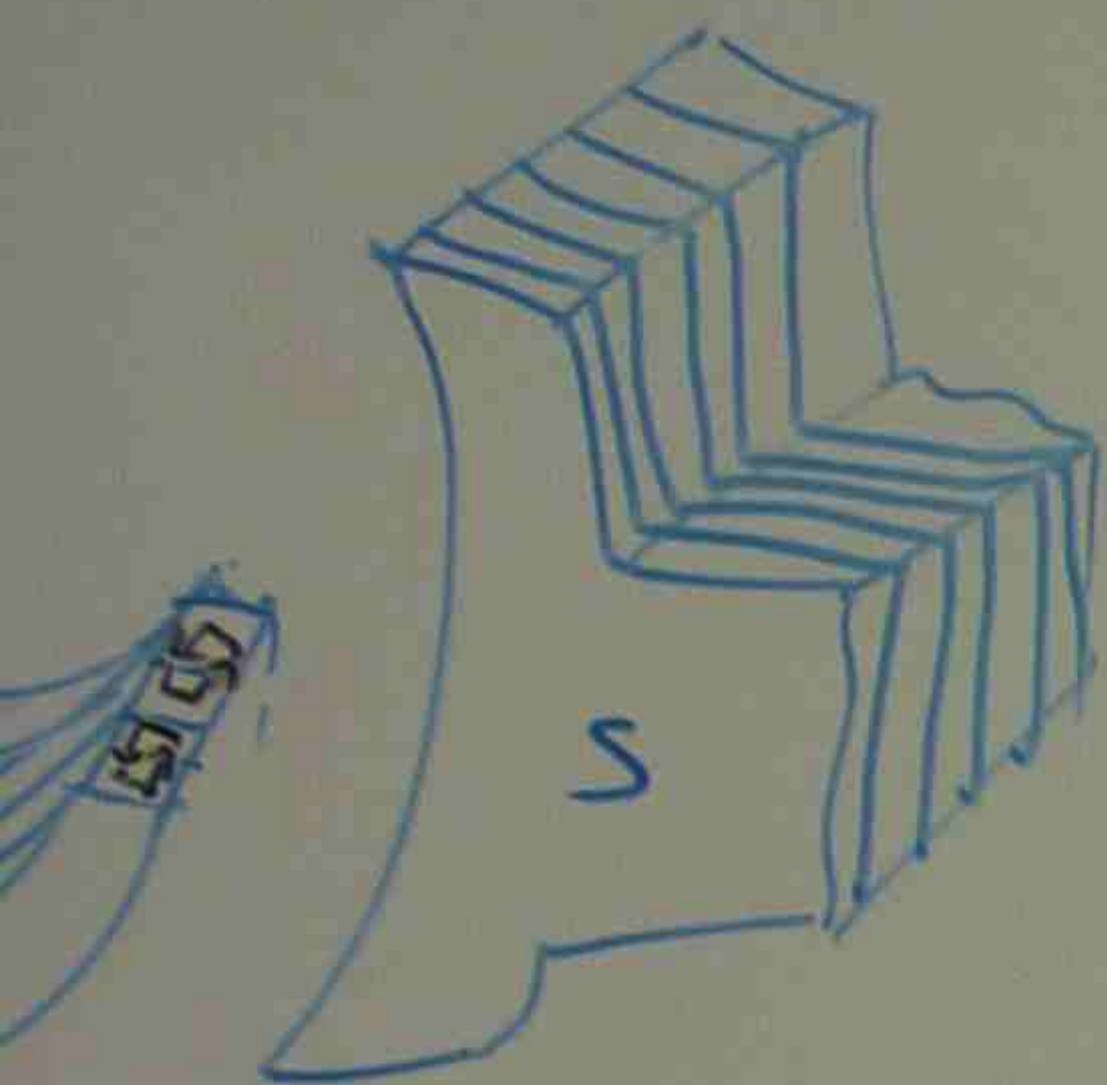

EDDY CURRENT LOSS DEPENDS ON
 F THE ALTERNATING CURRENT
 ARMATURE CORE
 S OF THE ARMATURE CORE
 SITY IN THE CORE
 OF THE IRON.

$$P_E = K_e f^2 t^2 B^2 V$$

WATT

P_E = EDDY CURRENT LOSS WATT

K_e = CONSTANT DEPENDING ON THE RESISTIVITY OF
 THE IRON AND DIMENSIONS EMPLOYED FOR
 THE FACTOR

f = FREQUENCY Hz

t = THICKNESS OF LAMINATION m

B = MAXIMUM FLUX DENSITY IN CORE T

V = VOLUME OF IRON IN CORE

STRAY LOSS = I_a^2

$I_a = I_b +$

$I_{field} = I_s$

STRAY LOSS = I_a^2

$= (2$

$=$

MACHINE

MACHINE TEM

By (a) THERE

(b) Emf

(c) con

R

C MACHINE

DEPENDS ON KIND OF BRUSH

$$P_h = K_h f B^{1.6} m \text{ WATT}$$


K_h = CONSTANT DEPENDING ON MATERIAL & UNIT USED

f = FREQUENCY (HZ)

B = MAXIMUM FLUX DENSITY (T)


m = MASS OF CORE (Kg)

EDDY CURRENT PATHS IN SOLID CORE

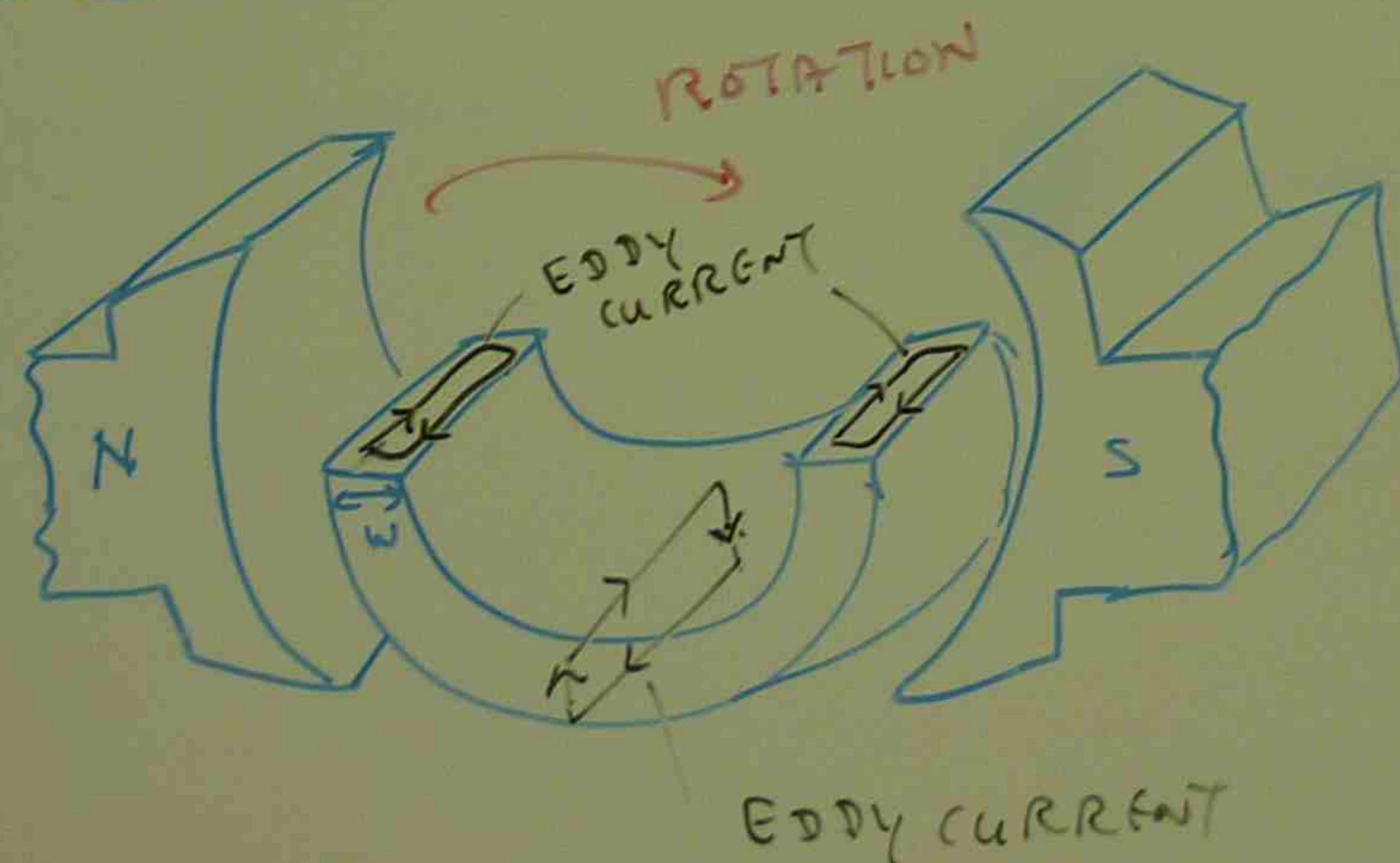

CORE

EDDY CURRENT PATHS

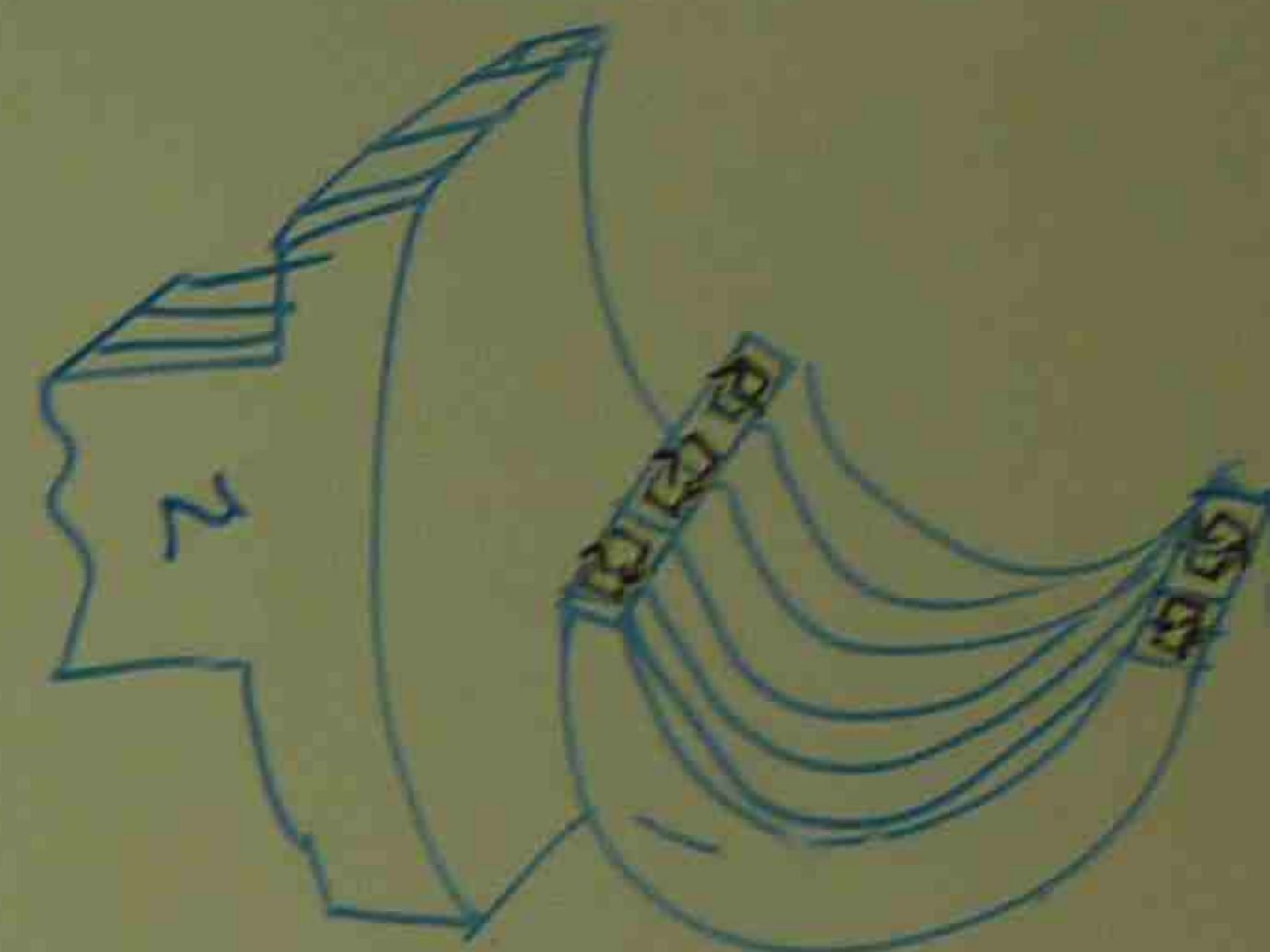

THE EDDY CURRENT

- FREQUENCY OF (OR) FLUX IN A
- THE THICKNESS OF LAMINATION
- THE FLUX DENSITY
- THE VOLUME OF

WATT


ON MATERIAL & UNIT USED

HZ)

DENSITY (T)


(Kg)

SOLID CORE

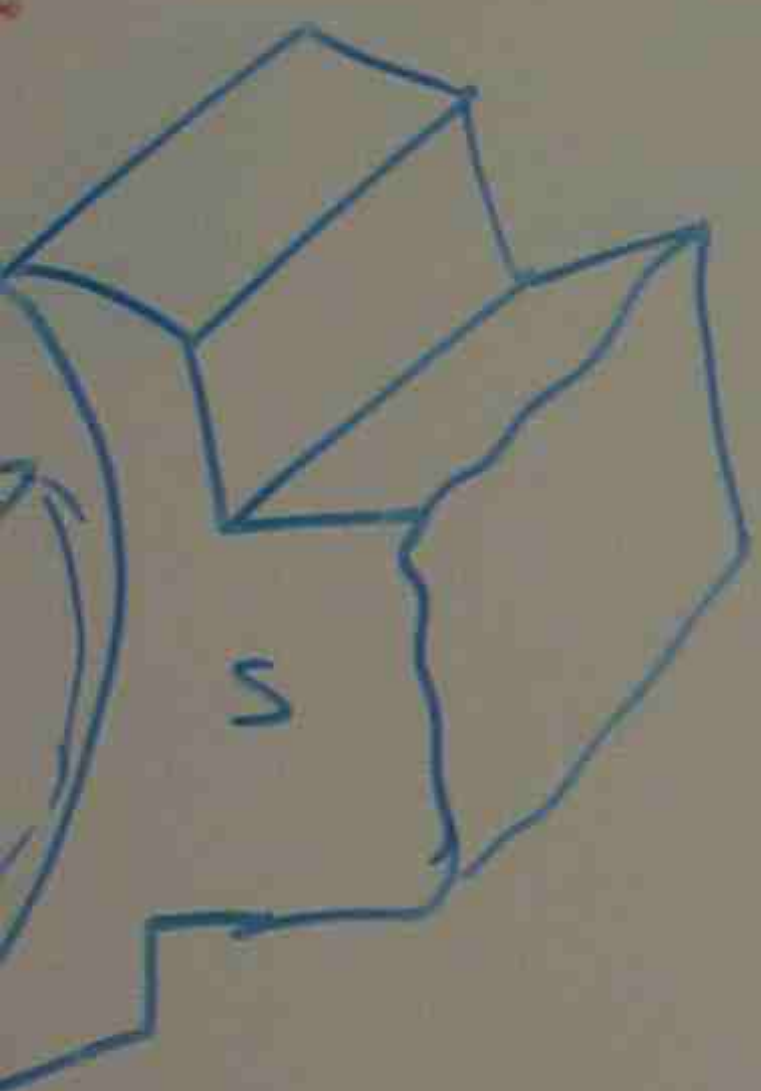

CURRENT

EDDY CURRENT PATHS IN LAMINATION

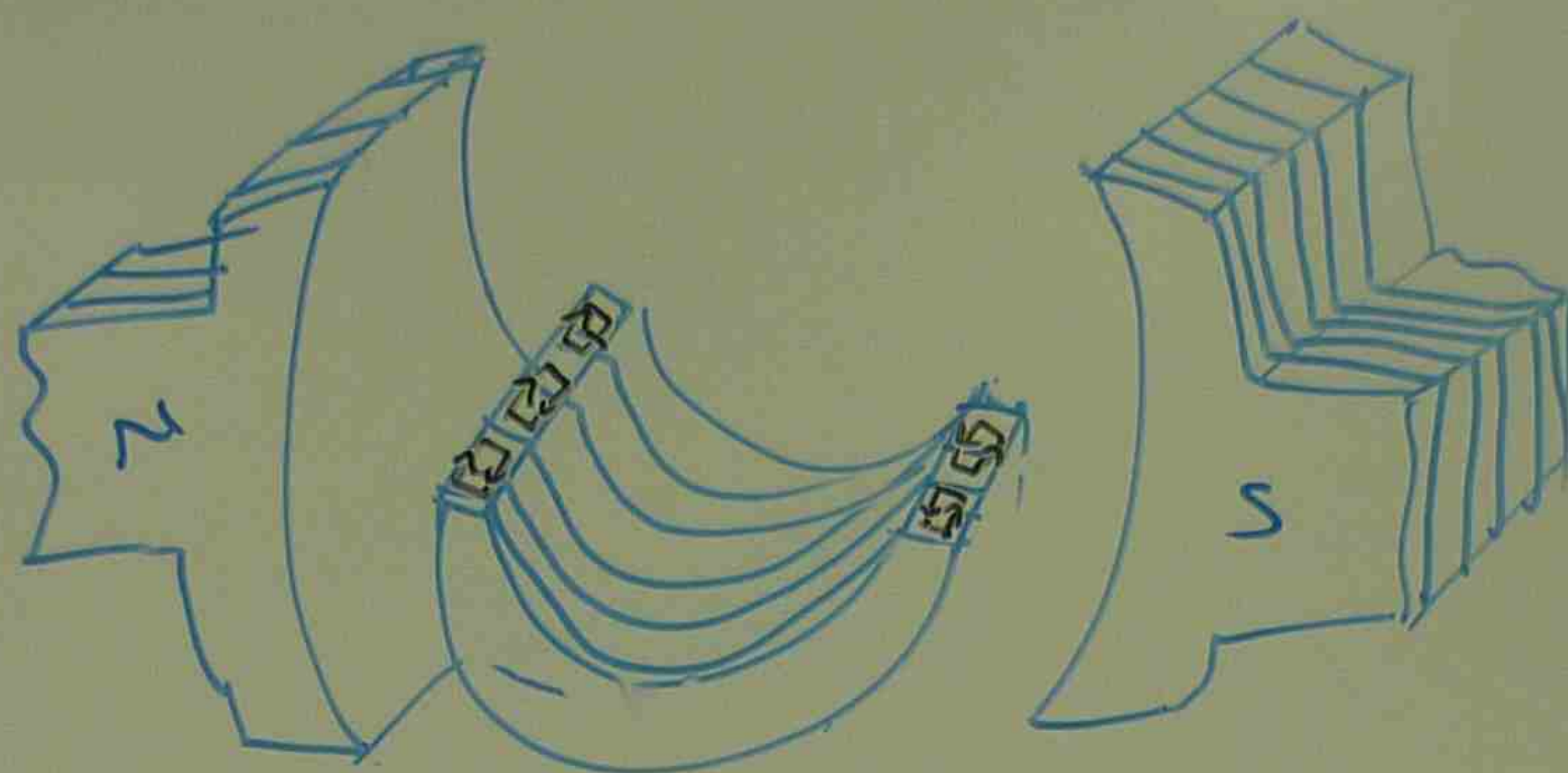

THE EDDY CURRENT LOSS DEPENDS ON

- FREQUENCY OF THE ALTERNATING CURRENT (OR) FLUX IN ARMATURE CORE
- THE THICKNESS OF THE ARMATURE CORE LAMINATION
- THE FLUX DENSITY IN THE CORE
- THE VOLUME OF THE IRON.

$$P_E = K_e f^2 t$$

P_E = EDDY CURRENT

K_e = CONSTANT DEPENDS ON THE IRON AND THE FACTOR

f = FREQUENCY

t = THICKNESS OF

B = MAXIMUM F

V = VOLUME OF

LOSS IN LAMINATION



Loss depends on
 the alternating current
 of the armature core
 in the core
 the iron.

$$P_E = K_e f^2 t^2 B^2 V$$

WATT

P_E = EDDY CURRENT LOSS WATT

K_e = CONSTANT DEPENDING ON THE RESISTIVITY OF
 THE IRON AND DIMENSIONS EMPLOYED FOR
 THE FACTOR

f = FREQUENCY Hz

t = THICKNESS OF LAMINATION mm

B = MAXIMUM FLUX DENSITY IN CORE T

V = VOLUME OF IRON IN CORE (m^3)

Ex CALCULATE EDDY
 LOSS IN CORE

$K_e = 3$, K_h

THICKNESS OF LAM

CORE FLUX DENSITY

VOLUME OF CORE

MASS OF CORE

$$P_h = K_h f^2 B^2 V$$

$$= 2 \times 60$$

$$= 120 \times 3$$

$$= 2388$$

$$= 2388$$

Ex CALCULATE EDDY CURRENT AND HYSTERESIS LOSSES FOR THE
GIVEN DC MACHINE

$$K_e = 3, \quad K_h = 2 \quad \text{FREQUENCY} = 60 \text{ Hz}$$

$$\text{THICKNESS OF LAMINATION} = 0.5 \text{ mm}$$

$$\text{CORE FLUX DENSITY} = 1.0 \text{ TESLA}$$

$$\text{VOLUME OF CORE} = 7 \text{ m}^3$$

$$\text{MASS OF CORE} = 50 \text{ kg}$$

$$P_h = K_h f^{1.6} B^2 m$$

$$= 2 \times 60 \times (1.0)^{1.6} \times 50$$

$$= 120 \times 39.8 \times 50$$

$$= 238800 \text{ WATT}$$

$$= 238.8 \text{ kW}$$

$$P_e = K_e f^2 B^2 V$$

$$= 3 \times (60)^2 \times (0.5 \times 10^{-3})^2 \times 100 \times 7$$

$$= 3 \times 3600 \times 0.25 \times 10^{-6} \times 100 \times 7$$

$$= 1890000 \times 10^{-6}$$

$$= 1.89 \text{ WATT}$$

PERCENTAGE VOLTAGE REGULATION

WHEN THE LOAD IS APPLIED ON A SELF-EXCITED SHUNT GENERATOR
THE TERMINAL VOLTAGE WILL DROP DUE TO THREE EFFECTS. THESE
ARE

- (1) THE DROP IN THE RESISTANCE OF THE ARMATURE WINDING
WHICH IS TERMED $I_a R_a$ DROP
- (2) THE EFFECT OF THE ARMATURE FIELD ON THE MAIN FIELD
WHICH WILL DECREASE THE EFFECTIVE FLUX
- (3) THE RESULTANT DROP IN (1) & (2)

$$\text{PERCENTAGE REGULATION} = \frac{E_g - V_{FL}}{V_{FL}} \times 100$$

V_{FL} = FULL LOAD RATED VOLTAGE

E_g = NO LOAD OPEN CIRCUIT
(GENERATED) VOLTAGE

Pb V_{FL}
REGU

% RE

Pb A 7
OF 47

SHUNT GENERATOR
EFFECTS. THESE

ATURE WINDING

THE MAIN FIELD
CUT

100

AGE

UT

E

Pb V_{FL} of a SHUNT GENERATOR IS 480 VOLT. WHAT IS PERCENTAGE REGULATION IF THE OPEN CIRCUIT VOLTAGE IS 510 V?

$$\begin{aligned}\% \text{ REGULATION} &= \frac{E_g - V_{FL}}{V_{FL}} \times 100 \\ &= \frac{510 - 480}{480} \times 100 \\ &= 6.89\%\end{aligned}$$

Pb A 75 kW 500 VOLT GENERATOR HAS A VOLTAGE REGULATION OF 4%. CALCULATE

(a) THE OPEN CIRCUIT VOLTAGE

(b) ASSUMING THE VOLTAGE VARIES UNIFORMLY BETWEEN

NO LOAD AND FULL LOAD CURRENT.

CALCULATE THE kW OUTPUT OF A TERMINAL VOLTAGE OF 510.

(a) $\% \text{ REG} =$

4 =

$$\frac{4 \times 500}{100} + 5$$

(b)

520V V_1

510V V_2



VOLT. WHAT IS PERCENTAGE
IS 510V?

$$(a) \quad \% REG = \frac{E_g - V_{FL}}{V_{FL}} \times 100$$

$$4 = \frac{E_g - 500}{500} \times 100$$


$$\frac{4 \times 500}{100} + 500 = E_g$$

$$E_g = 520V$$

(b)

520V V_1

510V V_2

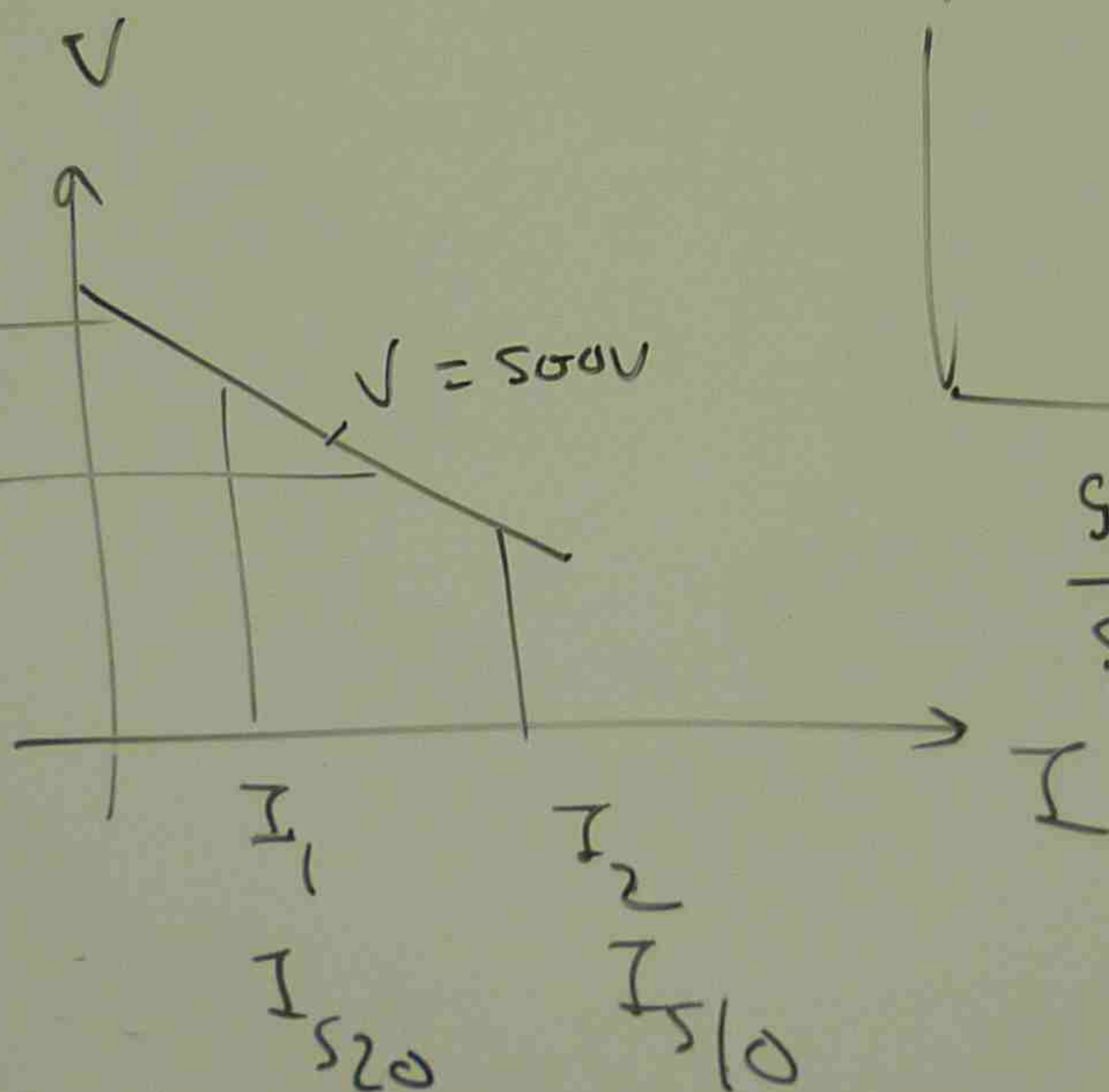

$$\frac{V_1 - V_2}{V_1 - V} = \frac{I_2}{I_1}$$

$$\frac{520 - 510}{520 - 500} = \frac{I_{510}}{I_{520}}$$

$V_1 = \text{NO LOAD VOLTAGE}$

$V = \text{FULL LOAD VOLTAGE}$

$V_2 = \text{ANY VOLTAGE}$

$$\frac{10}{20} = \frac{I_{510}}{I_{520}}$$

FULL LOAD CURRENT

$$\frac{10}{20} = \frac{I_{510}}{I_{520}}$$

$$I_{510} = 150$$

OUTPUT =

AS A VOLTAGE REGULATION

VARIES UNIFORMLY BETWEEN

CURRENT.

OUT OF A TERMINAL VOLTAGE

$$\frac{V_1 - V_2}{V_1 - V} = \frac{I_2}{I_1}$$

$$\frac{520 - 510}{520 - 500} = \frac{I_{510}}{I_{520}}$$

$V_1 = \text{NO LOAD VOLTAGE}$

$V = \text{FULL LOAD VOLTAGE}$

$V_2 = \text{ANY VOLTAGE}$

$$\frac{10}{20} = \frac{I_{510}}{I_{520}}$$

FULL LOAD CURRENT \Rightarrow TERMINAL VOLTAGE 500V

NO LOAD VOLTAGE 520V

$$\frac{10}{20} = \frac{I_{510}}{150}$$

$$I_{510} = 150 \times \frac{10}{20} = 75 \text{ Amp.}$$


$$\begin{aligned} \text{OUTPUT} &= V \times I = 510 \times 75 = 38250 \text{ W} \\ &= 38.25 \text{ kW} \end{aligned}$$

$$= \frac{\text{POWER}}{\text{TERMINAL VOLTAGE}}$$

$$= \frac{75 \times 10^3}{500}$$

$$I_{520} = 150 \text{ Amp.}$$

LOADING A

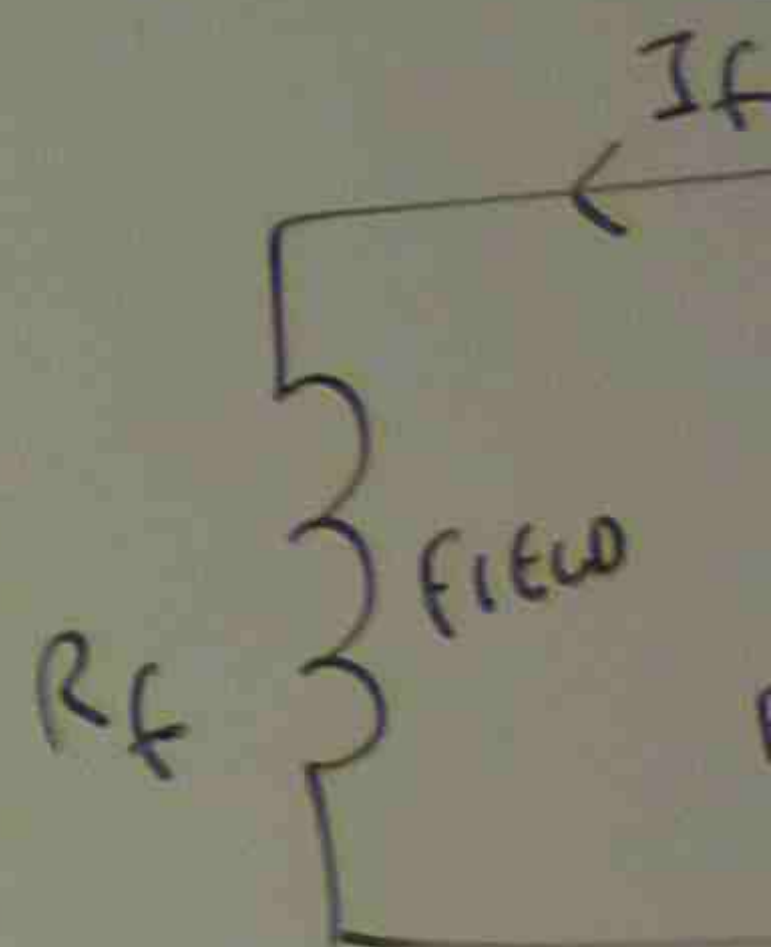


Eq

I

I

LOADING A GENERATOR

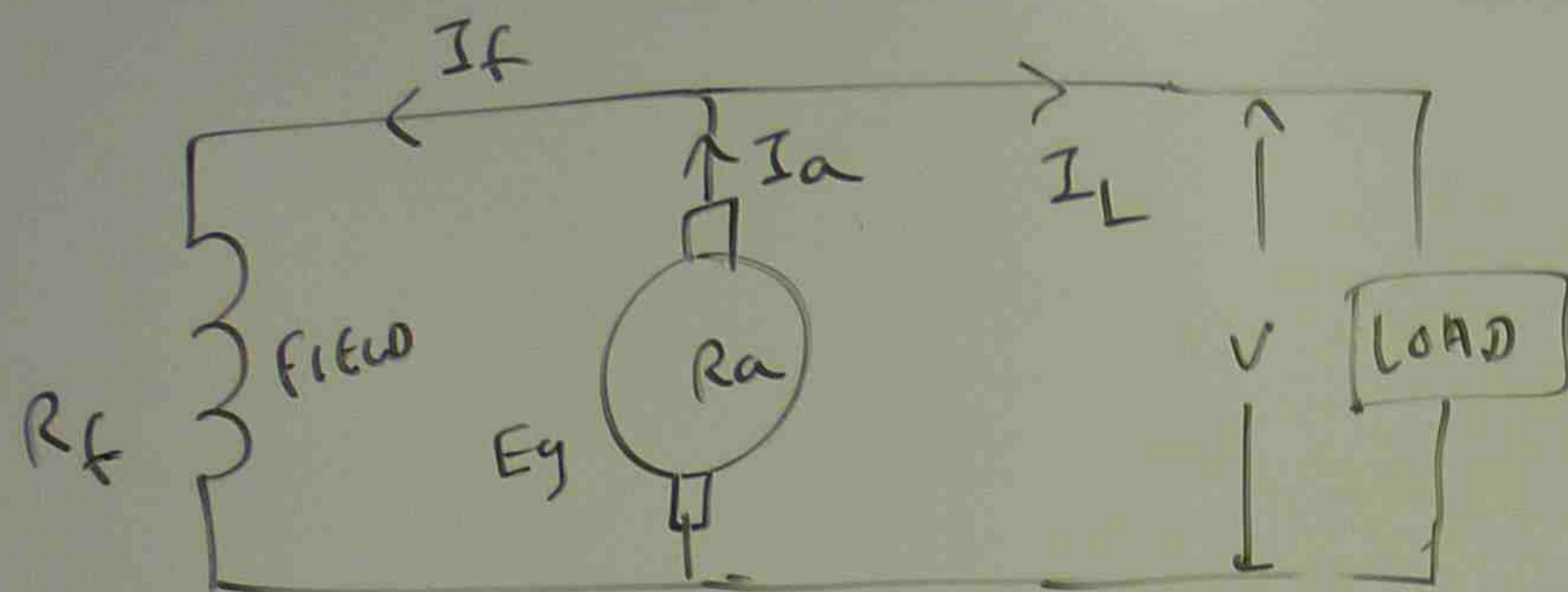

$$E_g = V + I_a R_a$$

$$I_a = I_L + I_f$$

$$I_f = \frac{V}{R_f}$$

GENERATED VOLTAGE EQUATION

$$E_g = \frac{\phi Z N}{60} \times \frac{P}{a}$$

E_g = GENERATED VOLTAGE (V)

ϕ = Flux (wb)

Z = NO. OF ARMATURE CONDUCTORS

N = SPEED (RPM)

P = NO. OF POLES

a = NO. OF ARMATURE PARALLEL PATHS

$$a = m \times P \quad \text{LAP}$$


$m = 1$ simplex

$= 2$ duplex

$= 3$ tripplex

$$a = m \times 2 \quad \text{WAVE}$$

LOADING A GENERATOR

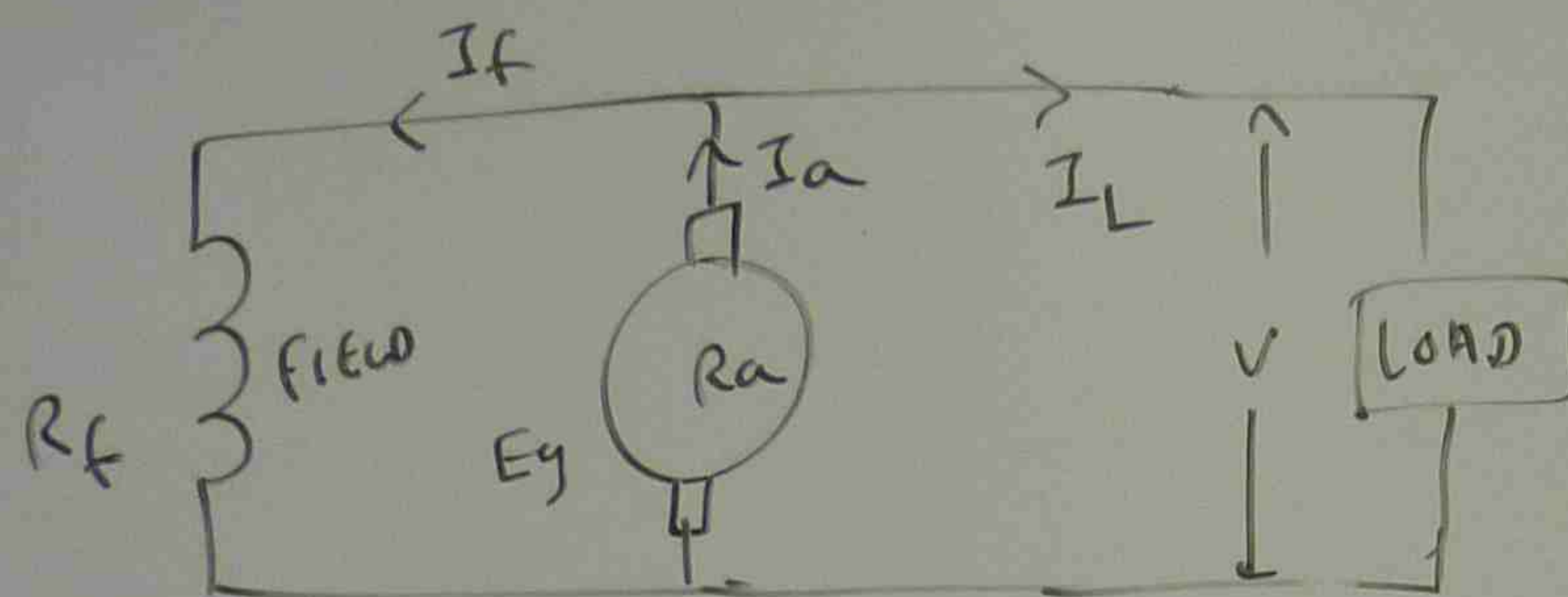

$$E_g = V + I_a R_a$$

$$I_a = I_L + I_f$$

$$I_f = \frac{V}{R_f}$$

GENERATED VOLTAGE EQUATION

$$E_g = \frac{\phi Z N}{60} \times \frac{p}{a}$$

E_g = GENERATED VOLTAGE (V)

ϕ = Flux (wb)

Z = NO. OF ARMATURE CONDUCTORS

N = SPEED (RPM)

p = NO. OF POLES

a = NO. OF ARMATURE PARALLEL PATHS

$$a = m \times p \quad \text{LAP}$$

$m = 1$ simplex

$= 2$ duplex

$= 3$ tripplex

$$a = m \times 2 \quad \text{WAVE}$$

POWER

TERMINAL
VOLTAGE

$$\frac{75 \times 10^3}{500}$$

150 Amp.


W

HW

TRANSFER FUNCTION OF SELF EXCITED MACHINE

$$E_g = \frac{\phi Z N}{60} \times \frac{P}{a}$$

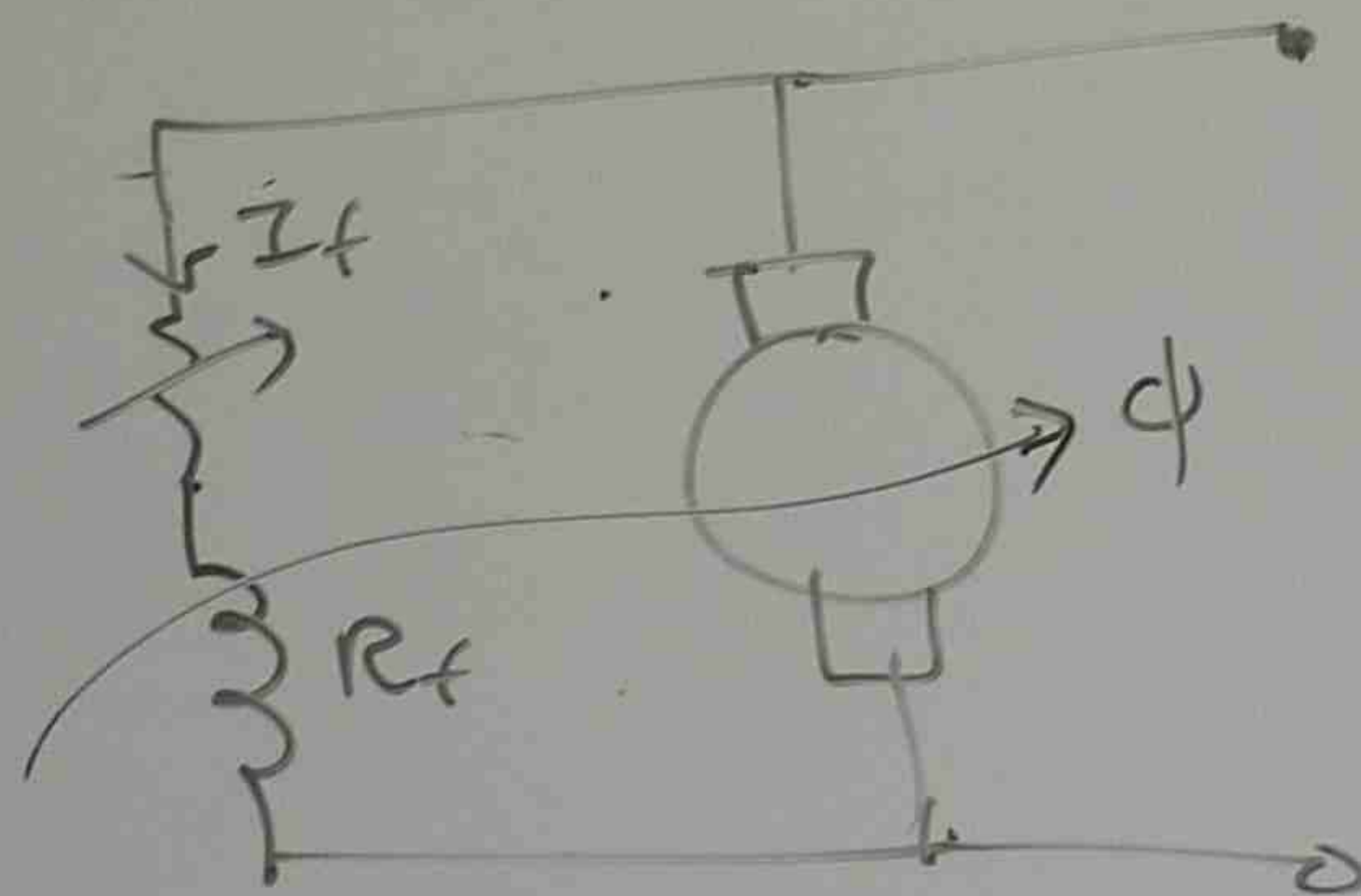ϕ = FIELD EXCITATION FLUX \propto FIELD CURRENT (I_f)



I_f →
FIELD EXCITATION
CURRENT

$$E_g = \frac{\phi Z N}{60} \times \frac{P}{a}$$

$$I_f \uparrow \rightarrow \phi \uparrow \rightarrow E_g \uparrow$$


By ADJUSTING THE FIELD RHEOSTAT, FIELD EXCITATION CURRENT IS VARIED AND IT AFFECTS THE GENERATED VOLTAGE E_g .

$$E_g = \frac{\phi Z N}{60} \times \frac{P}{a}$$


$$I_f \uparrow \rightarrow \phi \uparrow \rightarrow E_g \uparrow$$

CONSTANT (N)
(SPEED)

I_f
FIELD EXCITATION
CURRENT

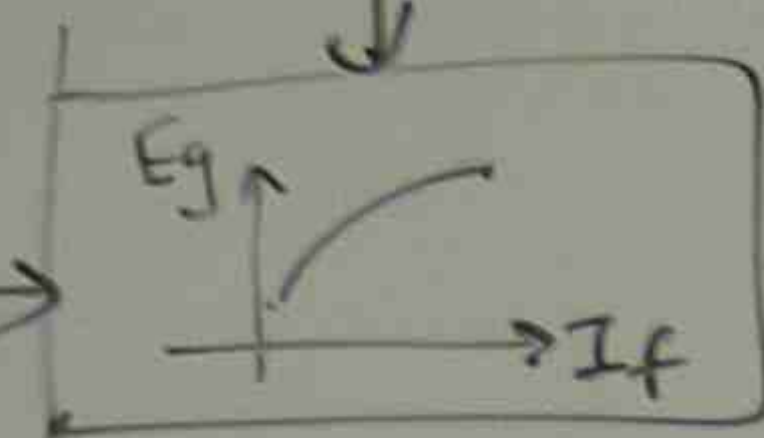

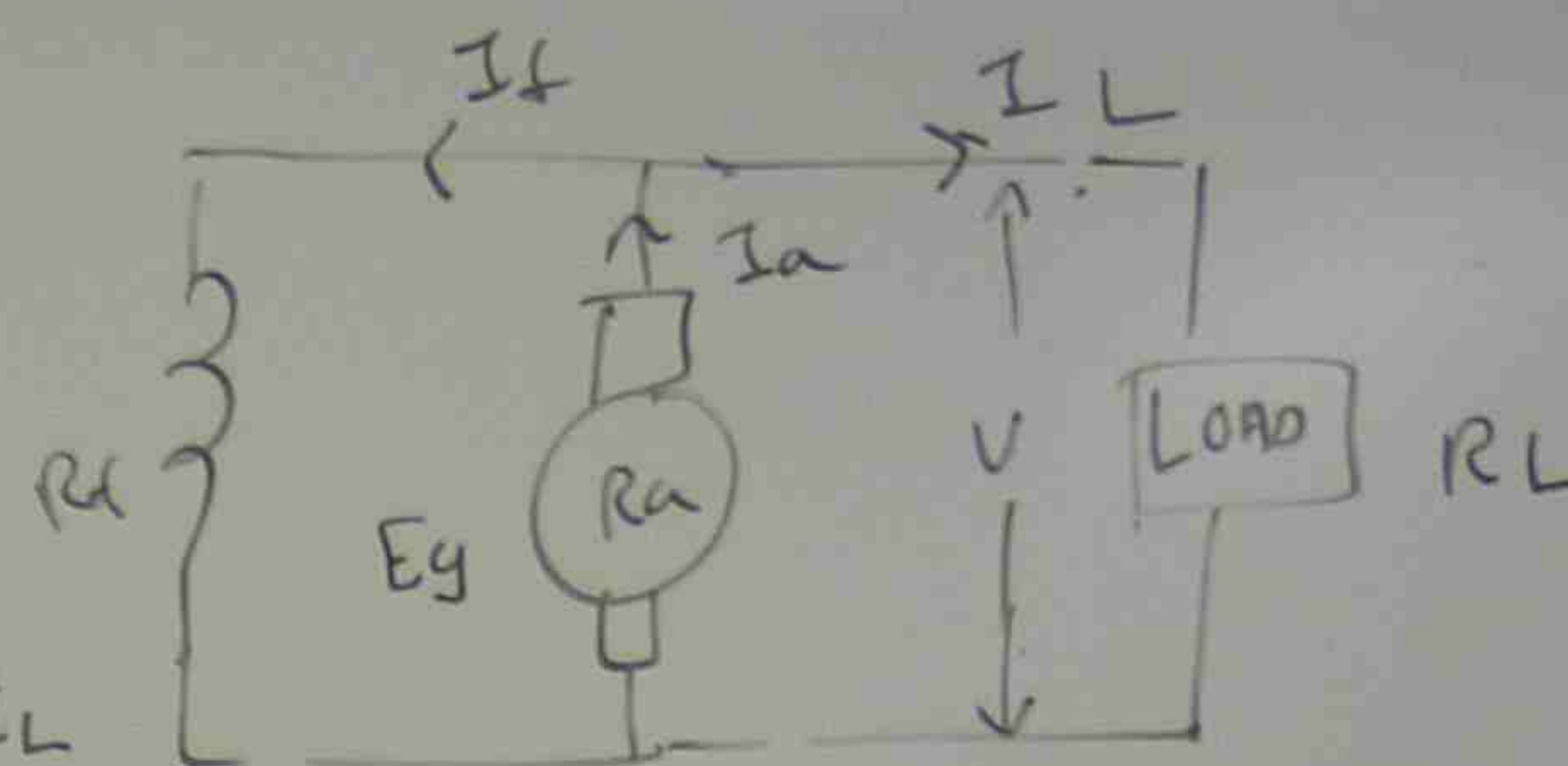TRANSFER FUNCTION
BLOCK DIAGRAM FOR
SELF EXCITED GENERATOR



$$E_g = V + I_a R_a$$

$$E_g - I_a R_a = V$$

$$\frac{V}{R_L} = I_L$$

$$I_a = I_L + I_f$$

$$I_a = \frac{V}{R_L} + I_f$$

FROM THE TRANSFER FUNCTION,

(1) CHANGE OF FIELD EXCITATION
CURRENT & SPEED AFFECTS E_g

(2) E_g IS RELATED TO TERMINAL
VOLTAGE V



(3) TERMINAL VOLTAGE " V "
IS RELATED TO LOAD
CURRENT I_L AND " I_f "
ARMATURE CURRENT I_a

$$(4) E_g - I_a R_a = V$$

TRANSFER FUNCTION OF SELF EXCITED MACHINE

$$E_g = \frac{\phi Z N}{60} \times \frac{P}{a}$$

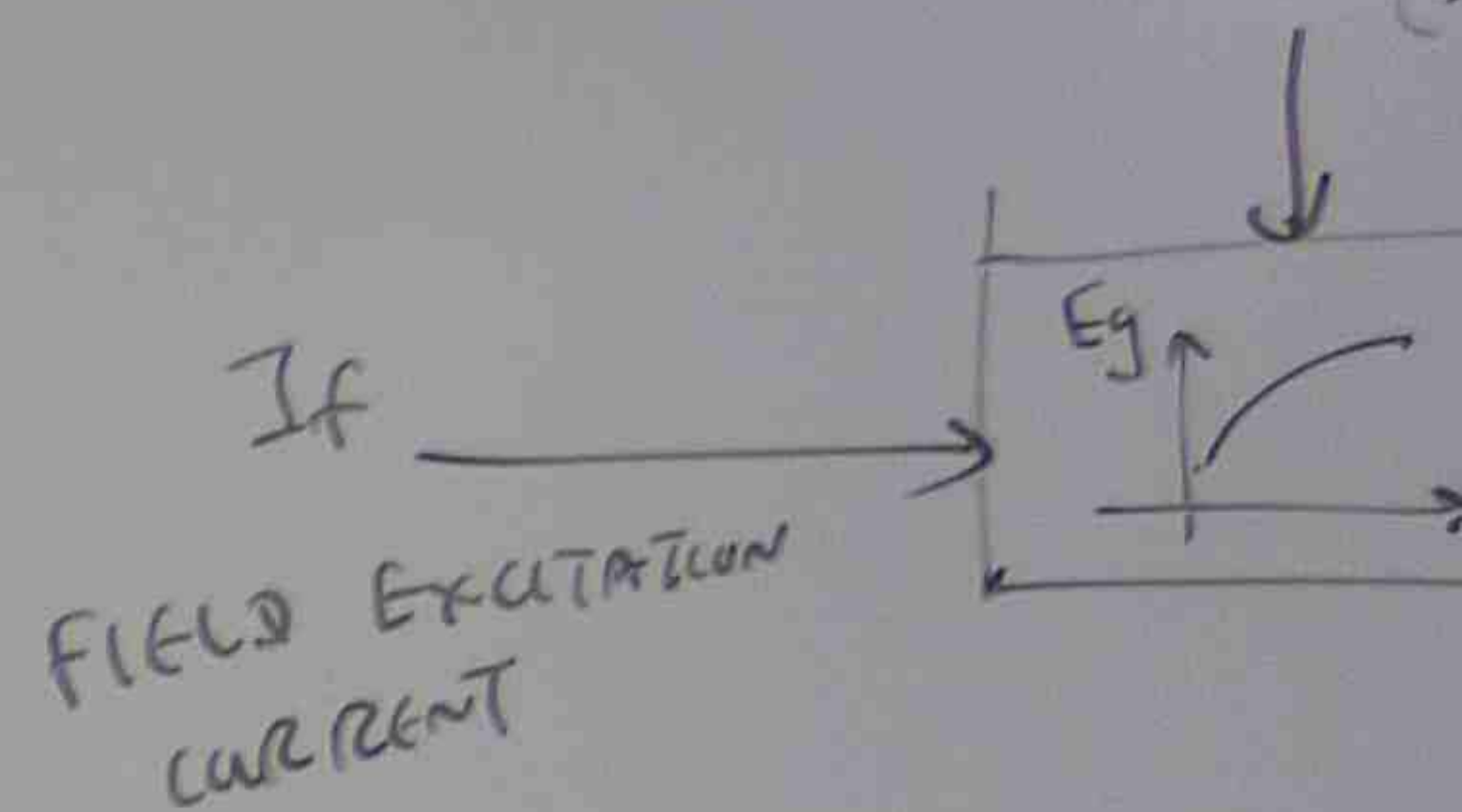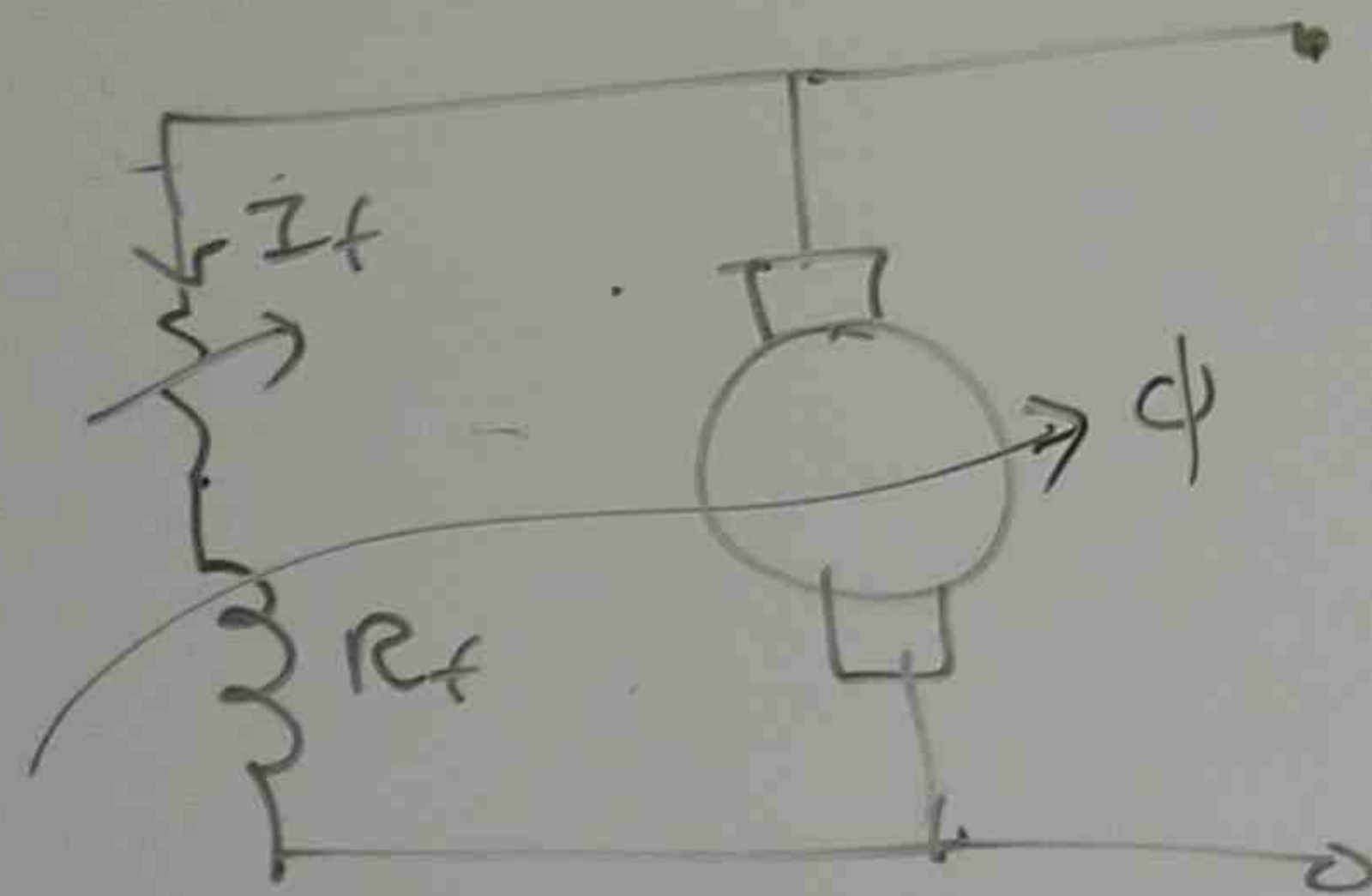ϕ = FIELD EXCITATION FLUX \propto FIELD CURRENT (I_f)



$$E_g = \frac{\phi Z N}{60} \times \frac{P}{a}$$

$$I_f \uparrow \rightarrow \phi \uparrow \rightarrow E_g \uparrow$$

By adjusting the field rheostat, field excitation current is varied and it affects the generated voltage E_g .


CONSTANT (N) (SPEED)

FIELD EXCITATION CURRENT I_f

$E_g = \frac{\Phi Z N}{60} \times \frac{P}{a}$

$I_f \uparrow \rightarrow \Phi \uparrow \rightarrow E_g \uparrow$

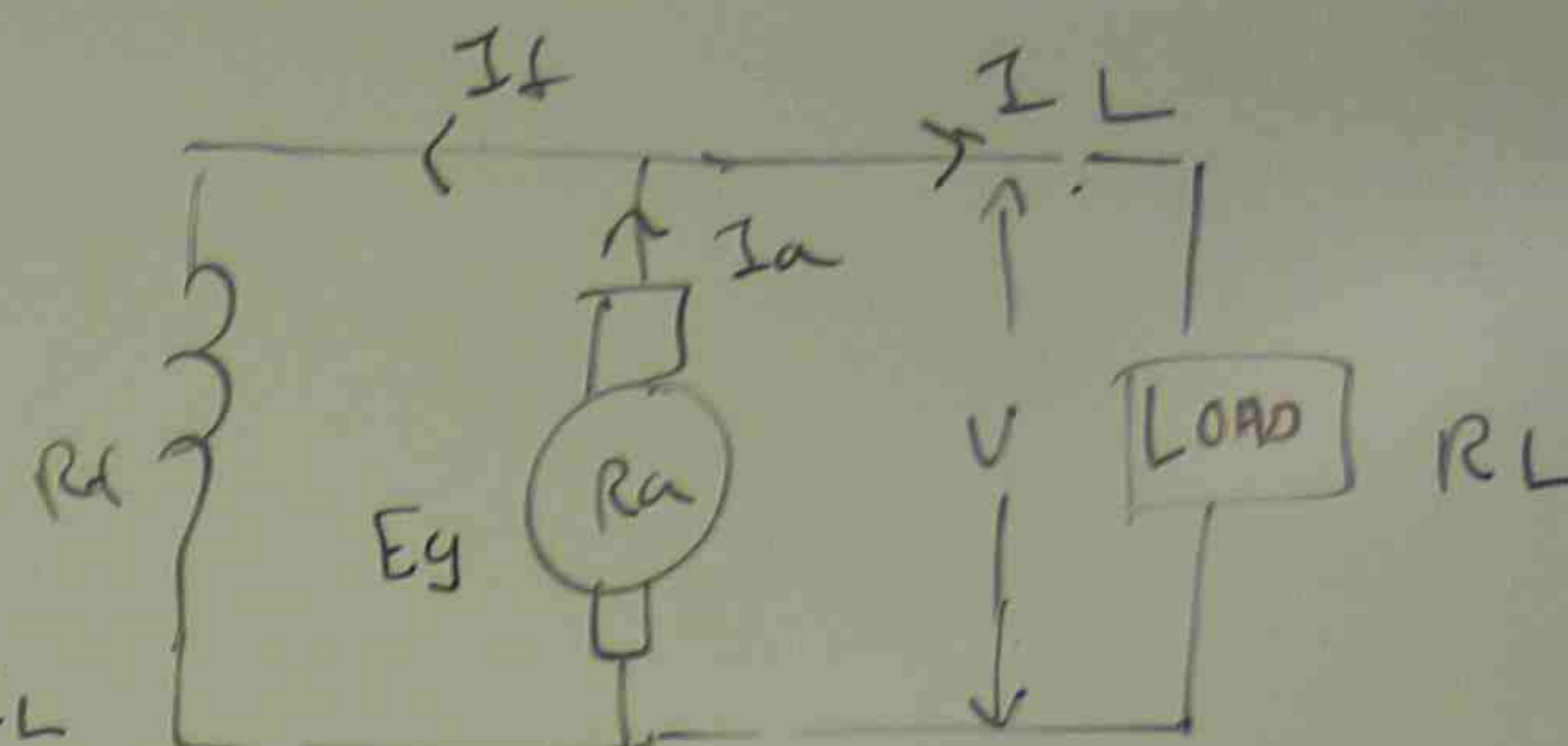TRANSFER FUNCTION
BLOCK DIAGRAM FOR
SELF EXCITED GENERATOR



$$E_g = V + I_a R_a$$

$$E_g - I_a R_a = V$$

$$\frac{V}{R_L} = I_L$$

$$I_a = I_L + I_f$$

$$I_a = \frac{V}{R_L} + I_f$$

FROM THE TRANSFER FUNCTION,

(1) CHANGE OF FIELD EXCITATION CURRENT & SPEED AFFECTS E_g



(2) E_g IS RELATED TO TERMINAL VOLTAGE V

(3) TERMINAL VOLTAGE " V " IS RELATED TO LOAD CURRENT I_L AND " " ARMATURE CURRENT I_a

$$(4) E_g - I_a R_a = V$$

Pb A 50 HP 250 V 1200 RPM SHUNT DC MOTOR HAS A RATED ARMATURE CURRENT OF 170 AMP AND RATED FIELD CURRENT OF 5 A. WHEN THE ROTOR IS BLOCKED, THE ARMATURE VOLTAGE 10V PRODUCES A 170A CURRENT FLOW AND FIELD VOLTAGE 250V PRODUCES A FIELD CURRENT FLOW OF 5A. AT NO LOAD WITH TERMINAL VOLTAGE EQUAL TO 240V, THE ARMATURE CURRENT IS EQUAL TO 13.2 AMP, FIELD CURRENT 4.8A. MOTOR SPEED IS 1150 RPM.

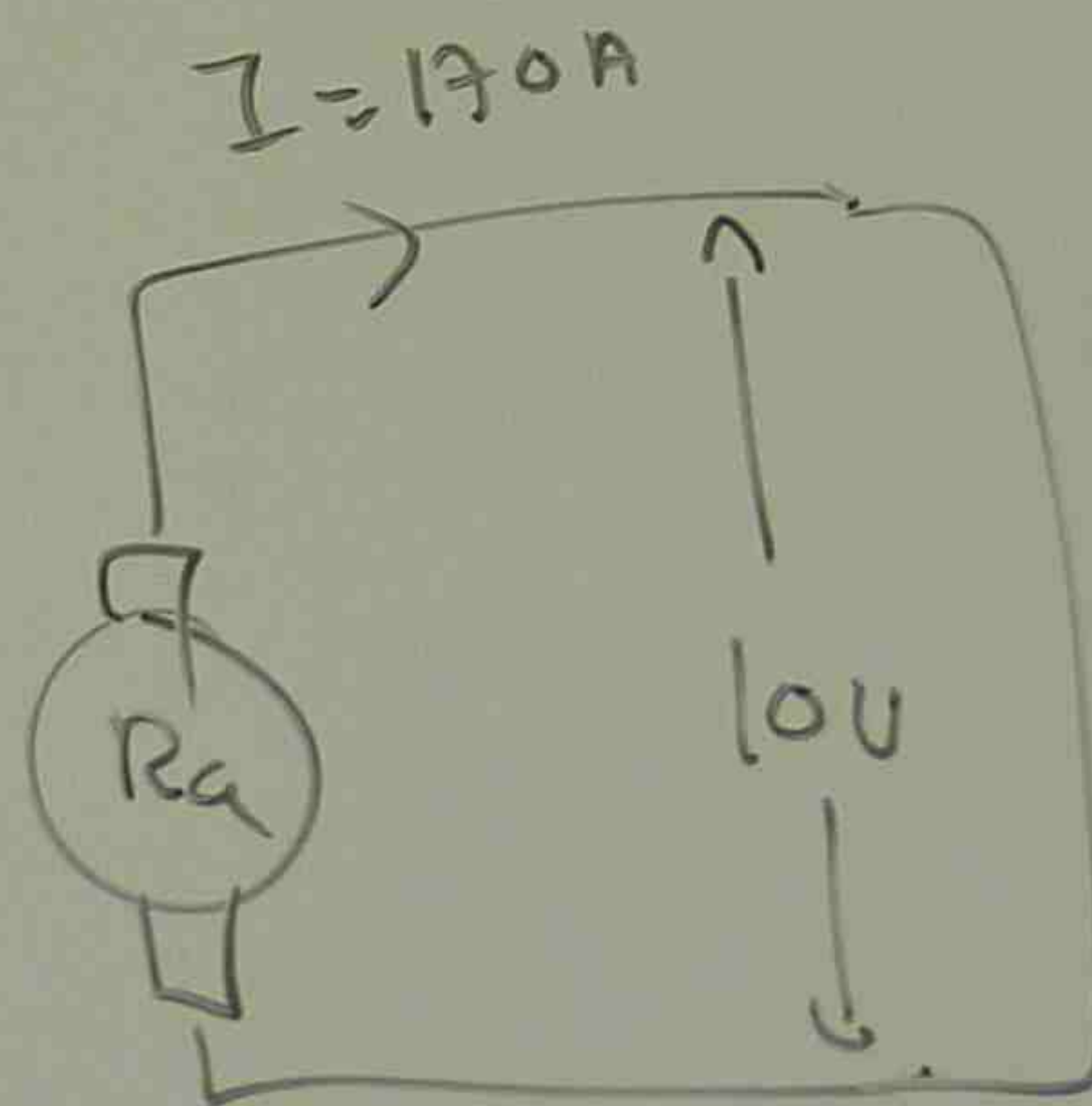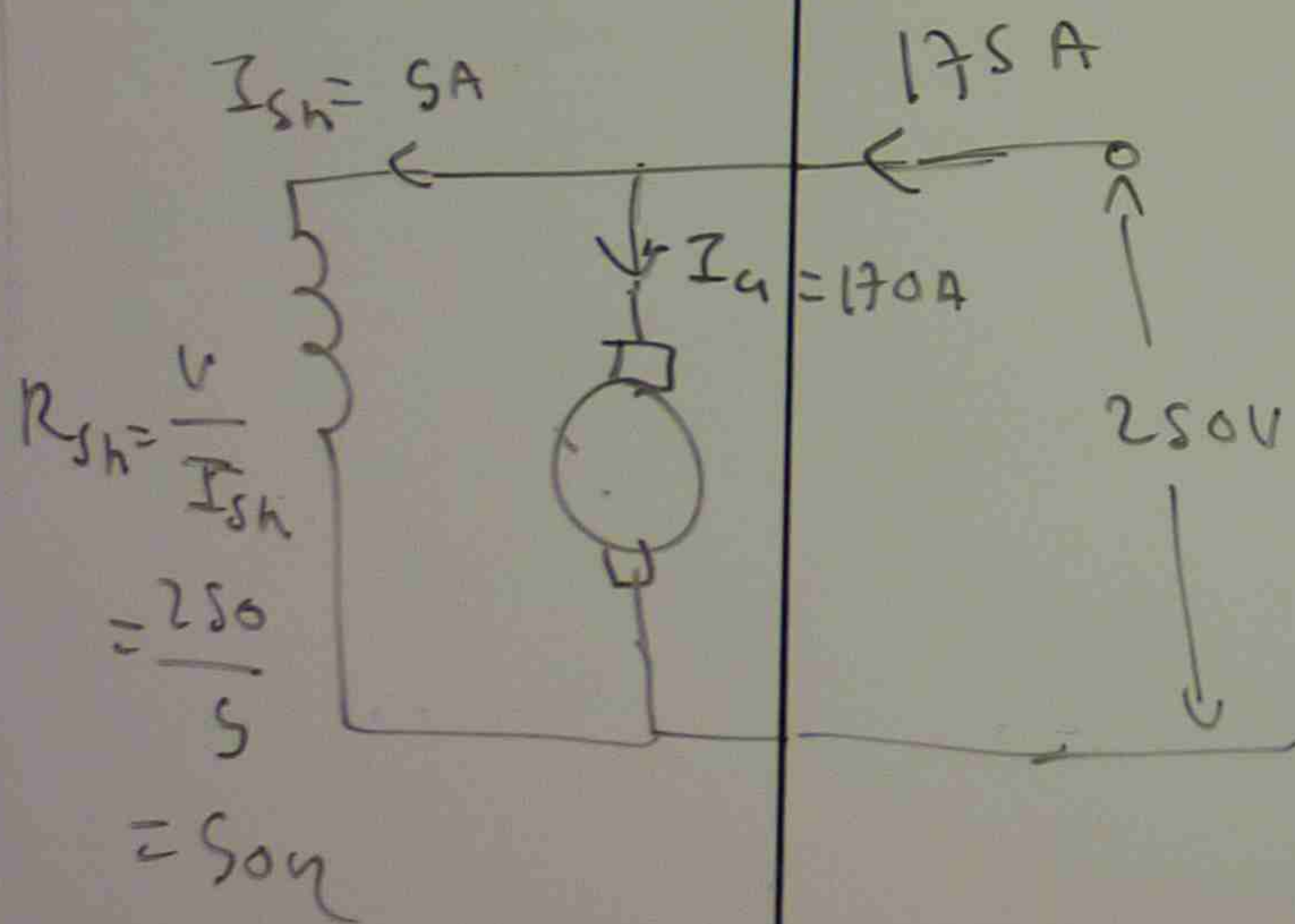- (a) How much power is output from this motor at rated condition
 (b) motor efficiency



BLOCKED ROTOR
 EQUIVALENT
 CIRCUIT


$$R_a = \frac{V}{I} = \frac{10}{170} = 0.06\Omega$$

50W

NO LOAD
 AV

$$= \frac{10}{170}$$

$$= 0.06 \Omega$$

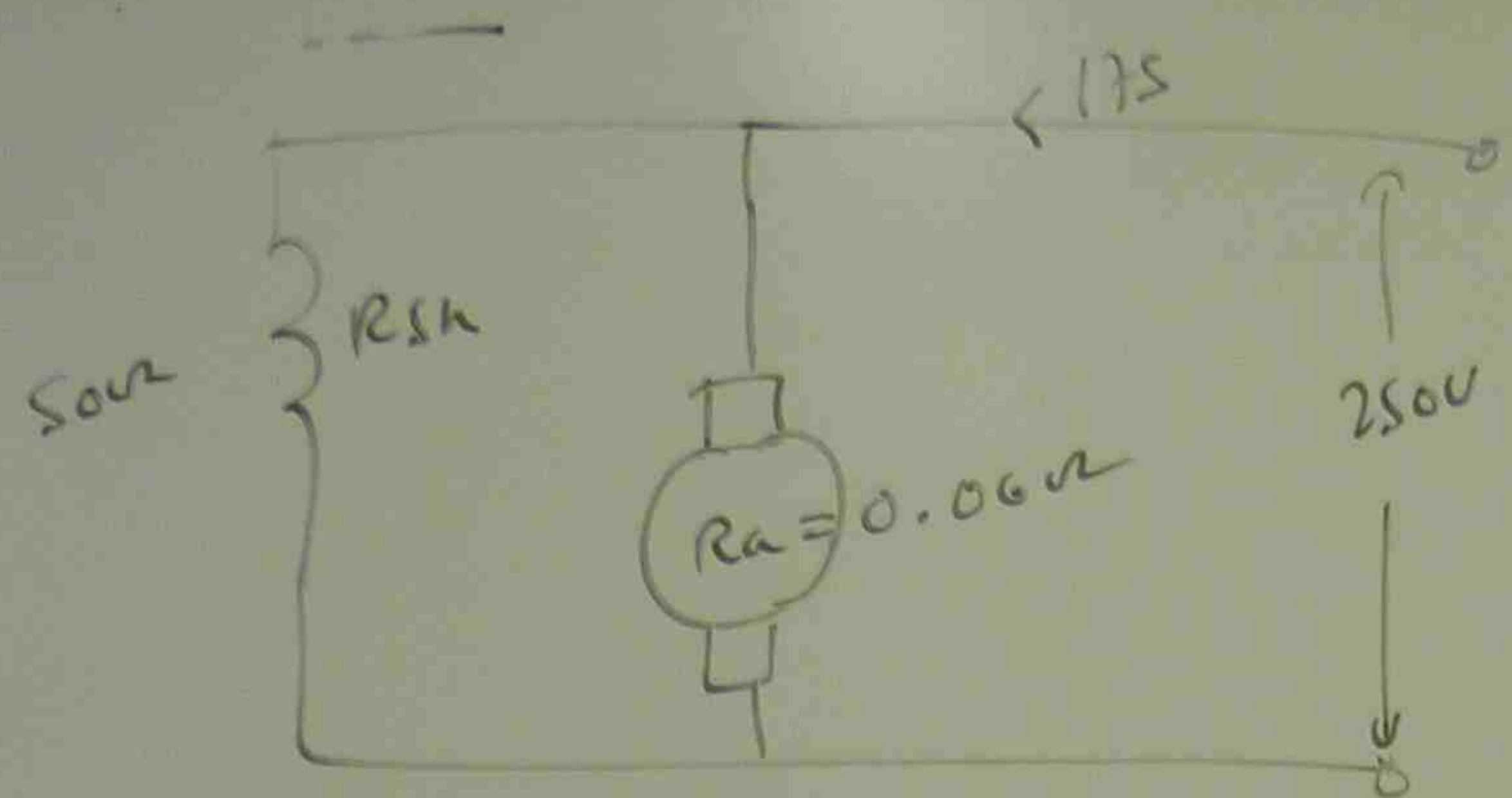

NO LOAD
ALL POWER LOSSES = ROTATIONAL LOSSES.

$$\text{ROTATIONAL LOSS} = \text{TERMINAL VOLTAGE AT NO LOAD} \times \text{NO LOAD ARMATURE CURRENT}$$

$$= 240 \times 13.2$$

$$= 3168 \text{ W}$$

RATED CONDITION POWER OUTPUT

OUTPUT POWER AT RATED CONDITION = IN

$$\text{Copper loss} = I_a^2 R_a + I^2 R_{sh}$$

$$= (170)^2 \times 0.06$$

$$\text{INPUT POWER} = VI =$$

$$\text{OUT PUT POWER} = 437$$

$$= 39$$

$$\text{Efficiency} = \frac{\text{OUT PUT}}{\text{INPUT}} \times 100$$

RATED CONDITION POWER OUTPUT

$$\text{OUTPUT POWER AT RATED CONDITION} = \text{INPUT POWER} - (\text{COPPER LOSS} + \text{ROTATIONAL LOSSES})$$

$$\begin{aligned} \text{Copper loss} &= I_a^2 R_a + I_{sh}^2 R_{sh} \\ &= (170)^2 \times 0.06 + (5)^2 \times 50 = 2984 \text{ WATT} \end{aligned}$$

$$\text{INPUT POWER} = V I = 250 \times 175 = 43750 \text{ WATT}$$

$$\begin{aligned} \text{OUT PUT POWER} &= 43750 - (2984 + 3168) \\ &= 39598 \text{ W} \end{aligned}$$

$$\text{Efficiency} = \frac{\text{OUT PUT}}{\text{INPUT}} \times 100 = \frac{39598}{43750} \times 100 = 90.5\%$$

X NO LOAD
ARMATURE
CURRENT

13.2

W

Pb

A SIX POLE WAVE WOUND DC GENERATOR HAS 410 ACTIVE CONDUCTORS. IF THE GENERATOR IS DRIVEN AT 750 RPM, CALCULATE THE OPEN CIRCUIT VOLTAGE IF USEFUL FLUX PER POLE IS 0.03 wb.

$$P = 6 \quad \text{WAVE}, \quad Z = 410$$

$$N = 750 \text{ RPM}$$

$$E_g = ?$$

$$\phi = 0.03 \text{ wb}$$

$$a = 2 \times m \quad \text{WAVE} \\ = 2 \times 1 = 2$$

a = NO. OF ARMATURE
PARALLEL PATHS.


$$E_g = \frac{\phi Z N}{60} \times \frac{P}{a}$$

$$= \frac{0.03 \times 410 \times 750}{60} \times \frac{6}{2}$$

EFFECT OF CHANGING FLUX AND SPEED ON VOLTAGE

$$E_g \propto \phi N$$
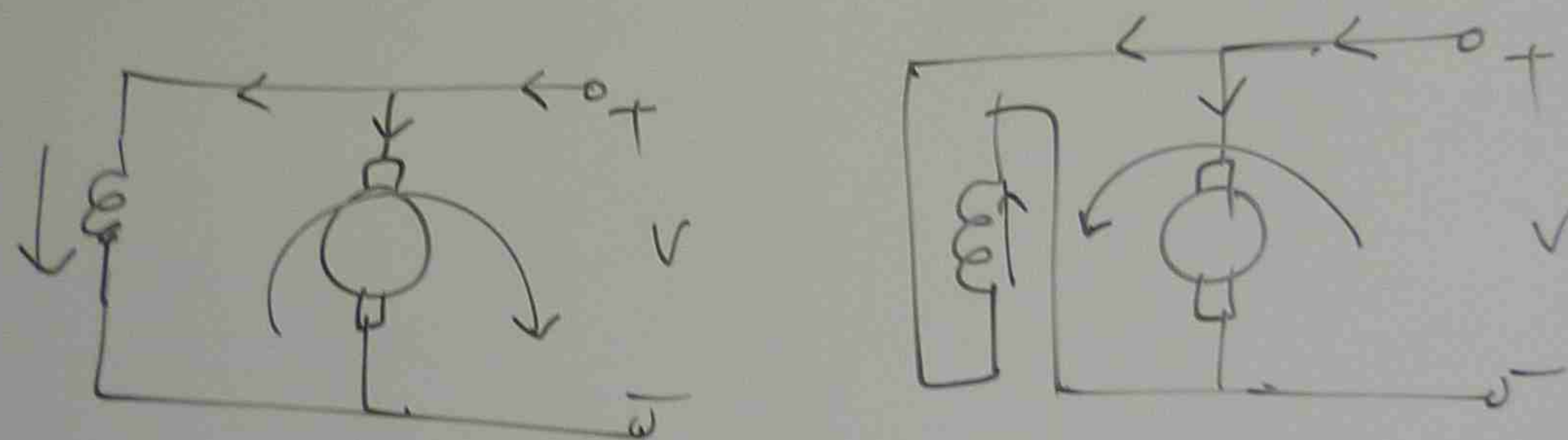
$$\frac{E_{g1}}{E_{g2}} = \frac{\phi_1 N_1}{\phi_2 N_2}$$



DC motor

By changing the field connection, motor rotation direction can be reversed.

ph

motor PA

$$R_a = 0.3 \Omega,$$

CALCULATE


(u)

$$WATT = \frac{2}{\dots}$$

$$3.75 \times 10^3 =$$

$$T = \frac{3}{\dots}$$

AND SPEED ON VOLTAGE

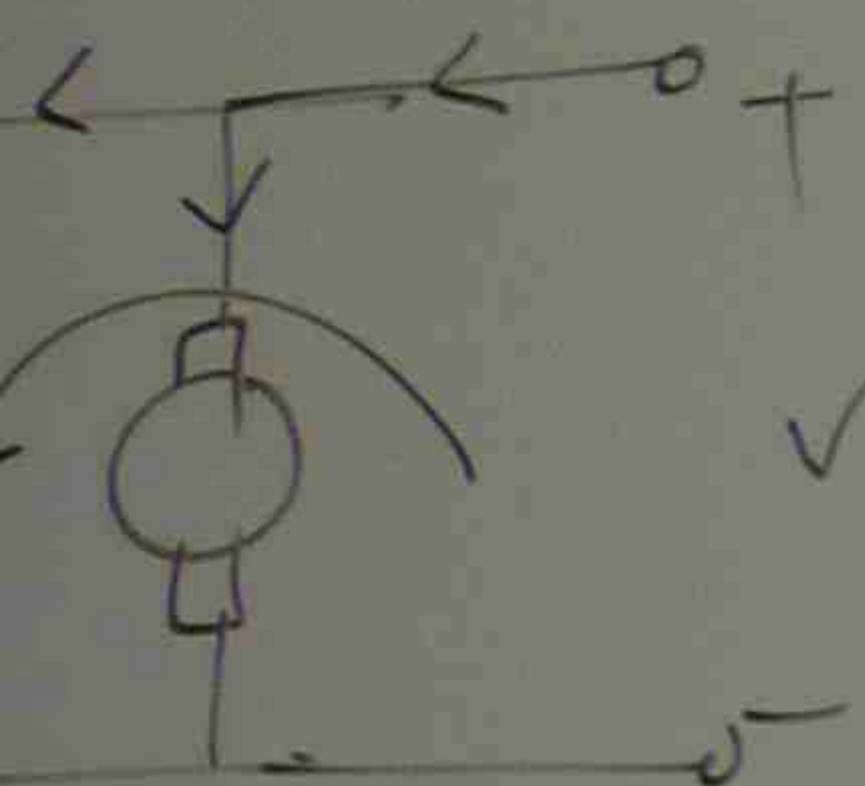

CONNECTION,
CAN BE

pb motor PARTICULARS \rightarrow 3.75 kW, 230 V, 10 Amp, 1750 RPM
 $R_a = 0.3 \Omega$, BRUSH DROP = 2 V ON LOAD.

CALCULATE

(a) FULL LOAD TORQUE

(b) INITIAL RUSH OF ARMATURE CURRENT AND CORRESPONDING TORQUE AT THE INSTANT THE FIELD RESISTANCE IS INCREASING TO REDUCE THE FIELD FLUX TO 0.96 OF ORIGINAL VALUE

(c) FINAL ARMATURE CURRENT, SPEED AND POWER CONSUMPTION


(4)

$$WATT = \frac{2 \pi NT}{60}$$

$$3.75 \times 10^3 = \frac{2 \times 3.1416 \times 1750 \times T}{60}$$

$$T = \frac{3.75 \times 10^3 \times 60}{2 \times 3.1416 \times 1750} = 20.47 \text{ N-m}$$

(b)

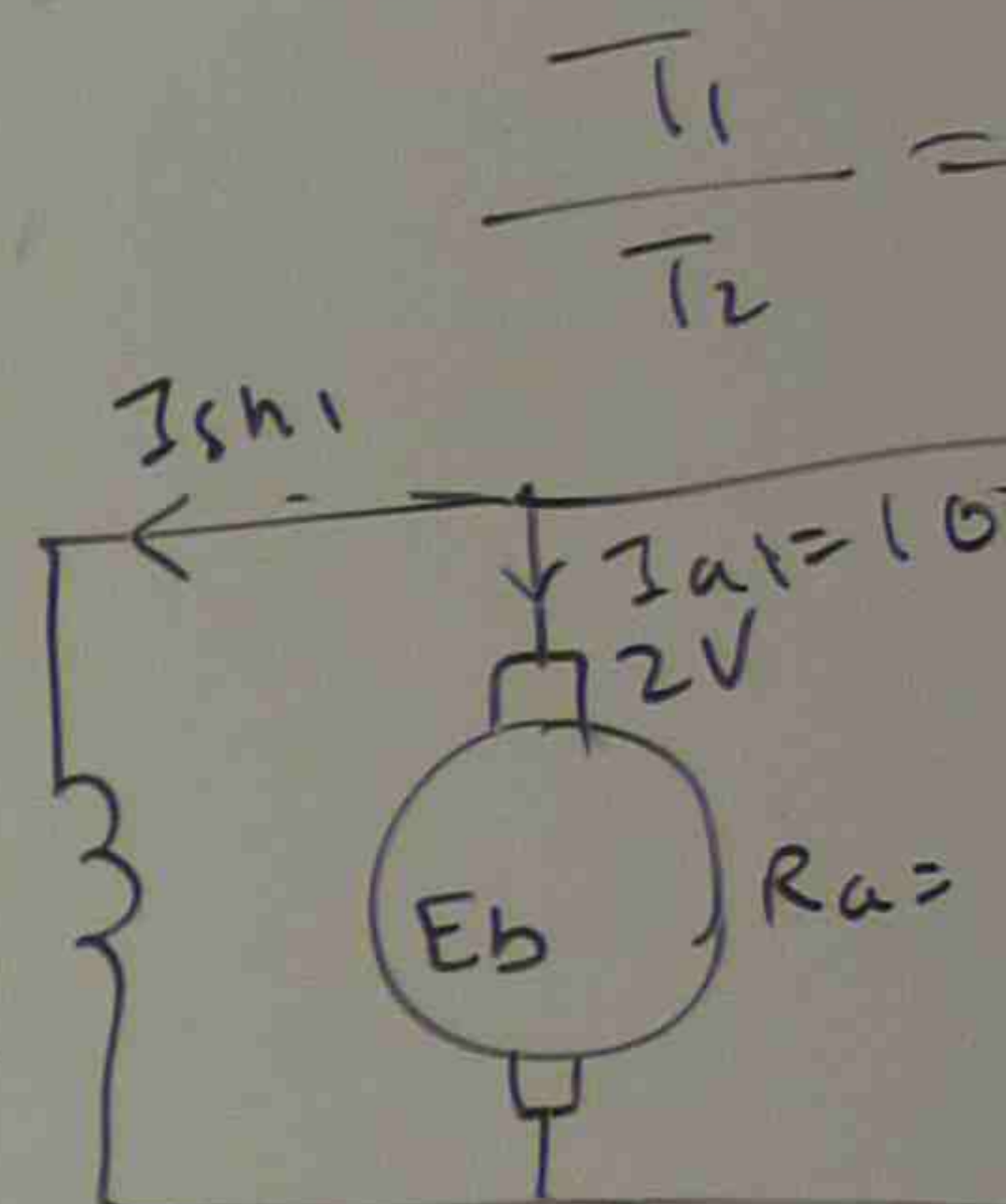

$$\frac{T_1}{T_2} =$$

$$I_{sh1} =$$


FIELD FLUX

(b)

$$T = K \phi I_a$$

motor torque
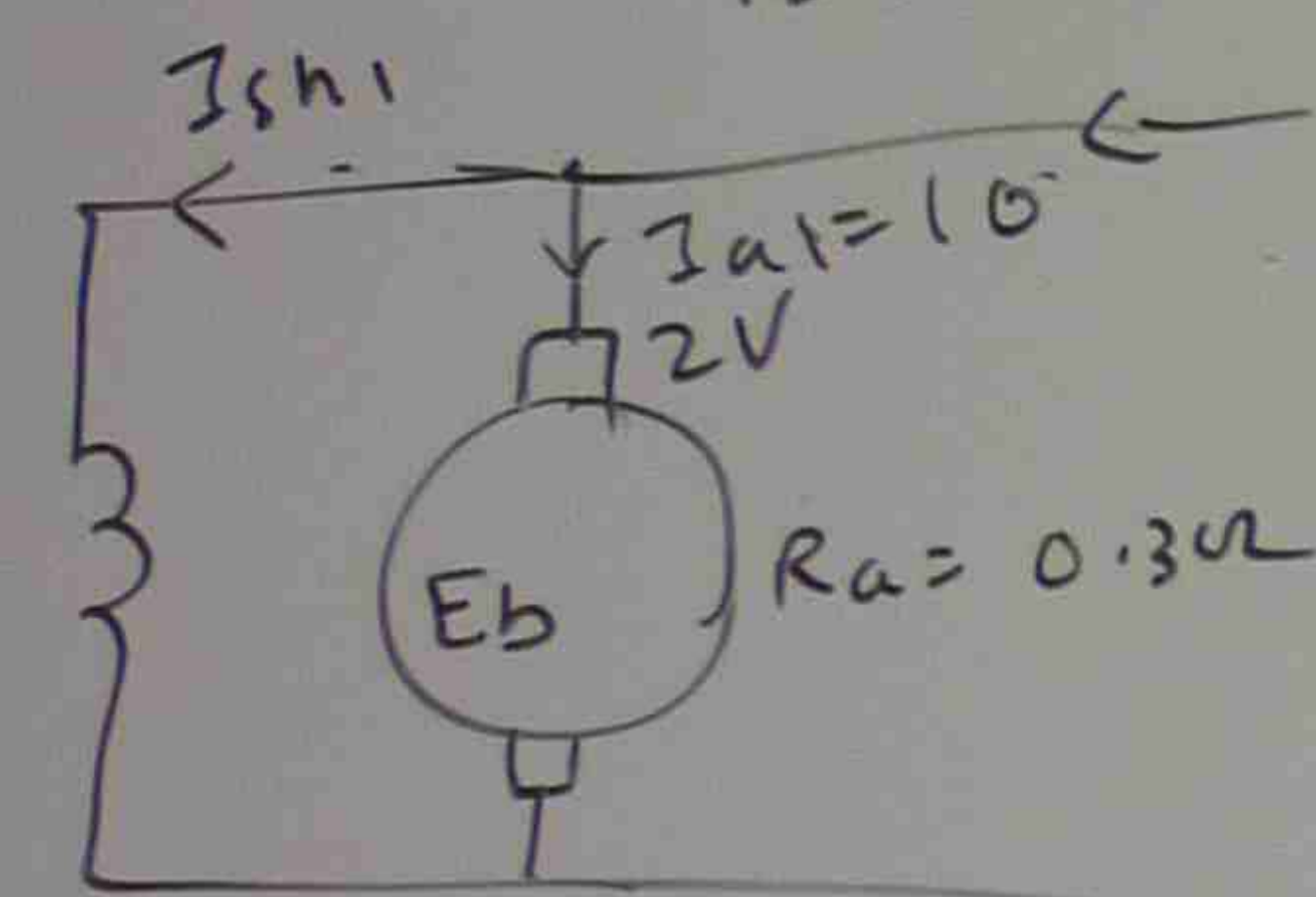
$$\frac{T_1}{T_2} = \frac{\phi_1 I_{a1}}{\phi_2 I_{a2}}$$



$$I_{FL} = \frac{\text{power}}{\text{VOLTAGE}}$$

$$= \frac{3750}{230}$$

$$= 16.3 \text{ Amp.}$$

$$I_{sh1} = 16.3 - 10 = 6.3 \text{ Amp.}$$

$$R_{\text{Brush}} = \frac{2V}{I_a}$$

$$= \frac{2}{10} = 0.2 \Omega$$

FIELD FLUX IS REDUCED

$$E_{b1} = V - (I_a R_a + \text{BRUSH DROP})$$

$$= 230 - (10 \times 0.3 + 2)$$

$$= 225 \text{ V}$$

$$\frac{E_{b1}}{E_{b2}} = \frac{\phi_1 N_1}{\phi_2 N_2}$$

$$\frac{225}{E_{b2}} = \frac{\phi_1 \times N_1}{0.96 \phi_1 \times N_2}$$

$$E_{b2} = 0.96 \times 225$$

$$= 216 \text{ V}$$

$$E_{b2} = V - (I_{a2} R_a + \text{BRUSH DROP})$$

$$216 = 230 - (I_{a2} \times 3 + I_{a2} \times R_b)$$

$$216 = 230 - (I_{a2} \times 0.3 + I_{a2} \times 0.2)$$

$$0.5 I_{a2} = 230 - 216 = 14$$

$$I_{a2} = \frac{14}{0.5} = 28 \text{ Amp.}$$

$$\frac{T_1}{T_2} = \frac{d_1 I_{a1}}{d_2 I_{a2}}$$

$$\frac{20.47}{T_2} = \frac{\phi_1}{0.96\phi_1} \times \frac{10}{28}$$

$$T_2 = \frac{20.47 \times 0.96 \times 28}{10}$$

$$= 55 \text{ N-m}$$

$$\frac{E_{b1}}{E_{b2}} = \frac{d_1 N_1}{d_2 N_2}$$

$$\frac{225}{216} = \frac{\phi_1 \times 1750}{0.96\phi_1 \times N_2}$$

$$N_2 = \frac{216 \times 1750}{225 \times 0.96}$$

$$= 1750 \text{ RPM}$$

$$P = 2\pi N_2 T$$

$$= \frac{2 \times 3.1416 \times 1750 \times 55}{60}$$

$$= 10079 \text{ WATT}$$

$$= 10.079 \text{ kW}$$

7.46 kW, 230V, 1750 RPM SHUNT MOTOR.
 ARMATURE RESISTANCE 0.35Ω . SHUNT FIELD
 RESISTANCE 62.2Ω .


(a) NO LOAD CURRENT IS 7.7 AMP. FULL LOAD
 EFFICIENCY 86%. BRUSH DROP 3 VOLT AT
 FULL LOAD
 CALCULATE % REGULATION

(b) A 2.65Ω RESISTANCE IS PLACED IN
 SERIES WITH ARMATURE CIRCUIT, CALCULATE
 NEW SPEED, % REGULATION, % POWER
 LOSS IN SERIES RESISTANCE IN RESPECT
 OF TOTAL POWER INPUT.

$$(a) \quad I_{FL} = \frac{\text{OUT PUT POWER}}{\text{VOLTAGE} \times \text{EFFICIENCY}}$$

$$= \frac{7.46 \times 10^3}{230 \times 0.86}$$

$$= 37.7 \text{ AMP.}$$

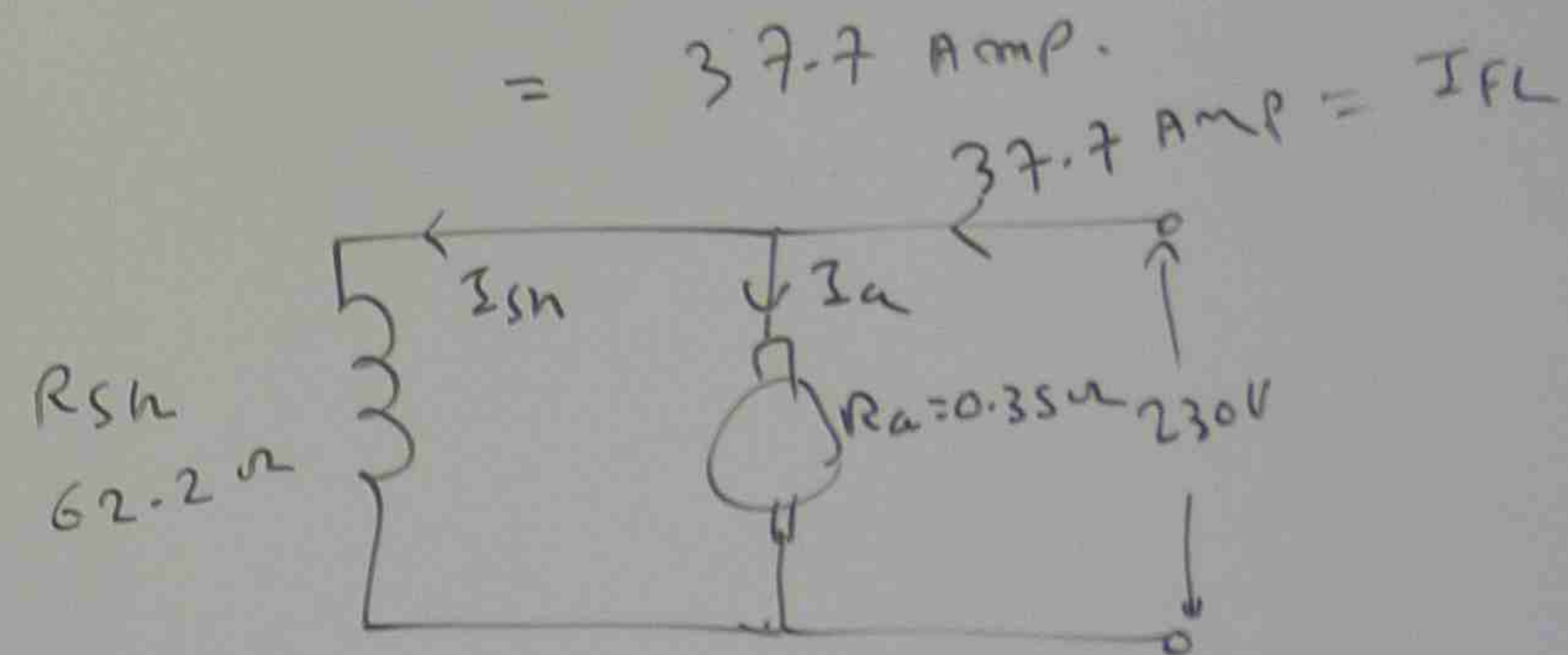

$$I_{sh} = \frac{V}{R_{sh}} = \frac{230}{62.2} = 3.7 \text{ AMP.}$$

$$I_a = I_{FL} - I_{sh} = 37.7 - 3.7 = 34 \text{ AMP}$$

$$N_{FL} = 1750 \text{ RPM}$$

$$I_{aFL} = 34 \text{ Amp}$$

$$N_{NL} = ?$$

$$\begin{aligned} I_{aNL} &= I_{NL} - I_{shNL} \\ &= 7.7 - 3.7 \\ &= 4 \text{ Amp.} \end{aligned}$$

$$\frac{E_{b1}}{E_{b2}} = \frac{\phi_1 N_1}{\phi_2 N_2}$$

$$\frac{V - (I_{aFL} R_a + \text{BRUSH DROP})}{V - (I_{aNL} R_a + \text{BRUSH DROP})} = \frac{\phi_1 N_1}{\phi_2 N_2}$$

$$\frac{230 - (34 \times 0.35 + 3)}{230 - (4 \times 0.35 + 3)} = \frac{\phi_1 N_1}{\phi_2 N_2}$$

$$\frac{215.1}{225.6} = \frac{1750}{N_2}$$

$$N_2 = \frac{1750 \times 225.6}{215.1} = 1850 \text{ RPM}$$

↓
 N_{NL}

$$\phi_1 = \phi_2$$

$$\% \text{ SPEED REGULATION} = \frac{N_{NL} - N_{FL}}{N_{FL}} \times 100$$

$$\begin{aligned} &= \frac{1850 - 1750}{1750} \times 100 \\ &= 5.7\% \end{aligned}$$

(b)

(b)

$$\begin{aligned} E_{b3} &= V - (I_a R_a + \text{brush drop}) \\ &= 230 - [34(0.35 + 2.65) + 3] \\ &= 125 \text{ V} \end{aligned}$$

$$\begin{aligned} \frac{E_{b2}}{E_{b3}} &= \frac{\cancel{\phi_2} N_2}{\cancel{\phi_3} N_3} \\ \frac{225.6}{125} &= \frac{1850}{N_3} \end{aligned}$$

$$\begin{aligned} N_3 &= \frac{1850 \times 125}{225} \\ &= 1020 \text{ rpm} \end{aligned}$$

$$\% \text{ REG} = \frac{N_{NL} - N_3}{N_3} \times 100$$

$$\begin{aligned} &= \frac{1850 - 1020}{1020} \times 100 \\ &= 81.3\% \end{aligned}$$

$$\begin{aligned} 2.65 \Omega \text{ power loss} &= I_a^2 \times 2.65 \\ &= 34^2 \times 2.65 = 3060 \text{ W} \end{aligned}$$

$$\begin{aligned} \% \text{ of power input} &= \frac{3060}{V_T \times I_{FL}} \times 100 \\ &= \frac{3060}{230 \times 37.7} \times 100 = 34.2\% \end{aligned}$$

Ph 7.46 kW, 230V, 1750 RPM SHUNT MOTOR.

ARMATURE RESISTANCE 0.35Ω . SHUNT FIELD
RESISTANCE 62.2Ω .


(a) NO LOAD CURRENT IS 7.7 AMP. FULL LOAD
EFFICIENCY 86%. BRUSH DROP 3 VOLT AT
FULL LOAD
CALCULATE % REGULATION

(b) A 2.65Ω RESISTANCE IS PLACED IN
SERIES WITH ARMATURE CIRCUIT, CALCULATE
NEW SPEED, % REGULATION, % POWER
LOSS IN SERIES RESISTANCE IN RESPECT
OF TOTAL POWER INPUT.

$$(a) \quad I_{FL} = \frac{\text{OUT PUT POWER}}{\text{VOLTAGE} \times \text{EFFICIENCY}}$$

$$= \frac{7.46 \times 10^3}{230 \times 0.86}$$

$$= 37.7 \text{ AMP.}$$

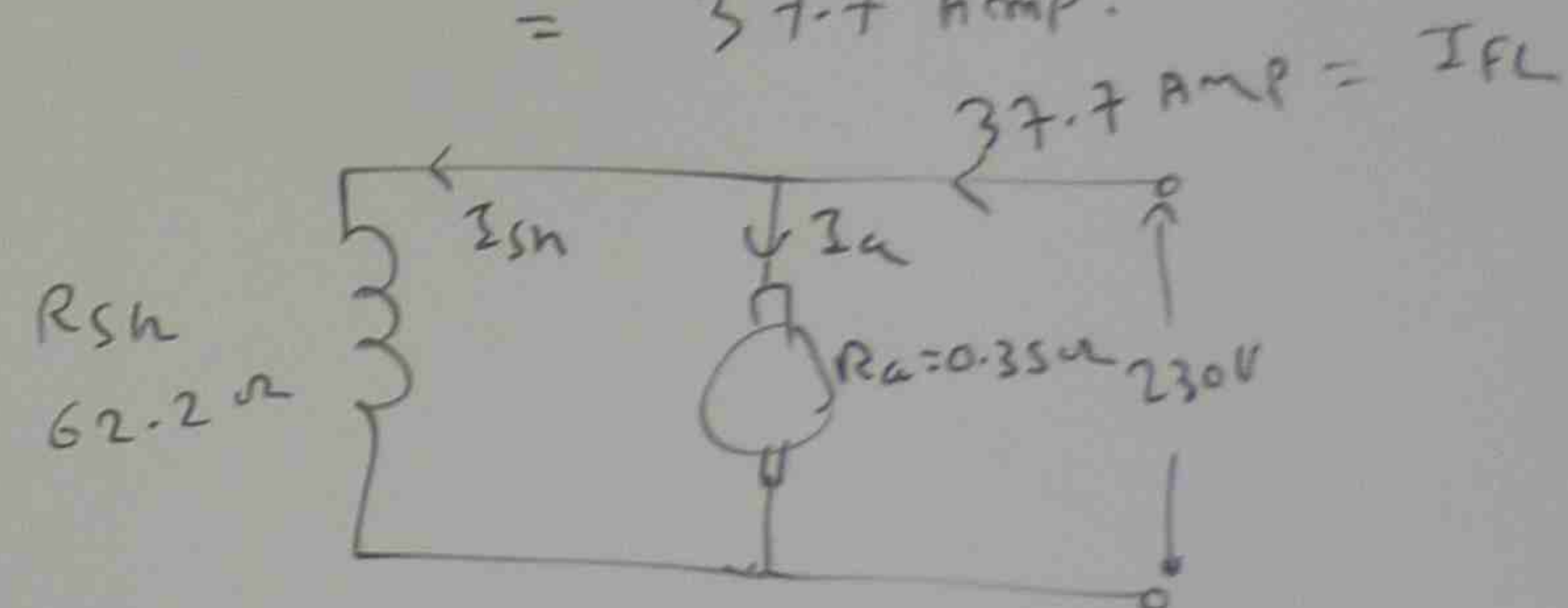

$$I_{sh} = \frac{V}{R_{sh}} = \frac{230}{62.2} = 3.7 \text{ AMP.}$$

$$I_a = I_{FL} - I_{sh} = 37.7 - 3.7 = 34 \text{ AMP}$$

$$N_{FL} = 1750 \text{ RPM}$$

$$I_{aFL} = 34 \text{ Amp}$$

$$N_{NL} = ?$$

$$\begin{aligned} I_{aNL} &= I_{NL} - I_{shNL} \\ &= 7.7 - 3.7 \\ &= 4 \text{ Amp} \end{aligned}$$

$$\frac{E_{b1}}{E_{b2}} = \frac{\phi_1 N_1}{\phi_2 N_2}$$

$$\frac{V - (I_{aFL} R_a + \text{BRUSH DROP})}{V - (I_{aNL} R_a + \text{BRUSH DROP})} = \frac{\phi_1 N_1}{\phi_2 N_2}$$

$$\phi_1 = \phi_2$$

$$\frac{230 - (34 \times 0.35 + 3)}{230 - (4 \times 0.35 + 3)} = \frac{N_1}{N_2}$$

$$\% \text{ SPEED REGULATION} = \frac{N_{NL} - N_{FL}}{N_{FL}} \times 100$$

$$\begin{aligned} &= \frac{1750 - 1850}{1750} \times 100 \\ &= 5.7\% \end{aligned}$$

$$\frac{215.1}{225.6} = \frac{1750}{N_2}$$

$$N_2 = \frac{1750 \times 225.6}{215.1} = 1850 \text{ RPM}$$

\downarrow
 N_{NL}

(b)

$$E_{b3} = V - (I_a R_a + \text{BRUSH DROP})$$

$$= 230 - [34(0.35 + 2.65) + 3]$$

$$= 125 \text{ V}$$

$$\frac{E_{b2}}{E_{b3}} = \frac{\cancel{\phi_2} N_2}{\cancel{\phi_3} N_3}$$

$$\frac{225.6}{125} = \frac{1850}{N_3}$$

$$N_3 = \frac{1250 \times 125}{225}$$

$$= 1020 \text{ rpm}$$

$$\% \text{ REG} = \frac{N_{NL} - N_3}{N_3} \times 100$$

$$= \frac{1850 - 1020}{1020} \times 100$$

$$= 81.3\%$$

$$2.65 \Omega \text{ power loss} = I_a^2 \times 2.65$$

$$= 34^2 \times 2.65 = 3060 \text{ W}$$

$$\% \text{ of power input} = \frac{3060}{V_T \times I_{FL}} \times 100$$

$$= \frac{3060}{230 \times 37.7} \times 100 = 34.2\%$$

REWS

1

REVISION (PART-1 FOR TEST 1)

- ① A MOTOR HAS A COMBINED MOMENT OF INERTIA 10 N-m s^2 AND INITIAL VELOCITY 200 RAD/s . IF THE TORQUE PRODUCED BY THE MOTOR IS INCREASED BY 50 N-m CALCULATE
- THE TIME FOR THE SPEED TO REACH 300 RAD/s
 - THE FINAL SPEED IF THE TORQUE WAS MAINTAINED FOR 10 SEC
 - THE TORQUE INCREASE NECESSARY TO OBTAIN AN INCREASE OF 50 RAD/s IN 2 SEC .

(a) $\omega_2 = \omega_1 + \alpha t$

$300 = 200 + 5 \times t$

$T = I \alpha$

$50 = 10 \times \alpha$

$\alpha = \frac{50}{10} = 5$

$t = \frac{300 - 200}{5} = 20 \text{ SEC}$

ω_2 = FINAL ANGULAR VELOCITY
 ω_1 = INITIAL ANGULAR VELOCITY
 α = ANGULAR ACCELERATION
 t = TIME

T = TORQUE, I = MOMENT OF INERTIA

REVISION (PART-1 FOR TEST 1)

- ① A MOTOR HAS A COMBINED MOMENT OF INERTIA 10 N-m s^2 AND INITIAL VELOCITY 200 RAD/s . IF THE TORQUE PRODUCED BY THE MOTOR IS INCREASED BY 50 N-m CALCULATE
- THE TIME FOR THE SPEED TO REACH 300 RAD/s
 - THE FINAL SPEED IF THE TORQUE WAS MAINTAINED FOR 10 SEC
 - THE TORQUE INCREASE NECESSARY TO OBTAIN AN INCREASE OF 50 RAD/s IN 25 SEC .

(a) $\omega_2 = \omega_1 + \alpha t$

$300 = 200 + 5 \times t$

$T = I \alpha$

$50 = 10 \times \alpha$

$\alpha = \frac{50}{10} = 5$

$t = \frac{300 - 200}{5} = 20 \text{ SEC}$

$\omega_2 = \text{FINAL ANGULAR VELOCITY}$

$\omega_1 = \text{INITIAL ANGULAR VELOCITY}$

$\alpha = \text{ANGULAR ACCELERATION}$

$t = \text{TIME}$

$T = \text{TORQUE}, I = \text{MOMENT OF INERTIA}$

$$(b) \omega_2 = \omega_1 + \alpha t$$

$$= 200 + 5 \times 10$$

$$= 250 \text{ rad/s}$$

$$(c) \alpha = \frac{\omega}{t} = \frac{50}{25} = 2 \text{ rad/s}^2$$

$$T = I \alpha$$

$$= 10 \times 2 = 20 \text{ N-m}$$

pb 1

pb 3

LAP



pb 2

EXPLAIN MAIN POLE AND INTER POLE

MAIN POLE

MAIN POLE IS THE POLE WHICH PRODUCES THE MAIN MAGNETIC FLUX NECESSARY FOR MACHINE OPERATION

INTER POLE

INTER POLES ARE THE MINOR POLES BETWEEN MAIN POLES TO IMPROVE COMMUTATION.

pb 3

CALCULATE THE COMMUTATOR BAR PITCH FOR THE FOLLOWING SIMPLEX WAVE WOUND ARMATURE, 4 POLES.

(a) 81 BARS (b) 131 BARS (c) 171 BARS

LAP



COMMUTATOR

$$\text{BAR PITCH} = \frac{S}{P}$$

S = SLOT NO.

WAVE



$$Y_c = \frac{C \pm m}{P/2}$$

COMMUTATOR BAR PITCH

C = NO. OF COMMUTATOR

BAR

m = PLEX NO.

Simplex m = 1

Duplex m = 2

+ = PROGRESSIVE

- = RETROGRESSIVE

$$(a) Y_c = \frac{81 \pm 1}{4/2} = \frac{81 \pm 1}{2} = \frac{82}{2} \text{ (or)} \frac{80}{2} = 41 \text{ (or)} 40$$

$$(b) Y_c = \frac{131 \pm 1}{4/2} = \frac{132}{2} \text{ (or)} \frac{130}{2} = 66 \text{ (or)} 65$$

$$(c) Y_c = \frac{171 \pm 1}{4/2} = \frac{172}{2} \text{ (or)} \frac{170}{2} = 86 \text{ (or)} 85$$

DC MACHINE TEST (1) REVISION

- ① A motor has a combined moment of inertia of 10 N-m^2 and an initial velocity of 200 radians per second. If the torque produced by the motor was increased by 50 N-m , calculate (a) the time for the speed to reach 300 radians/sec. (b) the final speed if the torque was maintained for 10 seconds. (c) the torque increase necessary to obtain an increase of 50 radians/second in 2.5 seconds.

② Explain (a) main pole (b) interpole

③ Calculate the commutator bar pitch for the following four pole simplex wave wound armature (a) 81 bars (b) 131 bars (c) 171 bars.

④ A 240 segment commutator rotates at 1500 rpm. If a brush spans 3 segments, calculate commutation time.

⑤ A four pole
conductors.
current is

⑥ An armature
generator
has a pole
magnetizing

⑦ A 75 kW
15% calc
the voltage
full load
terminal

⑧ provide
now with

⑨ The E
shunt

REVISION

MOMENT OF INERTIA OF 10 N-m^2
 OF 200 RADIAN PER SECOND. IF THE
 TORQUE WAS INCREASED BY 50 N-m
 FOR THE SPEED TO REACH 300 RADIAN/SEC.
 SPEED IF THE TORQUE WAS MAINTAINED
 INCREASE NECESSARY TO OBTAIN AN
 OF 50 RADIAN/SECOND IN 25 SECONDS.

INTER POLE

BAR PITCH FOR THE FOLLOWING
 AND ARMATURE
 31 BARS (c) 171 BARS.

OR ROTATES AT 1500 RPM. IF
 ENTS, CALCULATE COMMUTATION TIME.

(5) A FOUR POLES LAP WOUND ARMATURE HAS A TOTAL OF 720 ACTIVE CONDUCTORS. IF THE FLUX PER POLE IS 0.4 Wb AND THE ARMATURE CURRENT IS 31.4 AMP , CALCULATE THE TORQUE DEVELOPED.

(6) AN ARMATURE 0.5 m DIAMETER OF A SIX POLE LAP WOUND GENERATOR HAS 378 CONDUCTORS, CARRIES 800 AMP AND HAS A POLE ARC OF 0.17 m , CALCULATE THE CROSS MAGNETIZING ARMATURE REACTION AMPERE TURNS.

(7) A 75 KW 500 V GENERATOR HAS A VOLTAGE REGULATION 15% . CALCULATE (a) OPEN CIRCUIT VOLTAGE (b) ASSUMING THE VOLTAGE VARIES UNIFORMLY BETWEEN NO LOAD AND FULL LOAD CURRENT, CALCULATE KW OUTPUT FOR TERMINAL VOLTAGE OF 510 V

(8) PROVIDE YOUR OWN VIEW WHY AC GENERATORS ARE NOW WIDELY USED

(9) THE EXTERNAL CHARACTERISTICS OF A SELF EXCITED SHUNT GENERATOR IS AS FOLLOWS:-

TERMINAL VOLTAGE
 AMPERE

DETERMINE (a)

(10) SKETCH

(1) $I = 10$

$T = 50$

(a) $\omega_2 = 30$

$\omega_2 = 0$

$T = 1$

$S_0 = 10$

HAS A TOTAL OF 720 ACTIVE
0.4 wb AND THE ARMATURE
THE TORQUE DEVELOPED.

A SIX POLE LAP WOUND
CARRIES 800 AMP AND
CALCULATE THE CROSS
AMPERE TURNS.

A VOLTAGE REGULATION
VOLTAGE (b) ASSUMING
BETWEEN NO LOAD AND
KW OUTPUT FOR

AC GENERATORS ARE

OF A SELF EXCITED

WS:-

TERMINAL VOLTAGE	144	142	136	133	127	120	108	100
AMPERE	0	10	20	30	40	50	60	65

DETERMINE (a) THE LOAD VOLTAGE AND CURRENT FOR A LOAD
RESISTANCE OF 2Ω

(b) TOTAL LOAD RESISTANCE AND CURRENT FOR
A TERMINAL VOLTAGE OF 120V.

- (10) SKETCH (a) LONG SHUNT COMPOUND GENERATOR
(b) SHORT SHUNT COMPOUND GENERATOR
(c) SHUNT GENERATOR
(d) SERIES GENERATOR
(e) SEPARATELY EXCITED GENERATOR

$$(1) I = 10 \text{ N-m}^2, \omega_1 = 200 \text{ rad/s}$$

$$T = 500 \text{ N-m}$$

$$(a) \omega_2 = 300 \text{ rad/s} \quad t = ?$$

$$\omega_2 = \omega_1 + \alpha t$$

$$T = I \alpha$$

$$50 = 10 \alpha \rightarrow \alpha = \frac{50}{10} = 5 \text{ rad/s}^2$$

$$\omega_2 = \omega_1 + \alpha t$$

$$300 = 200 + 5 \times t$$

$$\frac{300 - 200}{5} = t$$

$$t = 20 \text{ sec}$$

$$(b) \omega_2 = \omega_1 + \alpha t$$

$$= 200 + 5 \times 10 = 250 \text{ rad/sec}$$

$$(c) \Delta \omega = 50 \text{ rad/sec}$$

$$\Delta t = 25 \text{ sec}$$

$$\alpha = \frac{\Delta \omega}{\Delta t} = \frac{50}{25} = 2 \text{ rad/s}^2$$

$$T = I \alpha = 10 \times 2 = 20 \text{ N-m}$$

2 (a) MAIN POLE IS THE MAJOR
POLE THAT PROVIDES MAIN
FLUX DENSITY

(b) THE INTER POLES ARE
PLACED BETWEEN THE MAIN POLES
TO IMPROVE THE COMMUTATION.

$$(b) \omega_2 = \omega_1 + \alpha t$$

$$= 200 + 5 \times 10 = 250 \text{ rad/sec}$$

$$(c) \Delta \omega = 50 \text{ rad/sec}$$

$$\Delta t = 25 \text{ sec}$$

$$\alpha = \frac{\Delta \omega}{\Delta t} = \frac{50}{25} = 2 \text{ rad/s}^2$$

$$T = I \alpha = 10 \times 2 = 20$$

N-m

2 (a) MAIN POLE IS THE MAJOR POLE THAT PROVIDES MAIN FLUX DENSITY

(b) THE INTER POLES ARE PLACED BETWEEN THE MAIN POLES TO IMPROVE THE COMMUTATION.

$$(3) \gamma = \frac{c \pm m}{P/2}$$

$$(a) \gamma = \frac{81 \pm 1}{4/2}$$

$$= \frac{81+1}{2} \text{ (or) } \frac{81-1}{2}$$

$$= 41 \text{ (or) } 40$$

$$(b) \gamma = \frac{131 \pm 1}{4/2}$$

$$= \frac{131+1}{2}$$

$$= \frac{131+1}{2} \text{ (or) } \frac{131-1}{2}$$


$$= 66 \text{ (or) } 65$$

$$(c) \gamma = \frac{171 \pm 1}{2}$$

$$= \frac{172}{2} \text{ (or) } \frac{170}{2}$$

$$= 86 \text{ (or) } 85$$

(4)

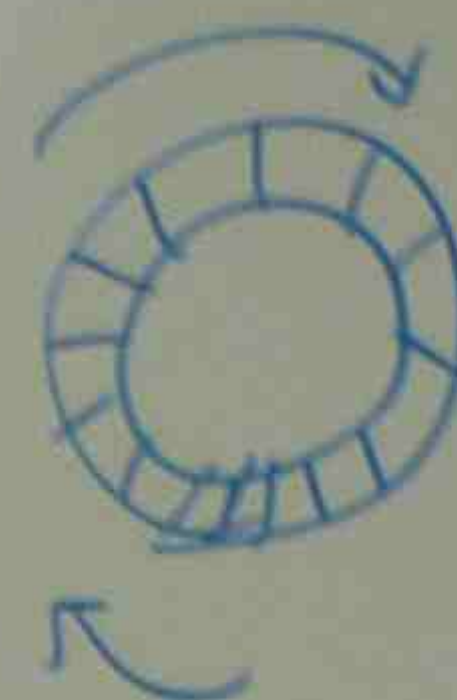

1 REVOLUTION \Rightarrow 240 SEGMENTS.

1500 RPM \rightarrow 1500 REVOLUTION \rightarrow 1 MINUTE
(or)
60 SEC

240 X 1500 SEGMENT \rightarrow 60 SEC

3 SEGMENT — ?
COMMUTATION TIME

$$\frac{60 \times 3}{240 \times 1500} = 5 \times 10^{-4} \text{ sec}$$

COMMUTATION TIME

(5) $p=4, z=$

$$I_a = 3$$

$$T = ?$$

$$T = \frac{\phi z}{2\pi}$$

$a =$ NO. OF AR
PARALL

$$a = m$$

$$= 1$$

$$T = \frac{0.1}{2}$$



240 SEGMENTS.

1500 REVOLUTION → 1 MINUTE
(OR)
60 SEC

SEGMENT → 60 SEC

SEGMENT — ?
COMMUTATION
TIME

$$\frac{3}{1500} = 5 \times 10^{-4} \text{ sec}$$

COMMUTATION TIME

⑤ $p=4, z=720, \phi=0.4 \text{ wb}$

$I_a = 31.4 \text{ Amp.}$

$T = ?$

$$T = \frac{\phi z I_a}{2\pi a} \quad \text{N-m}$$

$a = \text{No. of ARMATURE PARALLEL PATHS} = m \times p \quad (\text{LAP})$

$m = 1 \text{ simplex}$
 2 duplex

$a = m \times 2 \quad (\text{WAVE})$

$a = m \times p \quad (\text{LAP})$
 $= 1 \times 4 = 4$

$$T = \frac{0.4 \times 720 \times 31.4}{2 \times 3.1416 \times 4}$$

$= 144 \text{ N-m}$

⑥ $z=378, I_a=800, p=6$

POLE ARC = 0.17 m

$AT_c = ? \quad (\text{CROSS MAGNETIZING AMP-TURNS})$

$$AT_c = \frac{\text{pole arc/pole}}{\frac{\text{CIRCUMFERENCE}}{\text{No. of poles}}} \times \frac{z I_a}{2 a p}$$

LAP

$a = m \times p = 1 \times 6 = 6$

$\text{CIRCUMFERENCE} = \pi D$
 $= 3.1416 \times 0.5$

$$AT_c = \frac{0.17}{\frac{3.1416 \times 0.5}{6}} \times \frac{378 \times 800}{2 \times 6 \times 6}$$

$= 2740 \text{ AT/pole}$


⑦

$\% \text{ REG} = \frac{V_{NL}}{V_{FL}}$

$IS = \frac{V_{NL} - V_{FL}}{500}$

$\frac{IS \times 500}{100} = V_{NL}$

(a) $V_{NL} = \frac{IS \times 500}{100}$

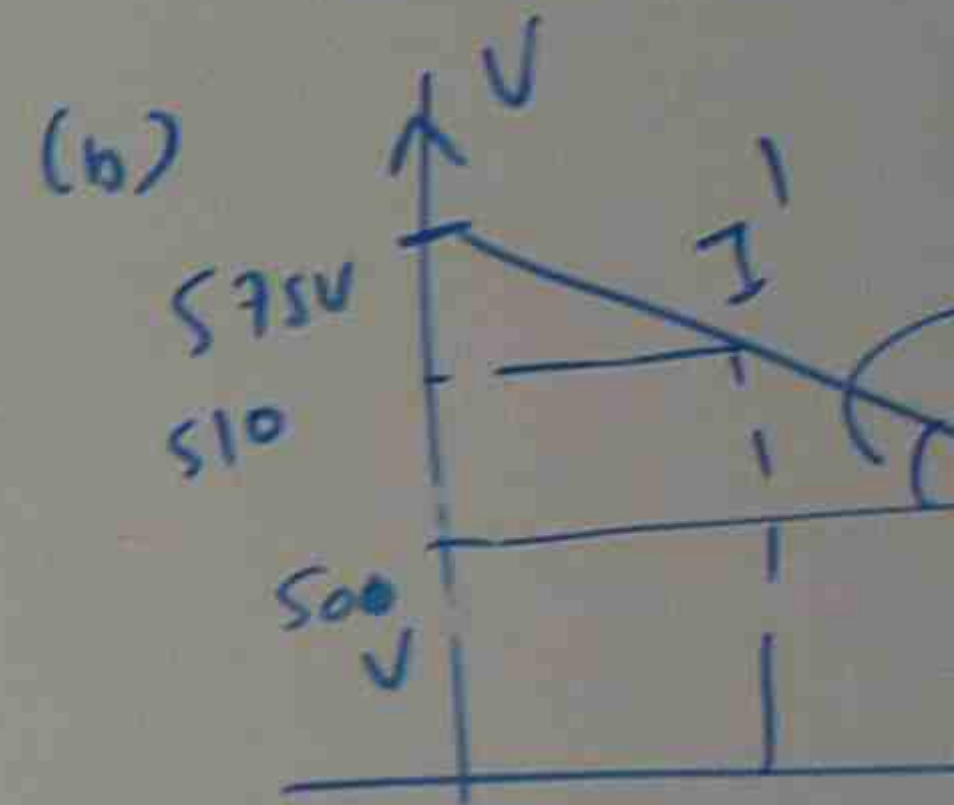

$I_{FL} = \frac{\text{RATED}}{\text{Full Load VOLTAGE}}$

$= \frac{75 \times 1000}{500}$
 $= 150$

$\phi = \text{GRADIENT}$

$$78, I_a = 800, p = 6$$

$$r_c = 0.17 \text{ m}$$

= ? (CROSS MAGNETIZING
AMP-TURNS)

$$\frac{\text{pole arc/pole}}{\text{circumference}} \times \frac{Z I_a}{2 a p}$$

$$x p = 1 \times 6 = 6$$

$$\text{RENC} = \pi \cdot \frac{1}{2}$$

$$= 3.1416 \times 0.5$$

$$\frac{0.17}{3.1416 \times 0.5} \times \frac{378 \times 800}{2 \times 6 \times 6}$$


$$2740 \text{ AT/pole}$$

$$\textcircled{7} \% \text{ REG} = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100$$

$$15 = \frac{V_{NL} - 500}{500} \times 100$$

$$\frac{15 \times 500}{100} = V_{NL} - 500$$
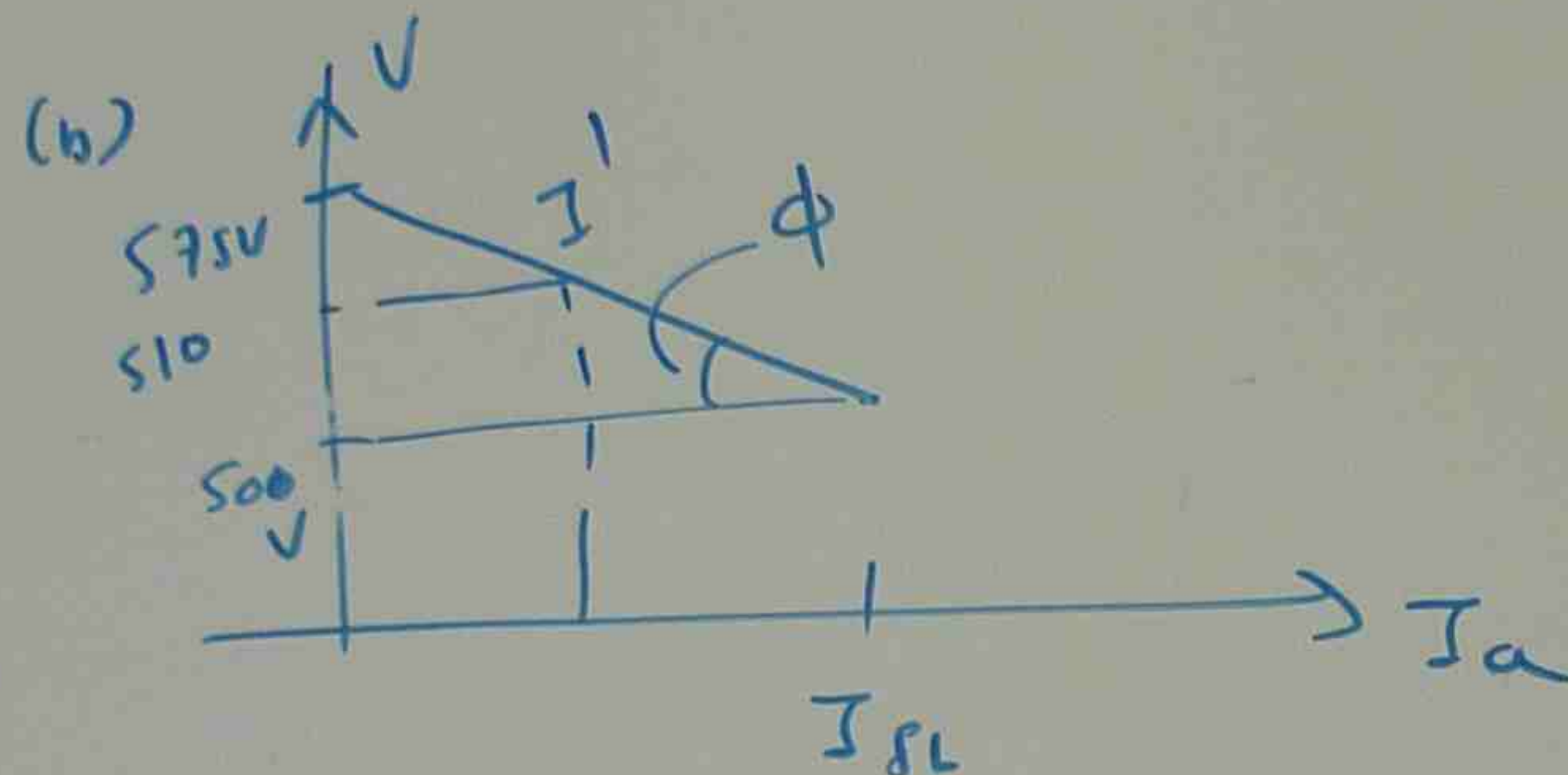
$$(a) V_{NL} = \frac{15 \times 500}{100} + 500 = 575 \text{ V}$$



$$I_{FL} = \frac{\text{RATED POWER}}{\text{FULL LOAD TERMINAL VOLTAGE}}$$

$$= \frac{75 \times 1000}{500}$$

$$= 150 \text{ Amp.}$$

$$\phi = \text{GRADIENT} = \frac{V_1 - V_2}{I_1 - I_2} = \frac{575 - 500}{0 - 150}$$

$$= \frac{75}{-150} = -0.5$$

$$\text{GRADIENT} = \frac{V_1 - V_2}{I_1 - I_2}$$

$$-0.5 = \frac{575 - 510}{0 - I_1}$$

$$-0.5 \times (-I_1) = 65$$

$$I_1 = \frac{65}{0.5} = 130 \text{ AMP}$$

⑧ AC GENERATORS ARE NOW WIDELY
USED BECAUSE

(a) AC VOLTAGE CAN BE EASILY
CHANGED THE LEVEL

(b) IT IS EASIER TO MAINTAIN
AC GENERATORS

(c) HIGHER POWER & VOLTAGE
CAN BE PRODUCED BY AC GENERATOR
THAN DC GENERATOR.


TERMINAL VOLTAGE	144	142	136	133	127	120	108	100
AMPERE	0	10	20	30	40	50	60	65

DETERMINE (a) THE LOAD VOLTAGE AND CURRENT FOR A LOAD RESISTANCE OF 2Ω








(b) TOTAL LOAD RESISTANCE AND CURRENT FOR A TERMINAL VOLTAGE OF 120V.



- (10) SKETCH (a) LONG SHUNT COMPOUND GENERATOR
(b) SHORT SHUNT COMPOUND GENERATOR
(c) SHUNT GENERATOR
(d) SERIES GENERATOR
(e) SEPARATELY EXCITED GENERATOR

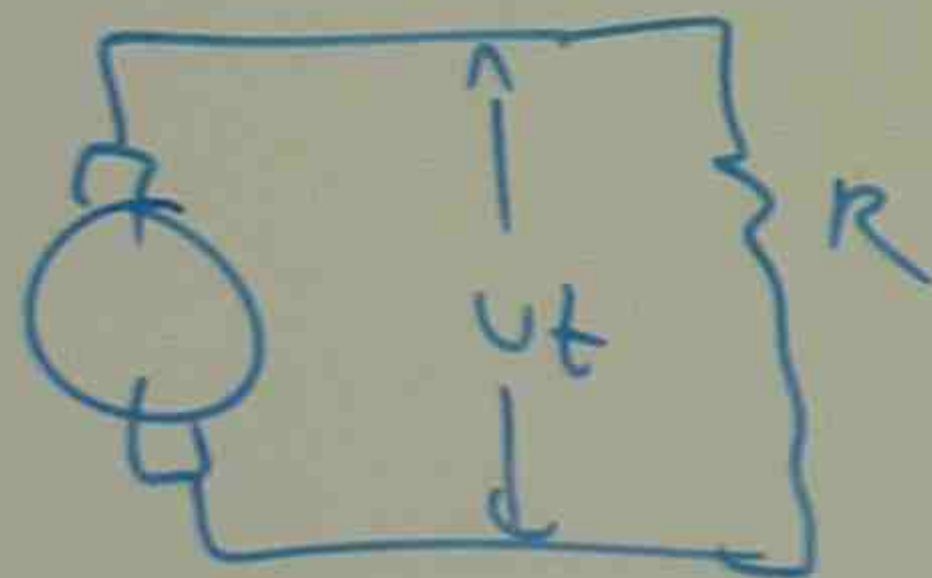(9) $V_t = I_L \times R_L$
 $R_L = \frac{V_t}{I_L}$




V_t	142	136	133	127	120	108	100
I_L	10	20	30	40	50	60	65
R_L	14.2 Ω	6.8	4.43	3.12	2.4	1.8	1.53 Ω

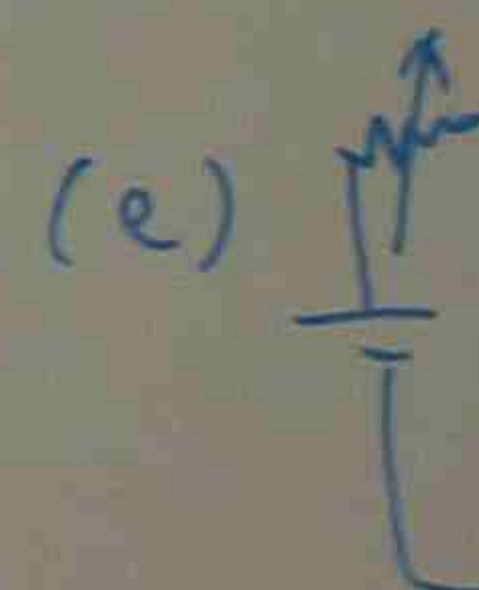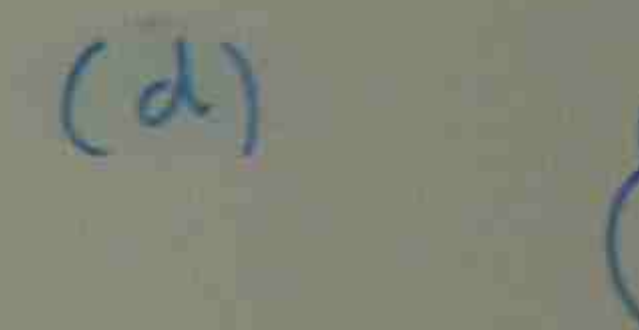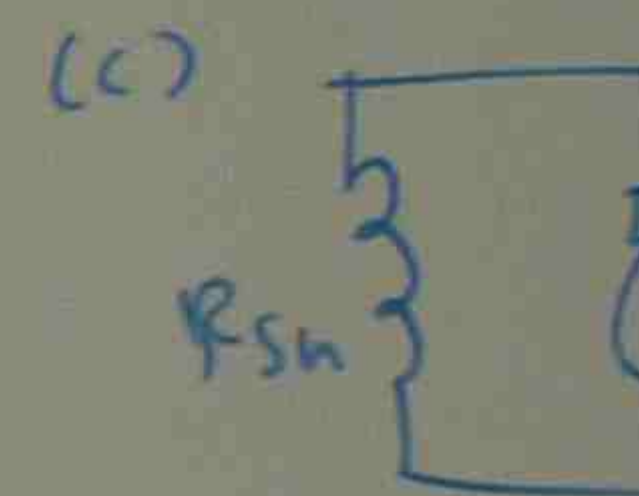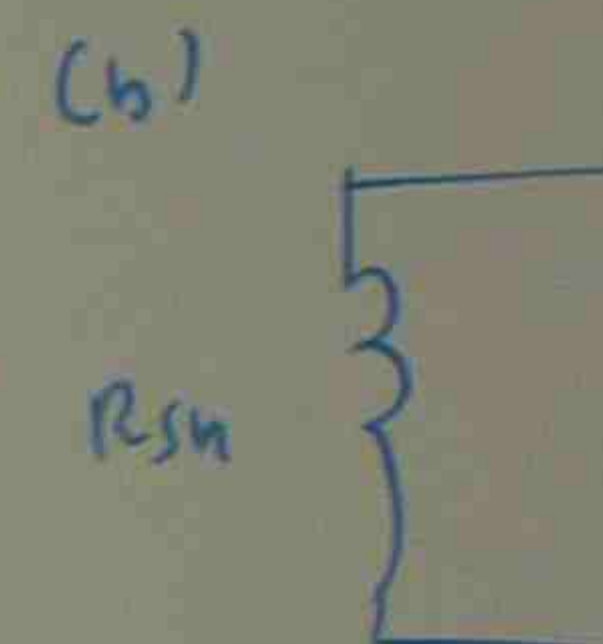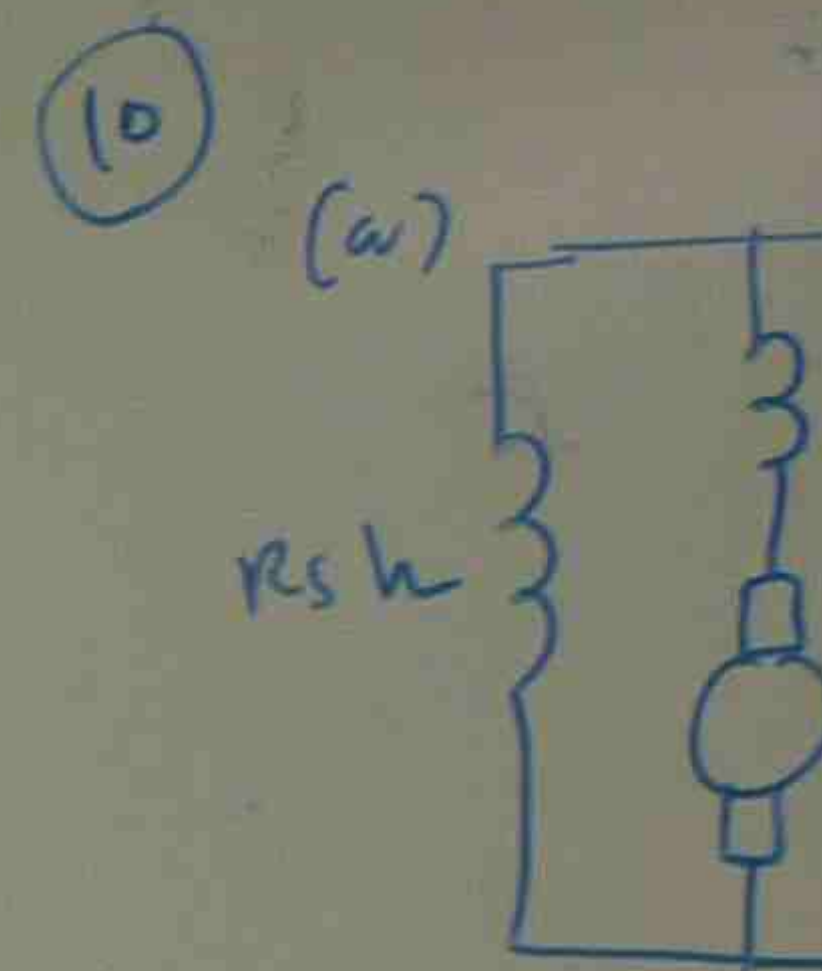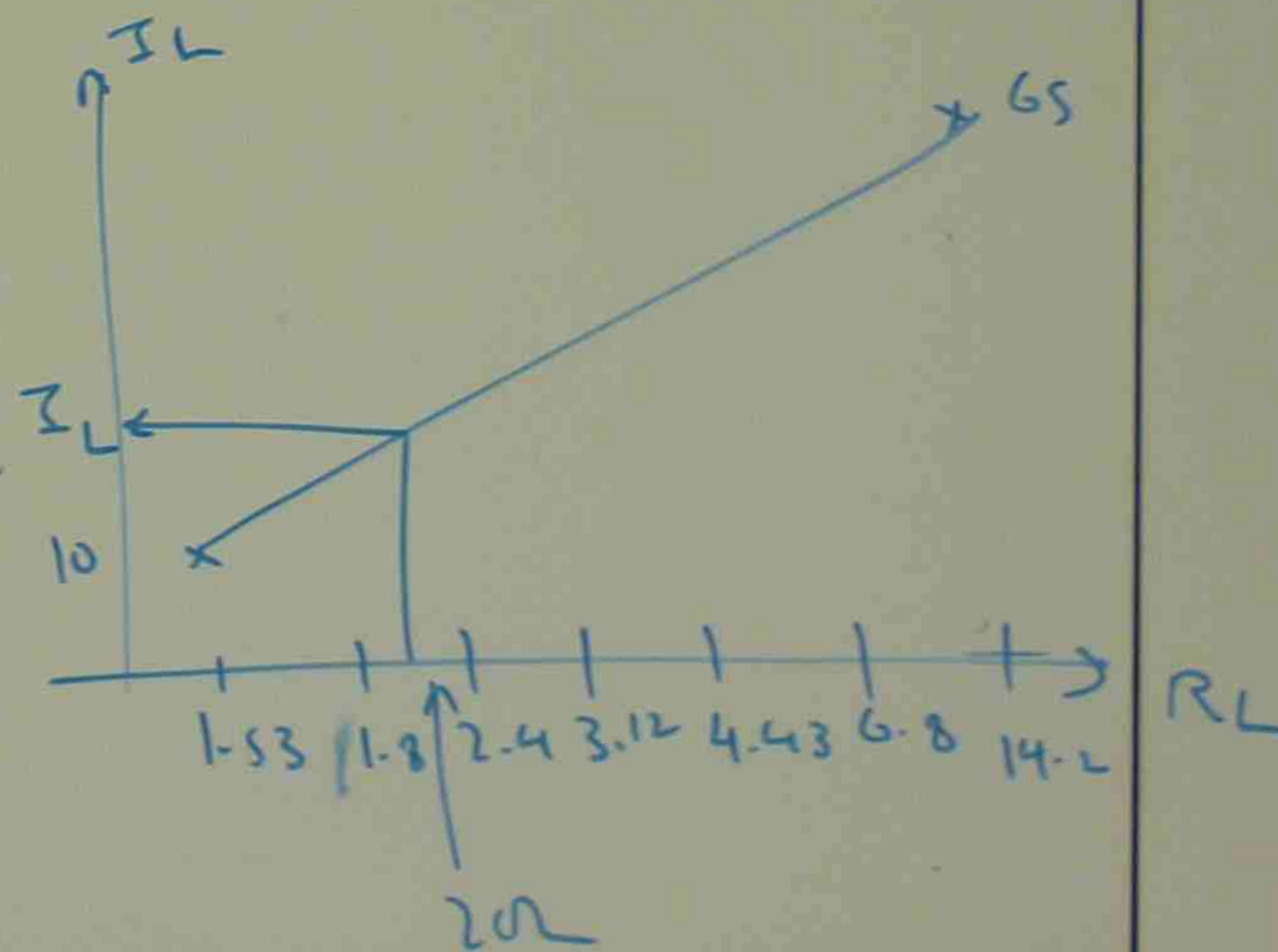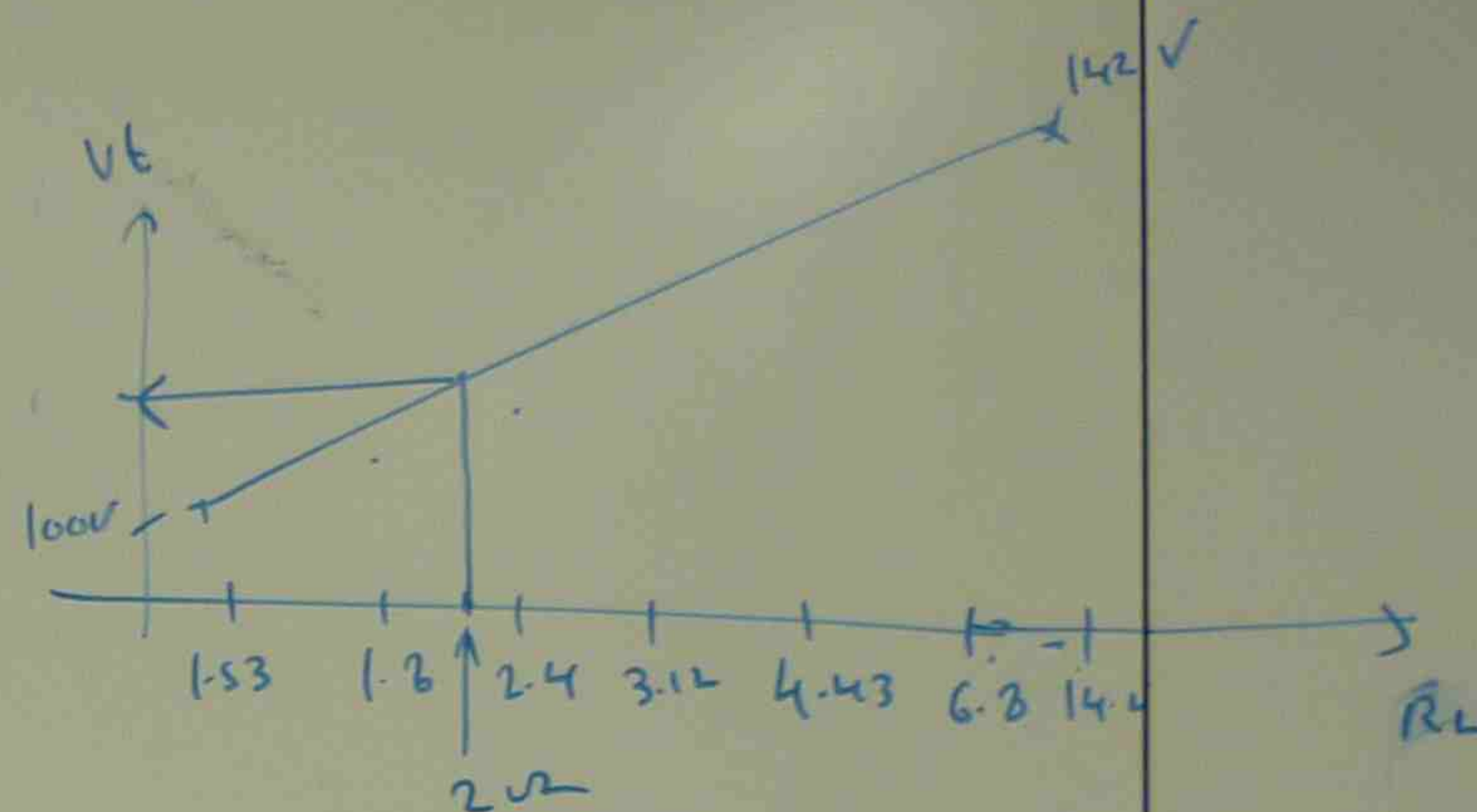


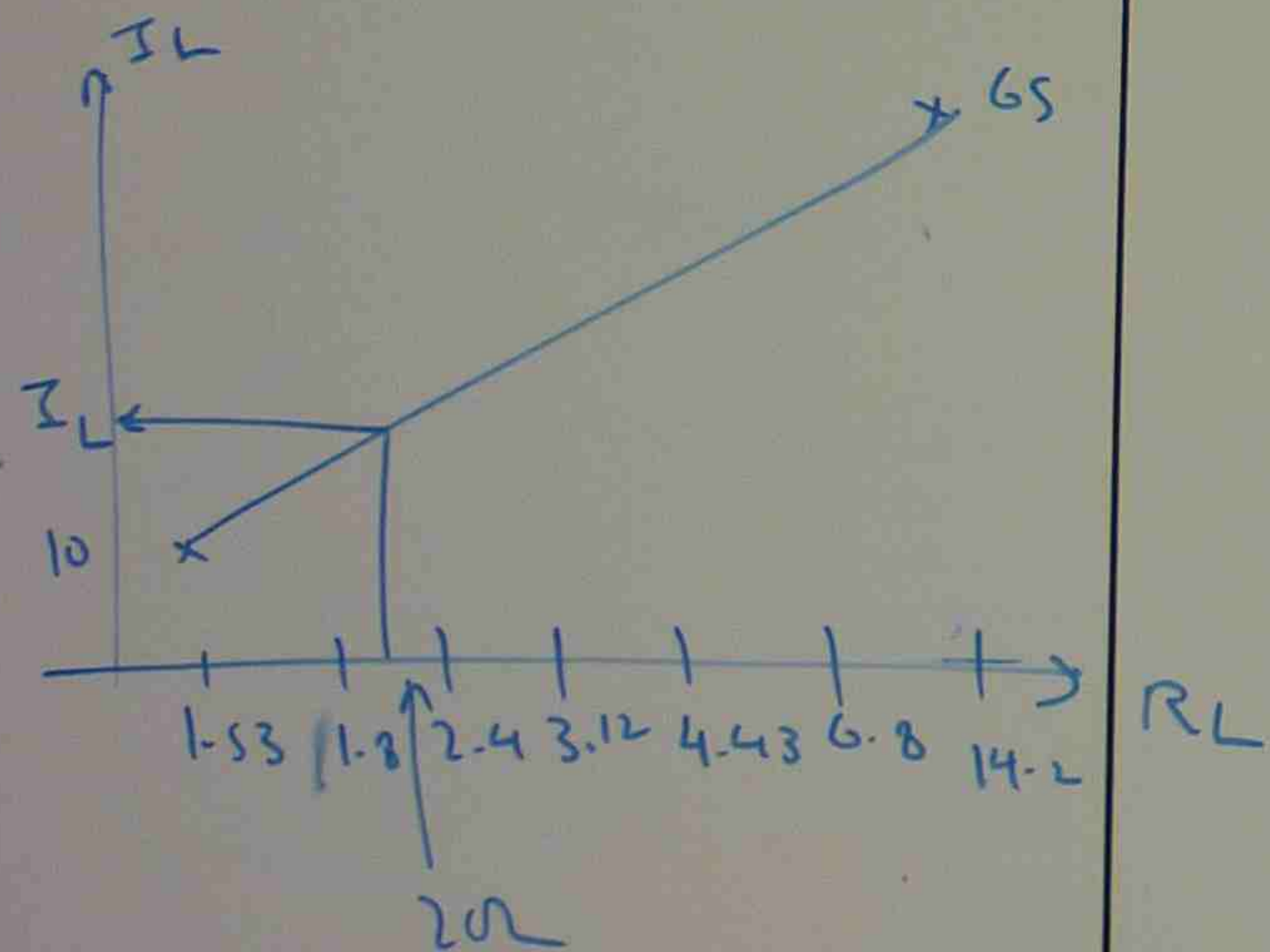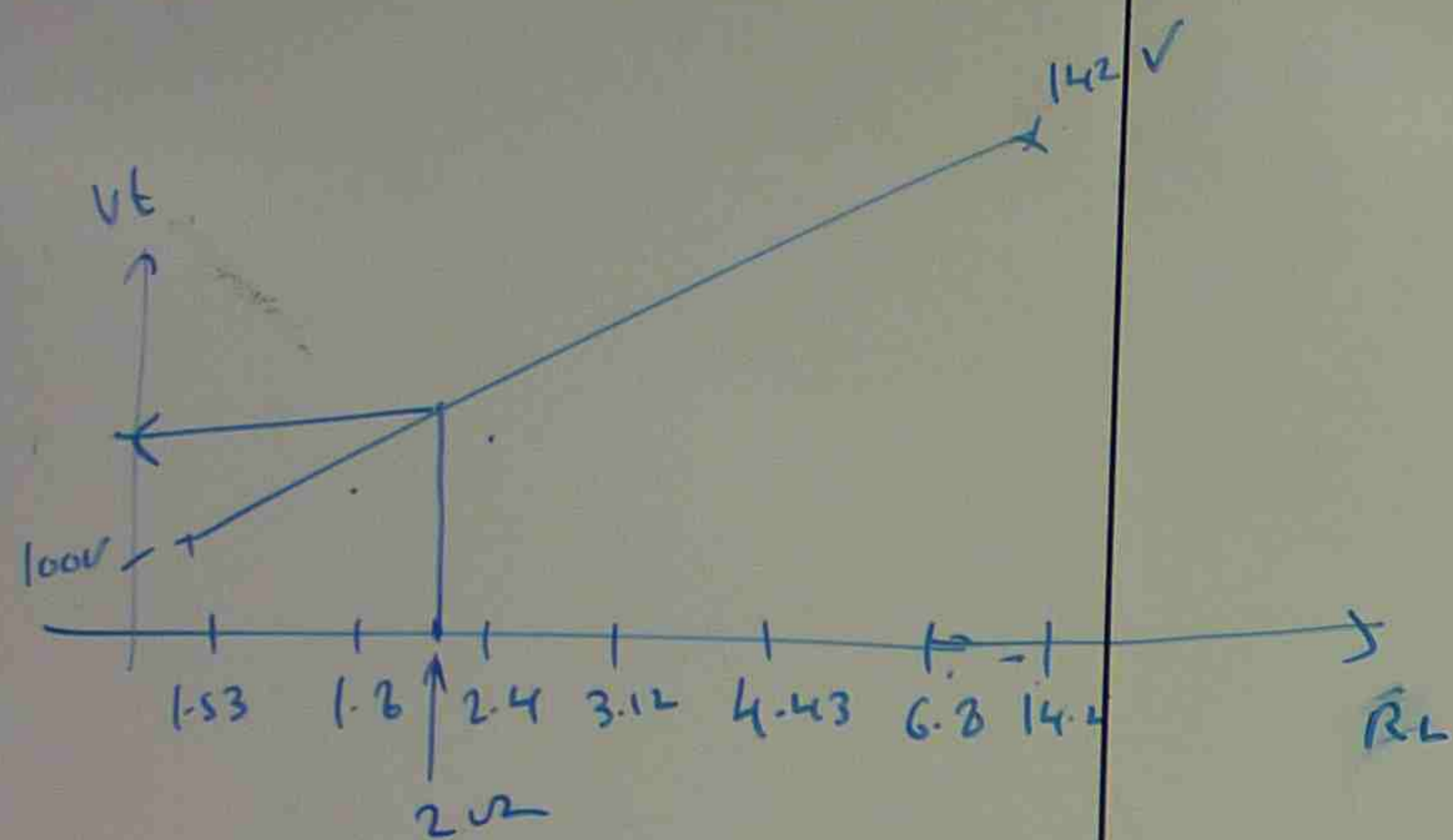


(10)

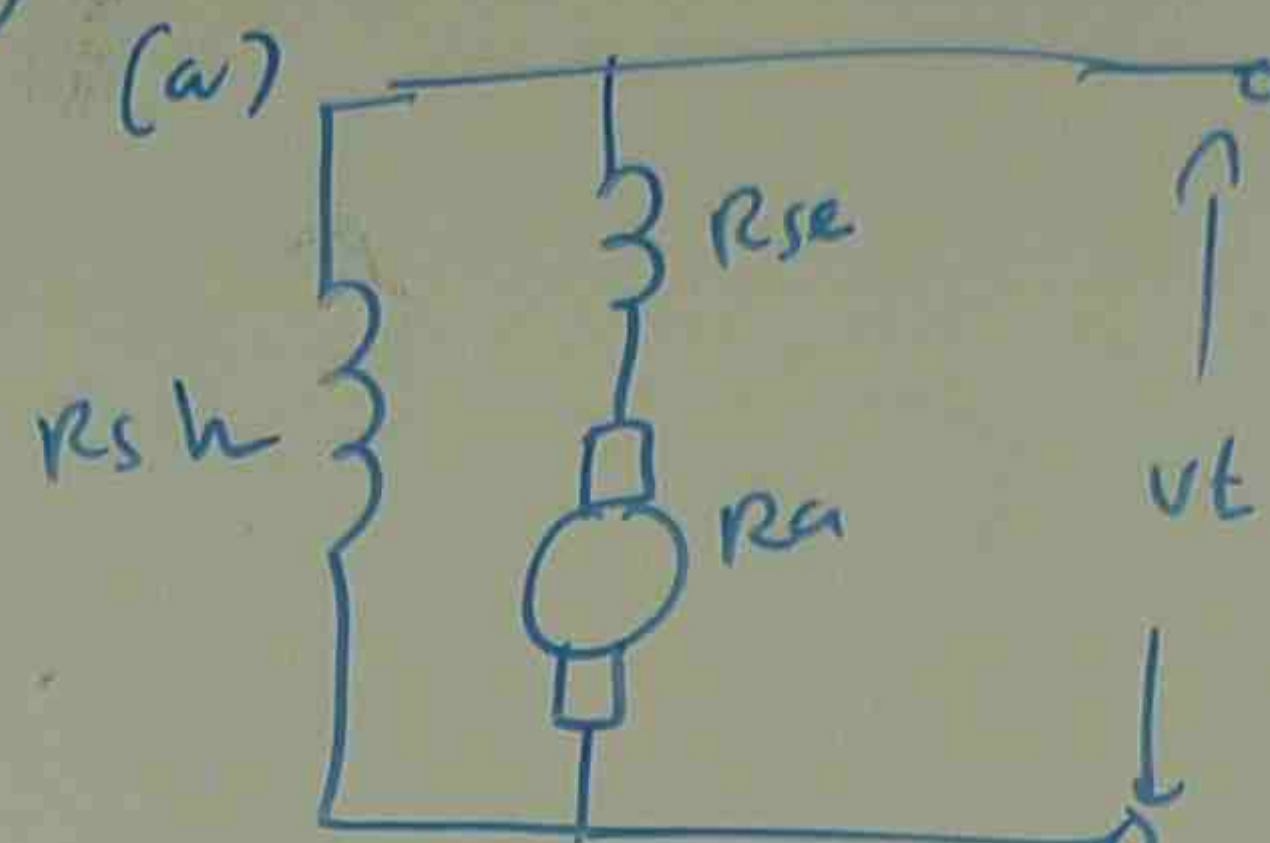


LONG SHUNT COMPOUND

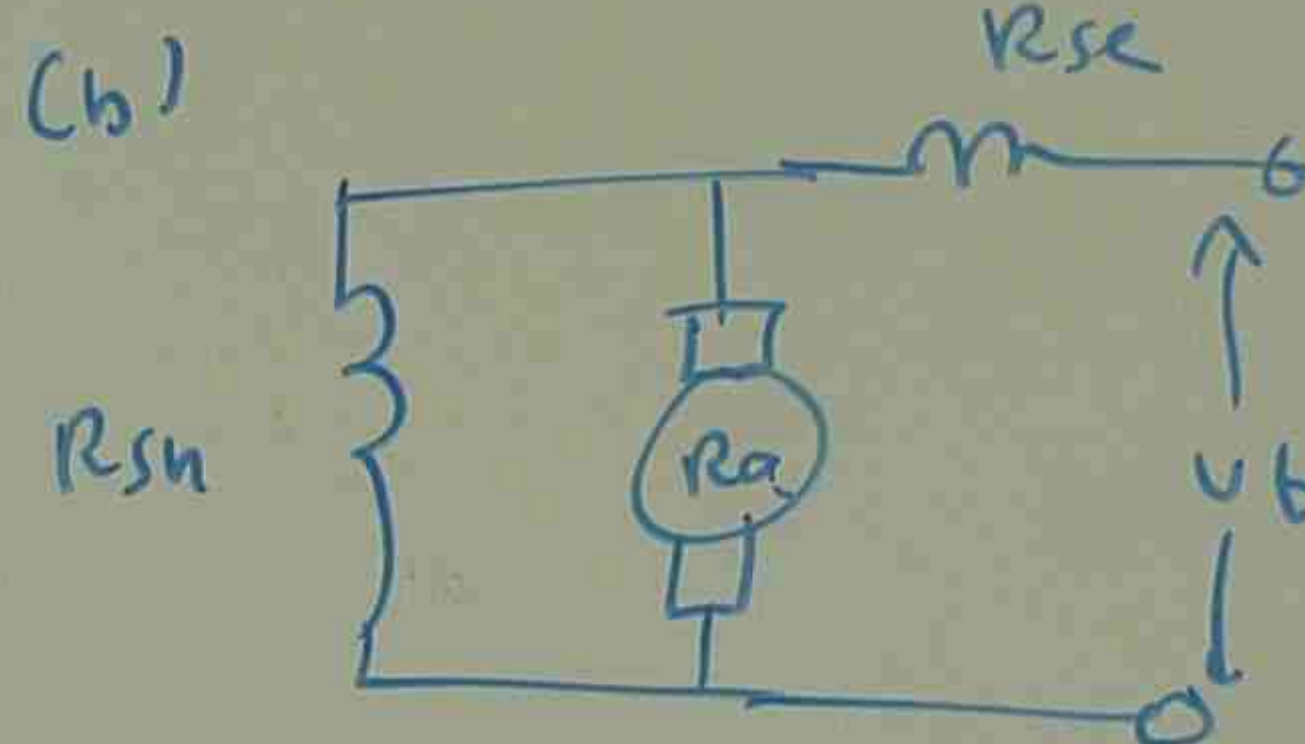


SHORT SHUNT COMPOUND

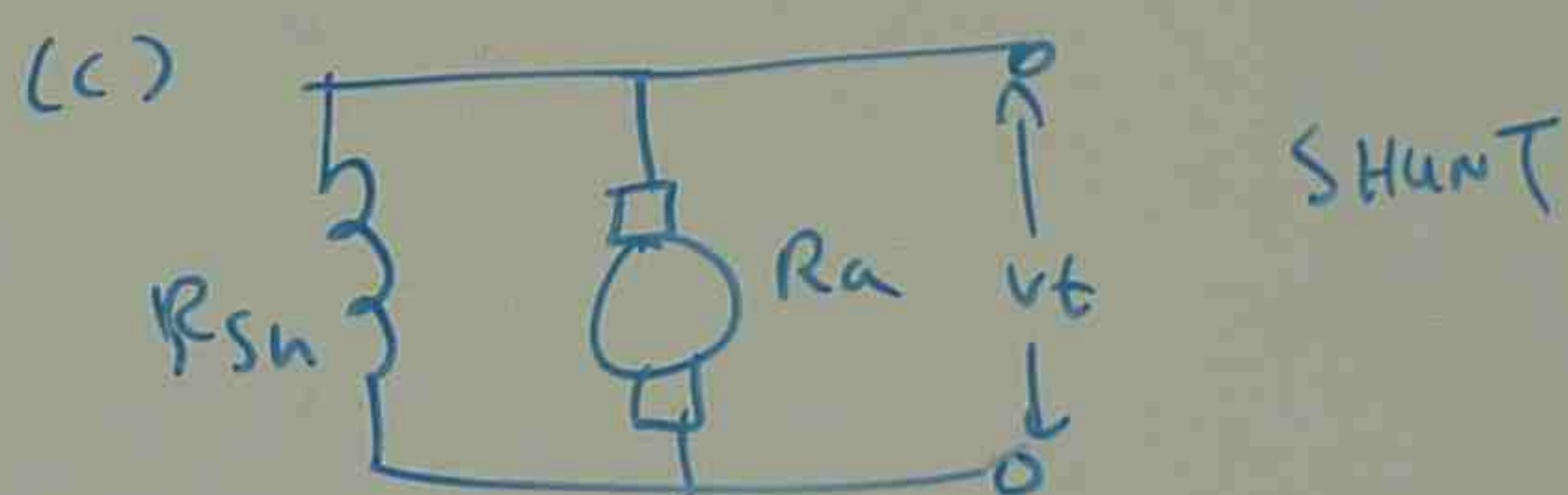

SHUNT

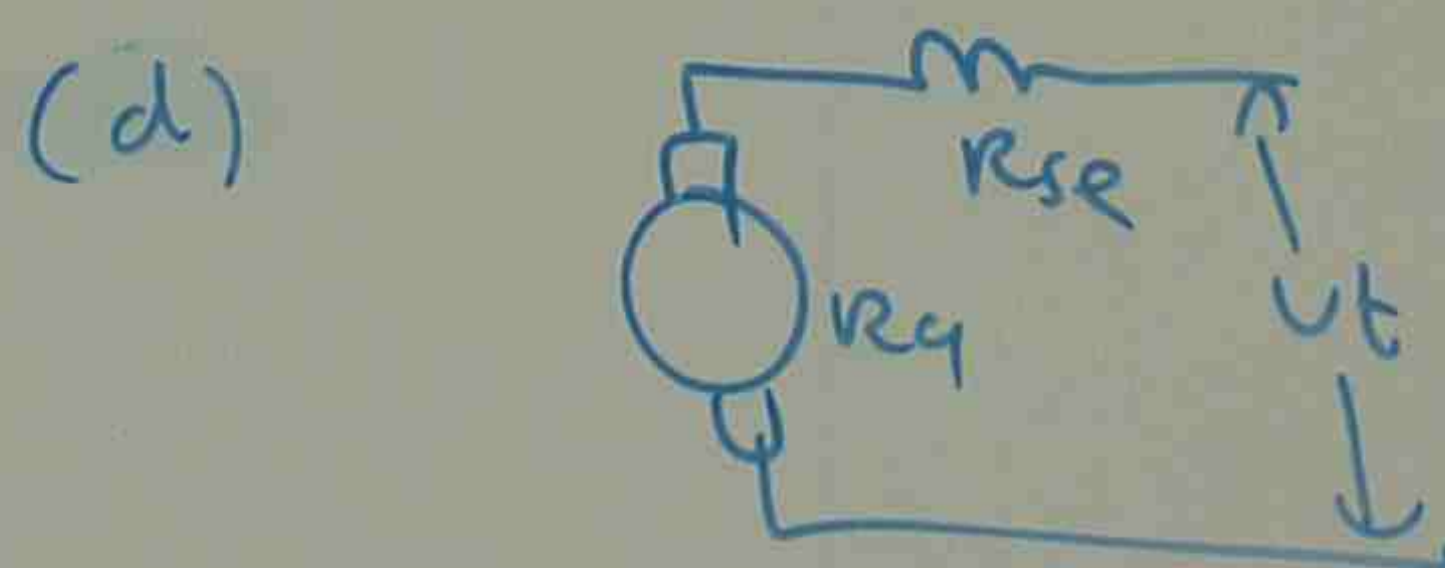

SERIES

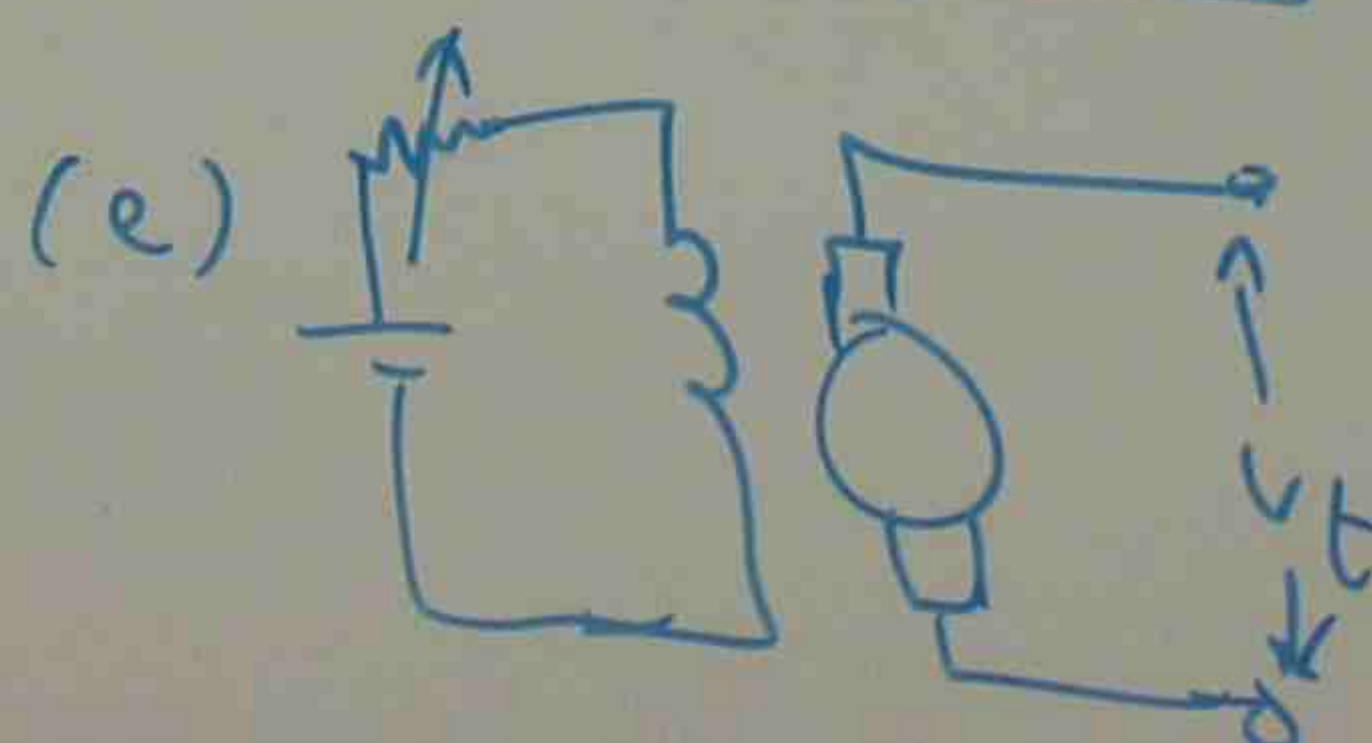

SEPARATELY
EXCITED

(5) $p = 4$, $z =$

$I_a = 31$

$T = ?$

$T = \frac{\phi z}{2\pi}$

$a = \text{No. of ARM
PARALLEL}$

$a = m$

$= 1$

$T = \frac{0.4}{2\pi}$

$= 1$

$$I_a = 800, p = 6$$

$$1.7 \text{ m}$$

(CROSS MAGNETIZING
AMP-TURNS)

$$\frac{\text{AT/pole}}{\text{pole}} \times \frac{2 I_a}{2ap}$$

$$1 \times 6 = 6$$

$$= \pi \cdot 7$$

$$= 3.1416 \times 0.5$$

$$\frac{5}{5} \times \frac{378 \times 800}{2 \times 6 \times 6}$$


$$\text{AT} / \text{pole}$$

$$\textcircled{7} \quad \% \text{ REG} = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100$$

$$15 = \frac{V_{NL} - 500}{500} \times 100$$

$$\frac{15 \times 500}{100} = V_{NL} - 500$$
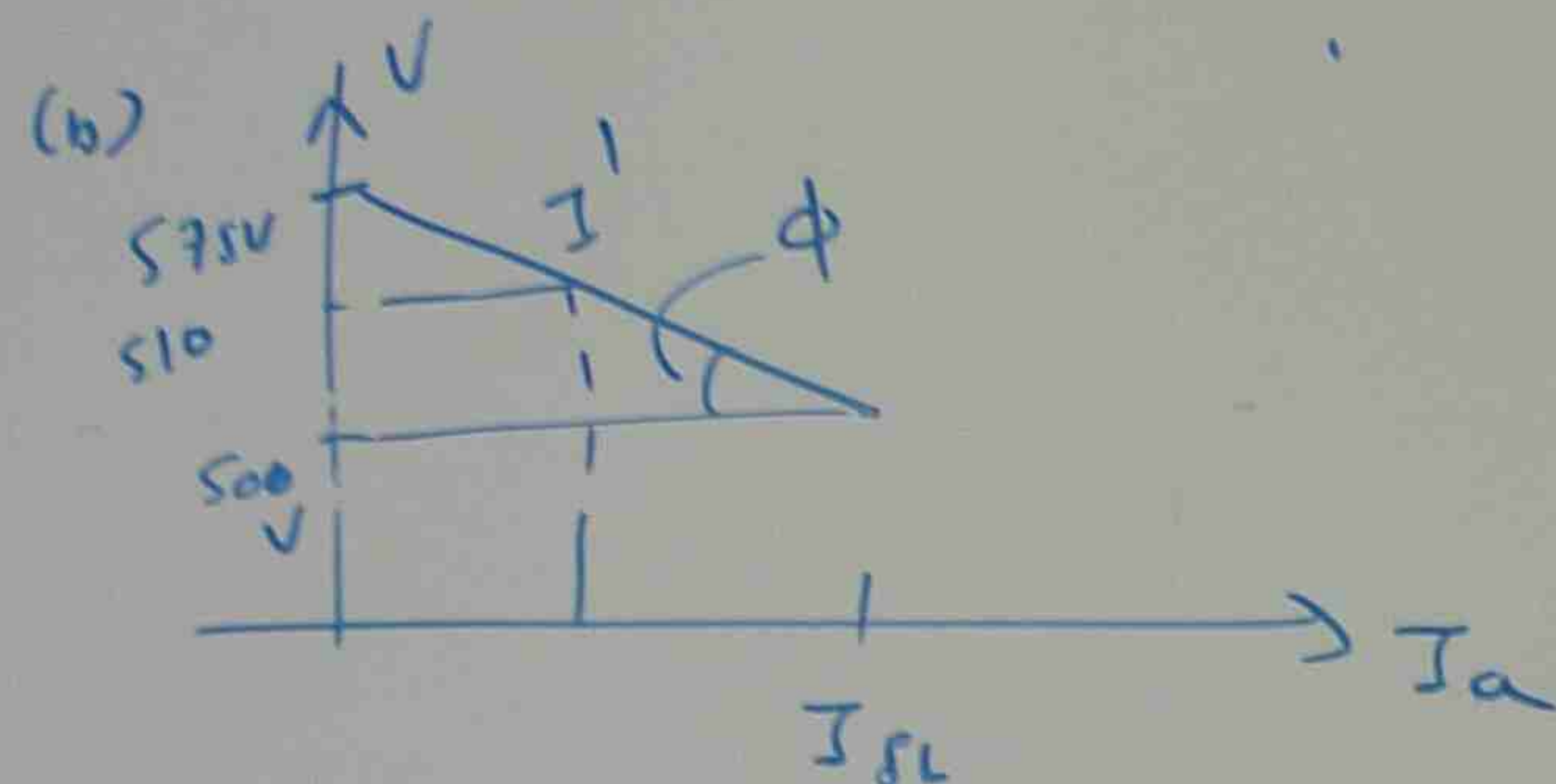
$$(a) \quad V_{NL} = \frac{15 \times 500}{100} + 500 = 575 \text{ V}$$



$$I_{FL} = \frac{\text{RATED POWER}}{\text{FULL LOAD TERMINAL VOLTAGE}}$$

$$= \frac{75 \times 1000}{500}$$

$$= 150 \text{ Amp.}$$

$$\phi = \text{GRADIENT} = \frac{V_1 - V_2}{I_1 - I_2} = \frac{575 - 500}{0 - 150}$$

$$= \frac{75}{-150} = -0.5$$

$$\text{GRADIENT} = \frac{V_1 - V}{I_1 - I'}$$

$$-0.5 = \frac{575 - 510}{0 - I'}$$

$$-0.5 \times (-I') = 65$$

$$I' = \frac{65}{0.5} = 130 \text{ Amp}$$

$$P_w = \frac{510 \times 130}{1000} = 66.3 \text{ kW}$$

$\textcircled{8}$ AC GENERATORS ARE NOW WIDELY
USED BECAUSE

(a) AC VOLTAGE CAN BE EASILY
CHANGED THE LEVEL

(b) IT IS EASIER TO MAINTAIN
AC GENERATORS

(c) HIGHER POWER & VOLTAGE
CAN BE PRODUCED BY AC GENERATOR
THAN DC GENERATOR.