

DC MOTOR CONTROL

SCR (Silicon Controlled Rectifier)


AC MOTOR SPEED CONTROL

DC MOTOR SPEED CONTROL

BLOCK DIAGRAM


AC INPUT

SCR UNIT


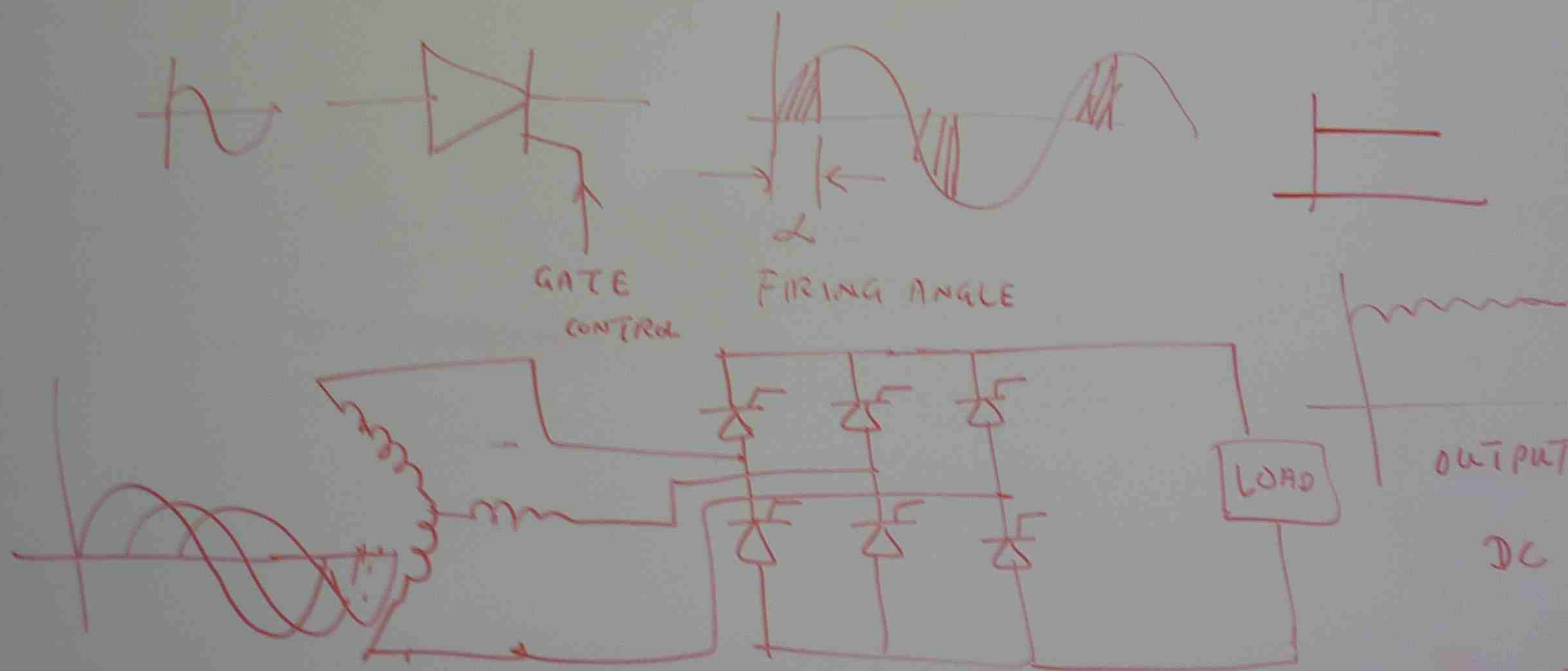


PRODUCED BY
HIGH FREQUENCY
SWITCHING PWM

BLOCK DIAGRAM OF SCR CONTROLLED MOTOR

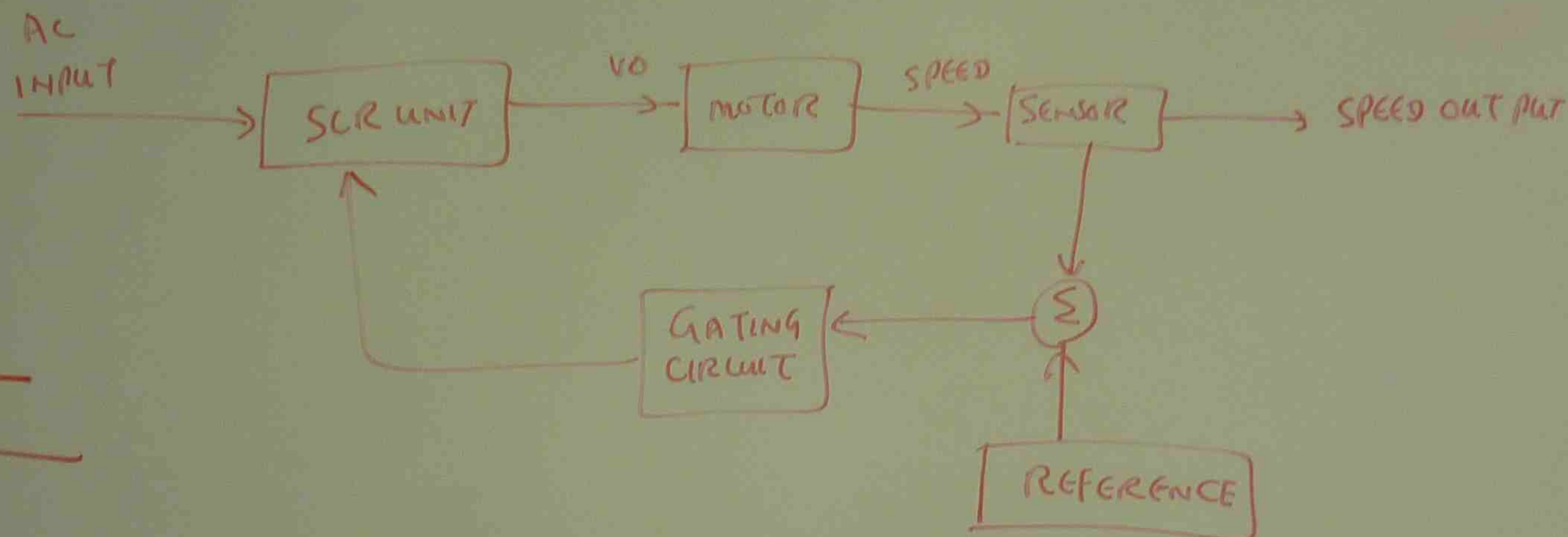

HEATING EFFECT OF RIPPLES

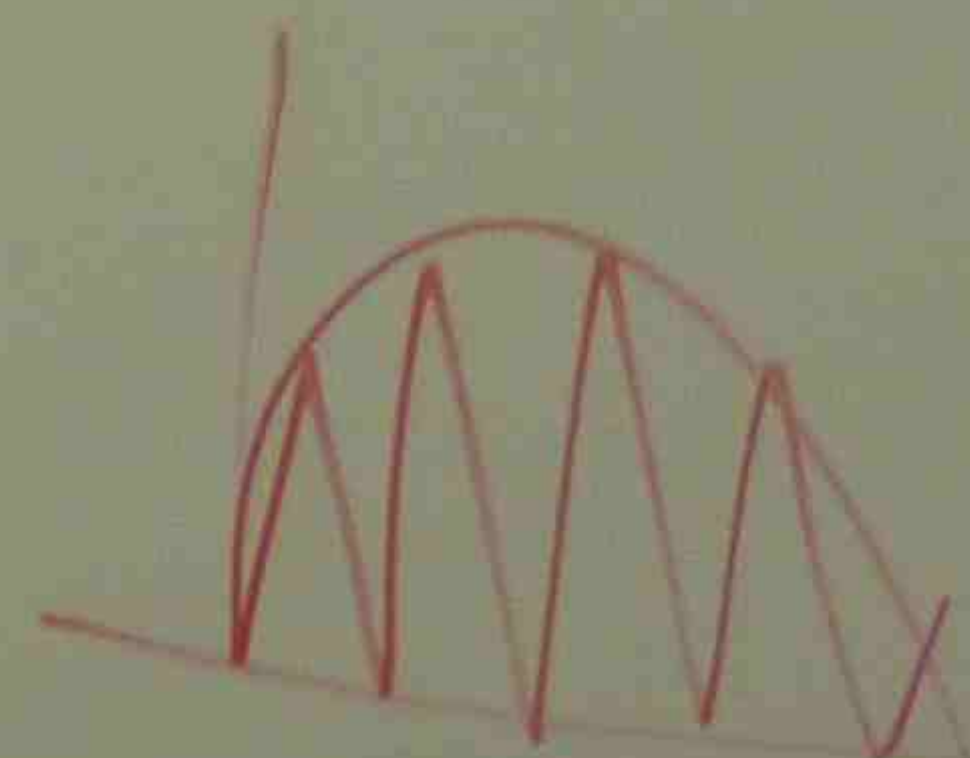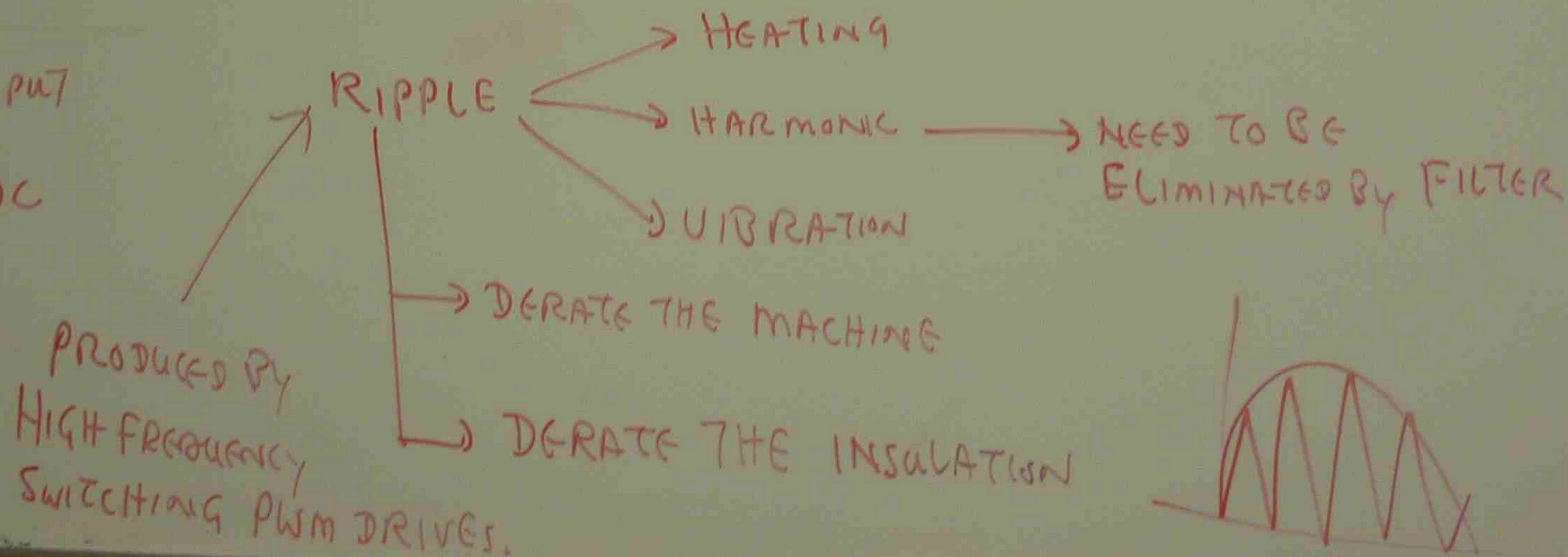


TOR OUT

$$k_t = \frac{P \cdot Z}{2\pi}$$

$$E_g = k_e$$


$$T = \frac{k_t \phi}{R_a}$$

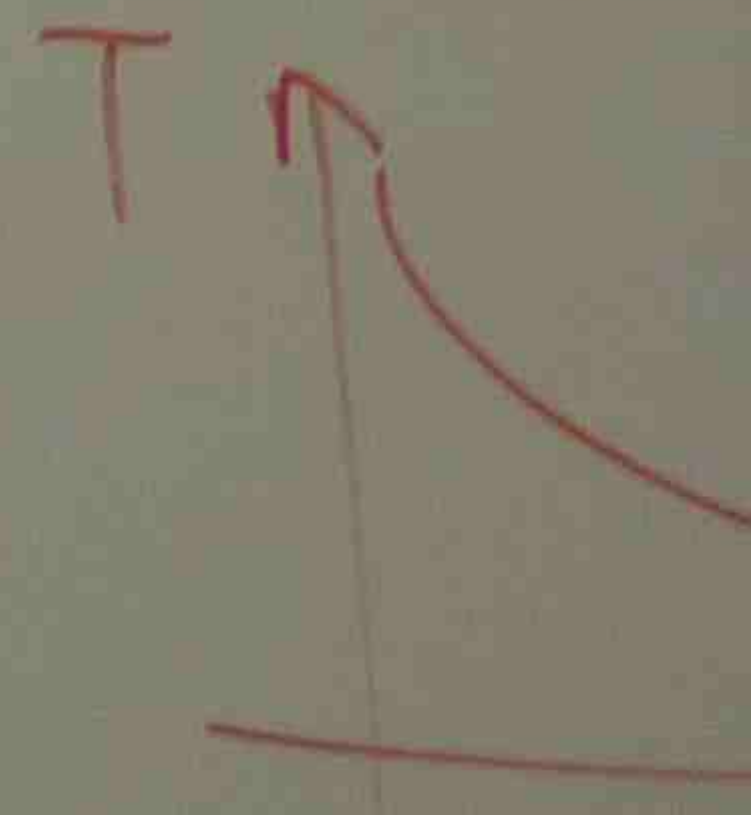


→ SPEED OUT PUT

ENCE

→ NEED TO BE ELIMINATED BY FILTER

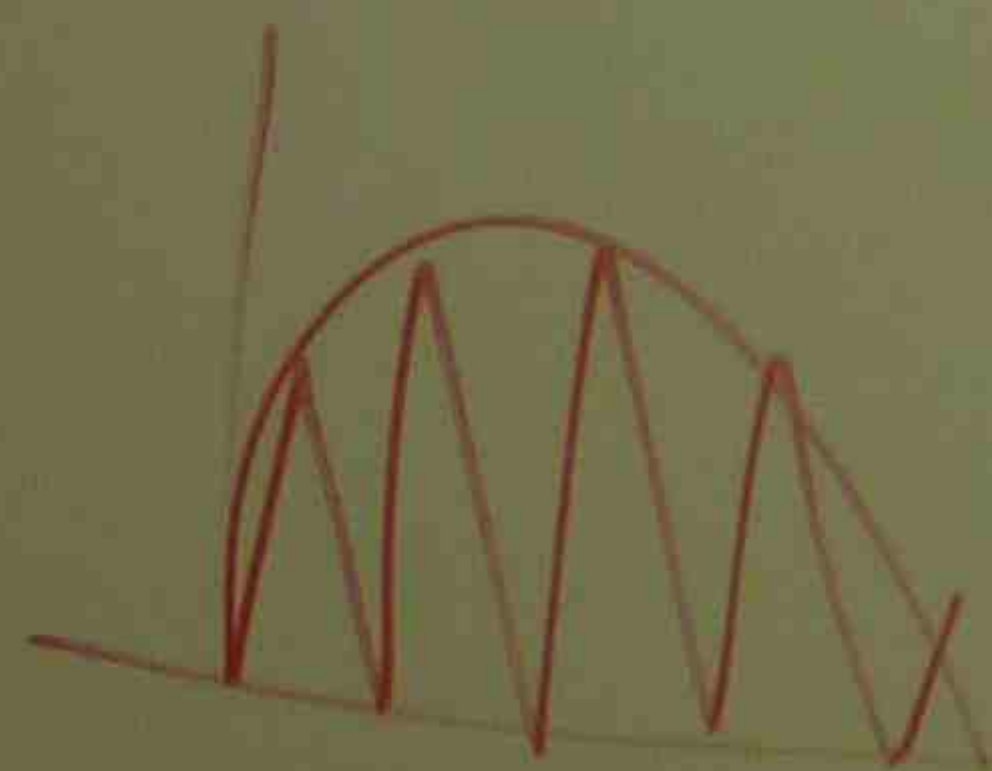

TORQUE - SPEED RELATIONSHIP

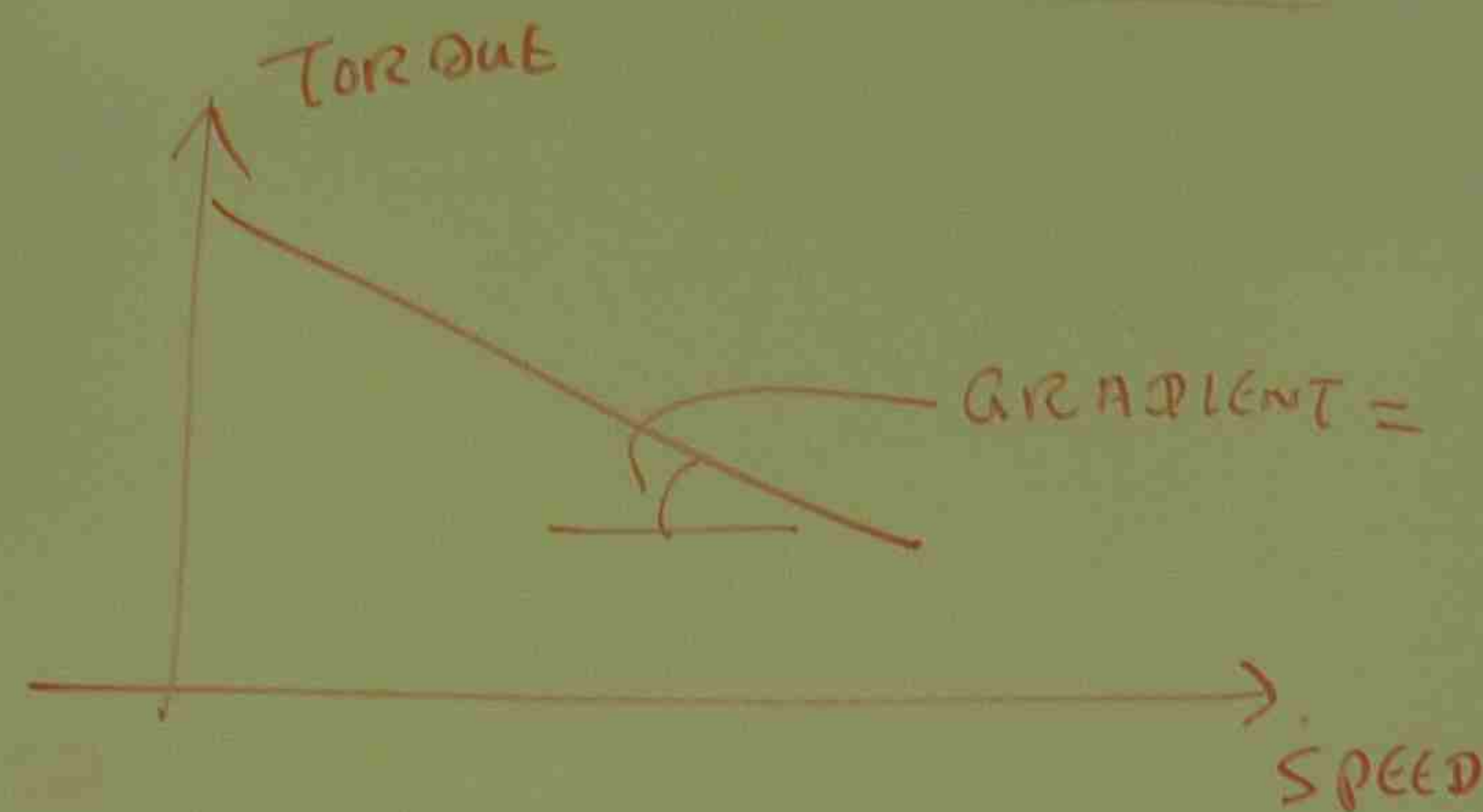

$$T = \frac{K_t \phi V_t}{R_a}$$

$$K_t = \frac{PZ}{2\pi a}, \quad K_e = \frac{PZ}{60a}$$

$$E_g = K_e \phi N$$

$$T = \frac{K_t \phi V_t}{R_a} - \frac{K_e K_t \phi^2 N}{R_a}$$



$T = \text{Torque}, \phi = \text{Flux}$
 $I_a = \text{ARMATURE CURRENT}$

$P = \text{NO. OF POLES}$

$Z = \text{ARMATURE CONDUCTORS}$

$a = \text{NO. OF ARMATURE PARALLEL PATHS.}$

$N = \text{SPEED}$

Pb A 4 POLES
 OF FLUX
 CONDUCTORS.

FUNCTION OF

$$T = \frac{K_t}{R_a}$$

$$K_t = \frac{PZ}{2\pi a}$$

$$K_e = \frac{PZ}{60a}$$

$$T =$$

$$T = \frac{k_t \phi V_t}{R_a}$$

$$\frac{k_e k_t \phi^2 R_a}{R_a}$$

Torque, ϕ = Flux
 Armature current
 No. of poles
 Armature conductors
 No. of armature parallel paths.
 Speed

Pb A 4 poles wound armature operating in a field of flux 0.01 webers is wound with 360 armature conductors. Determine the expression of Torque as a function of speed if $V_t = 250V$ and $R_a = 0.1 \Omega$.

$$T = \frac{k_t \phi V_t}{R_a} - \frac{k_e k_t \phi^2 R_a}{R_a}$$

$$k_t = \frac{P Z}{2 \pi a} = \frac{4 \times 360}{2 \times 3.1416 \times 2} = 114.5$$

$$a = 2 \text{ m} \quad \text{wave}$$

$$= 2 \times 1 = 2$$

$$k_e = \frac{P Z}{60 a} = \frac{4 \times 360}{60 \times 2} = 12$$

$$T = \frac{114.5 \times 0.01 \times 250}{0.1} - \frac{12 \times 114.5 \times (0.01)^2 \times 0.1}{0.1}$$

$$= 2860 - 1.38 \text{ N}$$

Duty Cycle

As well as
 of develop
 load at
 must be ab
 suffer an
 the heat
 currents
 the heati
 the rms


Pb 2

DUTY CYCLE

AS WELL AS SELECTING A MOTOR THAT IS CAPABLE OF DEVELOPING THE SUFFICIENT TORQUE TO DRIVE A LOAD AT THE REQUIRED SPEED, THE MOTOR SO CHOSEN MUST BE ABLE TO PROVIDE THIS TORQUE AND NOT SUFFER ANY UNDUE DAMAGE AS A CONSEQUENCE TO THE HEAT PRODUCED WITHIN THE MACHINE BY THE CURRENTS IN VARIOUS WINDINGS.

THE HEATING EFFECT IS THE FUNCTION OF R.M.S. THE RMS VALUE OF THE LOAD MUST BE OBTAINED.

Pb

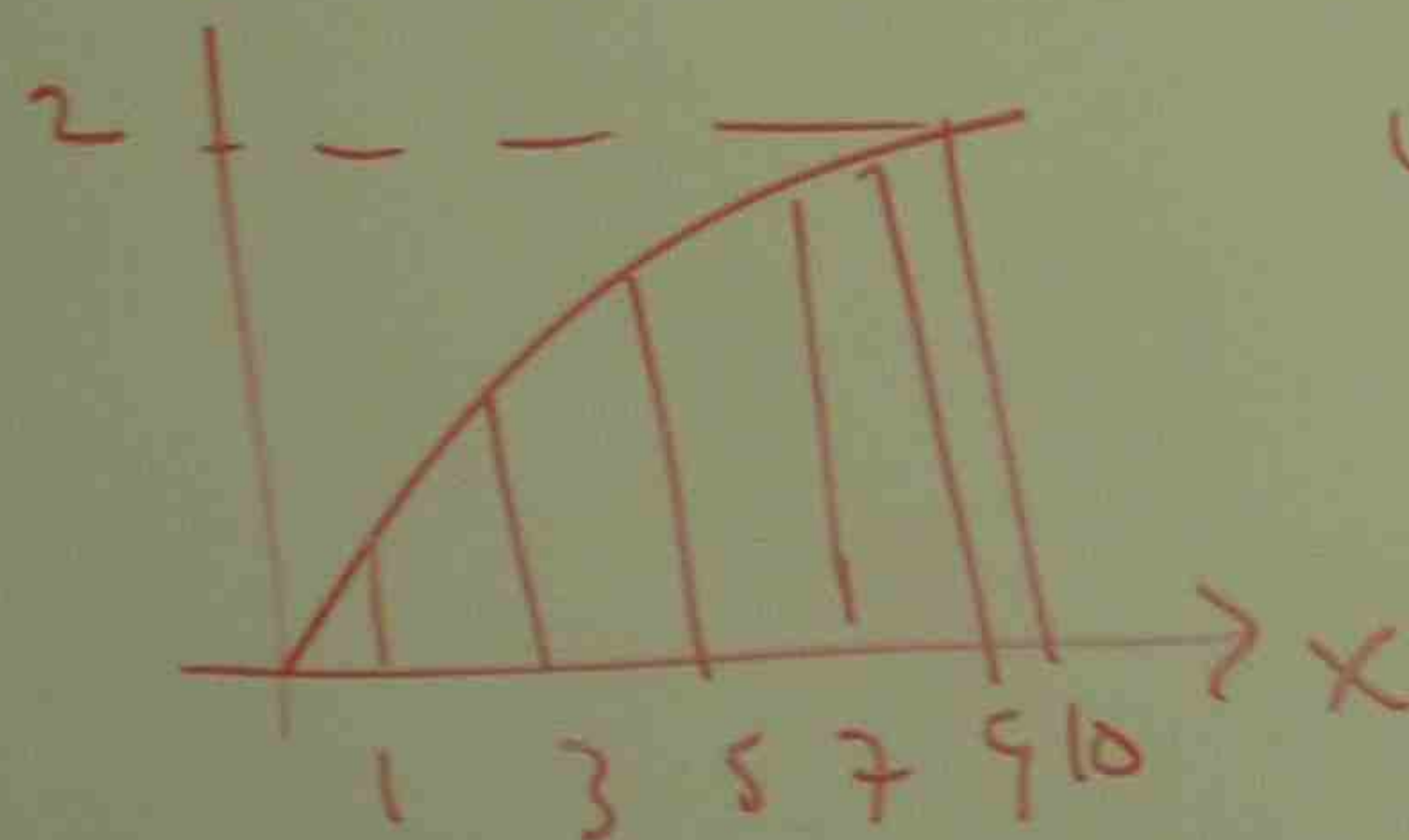

$$y = 0.2x$$

Find RMS

$$RMS = \sqrt{\frac{1}{y} \int_0^y y^2 dx}$$

$$y = 10$$

$$RMS = \sqrt{\frac{1}{10} \int_0^{10} (0.2x)^2 dx}$$

$$= \sqrt{\frac{1}{10} \int_0^{10} 0.04 x^2 dx}$$

$$= \sqrt{\frac{1}{10} \times 0.04 \int_0^{10} x^2 dx}$$

$$= \sqrt{\frac{1}{10} \times 0.04 \times \left[\frac{x^3}{3} \right]_0^{10}}$$


$$= \sqrt{\frac{1}{10} \times 0.04 \times \frac{10^3}{3}}$$

$$= 1.153$$

DUTY CYCLE


AS WELL AS SELECTING A MOTOR THAT IS CAPABLE OF DEVELOPING THE SUFFICIENT TORQUE TO DRIVE A LOAD AT THE REQUIRED SPEED, THE MOTOR SO CHOSEN MUST BE ABLE TO PROVIDE THIS TORQUE AND NOT SUFFER ANY UNDUE DAMAGE AS A CONSEQUENCE TO THE HEAT PRODUCED WITHIN THE MACHINE BY THE CURRENTS IN VARIOUS WINDINGS.

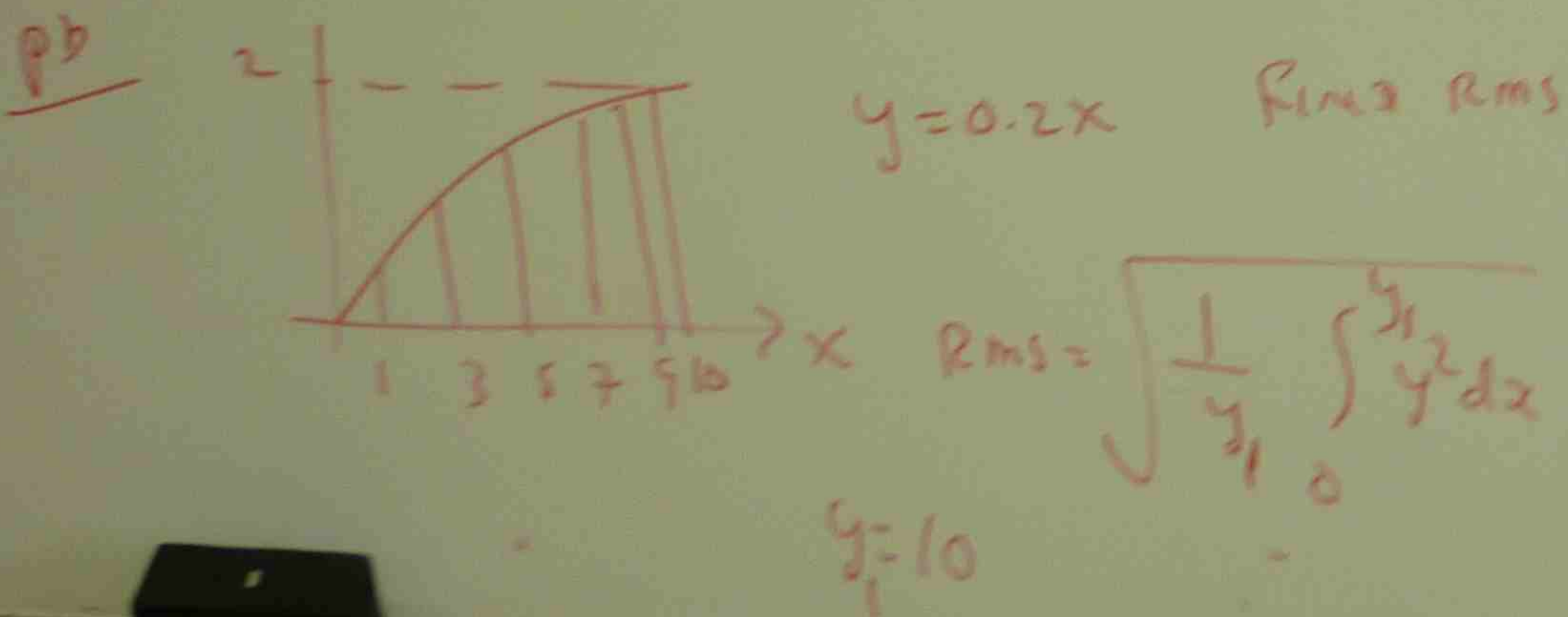THE HEATING EFFECT IS THE FUNCTION OF R.M.S. THE R.M.S VALUE OF THE LOAD MUST BE OBTAINED.



$$\begin{aligned} RMS &= \sqrt{\frac{1}{10} \int_0^{10} (0.2x)^2 dx} \\ &= \sqrt{\frac{1}{10} \int_0^{10} 0.04 x^2 dx} \\ &= \sqrt{\frac{1}{10} \times 0.04 \int_0^{10} x^2 dx} \\ &= \sqrt{\frac{1}{10} \times 0.04 \times \left[\frac{x^3}{3} \right]_0^{10}} \\ &= \sqrt{\frac{1}{10} \times 0.04 \times \frac{10^3}{3}} \\ &= 1.153 \end{aligned}$$

pb FIND RMS VALUE OF THE GIVEN GRAPH

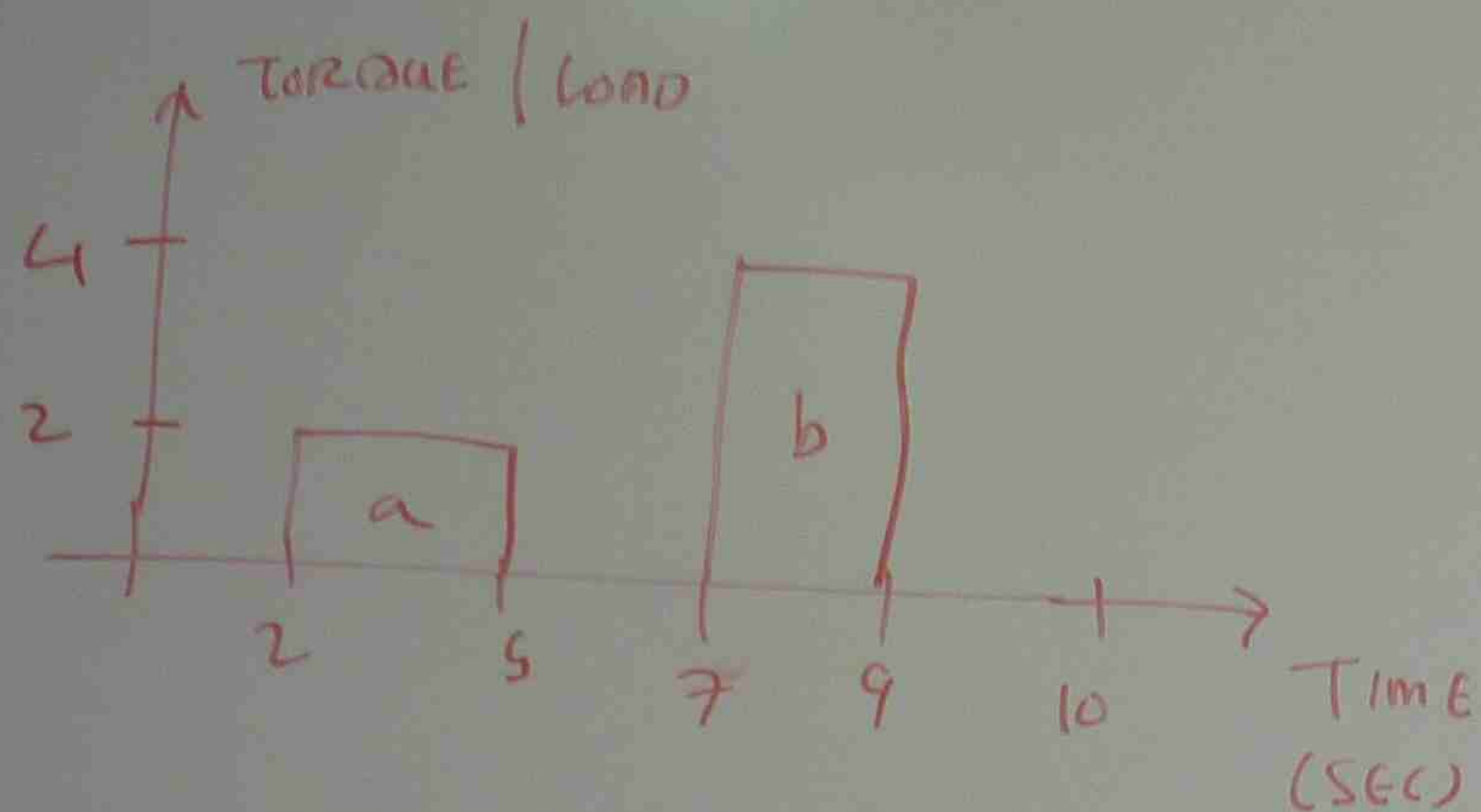

SECTION	DURATION	VALUE	AREA
a	2 → 5 (5-2=3) 3 Sec	2	DURATION × VALUE 3 × 2 = 6
b	7 → 9 (9-7=2) 2 Sec	4	4 × 2 = 8
		TOTAL	14

$$\text{AVERAGE} = \frac{\text{TOTAL AREA}}{\text{TOTAL DURATION}}$$

$$= \frac{14}{10}$$



$$= 1.4$$

$$\text{RMS} = \sqrt{\text{AVERAGE}}$$

$$= \sqrt{1.4}$$

$$= 1.183$$

DC MOTOR STARTERS

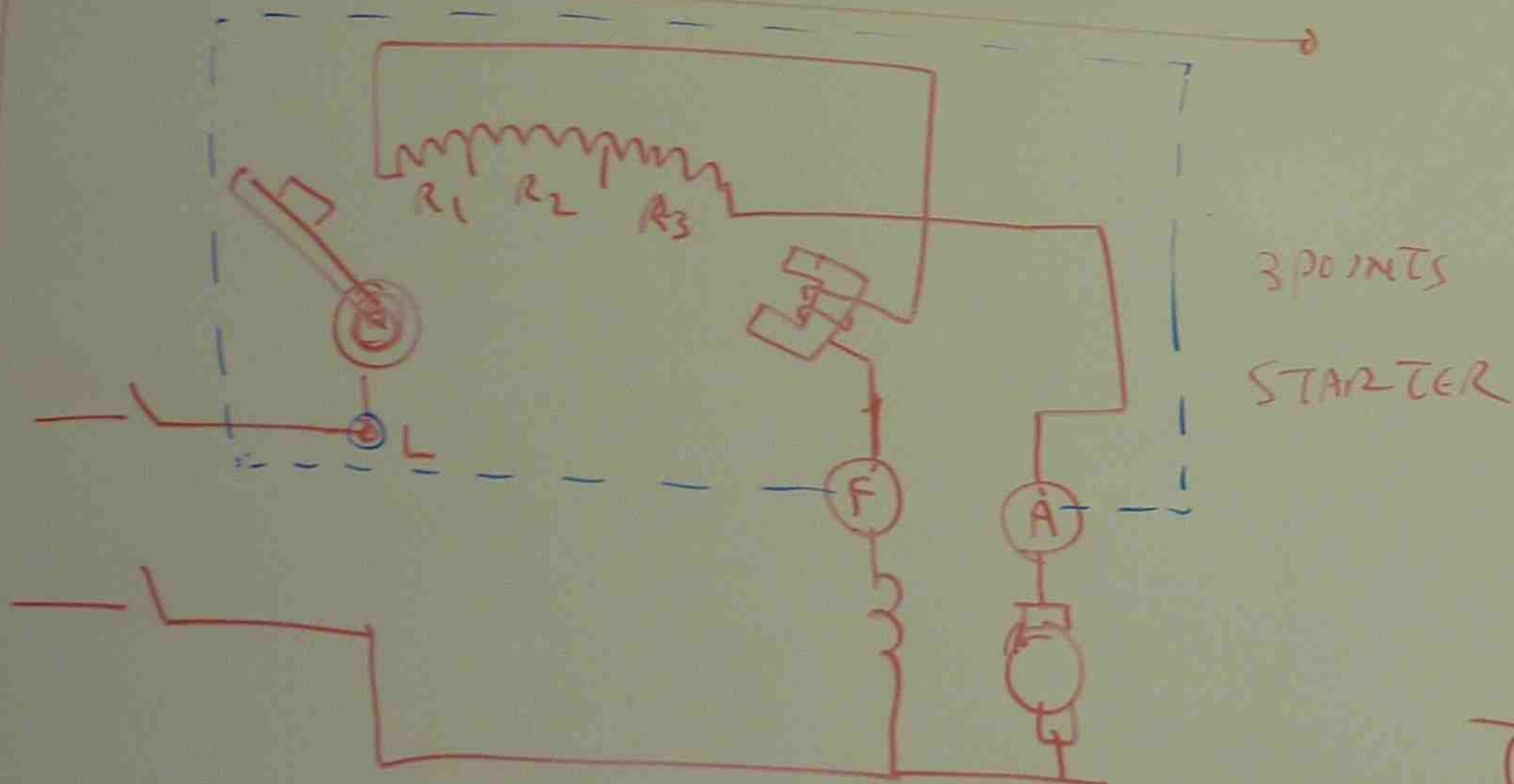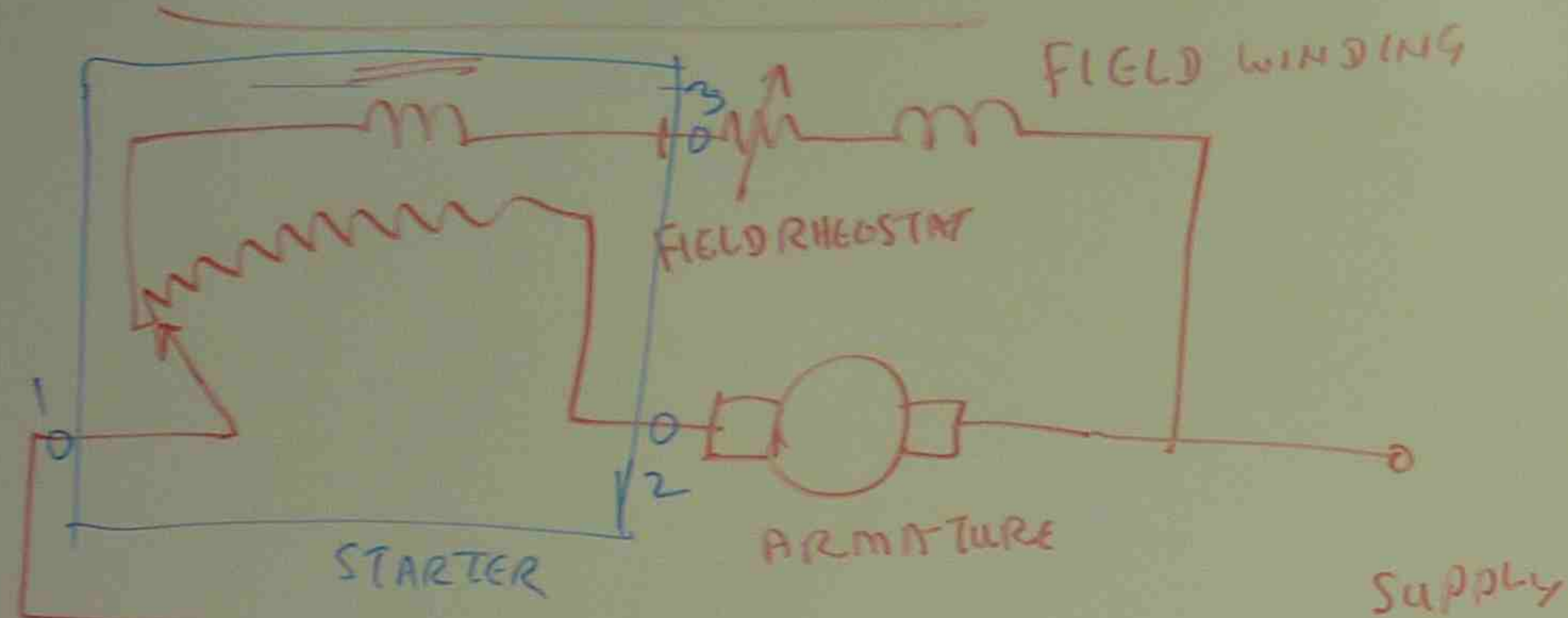

$$\left(\frac{I_{\max}}{I_{\min}} \right)^{n+1} = \frac{V_t}{I_r R_a}$$

n = NUMBERS OF STEPS

R_a = ARMATURE RESISTANCE

I_r = FULL LOAD CURRENT

$$\frac{I_s}{I_r} = \frac{R_k}{R_{k+1}}$$

I_s = INITIAL RESISTANCE STEP CURRENT (R_k)

I_r = FINAL RESISTANCE STEP CURRENT (R_{k+1})

Pb THE RESISTANCE OF THE ARMATURE OF A 240V DC SHUNT MOTOR IS 0.5Ω . IT IS REQUIRED THAT THE CURRENT AT STARTING BE LIMITED TO 200% OF FULL LOAD CURRENT AND FULL LOAD CURRENT IS 15 AMP.

DETERMINE (a) TOTAL RESISTANCE OF ARMATURE CIRCUIT AT STARTING

(b) THE NUMBERS OF STUDS ON THE STARTER

(c) RESISTANCE BETWEEN EACH STUD.

$$R_a = 0.5 \Omega \quad V_t = 240V, \quad I_r = 15 \text{ Amp}$$

$$I_s = 200\% I_r = 2 \times 15 = 30 \text{ Amp}$$

$$\left(\frac{I_{\max}}{I_{\min}} \right)^{n+1} = \frac{V_t}{I_r R_a}$$


$$\left(\frac{30}{15} \right)^{n+1} = \frac{240}{15 \times 0.5}$$

$$2^{n+1} = 32$$

$$\log 2^{n+1} = \log 32$$

$$(n+1) \log 2 = \log 32$$

$$n = \frac{\log 32}{\log 2}$$

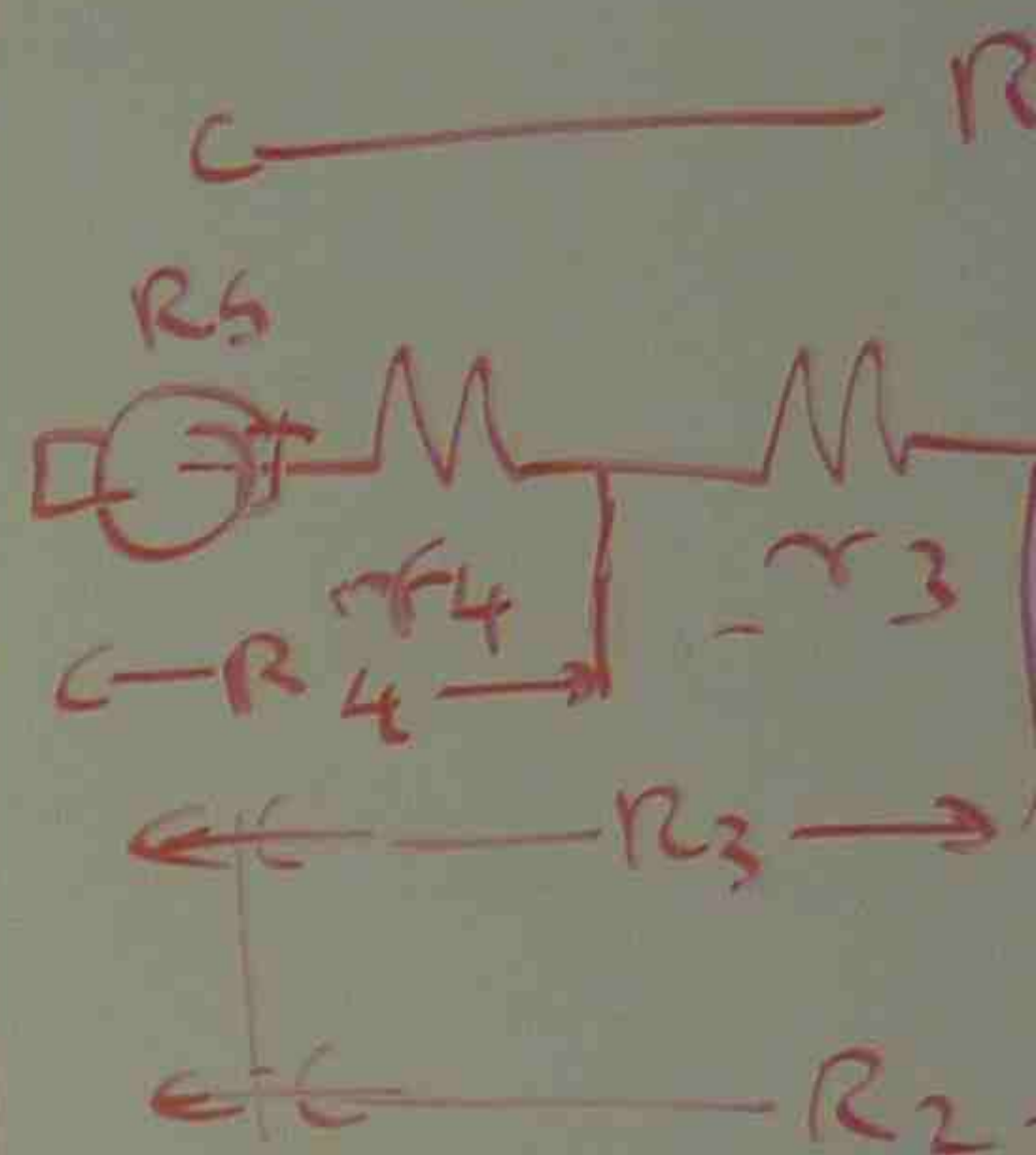


$$r_1 = R_1 - R$$

$$r_2 = R_2 - R$$

$$r_3 = R_3 - R$$

$$r_4 = R_4$$

$$n = \frac{\log 32}{\log 2} - 1 = 4$$

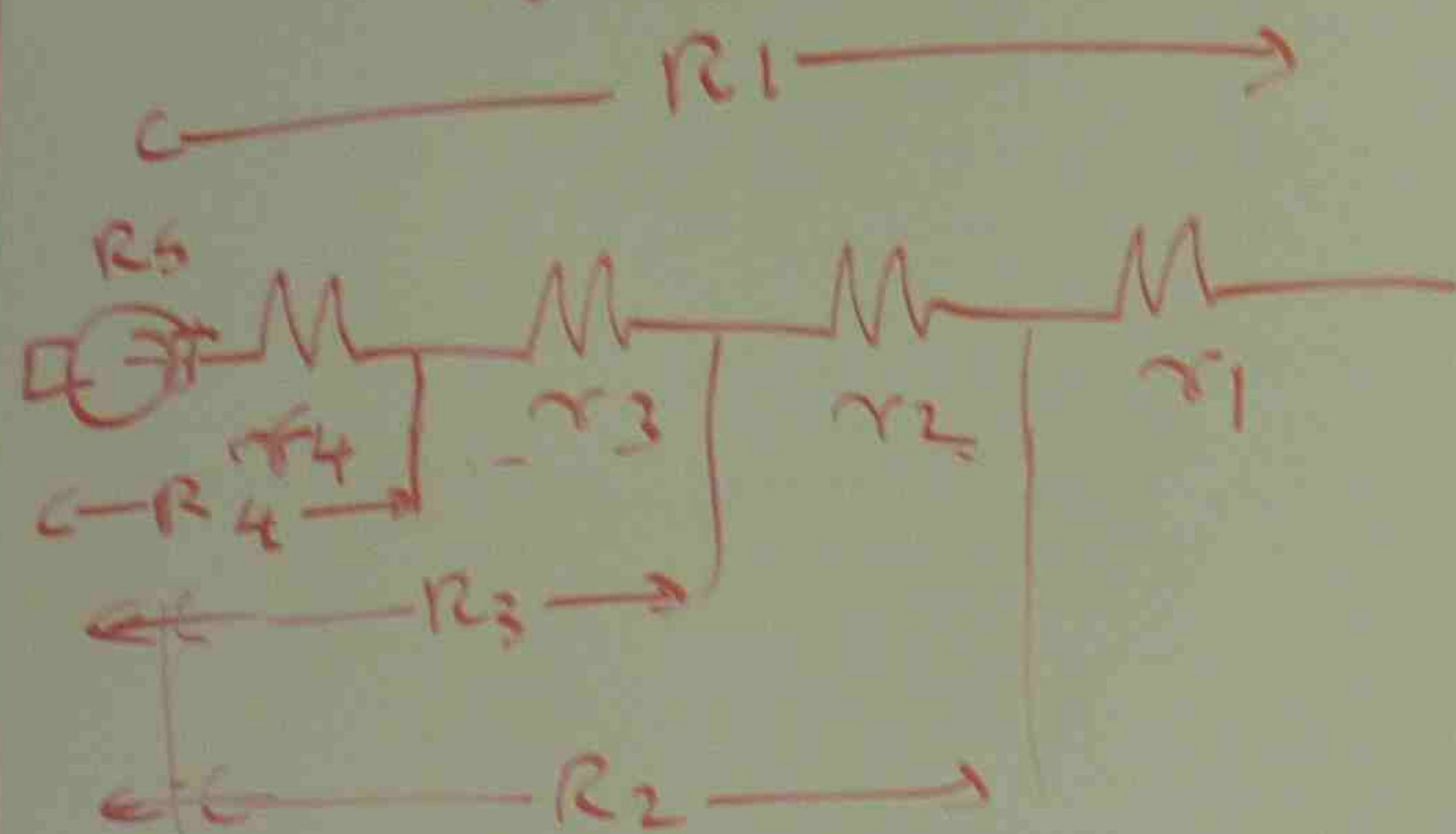

$$V_1 = R_1 - R_2$$

$$V_2 = R_2 - R_3$$

$$V_3 = R_3 - R_4$$

$$V_4 = R_4$$

$$\frac{I_s}{I_r} = \frac{R_k}{R_{k+1}}$$

$$\frac{30}{15} = \frac{R_k}{R_{k+1}}$$

$$2 = \frac{R_k}{R_{k+1}}$$

$$R_1 = \frac{V_t}{I_s}$$

$$= \frac{240}{30} = 8 \Omega$$

$$\frac{R_k}{R_{k+1}} = 2$$

$$k=1 \rightarrow \frac{R_1}{R_{1+1}} = 2$$

$$\frac{R_1}{R_2} = 2$$

$$\frac{8}{R_2} = 2$$

$$R_2 = \frac{8}{2} = 4 \Omega$$

$$k=2$$

$$\frac{R_2}{R_{2+1}} =$$

$$\frac{R_2}{R_3} =$$

$$\frac{4}{R_3} =$$

$$R_3 = \frac{4}{2}$$

$$k=3$$

$$\frac{R}{R_3} =$$

$$\frac{R_3}{R_4} =$$

$$\frac{2}{R_4} =$$

$$R_4 =$$

$$R_4 =$$

$$k=4 =$$

$$\frac{R_4}{R_5} =$$

$$R_5 =$$

$$\frac{I_s}{I_r} = \frac{R_k}{R_{k+1}}$$

$$\frac{30}{15} = \frac{R_k}{R_{k+1}}$$

$$2 = \frac{R_k}{R_{k+1}}$$

$$R_1 = \frac{V_t}{I_s}$$

$$= \frac{240}{30} = 8 \Omega$$

$$\frac{R_k}{R_{k+1}} = 2$$

$$\rightarrow \frac{R_1}{R_2} = 2$$

$$\frac{R_1}{R_2} = 2$$

$$\frac{8}{R_2} = 2$$

$$R_2 = \frac{8}{2} = 4 \Omega$$

$$k=2 \quad \frac{R_2}{R_{2+1}} = 2$$

$$\frac{R_2}{R_3} = 2$$

$$\frac{4}{R_3} = 2$$

$$R_3 = \frac{4}{2} = 2 \Omega$$

$$k=3 \quad \frac{R_3}{R_{3+1}} = 2$$

$$\frac{R_3}{R_4} = 2$$

$$\frac{2}{R_4} = 2$$

$$R_4 = \frac{2}{2} = 1 \Omega$$

$$k=4 =$$

$$\frac{R_4}{R_5} = 2 \rightarrow R_5 = \frac{R_4}{2} = \frac{1}{2} = 0.5$$

$$r_1 = R_1 - R_2$$

$$= 8 - 4 = 4 \Omega$$

$$r_2 = R_2 - R_3$$

$$= 4 - 2 = 2 \Omega$$


$$r_3 = R_3 - R_4$$

$$= 2 - 1 = 1 \Omega$$


$$r_4 = R_4 - R_5$$

$$= 1 - 0.5 = 0.5 \Omega$$


RELATION OF DC MOTORS

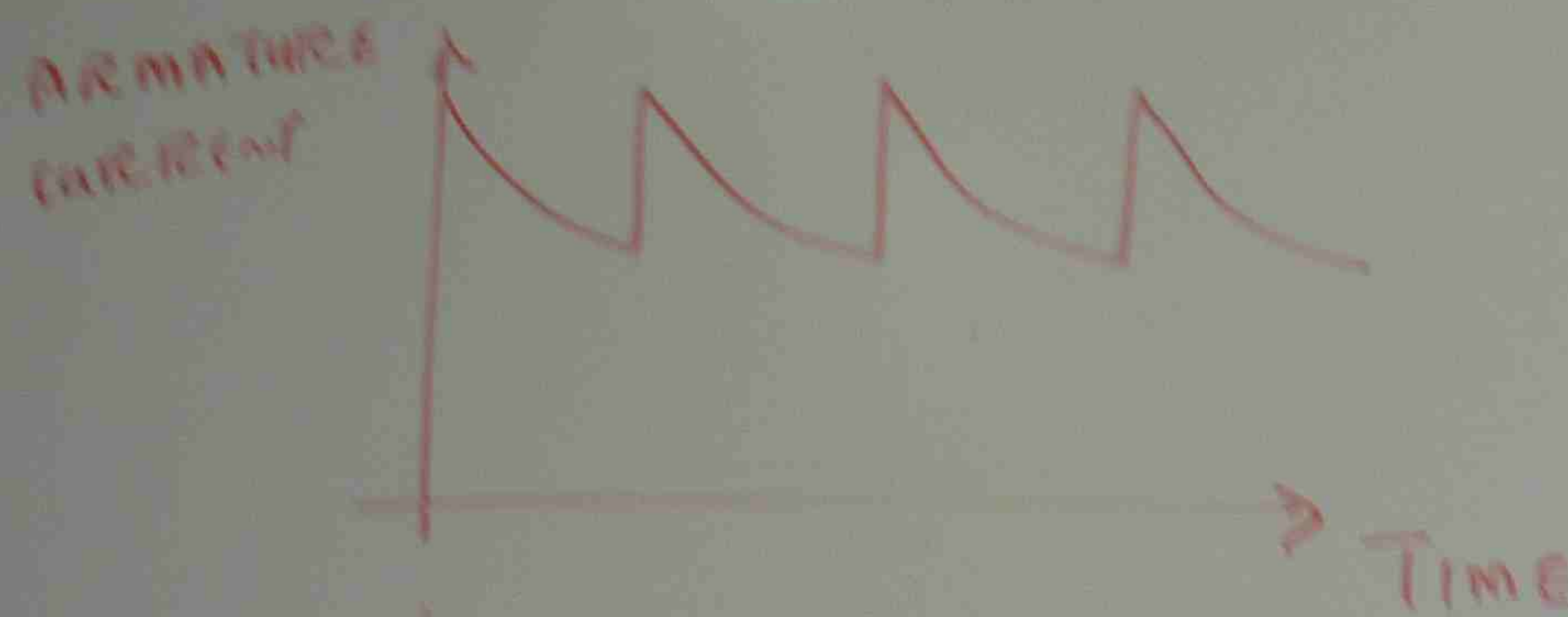

STARTERS

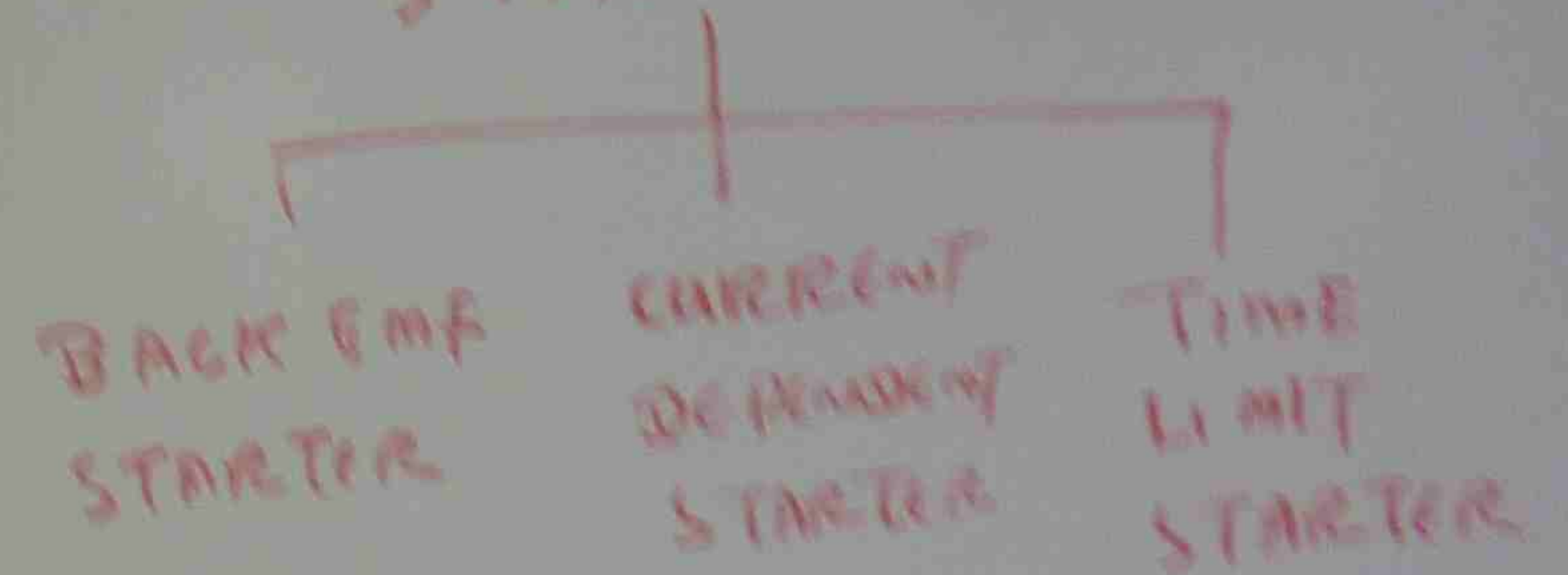

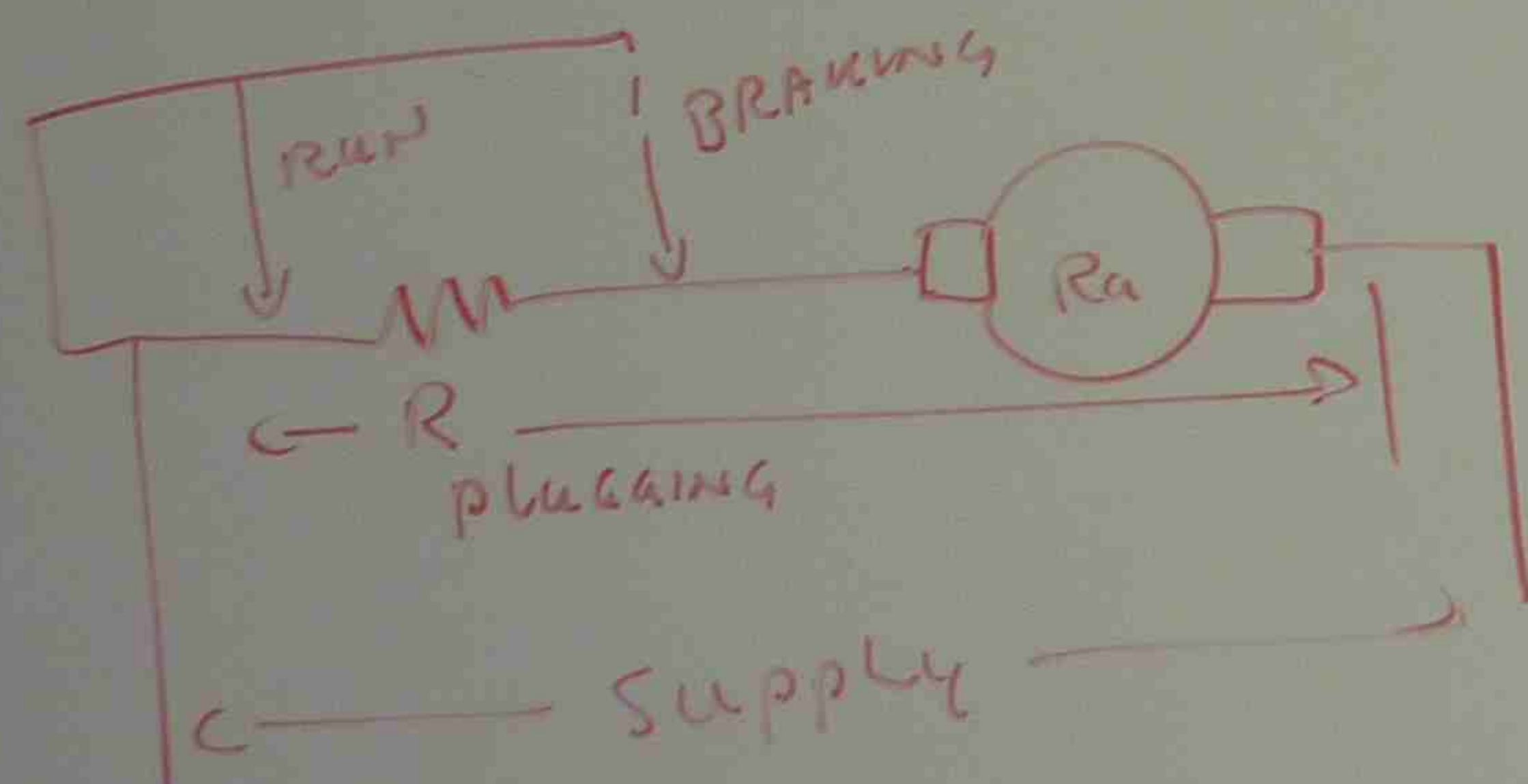Pb A 240V motor is required to be braked by plugging.
 IF THE ARMATURE CURRENT AT FULL LOAD IS 100 AMP AND
 THE ARMATURE RESISTANCE IS 0.1Ω , CALCULATE THE RESISTANCE
 OF BRAKING RESISTOR IF THE INITIAL BRAKING CURRENT
 IS LIMITED TO 150% OF FULL LOAD CURRENT AND BRUSH
 DROP IS 5 VOLT.



$$R_{\text{plugging}} = \frac{V_t - (V_b + E_b)}{I_{br}}$$

V_t = TERMINAL VOLTAGE

I_{br} = BRAKING CURRENT

V_b = BRUSH VOLTAGE DROP

E_b = BACK EMF


$$\begin{aligned} E_b &= V_t - (I_a R_a + V_b) \\ &= 240 - (100 \times 0.1 + 5) \\ &= 225 \text{ V} \end{aligned}$$

$$\begin{aligned} I_{br} &= 150\% I_a \\ &= 1.5 \times 100 = 150 \text{ AMP} \end{aligned}$$


$$\begin{aligned} R_{\text{plugging}} &= \frac{V_t - (V_b + E_b)}{I_{br}} \\ &= \frac{240 - (5 + 225)}{150} \\ &= 3.05\Omega \end{aligned}$$

$$\begin{aligned} \text{ADDITIONAL} \\ \text{RESISTANCE} &= 3.05 - 1 = 2.05\Omega \end{aligned}$$



DC MOTOR STARTERS

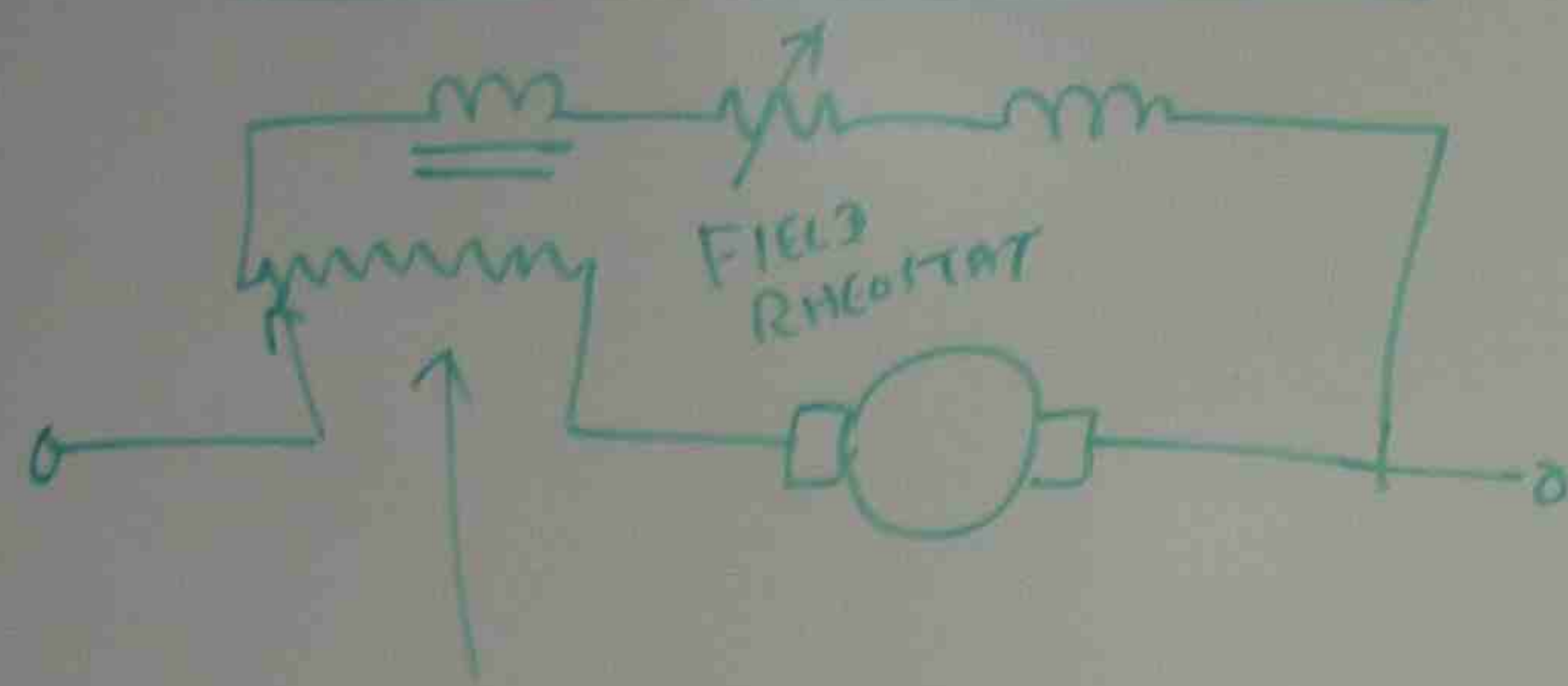

STARTING RESISTOR

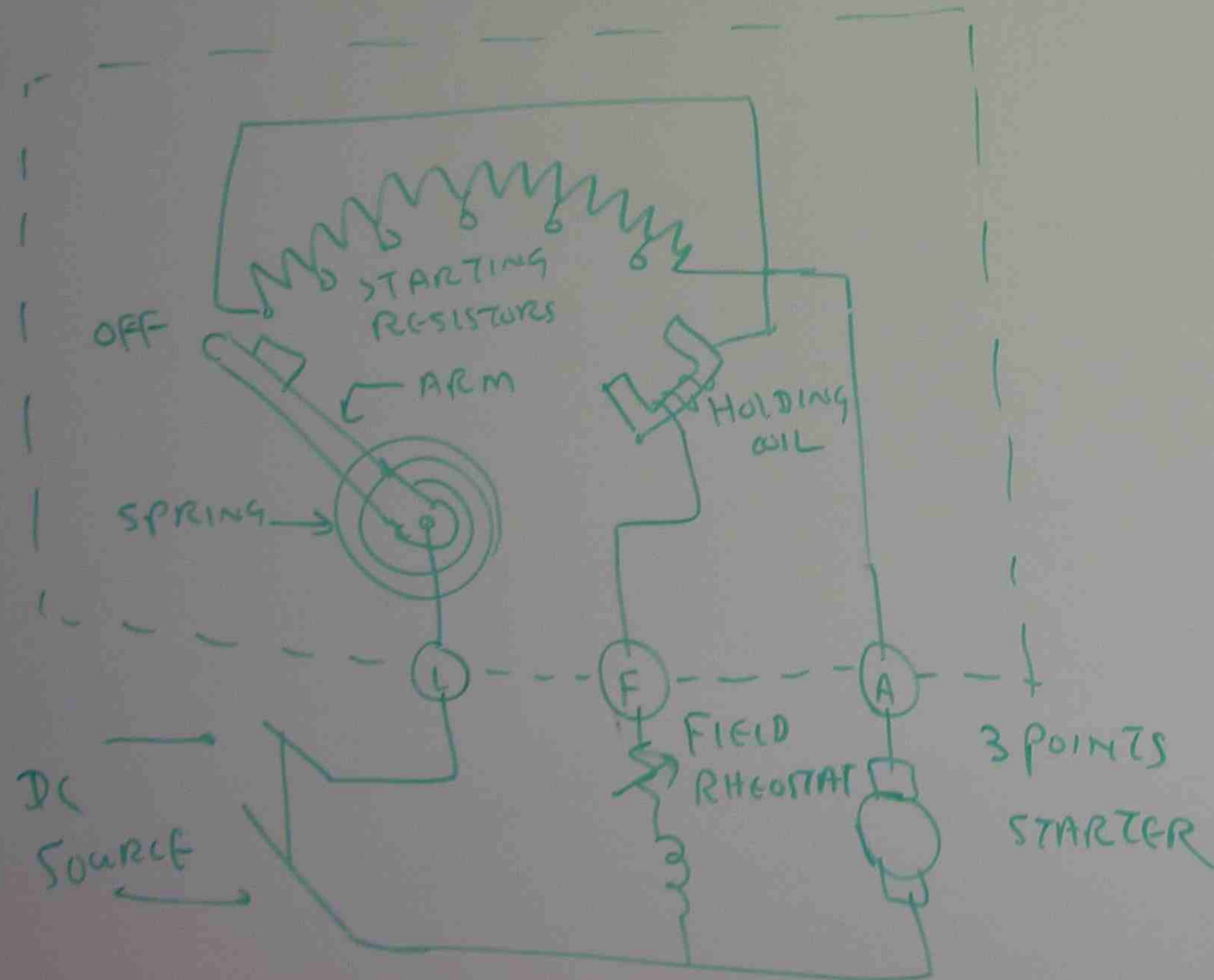

3 POINTS STARTER

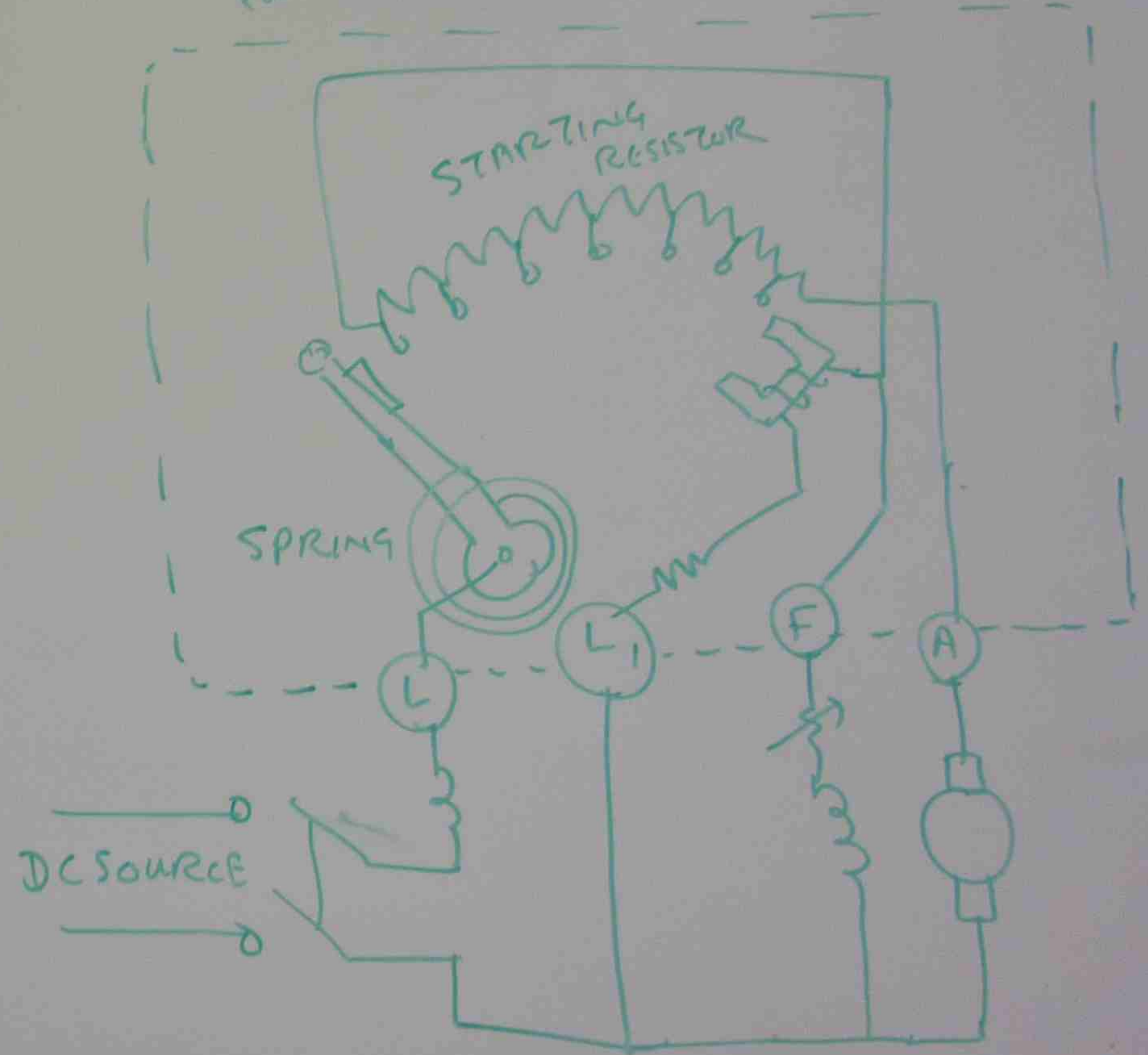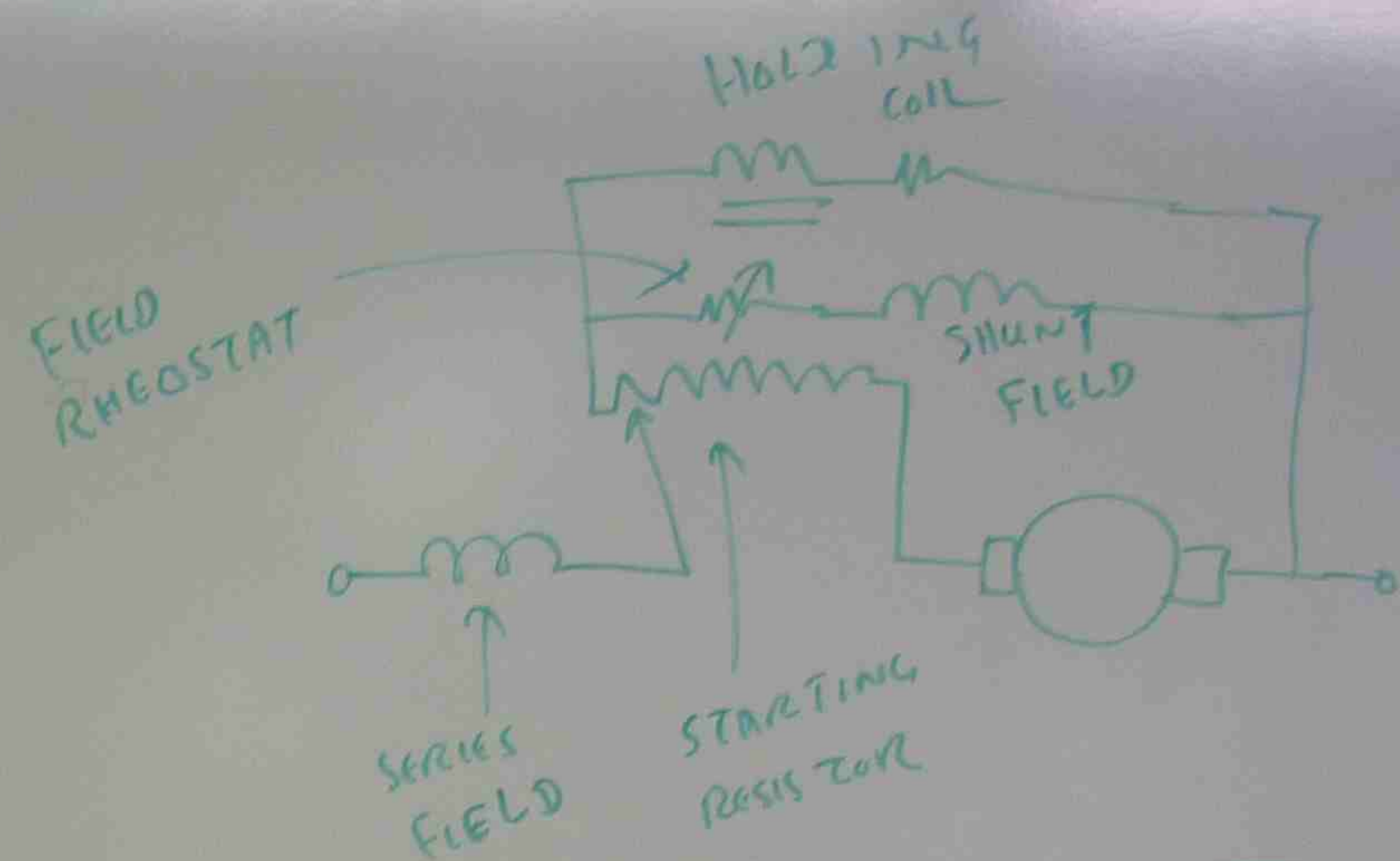

pb A 100 kW 500 V DC SHUNT MOTOR HAS AN ARMATURE RESISTANCE 0.2Ω AND FULL LOAD SPEED 920 RPM. IF THE LOAD HAS A TORQUE SPEED CURVE WHICH MAY BE DEFINED BY THE EXPRESSION.

$$T = 100 + 9.2 \times 10^{-4} N^2$$

AND THE MOTOR ARMATURE PARTICULARS ARE
 $Z = 756$ CONDUCTORS, $P = 4$ POLES PAIRS, $a = 8$ PARALLEL PATHS
 $\phi = 0.04$ WEBERS.

THE COMBINED INERTIA OF LOAD AND ARMATURE IS 100 N-m^2
 CALCULATE (a) STARTER RESISTANCES (b) SPEED AT EACH RESISTANCE STEP
 (c) TORQUE EFFICIENCY = 90% (CURRENT LIMIT 150%, 90%)

$$I_{FL} = \frac{100 \times 1000}{500 \times \frac{90}{100}} = 220 \text{ Amp}$$

$$I_{MAX} = 1.5 \times I_{FL} = 1.5 \times 220 = 330 \text{ Amp}$$

$$I_{MIN} = 0.9 \times I_{FL} = 0.9 \times 220 = 200 \text{ Amp.}$$

$$R_1 = \frac{V_t}{I_{MAX}} = \frac{500}{330} = 1.51 \Omega$$

$$\left(\frac{I_{MAX}}{I_{MIN}} \right)^m = \frac{R_1}{R_a}$$

$$\left(\frac{330}{200} \right)^m = \frac{1.51}{0.2}$$

$$1.65^m = 7.4$$

$$m \log 1.65 = \log 7.4$$

$$m = \frac{\log 7.4}{\log 1.65} = 4$$

$$R_2 = R_1 \times \left(\frac{I_{\min}}{I_{\max}} \right)$$

$$= 1.51 \times \left(\frac{200}{330} \right) = 0.92 \Omega$$

$$R_3 = R_2 \times \frac{I_{\min}}{I_{\max}}$$

$$= 0.92 \times \frac{200}{330} = 0.555 \Omega$$

$$R_4 = R_3 \times \frac{I_{\min}}{I_{\max}}$$

$$= 0.555 \times \frac{200}{330} = 0.336 \Omega$$

$$R_5 = R_4 \times \frac{I_{\min}}{I_{\max}}$$

$$= 0.336 \times \frac{200}{330} = 0.2 \Omega$$

$$\frac{E_{b1}}{E_{b2}} = \frac{\phi_1 N_1}{\phi_2 N_2}$$

Full Load

$$E_b = V_t - I_a R_a$$

$$= 500 - 220 \times 0.2$$

$$= 455.4 \text{ V}$$

REF $N = 920 \text{ RPM}$

$$R_1 = 1.51 \Omega$$

$$E_{b1} = V_t - I_1 \times R_1$$

$$= 500 - 200 \times 1.51 = 198 \text{ V}$$

$$\frac{E_b}{E_{b1}} = \frac{\phi N}{\phi N_1} \rightarrow \frac{455.4}{198} = \frac{920}{N_1}$$

$$N_1 = \frac{920 \times 198}{455.4}$$

$$= 400 \text{ RPM}$$

$$R_2 = 0.92 \Omega$$

$$E_{b2} = V_t - I$$

$$= 500 - 220$$

$$= 316$$

$$\frac{E_b}{E_{b2}} = \frac{\phi}{\phi}$$

$$\frac{455.4}{316} =$$

$$N_2 = 625$$

$$R_3 = 0.55$$

$$E_{b3} = V -$$

$$= 500$$

$$= 3$$

$$\frac{E_b}{E_{b3}} = \frac{\phi}{\phi}$$

$$R_2 = 0.92 \Omega$$

$$\begin{aligned} E_{b2} &= V_t - I_1 \times R_2 \\ &= 500 - 200 \times 0.92 \\ &= 316 \text{ V} \end{aligned}$$

$$\frac{E_b}{E_{b2}} = \frac{\phi N}{\phi N_2}$$

$$\frac{455.4}{316} = \frac{920}{N_2}$$

$$N_2 = 625 \text{ RPM}$$

$$R_3 = 0.555 \Omega$$

$$\begin{aligned} E_{b3} &= V - I_1 R_3 \\ &= 500 - 200 \times 0.555 \\ &= 389 \text{ V} \end{aligned}$$

$$\frac{E_b}{E_{b3}} = \frac{\phi N}{\phi N_3} \rightarrow \frac{455.4}{389} = \frac{920}{N_3}$$

$$N_3 = 780 \text{ RPM}$$

$$R_4 = 0.336 \Omega$$

$$\begin{aligned} E_{b4} &= V_t - I_1 R_4 \\ &= 500 - 200 \times 0.336 \\ &= 455 \text{ V} \end{aligned}$$

$$\frac{E_b}{E_{b4}} = \frac{\phi N}{\phi N_4}$$

$$\frac{455.4}{455} = \frac{920}{N_4}$$

$$N_4 = 860 \text{ RPM}$$


$$R_5 = 0.2 \Omega$$

$$\begin{aligned} E_{b5} &= V_t - I_1 R_5 \\ &= 500 - 200 \times 0.2 \\ &= 460 \text{ V} \end{aligned}$$

$$\frac{E_b}{E_{b5}} = \frac{\phi N}{\phi N_5}$$

$$\frac{455.4}{460} = \frac{920}{N_5}$$

$$N_5 \approx 920 \text{ RPM}$$

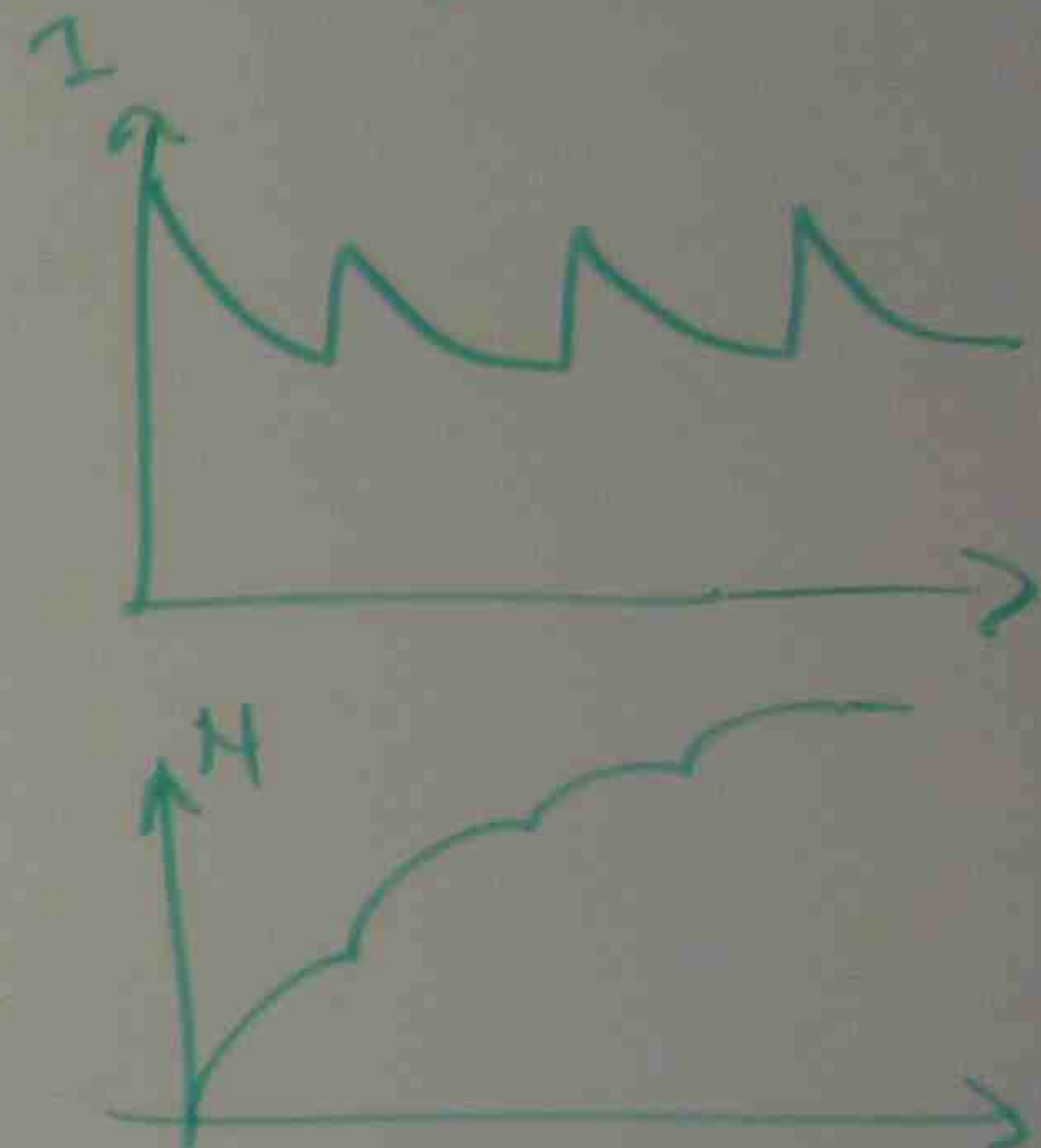

$$T = \frac{N_t \phi V_t}{R_a}$$

$$k_e = \frac{P Z}{60 a}$$

$$k_e = \frac{8 \times 756}{60 \times 8}$$

$$k_t = \frac{8 \times 756}{2 \times 3.1416 \times}$$

$$R_4 = 0.336 \Omega$$

$$E_{b4} = V_t - I_1 R_4$$

$$= 500 - 200 \times 0.336$$

$$= 455 \text{ V}$$

$$\frac{E_b}{E_{b4}} = \frac{\phi N}{\phi N_4}$$

$$\frac{455.4}{455} = \frac{920}{N_4}$$

$$N_4 = 860 \text{ RPM}$$

$$R_5 = 0.2 \Omega$$

$$E_{b5} = V_t - I_1 R_5$$

$$= 500 - 200 \times 0.2$$

$$= 460 \text{ V}$$

$$\frac{E_b}{E_{b5}} = \frac{\phi N}{\phi N_5}$$

$$\frac{455.4}{460} = \frac{920}{N_5}$$

$$N_5 \approx 920 \text{ RPM}$$



$$T = \frac{12 \times 0.1 \times 500}{0.2} - \frac{12.6 \times 12 \times 0.1^2 \times N}{0.2}$$

$$T = 1600 - 1.62 \text{ N}$$

$$T = \frac{k_t \phi V_t}{R_a} - \frac{k_e k_t \phi^2 N^2}{R_a}$$

$$k_e = \frac{p \tau}{60 a} \quad , \quad k_t = \frac{p \tau}{2 \pi a}$$

$$k_e = \frac{8 \times 756}{60 \times 8} = 12.6$$

$$k_t = \frac{8 \times 756}{2 \times 3.14 \times 8} = 121$$

$$R_4 = 0.336 \Omega$$

$$E_{b4} = V_t - I_1 R_4$$

$$= 500 - 200 \times 0.336$$

$$= 455 \text{ V}$$

$$\frac{E_b}{E_{b4}} = \frac{\phi N}{\phi N_4}$$

$$\frac{455.4}{455} = \frac{920}{N_4}$$

$$N_4 = 860 \text{ RPM}$$

$$R_5 = 0.2 \Omega$$

$$E_{b5} = V_t - I_1 R_5$$


$$= 500 - 200 \times 0.2$$

$$= 460 \text{ V}$$

$$\frac{E_b}{E_{b5}} = \frac{\phi N}{\phi N_5}$$

$$\frac{455.4}{460} = \frac{920}{N_5}$$

$$N_5 \approx 920 \text{ RPM}$$

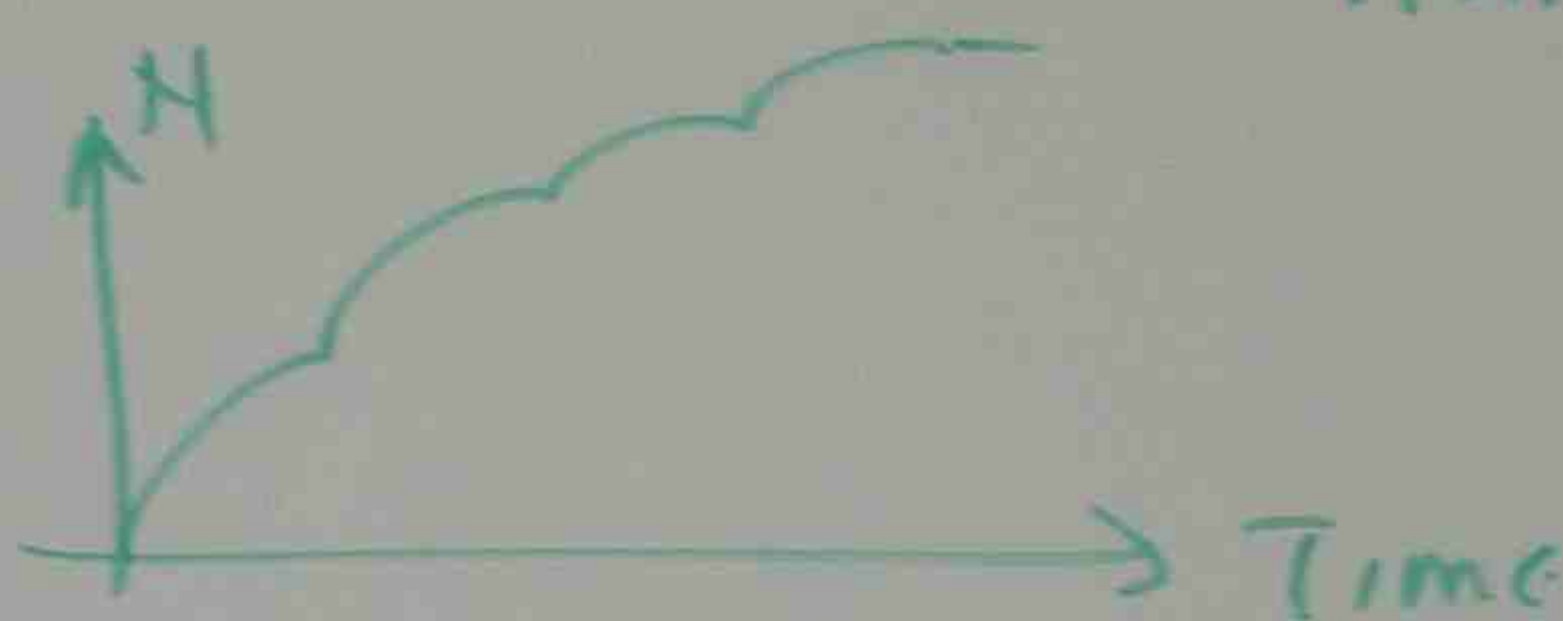

$$T = \frac{121 \times 0.1 \times 500}{0.2} - \frac{12.6 \times 121 \times 0.1^2 \times N}{0.2}$$

$$T = 30250 - 76023 \text{ N}$$


$$T = \frac{\pi t \phi V_t}{R_a} - \frac{k_e k_t \phi^2 N^2}{R_a}$$

$$k_e = \frac{p z}{60 a}, \quad k_t = \frac{p z}{2 \pi a}$$


$$k_e = \frac{8 \times 756}{60 \times 8} = 12.6$$

$$k_t = \frac{8 \times 756}{2 \times 3.1416 \times 8} \approx 121$$

POWER FLOW DIAGRAM OF DC GENERATOR

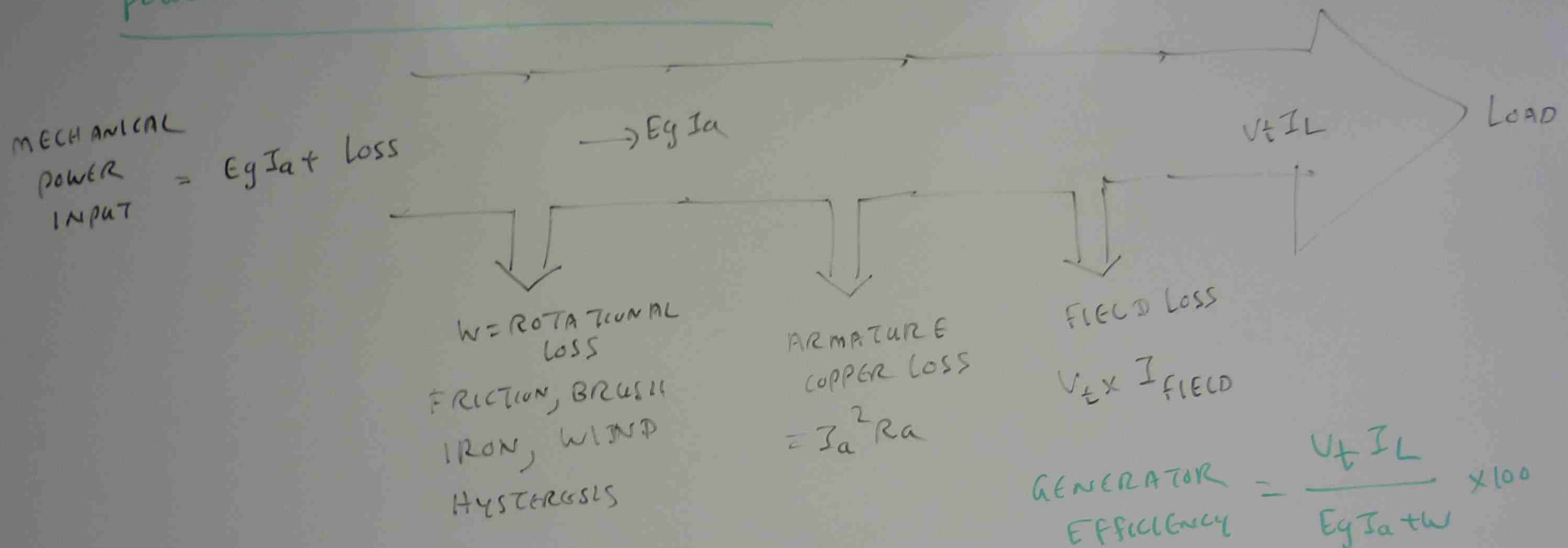


DC MOTOR

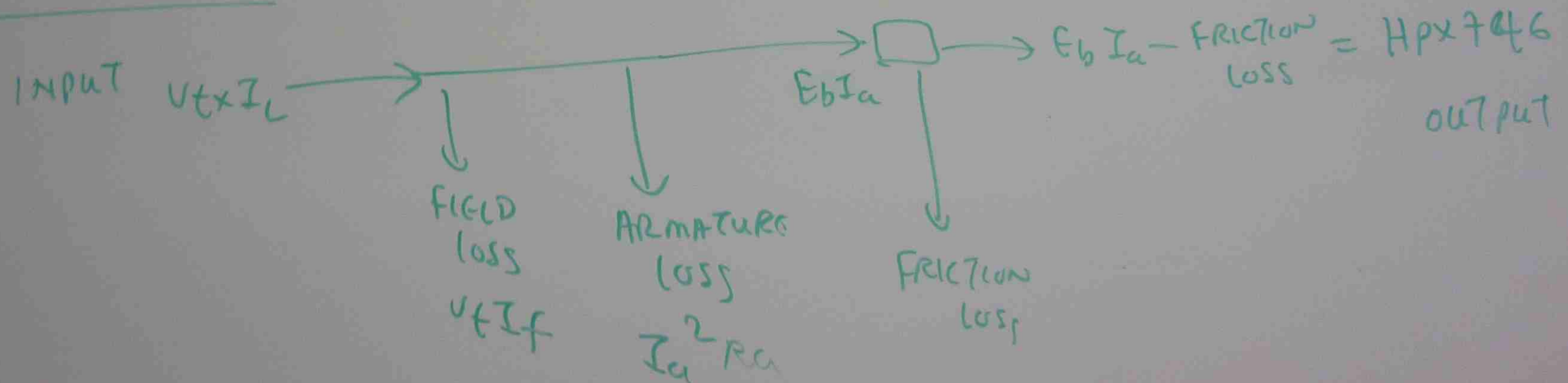

pb THE WINDING RESISTANCE OF A 500V, 60KW DC SHUNT MOTOR ARE $R_a = 0.2\Omega$ $R_f = 200\Omega$
 IF MECHANICAL LOSSES ARE 1.4KW, DETERMINE THE EFFICIENCY OF THE MACHINE

(a) WHEN THE LINE CURRENT IS 102.5 AMP

(b) AT FULL LOAD.

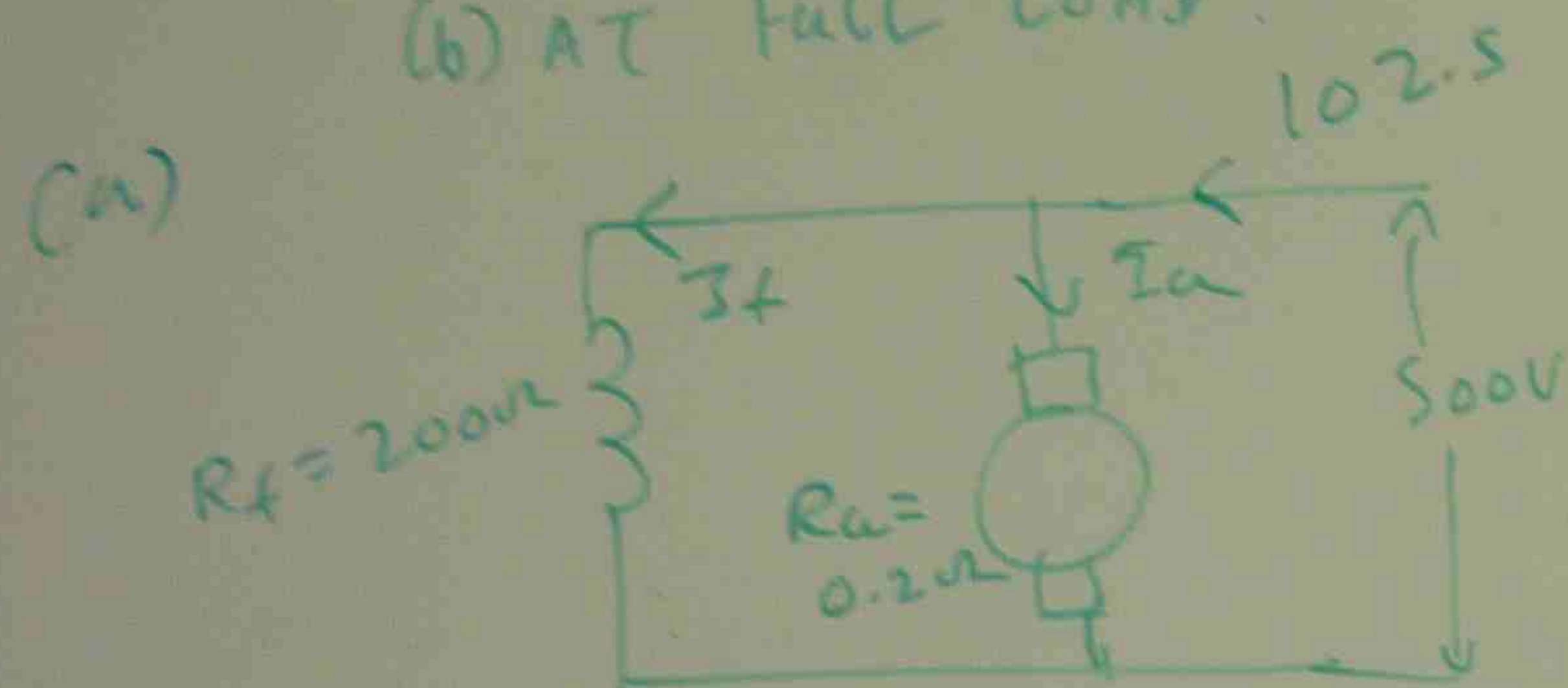

$$I_f = \frac{500}{200} = 2.5 \text{ A}$$

$$I_a = I_L - I_f = 102.5 - 2.5 = 100 \text{ Amp.}$$

$$P_{in} = V_t \times I_L = 500 \times 102.5 = 51250 \text{ WATT}$$

$$P_{losses} = I_a^2 R_a + I_f^2 R_f + 1400 = 100^2 \times 0.2 + 2.5^2 \times 200 + 1400 = 4650 \text{ W}$$

$$\% \eta = \frac{P_{in} - P_{loss}}{P_{in}} \times 100$$

$$= \frac{51250 - 4650}{51250} \times 100$$

$$= 90.93\%$$

0.2 Ω $R_f = 200 \Omega$
MACHINE

(b) AT FULL LOAD

$$P_{out} = 60 \text{ kW} = 60,000 \text{ W}$$

$$P_{out} = E_g I_a - W \Rightarrow E_g I_a = P_{out} + W$$

$$E_g I_a = 60,000 + 1400 = 61400$$

$$E_g = V_t - I_a R_a$$

$$(V_t - I_a R_a) I_a = 61400$$

$$(500 - I_a \times 0.2) I_a = 61400$$

$$500 I_a - 0.2 I_a^2 = 61400$$

$$0.2 I_a^2 - 500 I_a + 61400 = 0$$

$$A x^2 + B x + C = 0$$

$$x = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$

$$I_a = \frac{-(-500) \pm \sqrt{(-500)^2 - 4 \times 0.2 \times 61400}}{2 \times 0.2}$$

$$= 129.5 \text{ (or) } 2315$$

$$P_{in} = P_{out} + \text{ROTATIONAL LOSS} + I_a^2 R_a + I_f^2 R_f$$

$$= 60000 + 1400 + (129.5)^2 \times 0.2 + 2.5^2 \times 200$$


$$= 66000 \text{ WATT}$$

$$\% \eta = \frac{P_{out}}{P_{in}} \times 100$$

$$= \frac{60000}{66000} \times 100 = 90.9\%$$


DC MOTOR STARTERS

CIRCUIT ANALYSIS

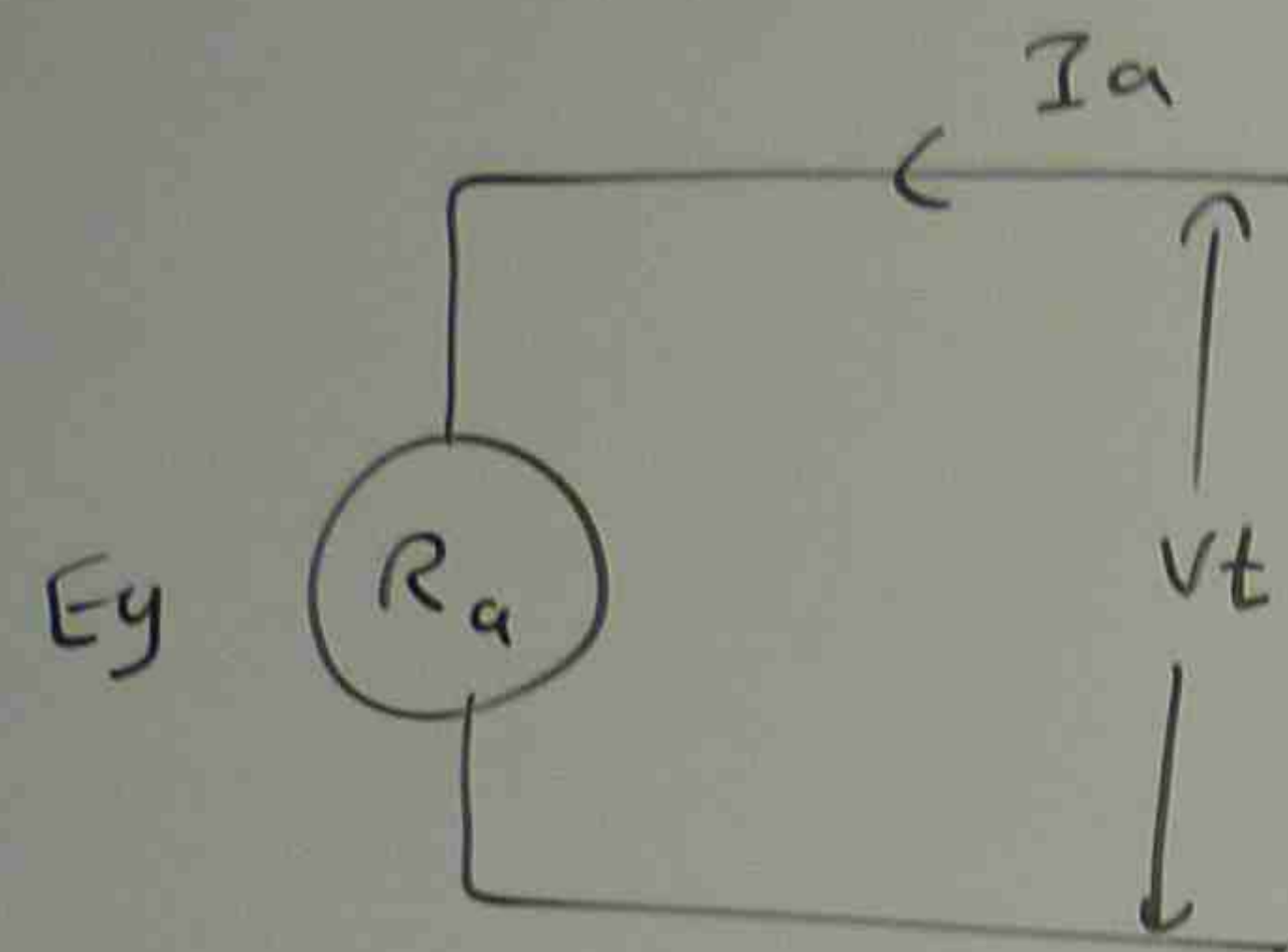

$$E_g = V_t - I_a R_a$$

$$I_a = \frac{V_t - E_g}{R_a}$$

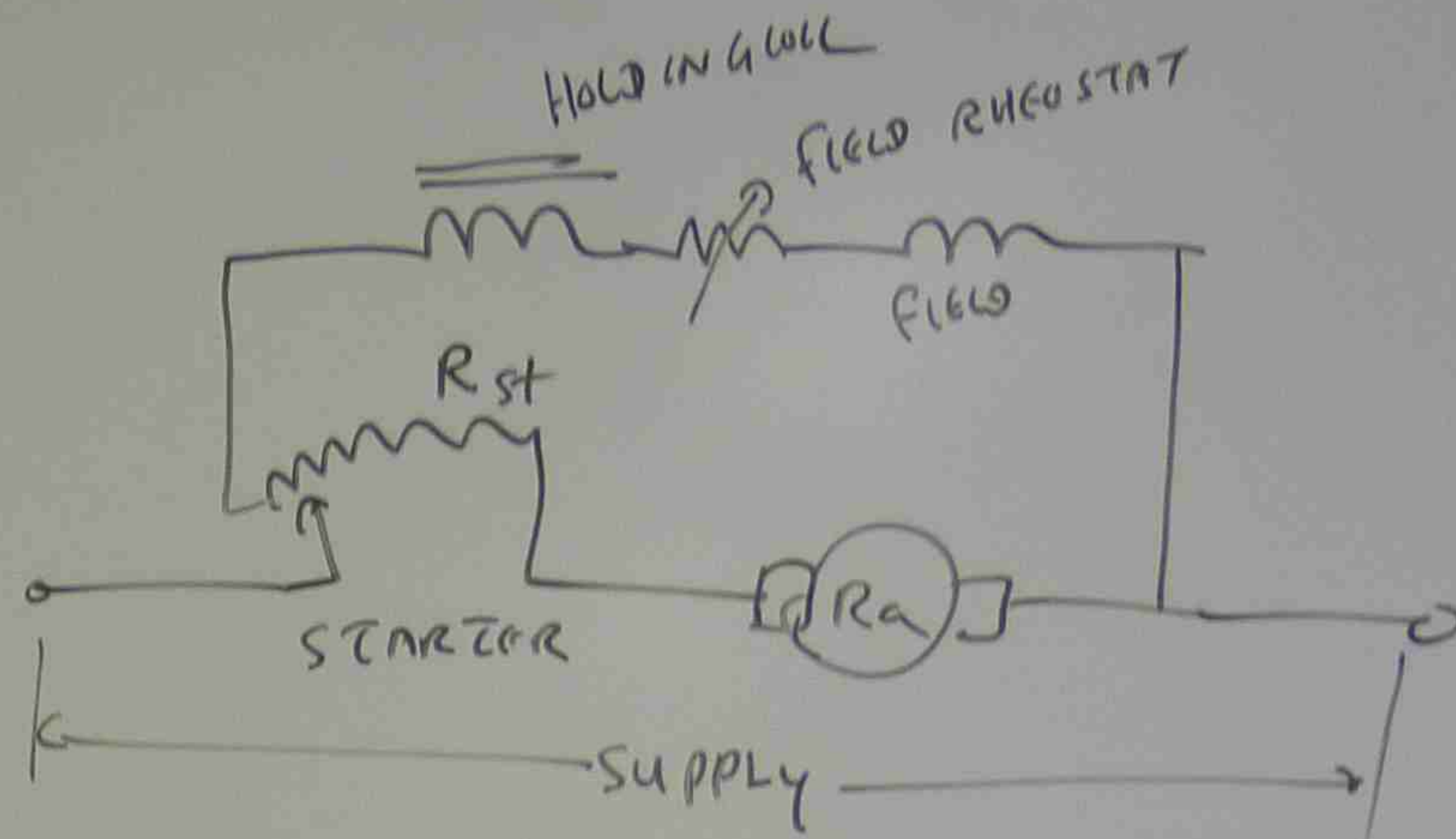

$$I_a = \frac{V_t - E_g}{R_a + R_{st}}$$

$$E_g = \frac{\phi Z N}{60} \times \frac{P}{a}$$

E_g = BACK EMF

ϕ = Flux

Z = ARMATURE CONDUCTORS

N = SPEED

P = NO. OF POLES

a = NO. OF ARMATURE PARALLEL PATHS.

AT START

ACCORDING TO

STARTING

LARGE

RESISTOR

(pb) THE RESISTOR

FULL


(a) IF

LOAD

RE

(b) D

1

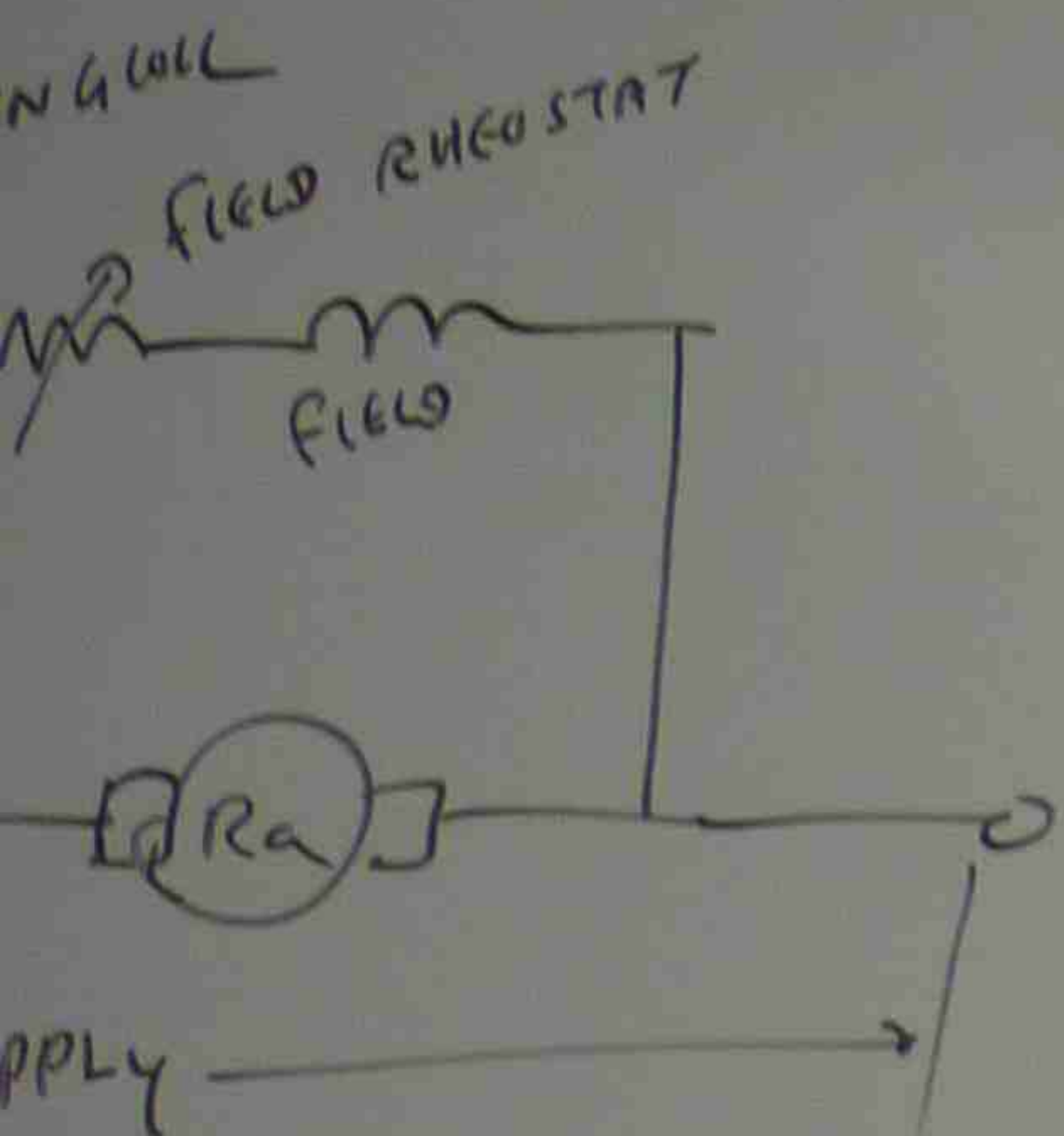

AT STARTING TIME, N IS SMALL AS IT STARTS FROM ZERO SPEED.

ACCORDING TO $E_g = \frac{\phi Z N}{60} \times \frac{P}{a}$, E_g IS SMALL.


STARTING CURRENT $I_a = \frac{V_t - E_g}{R_a}$ IS LARGE.

LARGE STARTING CURRENT NEEDS TO BE LIMITED BY STARTING RESISTOR.

(pb) THE ARMATURE OF A 230V SHUNT MOTOR HAS A RESISTANCE OF 0.88Ω AND TAKES 28.2 AMP AT FULL LOAD.

(a) IF I_a IS NOT TO EXCEED 150% OF NORMAL FULL LOAD CURRENT AT STARTING, CALCULATE STARTING RESISTANCE

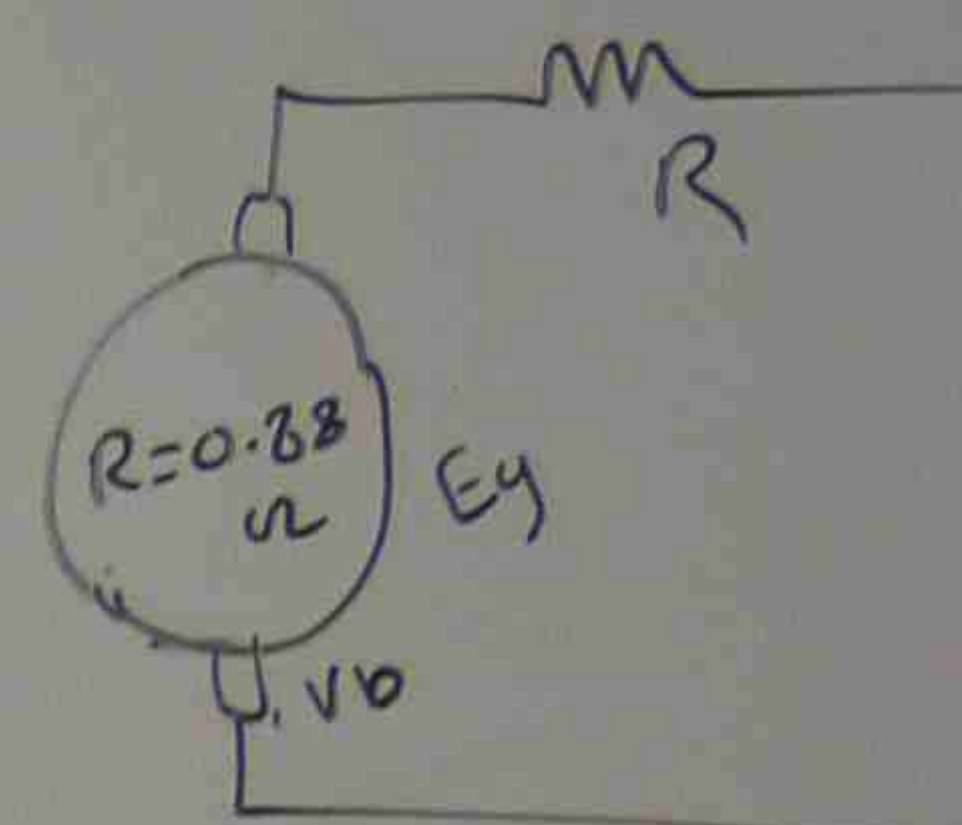(b) DETERMINE I_a IF NO STARTING RESISTANCE IS INSERTED. ASSUME BRUSH DROP 3V.



(a)

$$I_{st} = \frac{V_t}{R_a}$$

$$\frac{150}{100} \times 28.2 = \frac{230 - 3}{0.88 + R}$$

$$0.88 + R = \frac{227}{150 \times 28.2}$$

$$R = \frac{227 \times 100}{150 \times 28.2} - 0.88$$

(b) $I_{st} = \frac{V_t - 3}{R_a}$

ARMATURE PARALLEL PATHS.

AS IT STARTS FROM ZERO SPEED.

E_g IS SMALL.

$\frac{-E_g}{R_a}$ IS LARGE.


IS TO BE LIMITED BY STARTING

230V SHUNT MOTOR HAS A
AND TAKES 28.2 AMP AT

150% OF NORMAL FULL
LOAD, CALCULATE STARTING

STARTING RESISTANCE IS

2V DROP 3V.

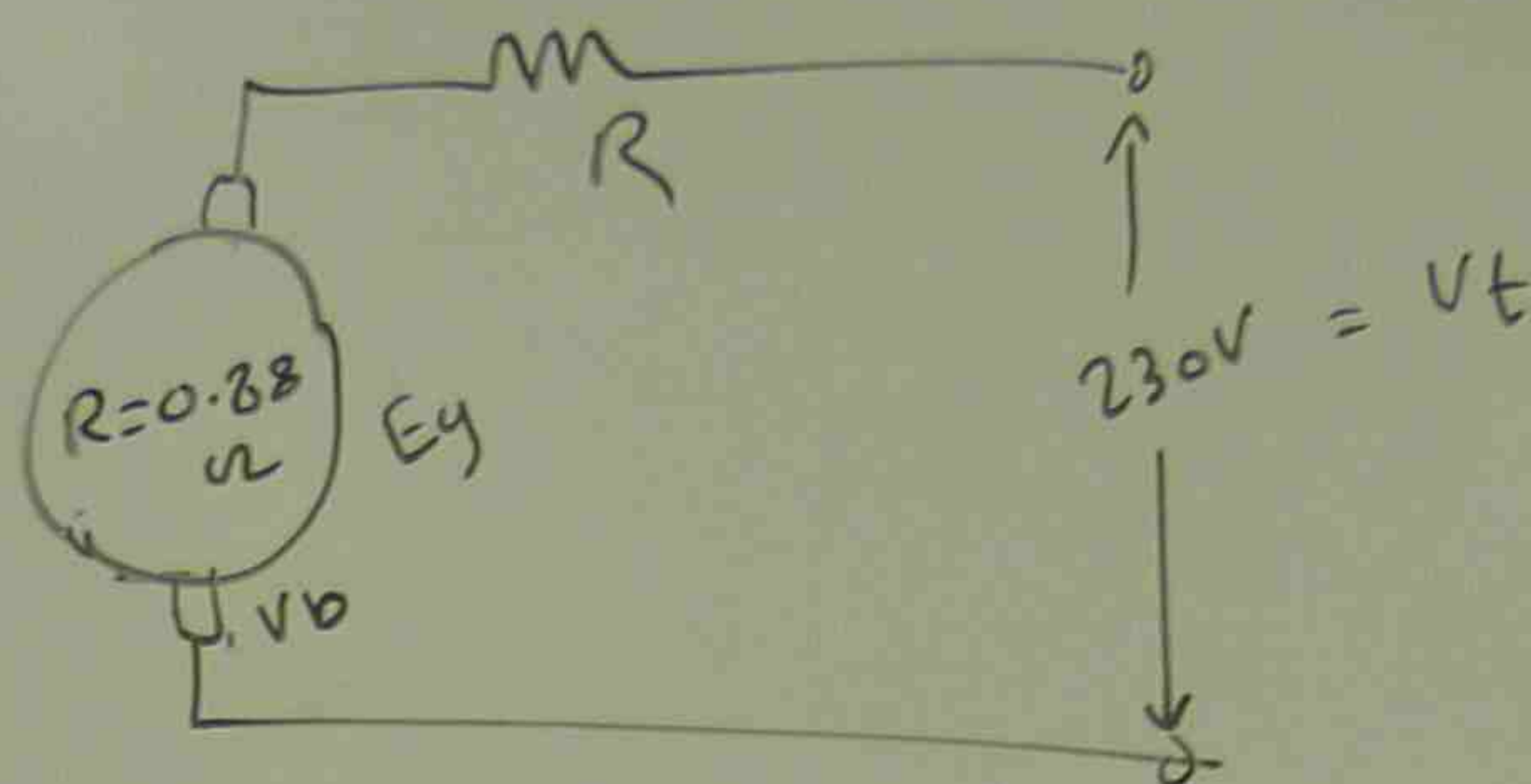

(a)

$$I_{st} = \frac{V_t - (E_g + V_b)}{R_a + R}$$

$$\frac{150}{100} \times 28.2 = \frac{230 - (0 + 3)}{0.88 + R}$$

$$0.88 + R = \frac{227 \times 100}{150 \times 28.2}$$


$$R = \frac{227 \times 100}{150 \times 28.2} - 0.88 = 4.55 \Omega$$

(b)

$$I_{st} = \frac{V_t - (E_g + V_b)}{R_a} = \frac{230 - (0 + 3)}{0.88} = \frac{227}{0.88} = 257 \text{ Amp.}$$


DC MOTOR STARTERS

CIRCUIT ANALYSIS

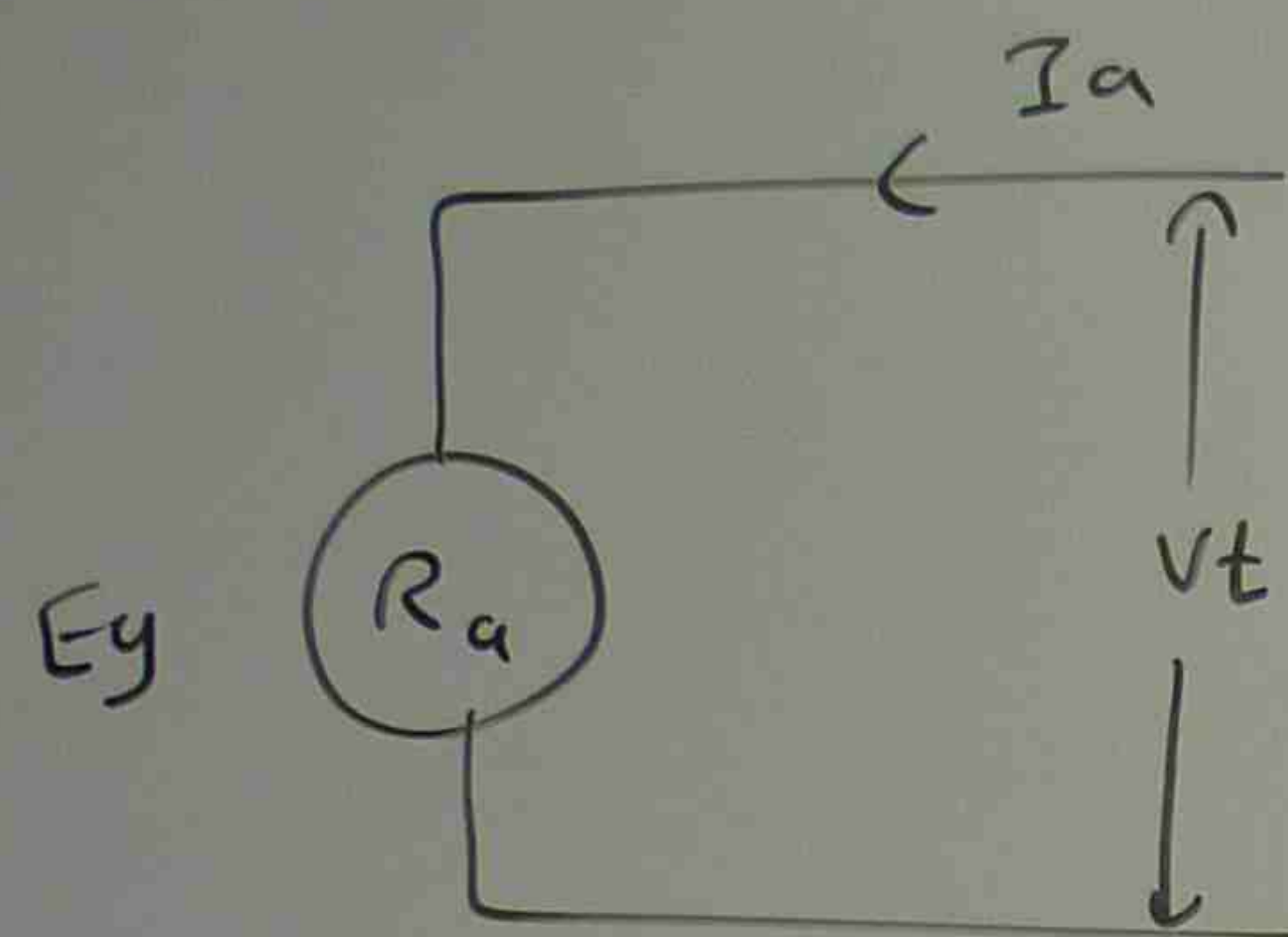

$$E_g = V_t - I_a R_a$$

$$I_a = \frac{V_t - E_g}{R_a}$$

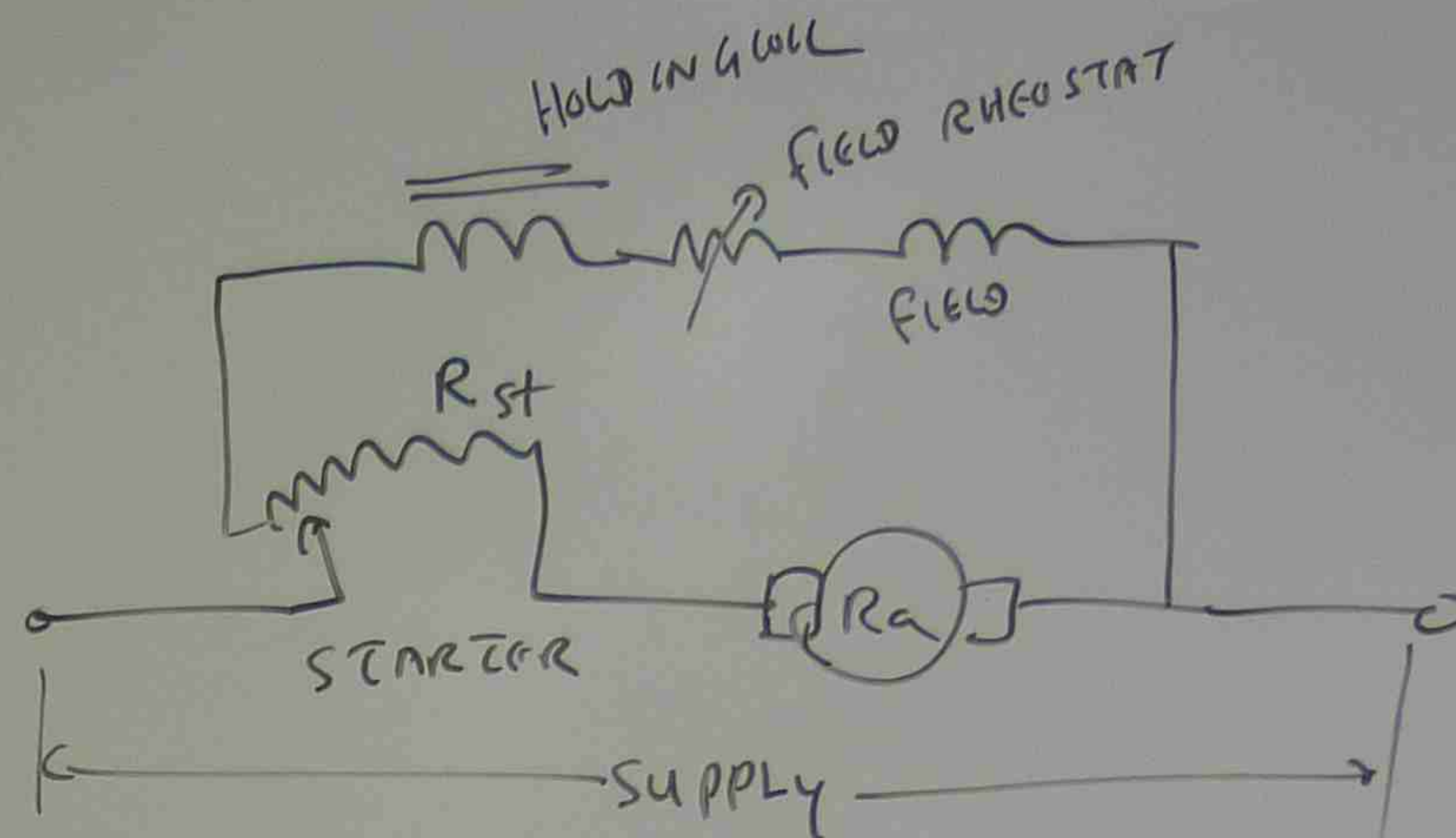

$$I_a = \frac{V_t - E_g}{R_a + R_{st}}$$

$$E_g = \frac{\phi Z N}{60} \times \frac{P}{a}$$

E_g = BACK EMF

ϕ = FLUX

Z = ARMATURE CONDUCTORS

N = SPEED

P = NO. OF POLES

a = NO. OF ARMATURE PARALLEL PATHS.

AT START

ACCORDING

STARTING

LARGE S

RESISTOR

(pb) THE
RESIS


FULL

(a) IF

LOAD

R

(b) D

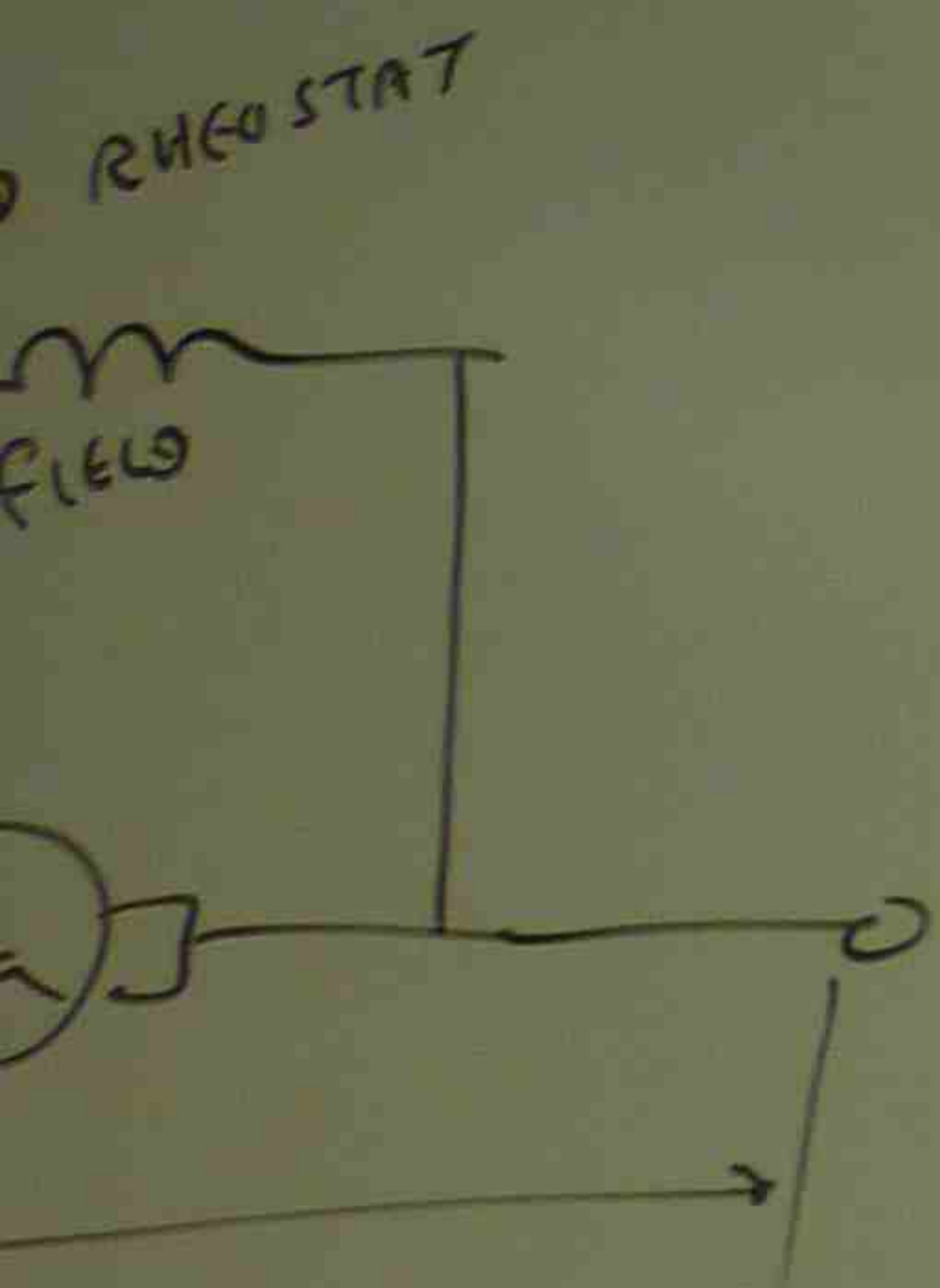

AT STARTING TIME, N IS SMALL AS IT STARTS FROM ZERO SPEED.

ACCORDING TO $E_g = \frac{\phi Z N}{60} \times \frac{P}{a}$, E_g IS SMALL.


STARTING CURRENT $I_a = \frac{V_t - E_g}{R_a}$ IS LARGE.

LARGE STARTING CURRENT NEEDS TO BE LIMITED BY STARTING RESISTOR.

(pb) THE ARMATURE OF A 230V SHUNT MOTOR HAS A RESISTANCE OF 0.88Ω AND TAKES 28.2 AMP AT FULL LOAD.

(a) IF I_a IS NOT TO EXCEED 150% OF NORMAL FULL LOAD CURRENT AT STARTING, CALCULATE STARTING RESISTANCE

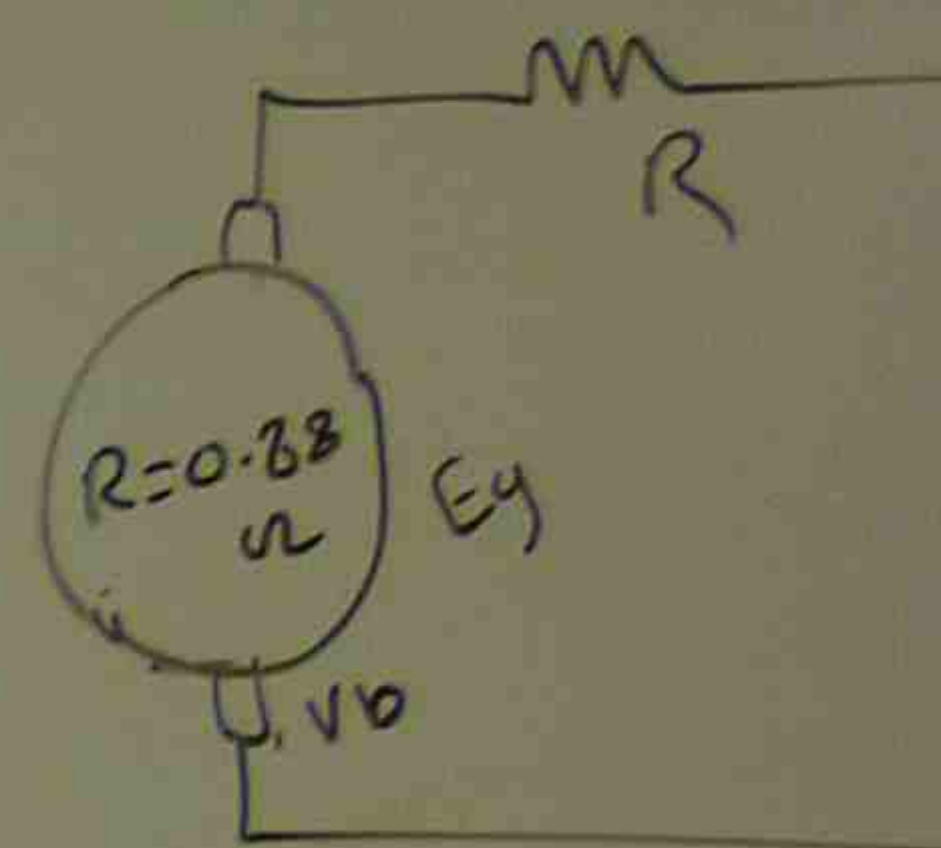(b) DETERMINE I_a IF NO STARTING RESISTANCE IS INSERTED. ASSUME BRUSH DROP 3V.



(a)

$$I_{st} = \frac{V_t}{R_a}$$

$$\frac{150}{100} \times 28.2 = \frac{230 - 3}{0.88 + R}$$

$$0.88 + R = \frac{227}{150 \times 28.2}$$

$$R = \frac{227}{150 \times 28.2} - 0.88$$

(b) $I_{st} = \frac{V_t - 3}{R_a}$

DUCTORS

USE PARALLEL PATHS.

IT STARTS FROM ZERO SPEED.

E_g IS SMALL.

IS LARGE.

BE LIMITED BY STARTING


SHUNT MOTOR HAS A
TAKES 28.2 AMP AT

150% OF NORMAL FULL

CALCULATE STARTING

STARTING RESISTANCE IS

DROP 3V.

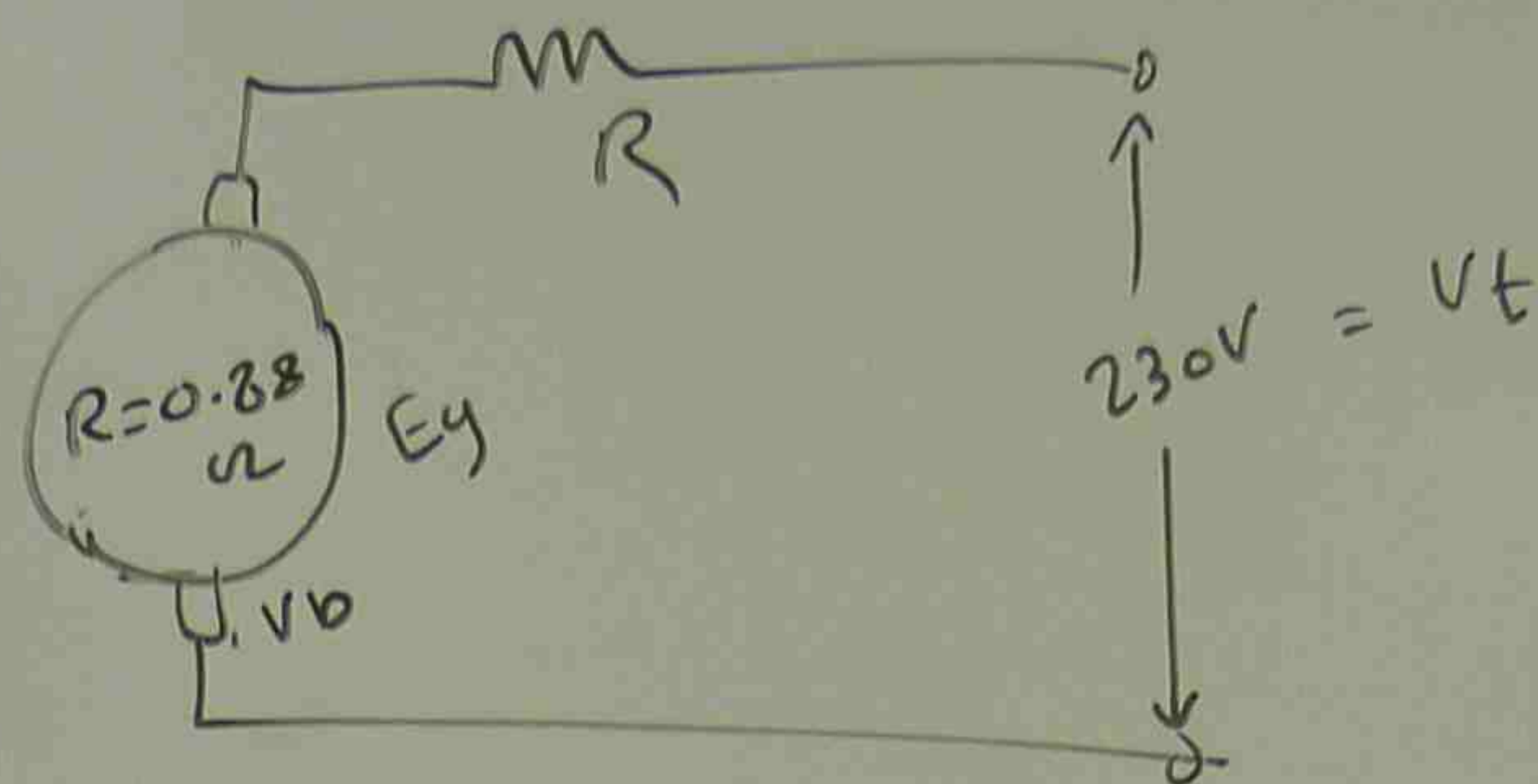

$$(a) \quad I_{st} = \frac{V_t - (E_g + V_b)}{R_a + R}$$

$$\frac{150}{100} \times 28.2 = \frac{230 - (0 + 3)}{0.88 + R}$$


$$0.88 + R = \frac{227 \times 100}{150 \times 28.2}$$

$$R = \frac{227 \times 100}{150 \times 28.2} - 0.88 = 4.55 \Omega$$

$$(b) \quad I_{st} = \frac{V_t - (E_g + V_b)}{R_a} = \frac{230 - (0 + 3)}{0.88} = \frac{227}{0.88} = 257 \text{ Amp.}$$

DYNAMIC BRAKING

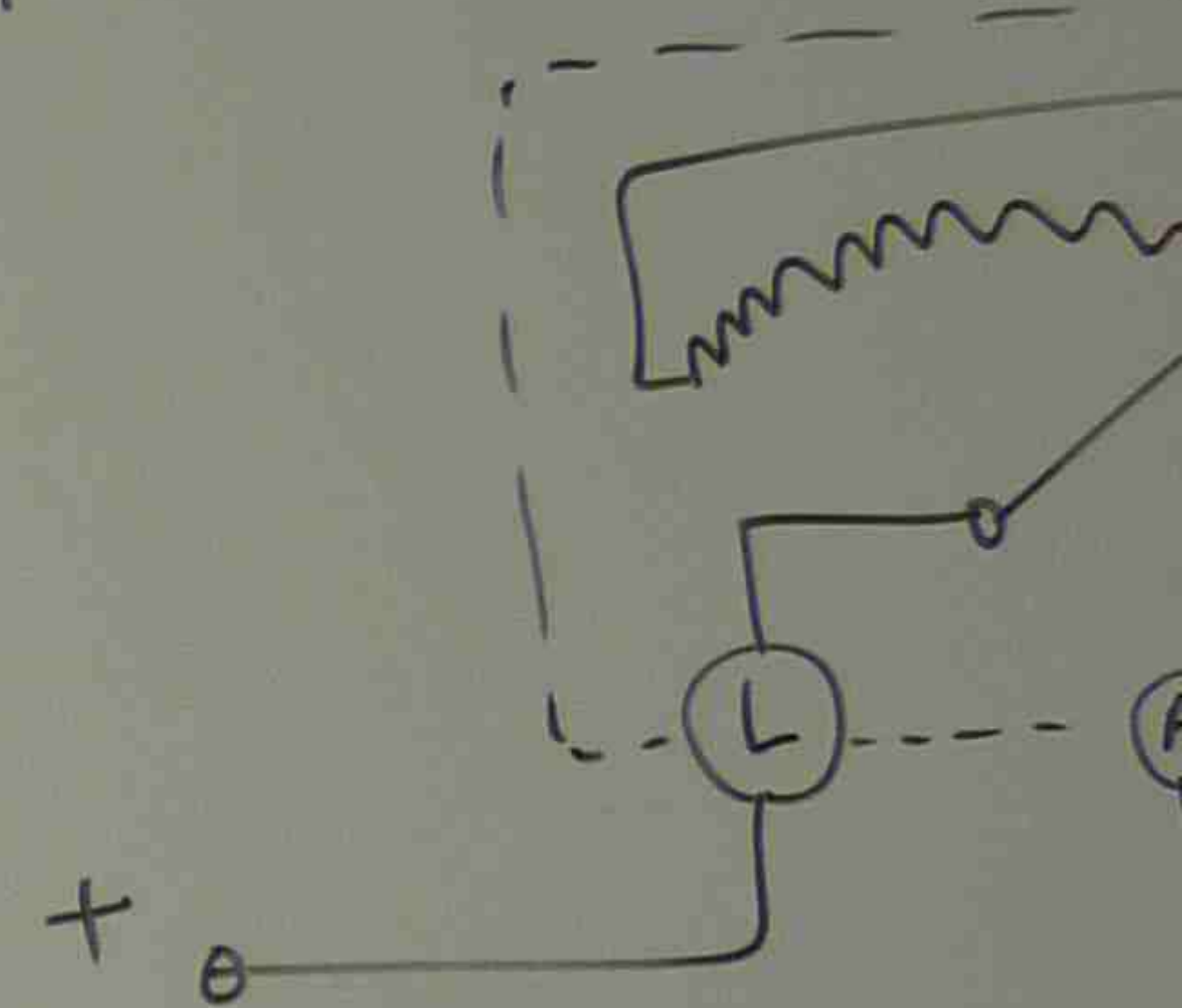
WHEN THE STOP SWITCH IS
IS DISSIPATED IN DYNAMIC
STOPPED IMMEDIATELY.



$$I_{br} = \frac{E_g - V}{R_{brt}}$$

DYNAMIC BRAKING

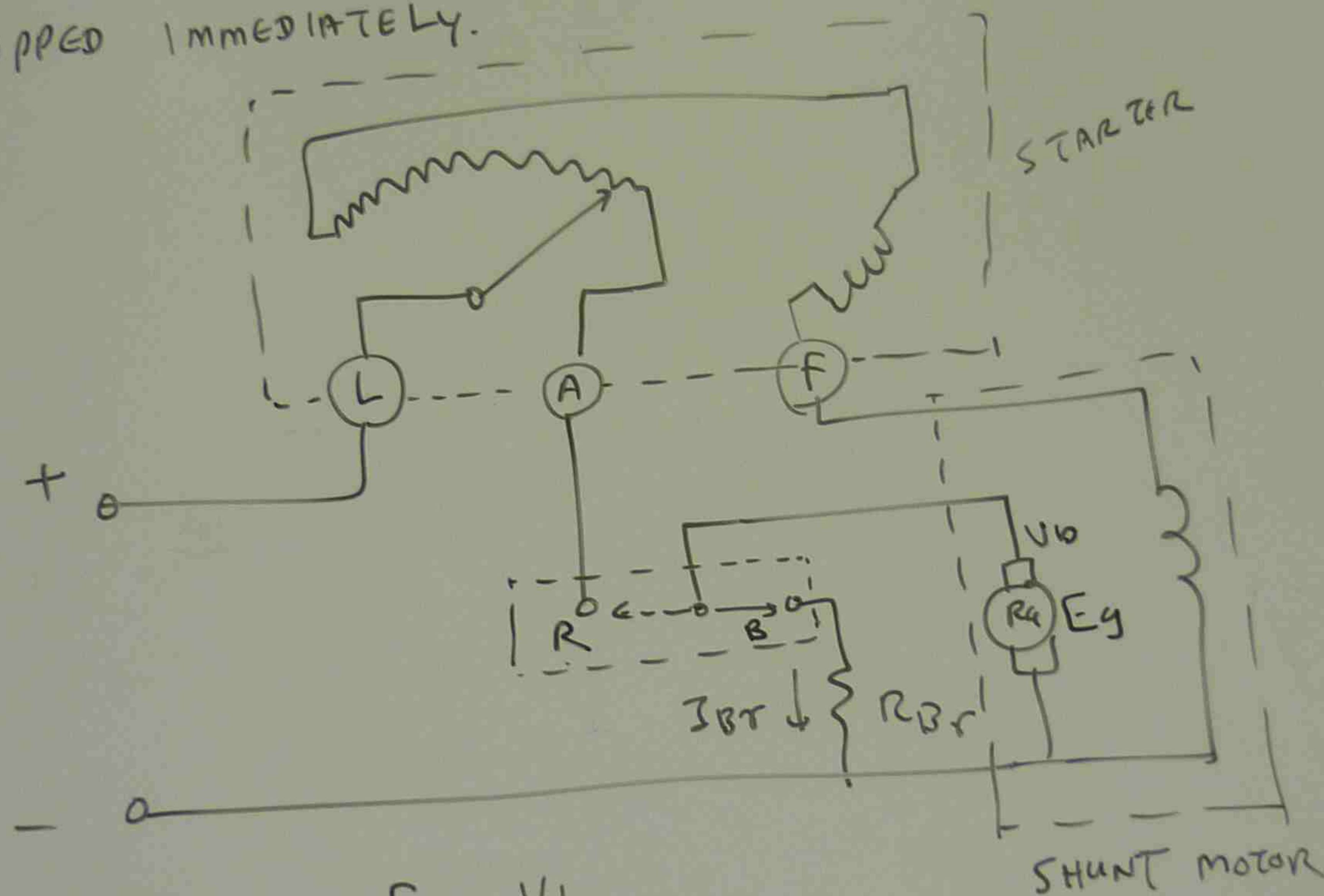WHEN THE STOP SWITCH IS PRESSED, THE ENERGY STORED IN MOTOR ARMATURE IS DISSIPATED IN DYNAMIC BRAKING RESISTOR. THEREFORE, THE MOTOR IS STOPPED IMMEDIATELY.



$$I_{br} = \frac{E_g - V_b}{R_{br} + R_a}$$

$$= 4.55 \Omega$$

$$\frac{0 - (0 + 3)}{0.88} = \frac{22}{0.88}$$

$$= 25 \text{ Amp.}$$

Pb THE BRAKE
SERIES WOUND
TO BE LIMITED
CALCULATE THE

ASSUME E_g

$$I_{br} =$$

$$E_g =$$

$$R_a =$$

$$R_b$$

$$I_{br}$$

$$R_{br}$$

TORED IN MOTOR ARMATURE
FORCE, THE MOTOR IS

pb THE BRAKING CURRENT OF A 12.5 KW 230V 58 AMP MOTOR
SERIES WOUND, TOTAL ARMATURE AND FIELD RESISTANCE 0.28Ω IS
TO BE LIMITED TO 1.75 TIMES MOTOR FULL LOAD RATING.
CALCULATE THE VALUE OF THE DYNAMIC BRAKING RESISTOR.

ASSUME E_g IS 94% OF RATED VOLTAGE AND BRUSH DROP IS 3V.

$$I_{br} = 1.75 I_{FL} = 1.75 \times 58$$

$$E_g = 0.94 \times 230 \quad \checkmark$$

$$R_a = 0.28 \Omega$$

$$V_b = 3V$$

$$R_{br} = ?$$

$$I_{br} = \frac{E_g - V_b}{R_{br} + R_a}$$

$$R_{br} + R_a = \frac{E_g - V_b}{I_{br}}$$

$$R_{br} = \frac{E_g - V_b}{I_{br}} - R_a$$

$$= \frac{0.94 \times 230 - 3}{1.75 \times 58} - 0.28$$

$$= 1.82 \Omega$$

ACCELERATION

$$t = \frac{\Delta N}{\dots}$$

t = TIME

ΔN = CHANGE

I = MOMENT

T = TORQUE

IT IS REQ

SUITABLE PER

THE TORQUE

ACCELERATION

THE TORQUE

LIMITING RE

THE DAMAG

W 230V 58 Amp MOTOR

FIELD RESISTANCE 0.28 Ω IS

FULL LOAD RATING.

BRAKING RESISTOR.

VOLTAGE AND BRUSH DROP IS 3V.

$$\frac{E_g - V_b}{I_{br}} - R_a$$

$$\frac{3.94 \times 230 - 3}{1.75 \times 58} - 0.28$$

$$= 1.82 \Omega$$

$$= 1.82 \Omega$$

ACCELERATION TIME CONSIDERATION

$$t = \frac{\Delta N (2\pi I)}{60 T} \quad \underline{\underline{\text{sec}}}$$

t = TIME (sec)

ΔN = CHANGE IN SPEED (RPM)

I = MOMENT OF INERTIA N-m^2

T = TORQUE (N-m)

IT IS REQUIRED THAT THE MOTOR IS TO HAVE THE SUITABLE PERFORMANCE AT THE STARTING TO ENSURE THAT THE TORQUE PRODUCED BY CHOSEN MOTOR IS CAPABLE OF

ACCELERATING THE ASSOCIATED SYSTEM.




THE TORQUE PRODUCED UNDER THE RESTRICTION OF CURRENT LIMITING RESISTOR MUST HAVE APPROPRIATE VALUE TO PREVENT THE DAMAGE.

CHARACTERISTICS OF DC MOTORS

SERIES MOTOR




THE SERIES EXCITED MOTOR IS USED FOR ITS GOOD STARTING TORQUE CHARACTERISTICS

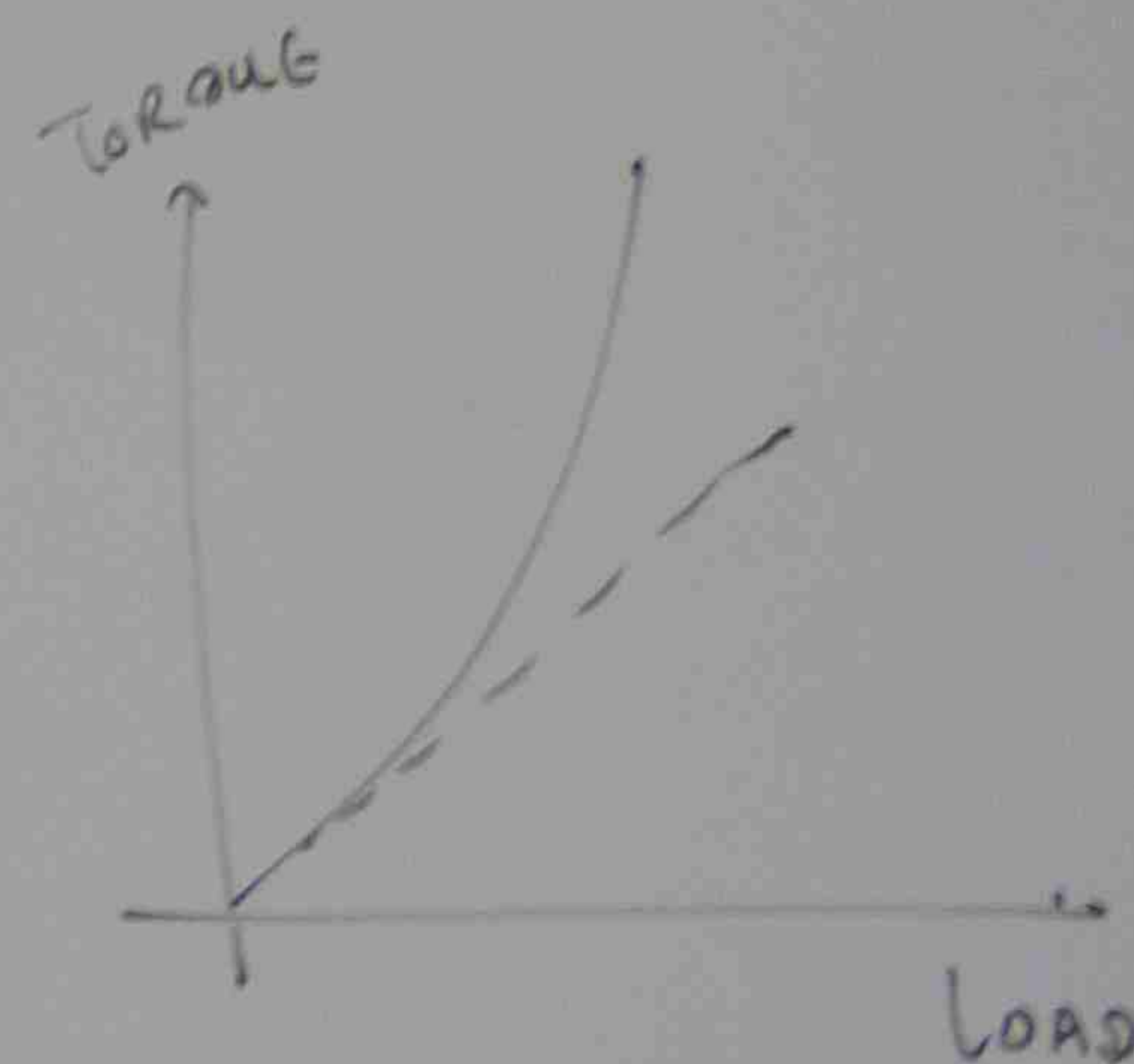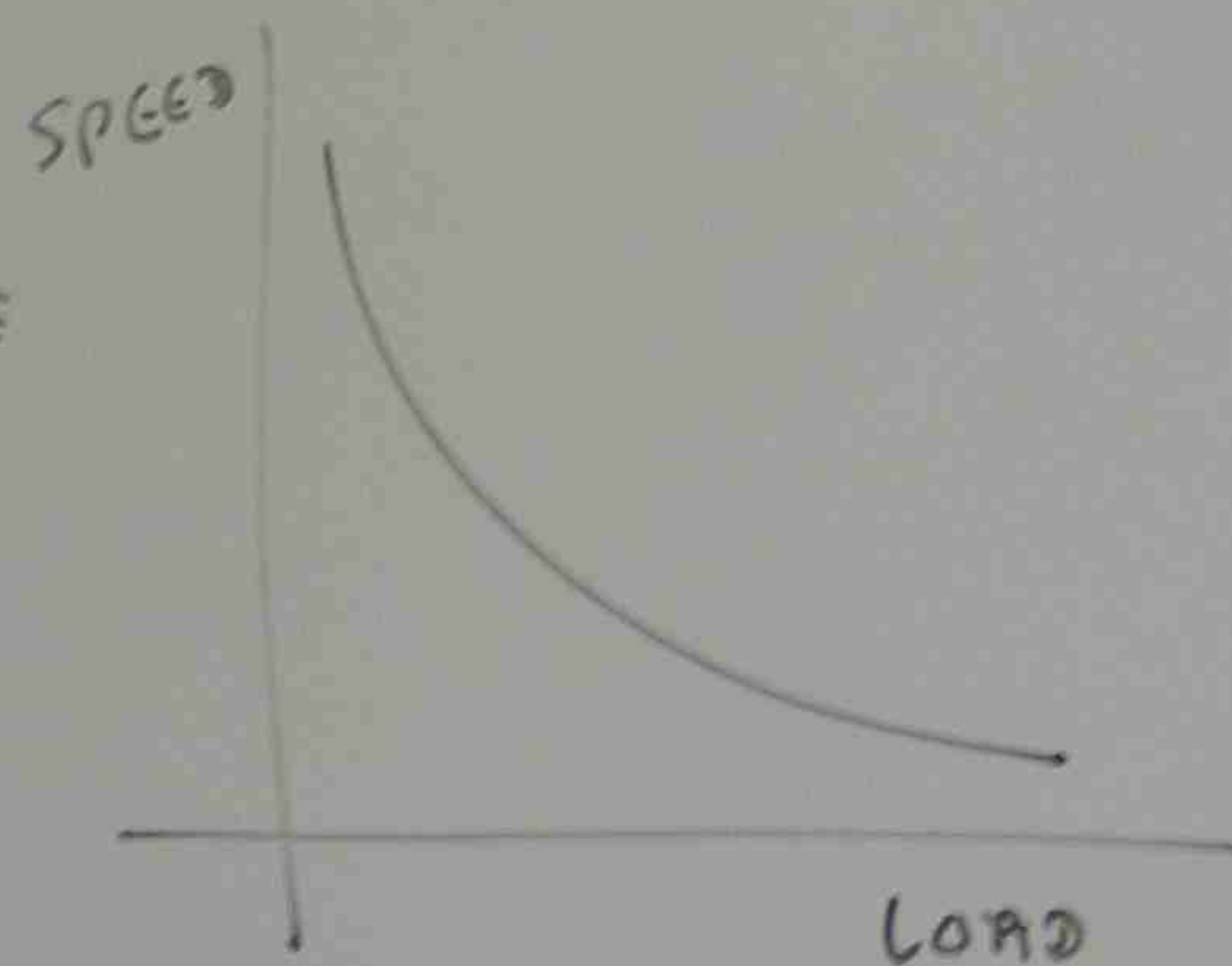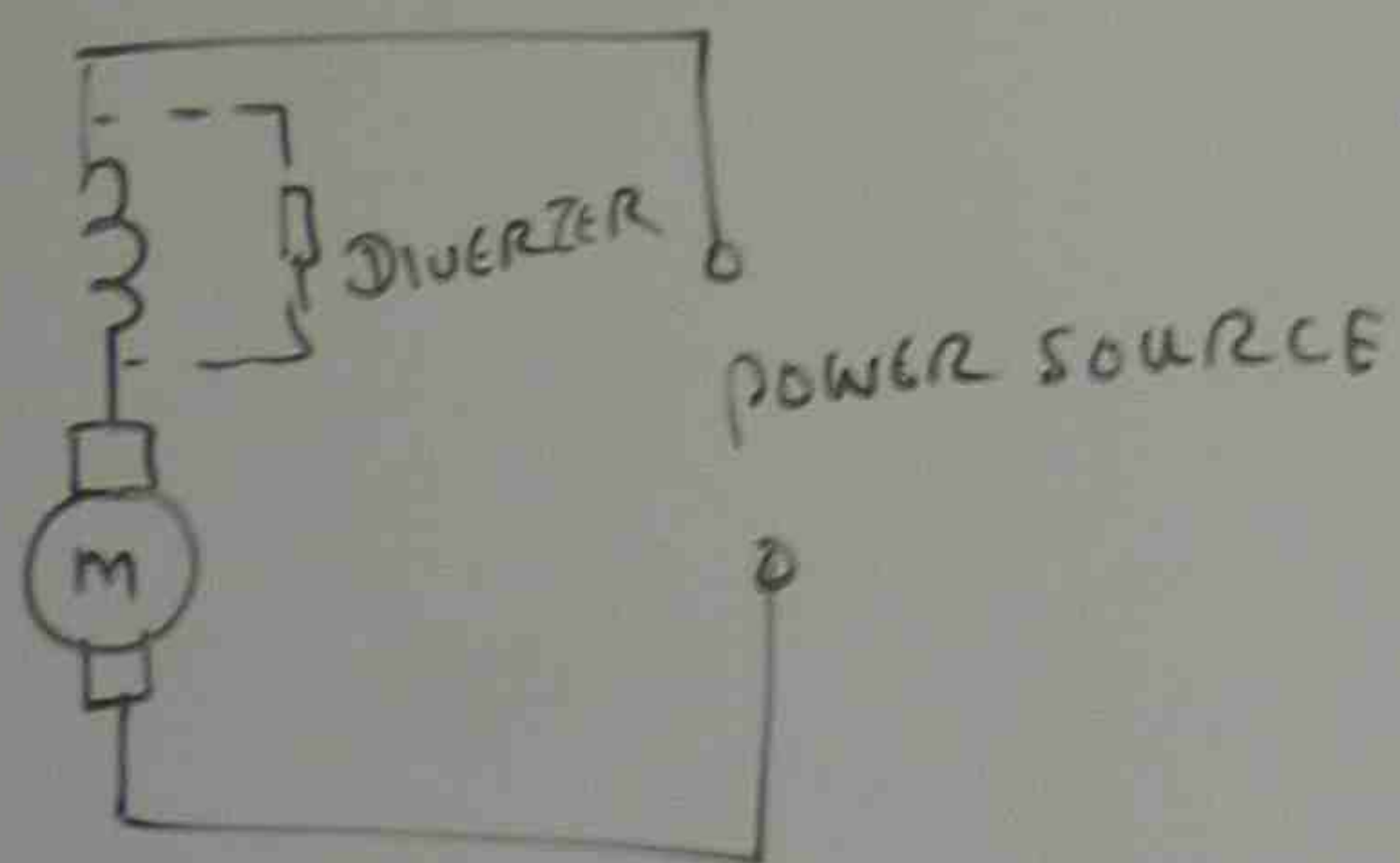Eg. TRAMS, ELEVATORS, CRANES, STARTER MOTORS




SHUNT MOTOR

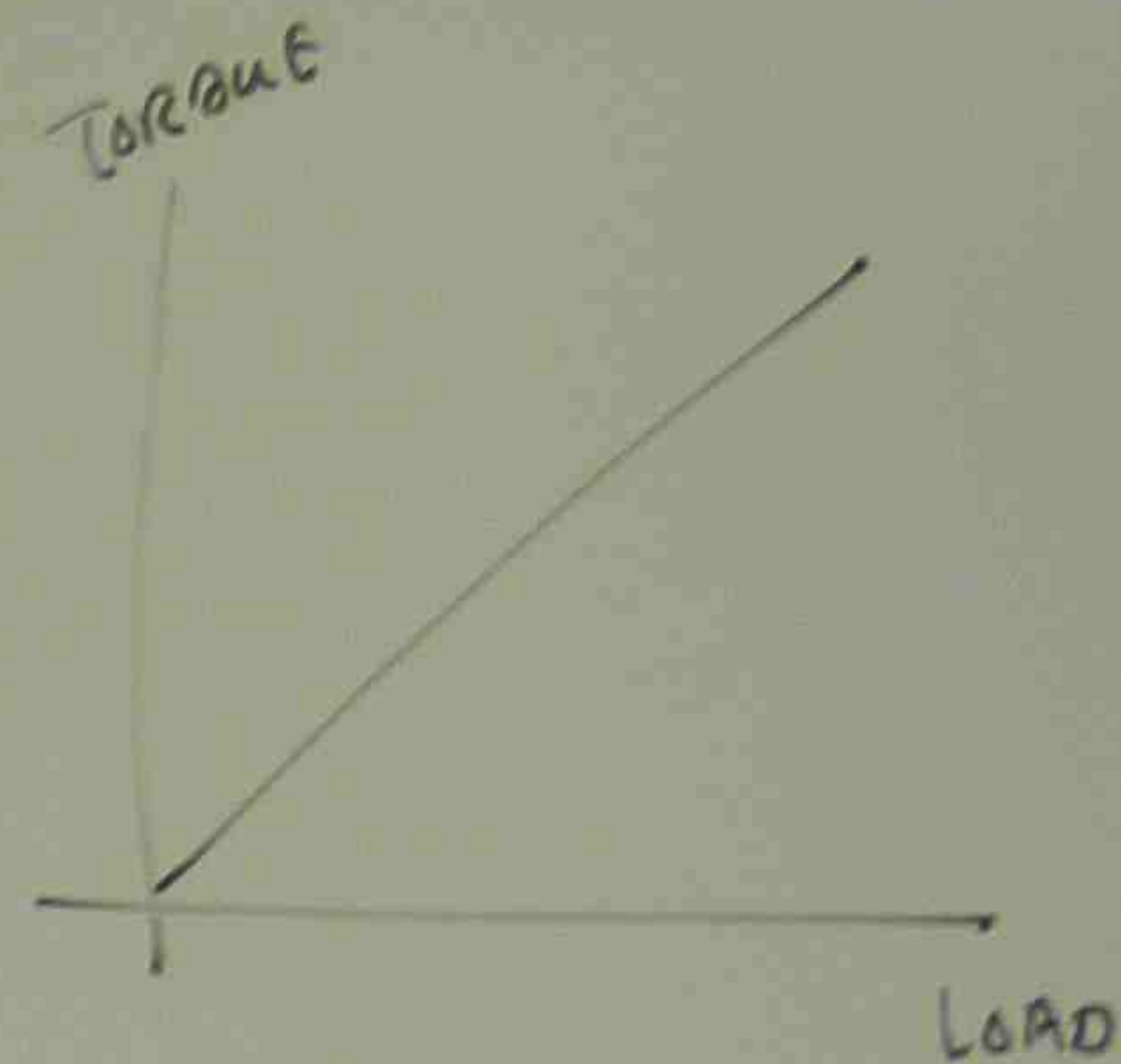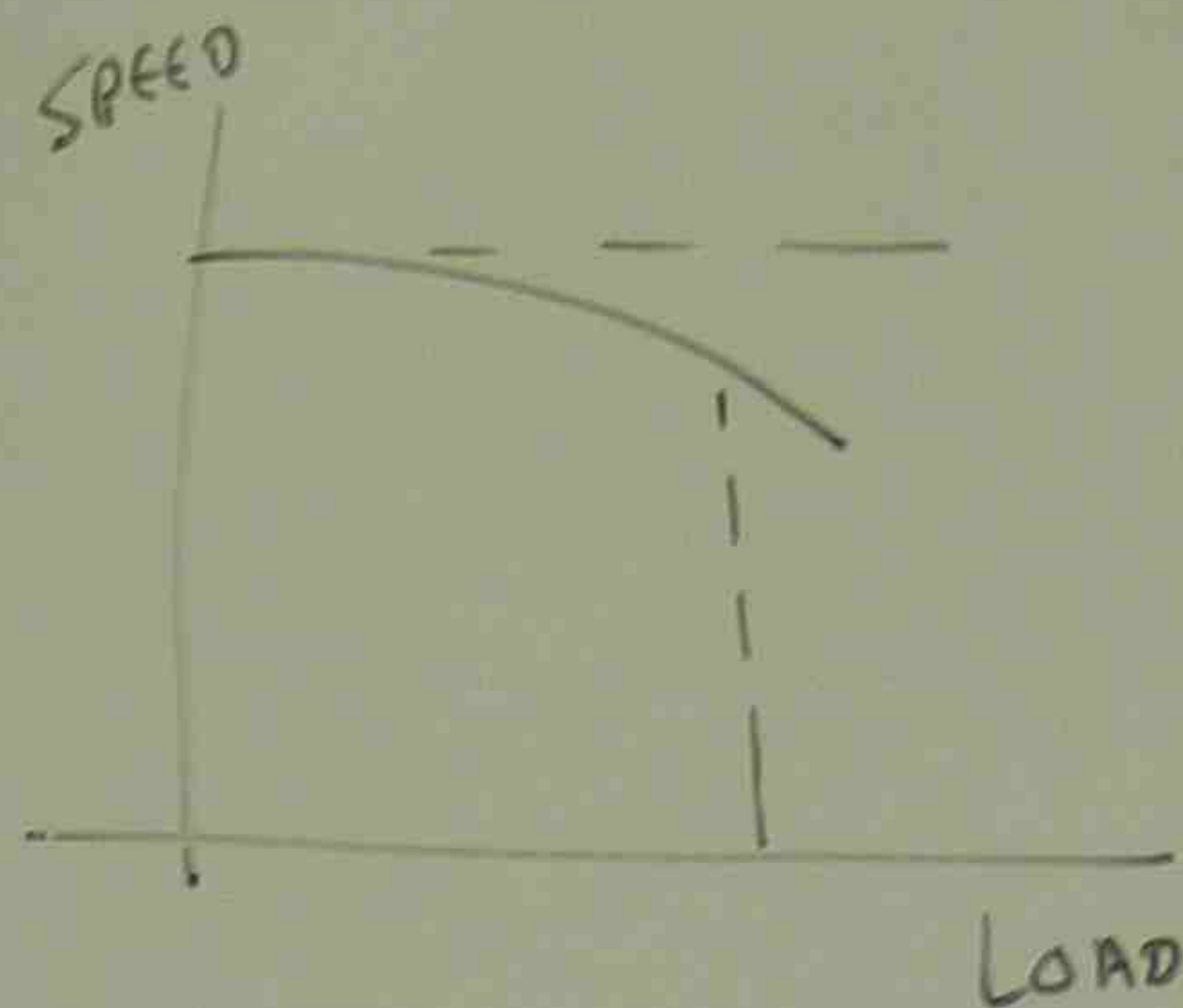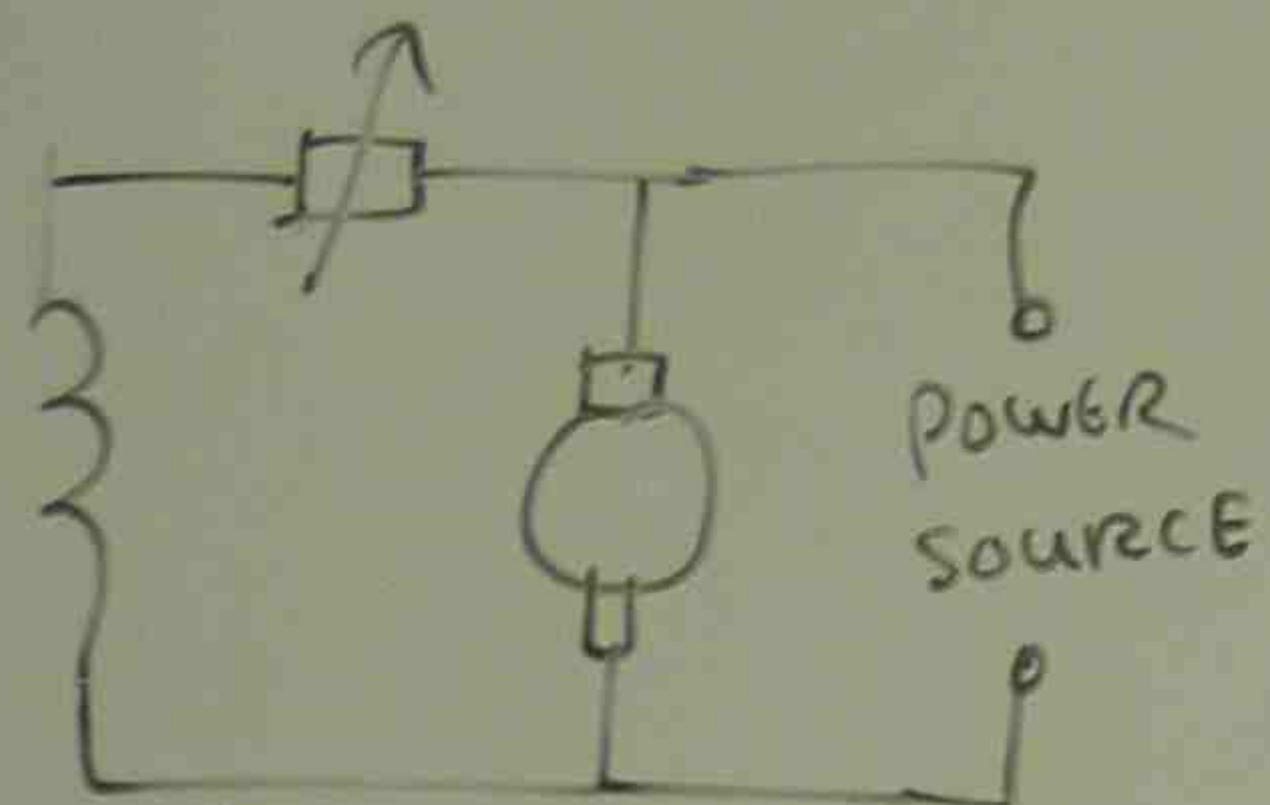THE SHUNT EXCITED MOTOR IS USED FOR ITS FAIRLY
CONSTANT SPEED CHARACTERISTICS





DIFFERENTIAL

$\phi_{sh} - \phi_{se}$
~ ~ ~ ~ ~

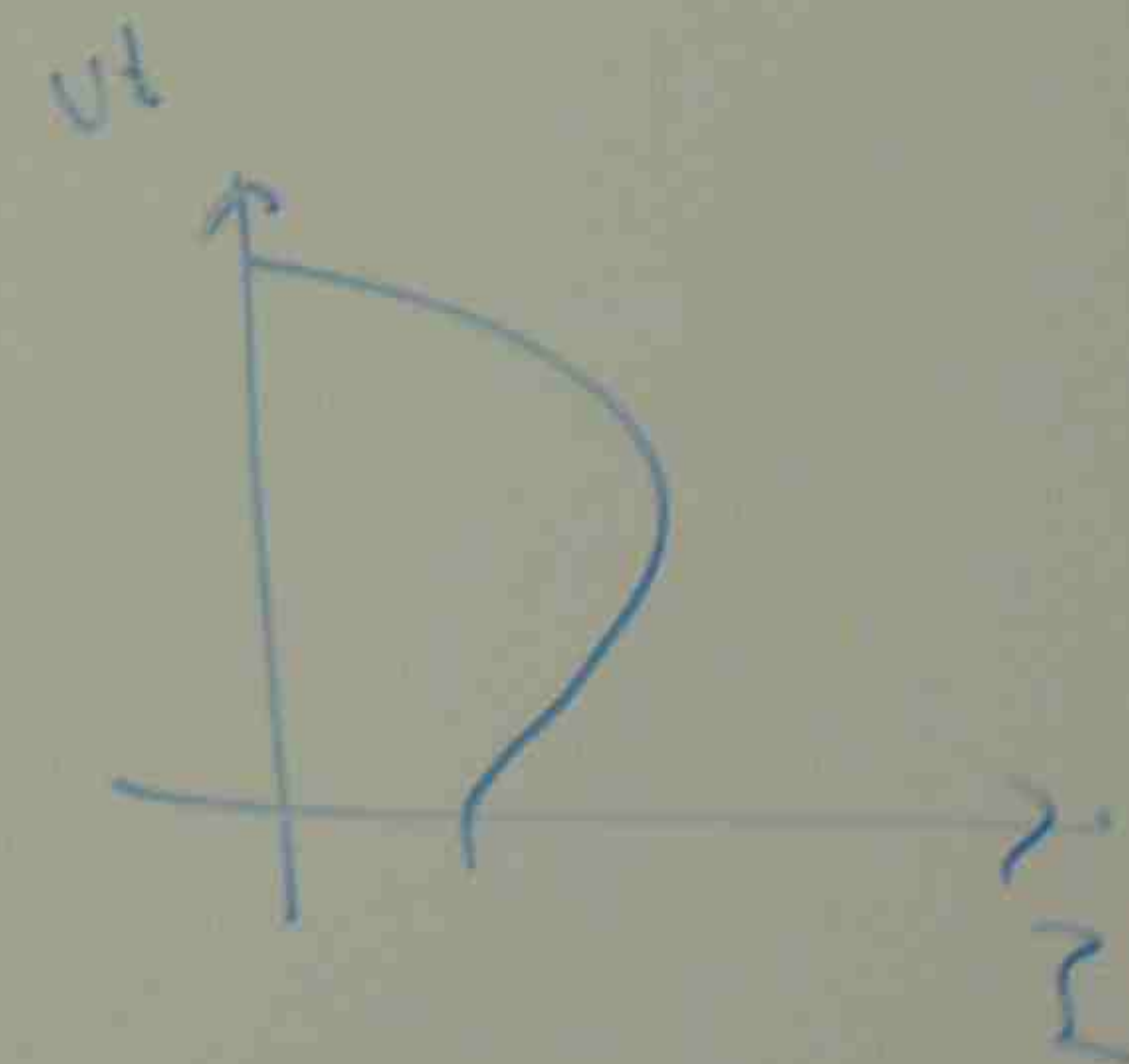


COMPOUND MOTOR

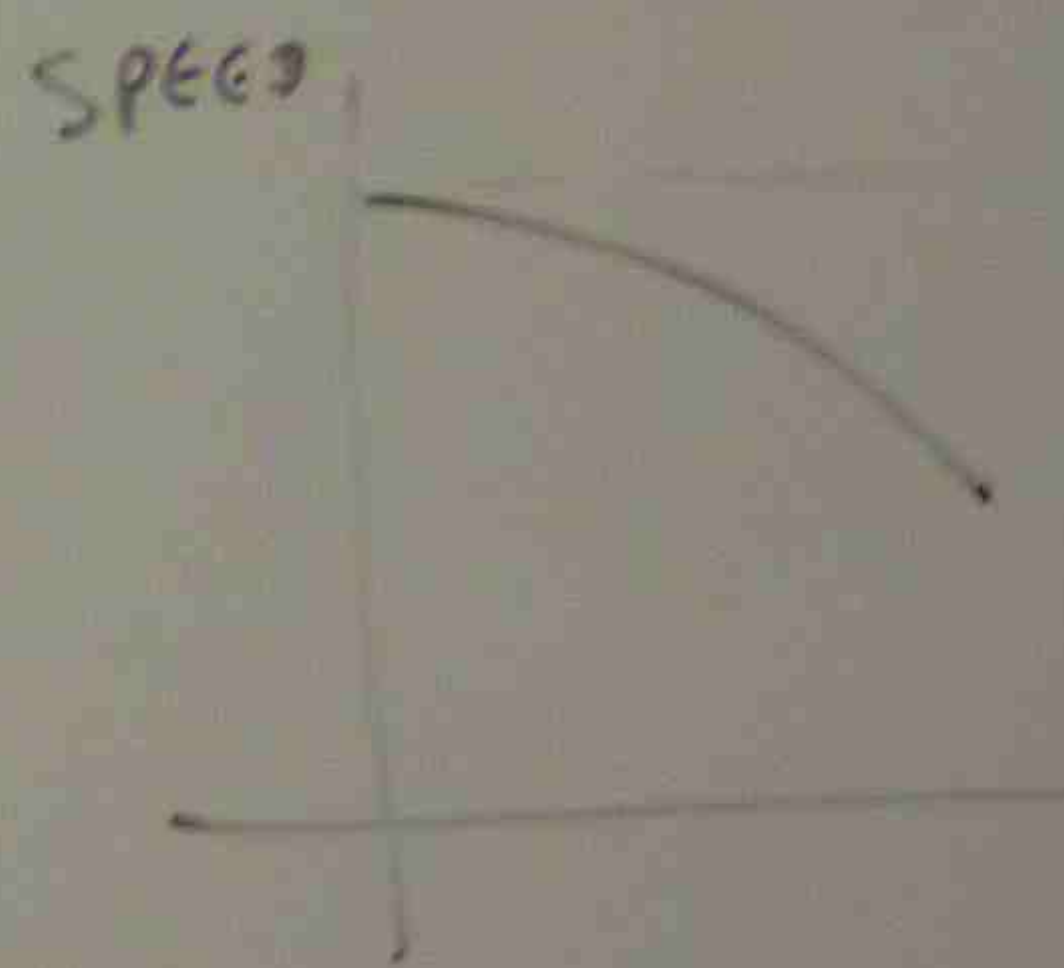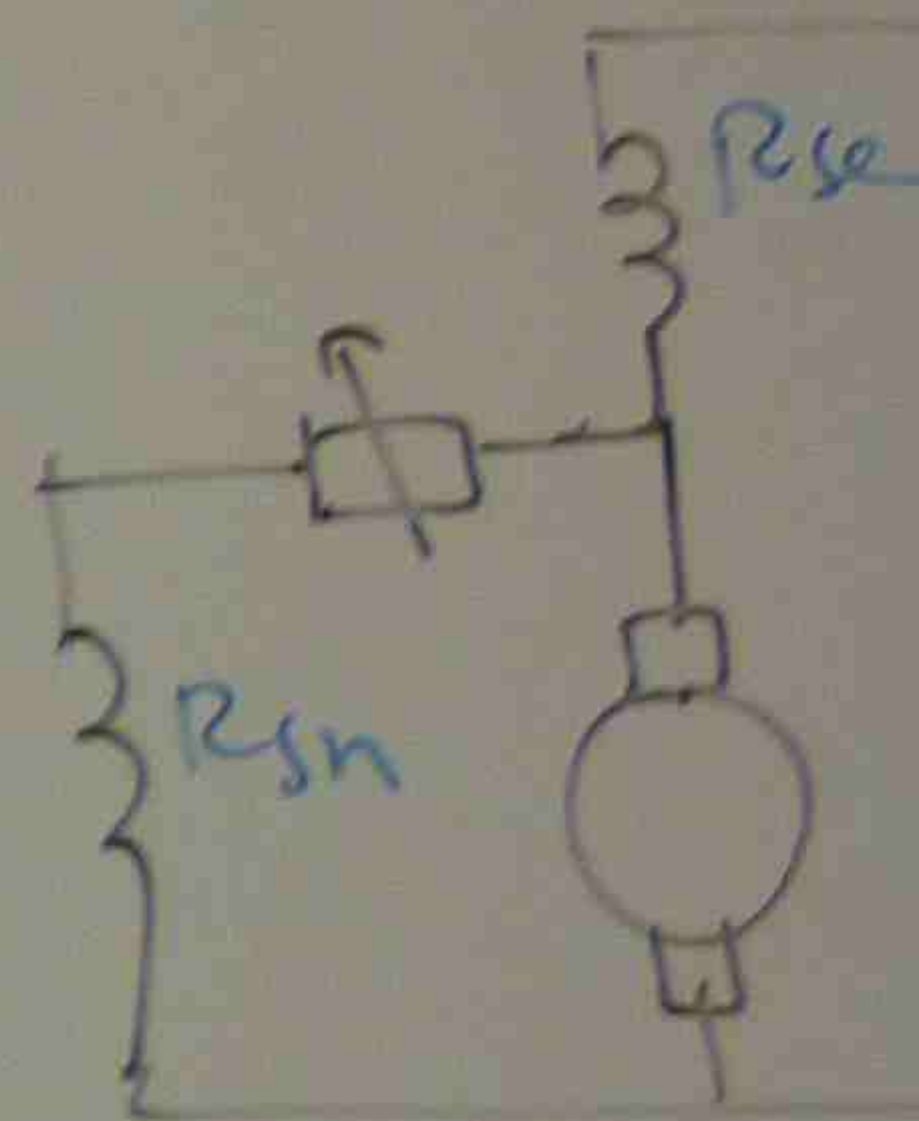THE CUMULATIVE
THE CHARACTERISTICS
SHUNT MOTORS.
SHEARS, ROLLING




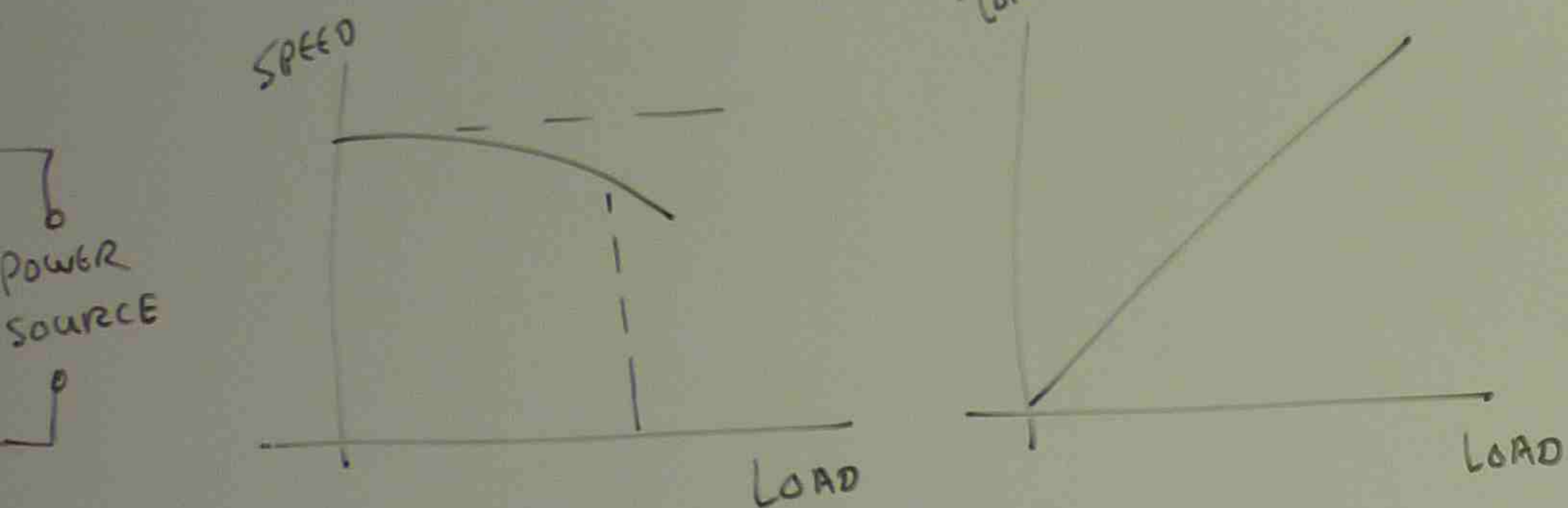DIFFERENTIAL COMPOUND MOTOR IS USED FOR ITS FAIRLY CHARACTERISTICS




DIFFERENTIAL

$\phi_{sh} - \phi_{se}$

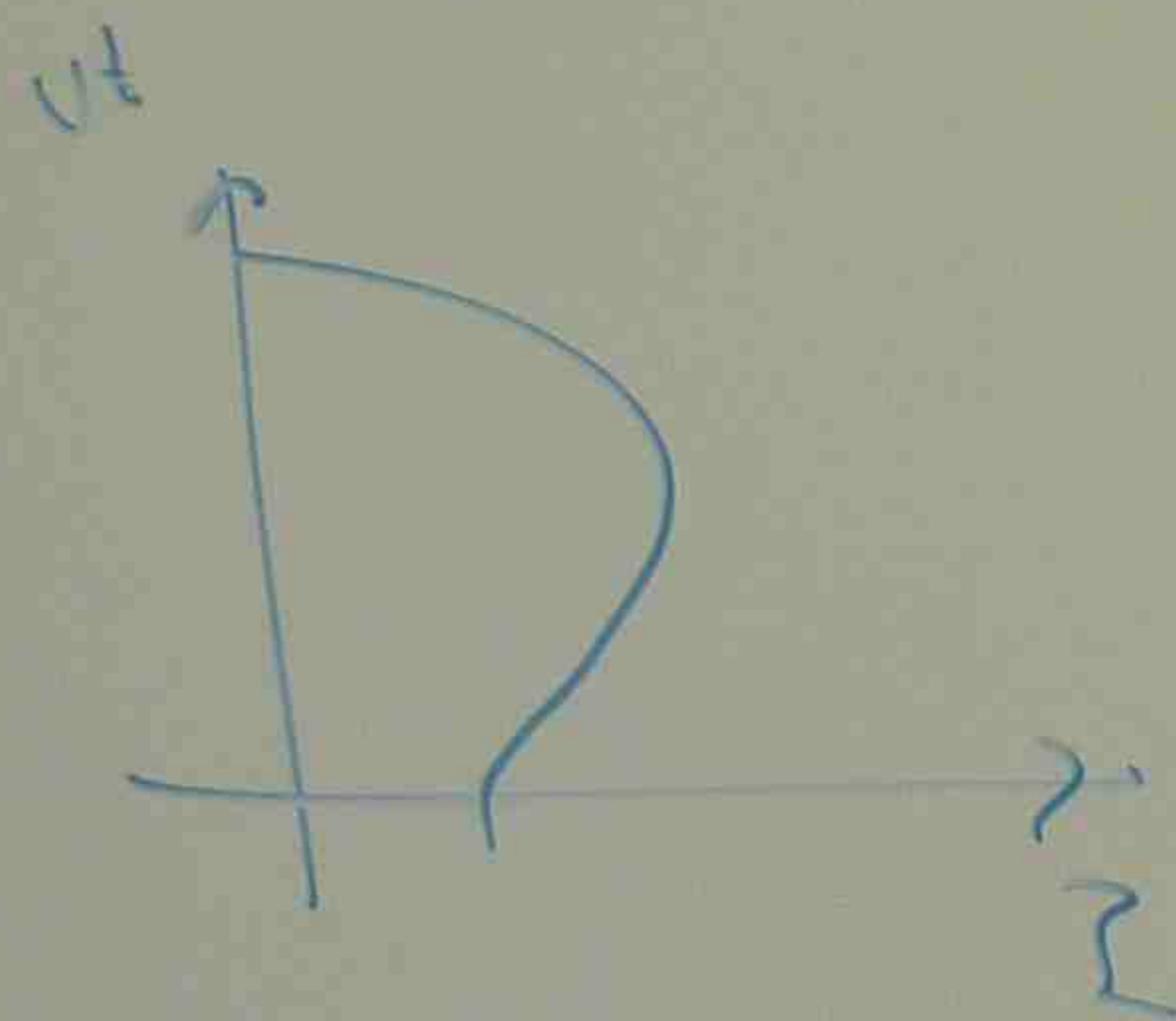

COMPOUND MOTOR

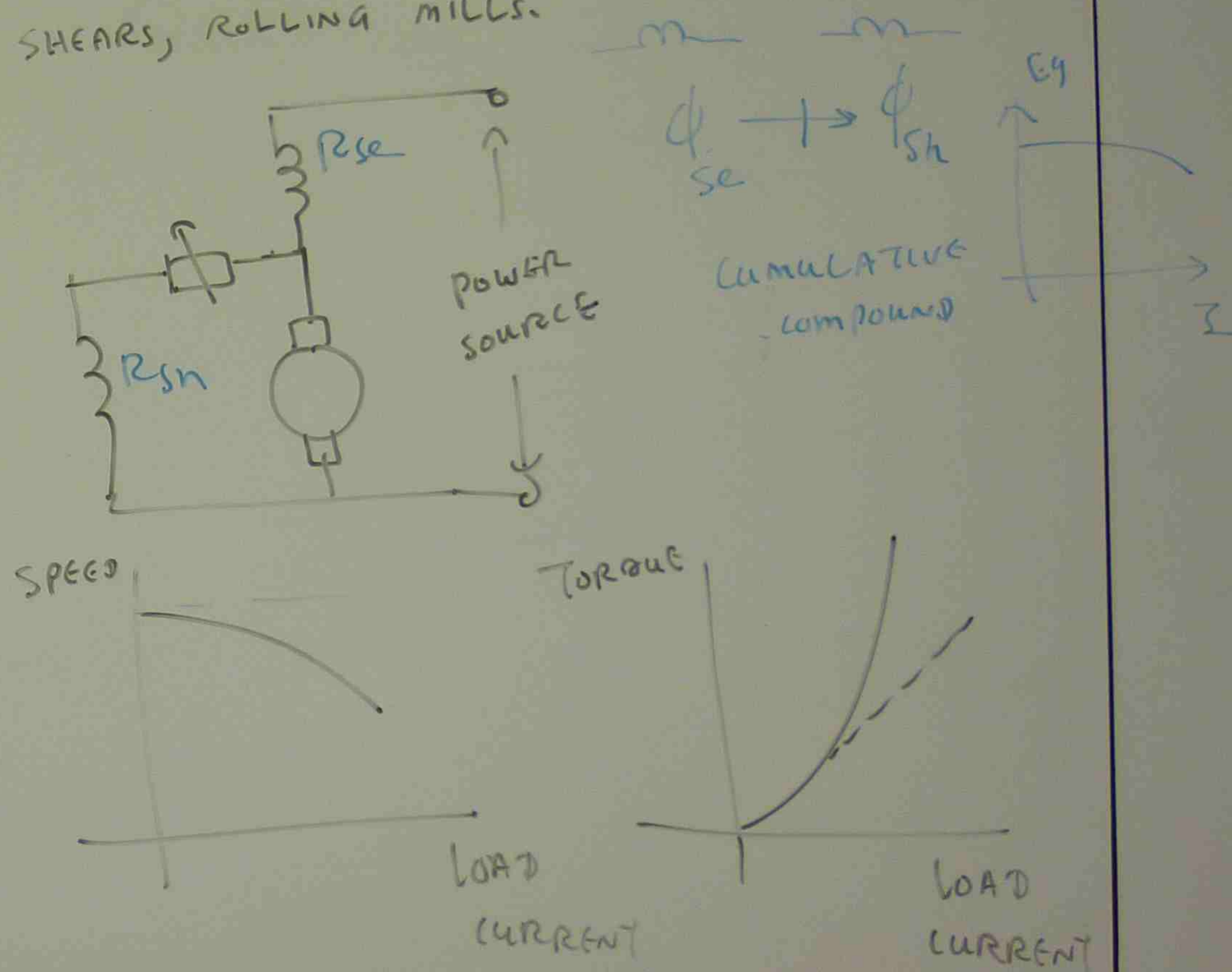THE CUMULATIVE COMPOUNDED MOTOR COMBINES THE CHARACTERISTICS OF BOTH THE SERIES AND SHUNT MOTORS. APPLICATIONS ARE PUNCHES, SHEARS, ROLLING MILLS.



DC MOTOR SPEED CONTROL

$$E_b = \frac{\phi Z N}{60} \times \frac{p}{a}$$


ϕ = Flux

Z = ARMATURE CONDUCTORS


N = SPEED

p = NO. OF POLES

a = NO. OF ARMATURE PARALLEL PATHS

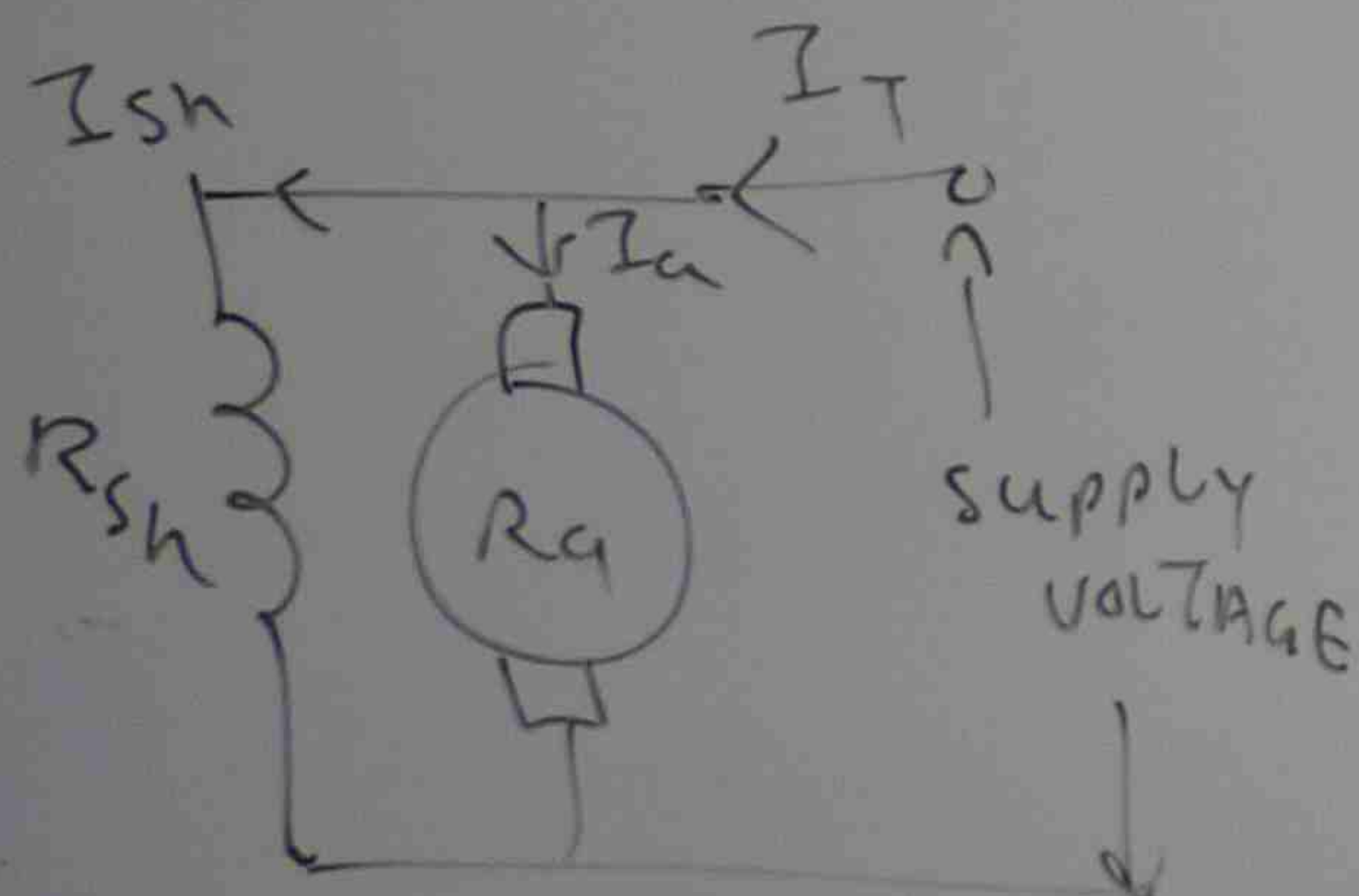

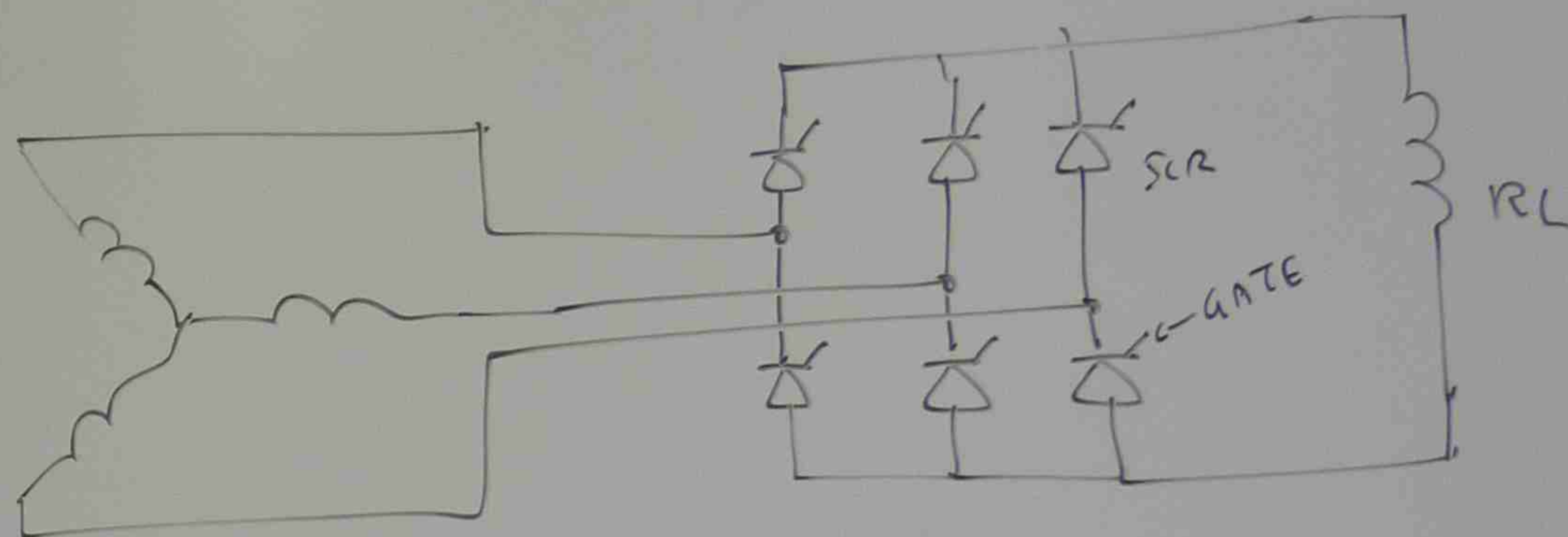
By adjusting field current, DC motor speed can be controlled




SCR (SILICON CONTROLLED RECTIFIER)

AC motor
SPEED CONTROL

DC motor
SPEED CONTROL

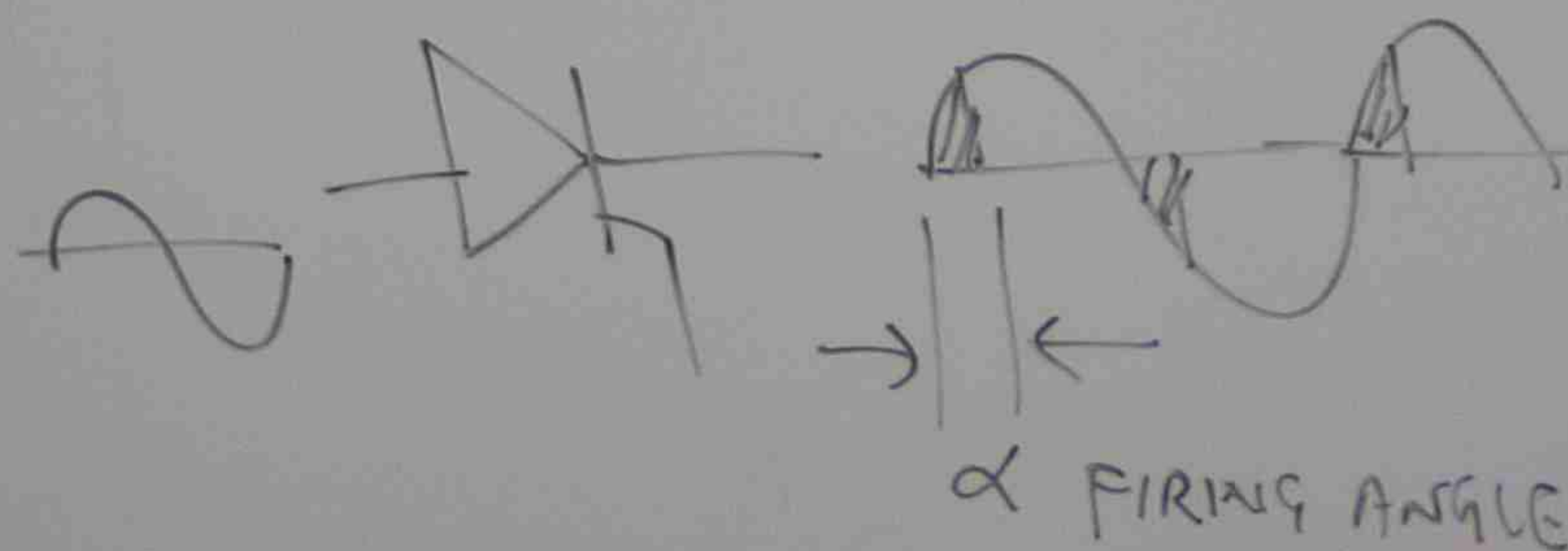


SPEED CAN BE CONTROLLED

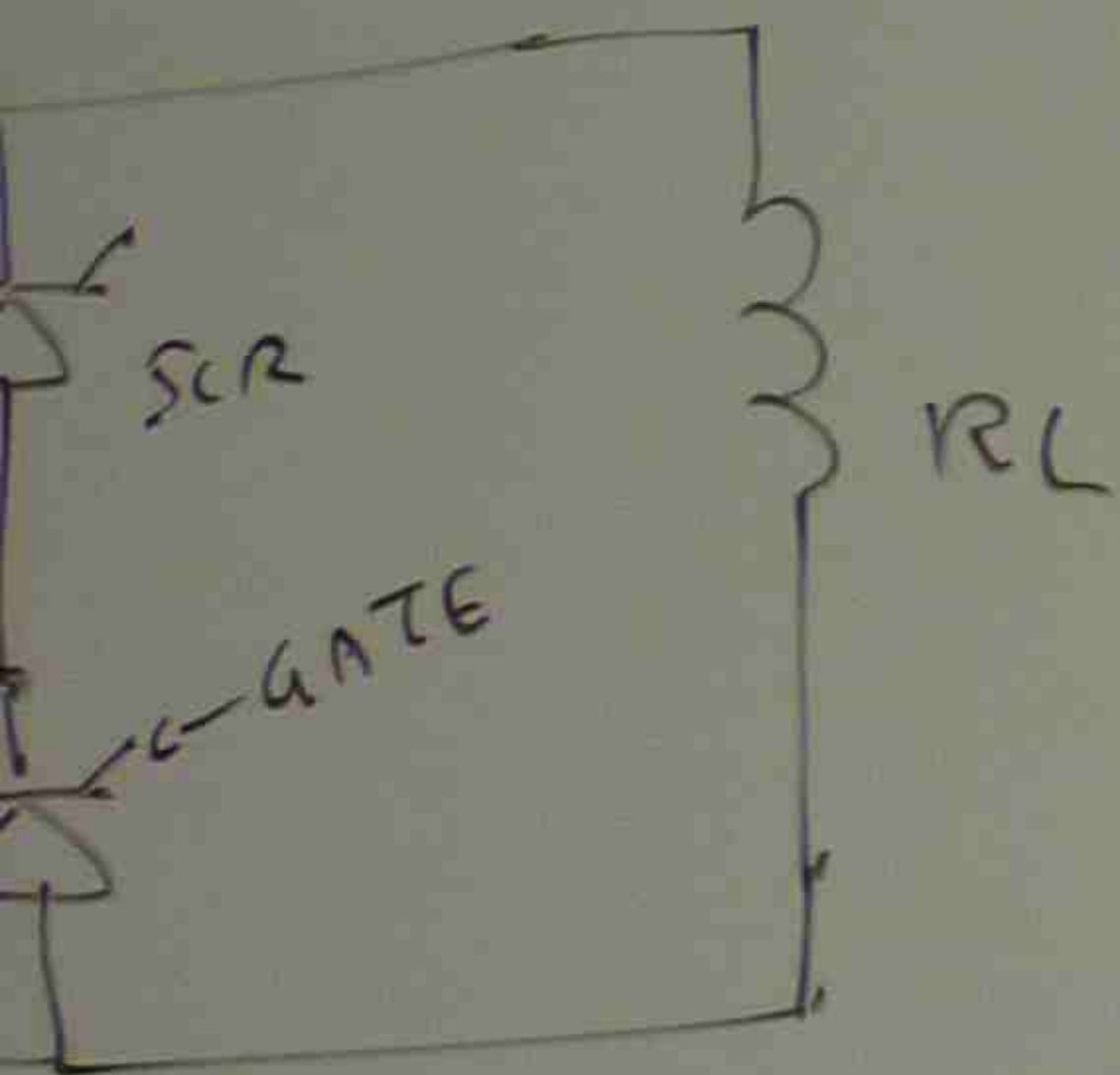


RECTIFIER)

CONTROL


BLOCK DIAGRAM OF SCR CONTROLLED MOTOR

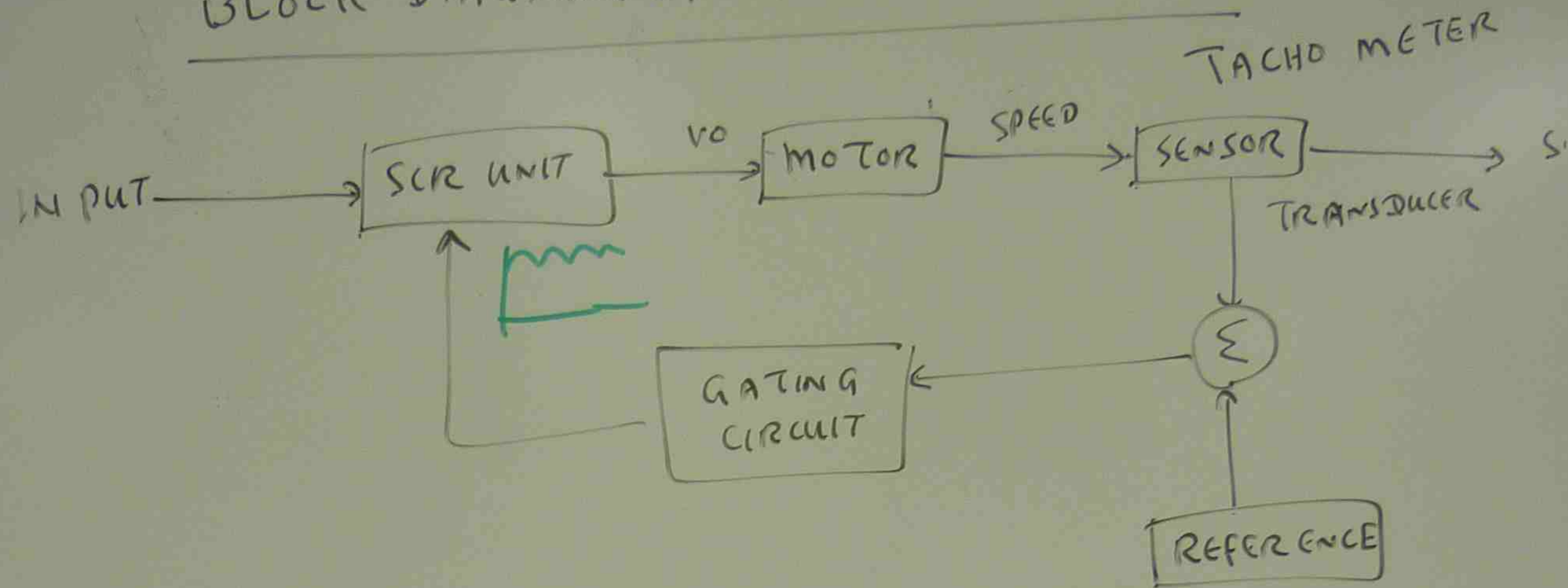

HEATING EFFECT OF RIPPLE


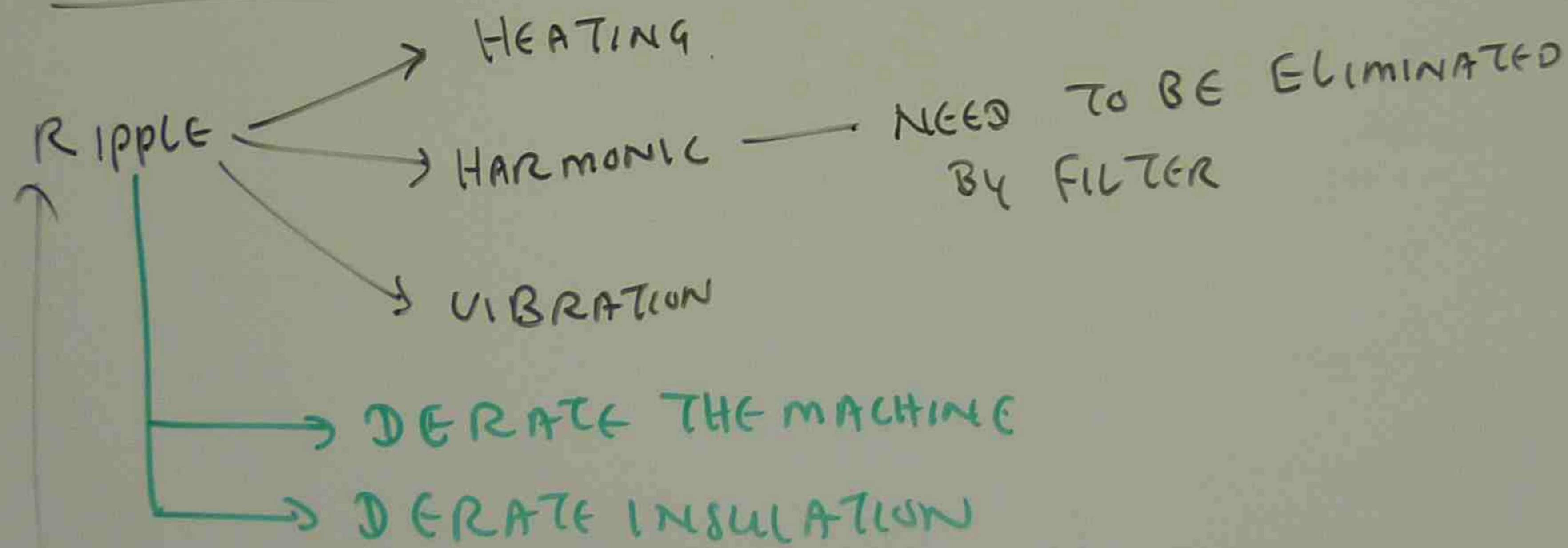


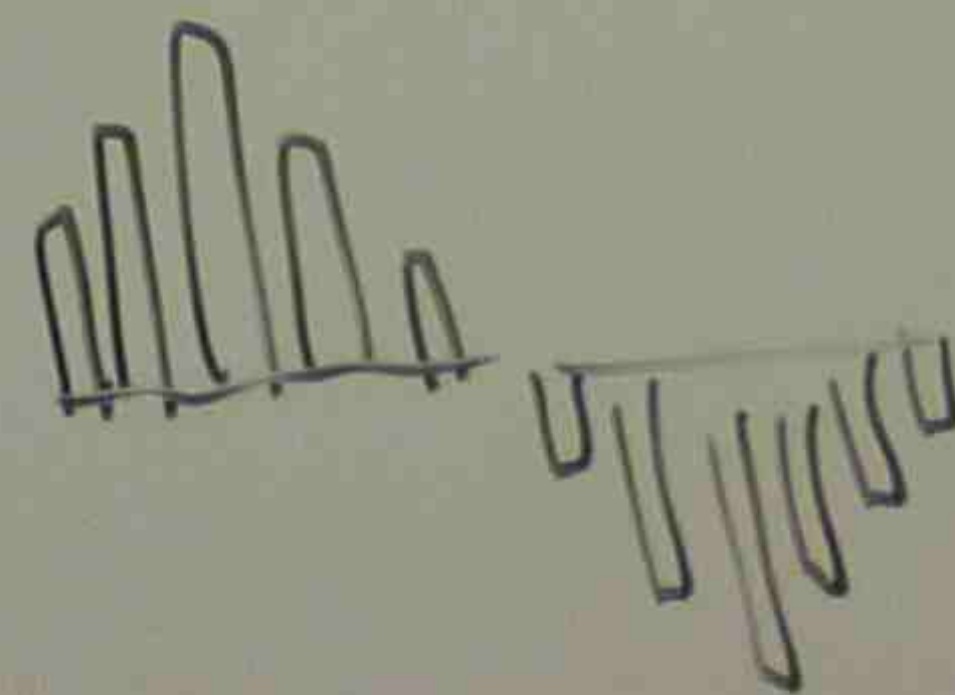
PRODUCED BY
HIGH FREQUENCY
SWITCHING CIRCUITS
PWM DRIVES




PWM - PULSE WIDTH
MODULATION

$$N = \frac{120f}{P}$$

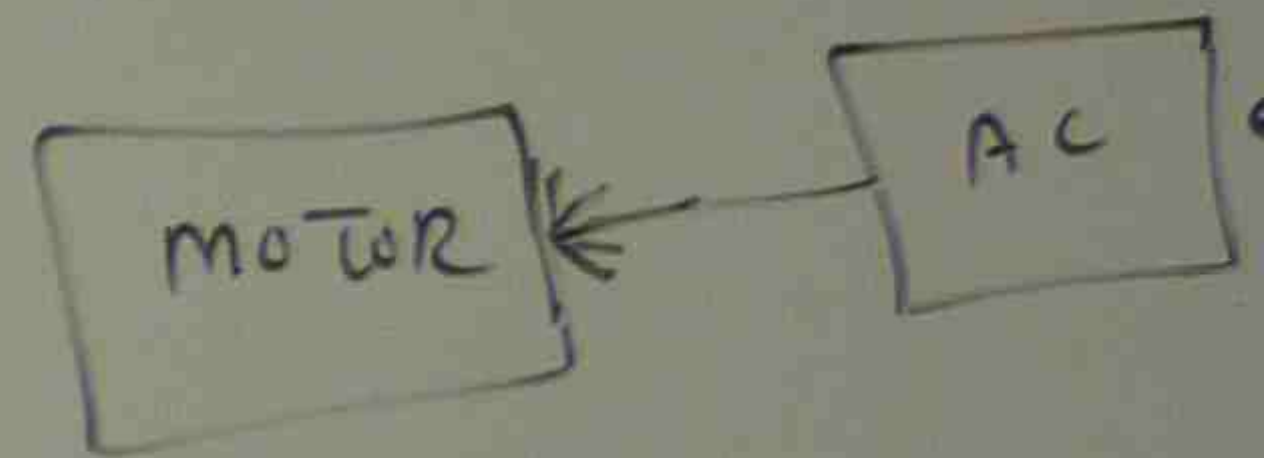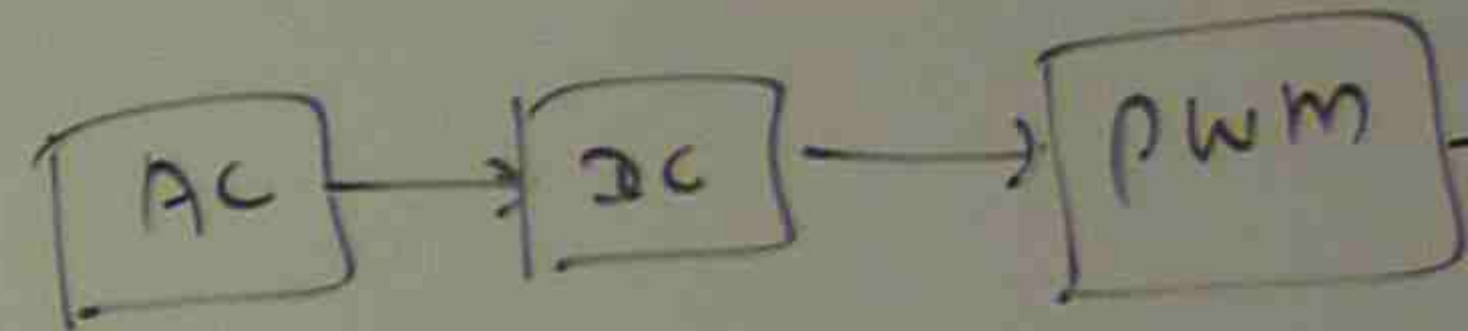

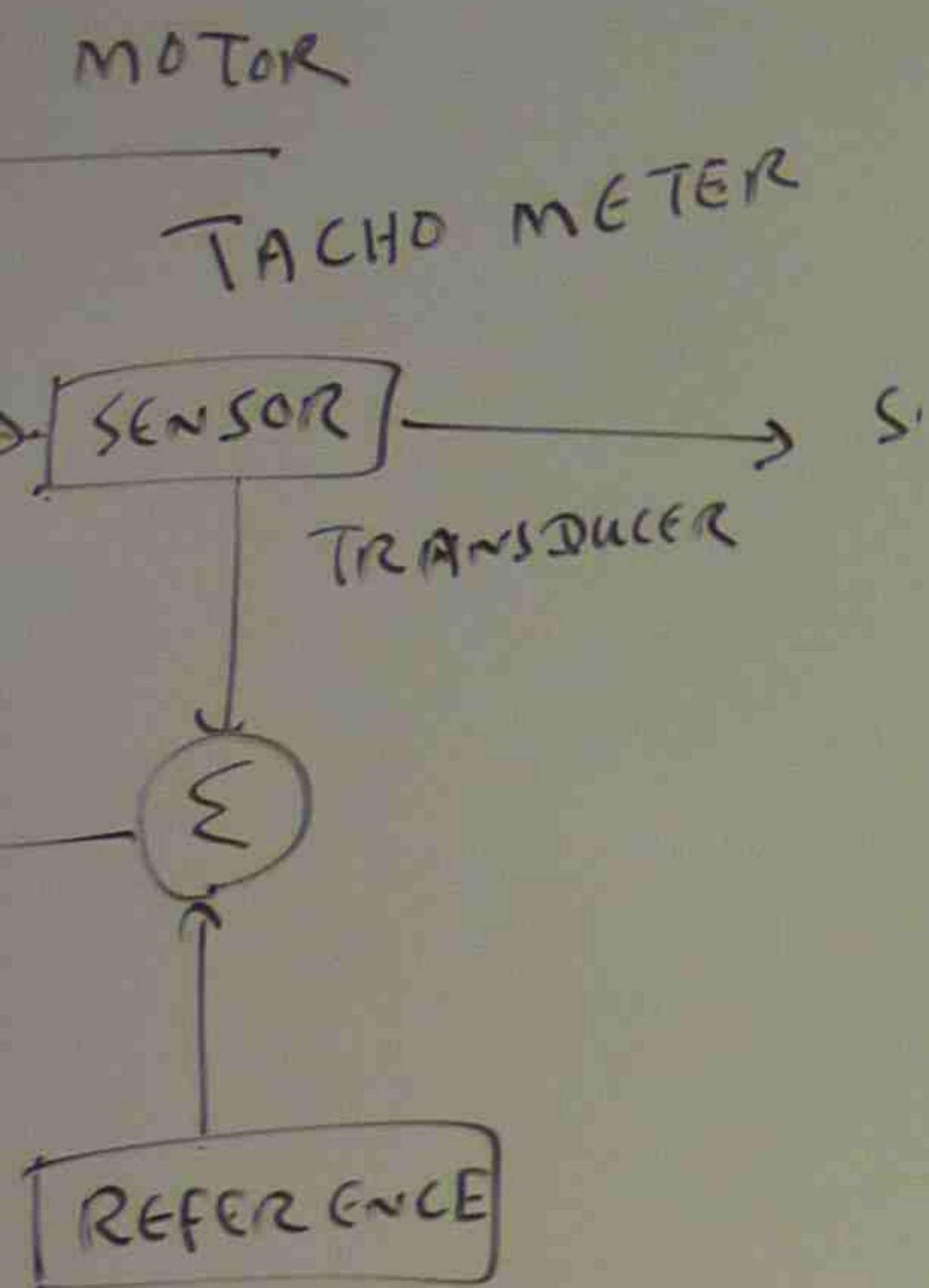


$$N = \frac{120 f}{P}$$

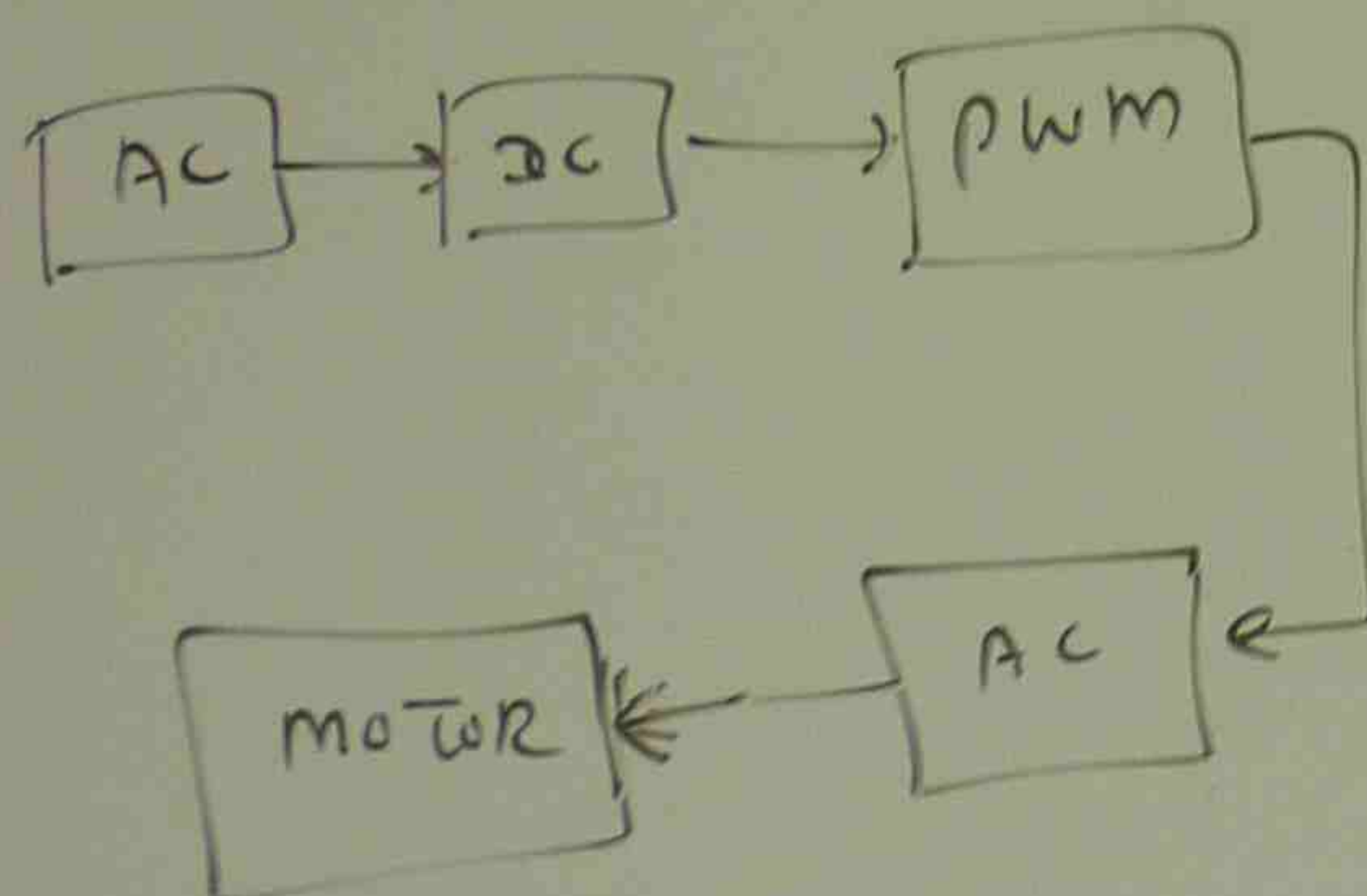


MINATED

WM - PULSE WIDTH MODULATION

SPEED CONTROL

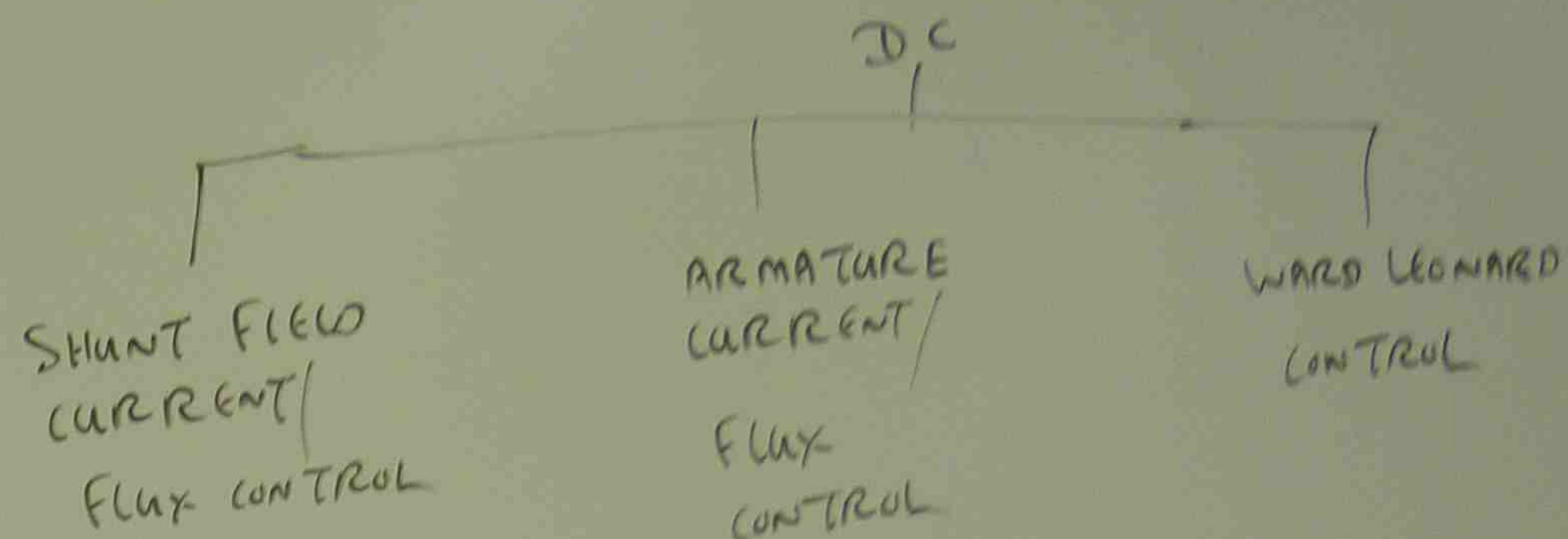

WARD LEONARD SYSTEM

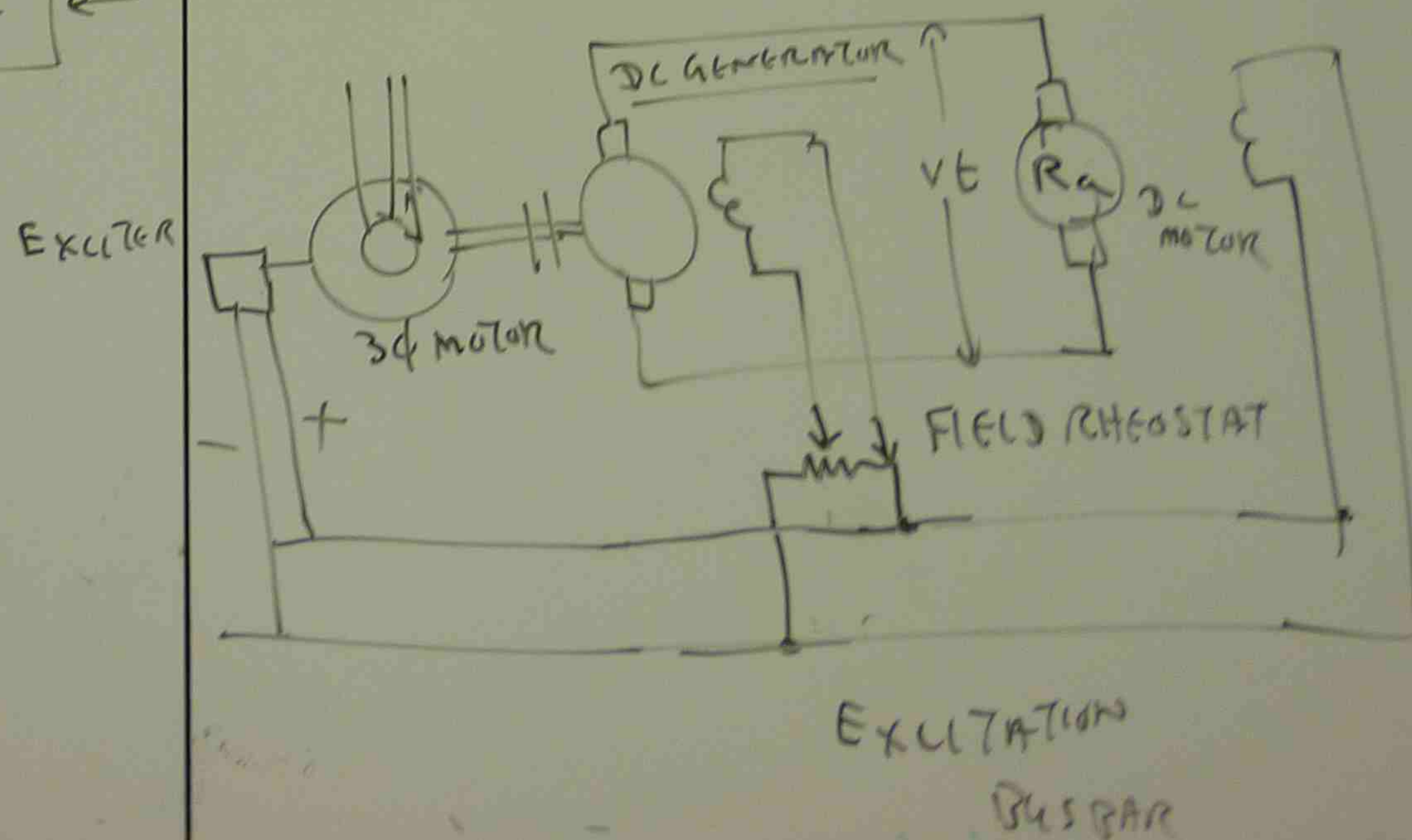

WARD LEONARD

DC GENERATOR

DC MOTOR

DC GENERATOR

BY FIELD

GENERATOR

FIELD

GENERATOR

CURRENT

ARMATURE

WARD LEONARD SYSTEM

DC GENERATOR GENERATED VOLTAGE IS SUPPLIED TO DC MOTOR ARMATURE.

DC GENERATOR FIELD EXCITATION IS VARIED BY FIELD RHEOSTAT.

GENERATED VOLTAGE DEPENDS ON DC GENERATOR FIELD EXCITATION.

GENERATED VOLTAGE INCLUDES THE VARIABLE CURRENT SUPPLIED TO DC MOTOR ARMATURE AND MOTOR SPEED IS VARIED

DC MOTOR TORQUE-SPEED RELATIONSHIP

$$T = K_t \phi I_a$$

$T = \text{TORQUE, (N-m)}$, $\phi = \text{FLUX (wb)}$, $I_a = \text{ARMATURE CURRENT (amp)}$

$$K_t = \frac{P Z}{2 \pi a}$$

$P = \text{NO. OF POLES}$

$Z = \text{NO. OF CONDUCTORS IN ARMATURE}$

$a = \text{NO. OF ARMATURE PARALLEL PATHS}$

$$E_g = K_e \phi N$$

$E_g = \text{GENERATED VOLTAGE}$

$$K_e = \frac{P Z}{60 a}$$

RELATIONSHIP

I_a = ARMATURE
CURRENT (Amp)

F POLES

OF CONDUCTORS IN

ARMATURE

OF ARMATURE

PARALLEL PATHS

GENERATED VOLTAGE

$$T = \frac{k_t \phi V_t}{R_a} = \frac{k_e k_t \phi^2 N}{R_a}$$

pb A 4 POLE WAVE WOUND ARMATURE OPERATING
IN A FIELD OF FLUX 0.01 Wb IN WOUND WITH
360 ARMATURE CONDUCTORS.

DETERMINE THE EXPRESSION OF TORQUE AS
A FUNCTION OF SPEED IF $V_t = 250V$ AND

$R_a = 0.1 \Omega$.

$$T = \frac{k_t \phi v_t}{Ra} - \frac{k_e k_t \phi^2 N}{Ra}$$

$$k_t = \frac{p z}{2 \pi a}$$

$$a = \frac{p z}{2 m} \quad \text{for LAP}$$

$$2 m \quad \text{for WAVE}$$

$$= \frac{4 \times 360}{2 \times 3.1416 \times 2}$$

ASSUME SIMPLEX WAVE

$$m = 1$$

$$= 114.5$$

$$a = 2 \times m = 2 \times 1 = 2$$

$$k_e = \frac{p z}{60 a} = \frac{4 \times 360}{60 \times 2} = 12$$

$$T = \frac{114.5 \times 0.01 \times 250}{0.1} - \frac{12 \times 114.5 \times (0.01)^2 \times N}{0.1}$$

$$T = 2800 - 1.38 N$$

$$\text{NO LOAD} \rightarrow T = 0$$

$$0 = 2800 - 1.38 N$$

$$1.38 N = 2800$$

$$N = \frac{2800}{1.38} = 2028 \text{ RPM}$$

N

FOR LAP

FOR WAVE

COMPLEX WAVE




$$2 \times 1 = 2$$

$$\frac{114.5 \times (0.01)^2 \times N}{0.1}$$

$$38 N = 2800$$

$$N = \frac{2800}{1.38} = 2028 \text{ RPM}$$

DC MOTOR TORQUE & SPEED RELATIONSHIP

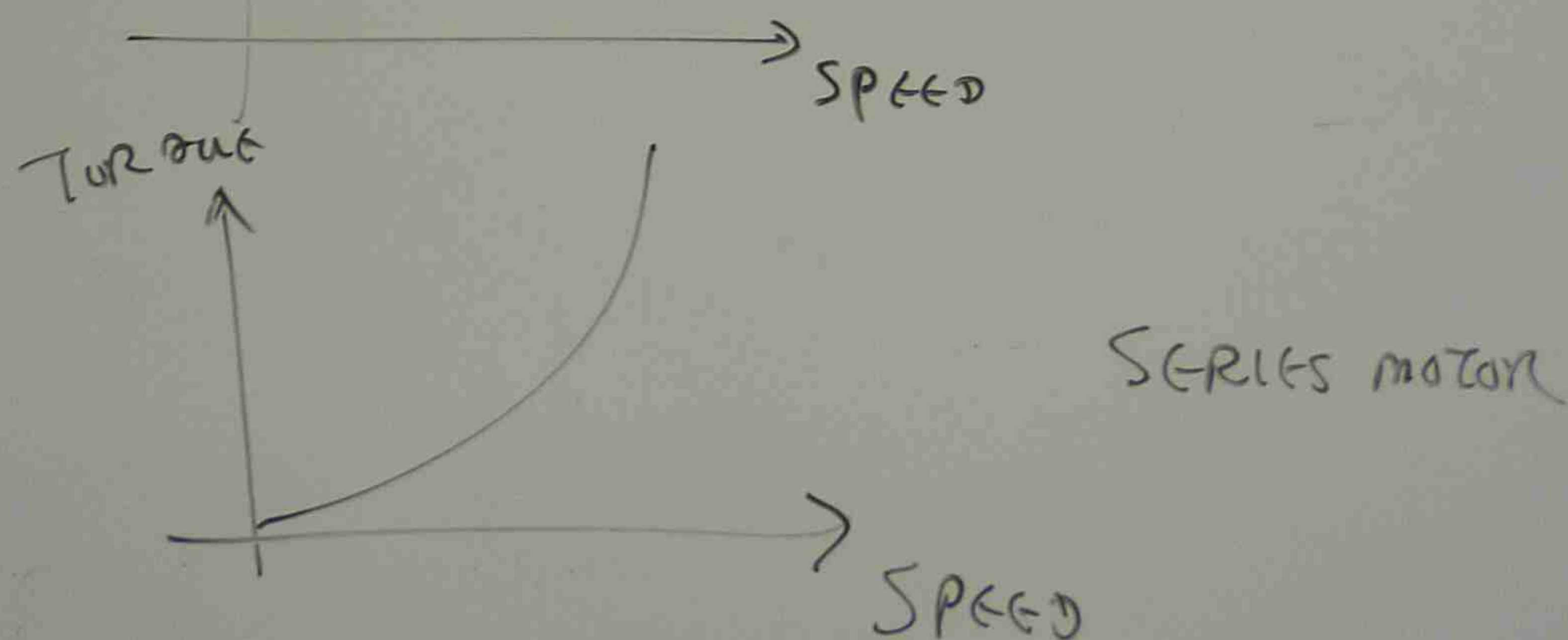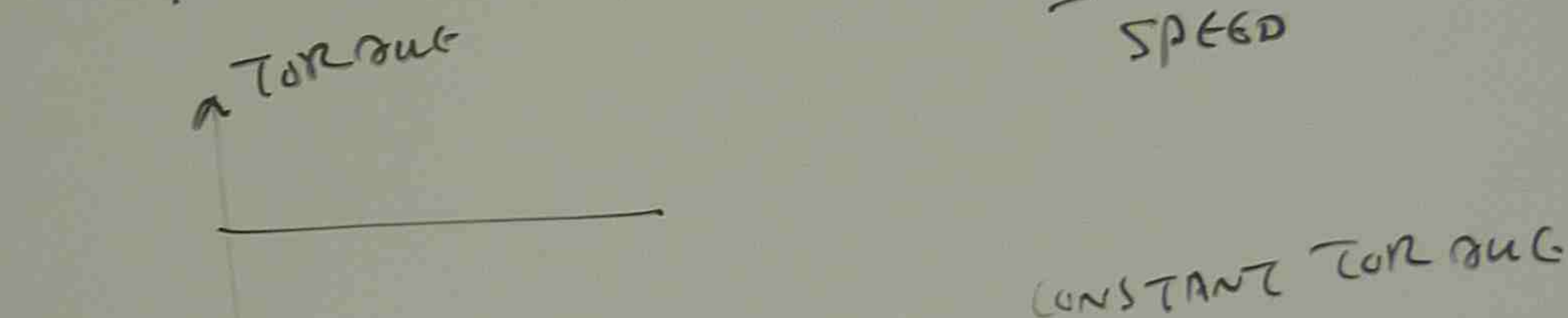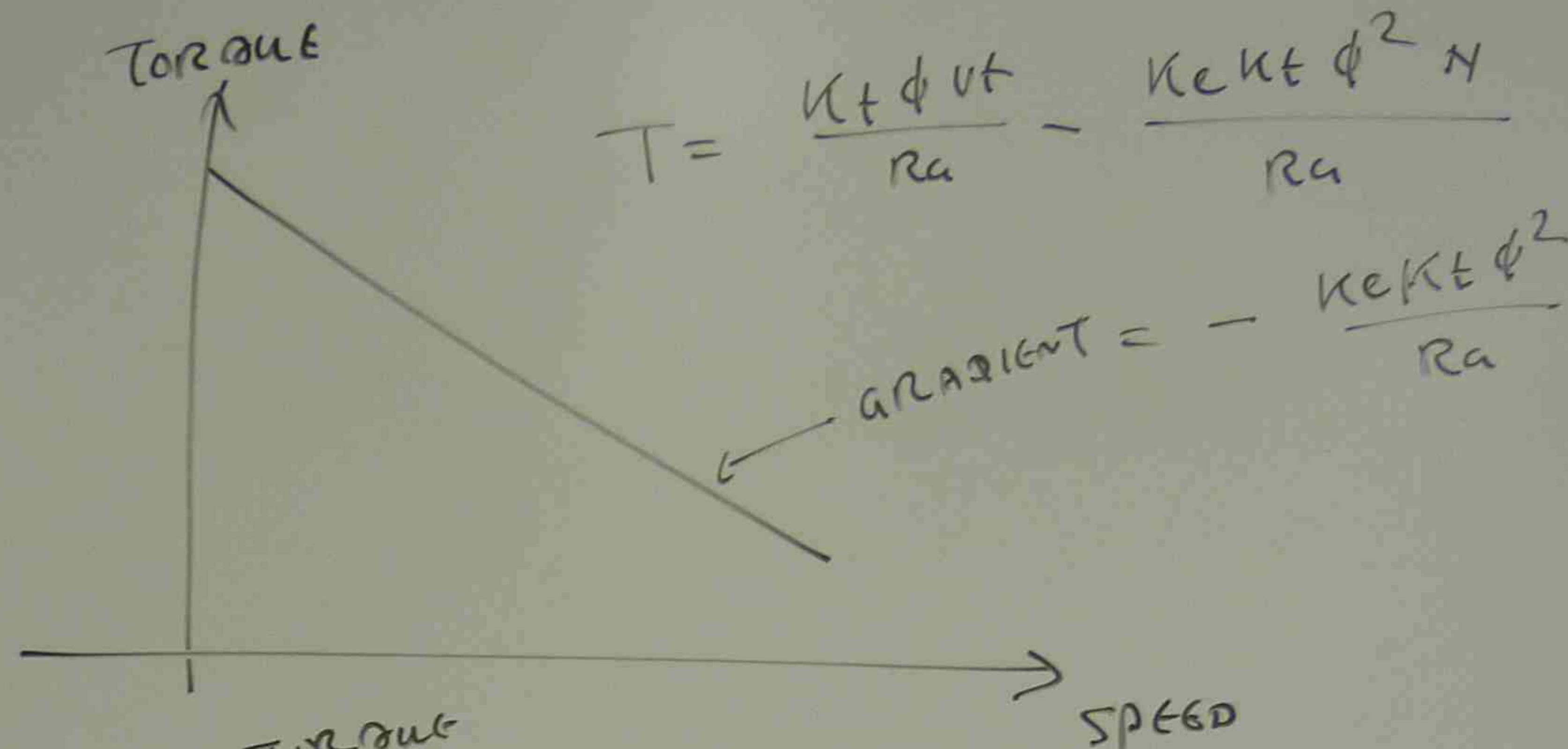

MATCH THE MOTOR

pb For motor
For load

TO MATCH THE
SPEED IN EACH

motor &

motor
2860

28

SPEED RELATIONSHIP

$$\frac{E_b}{R_a} - \frac{k_e k_t \phi^2 N}{R_a}$$

$$\text{GRADIENT} = - \frac{k_e k_t \phi^2}{R_a}$$

→ SPEED

CONSTANT TORQUE

SERIES MOTOR

SPEED

MATCH THE MOTOR AND DRIVE SYSTEM.

pb

FOR MOTOR $T = 2860 - 1.38 N$

FOR LOAD (i) $T = 50 + 1.25 N$

(ii) $T = 50 + 0.625 \times 10^{-4} N^2$

TO MATCH THE MOTOR AND LOAD, CALCULATE THE EQUILIBRIUM SPEED IN EACH INSTANCE.

MOTOR & LOAD $T = 50 + 1.25 N$

MOTOR TORQUE = LOAD TORQUE

$$2860 - 1.38 N = 50 + 1.25 N$$

$$2860 - 50 = 1.38 N + 1.25 N$$

$$2.63 N = 2810$$

$$N = \frac{2810}{2.63} = 1087 \text{ RPM}$$

motor & load $T = 50 + 0.625 \times 10^{-4} N^2$

motor Torque = Load Torque

$2860 - 1.38 N = 50 + 0.625 \times 10^{-4} N^2$

$0.625 \times 10^{-4} N^2 + 1.38 N - 2810 = 0$

$Ax^2 + Bx + C = 0$

$$X = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$

$X = N, A = 0.625 \times 10^{-4}, B = 1.38, C = -2810$

$$N = \frac{-1.38 \pm \sqrt{(1.38)^2 - 4 \times 0.625 \times 10^{-4} \times (-2810)}}{2 \times 0.625 \times 10^{-4}}$$

$$N = \frac{-1.38 \pm 1.622}{1.25 \times 10^{-4}}$$

$$= \frac{-1.38 + 1.622}{1.25 \times 10^{-4}}$$

$$= 1930 \text{ rpm}$$


DPDT
SWITCH

$$N = \frac{-1.38 \pm 1.622}{1.25 \times 10^{-4}}$$


$$= \frac{-1.38 + 1.622}{1.25 \times 10^{-4}}$$

$$= 1930 \text{ rpm}$$

DC MOTOR BRAKING

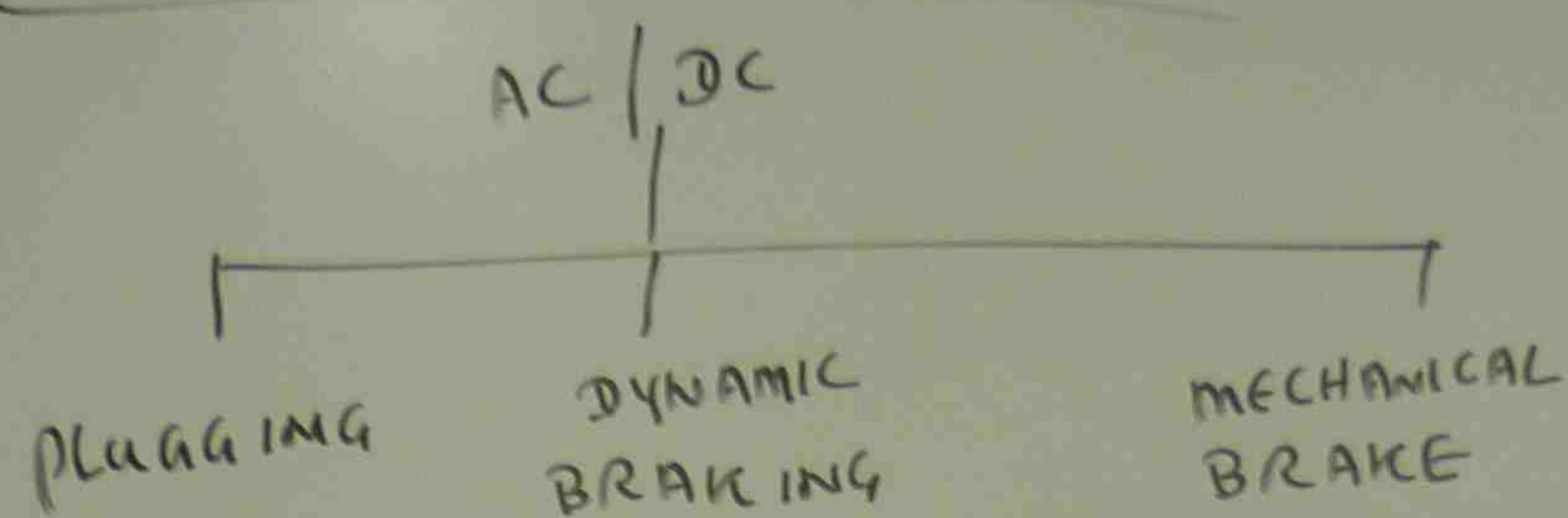


BRAKING BY PLUGGING

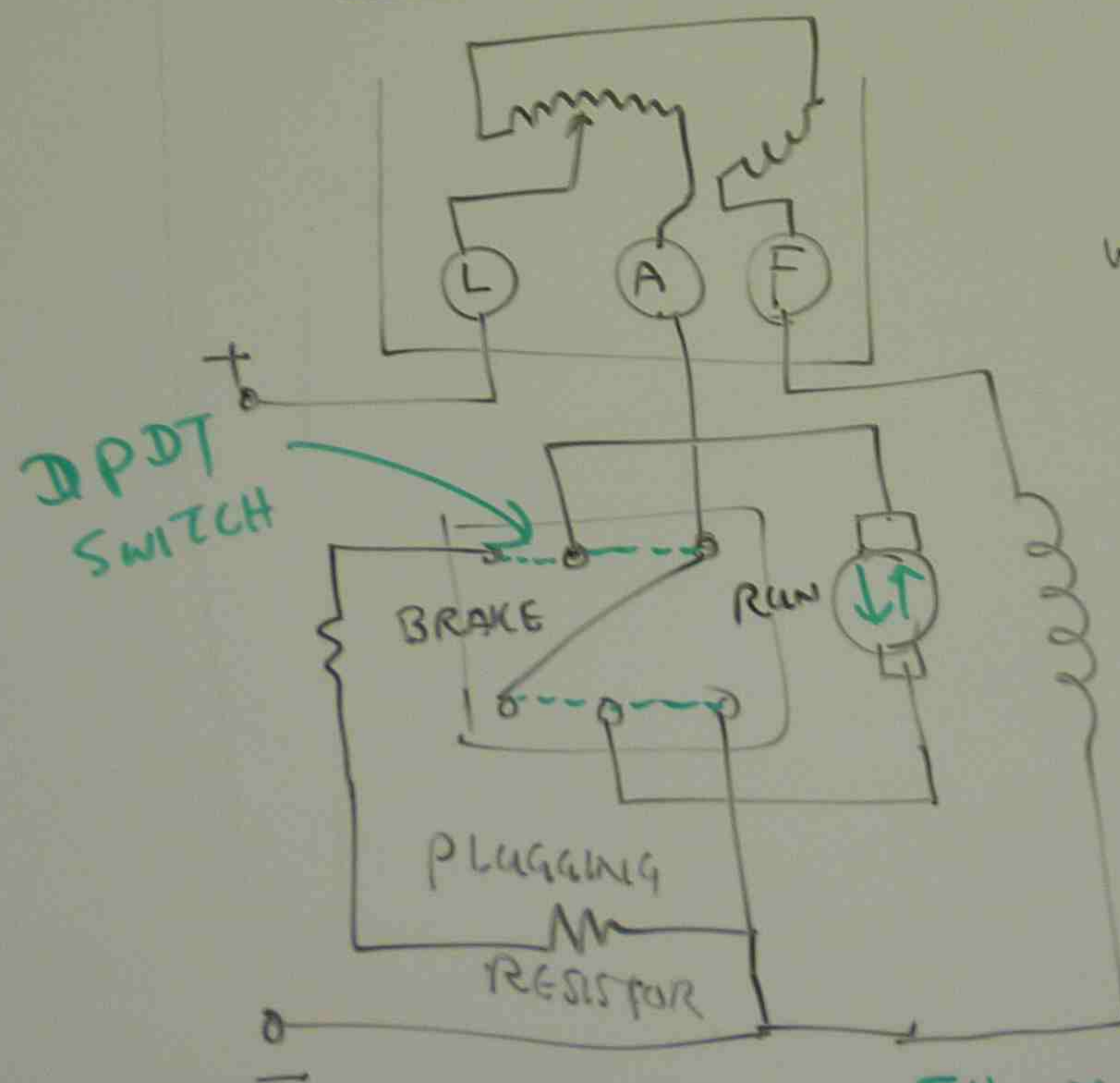

WHEN THE STOP SWITCH IS PRESSED, MOTOR TERMINAL CONNECTION IS REVERSED. REVERSED SUPPLY CANCELS THE MOTOR ROTATIONAL INERTIA AND MOTOR IS STOPPED IMMEDIATELY. THEN MOTOR IS CUT OFF FROM SUPPLY.

BRAKING B

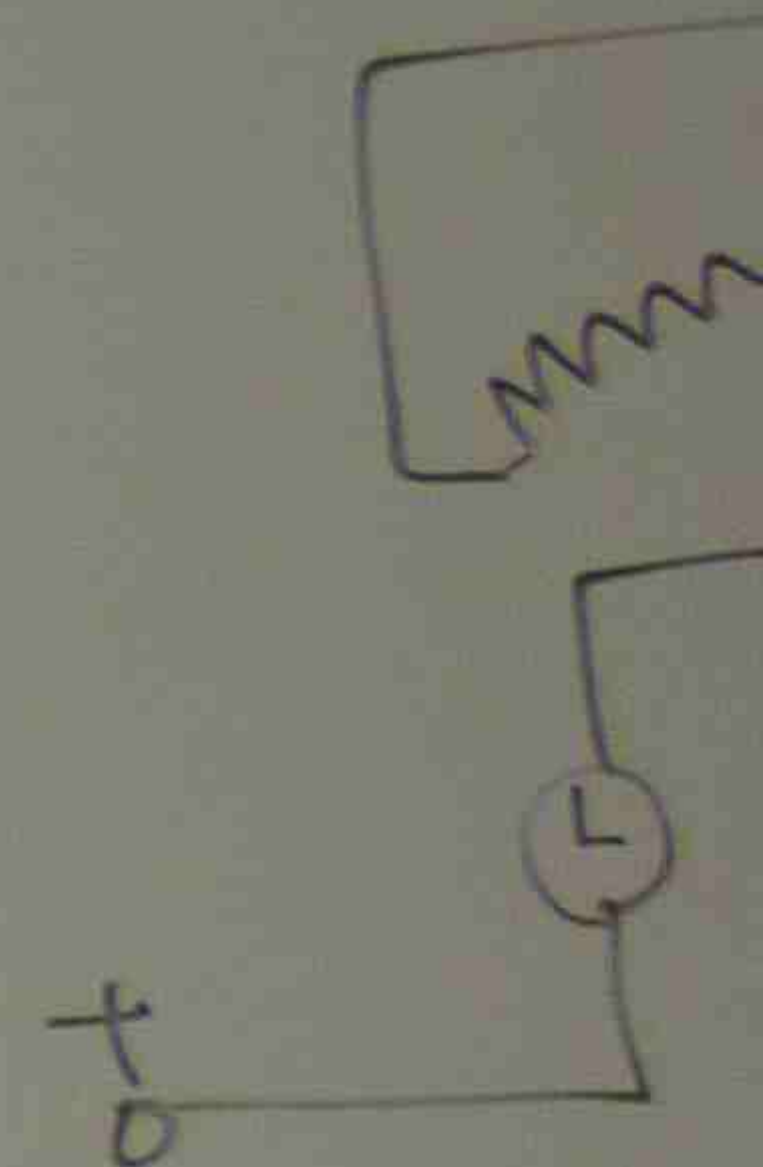


WHEN STOP IS CONNECTED RESISTOR IS DISCONNECTED FROM MOTOR

MECHANICAL
BRAKE

WHEN THE STOP SWITCH IS
PRESSED, MOTOR TERMINAL
CONNECTION IS REVERSED.
REVERSED SUPPLY CANCELS
THE MOTOR ROTATIONAL
INERTIA AND MOTOR IS
STOPPED IMMEDIATELY.

THEN MOTOR IS CUT OFF
FROM SUPPLY.

BRAKING BY DYNAMIC BRAKING

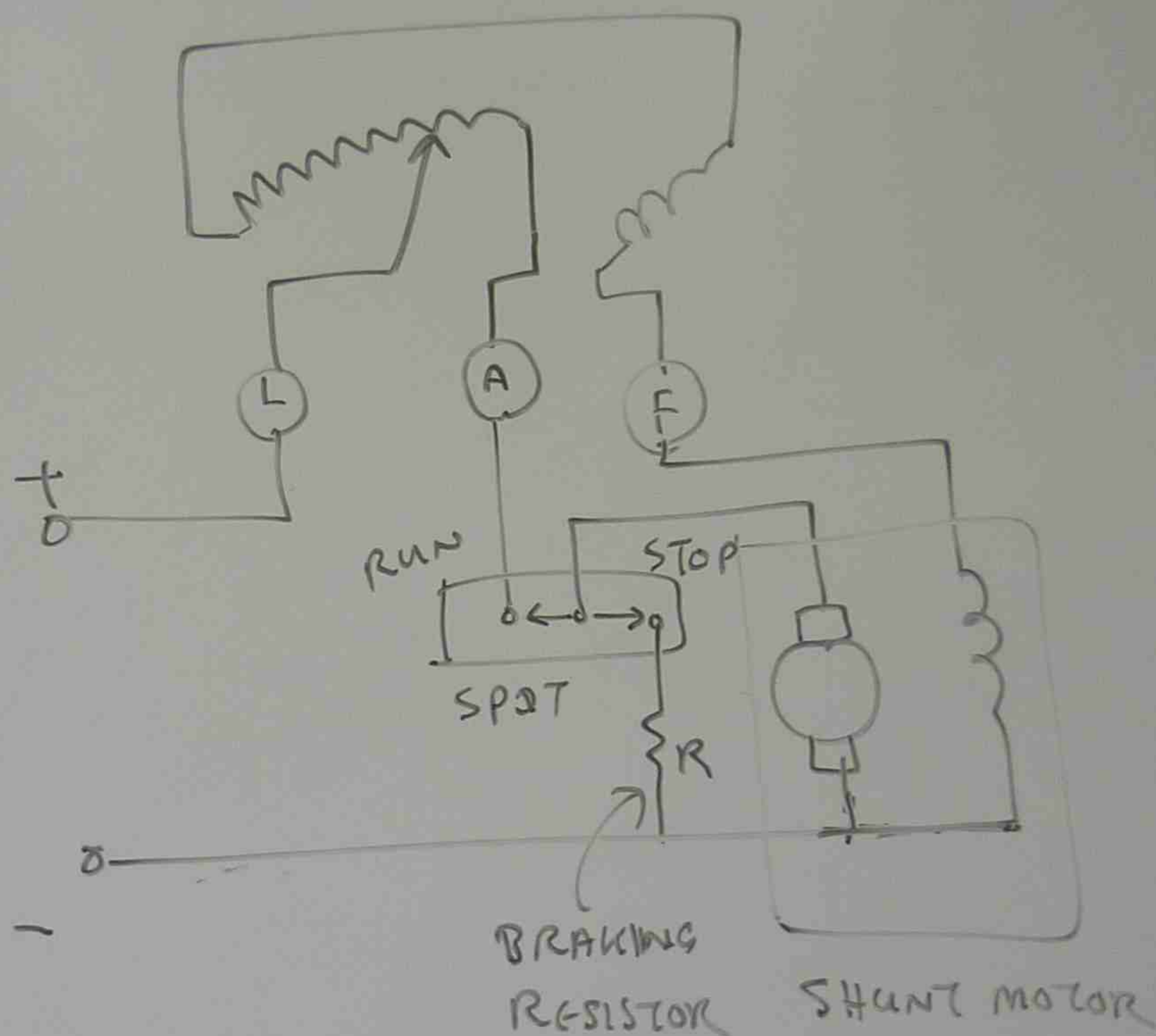

WHEN STOP BUTTON IS PRESSED, MOTOR TERMINAL
IS CONNECTED TO EXTERNAL DYNAMIC BRAKING
RESISTOR. THE STORED ENERGY IN MOTOR ARMATURE
IS DISSIPATED IN DYNAMIC BRAKING RESISTOR AND
MOTOR IS STOPPED.