

**St Clements University-Higher Education School-Niue**

**Highlight Computer Group-IQY Technical College**

**BAE 408 Analogue & Digital Electronics Test**

**Each 10 marks , Total 100 marks**

- Q1. Sketch & explain switching regulator supply.
- Q2. Sketch & explain CMOS logic.
- Q3. Explain choke input filter & capacitor input filter with circuit.
- Q4. Explain the principle of modulation.
- Q5. Explain the pulse code modulation.
- Q6. Explain integrator/ differentiator & limiter.
- Q7. Explain flip flop
- Q8. Describe J-K Flip flop
- Q9. describe application of SCR.
- Q10. Explain shift registrar.