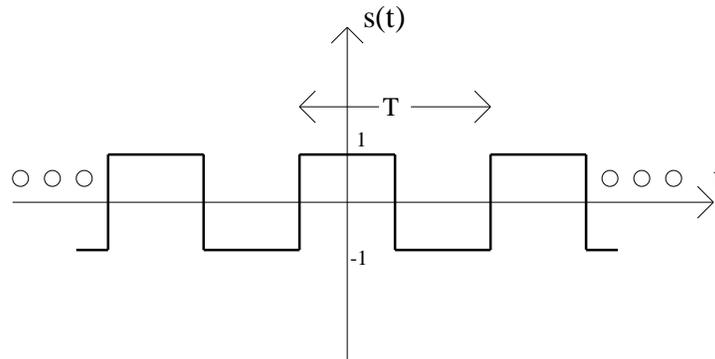


MIXERS

13.1 SINGLE-ENDED MIXERS AND BASIC THEORY




$$s(t) = \frac{2}{jP} \sum_{n=\pm\text{odd}} \frac{1}{n} e^{jn\omega_o t} \quad \text{and} \quad S(\omega) = -4j \sum_{n=\pm\text{odd}} \frac{1}{n} \mathbf{d}(\omega - n\omega_o)$$


$$\text{where } \omega_o = \frac{2P}{T}$$

$\mathbf{d}(\omega) = 2P\mathbf{d}(f)$ and $\mathbf{d}(\omega - \omega_o) = 2P\mathbf{d}(f - f_o)$ as can be seen since
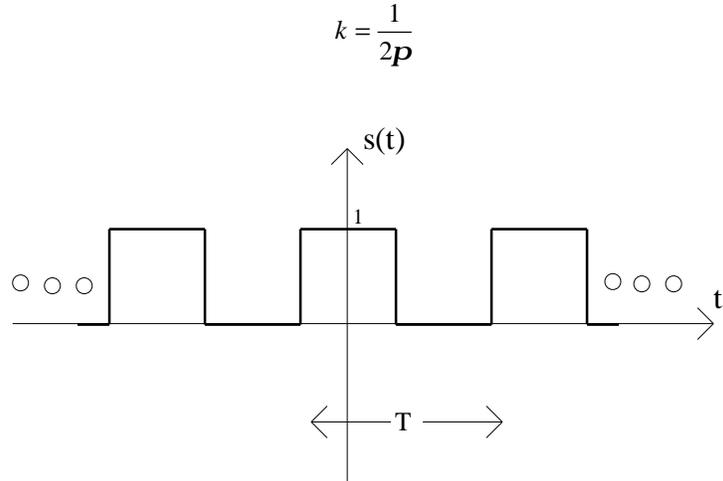
$$\begin{aligned} \int_{-\infty}^{+\infty} \mathbf{d}(\omega) d\omega &= 1 \\ \int_{-\infty}^{+\infty} \mathbf{d}(2P f) 2P df &= 1 \\ \int_{-\infty}^{+\infty} k \mathbf{d}(f) 2P df &= 1 \\ k \int_{-\infty}^{+\infty} \mathbf{d}(f) df &= \frac{1}{2P} \end{aligned}$$


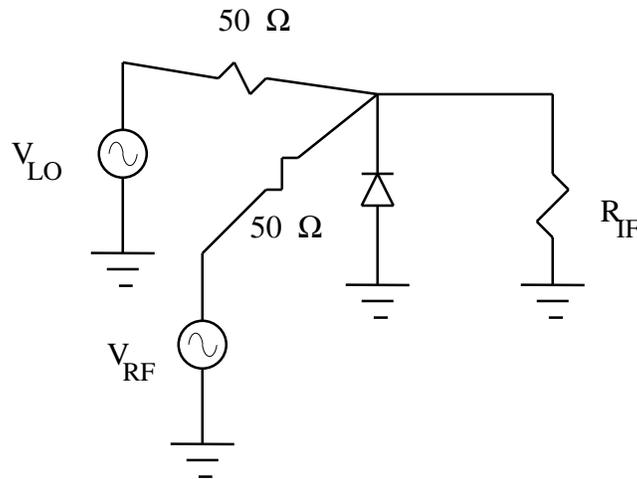
$$s(t) = \frac{1}{2} + \frac{1}{jP} \sum_{n=\pm odd} \frac{1}{n} e^{jn\omega_o t} \quad \text{and} \quad S(\omega) = p\mathbf{d}(\omega) - 2j \sum_{n=\pm odd} \frac{1}{n} \mathbf{d}(\omega - n\omega_o)$$




Single Ended Mixer (One Diode)

Assuming ideal diodes (open or short circuit) and assuming that the local oscillator controls the state of the diodes then

$$v_{LO}(t) = \frac{2V_{LO}}{jP} \sum_{n=\pm odd} \frac{1}{n} e^{jn\omega_o t} \quad \text{and} \quad V_{LO}(\omega) = -4jV_{LO} \sum_{n=\pm odd} \frac{1}{n} \mathbf{d}(\omega - n\omega_o)$$

If
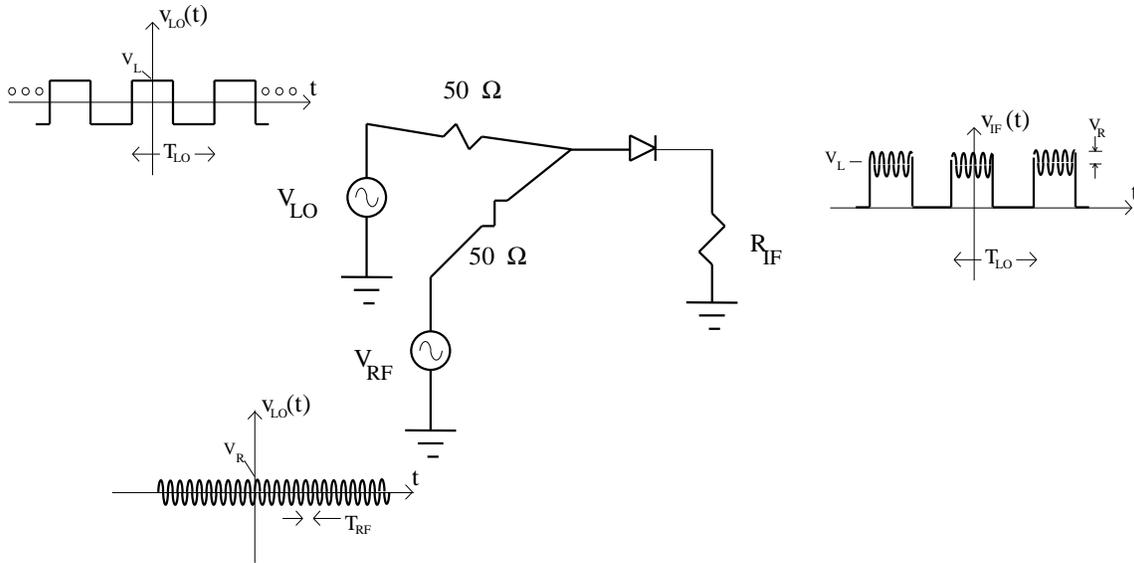
$$v_{RF}(t) = V_R \cos \omega_R t = \frac{V_R}{2} (e^{+j\omega_R t} + e^{-j\omega_R t})$$



$$v_{IF}(t) = [V_{LO} + v_{RF}(t)] \cdot s(t) = \left[V_{LO} + \frac{V_R}{2} (e^{+j\omega_R t} + e^{-j\omega_R t}) \right] \cdot \left[\frac{1}{2} + \frac{1}{jP} \sum_{n=\pm\text{odd}} \frac{1}{n} e^{jn\omega_L t} \right]$$

$$= V_{LO} \left[\frac{1}{2} + \frac{1}{jP} \sum_{n=\pm\text{odd}} \frac{1}{n} e^{jn\omega_L t} \right] + \frac{V_R}{2} (e^{+j\omega_R t} + e^{-j\omega_R t}) \left[\frac{1}{2} + \frac{1}{jP} \sum_{n=\pm\text{odd}} \frac{1}{n} e^{jn\omega_L t} \right]$$

$$v_{IF}(t) = \frac{V_{LO}}{2} + \frac{V_{LO}}{jP} \sum_{n=\pm\text{odd}} \frac{1}{n} e^{jn\omega_L t} + \frac{V_R}{4} (e^{+j\omega_R t} + e^{-j\omega_R t}) + \frac{V_R}{j2P} (e^{+j\omega_R t} + e^{-j\omega_R t}) \sum_{n=\pm\text{odd}} \frac{1}{n} e^{jn\omega_L t}$$

$$= \frac{V_{LO}}{2} + \frac{V_{LO}}{jP} \sum_{n=\pm\text{odd}} \frac{1}{n} e^{jn\omega_L t} + \frac{V_R}{4} (e^{+j\omega_R t} + e^{-j\omega_R t}) + \frac{V_R}{j2P} e^{+j\omega_R t} \sum_{n=\pm\text{odd}} \frac{1}{n} e^{jn\omega_L t} + \frac{V_R}{j2P} e^{-j\omega_R t} \sum_{n=\pm\text{odd}} \frac{1}{n} e^{jn\omega_L t}$$

$$= \frac{V_{LO}}{2} + \frac{V_{LO}}{jP} \sum_{n=\pm\text{odd}} \frac{1}{n} e^{jn\omega_L t} + \frac{V_R}{4} (e^{+j\omega_R t} + e^{-j\omega_R t}) + \frac{V_R}{j2P} \sum_{n=\pm\text{odd}} \frac{1}{n} e^{j(\omega_R + n\omega_L)t} + \frac{V_R}{j2P} \sum_{n=\pm\text{odd}} \frac{1}{n} e^{j(n\omega_L - \omega_R)t}$$

$$V_{IF}(\omega) = \text{--- Fix ---} \frac{V_{LO}}{2} + \frac{V_{LO}}{jP} \sum_{n=\pm\text{odd}} \frac{1}{n} e^{jn\omega_L t} + \frac{V_R}{4} (e^{+j\omega_R t} + e^{-j\omega_R t}) + \frac{V_R}{j2P} \sum_{n=\pm\text{odd}} \frac{1}{n} e^{j(\omega_R + n\omega_L)t} + \frac{V_R}{j2P} \sum_{n=\pm\text{odd}} \frac{1}{n} e^{j(n\omega_L - \omega_R)t}$$

```

function mixer2()
% to illustrate mixer as a switching action
% where LO close to RF in frequency
%units
ns=1e-9; GHz=1e9;
fRF=10*GHz; wRF=2*pi*fRF;
Fpts=[1:451];
dBlimit=-65;
Tpts=[1:200];
fLO=9*GHz; wLO=2*pi*fLO;
deltat=.004*ns;
t=[0:1999]*deltat;
Nt=length(t);
RF=1*sin(wRF*t);
%plot(t/ns,RF);
psRF=abs(fft(RF.*hanning(Nt))*2/Nt);
psRF(1)=psRF(1)/2;
psRFdB=20*log10(psRF);A=find(psRFdB<dBlimit);
psRFdB(A)=dBlimit*ones(size(A));
FREQ=(1/max(t))*[0:Nt-1]/GHz;

figure; plot(FREQ(Fpts),psRFdB(Fpts))
axis([0,max(FREQ(Fpts)),dBlimit, 0])
ylabel('dB');xlabel('Frequency (GHz)')
title('Power Spectrum of RF signal')

LO=sin(wLO*t);% LO=2*(LO>=0)-1;

psLO=abs(fft(LO.*hanning(Nt))*2/Nt);
psLO(1)=psLO(1)/2;
psLOdB=20*log10(psLO);A=find(psLOdB<dBlimit);
psLOdB(A)=dBlimit*ones(size(A));

figure; plot(FREQ(Fpts),psLOdB(Fpts))
axis([0,max(FREQ(Fpts)),dBlimit, 0])
ylabel('dB');xlabel('Frequency (GHz)')
title('Power Spectrum of LO signal')

Combine=RF+LO;
IFt=Combine.*(Combine>0);
figure; plot(Tpts*deltat/ns,IFt(Tpts))
ylabel('volts');Xlabel('Time (nsec)')
title('IF time domain signal')

psIF=abs(fft(IFt.*hanning(Nt))*2/Nt);
psIF(1)=psIF(1)/2;
psIFdB=20*log10(psIF);A=find(psIFdB<dBlimit);
psIFdB(A)=dBlimit*ones(size(A));

figure; plot(FREQ(Fpts),psIFdB(Fpts))
axis([0,max(FREQ(Fpts)),dBlimit, 0])
ylabel('dB');xlabel('Frequency (GHz)')
title('Power Spectrum of IF signal')

RFp=RF.*(LO>0);
figure; plot(Tpts*deltat/ns,RFp(Tpts))
ylabel('volts');Xlabel('Time (nsec)')
title('RFp time domain signal')

psRFp=abs(fft(RFp.*hanning(Nt))*2/Nt);
psRFp(1)=psRFp(1)/2;
psRFpdB=20*log10(psRFp);A=find(psRFpdB<dBlimit);
psRFpdB(A)=dBlimit*ones(size(A));

figure; plot(FREQ(Fpts),psRFpdB(Fpts))
axis([0,max(FREQ(Fpts)),dBlimit, 0])
ylabel('dB');xlabel('Frequency (GHz)')
title('Power Spectrum of Pulsed RF signal')

```

```

LOp=LO.*(LO>0);
figure; plot(Tpts*deltat/ns,LOp(Tpts))
ylabel('volts');Xlabel('Time (nsec)')
title('LOp time domain signal')

psLOp=abs(fft(LOp.*hanning(Nt))*2/Nt);
psLOp(1)=psLOp(1)/2;
psLOpdB=20*log10(psLOp);A=find(psLOpdB<dBlimit);
psLOpdB(A)=dBlimit*ones(size(A));

figure; plot(FREQ(Fpts),psLOpdB(Fpts))
axis([0,max(FREQ(Fpts)),dBlimit, 0])
ylabel('dB');xlabel('Frequency (GHz)')
title('Power Spectrum of Pulsed LO signal')

RFsw=RF.*(LO>0)-RF.*(LO<0);
figure; plot(Tpts*deltat/ns,RFsw(Tpts))
ylabel('volts');Xlabel('Time (nsec)')
title('RFsw time domain signal')

psRFsw=abs(fft(RFsw.*hanning(Nt))*2/Nt);
psRFsw(1)=psRFsw(1)/2;
psRFswdB=20*log10(psRFsw);A=find(psRFswdB<dBlimit);
psRFswdB(A)=dBlimit*ones(size(A));

figure; plot(FREQ(Fpts),psRFswdB(Fpts))
axis([0,max(FREQ(Fpts)),dBlimit, 0])
ylabel('dB');xlabel('Frequency (GHz)')
title('Power Spectrum of PSK RF signal')

```

