

$$i_n(\omega t) = \frac{\sqrt{2} V_0}{(R^2 + X^2)^{1/2}} \sin(\omega t - \phi) \quad (0 < \omega t < \beta)$$

$$X = -\frac{1}{\omega C} \quad \tau = RC$$

$$i_r(\omega t) = -i_c(\omega t) = i_r(\beta) e^{-t/\tau} \quad (\beta < \omega t < \gamma)$$

$$i_r(\beta) = \frac{\sqrt{2} V_0 \sin \beta}{R}$$

$$V_n = V_0 \quad (0 < \omega t < \beta)$$

$$V_n = i_r(\omega t) R \quad (\beta < \omega t < \gamma)$$

$$V_n = 0 \quad (\gamma < \omega t < 2\pi)$$

$$V_n = \frac{3\sqrt{2}}{\pi} V_0 \cdot 0.866 \cos \alpha \quad (0 < \alpha < \frac{\pi}{6})$$

$$V_n = \frac{3\sqrt{2}}{\pi} V_0 [0.5 \cos(\alpha + \frac{\pi}{6}) + 0.5] \quad (\frac{\pi}{6} < \alpha < \frac{\pi}{2})$$


for 3φ full wave rectifier ckt,

$$V_n = \frac{-6}{\sqrt{2} \pi} V_0 \cos \omega t \Big|_{\alpha_1}^{\alpha_2}$$

$$V_n = \frac{-6}{\sqrt{2} \pi} V_0 \cos \omega t \Big|_{\frac{\pi}{3}}^{\frac{5\pi}{3}} = 1.35 V_0$$

$$V_n = \frac{6}{\sqrt{2} \pi} V_0 \cos \alpha \quad (0 < \alpha < \frac{\pi}{3})$$

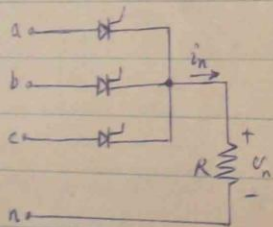3-3 Three phase rectifier resistance load



3φ half wave rectifier ckt

$$V_n = \frac{3}{2\pi} \int_{\alpha_1}^{\alpha_2} \sqrt{2} V_0 \sin \omega t \, d(\omega t)$$

$$= \frac{-3}{\sqrt{2} \pi} [V_0 \cos \omega t]_{\frac{\pi}{6}}^{\frac{5\pi}{6}} = 1.17 V_0$$