

The equivalent circuit can be redrawn as in Figure 17-4 (b). The impedance  $Z_d$  is drawn as a capacitive impedance, because that is what is in the important case of a capacitor motor. The current in this impedance is

$$I_{mf} - I_{mb} = -jaI_a \quad \dots (17-30)$$

Equations 17-27 and 17-28 and the equivalent circuit of Figure 17-4 are applicable to a wide variety of induction-motor types. For example, if the stator-circuit impedances are equal when referred to the same winding then  $Z_d = 0$  and the forward and backward fields are independent of one another; this special case is exactly like that of the symmetrical motor. If  $Z_d = 0$  and if the referred voltages form a balanced 2-phase system of positive sequence, then Figure 17-4 (b) reduces to the equivalent for balanced operation. If winding a is open, then  $Z_d$  is an open circuit; this is the special case of single-phase operation. For this special case  $I_a = 0$ , and Equations 17-11 and 17-12 become

$$I_{mf} = I_{mb} = \frac{1}{2} I_m$$

The equivalent circuit then reduces to  $V_m$  applied to the combination of  $2Z_{1m}$  in series with the forward-and backward-field impedances. Division of the impedances by 2 gives the equivalent circuit of Figure 17-5.

Figure 17-5. Equivalent circuits for a single-phase induction motor.

Equations 17-27 and 17-28 can be solved for the currents, giving

$$I_{mf} = \frac{V_{mf}(Z_o + Z_b) + V_{mb}Z_d}{(Z_o + Z_f)(Z_o + Z_b) - Z_d^2} \quad \dots (17-31)$$

$$I_{mb} = \frac{V_{mb}(Z_o + Z_f) + V_{mf}Z_d}{(Z_o + Z_f)(Z_o + Z_b) - Z_d^2} \quad \dots (17-32)$$

The power delivered to the forward field by phase m of the stator is  $I_{mf}^2 R_f$ , and since the internal behaviour of the motor for the forward-field components is the same as that of a balanced 2-phase motor, the total power  $P_{af}$  delivered to the forward field by both phases of the stator therefore is

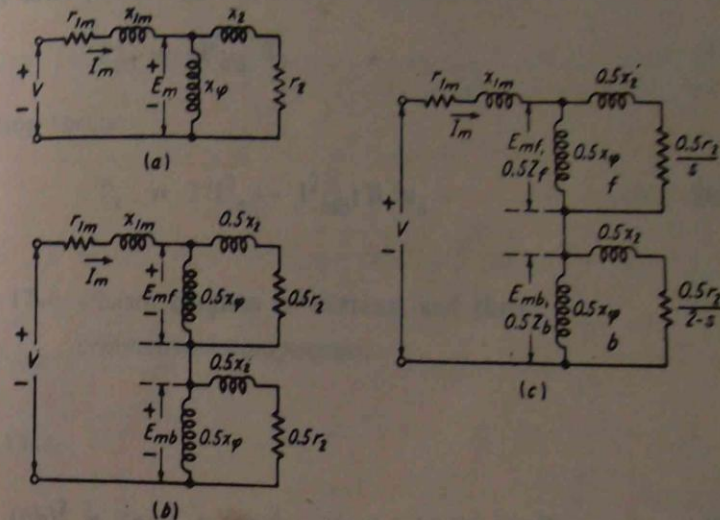


Fig. 17-5.

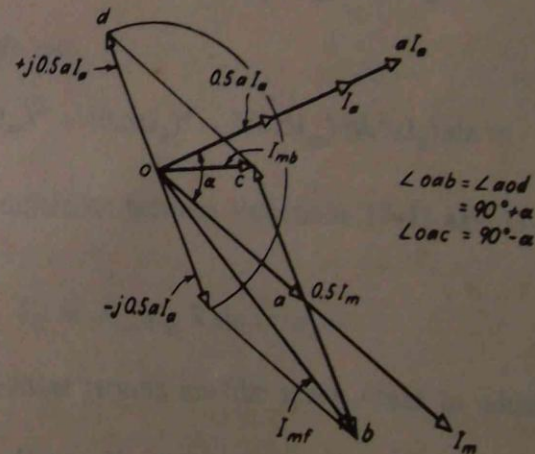


Fig. 17-6.