

Principles of chopper operation

A chopper is a thyristor on/off switch that connects ^{load} to & disconnects it from the supply & produces a chopped load voltage from a constant input supply voltage.

This process is illustrated below.

