
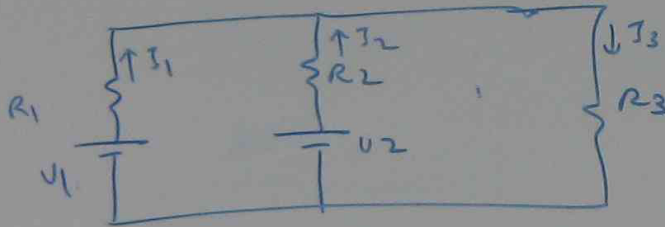


SUPER POSITION THEOREM

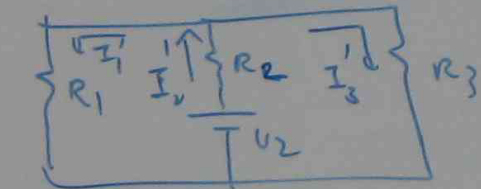THE CURRENTS FLOWS IN A CIRCUIT CAN BE DETERMINED BY KILLING THE SOURCES ALTERNATIVELY AND VECTORIALLY ADDING THE CURRENTS.



KILL V_1 , FIND I_1, I_2, I_3




$$I_2' = \frac{V_2}{\frac{R_1 \times R_3}{R_1 + R_3} + R_2}$$

$$I_1' = I_2' \times \frac{R_3}{R_1 + R_3} \quad \downarrow$$

$$I_3' = I_2' \times \frac{R_1}{R_1 + R_3} \quad \downarrow$$

KILL V_2 FIND I_1, I_2, I_3

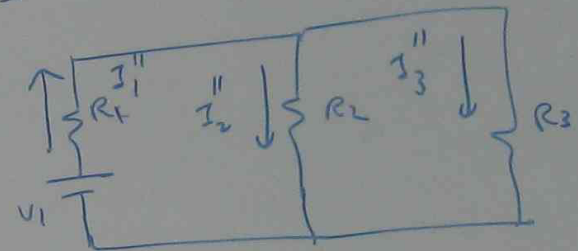

$$I_1'' = \frac{V_1}{R_1 + \frac{R_2 \times R_3}{R_2 + R_3}} \quad \uparrow$$

$$I_2'' = I_1'' \times \frac{R_3}{R_2 + R_3} \quad \downarrow$$


$$I_3'' = I_1'' \times \frac{R_2}{R_2 + R_3} \quad \downarrow$$

$$I_1 = I_1^I + I_1^{II} = I_2^I \times \frac{R_3}{R_1 + R_3} \downarrow - \frac{V_1}{R_1 + \frac{R_2 R_3}{R_2 + R_3}} \uparrow$$

$$I_2 = I_2^I + I_2^{II} = \frac{V_2}{\frac{R_1 R_3}{R_1 + R_3} + R_2} \uparrow - I_1^{II} \times \frac{R_3}{R_2 + R_3} \downarrow$$

$$I_3 = I_3^I + I_3^{II} = I_2^I \times \frac{R_1}{R_1 + R_3} \downarrow + I_1^{II} \times \frac{R_2}{R_2 + R_3} \downarrow$$

PRACTICAL (i) CONNECT THE GIVEN CIRCUIT

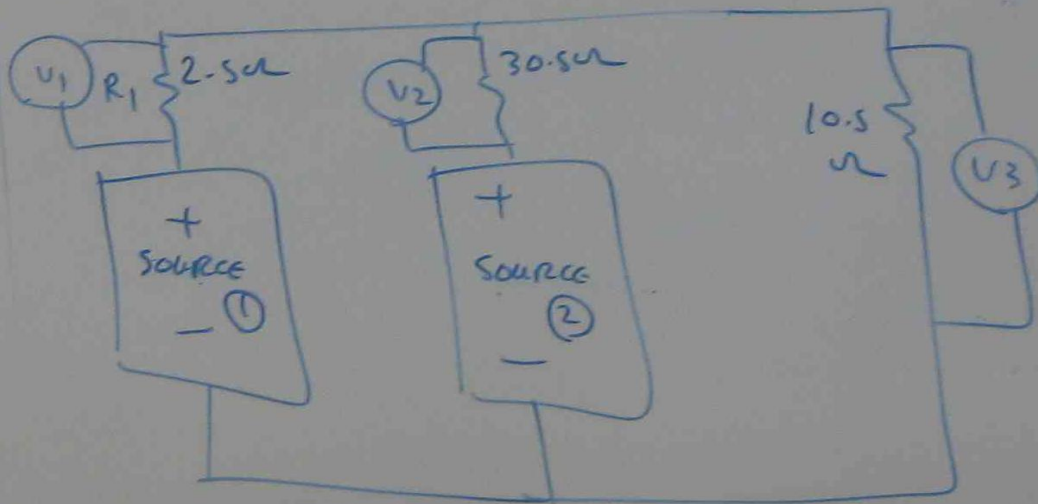

SWITCH ON SOURCE ①, TAKE V_1, V_2, V_3

V_1	$I_1 = \frac{V_1}{R_1}$	V_2	$I_2 = \frac{V_2}{R_2}$	V_3	$I_3 = \frac{V_3}{R_3}$

SWITCH OFF SOURCE ①, SWITCH ON SOURCE ②, TAKE V_1, V_2, V_3

V_1	$I_1'' = \frac{V_1}{R_1}$	V_2	$I_2'' = \frac{V_2}{R_2}$	V_3	$I_3'' = \frac{V_3}{R_3}$

THEN ADD I_1' & I_1'' , I_2' & I_2'' , I_3' & I_3''

$$I_1 = I_1' + I_1'' \quad \left| \quad I_2 = I_2' + I_2'' \quad \right| \quad I_3 = I_3' + I_3''$$

SWITCH ON BOTH SOURCE ① & ② TAKE V_1, V_2, V_3

V_1	$I_1 = \frac{V_1}{R_1}$	V_2	$I_2 = \frac{V_2}{R_2}$	V_3	$I_3 = \frac{V_3}{R_3}$

