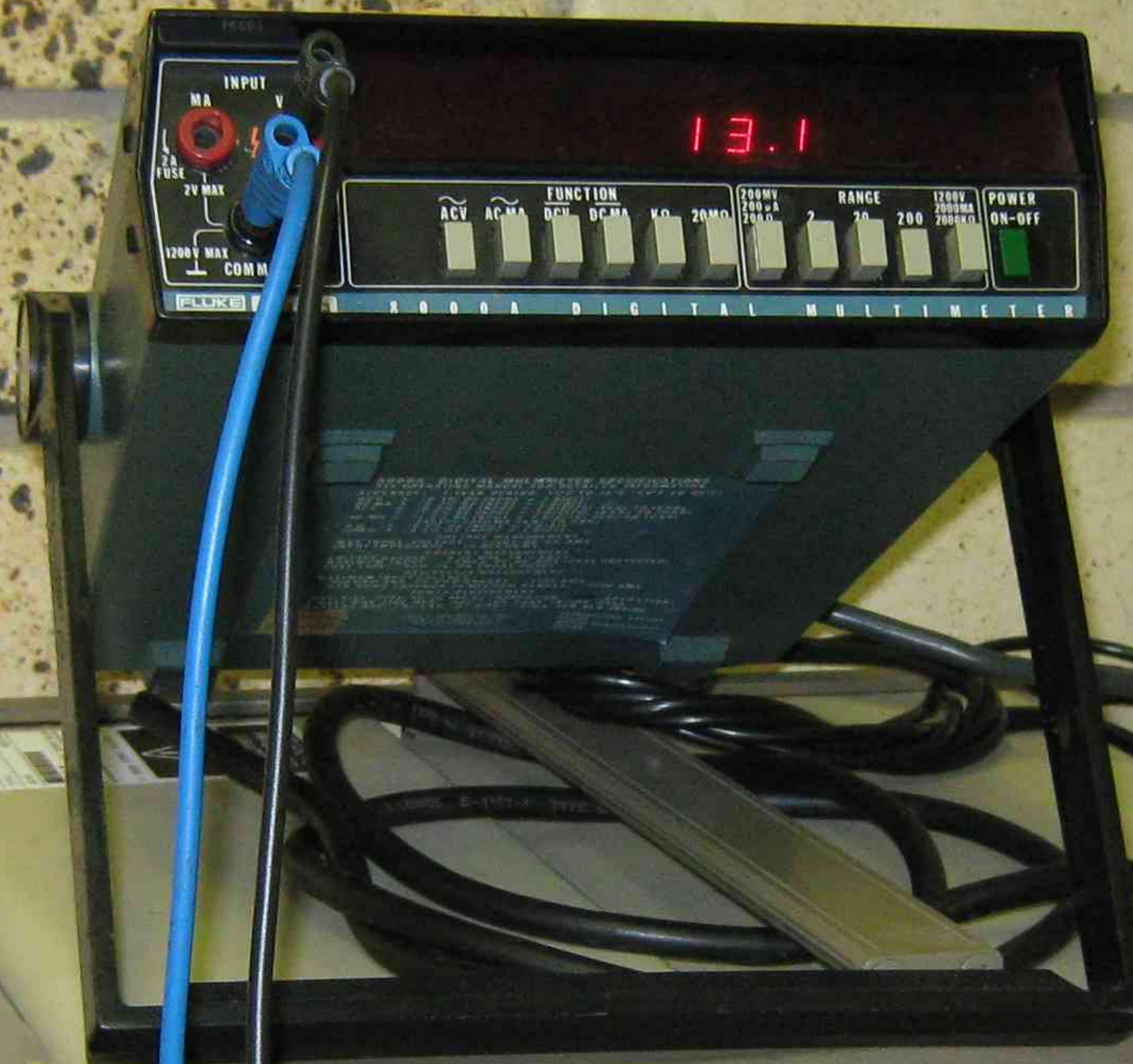


H.2.11

01.3

FUNCTION RANGE POWER
ON-OFF
ACV ACMA DCV DCMA KΩ 20MΩ 200MV 200μA 200Ω 2 20 200 1200V 2000MA 2000KΩ
8000A DIGITAL MULTIMETER

SWITCH №1



JUNK

⚡
ISOLATE
BEFORE
OPENING






Exp 31

$$HL = NI$$

\uparrow magnetic length
 \uparrow no. of turns
 \uparrow current

$$L = \frac{N^2 \mu_0 \mu_r A_c}{l}$$

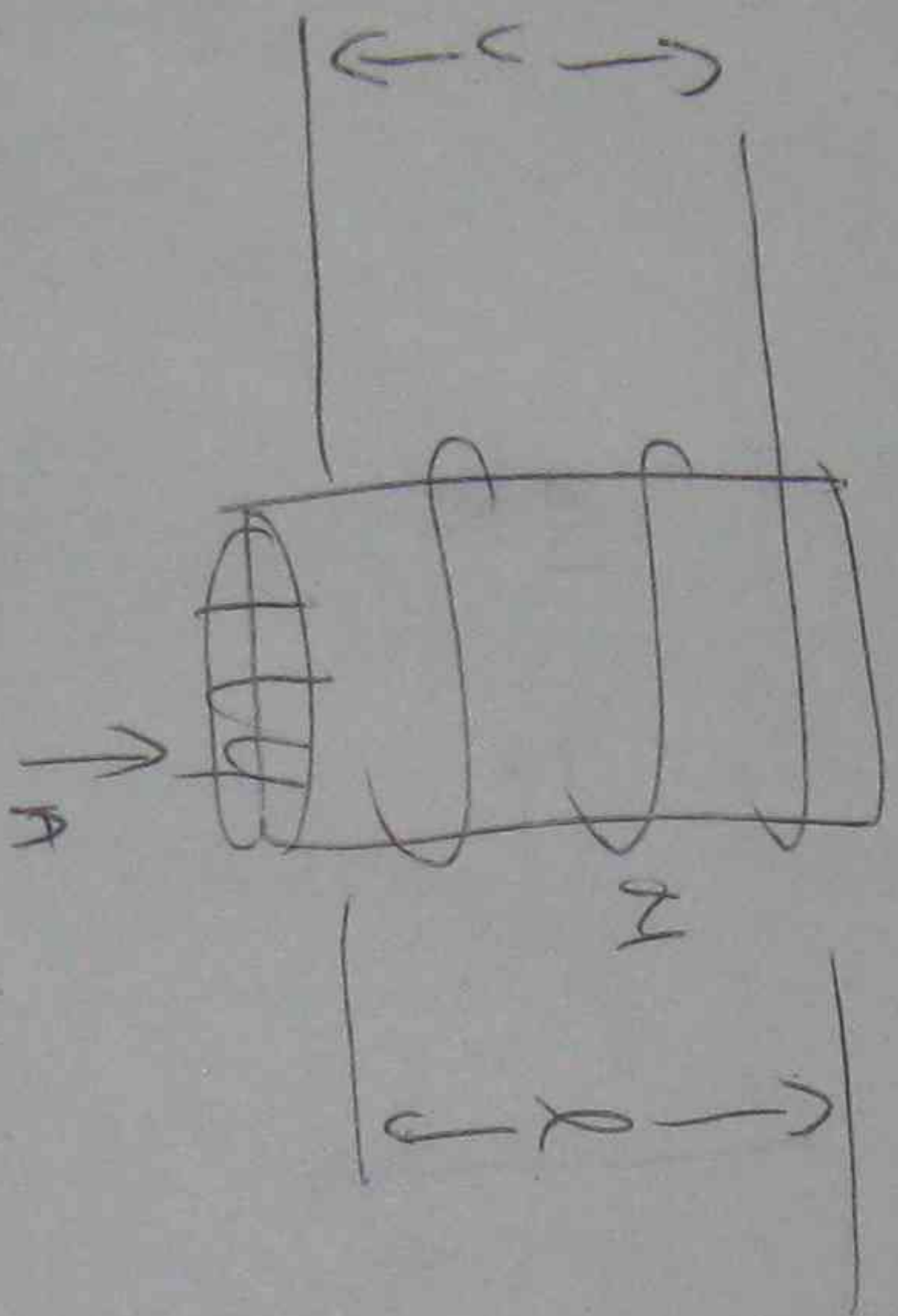
\uparrow Inductance
 \uparrow no. of turns
 \uparrow length of coil
 \uparrow μ_r core of core



$$2\pi f L = \frac{V}{I} = X_L$$

$$\omega L = \frac{V}{2\pi f I}$$

Then find μ_r constant

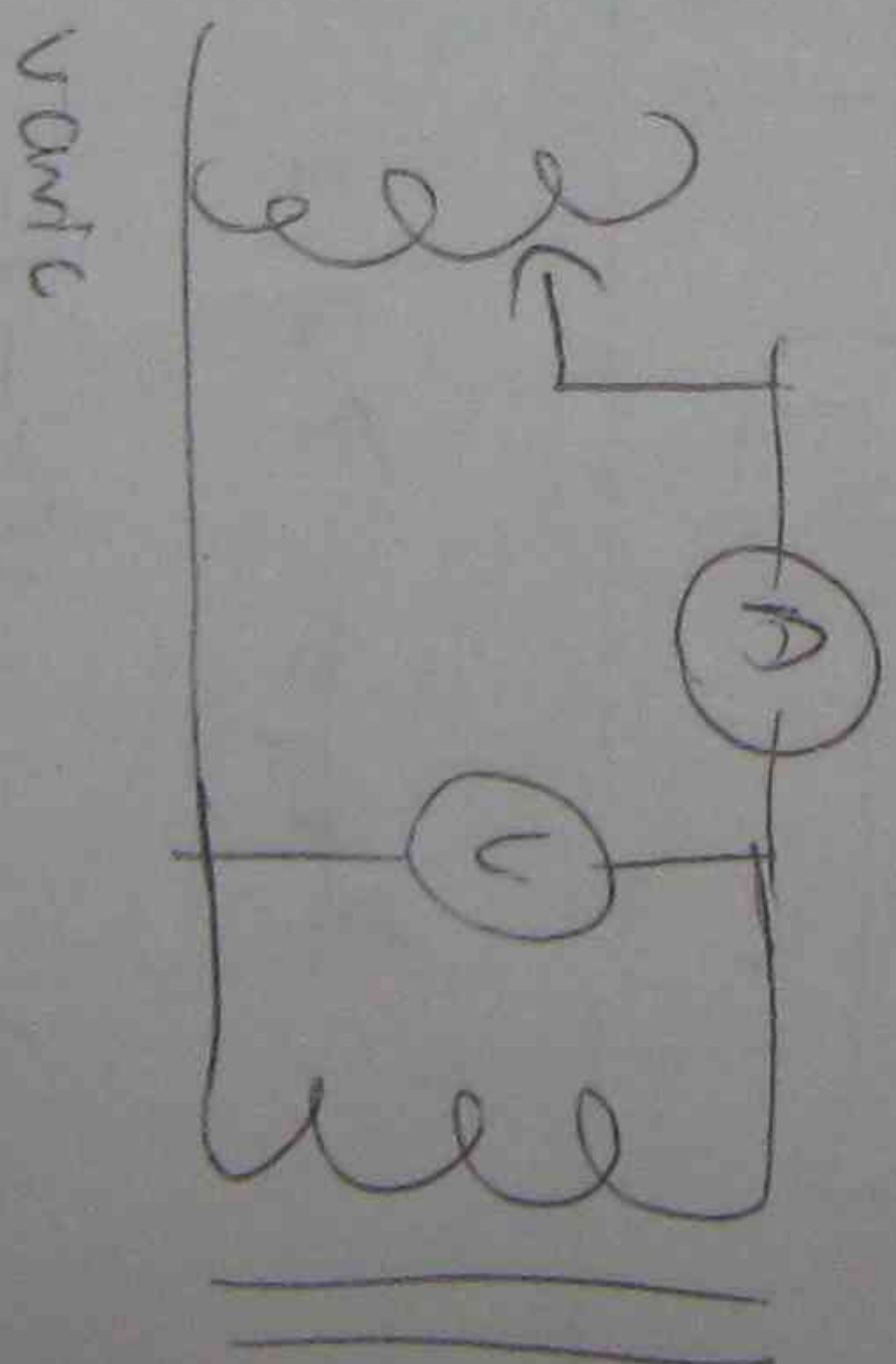



$$\mu_r = \frac{L}{\mu_0 \mu_r} = 4\pi \times 10^{-7} \mu_r$$

Power Transformer

Exp (31) Magnetic Properties of various Transformer

cores

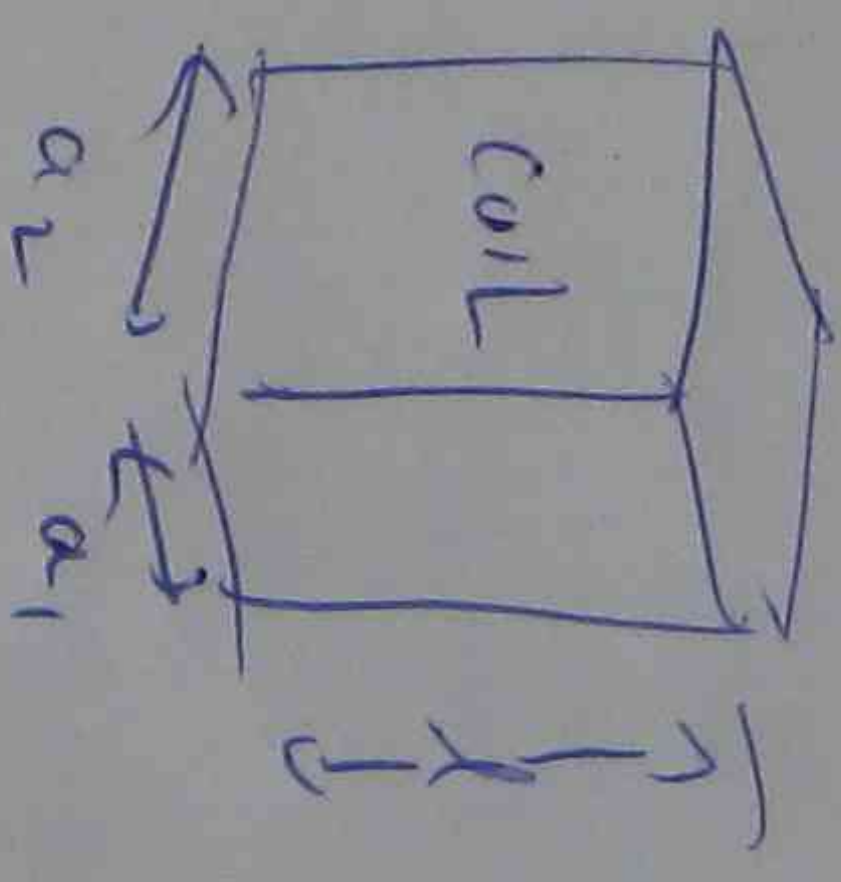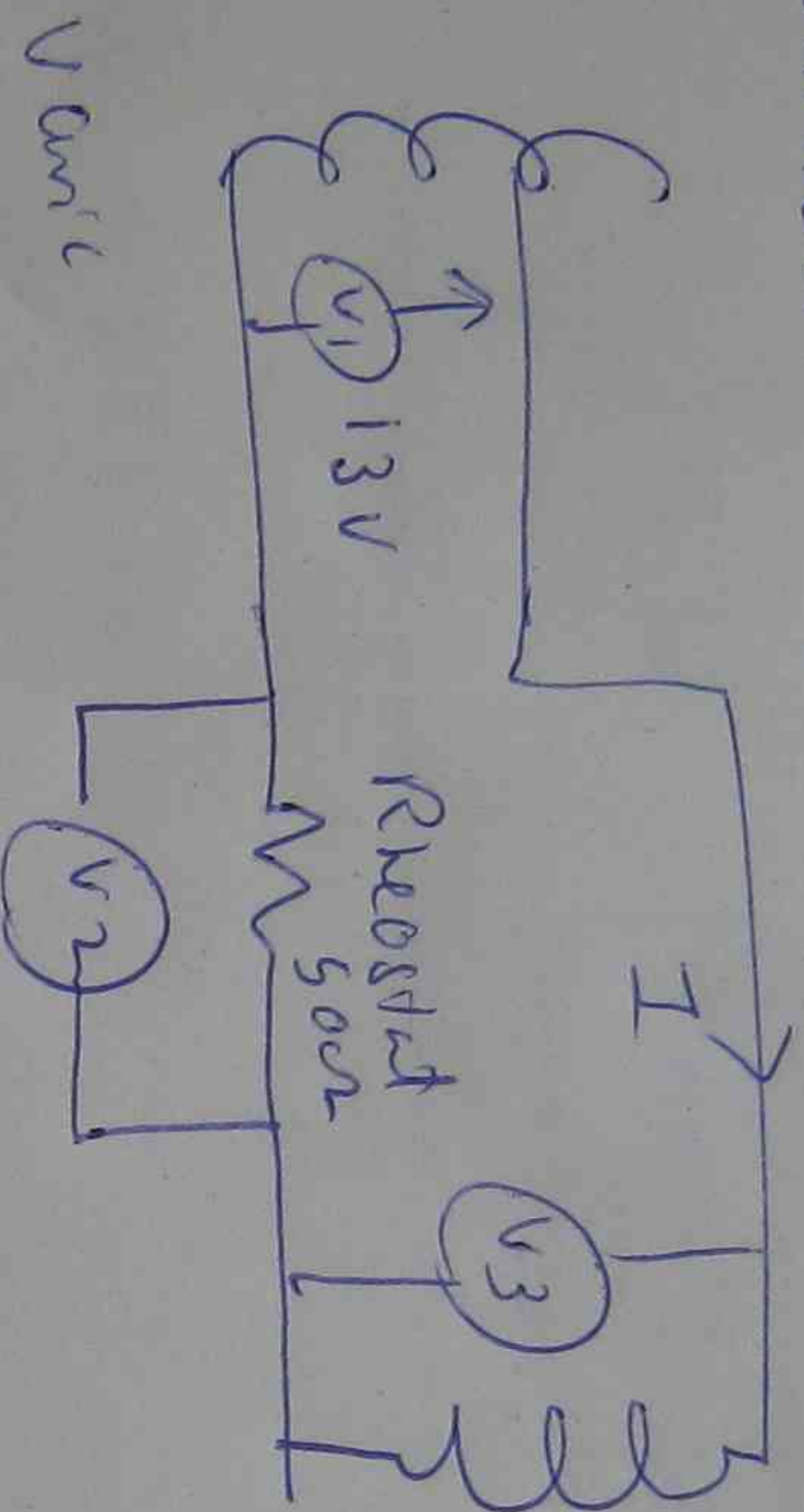- ① count no. of turns N , measure l & $A = a_1 \times a_2$
- ② connect the given circuit



Measure V_1, V_2, V_3

calculate $I = \frac{V_2}{R_{\text{rheostat}}}$

$$X = \frac{V_3}{I}$$

$$L = \frac{X}{2\pi f}$$

~~count~~ ~~attract~~

③ calculate $L = \frac{N^2 \mu A}{l}$

④

$$f = 50 \text{ Hz}$$

Substitute

$$\mu_0 = 4\pi \times 10^{-7}$$

and


calculate μ_r

Power Transformer

EP33

Properties of Series & Parallel connected coils & inductive reactance

(1) Connect the given circuit

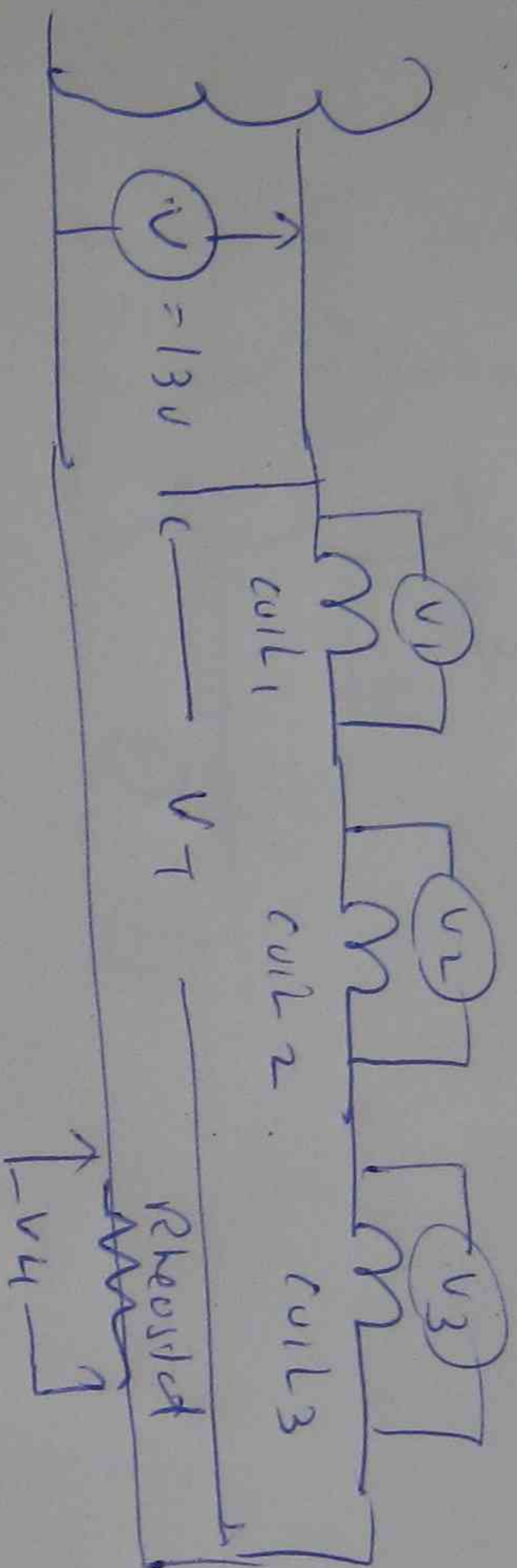

Varic

(2) measure V_1, V_2, V_3, V_4 &


(3) calculate $I = \frac{V_4}{I}$

(4) calculate $X_T = \frac{V}{I}$

(5) calculate $X_{L1} = \frac{V_1}{I}$, $X_{L2} = \frac{V_2}{I}$, $X_{L3} = \frac{V_3}{I}$

(6) compare X_T & $X_{L1} + X_{L2} + X_{L3}$

(7) connect the given circuit

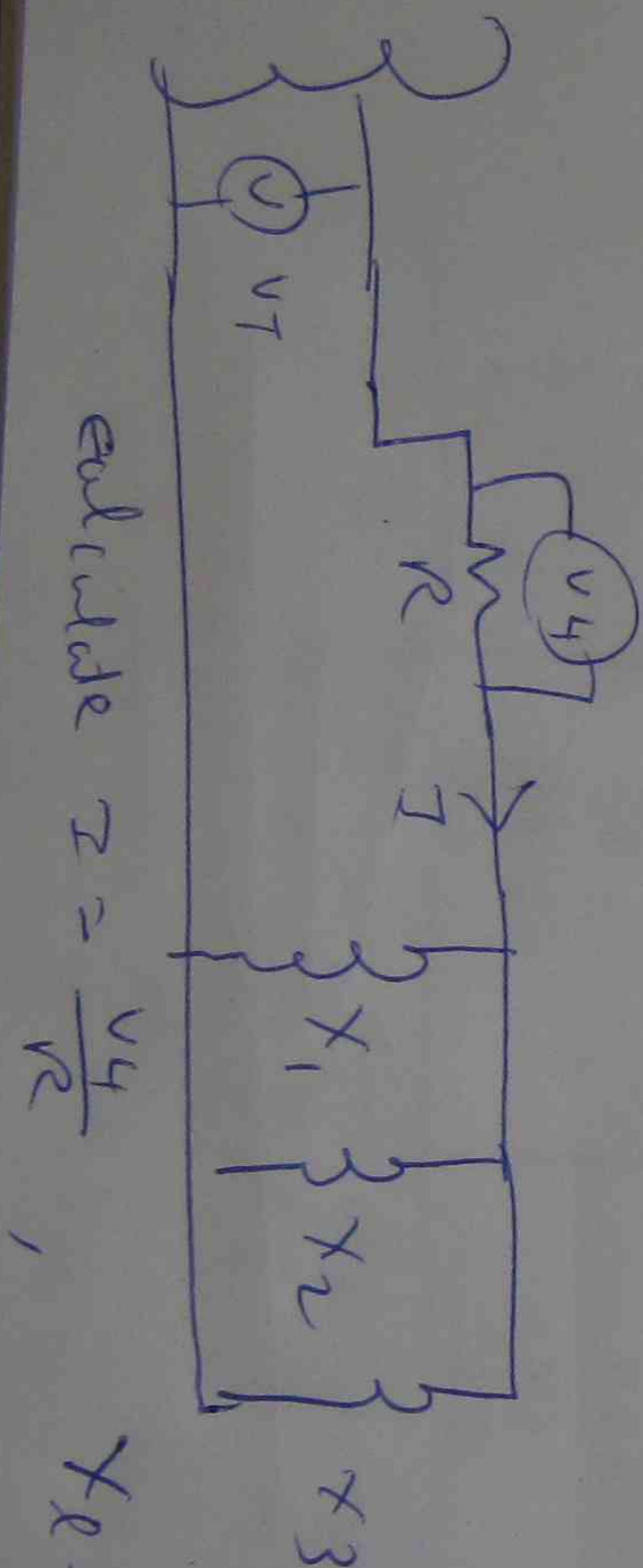

Take V_T, V_4

calculate $I = \frac{V_4}{R}$, $X_T = \frac{V_T - V_4}{I}$

RECORDED DATA (II)


Exp (31)

$$H L = N I$$

\uparrow magnetic field
 \uparrow length of solenoid
 \uparrow no. of turns
 \uparrow current

$$L = \frac{N^2 \mu_0 \mu_r A_c}{l}$$

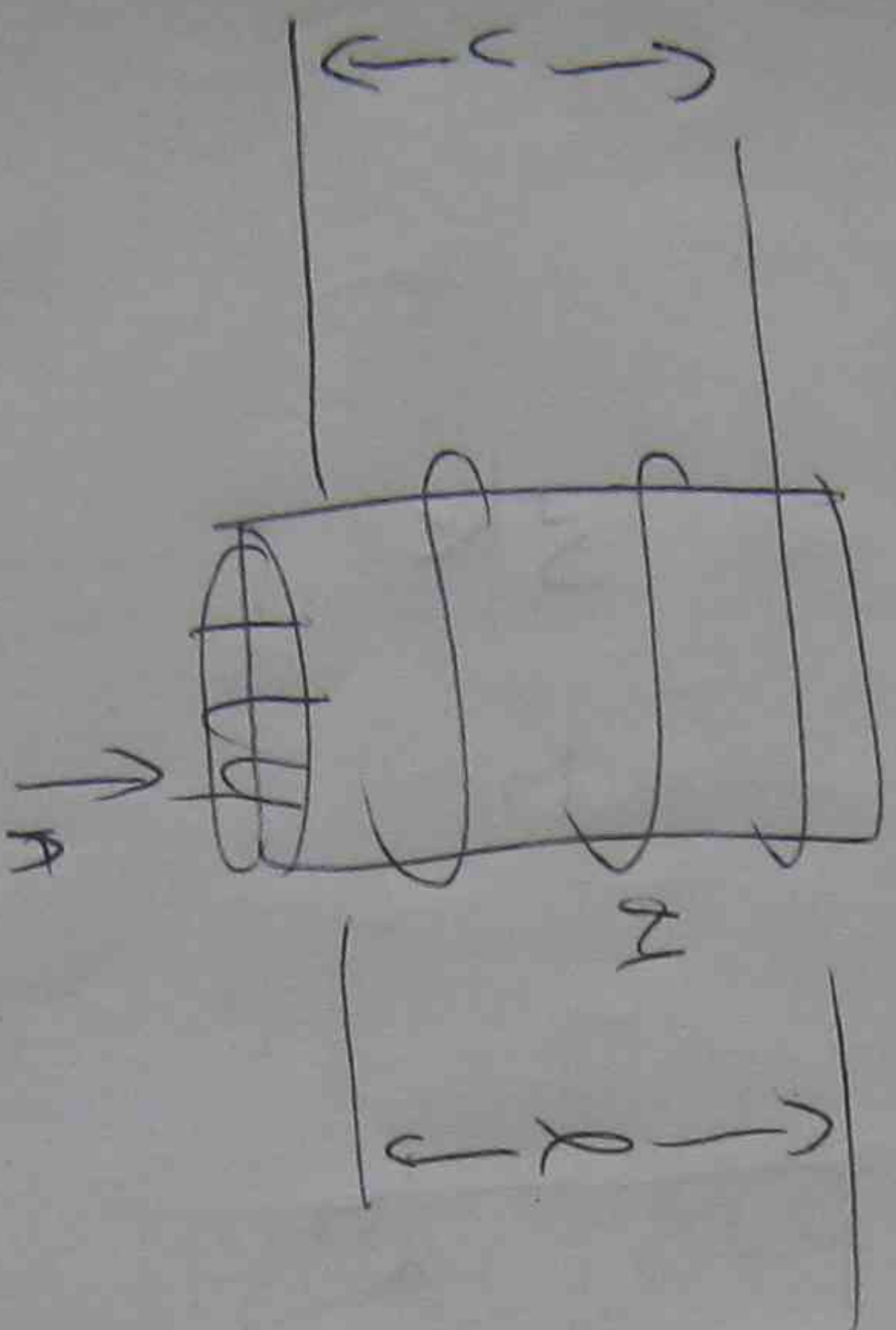
\uparrow Inductance
 \uparrow no. of turns
 \uparrow length of coil
 \uparrow area of core



$$2\pi f L = \frac{V}{I} = X_L$$

$$\therefore L = \frac{V}{2\pi f I}$$

Then find μ_r constant

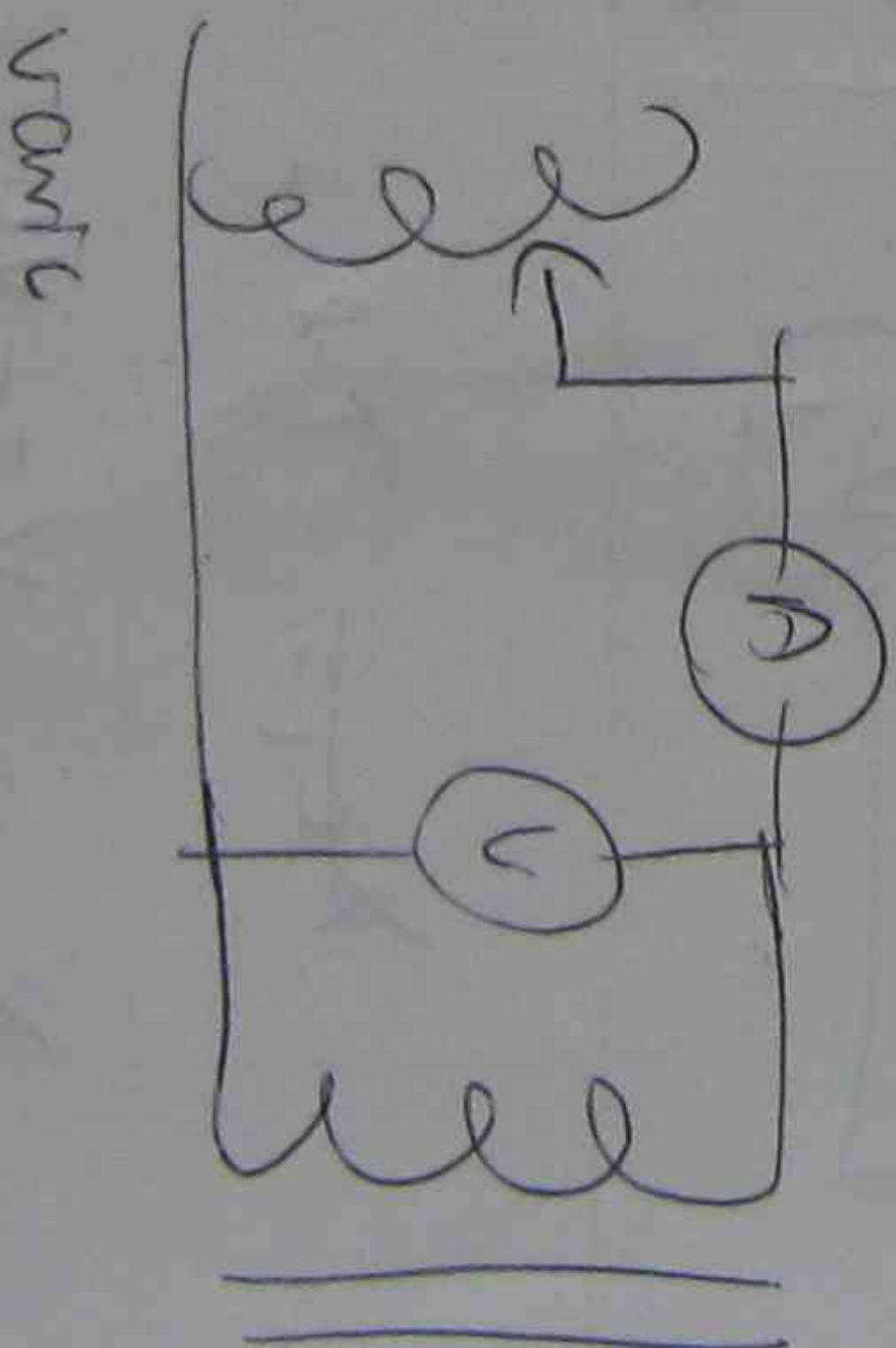

$$\mu_r = \frac{\mu}{\mu_0} = \frac{4\pi \times 10^{-7} \times f \times I \times N^2}{L}$$

Required $L = ?$


Put P_R

Put L

Calculate M

Test

Exp (33)

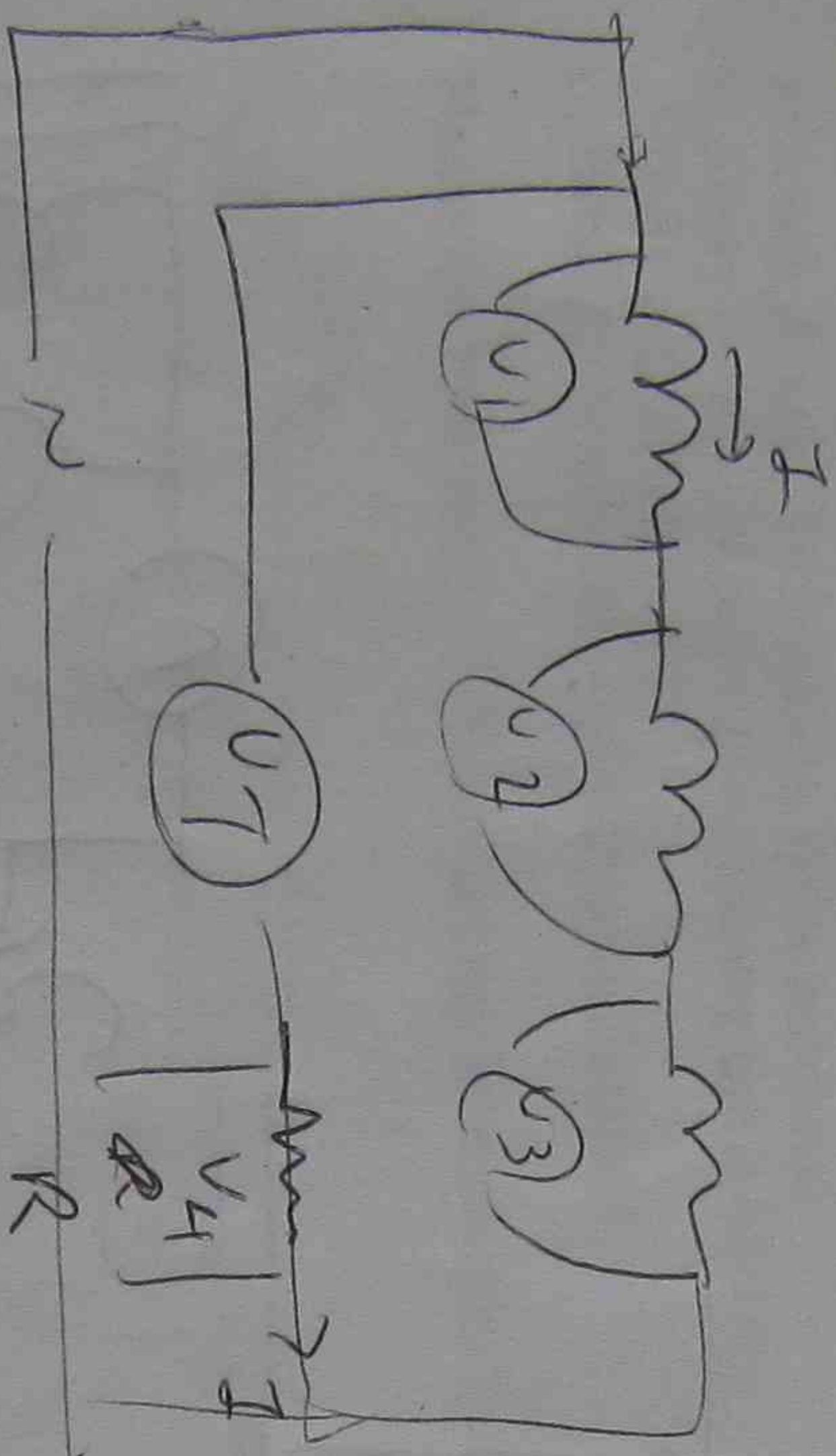

$$I = \frac{V_4}{R}$$

$$X_{L1} = X_{L2} = \frac{V_1}{I}$$


$$X_{L1} = \frac{V_2}{I}$$

$$X_{L3} = \frac{V_3}{I}$$

$$X_{L2} = \frac{V_T - V_4}{I}$$

$$X_{L1} + X_{L2} + X_{L3} = X_{LT}$$

(or)
not

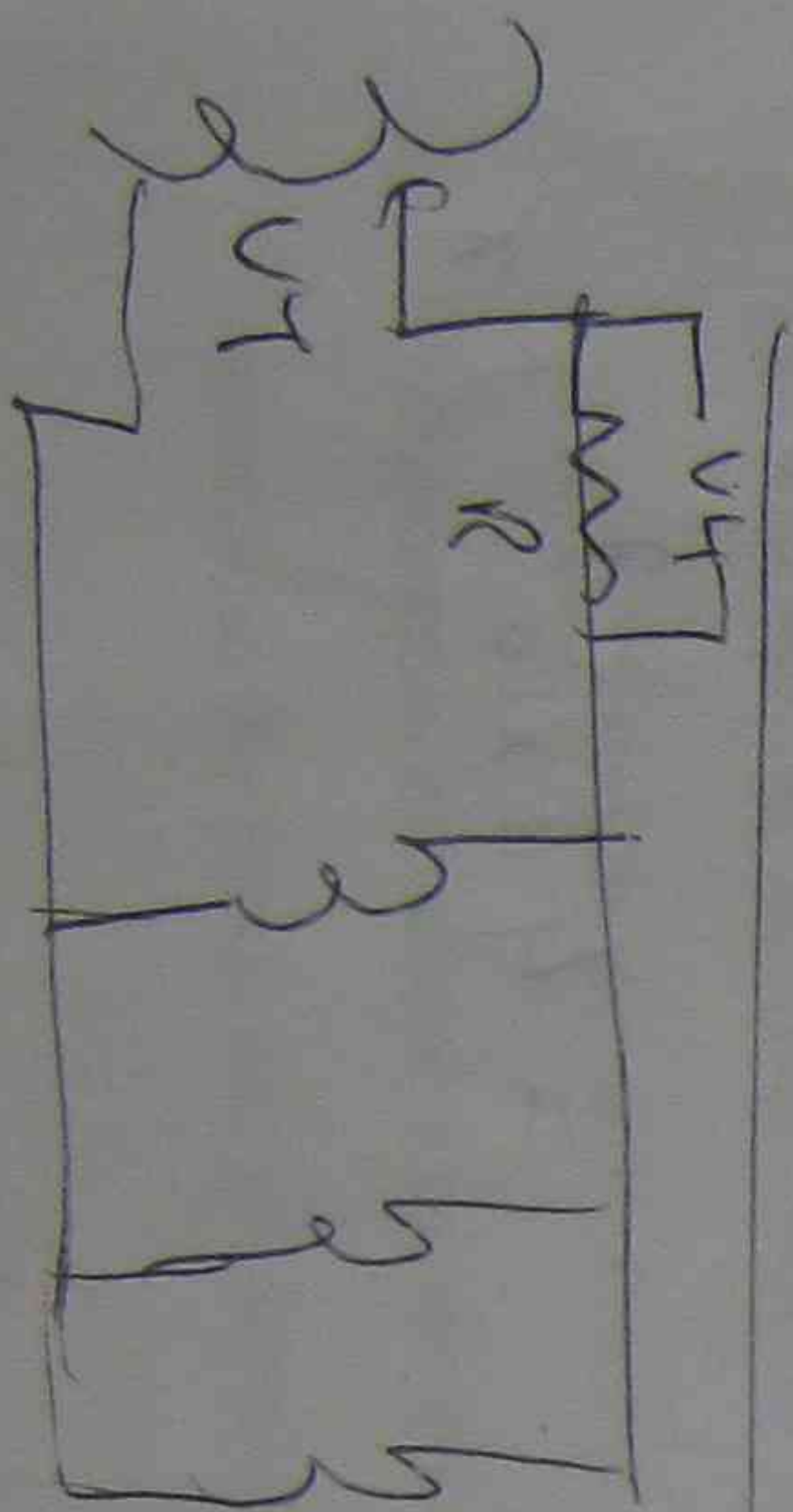

Connce



$$X_{LT} = I_{T2} = \frac{V_4}{R}$$

$$X_{LT} = \frac{V_T - V_4}{I_T}$$

$$\frac{1}{X_{LT}} = \frac{1}{X_{L1}} + \frac{1}{X_{L2}} + \frac{1}{X_{L3}}$$

$$50 \times 9 \sim 450 (N)$$

CP 31

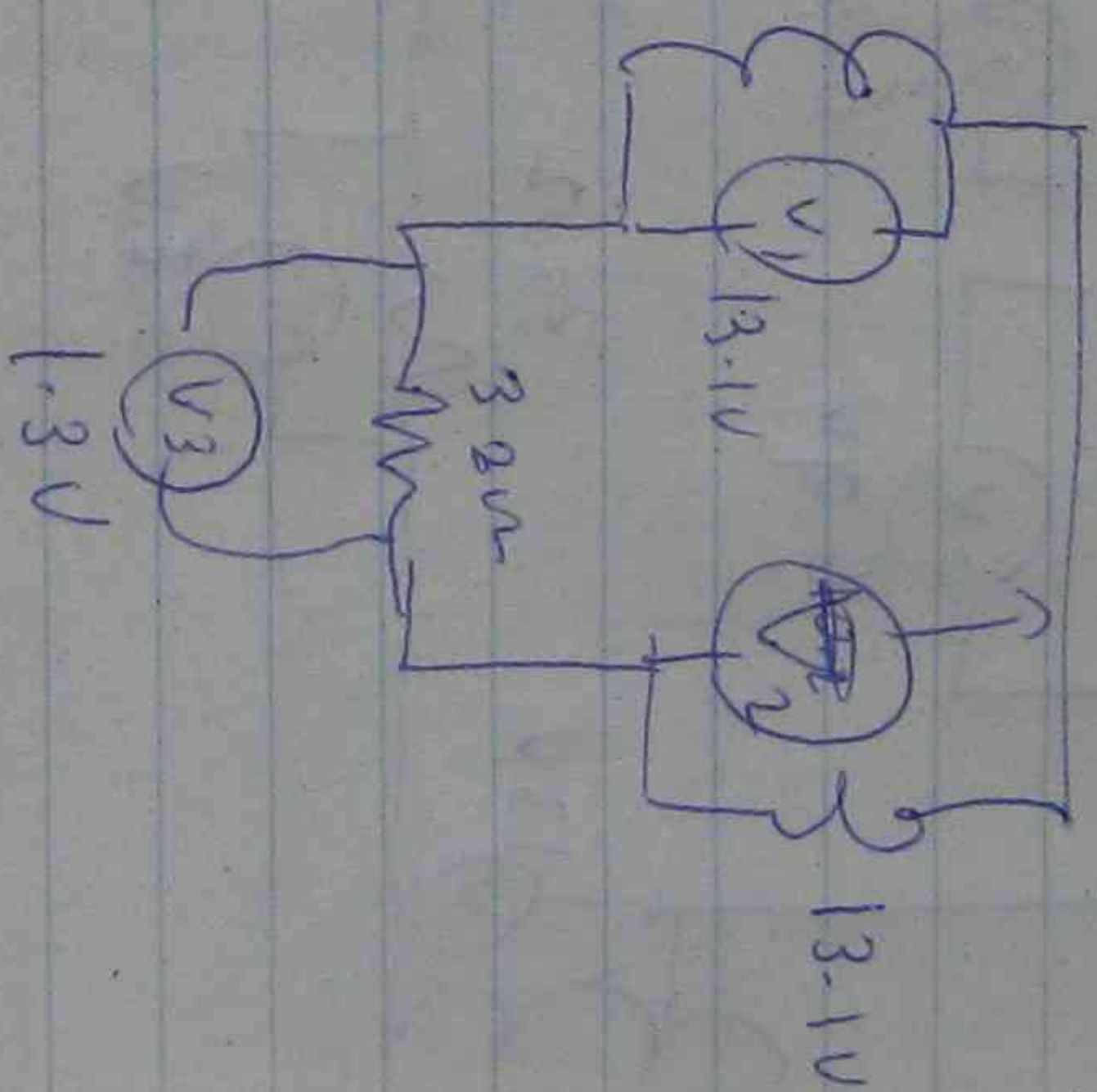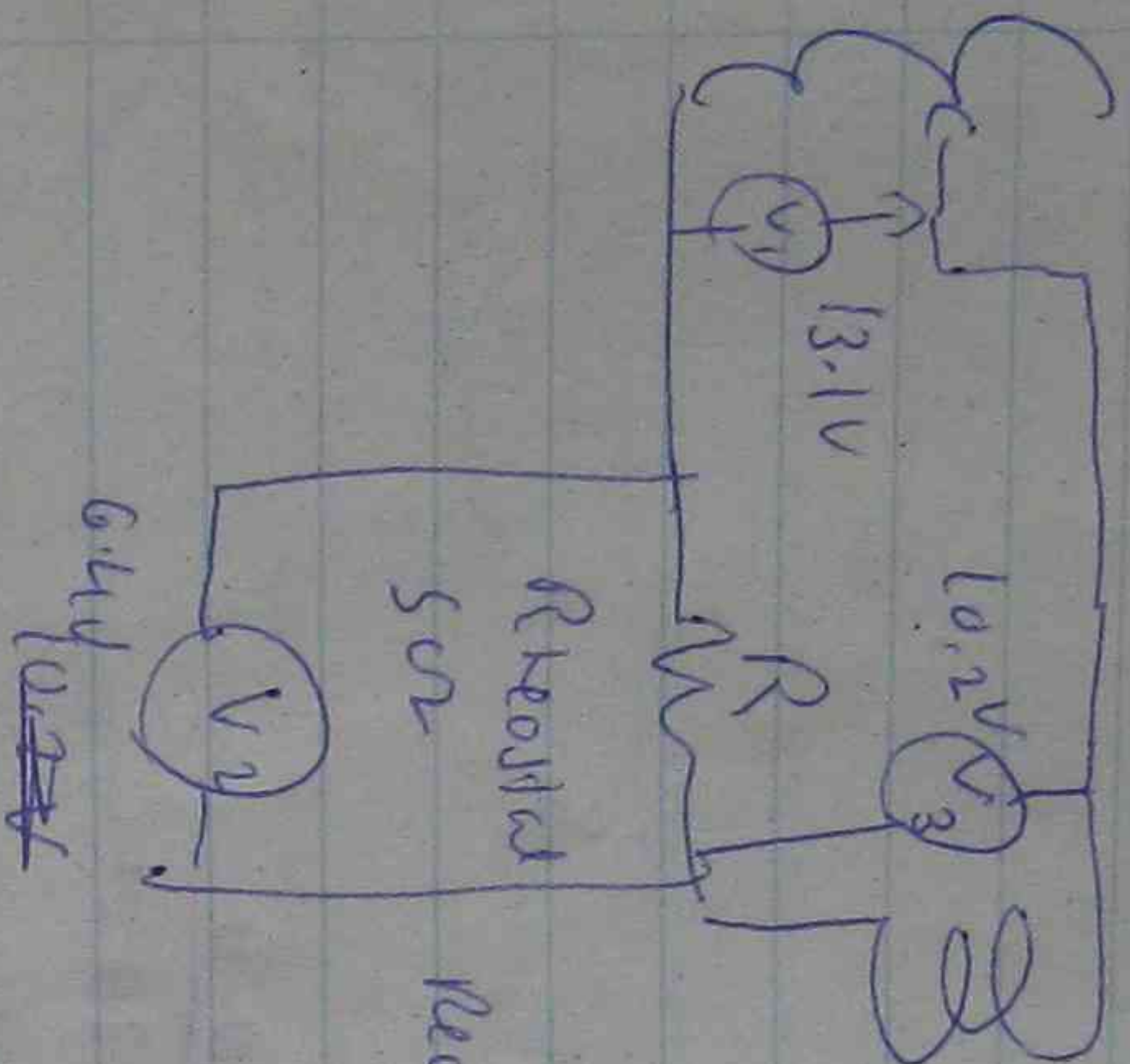

$$I = \frac{1.3}{39} = 0.0342 \text{ A}$$

$$X = \frac{13.1}{0.0342} = 383 \Omega$$

$$2 \pi f L = 383$$

$$314 \times L = 383$$

$$L = \frac{383}{314} = 1.21 \text{ H}$$

$$L = \frac{N^2 \mu A}{\lambda}$$

$$\lambda = 65 \text{ mm} = 65 \times 10^{-3}$$

$$1.21 = 450^2 \times \mu \times 50 \times 32 \times 10^{-6}$$

$$\mu = 50 \times 32 \text{ mm}^2$$

$$65 \times 10^{-3}$$

$$= 50 \times 10^{-3} \times 32 \times 10^{-3}$$

$$\therefore f = \frac{1.21 \times 65 \times 10^{-3}}{450^2 \times 50 \times 32 \times 10^{-6}}$$


$$= \frac{1.21 \times 65 \times 10^{-3}}{450 \times 450 \times 50 \times 32} = 2.42 \times 10^{-4}$$

$$\rho_0 \mu_r \sim 2.42 \times 10^{-4}$$

$$4 \pi \times 10^{-7} \mu_r \sim 2.42 \times 10^{-4}$$


$$\mu_r = \frac{2.42 \times 10^{-4} \times 10^7}{4 \times 3.1416} = \frac{2.42 \times 10^3}{4 \times 3.1416} = 192$$

EP 33

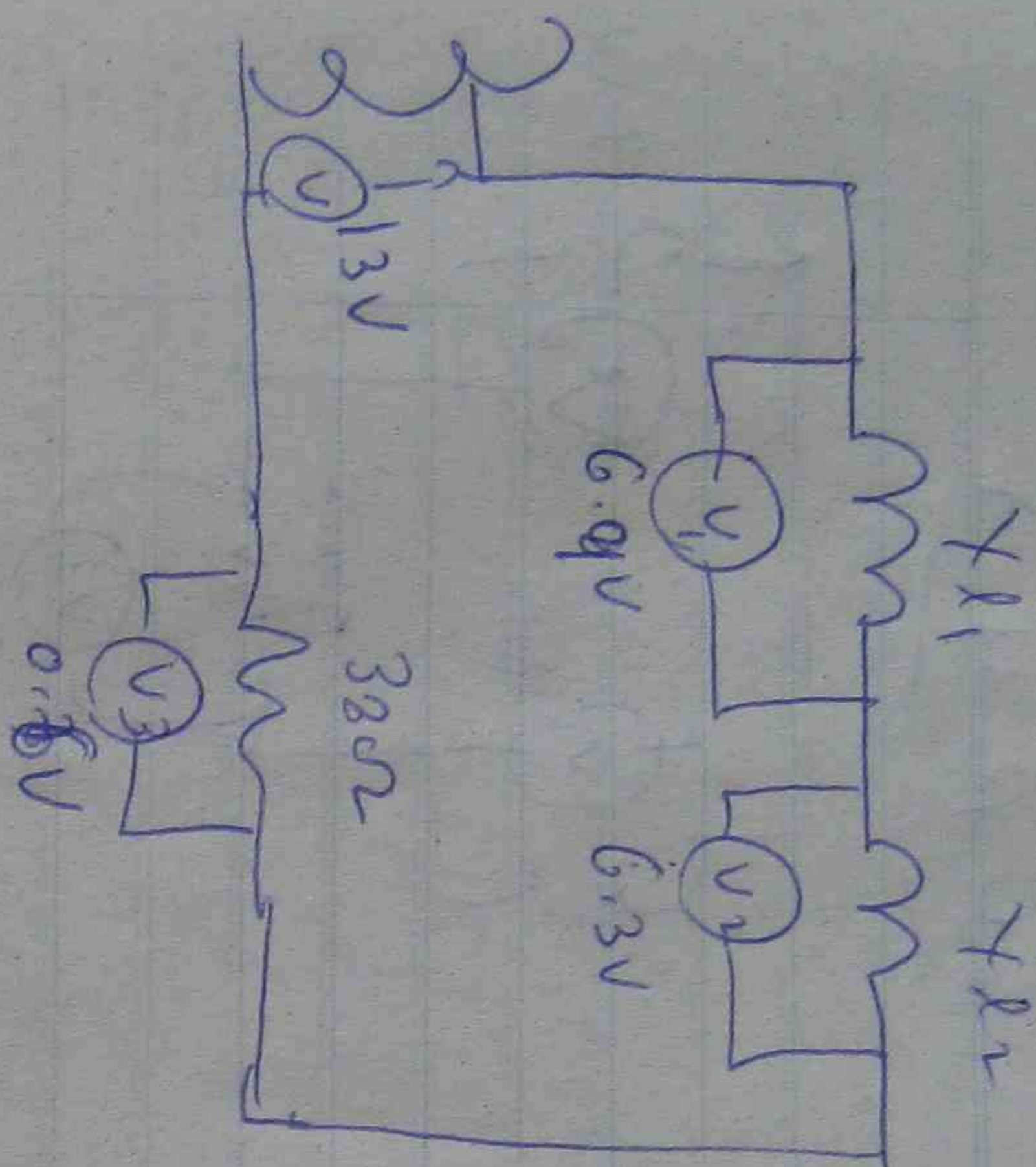

$$I = \frac{0.6}{30\Omega} = 2 \times 10^{-2} \text{ A}$$
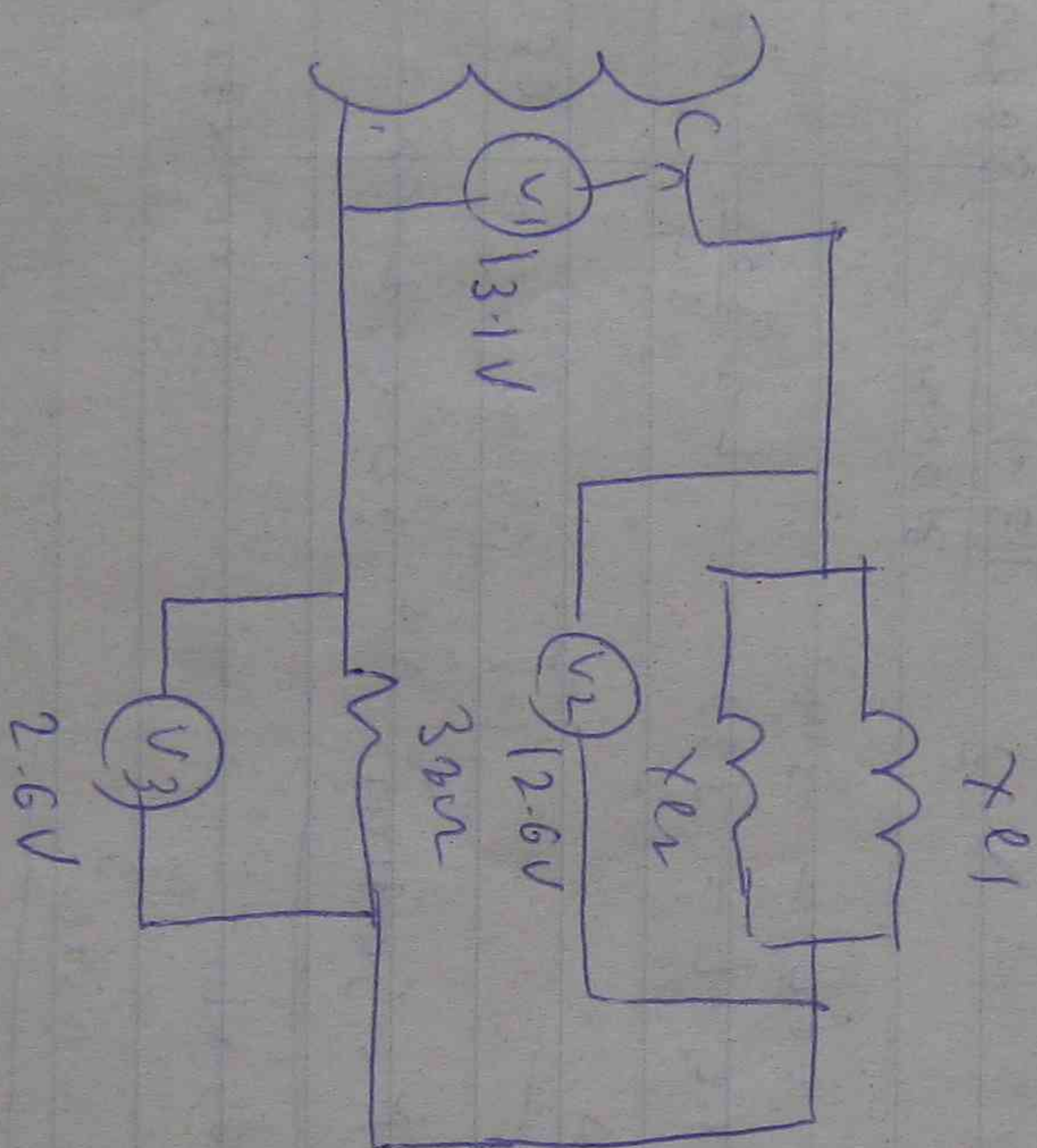
$$X_{R1} = \frac{V_1}{I}, \quad X_{R2} = \frac{V_2}{I}$$



$$I = \frac{2.6V}{30\Omega}$$

$$X_{R2} = \frac{V_1 - V_3}{\frac{2.6}{30}}$$