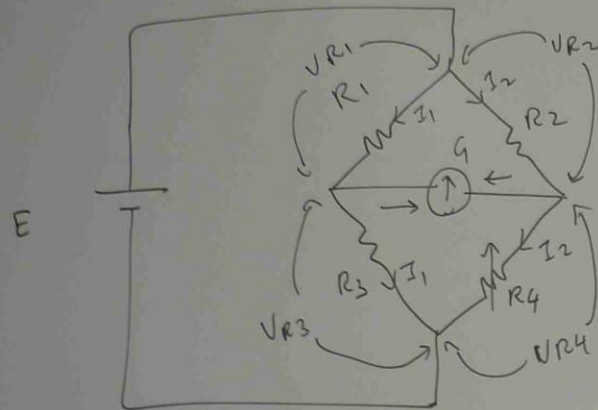


WHEATSTONE BRIDGE



ⓖ - GALVANOMETER



CENTRE ZERO METER

ADJUST THE VALUE OF VARIABLE RESISTOR " R_4 " TO BALANCE THE BRIDGE.

AT THE BALANCED CONDITION

$$V_{R1} = V_{R2}$$

AND

$$V_{R3} = V_{R4}$$

NO CURRENT FLOWS INTO GALVANOMETER

$$V_{R1} = I_1 R_1$$

AND

$$V_{R2} = I_2 R_2$$

$$V_{R3} = I_1 R_3$$

$$V_{R4} = I_2 R_4$$


$$I_1 R_1 = I_2 R_2 \quad \text{--- (1)}$$

$$I_1 R_3 = I_2 R_4 \quad \text{--- (2)}$$

$$\frac{\textcircled{1}}{\textcircled{2}} \quad \frac{I_1 R_1}{I_1 R_3} = \frac{I_2 R_2}{I_2 R_4}$$

$$\frac{R_1}{R_3} = \frac{R_2}{R_4}$$


$$R_1 R_4 = R_2 R_3$$

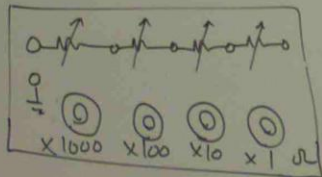

FOUR DECADE STANDARD RESISTANCE BOX

Pb ①

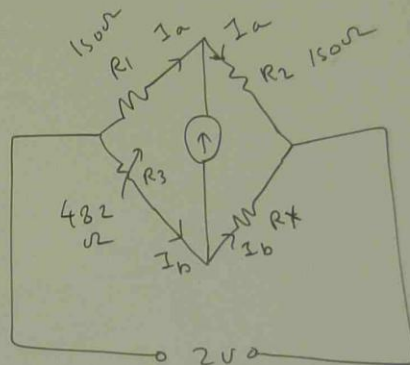THE CIRCUIT SHOWN IN FIGURE HAS BEEN SET UP TO MEASURE THE RESISTANCE OF R_X . THE BRIDGE IS BALANCED BY VARIATION OF R_3 AND AT BALANCE, ITS VALUE IS FOUND TO BE 482Ω . IF R_1 AND R_2 BOTH HAVE THE VALUES OF 150Ω , CALCULATE THE VALUE OF R_X AT BALANCE



$$V_{R_1} = V_{R_3}$$

$$V_{R_2} = V_{R_X}$$

$$I_a R_1 = I_b R_3 \quad \text{--- (1)}$$

$$I_a R_2 = I_b R_X \quad \text{--- (2)}$$


$$\frac{\textcircled{1}}{\textcircled{2}} \quad \frac{I_a R_1}{I_a R_2} = \frac{I_b R_3}{I_b R_X}$$

$$\frac{R_1}{R_2} = \frac{R_3}{R_X}$$

$$R_1 R_X = R_2 R_3$$

pb ①

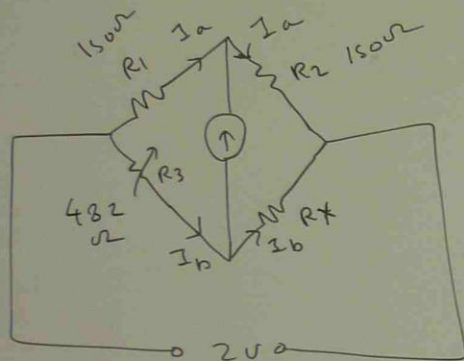THE CIRCUIT SHOWN IN FIGURE HAS BEEN SET UP TO MEASURE THE RESISTANCE OF R_x . THE BRIDGE IS BALANCED BY VARIATION OF R_3 AND AT BALANCE, ITS VALUE IS FOUND TO BE 482Ω . IF R_1 AND R_2 BOTH HAVE THE VALUES OF 150Ω , CALCULATE THE VALUE OF R_x AT BALANCE



$$V_{R1} = V_{R3}$$

$$V_{R2} = V_{R_x}$$

$$I_a R_1 = I_b R_3 \quad \text{--- (1)}$$

$$I_a R_2 = I_b R_x \quad \text{--- (2)}$$

$$\frac{\text{①}}{\text{②}}$$

$$\frac{I_a R_1}{I_a R_2} = \frac{I_b R_3}{I_b R_x}$$

$$\frac{R_1}{R_2} = \frac{R_3}{R_x}$$

$$R_1 R_x = R_2 R_3$$

$$R_x = \frac{R_2 R_3}{R_1}$$

$$= \frac{150 \times 482}{150}$$


$$= 482 \Omega$$

Prob 2

THE FOLLOWING BRIDGE CIRCUIT HAS THE FOLLOWING VALUES AT BALANCE.

$$R_1 = 1000 \Omega, \quad R_2 = 1000 \Omega, \quad R_3 = 27.15 \Omega.$$

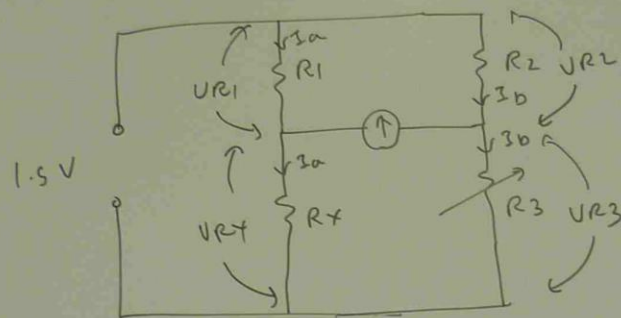CALCULATE THE VALUE OF THE UNKNOWN RESISTOR R_x .



BALANCED

$$V_{R1} = V_{R2} \quad \text{AND} \quad V_{Rx} = V_{R3}$$

$$I_a R_1 = I_b R_2 \quad \text{--- (1)} \quad \& \quad I_a R_x = I_b R_3 \quad \text{--- (2)}$$

①
②

$$\frac{I_a R_1}{I_a R_x} = \frac{I_b R_2}{I_b R_3}$$

$$\frac{R_1}{R_x} = \frac{R_2}{R_3}$$

$$R_1 R_3 = R_2 R_x$$


$$R_x = \frac{R_1 R_3}{R_2}$$

$$= \frac{1000 \times 27.15}{1000}$$

$$= 27.15 \Omega$$

Pb ③

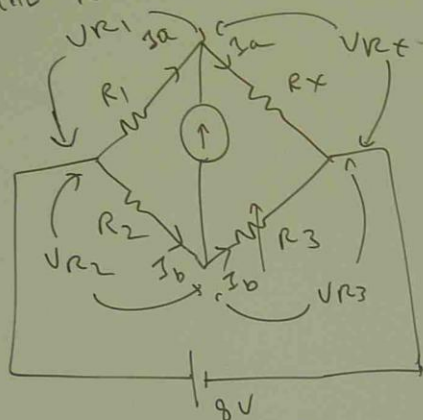THE CIRCUIT GIVEN IN THE FIGURE IS TO BE USED TO CONFIRM THE VALUE OF THE RESISTOR R_3 WHICH HAS VALUES FROM 0 TO 10 K Ω IN 100 STEPS. $R_x = 8.25 \text{ m}\Omega$ STANDARD RESISTORS WITH VALUES OF 10 Ω , 100 Ω , 1 K Ω AND 100 K Ω ARE AVAILABLE FOR USE AS RATIO ARMS SUGGEST THE COMBINATION TO GIVE THE BEST RESULTS FOR THE REQUIRED MEASUREMENT.



BALANCED

$$V_{R1} = V_{R2} \quad \text{--- (1)}$$

$$V_{Rx} = V_{R3} \quad \text{--- (2)}$$

$$I_a R_1 = I_b R_2 \quad \text{--- (1)}$$

$$I_a R_x = I_b R_3 \quad \text{--- (2)}$$

$$\frac{\text{①}}{\text{②}} \quad \frac{R_1}{R_x} = \frac{R_2}{R_3} \Rightarrow \frac{R_x}{R_1} = \frac{R_3}{R_2}$$

$$R_x = 8.25 \text{ m}\Omega$$

$$\text{Assume } R_1 = 10 \text{ K}\Omega$$

$$R_2 = 10 \text{ K}\Omega$$


$$\frac{8.25 \times 10^{-3} \text{ K}\Omega}{10 \text{ K}\Omega} = \frac{R_3}{10 \text{ K}\Omega}$$

$$R_3 = 8.25 \text{ m}\Omega$$

Pb 4

A WHEATSTONE BRIDGE IS ARRANGED AS SHOWN IN FIGURE.

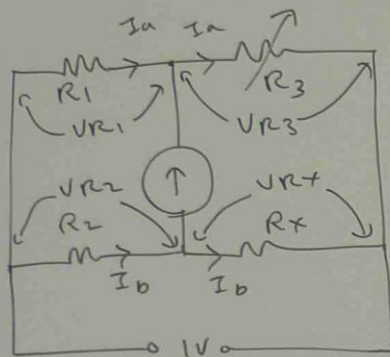THE TWO ARMS R_1 AND R_2 HAVE VALUES OF 1000Ω AND 10Ω RESPECTIVELY. AND AT BALANCE, THE VARIABLE R_3 IS FOUND TO BE SET AT 154Ω . CALCULATE THE VALUE OF THE UNKNOWN RESISTOR " R_x ".



$$R_1 = 1000\Omega, R_2 = 10\Omega$$

$$R_3 = 154\Omega, R_x = ?$$

AT BALANCED CONDITION

$$V_{R1} = V_{R2} \quad \text{--- (1)}$$

$$V_{R3} = V_{Rx} \quad \text{--- (2)}$$

$$I_a R_1 = I_b R_2 \quad \text{--- (1)}$$

$$I_a R_3 = I_b R_x \quad \text{--- (2)}$$

$$R_x = \frac{R_2 R_3}{R_1}$$

$$= \frac{10 \times 154}{1000} = \frac{1540}{1000} = 1.54\Omega$$


(1)
(2)

$$\frac{R_1}{R_3} = \frac{R_2}{R_x}$$

$$R_1 R_x = R_2 R_3$$

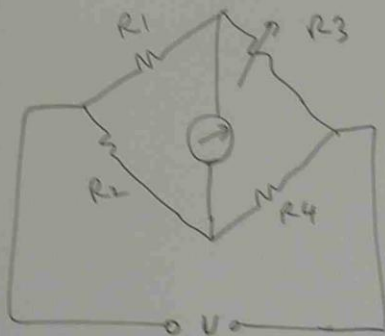EXERCISE

- ① THE CIRCUIT FOR A WHEATSTONE BRIDGE IS SHOWN IN FIGURE.
IF $R_1 = R_2 = 1\text{ k}\Omega$ AND R_3 AT BALANCE IS 1537Ω ,
THE VALUE OF R_4 WILL BE




- (a) 1.537Ω
(b) $1.537\text{ m}\Omega$
(c) 537Ω
(d) 1537Ω

- ② THE BALANCE EQUATION FOR THE GIVEN BRIDGE CIRCUIT WILL BE




- (a) $R_x = \frac{R_1}{R_2 R_3}$
(b) $R_x = \frac{R_1 R_2}{R_3}$
(c) $R_x = \frac{R_2 R_3}{R_1}$
(d) $R_x = R_1 R_2 R_3$


ELECTRO CHEMISTRY

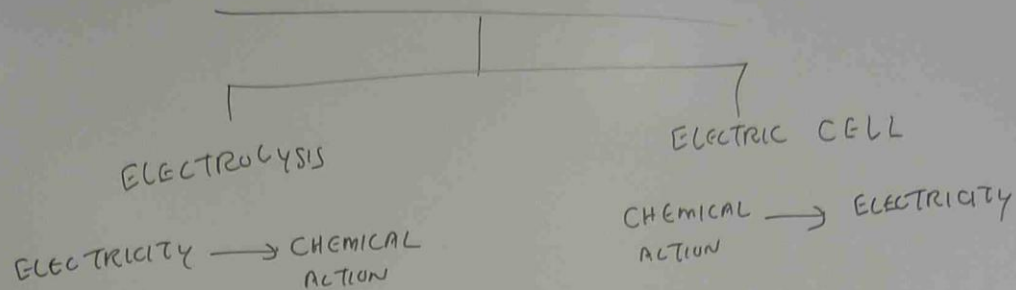

ELECTROPLATING

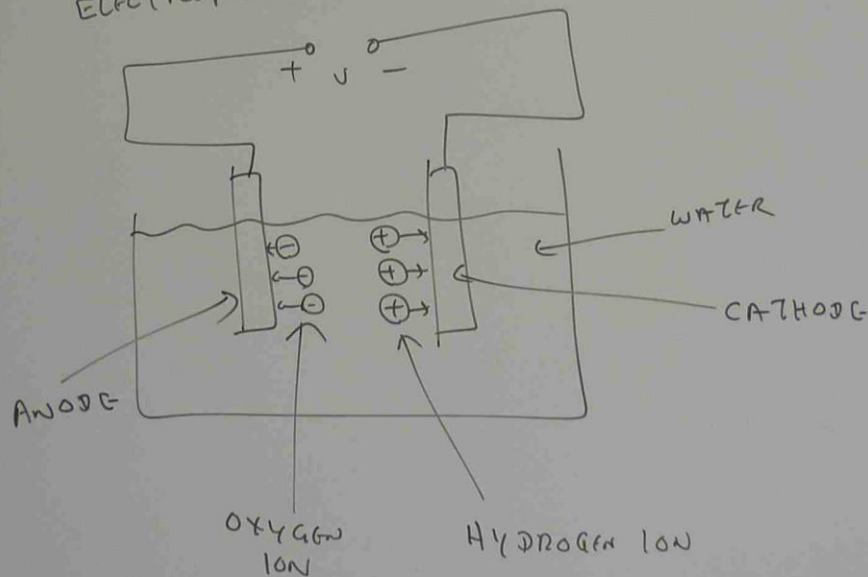

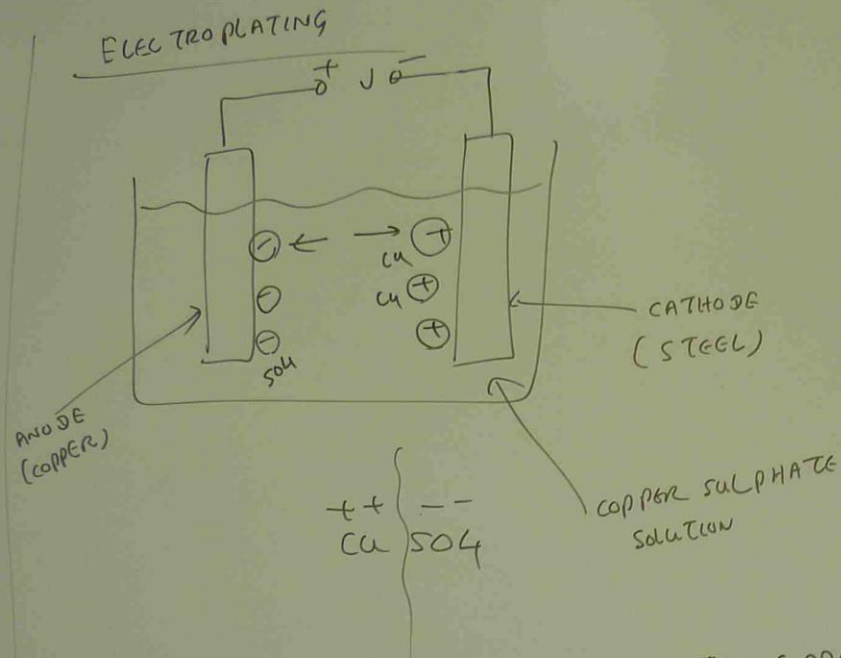ELECTRIC CURRENT FLOWS IN TO WATER.
WATER MOLECULE IS DISSOLVED INTO ⊖ OXYGEN
AND ⊕ HYDROGEN IONS.




COPPER PLATE IS CONNECTED TO COPPER
BAR (ANODE) (+) AND CATHODE STEEL IS
CONNECTED TO (-) TERMINAL.

COPPER SULPHATE $Cu^{++} SO_4^{--}$ IS DISSOLVED INTO
POSITIVE COPPER AND NEGATIVE SULPHATE

\oplus ANODE ATTRACTS $\ominus SO_4$
 \ominus CATHODE-STEEL ATTRACTS
 $\oplus Cu$.

STEEL IS COVERED WITH COPPER.

THE ELECTRIC CELL

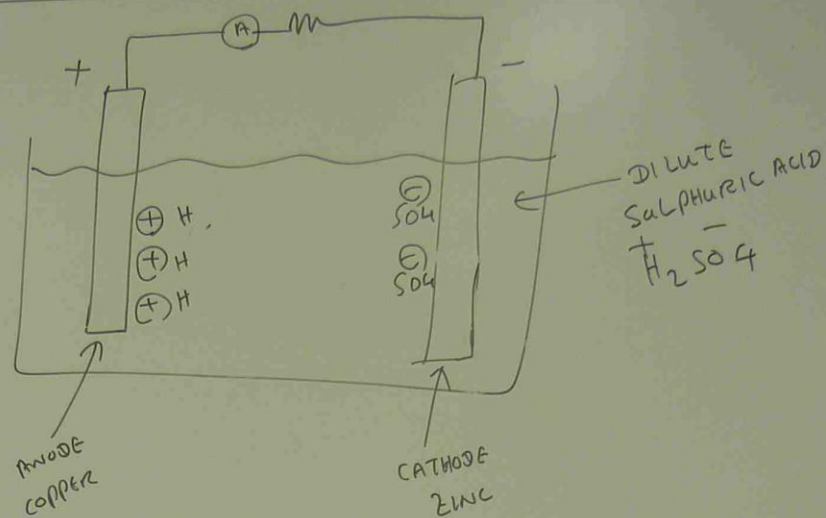


DILUTE SULPHURIC H_2SO_4 IS DISSOLVED
 INTO \oplus HYDROGEN AND \ominus SULPHATE IONS.

\oplus HYDROGEN IONS COVER ANODE COPPER BAR
 AND MAKE \oplus TERMINAL

\ominus SULPHATE IONS COVER CATHODE ZINC BAR
 AND MAKE \ominus TERMINAL.

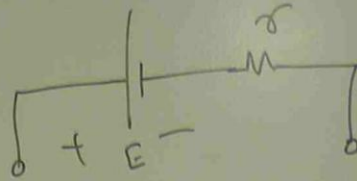
ELECTRICAL CURRENT FLOWS FROM $(+)$ TO $(-)$ TERMINAL



EQUIVALENT DIAGRAM FOR BATTERY

E - ELECTROMOTIVE FORCE (V)

r - INTERNAL RESISTANCE OF BATTERY

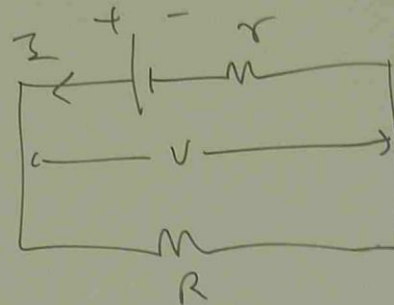

V = TERMINAL VOLTAGE

$$E = V + I r$$

$$I = \frac{E}{R + r}$$

pb ①


A CELL HAS AN EMF OF $1.5V$ AND INTERNAL RESISTANCE 0.5Ω .
CALCULATE ITS TERMINAL VOLTAGE AT

- (a) NO LOAD (b) WHEN PROVIDING A CURRENT OF $200mA$
(c) WHEN CONNECTED TO A LOAD OF RESISTANCE 8Ω .

(a) $E = V + I r$


$E = V = 1.5V$

(b)

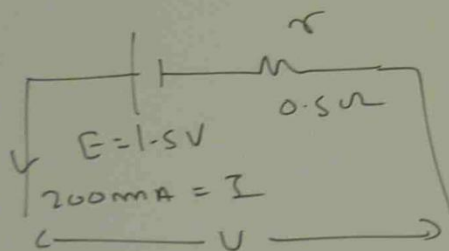


$$\begin{aligned} V &= E - I r \\ &= 1.5 - 200 \times 10^{-3} \times 0.5 \\ &= 1.5 - 0.2 \times 0.5 \\ &= 1.5 - 0.1 \\ &= 1.4V \end{aligned}$$

(c)

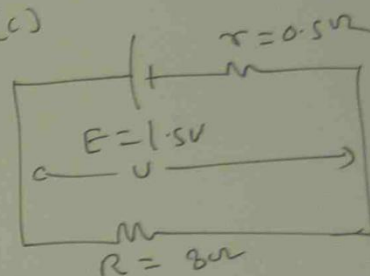

$$\begin{aligned} I &= \frac{E}{R + r} \\ &= \frac{1.5}{8 + 0.5} \\ &= \frac{1.5}{8.5} = 0.176A \end{aligned}$$
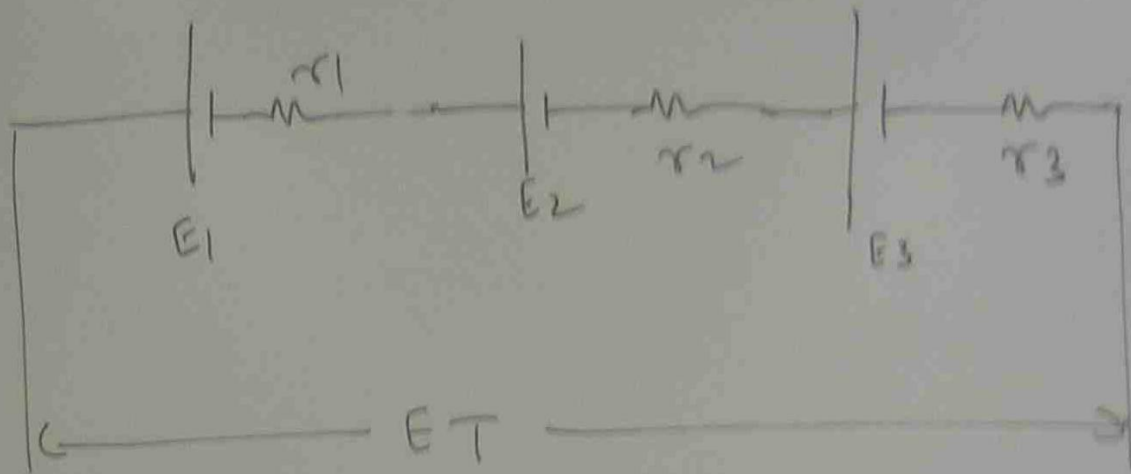
$$\begin{aligned} V &= E - I r \\ &= 1.5 - 0.176 \times 0.5 \\ &= 1.41V \end{aligned}$$



$$E_T = E_1 + E_2 + E_3 + \dots$$

$$r_T = r_1 + r_2 + r_3 + \dots$$

pb 2


A BATTERY IS MADE BY CONNECTING EIGHT CELLS IN SERIES.
EACH OF THE CELLS HAS AN EMF OF 1.5V AND AN INTERNAL
RESISTANCE OF 0.35Ω .

CALCULATE (a) THE EMF AND THE INTERNAL RESISTANCE OF
THE BATTERY

(b) THE TERMINAL VOLTAGE WHEN SUPPLYING A CURRENT
OF 300mA


(c) THE CURRENT AND TERMINAL VOLTAGE WHEN A
LOAD OF RESISTANCE 15Ω IS CONNECTED TO THE BATTERY.

(a)

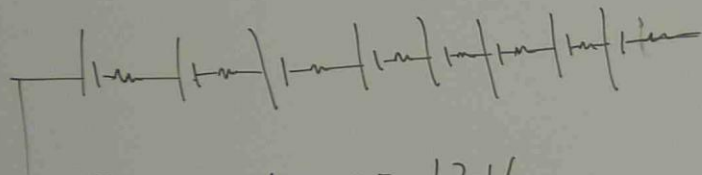


$$E = 8 \times 1.5\text{V} = 12\text{V}$$

$$r = 8 \times 0.35 = 2.8\Omega$$

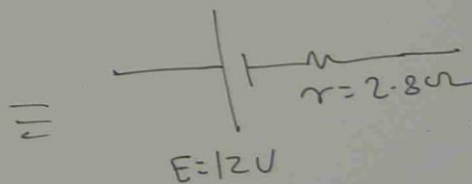


(b)

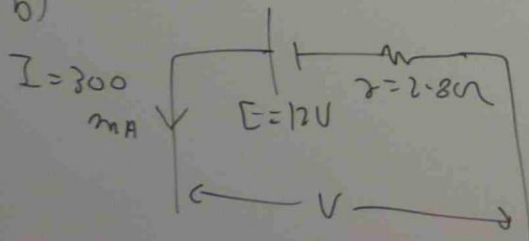

$$V = E - Ir = 12 - 0.3 \times 2.8$$
$$= 11.16\text{V}$$

(c)

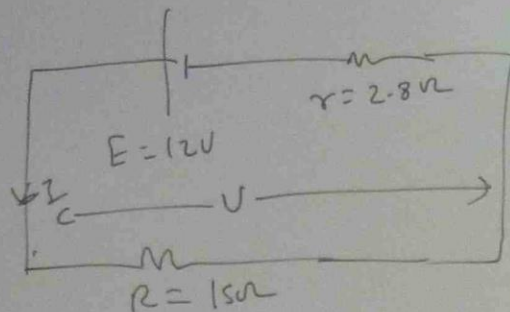

$$I = \frac{E}{R + r}$$

$$= \frac{12}{15 + 2.8}$$

$$= \frac{12}{17.8} = 0.674 \text{ AMP.}$$

$$V = E - I r$$

$$= 12 - 0.674 \times 2.8$$

$$= 10.11V$$

EXERCISE

① A DRY BATTERY INTENDED TO POWER A PERSONAL STEREO IS MADE UP OF SIX SERIES CONNECTED CELLS. EACH WITH EMF $1.5V$ AND INTERNAL RESISTANCE 0.08Ω .

THE EMF AND INTERNAL RESISTANCE OF THE BATTERY WILL BE

- (a) $9V$, 0.08Ω (b) $6V$, 0.48Ω
 (c) $9V$, 4.8Ω (d) $9V$, 0.48Ω

② A BATTERY WITH AN EMF $15V$ AND INTERNAL RESISTANCE 1.4Ω DELIVERS $350mA$ TO ELECTRONIC CIRCUIT. TERMINAL VOLTAGE WILL BE

- (a) $4.9V$ (b) $10.1V$ (c) $14.51V$ (d) $15.49V$

③ A $6V$ BATTERY WITH INTERNAL RESISTANCE 0.8Ω IS CONNECTED TO A CIRCUIT WITH 8.2Ω . THE DRAIN CURRENT IS

- (a) $667mA$ (b) $772mA$ (c) $1.5A$
 (d) $1.77A$