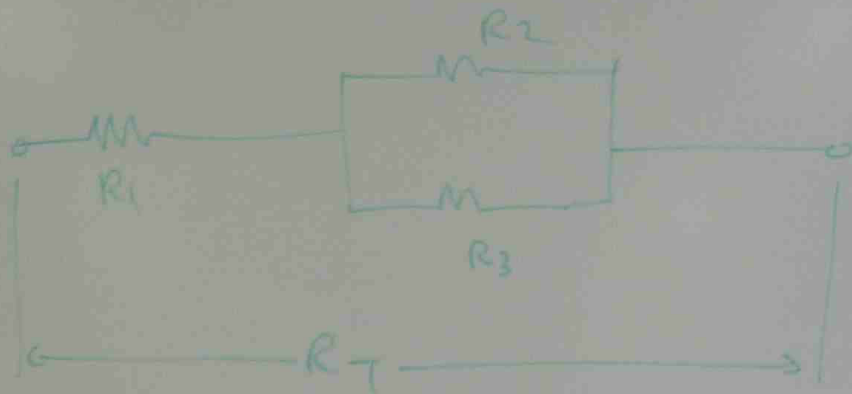


DC SERIES AND PARALLEL CIRCUITS



$$R_{23} = \frac{R_2 R_3}{R_2 + R_3}$$

$$R_T = R_1 + R_{23} = R_1 + \frac{R_2 R_3}{R_2 + R_3}$$


Pb ①

A 1Ω RESISTOR IS CONNECTED IN SERIES WITH THE PARALLEL COMBINATION OF A 6Ω AND A 3Ω RESISTOR TO A $6V$ SUPPLY.

CALCULATE (a) THE EFFECTIVE OVER ALL RESISTANCE OF THE CIRCUIT

(b) THE CURRENT IN EACH OF THE THREE

RESISTORS.

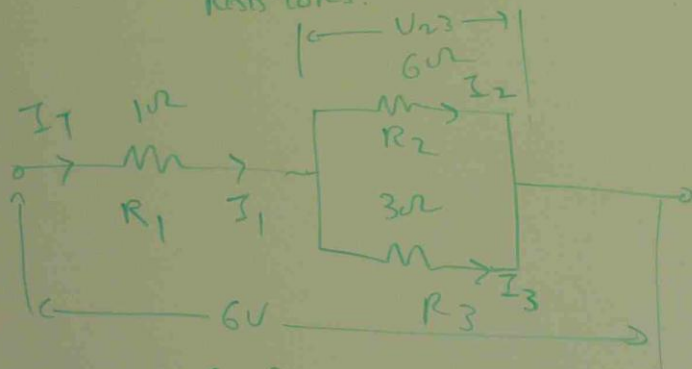

$$I_T = \frac{6}{3} = 2 \text{ Amp.} \Rightarrow I_1 = 2A$$

$$R_1 (1\Omega) \text{ CURRENT} = 2 \text{ Amp}$$

$$V_{23} = I_T \times R_{23}$$

$$= 2 \times 2 = 4V$$

$$I_2 = \frac{V_{23}}{R_2} = \frac{4}{6} = 0.66 \text{ Amp}$$

$$R_{23} = \frac{6 \times 3}{6 + 3} = \frac{18}{9} = 2\Omega$$

$$(a) R_T = R_1 + R_{23} = 1 + 2 = 3\Omega$$

RIES WITH THE PARALLEL
RESISTOR TO A 6 V

ALL RESISTANCE OF THE

OF THE THREE

$$I_T = \frac{6}{3} = 2 \text{ Amp.} \Rightarrow I_1 = 2 \text{ A}$$

$R_1 (1\Omega)$ CURRENT = 2 Amp


$$V_{23} = I_T \times R_{23}$$

$$= 2 \times 2 = 4 \text{ V}$$

$$I_2 = \frac{V_{23}}{R_2} = \frac{4}{6} = 0.66 \text{ Amp}$$


$$I_3 = \frac{V_{23}}{R_3} = \frac{4}{3} = 1.33 \text{ Amp.}$$

CURRENT DIVIDER RULE

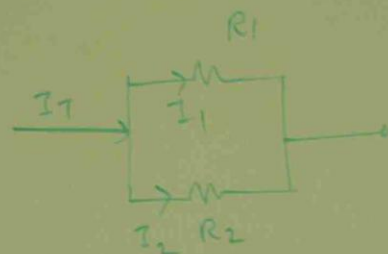

$$I_1 = I_T \times \frac{R_2}{R_1 + R_2}$$
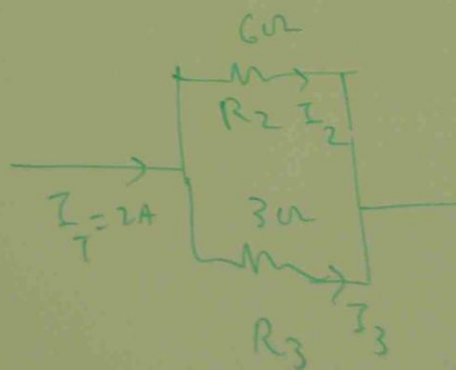
$$I_2 = I_T \times \frac{R_1}{R_1 + R_2}$$



$$I_2 = I_T \times \frac{R_3}{R_2 + R_3}$$

$$= 2 \times \frac{3}{6+3}$$


$$= \frac{6}{9} = 0.66 \text{ A}$$

$$I_3 = I_T \times \frac{R_2}{R_2 + R_3} = 2 \times \frac{6}{6+3} = \frac{12}{9} = 1.33 \text{ A}$$

Pb(2)


RESISTORS OF $2.2\text{ k}\Omega$ AND $7.8\text{ k}\Omega$ ARE CONNECTED IN SERIES AND IN PARALLEL ACROSS THEM IS A SECOND SERIES GROUP OF $3.3\text{ k}\Omega$ AND $2.7\text{ k}\Omega$ RESISTORS. THE COMPLETE CIRCUIT IS CONNECTED TO A 9V SUPPLY.

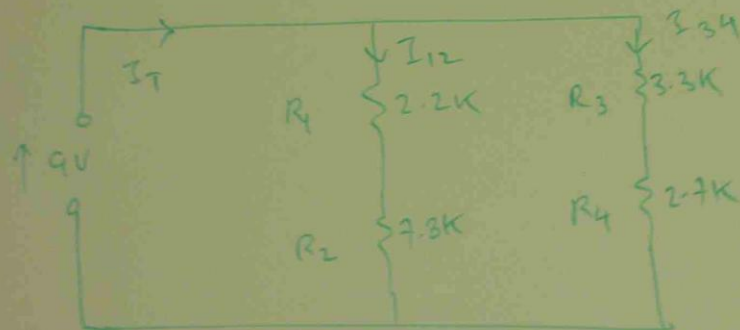CALCULATE (a) THE TOTAL RESISTANCE OF THE CIRCUIT AND (b) THE CURRENT FROM THE SUPPLY AND IN EACH RESISTOR.



$$R_{12} = R_1 + R_2 = 2.2 + 7.8 = 10\text{ k}\Omega$$
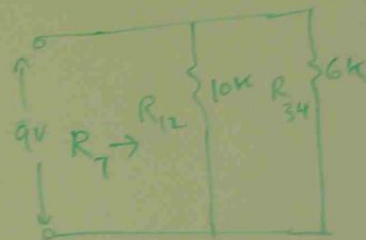
$$R_{34} = R_3 + R_4 = 3.3 + 2.7 = 6\text{ k}\Omega$$



$$R_T = \frac{R_{12} \times R_{34}}{R_{12} + R_{34}}$$

$$= \frac{10 \times 6}{10 + 6}$$

$$= \frac{60}{16} = 3.75\text{ k}\Omega$$

$$I_T = \frac{9\text{V}}{R_T}$$

$$I_{12} = \frac{9}{R_{12}}$$

$$I_{34} = \frac{9}{6\text{ k}\Omega}$$

Pb(3)

FIVE RESISTOR GROUPING TO A

CALCULATE

(a)

(b)

(c)

$$I_T = \frac{9V}{R_T} = \frac{9}{3.75K} = \frac{9}{3.75 \times 10^3} = 2.4 \times 10^{-3} A \\ = 2.4 \text{ mA}$$

$$I_{12} = \frac{9}{R_{12}} = \frac{9}{10K} = \frac{9}{10 \times 10^3} = 0.9 \times 10^{-3} A \\ = 0.9 \text{ mA}$$

$$I_{34} = \frac{9}{6K} = \frac{9}{6 \times 10^3} = 1.5 \times 10^{-3} = 1.5 \text{ mA}$$

pb(3)


FIVE RESISTORS ARE CONNECTED IN SERIES-PARALLEL GROUPING TO A 6V SUPPLY AS SHOWN IN FIGURE

CALCULATE

(a) TOTAL RESISTANCE OF THE CIRCUIT

(b) THE CURRENT PROVIDED BY THE SUPPLY

(c) THE CURRENT FLOWING IN 2Ω RESISTOR.

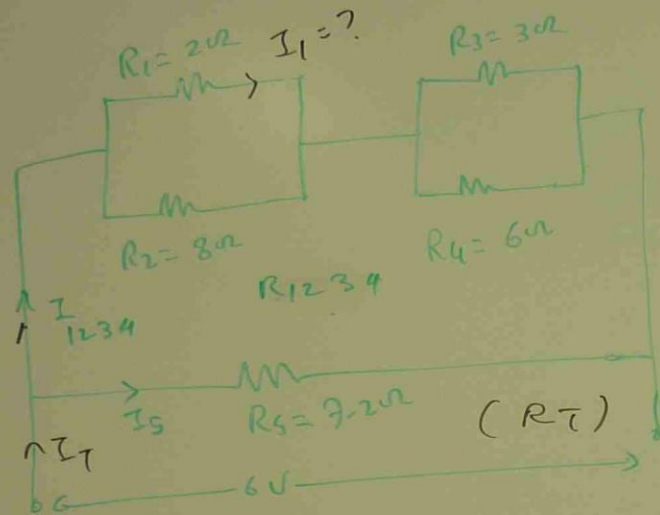

$$I_{1234} = I_T \times \frac{R_5}{R_{1234} + R_5} = 2.5 \times \frac{7.2}{3.6 + 7.2} = 2.5 \times \frac{7.2}{10.8} = 1.66 \text{ Amp}$$

$$I_1 = I_{1234} \times \frac{R_2}{R_1 + R_2}$$

$$= 1.66 \times \frac{8}{2 + 8}$$

$$= 1.66 \times \frac{8}{10}$$

$$= 1.33 \text{ Amp}$$

$$R_{12} = \frac{2 \times 8}{2 + 8} = 1.6 \Omega$$

$$R_{34} = \frac{3 \times 6}{3 + 6} = 2 \Omega$$

$$R_{1234} = R_{12} + R_{34} = 1.6 + 2 = 3.6 \Omega$$

(a)

$$R_T = \frac{R_{1234} \times R_5}{R_{1234} + R_5} = \frac{3.6 \times 7.2}{3.6 + 7.2} = \frac{3.6 \times 7.2}{10.8} = 2.4 \Omega$$

$$(b) I_T = \frac{V}{R_T} = \frac{6}{2.4} = 2.5 \text{ A}$$

INPUT power + OUTPUT power + EFFICIENCY



$$\text{INPUT power} = V \times I$$

$$T = \text{TORQUE}$$



$$T = \text{FORCE} \times \text{RADIUS}$$

$$T = F \times r$$


$$N = \text{SPEED (RPM)}$$

Prob (1) AN ELECTRIC MOTOR HAS A TOTAL power INPUT of 1200 W AND AN OUTPUT of 1000 W.
CALCULATE PER UNIT AND PERCENTAGE EFFICIENCIES.

$$\begin{aligned} \text{P.u (PER UNIT) EFFICIENCY} &= \frac{\text{OUTPUT POWER}}{\text{INPUT POWER}} \\ &= \frac{1000}{1200} = 0.833 \end{aligned}$$

$$\begin{aligned} \% \text{ EFFICIENCY} &= \frac{\text{OUTPUT POWER}}{\text{INPUT POWER}} \times 100 \\ &= \frac{1000}{1200} \times 100 = 83.3\% \end{aligned}$$

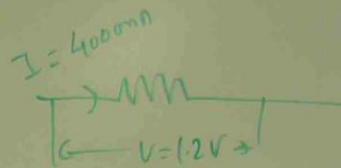Pb 2 A RESISTOR HAS A VOLTAGE OF 1.2V ACROSS IT AND CARRIES A CURRENT OF 400mA. IF THE RESISTOR HAS A POWER RATING OF 0.5W, IS IT OPERATION LIKELY TO BE SATISFACTORY?



$$\begin{aligned} \text{Power} &= V \times I = 1.2 \times 400 \times 10^{-3} \\ &= 0.48 \text{ WATT} \end{aligned}$$

ACTUAL POWER 0.48W IS LESS THAN RATED POWER OF RESISTOR, THE RESISTOR WILL NOT BE OVER HEATED AND IT'S OPERATION IS SATISFACTORY


Pb 3 THE VOLTAGE ACROSS A 12Ω RESISTOR IS 0.8V, CALCULATE THE POWER DISSIPATED IN IT.

$$\begin{aligned} P &= \frac{V^2}{R} = \frac{(0.8)^2}{12} = 0.0533\text{W} \\ &= 53.3\text{mW} \end{aligned}$$

$$\begin{aligned} \text{P.u (PER UNIT) EFFICIENCY} &= \frac{\text{OUTPUT POWER}}{\text{INPUT POWER}} \\ &= \frac{1000}{1200} = 0.833 \end{aligned}$$

$$\begin{aligned} \% \text{ EFFICIENCY} &= \frac{\text{OUTPUT POWER}}{\text{INPUT POWER}} \times 100 \\ &= \frac{1000}{1200} \times 100 = 83.3\% \end{aligned}$$

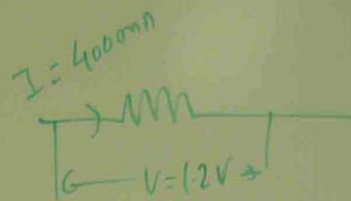Pb ② A RESISTOR HAS A VOLTAGE OF 1.2V ACROSS IT AND CARRIES A CURRENT OF 400mA. IF THE RESISTOR HAS A POWER RATING OF 0.5W, IS IT OPERATION LIKELY TO BE SATISFACTORY?



$$\begin{aligned} \text{Power} &= V \times I = 1.2 \times 400 \times 10^{-3} \\ &= 0.48 \text{ WATT} \end{aligned}$$

ACTUAL POWER 0.48W IS LESS THAN RATED POWER OF RESISTOR, THE RESISTOR WILL NOT BE OVER HEATED AND IT'S OPERATION IS SATISFACTORY

Pb ③ THE VOLTAGE ACROSS A 12Ω RESISTOR IS 0.8V, CALCULATE THE POWER DISSIPATED IN IT.

$$\begin{aligned} P &= \frac{V^2}{R} = \frac{(0.8)^2}{12} = 0.0533\text{W} \\ &= 53.3\text{mW} \end{aligned}$$


Pb 4

A $47 \text{ k}\Omega$ resistor is carrying a current of 6 mA . Calculate the power dissipated.

$$P = I^2 R = (6 \times 10^{-3})^2 \times 47 \times 10^3 = 36 \times 10^{-6} \times 47 \times 10^3 = \frac{36 \times 47}{1000} = 1.69 \text{ W}$$

Pb 5

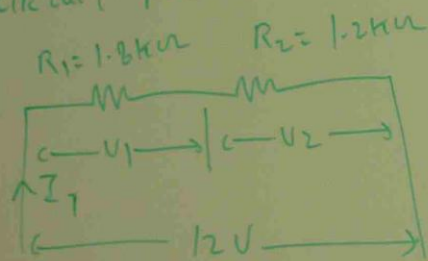A circuit has resistors of $1.8 \text{ k}\Omega$ and $1.2 \text{ k}\Omega$ connected in series to a 12 V supply. Calculate the power dissipated in each resistor and total circuit power.



$$R_T = R_1 + R_2 = 1.8 + 1.2 = 3 \text{ k}\Omega$$


$$I_T = \frac{V}{R_T} = \frac{12}{3 \times 10^3} = 0.4 \times 10^{-3} \text{ A (mA)}$$

$$P_1 = I_T^2 \times R_1 = (0.4 \times 10^{-3})^2 \times 1.8 \times 10^3 = 0.16 \times 10^{-6} \times 1.8 \times 10^3 = 0.0288 \text{ W} \quad (\text{or}) \quad 28.8 \text{ mW}$$

$$P_2 = I_T^2 \times R_2 = (0.4 \times 10^{-3})^2 \times 1.2 \times 10^3$$

$$= 0.16 \times 10^{-6} \times 1.2 \times 10^3 = 0.0192 \text{ W} \quad (\text{or}) \quad 19.2 \text{ mW}$$
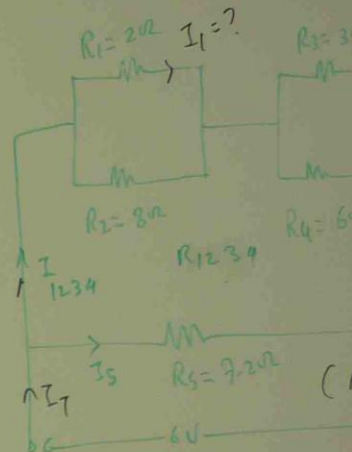
$$P_T = P_1 + P_2 = 28.8 + 19.2 = 48 \text{ mW}$$



$$R_{12} = \frac{2 \times 8}{2 + 8} = 1.6 \Omega$$

$$R_{34} = \frac{3 \times 6}{3 + 6} = 2 \Omega$$


$$R_{1234} = R_{12} + R_{34} = 1.6 + 2 = 3.6 \Omega$$

$$R_T = \frac{R_{1234} \times R_5}{R_{1234} + R_5}$$

$$(b) I_T = \frac{V}{R_T} = \frac{6}{2.4} = 2.5 \text{ A}$$

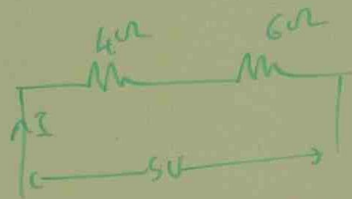
EXERCISE

- ① THE POWER DISSIPATED IN 4Ω RESISTOR OF THE CIRCUIT IS



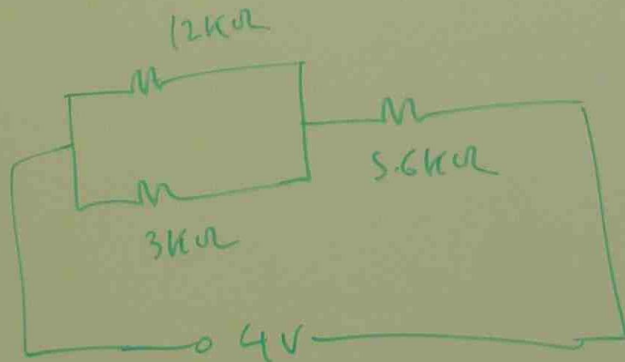- (a) 0.1W (b) 2.5W (c) 1.5W (d) 1W

- ② THE POWER DISSIPATED IN $12\text{K}\Omega$ RESISTOR IS



- (a) 1.4mW (b) $120\mu\text{W}$ (c) $75\mu\text{W}$ (d) 2mW