

$$\rightarrow T_{st} = 0.4 T_{FL}$$

DOL

AUTOMATIC REDUCED VOLTAGE STARTERS

PRIMARY RESISTANCE STARTING

IN PRIMARY RESISTANCE STARTING, A RESISTOR IS CONNECTED IN EACH MOTOR LINE TO PRODUCE A VOLTAGE DROP TO THE MOTOR STARTING CURRENT.



A TIMING RELAY SHORTS OUT THE RESISTORS AFTER THE MOTOR HAS ACCELERATED. THE MOTOR IS STARTED AT REDUCED VOLTAGE BUT OPERATES AT LINE VOLTAGE

OPERATION WHEN START IS PRESSED, THE CURRENT FLOWS 1, 2, 3, 4, 5, 6, 7

(S) COIL IS ENERGIZED, 5 CONTACTORS ARE CLOSED, MOTOR STARTS WITH SERIES RESISTANCE.

(TR) COIL IS ALSO ENERGIZED. (TR) COIL TRIES TO CLOSE TRTC.

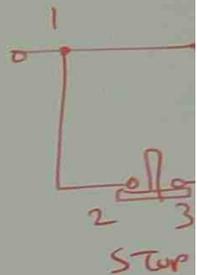
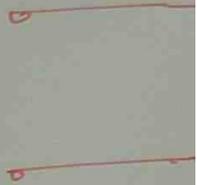
BUT TRTC CONTACT DOES NOT CLOSE IMMEDIATELY. IT WAITS FOR SOME TIME. DURING THIS TIME, MOTOR STARTING CURRENT IS



TR - Time
Rel
Co

TRTC -

REDUCED

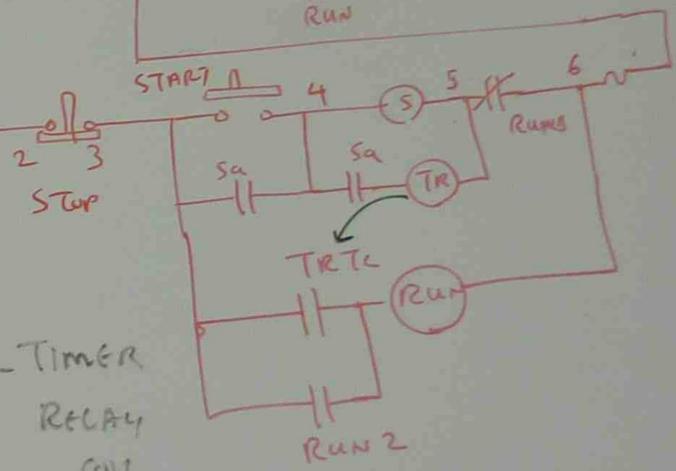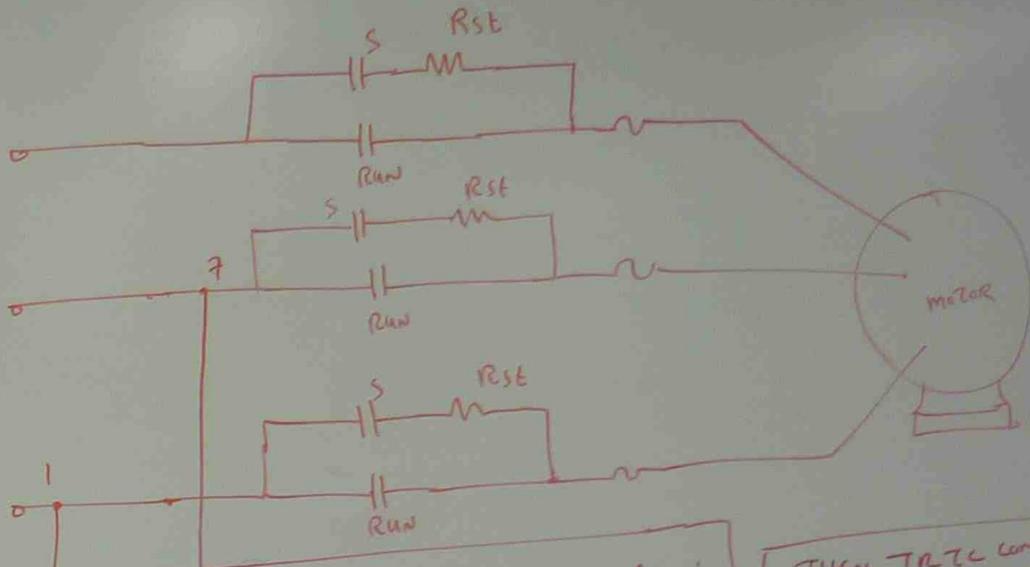

TR-TIMER
RELAY
COIL

TRC - TIMER RELAY
TIMING CONTACT
REDUCED

When TRC contact is closed.
It energizes RUN coil.
RUN coil close all RUN
contacts. motor is supplied
with full voltage.
Normally closed RUN contact
is opened. 5 coil loses the
supply. All 5 contacts
are opened.
RUN 2 contact also close
and TRC contact is then
bypassed.

STAR-DELTA STARTER

AT STARTING, MOTOR WINDING MUST BE CONNECTED IN STAR TO START WITH REDUCED VOLTAGE.


AT THE RUNNING, MOTOR WINDING MUST BE CONNECTED IN DELTA TO RUN WITH FULL VOLTAGE.

THE SWITCH WHICH CAN OPERATE NORMALLY CLOSED & NORMALLY OPEN CONTACTS IS REQUIRED FOR STAR HOLDING COIL AND DELTA HOLDING COIL SO THAT STAR CONTACTS AND DELTA CONTACTS WILL NOT CLOSE AT THE SAME TIME.

OPERATION

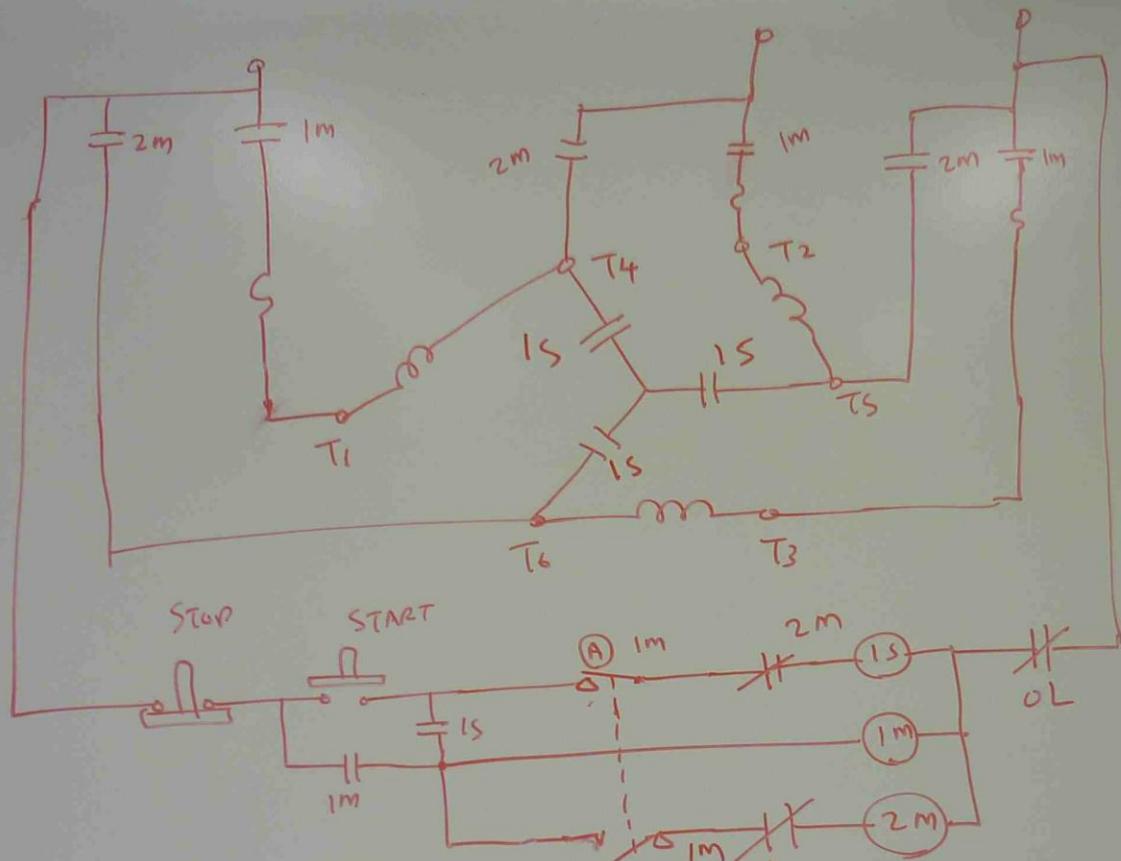- WHEN THE START SWITCH IS PRESSED, THE CURRENT WILL FLOW THROUGH STOP, START, (A) I_m , $2I_m$, (IS) COIL.
- ALL IS CONTACTS ARE CLOSED. THE CURRENT ALSO PASSES THROUGH (I_m) COIL. ALL I_m CONTACTS ARE ALSO CLOSED. MOTOR STARTS WITH λ CONNECTION.
- (I_m) COIL TRIES TO OPEN A I_m CONTACT BUT IT IS CLOSED AFTER SOME TIME. WHEN A I_m IS OPEN, B I_m IS CLOSED.





2M coil also open
 the normally closed
 2M contactor 1

1S coil is de-energized
 all 1S contacts are
 open.

STARTING, 1M, 1S closes
RUNNING, 1M, 2M closes, 1S open

Thus 2M coil is energized and 2M contacts
 are closed. Motor runs at delta

- WHEN START BUTTON IS PRESSED, CURRENT FLOWS FROM 1-2-3-4-5-6 AND ENDS AT 7.

- (1S) COIL IS ENERGIZED. IT CLOSSES ALL 1S CONTACTS. THEN (2S) COIL IS ENERGIZED. 2(S) CONTACTS ARE CLOSED

- CLOSING OF 1(S), 2(S) CONTACTS ENERGIZES TRANSFORMER WINDING.

- 7% VOLTAGE IS APPLIED TO MOTOR TERMINAL. MOTOR STARTS WITH REDUCED VOLTAGE.

- 2(S) COIL CLOSSES TIME DELAY CONTACT

2(S). THEN (R) COIL IS ENERGIZED.

R CONTACTS ARE CLOSED. MOTOR RUNS AT FULL VOLTAGE.

NORMALLY CONTACT R POINT (A) IS OPEN


(1S) COIL IS DE-ENERGIZED AND IT OPENS

(1S), 2(S) CONTACTS.

- TRANSFORMER IS REMOVED FROM SUPPLY

- VEL SW IS ATTACHED TO MOTOR SHAFT. IT IS CLOSED ONLY MOTOR RUNNING TIME. BY THIS WAY MOTOR WINDING WILL NOT GET FULL VOLTAGE WITHOUT RUNNING.

AUTOMATIC AUTO TRANSFORMER STARTER

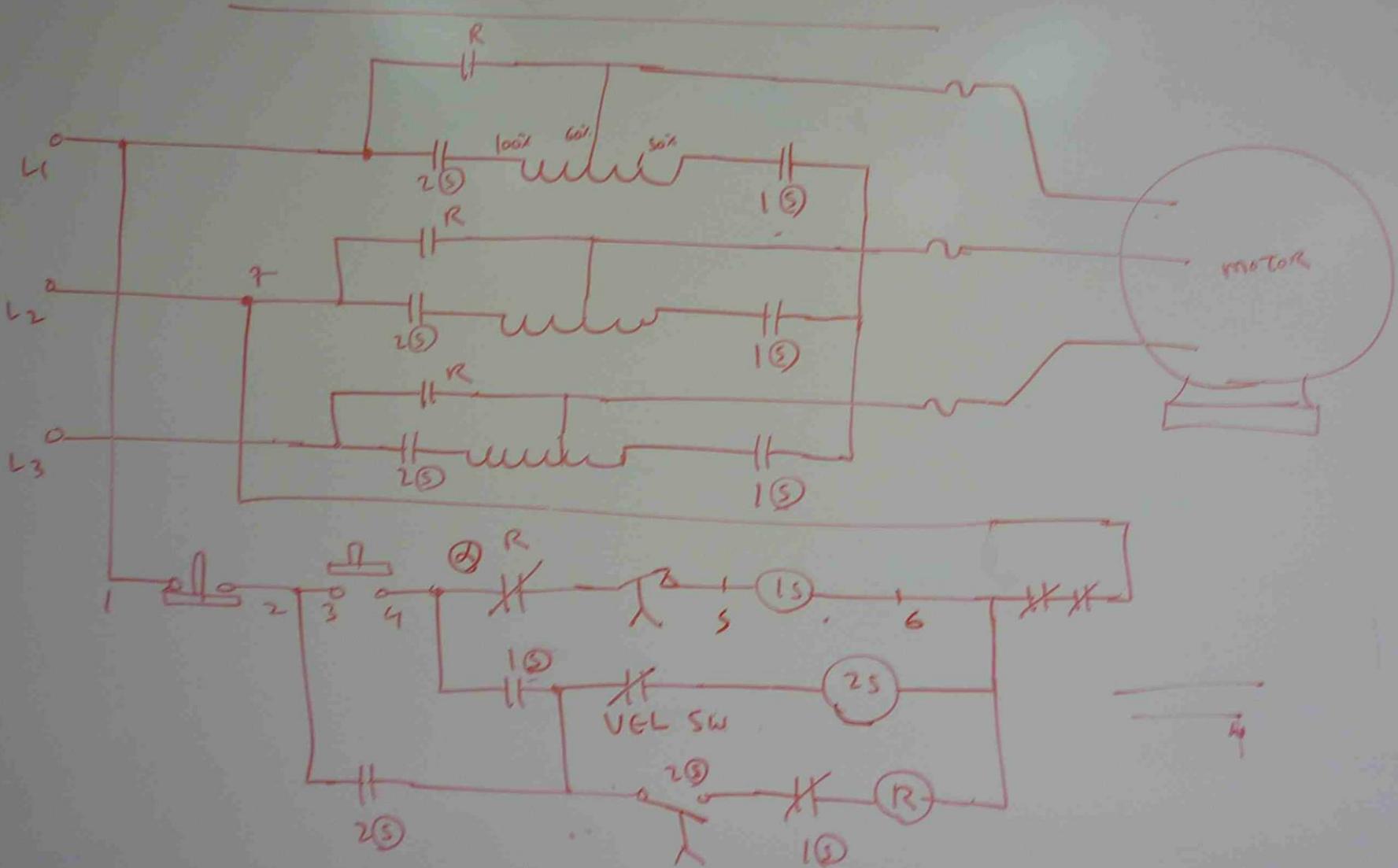

- WHEN START BUTTON IS PRESSED, CURRENT FLOWS FROM 1-2-3-4-5-6 AND ENDS AT 7.

- (1S) COIL IS ENERGIZED. IT CLOSSES ALL 1S CONTACTS. THEN (2S) COIL IS ENERGIZED. 2(S) CONTACTS ARE CLOSED

- CLOSING OF 1(S), 2(S) CONTACTS ENERGIZES TRANSFORMER WINDING.

- 7. VOLTAGE IS APPLIED TO MOTOR TERMINAL. MOTOR STARTS WITH REDUCED VOLTAGE.

- 2(S) COIL CLOSSES TIME DELAY CONTACT 2(S). THEN (R) COIL IS ENERGIZED.

R CONTACTS ARE CLOSED. MOTOR RUNS AT FULL VOLTAGE.

NORMALLY CONTACT R POINT (d) IS OPEN



(1S) COIL IS DE-ENERGIZED AND IT OPENS

(1S), 2 (S) CONTACTS.

- TRANSFORMER IS REMOVED FROM SUPPLY

- VEL SW IS ATTACHED TO MOTOR SHAFT. IT IS CLOSED ONLY MOTOR RUNNING TIME. BY THIS WAY MOTOR WINDING WILL NOT GET FULL VOLTAGE WITHOUT RUNNING.

CONSEQUENT POLE STARTER

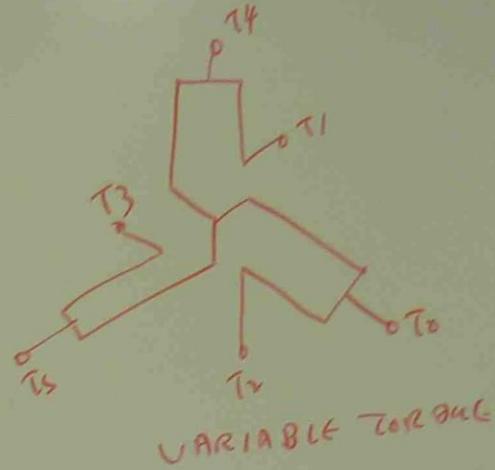
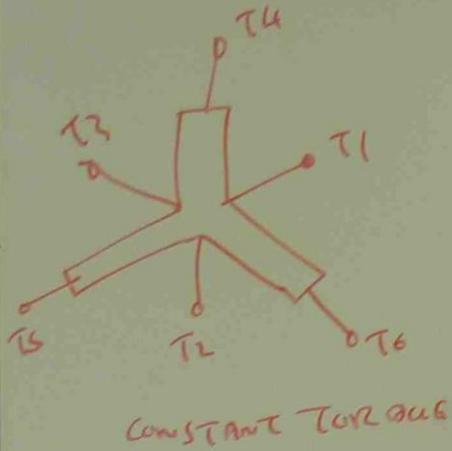



SPEED	SUPPLY LINE			OPEN	TOGETHER
	L ₁	L ₂	L ₃		
LOW	T ₁	T ₂	T ₃	T ₄ T ₅ T ₆	NONE
HIGH	T ₆	T ₄	T ₅	NONE	T ₁ T ₂ T ₃

SOLID STATE REGULATED VOLTAGE STARTER







SILICON CONTROLLED RECTIFIER (SCR)

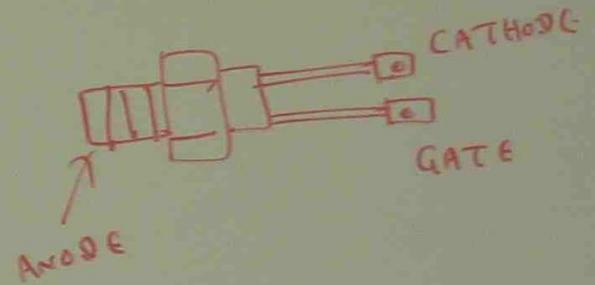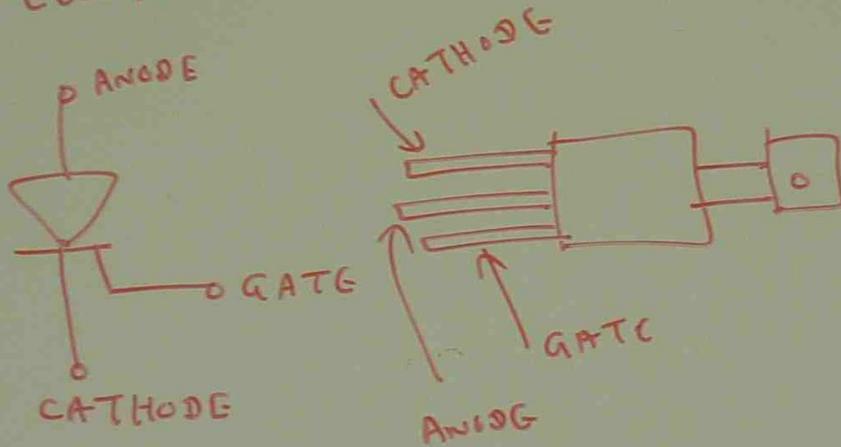THE SILICON CONTROLLED RECTIFIER (SCR / THYRISTOR) IS THE DEVICE USED MOST OFTEN TO CONTROL THE ELECTRIC MOTORS



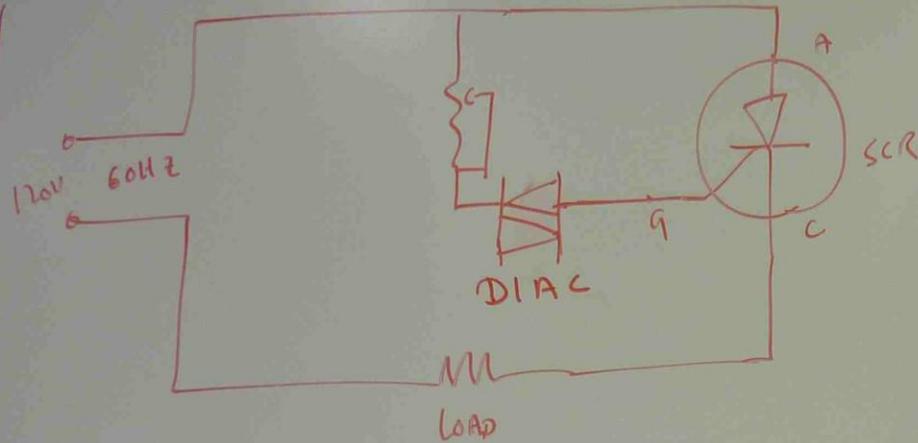

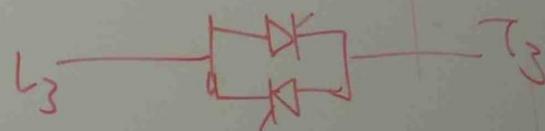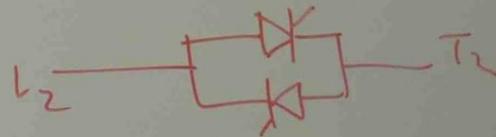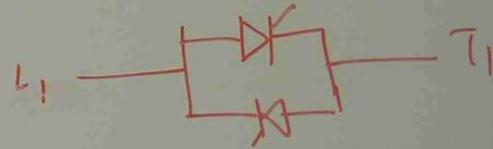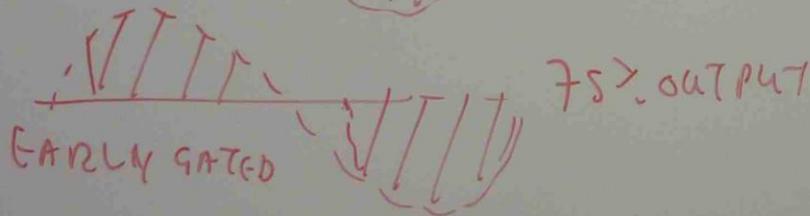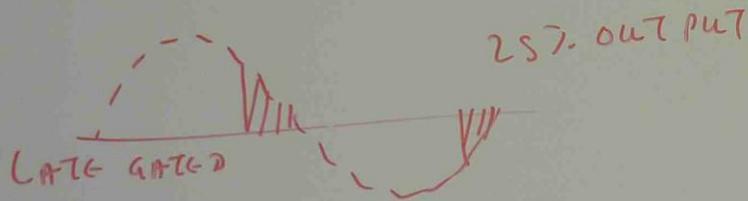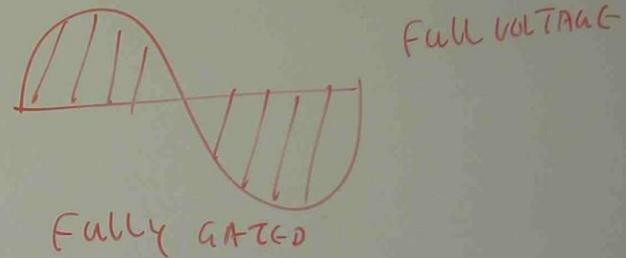DEPENDING ON TIME TO APPLY THE PULSE, GATE CONDUCTION VARIES MOTOR SPEED IS CONTROLLED BY GATE CONDUCTION.




3 ϕ SYSTEM


WOUND ROTOR MOTOR

THE WOUND ROTOR MOTOR IS DIFFERENT FROM THE SCRAPPEL CAGE MOTOR IT HAS THE WIRE COIL WINDINGS IN IT'S ROTOR INSTEAD OF A SERIES OF CONDUCTING BARS IN ROTOR. INSERTING THE EXTERNAL RESISTANCE IN THE MOTOR CIRCUIT WHEN THE STARTING WILL DEVELOP A HIGH TORQUE WITH A COMPARATIVELY LOW STARTING CURRENT.

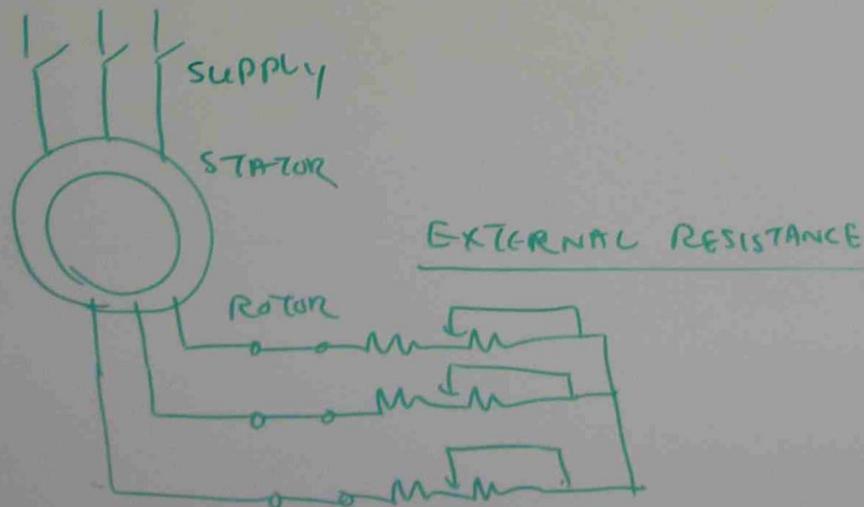AS THE MOTOR COMES UP TO SPEED, THE RESISTANCE IS GRADUALLY REMOVED. AT THE FULL SPEED, THE ROTOR IS SHORT CIRCUITED. SPEED CAN BE REGULATED WITHIN THE SPEED BY VARYING THE AMOUNT OF RESISTANCE



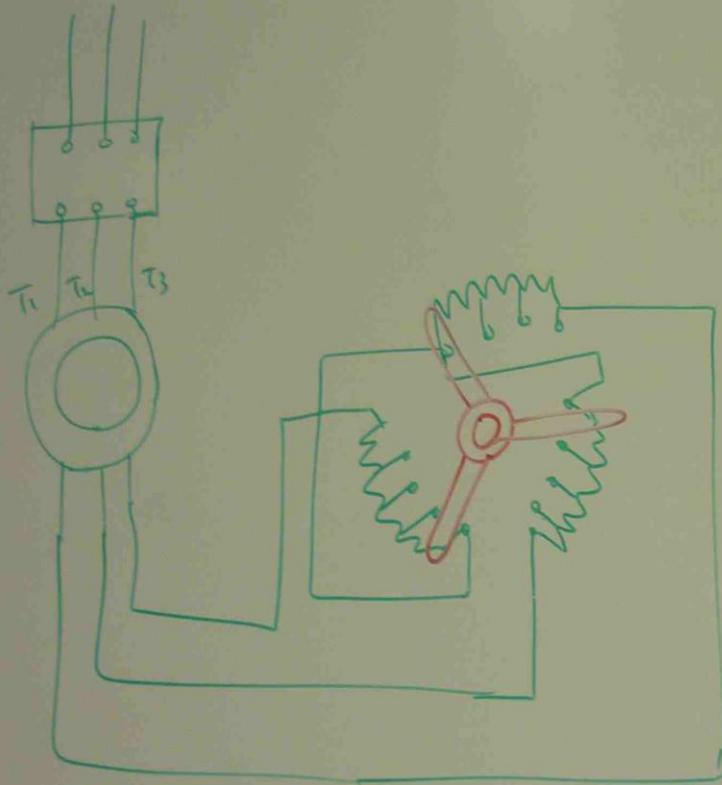STARTER CONTROLLER WITH WOUND ROTOR MOTOR



DRUM CONTROLLER

SPEED REGULATION BY RESISTANCE

RESISTORS CAN BE USED TO REGULATE THE SPEED IF THEY ARE OF PROPER SIZE TO PREVENT THE OVERHEATING FROM CONSTANT USE.

THE RESISTORS USED IN THE STARTING PERIOD ARE USED ONLY FOR A SHORT TIME. BUT THOSE USED FOR CONTINUOUS MOTOR SPEED REGULATION ARE IN USE FOR LONGER PERIOD OF TIME.

- BY PLACING A HIGH RESISTANCE IN THE ROTOR CIRCUIT, IT IS POSSIBLE TO START THE MOTOR AND PRODUCE HIGH STARTING TORQUE WITH LOW STARTING CURRENT.


TYPE OF STARTERS

MULTI SWITCH STARTER

DRUM CONTROLLER

MAGNETIC STARTER

MULTI SWITCH STARTER

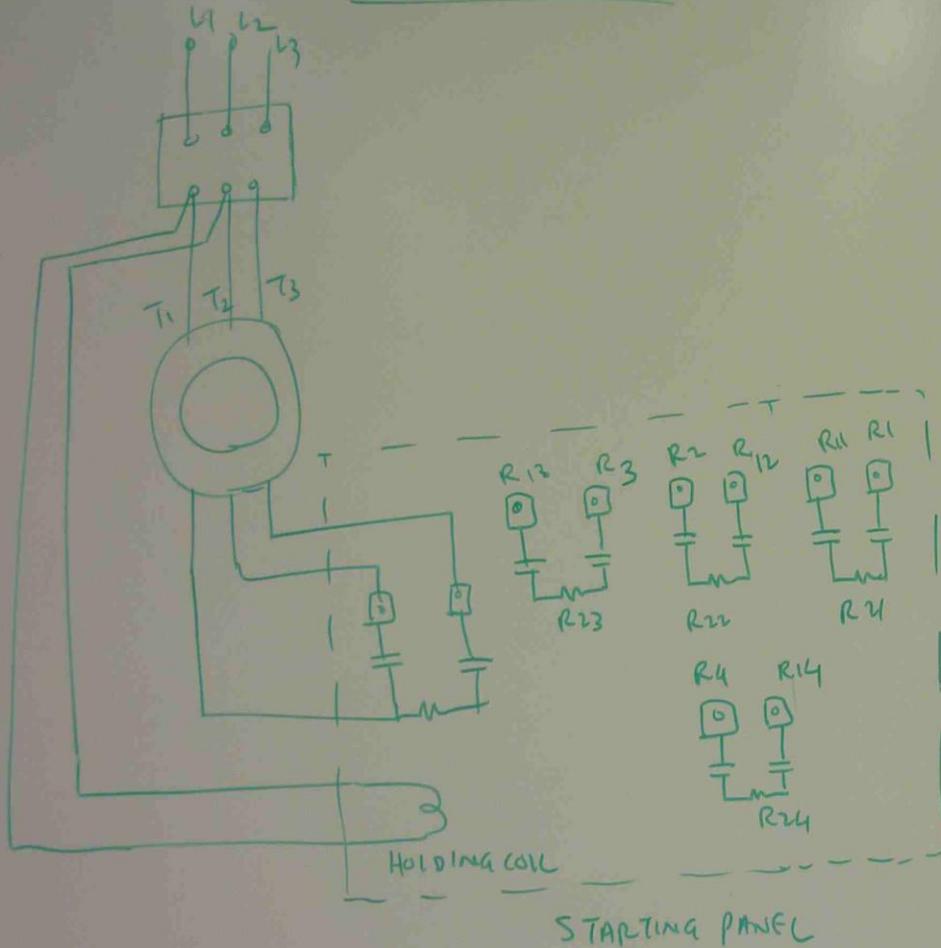

- THIS TYPE OF STARTER IS USED IN THE SECONDARY CIRCUIT OF LARGE WOUND ROTOR INDUCTION MOTOR UP TO 2000 HP WITH ROTOR CURRENT UP TO 1000 AMP.

- CONTACT LEVERS (DOUBLE POLE) ARE CLOSED IN A PRE-DETERMINED SEQUENCE MECHANICALLY.

- WHEN THE FINAL SWITCH HAS BEEN CLOSED, IT IS HELD IN A PLACE BY A MAGNETIC COIL.

DRUM CONTROLLERS

DRUM CONTROLLERS CAN BE USED FOR STARTING AND FOR SPEED CONTROL OF THE WOUND ROTOR MOTOR.

THEY ARE MADE TO HANDLE BOTH STATOR AND ROTOR CIRCUITS.

APPLICATION OF SLIP RING MOTORS

USE WITH MOTOR DRIVEN CONTROLLERS IN LARGE AIR CONDITIONING PLANTS, BLOWERS STOCKER.

WOUND ROTOR MOTOR CAN BE STARTED WITH A LOAD AND WITHOUT DRAWING TOO MUCH CURRENT. THEY CAN BE USED FOR SUCH LOADS AS THOSE BACK PRESSURE SETUP BY FLUIDS AND GASES. THEY ARE ALSO USED IN ELEVATORS AND CRANES. THEY CAN ALSO BE USED FOR THE PLACE WHERE SPEED RANGE IS SMALL (COMPRESSOR / CONVEYER)

DISADVANTAGE

- HIGHER INITIAL COST
- SLIP RINGS AND BRUSHES NEED MAINTENANCE FROM TIME TO TIME
- RESISTORS AND SWITCHING ARRANGEMENT REQUIRE PERIODIC INSPECTION & MAINTENANCE.

ADVANTAGE OF SQUIRREL CAGE INDUCTION MOTOR

EXCELLENT PROPERTIES FOR SPEED ABOVE 600 RPM


DISADVANTAGE

- SPEED CONTROL IS DIFFICULT
- ADDITIONAL REDUCED CURRENT / VOLTAGE STARTING IS REQUIRED

- AT LOWER SPEED, THEY CAN BE HEAVY, COSTLY, LOW PERFORMANCE LOW EFFICIENCY.

FREQUENCY / SPEED CONTROL

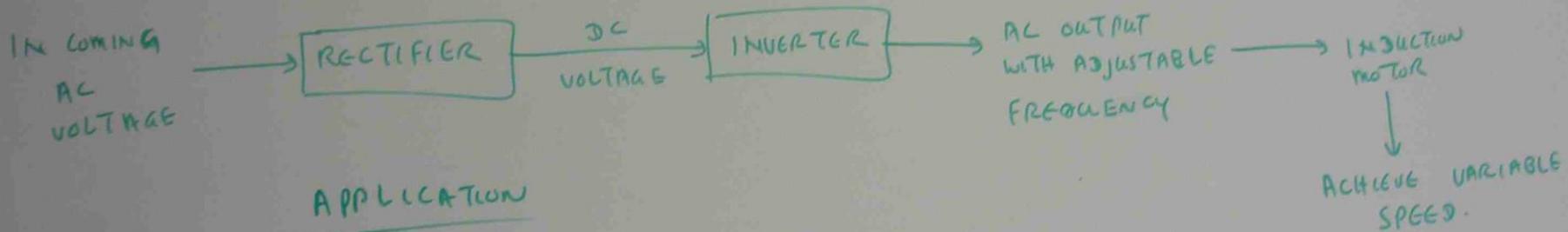SOLID STATE AC MOTOR CONTROL IS ACCOMPLISHED BY CHANGING THE FREQUENCY OF THE POWER SOURCE. MOTOR SPEED IS ADJUSTED BY CONTROLLING THE OUTPUT VOLTAGE AND FREQUENCY OF THE UNIT.



APPLICATION


FOOD PACKING PLANT

PAPER MILL

CEMENT PLANT

CENTRIFUGAL PUMP

BLOWERS.

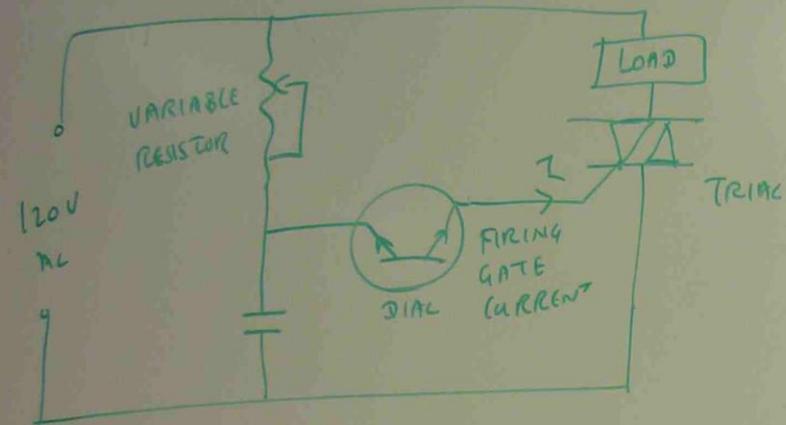

VARIABLE FIRING GATE CURRENT IS CONTROLLED BY VARIABLE RESISTOR.

MULTI SPEED STARTERS

AUTO MATIC CONTROL OF THE SPEEDS.

- LOW SPEED COMPELLING RELAY
- AUTOMATIC SEQUENCE ACCELERATING RELAY
- AUTOMATIC SEQUENCE DECELERATING RELAY

MOTOR PROTECTION

- PROTECTION AGAINST LOW VOLTAGE
- TIME DELAY PROTECTION
- LIGHTNING P PROTECTION
- SURGE SUPPRESSOR

WHEN SOLID STATE CONTROLS ARE UTILIZED IN CIRCUITS THAT HAVE ELECTROMAGNETIC DEVICES, THERE ARE PROBLEMS WITH THE POWER SOURCE.

SURGE SUPPRESSORS ARE UTILIZED TO LIMIT THE VOLTAGE TRANSIENTS FOR APPLICATIONS REQUIRING INTERFACE WITH SOLID STATE COMPONENTS.

LIGHTNING PROTECTION


SURGE ARRESTERS

- 1500A AT 2200V
- 5000A AT 2900V
- 10,000A AT 3400V
- 20,000A AT 4000V

JOGGING, PLUGGING, BRAKING


JOGGING

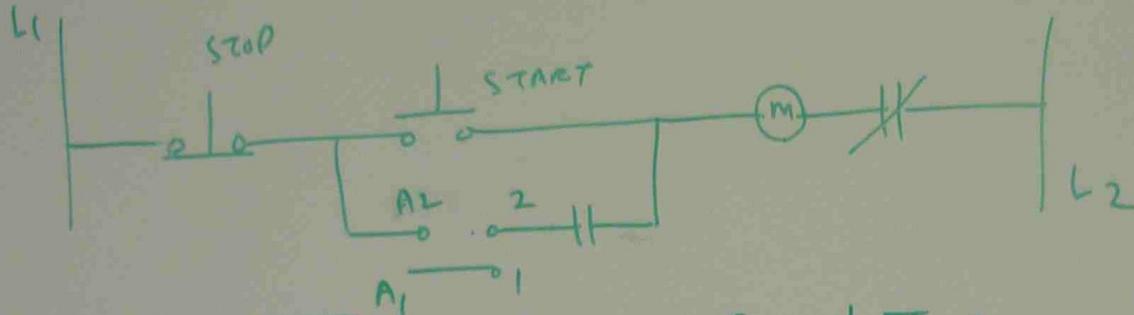MOMENTARY OPERATION OF A MOTOR FROM REST FOR THE PURPOSE OF ACCOMPLISHING SMALL MOVEMENT OF DRIVEN MACHINE.




RUN | JOG

A ₁	1	
A ₂		1
	JOG	RUN

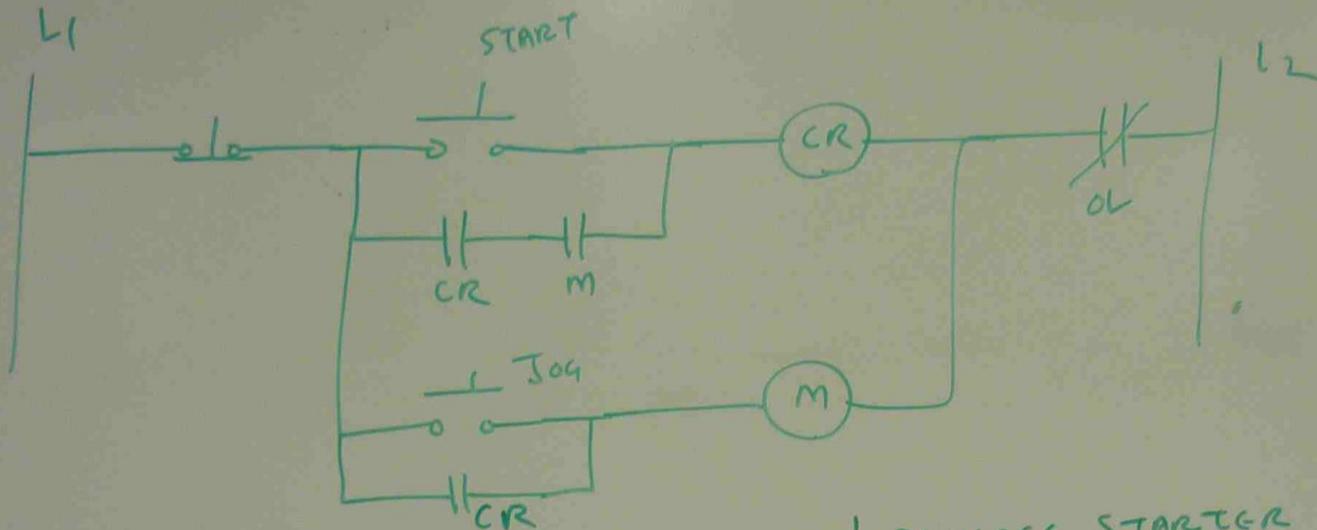

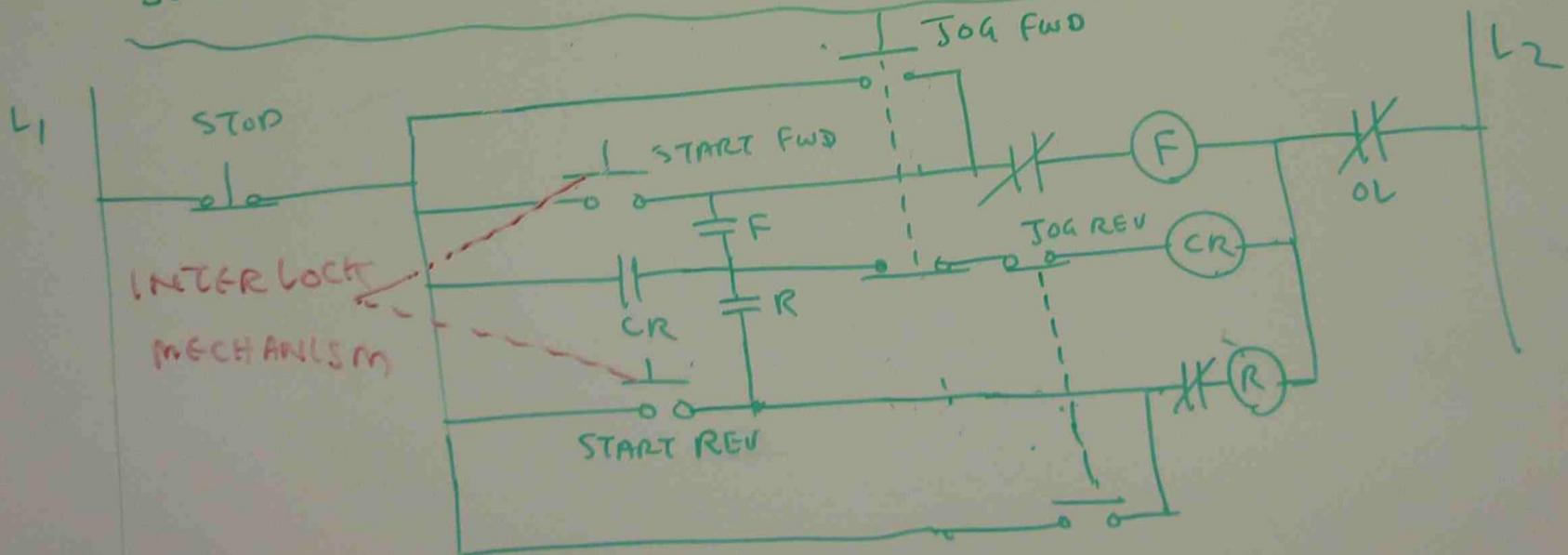JOGGING USING A FORWARD / REVERSE STARTER





PLUGGING

A SYSTEM OF BRAKING IN WHICH THE MOTOR CONNECTIONS ARE REVERSED SO THAT THE MOTOR DEVELOPS A COUNTER TORQUE.

MOTOR IS RUN IN ONE DIRECTION ONLY AND MUST COME TO COMPLETE A STOP WHEN THE STOP BUTTON IS PRESSED.

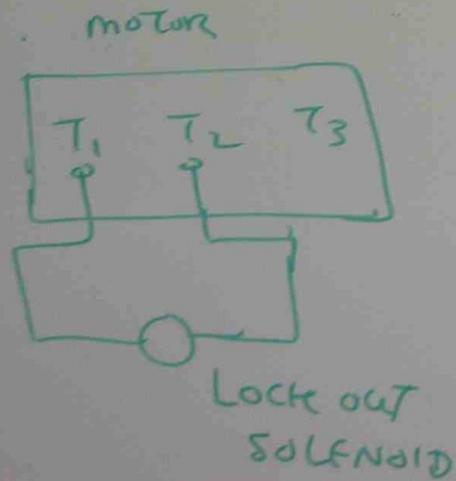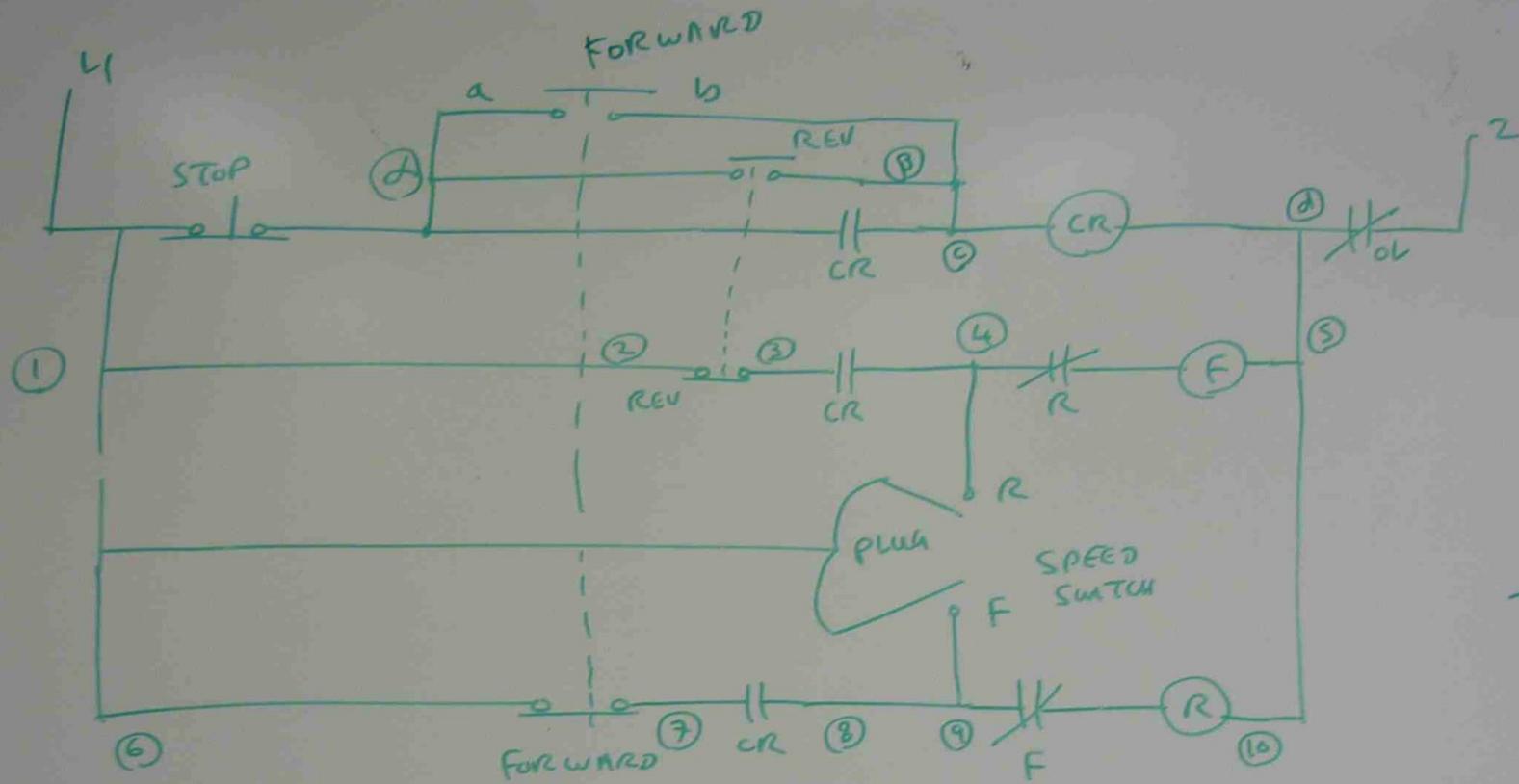REVERSE CONTACTOR OF THE REVERSING SWITCH IS USED ONLY FOR PLUG STOPPING AND NOT FOR RUNNING IN REVERSE.



FORWARD RUNNING

- PRESS FORWARD SWITCH

- CURRENT FLOWS a, b, c, d AND (CR) IS ENERGIZED

CR CONTACTS ARE CLOSED.

THEN THE CURRENT FLOWS (1)(2)(3)(4)(5)

(F) COIL IS ENERGIZED ~~X~~ F IS OPEN.

MOTOR RUN WITH FORWARD

OPENING OF ~~X~~ F PREVENTS (R) COIL TO BE ENERGIZED.

REVERSE RUNNING

PRESS REVERSE SWITCH

CURRENT FLOWS d, c, b, a AND (CR) IS ENERGIZED.

CR CONTACTS ARE CLOSED

CURRENT FLOWS (6)(7)(8)(9)(10) AND (R) COIL IS ENERGIZED.

~~X~~ R IN SERIES WITH (F) IS OPEN

MOTOR RUNS IN REVERSE

OPENING OF ~~X~~ R PREVENTS (F) COIL TO BE ENERGIZED

REVERSE RUNNING

PRESS REVERSE SWITCH

CURRENT FLOWS α , β , c , d AND \textcircled{CR} IS ENERGIZED.

CR CONTACTS ARE CLOSED

CURRENT FLOWS $\textcircled{6}$ $\textcircled{7}$ $\textcircled{8}$ $\textcircled{9}$ $\textcircled{10}$ AND \textcircled{R} COIL IS ENERGIZED.

X_R IN SERIES WITH \textcircled{F} IS OPEN

MOTOR RUNS IN REVERSE

OPENING OF X_R PREVENTS \textcircled{F} COIL TO BE ENERGIZED

TO STOP IMMEDIATELY
WHILE RUNNING FORWARD

PRESS STOP AND F-PLUG SWITCH

\textcircled{R} COIL WILL BE ENERGIZED AND TRIES TO TURN THE MOTOR IN OPPOSITE DIRECTION

AS SOON AS MOTOR STOPS, LOCK OUT SOLENOID DEACTIVATES PLUG SWITCH

TO STOP IMMEDIATELY, WHILE
RUNNING REVERSE

PRESS STOP AND R-PLUG SWITCH

\textcircled{F} COIL WILL BE ENERGIZED AND TRIES TO RUN MOTOR IN OPPOSITE DIRECTION.

THEN MOTOR
WILL STOP
IMMEDIATELY


BRAKING

ELECTRIC MOTORS CAN BE BROUGHT TO STOP OR BRAKED BOTH ELECTRICALLY AND MECHANICALLY.

DYNAMIC BRAKING

DYNAMIC BRAKING OF AN AC INDUCTION MOTOR IS GENERALLY ACCOMPLISHED BY EXCITING ITS STATOR WINDING WITH DC CURRENT. THE AMOUNT OF BRAKING TORQUE IS DIRECTLY PROPORTIONAL TO DC CURRENT PASSING THROUGH THE STATOR WINDING OF THE MOTOR.

EX MOTOR
WILL STOP
IMMEDIATELY

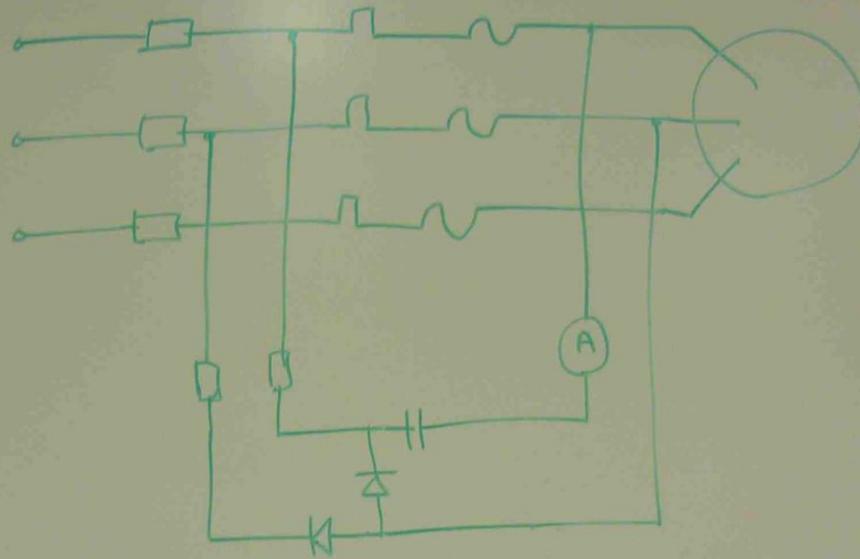

ADVANTAGE

NO FRICTION / WEAR / MAINTENANCE
 ADJUSTABLE / SOFT START CAPACITY

DISADVANTAGE

ELECTRIC MOTOR BRAKE WILL NOT STOP
 THE MOTOR IF POWER IS LOST OR
 DISCONNECTED.

MECHANICAL BRAKING


ELECTRO MAGNET HOLDS THE BRAKE SHOE AWAY FROM THE MOTOR SHAFT WHENEVER THE MOTOR IS ENERGIZED

MAGNETIC BRAKE

REQUIRES TORQUE TO STOP THE MOTOR
(BRAKE TORQUE)

$$= \frac{\text{RATED HP} \times 5252}{\text{RATED RPM}}$$

HYDRAULIC BRAKE

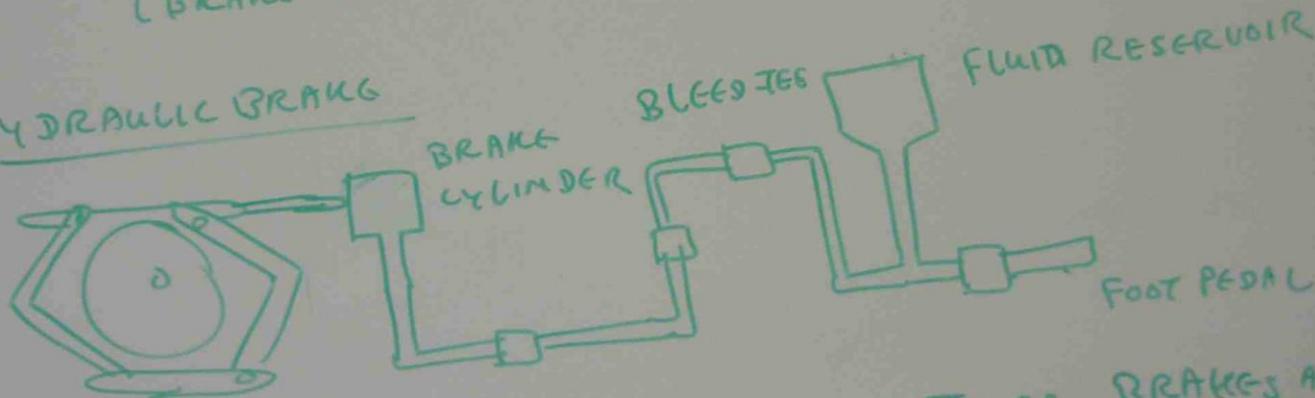

- HYDRAULICALLY APPLIED SHOE TYPE BRAKES ARE USED
- USED FOR CRANE, TRAVEL DEVICE, MILL MACHINING, CONVEYORS.