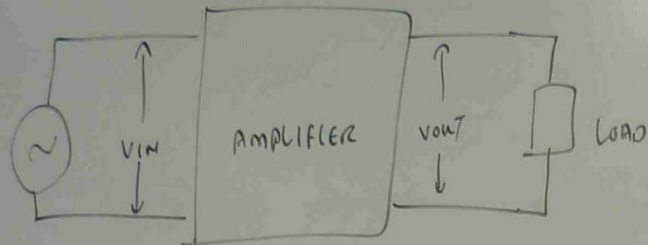


INPUT  
OUTPUT

SIGNAL  
SOURCE



INPUT AND OUTPUT CONNECTION TO  
AMPLIFIER.

GAIN

AN AMPLIFIER CAN PRODUCE A GAIN IN THE  
SIGNAL VOLTAGE, CURRENT AND POWER

$$A_v = \frac{V_{out}}{V_{in}}$$

$A_v$  = VOLTAGE GAIN

$V_{in}$  = INPUT VOLTAGE

$V_{out}$  = OUTPUT VOLTAGE

$$A_i = \frac{I_{out}}{I_{in}}$$

$$A_p = \frac{P_{out}}{P_{in}}$$

P.V.

GAIN IN d.B (DECIBEL) UNIT

POWER GAIN IN dB

$$dB = 10 \log \frac{P_{out}}{P_{in}}$$

VOLTAGE GAIN IN dB

$$dB = 20 \log \frac{V_{out}}{V_{in}}$$

CURRENT GAIN IN dB

$$dB = 20 \log \frac{I_{out}}{I_{in}}$$

ph

AN AMPLIFIER DEVELOPS 10W FOR AN INPUT POWER OF 1mW  
CALCULATE THE POWER GAIN OF AMPLIFIER IN dB.

$$\begin{aligned} \text{dB} &= 10 \log \frac{P_{\text{OUT}}}{P_{\text{IN}}} = 10 \log \frac{10}{1 \times 10^{-3}} = 10 \log 10 \times 10^3 \\ &= 10 \log 10^4 = 10 \times 4 \log 10 = 40 \text{ dB} \end{aligned}$$

ph



AN AMPLIFIER FED WITH 50mV SIGNAL PRODUCES A 2V  
OUT PUT. CALCULATE THE GAIN.

$$A_v = \frac{V_{\text{OUT}}}{V_{\text{IN}}} = \frac{2}{50 \times 10^{-3}} = \frac{2000}{50} = 40$$


# BIPOLAR JUNCTION TRANSISTORS


BJT- BIPOlar Junction TRANSISTOR

NPN PNP

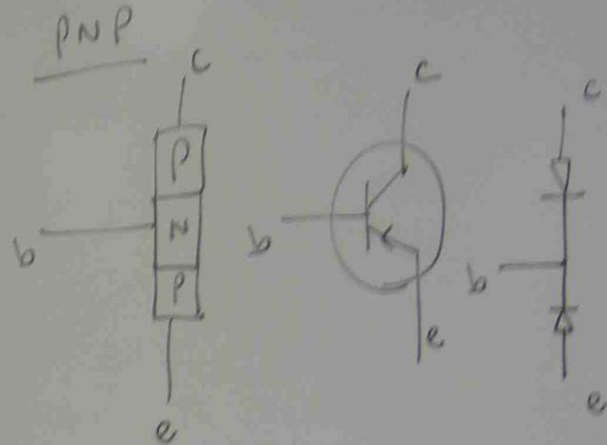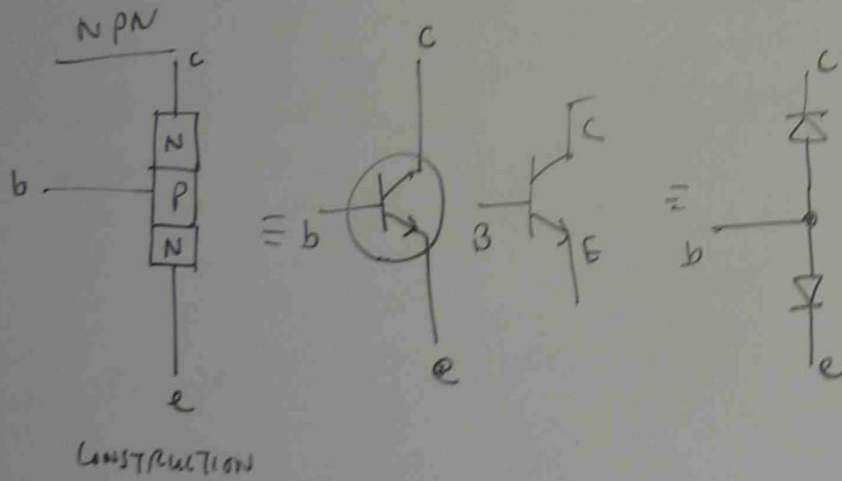

TRANSISTOR OPERATION


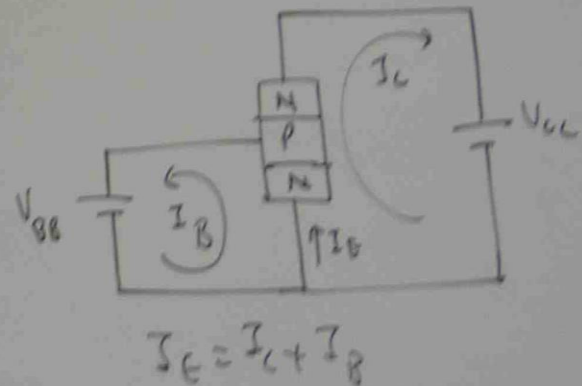


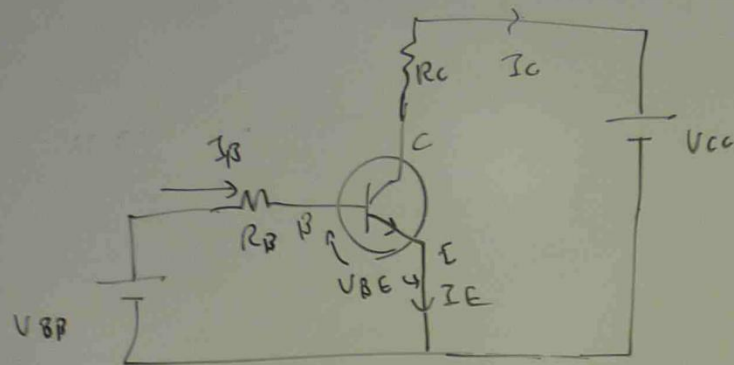


$$\alpha = \frac{I_C}{I_E}$$

$$\beta = \frac{I_C}{I_B}$$


### TRANSISTOR BIASING DIAGRAM

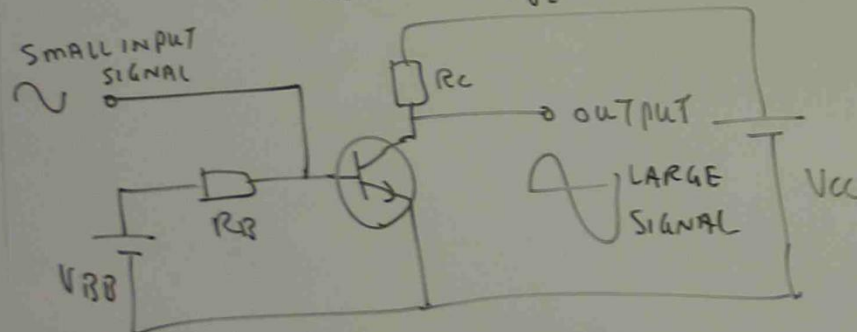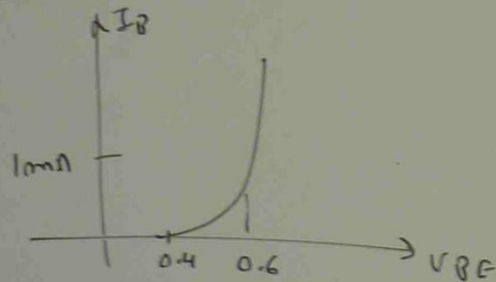

### DARLINGTON PAIR

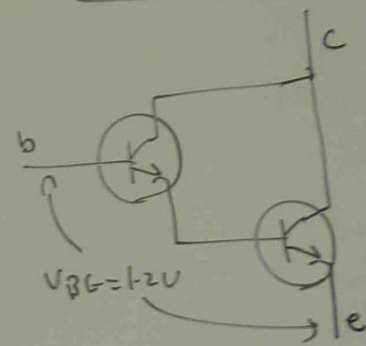

### NPN DARLINGTON PAIR

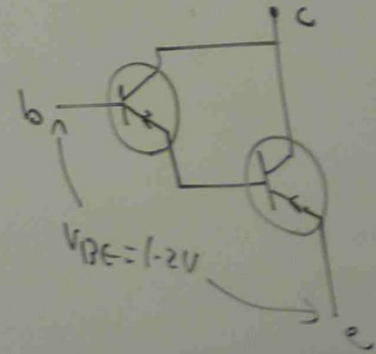

### PNP DARLINGTON PAIR

### CLASS A

- THIS TYPE OF AMPLIFIER PRODUCES AN OUTPUT OVER THE FULL CYCLE  $360^\circ$  OF INPUT CYCLE

### CLASS B

PRODUCE AN OUTPUT FOR ONLY  $\frac{1}{2}$  OF INPUT CYCLE  $180^\circ$

### CLASS A B



THIS TYPE COMPARE BETWEEN CLASS A & B

### CLASS C

THE TRANSISTOR CONDUCTS FOR LESS THAN  $180^\circ$  OF INPUT WAVE FORM.



## TRANSISTOR BIASING CIRCUITS

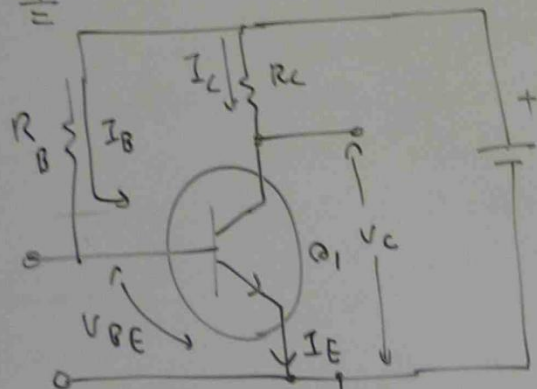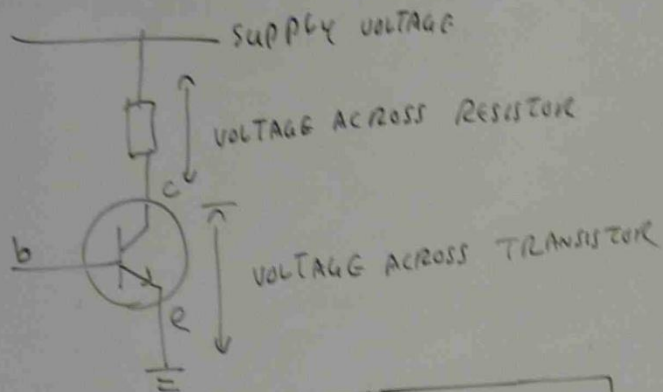

$V_{CE}$  - VOLTAGE AT COLLECTOR  
RESPECT TO BASE

$V_{BE}$  - VOLTAGE AT BASE RESPECT TO  
EMITTER

$V_{RE}$  - VOLTAGE  
ACROSS  
EMITTER  
RESISTOR

$V_{RB}$  - VOLTAGE  
ACROSS  
BASE RESISTOR

$V_{CC}$  - SUPPLY  
VOLTAGE

$V_{RC}$  - VOLTAGE ACROSS  
COLLECTOR RESISTOR

$V_{BE}$  - VOLTAGE ACROSS  
BASE RESPECT TO  
EMITTER

$I_C$  - COLLECTOR CURRENT

$I_B$  - BASE CURRENT

$I_E$  - EMITTER CURRENT.

$$I_B = \frac{V_C - 0.6}{R_B}$$

$$I_C = \beta I_B$$

$$I_E = I_C$$

$$V_E = 0 \text{ V}$$

$$V_B = 0.6 \text{ V}$$

$$V_C = V_{CC} - I_C R_C$$

