
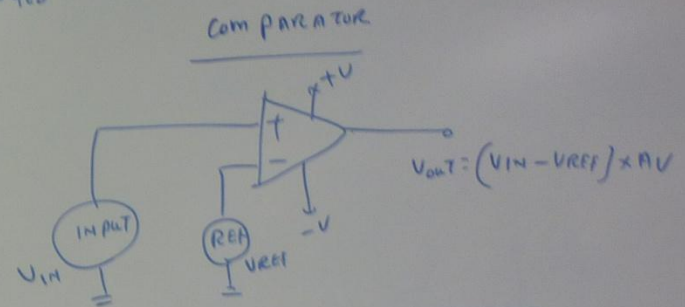


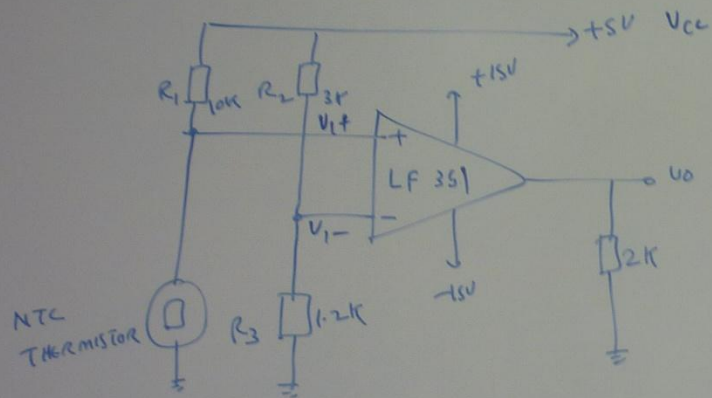Pb → AN NTC (NEGATIVE TEMPERATURE COEFFICIENT) THERMISTOR IS EMPLOYED TO CONTROL THE TEMPERATURE AS SHOWN BELOW



$$R_t = R_0(1 + \alpha \Delta t)$$

| TEMPERATURE (°C) | 20    | 25    | 30   | 35   | 40   | 45  | 50   | 55   | 60   | 65   | 70  | 75   | 80  |
|------------------|-------|-------|------|------|------|-----|------|------|------|------|-----|------|-----|
| R (KΩ)<br>(RNTC) | 9.5   | 8.2   | 6.8  | 5.7  | 4.9  | 4.3 | 3.7  | 3.3  | 3    | 2.7  | 2.5 | 2.3  | 2.2 |
| V <sub>I+</sub>  | 2.436 | 2.252 | 2.02 | 1.81 | 1.64 | 1.5 | 1.35 | 1.24 | 1.15 | 1.06 | 1   | 0.93 | 0.9 |

DRAW V<sub>I+</sub> GRAPH

$$V_{I(+)} = V_{CC} \times \frac{R_{NTC}}{R_1 + R_{NTC}}$$


$$V_{I(-)} = V_{CC} \times \frac{R_3}{R_2 + R_3}$$

IF  $R_{NTC} = 9.5 k\Omega$   
 $R_1 = 10 k$

$$V_{I(+)} = \frac{9.5}{10 + 9.5} \times 5 = 2.435$$

IF  $R_{NTC} = 8.2 k\Omega$   
 $R_1 = 10 k$
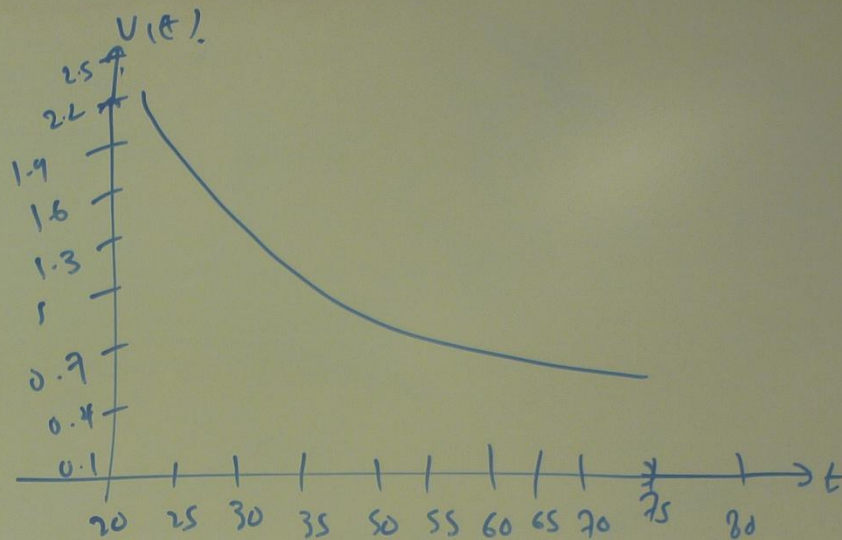
$$V_{I(+)} = \frac{8.2}{10 + 8.2} \times 5 = 2.252 \Omega$$



IN ABOVE PROBLEM

(i) CALCULATE INPUT VOLTAGE

$$V_{I(-)}$$

(ii) DETERMINE THE TRANSITION TEMPERATURE

(iii) DETERMINE THE VALUE OF  $R_3$  FOR  $70^\circ C$  TRANSITION TEMPERATURE

(iv) SHOW A RELAY INTERFACE CIRCUIT TO THE OUTPUT TERMINAL TO OPERATE A 240V HEATING ELEMENT.



$$V_{i(+)} = V_{cc} \times \frac{R_{NTC}}{R_1 + R_{NTC}}$$


$$V_{i(-)} = V_{cc} \times \frac{R_3}{R_2 + R_3}$$

IF  $R_{NTC} = 9.5 k\Omega$   
 $R_1 = 10 k$

$$V_{i(+)} = \frac{9.5}{10 + 9.5} \times 5 = 2.435$$

IF  $R_{NTC} = 8.2 k\Omega$   
 $R_1 = 10 k$
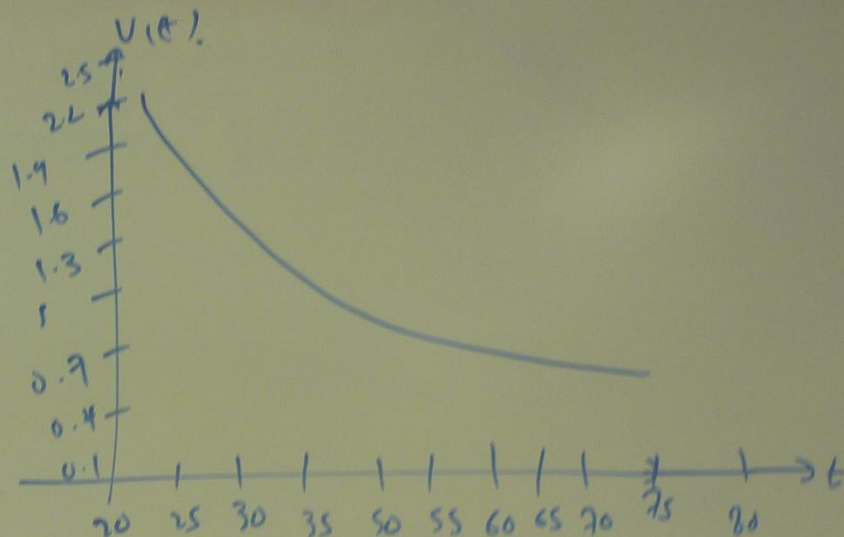
$$V_{i(+)} = \frac{8.2}{10 + 8.2} \times 5 = 2.252$$



IN ABOVE PROBLEM

(i) CALCULATE INVERTING INPUT VOLTAGE

$$V_{i(-)}$$

(ii) DETERMINE THE TRANSITION TEMPERATURE

(iii) DETERMINE THE VALUE OF  $R_3$  FOR  $70^\circ C$  TRANSITION TEMPERATURE

(iv) SHOW A RELAY INTERFACE CIRCUIT TO THE OUTPUT TERMINAL TO OPERATE A 240V HEATING ELEMENT.

$$(k) V_1(-) = V_{cc} \times \frac{R_3}{R_3 + R_2}$$

$$(i) = 5 \times \frac{1.2}{1.2 + 3}$$

$$= 1.043 \text{ V}$$

$$\text{AT } 50^\circ\text{C}, V_1(+) < V_1(-)$$

1.35V      1.43V

(ii)  $50^\circ\text{C}$  IS TRANSITION TEMPERATURE

FOR  $70^\circ\text{C}$  TEMPERATURE TO  
BECOME TRANSITION TEMPERATURE

$V_1(-)$  MUST BE AT LEAST 1V

$$V_1(-) = V_{cc} \times \frac{R_3}{R_2 + R_3}$$


$$1 = 5 \times \frac{R_3}{R_3 + 3}$$

$$1 = \frac{5R_3}{R_3 + 3}$$

$$R_3 + 3 = 5R_3$$



$$4R_3 = 3$$

$$R_3 = 0.75 \text{ k}\Omega$$

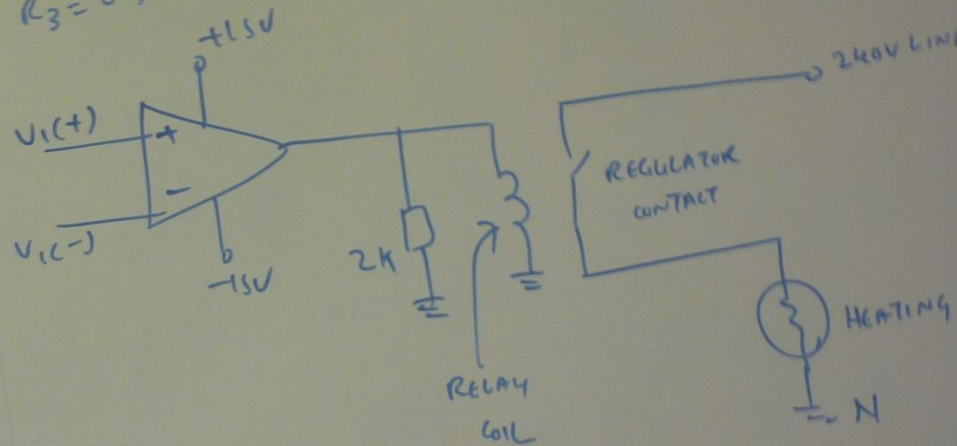



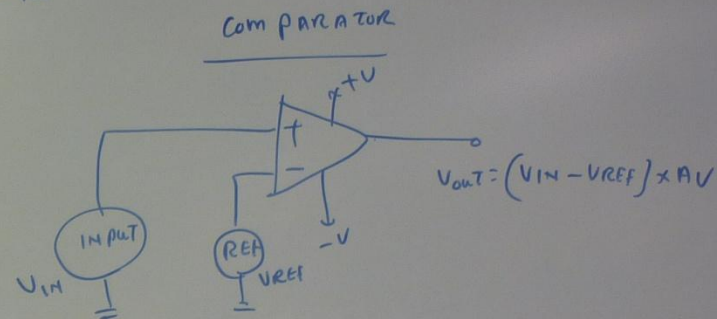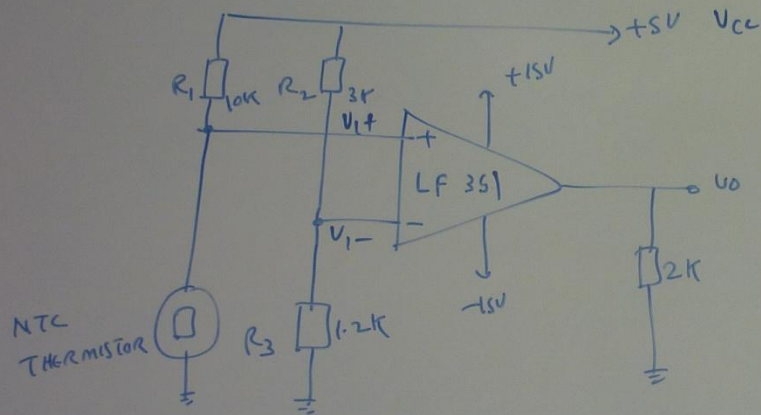pb AN NTC (NEGATIVE TEMPERATURE COEFFICIENT) THERMISTOR IS EMPLOYED TO CONTROL THE TEMPERATURE AS SHOWN BELOW



$$R_t = R_0(1 + \alpha \Delta T)$$

| TEMPERATURE (°C) | 20    | 25    | 30   | 35   | 40   | 45  | 50   | 55   | 60   | 65   | 70  | 75   | 80  |
|------------------|-------|-------|------|------|------|-----|------|------|------|------|-----|------|-----|
| R (kΩ)<br>(RNTC) | 9.5   | 8.2   | 6.8  | 5.7  | 4.9  | 4.3 | 3.7  | 3.3  | 3    | 2.7  | 2.5 | 2.3  | 2.2 |
| V <sub>1+</sub>  | 2.436 | 2.252 | 2.02 | 1.81 | 1.64 | 1.5 | 1.35 | 1.24 | 1.15 | 1.06 | 1   | 0.93 | 0.9 |

DRAW V<sub>1+</sub> GRAPH

$$V_{in} - V_{REF} \times AV$$

$$V_{I(+)} = V_{CC} \times \frac{R_{NTC}}{R_1 + R_{NTC}}$$


$$V_{I(-)} = V_{CC} \times \frac{R_3}{R_2 + R_3}$$

IF  $R_{NTC} = 9.5 k\Omega$   
 $R_1 = 10 k\Omega$

$$V_{I(+)} = \frac{9.5}{10 + 9.5} \times 5 = 2.435$$

IF  $R_{NTC} = 8.2 k\Omega$   
 $R_1 = 10 k\Omega$
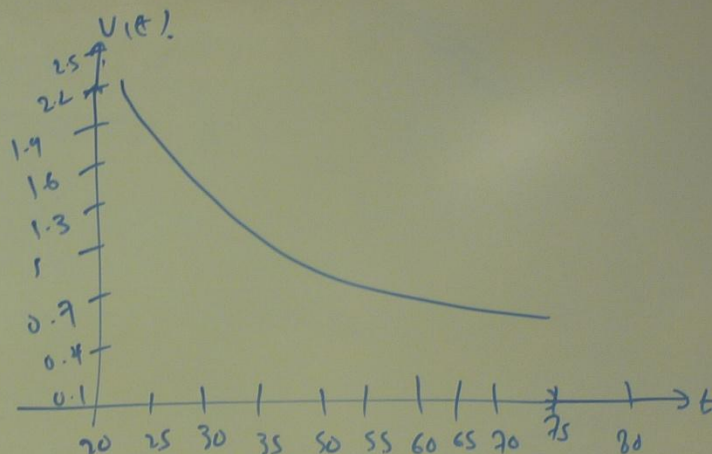
$$V_{I(+)} = \frac{8.2}{10 + 8.2} \times 5 = 2.252$$



IN ABOVE PROBLEM

(i) CALCULATE INVERTING INPUT VOLTAGE

$$V_{I(-)}$$

(ii) DETERMINE THE TRANSITION TEMPERATURE

(iii) DETERMINE THE VALUE OF  $R_3$  FOR  $70^\circ C$  TRANSITION TEMPERATURE

(iv) SHOW A RELAY INTERFACE CIRCUIT TO THE OUTPUT TERMINAL TO OPERATE A 240V HEATING ELEMENT.

(b) V  
 (i)

AT SO

(ii) so c

(iii)



$$\begin{aligned}
 (b) \quad V_1(-) &= V_{cc} \times \frac{R_3}{R_2 + R_3} \\
 (i) \quad &= 5 \times \frac{1.2}{1.2 + 3} \\
 &= 1.043 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 \text{AT } 50^\circ\text{C}, \quad V_1(+) &< V_1(-) \\
 1.35 \text{ V} \quad &1.43 \text{ V}
 \end{aligned}$$

(ii)  $50^\circ\text{C}$  IS TRANSITION TEMPERATURE

(iii) FOR  $70^\circ\text{C}$  TEMPERATURE TO  
BECOME TRANSITION TEMPERATURE  
 $V_1(-)$  MUST BE AT LEAST 1V


$$\begin{aligned}
 V_1(-) &= V_{cc} \times \frac{R_3}{R_2 + R_3} \\
 1 &= 5 \times \frac{R_3}{R_3 + 3}
 \end{aligned}$$


$$1 = \frac{5R_3}{R_3 + 3}$$

$$R_3 + 3 = 5R_3$$

$$4R_3 = 3$$

$$R_3 = 0.75 \text{ k}\Omega$$

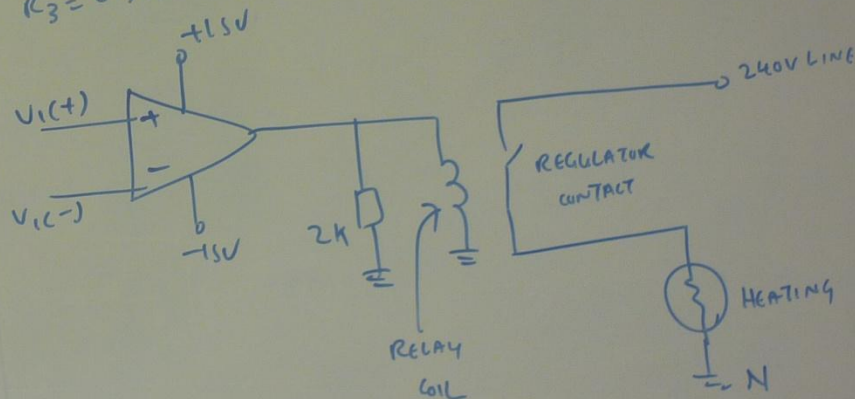

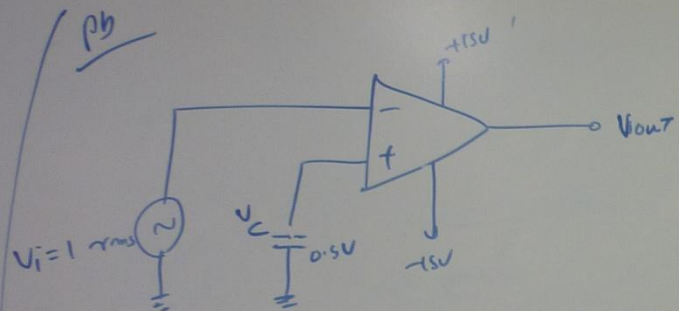


DRAW BOTH INPUT AND OUTPUT WAVE FORMS

$$V_{i \text{ MAX}} = \sqrt{2} V_{i \text{ rms}} = 1.4142 \times 1 = 1.4142 \text{ V}$$



$$V_i < V_c = - \text{VOLTAGE}$$

$$V_i > V_c = + \text{VOLTAGE}$$

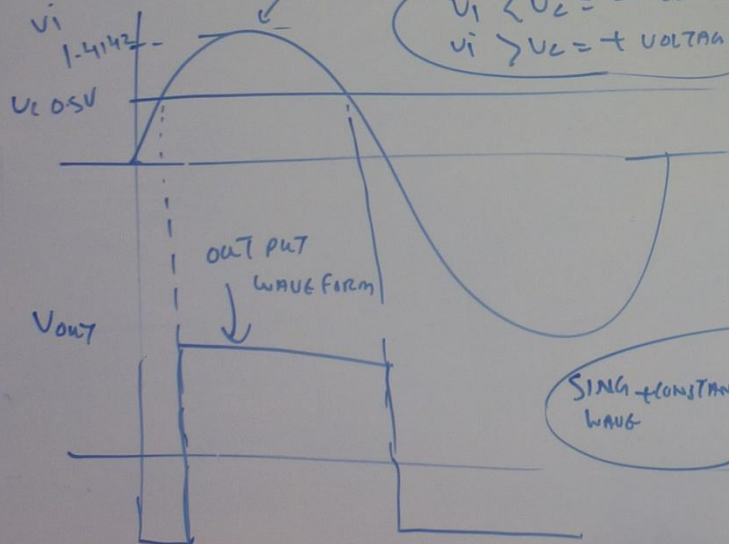

SIN + CONSTANT  $\Rightarrow$  SQUARE WAVE


### BASIC PWM CIRCUIT

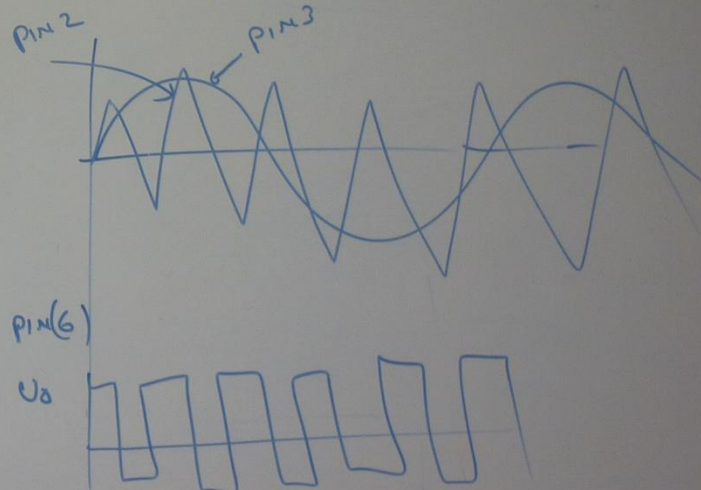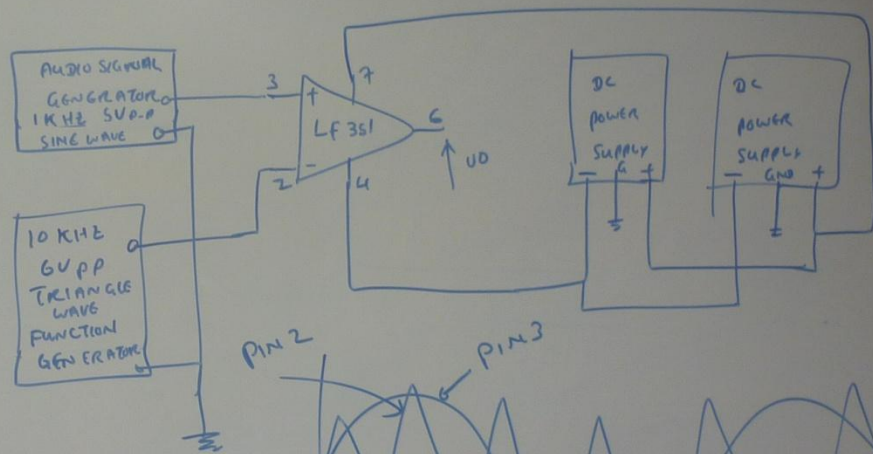



ph

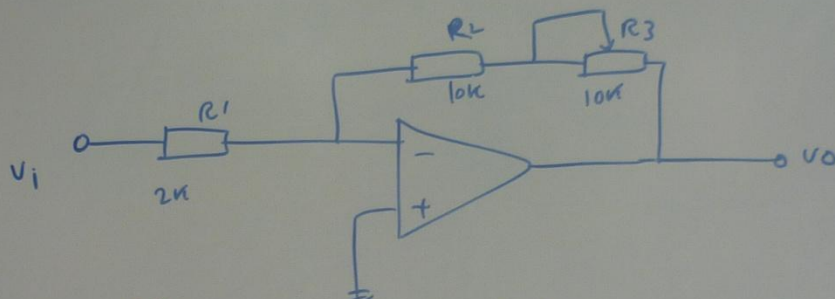FOR THE AMPLIFIER CIRCUIT SHOWN BELOW, DETERMINE MINIMUM VOLTAGE GAIN AND MAXIMUM VOLTAGE GAIN.




$$A_v = -\frac{R_f}{R_i} = -\frac{(R_2 + R_3)}{R_1}$$

$$\text{MAX } R_3 = 10k \rightarrow A_v = -\frac{(10+10)}{2} = -10$$

$$\text{MIN } R_3 = 0 \rightarrow A_v = -\frac{(10+0)}{2} = -5$$

ph

FOR THE CIRCUIT THE CURRENT

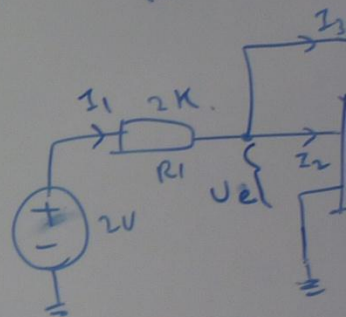

$$I_1 = \frac{V_{in}}{R_1} = \frac{2}{2}$$

$$I_2 = 0$$


$$\therefore I_1 = I_3 = 1$$

$$V_{Ref} = I_3$$

$$= 1$$

$$= 1$$

BELOW, DETERMINE  
INPUT GAIN.

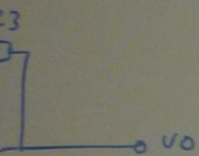


$$\frac{v_o}{v_i} = -10$$

$$\frac{v_o}{v_i} = -5$$

PROBLEM FOR THE CIRCUIT SHOWN BELOW FIND

THE CURRENT  $I_1 \sim I_5$

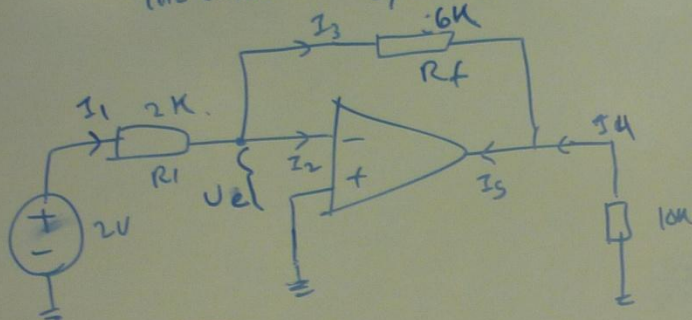

$$I_1 = \frac{V_{in}}{R_1} = \frac{2}{2k} = 1 \text{ mA}$$

$$I_2 = 0$$

$$\therefore I_1 = I_3 = 1 \text{ mA}$$

$$V_{ref} = I_3 \times R_f$$

$$= 1 \text{ mA} \times 6k$$

$$= 6 \text{ V}$$

$$V_o = V_c - V_{ref}$$

$$= 0 - 6 = -6 \text{ V}$$

$$I_4 = \frac{V_{out}}{R_4} = \frac{-6}{10}$$

$$= -0.6 \text{ mA}$$


$$I_5 = I_3 + I_4$$

$$= 1 + (-0.6)$$

$$= 0.4 \text{ mA}$$


$$I_1 \sim I_5 = 1 - 0.4$$

$$= 0.6 \text{ mA}$$

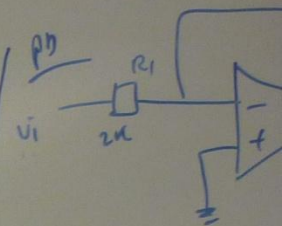

DETERMINE IN

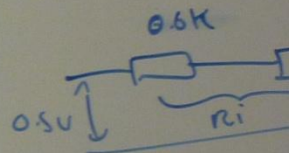PURPOSE SIGNAL  
GENERATOR  
1 kHz 0.5V<sub>pp</sub>  
R<sub>o</sub> = 600Ω



$$R_i = 0$$




$$V_o = V_c - V_{ref}$$

$$= 0 - 6 = -6 \text{ V}$$

$$I_4 = \frac{V_{out}}{R_4} = \frac{-6}{10} \\ \approx -0.6 \text{ mA}$$


$$I_5 = I_3 + I_4 \\ = 1 + (-0.6) \\ \approx 0.4 \text{ mA}$$
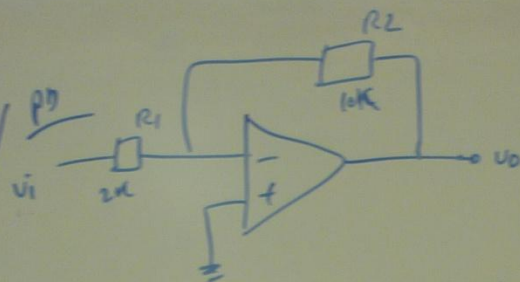
$$I_1 \sim I_5 = 1 - 0.4 \\ \approx 0.6 \text{ mA}$$




DETERMINING IN PUT RESISTANCE

$$R_{in} = R_1 = 2 \text{ K}$$

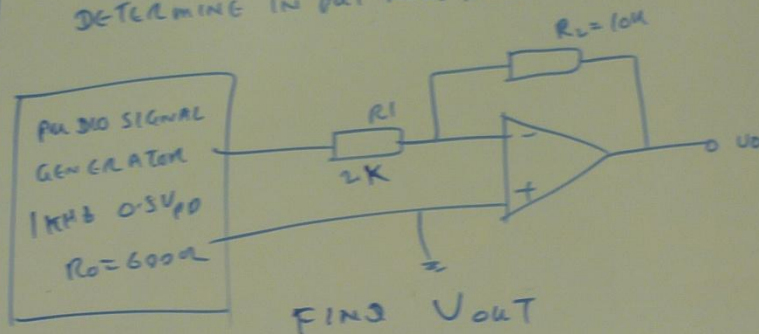

FIND  $V_{out}$

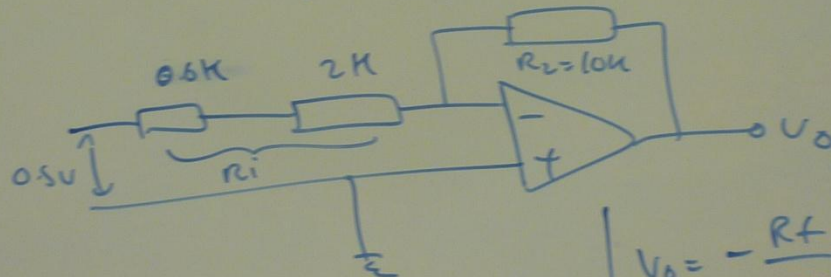

$$R_i = 0.6 + 2 = 2.6 \text{ K}$$

$$V_o = -\frac{R_f}{R_i} \times V_{in} \\ = -\frac{10}{2.6} \times 0.5 \\ \approx -1.92 \text{ V}$$


(b)  
(i)

AT

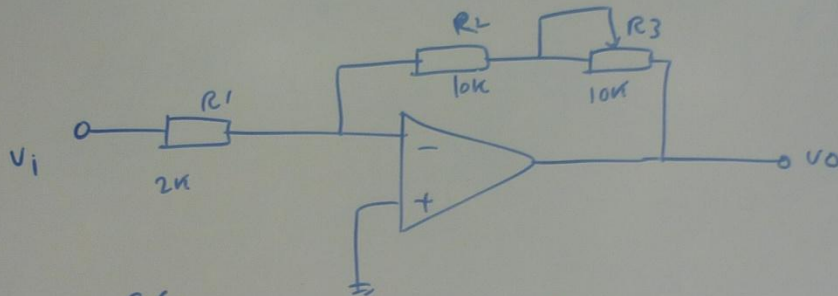(ii) so

(iii)

pb FOR THE AMPLIFIER CIRCUIT SHOWN BELOW, DETERMINE MINIMUM VOLTAGE GAIN AND MAXIMUM VOLTAGE GAIN.




$$A_v = -\frac{R_f}{R_i} = -\frac{(R_2 + R_3)}{R_1}$$

$$\text{MAX } R_3 = 10k \rightarrow A_v = -\frac{(10+10)}{2} = -10$$

$$\text{MIN } R_3 = 0 \rightarrow A_v = -\frac{(10+0)}{2} = -5$$

pb FOR THE CIR  
THE CURRENT

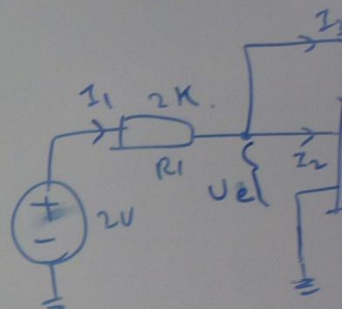

$$I_1 = \frac{V_{in}}{R_1} = \frac{2}{2}$$

$$I_2 = 0$$

$$\therefore I_1 = I_3 = 1$$


$$V_{R2} = I_3$$

$$= 1$$

$$= 6$$



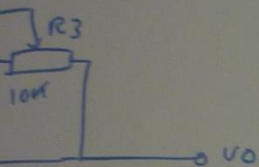Q.1. IN CIRCUIT SHOWN BELOW, DETERMINE  
MAXIMUM VOLTAGE GAIN.




$$\frac{(10+10)}{2} = -10$$

$$\frac{(10+10)}{2} = -5$$

Q.2. FOR THE CIRCUIT SHOWN BELOW FIND

THE CURRENT  $I_1 \sim I_5$

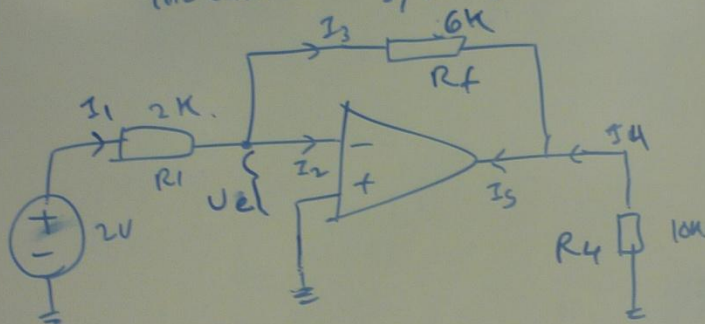

$$I_1 = \frac{V_{in}}{R_1} = \frac{2}{2K} = 1 \text{ mA}$$

$$I_2 = 0$$

$$\therefore I_1 = I_3 = 1 \text{ mA}$$

$$V_{Ref} = I_3 \times R_f$$

$$= 1 \text{ mA} \times 6K$$

$$= 6V$$

$$V_o = V_e - V_{Ref}$$

$$= 0 - 6 = -6V$$

$$I_4 = \frac{V_{out}}{R_4} = \frac{-6}{10}$$

$$= -0.6 \text{ mA}$$


$$I_5 = I_3 + I_4$$

$$= 1 + (-0.6)$$

$$= 0.4 \text{ mA}$$


$$I_1 \sim I_5 = 1 - 0.4$$

$$= 0.6 \text{ mA}$$

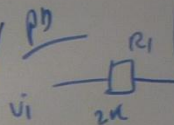

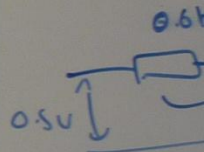Q.3. DETERMINE

AUDIO SIGNAL  
GENERATOR  
1KHz 0.5V<sub>pp</sub>  
 $R_o = 600\Omega$




$$V_o = V_c - V_{ref}$$

$$= 0 - 6 = -6 \text{ V}$$

$$I_4 = \frac{V_{out}}{R_4} = \frac{-6}{10} = -0.6 \text{ mA}$$


$$I_5 = I_3 + I_4 = 1 + (-0.6) = 0.4 \text{ mA}$$
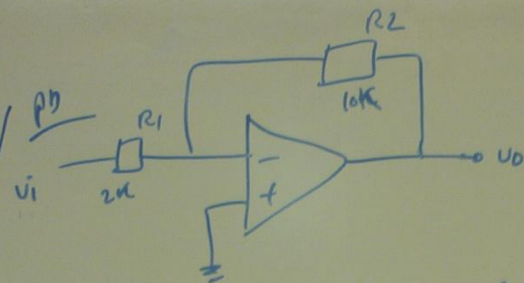
$$I_1 \sim I_5 = 1 - 0.4 = 0.6 \text{ mA}$$




DETERMINING IN PUT RESISTANCE

$$R_{in} = R_1 = 2 \text{ k}$$

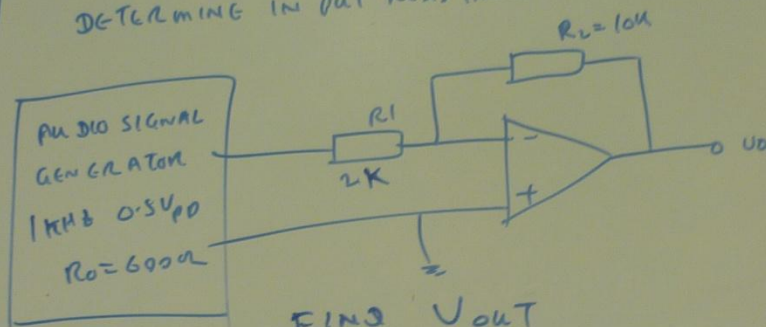

FIND  $V_{out}$

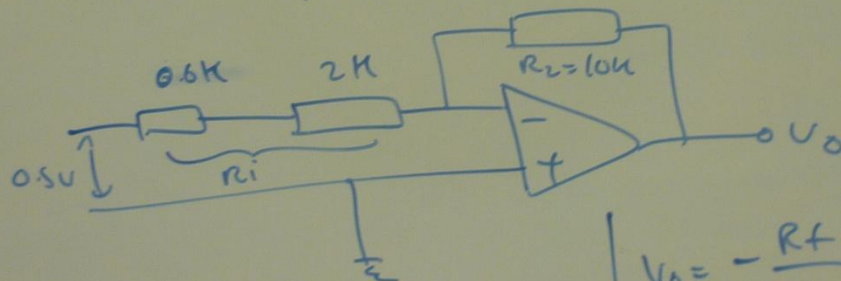


$$R_i = 0.6 + 2 = 2.6 \text{ k}$$

$$V_o = -\frac{R_f}{R_i} \times V_{in} = -\frac{10}{2.6} \times 0.5 = -1.92 \text{ V}$$




pb

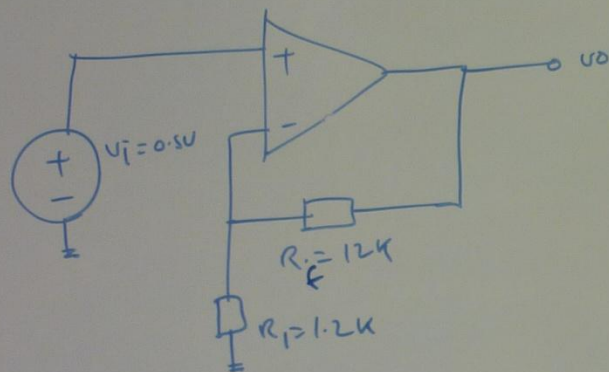FOR THE GIVEN CIRCUIT, CALCULATE  
OUT PUT VOLTAGE



$$\begin{aligned}
 V_o &= \left[ 1 + \frac{R_f}{R_i} \right] V_i \\
 &= \left[ 1 + \frac{12}{1} \right] \times 0.5 \\
 &= [13] \times 0.5 \\
 &= 6.5V
 \end{aligned}$$

pb

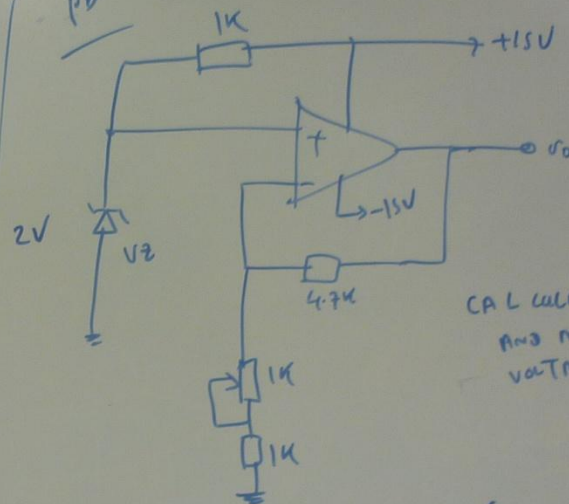

CALCULATE MAXIMUM  
AND MINIMUM OUT PUT  
VOLTAGES

$$V_o = (V_{IN} - V_z) \left( 1 + \frac{R_f}{R_i} \right)$$

$$\frac{R_i = 1k}{V_o = (15 - 2) \left( 1 + \frac{4.7}{1} \right) = 39V}$$

$$\frac{R_i = 2k}{V_o = (15 - 2) \left( 1 + \frac{4.7}{2} \right) = 65V}$$

pb

$$V_i = 1 \text{ rms}$$

OR

$$V_i \text{ max}$$


$$V_i$$

$$V_o \text{ rms}$$

$$V_{out}$$

pb

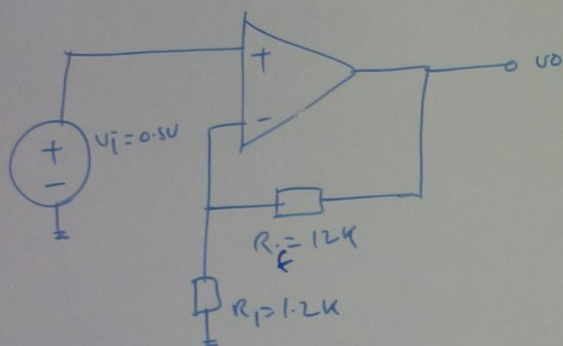FOR THE GIVEN CIRCUIT, CALCULATE  
OUT PUT VOLTAGE




$$V_o = \left[ 1 + \frac{R_f}{R_i} \right] V_i$$

$$= \left[ 1 + \frac{12}{1} \right] \times 0.5$$

$$= [13] \times 0.5$$

$$= 6.5V$$

pb

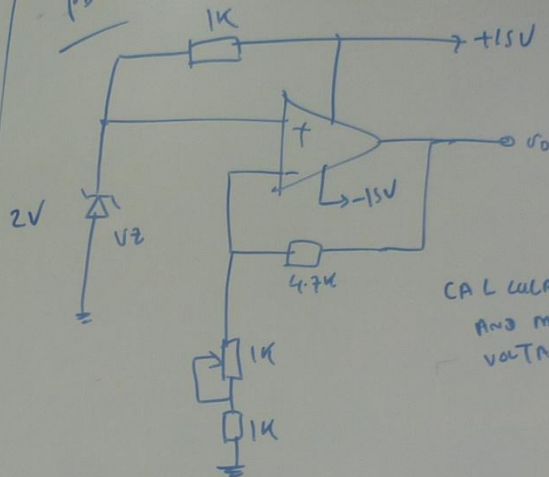

CALCULATE MAXIMUM  
AND MINIMUM OUT PUT  
VOLTAGES

$$V_o = (V_{IN} - V_z) \left( 1 + \frac{R_f}{R_i} \right)$$

$$\frac{R_i = 1k}{}$$

$$V_o = (15 - 2) \left( 1 + \frac{4.7}{1} \right) = 39V$$

$$\frac{R_i = 2k}{}$$

$$V_o = (15 - 2) \left( 1 + \frac{4.7}{2} \right) = 65V$$

pb

