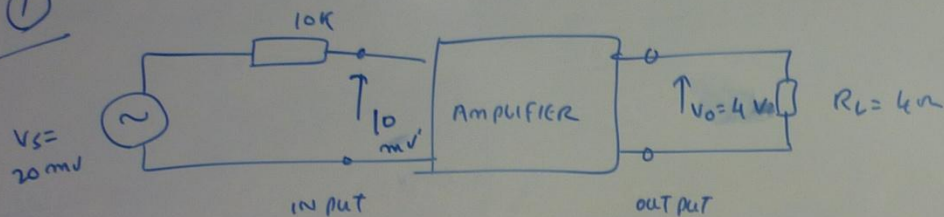


POWER AMPLIFIER CIRCUIT CALCULATIONS

pb ①



- FIND (a) VOLTAGE GAIN (b) INPUT CURRENT
(c) OUTPUT CURRENT (d) CURRENT GAIN.
(e) OUTPUT POWER (f) POWER GAIN
(g) TRAN RESISTANCE (h) TRANS CONDUCTANCE.

$$(a) \text{ VOLTAGE GAIN (AV)} = \frac{V_o}{V_{in}} = \frac{4}{10 \times 10^{-3}} = \frac{4000}{10} = 400$$

$$(b) \text{ VOLTAGE DROP ACROSS } 10 \text{ k}\Omega \text{ RESISTOR} = 20 - 10 = 10 \text{ mV}$$

$$I = \frac{10 \text{ mV}}{10 \text{ k}} = \frac{10 \times 10^{-3}}{10 \times 10^3} = 1 \times 10^{-6} = 1 \mu\text{A}$$

$$(c) I_{out} = \frac{4 \text{ V}}{4 \Omega} = 1 \text{ A}$$

$$(d) \text{ CURRENT GAIN} = \frac{I_{out}}{I_{in}} = \frac{1}{1 \mu\text{A}} = \frac{1}{1 \times 10^{-6}} = \frac{10^6}{1} = 10^6$$

$$(e) P_{out} = V_{out} \times I_{out} = 4 \times 1 = 4 \text{ W}$$

$$(f) P_{in} = V_{in} \times I_{in} = 10 \times 10^{-3} \times 1 \times 10^{-6} = 10 \times 10^{-9} \text{ W}$$

$$P_{out} = 4 \text{ W}$$

$$(c) I_{out} = \frac{4V}{4\Omega} = 1A$$

$$(d) \text{ CURRENT GAIN} = \frac{I_{out}}{I_{in}} = \frac{1}{1 \times 10^{-6}} = 10^6$$

$$(e) P_{out} = V_{out} \times I_{out} = 4 \times 1 = 4W$$

$$(f) P_{in} = V_{in} \times I_{in} = 10 \times 10^{-3} \times 1 \times 10^{-6} = 10 \times 10^{-9} W$$

$$P_{out} = 4W$$


$$A_p = \frac{P_{out}}{P_{in}} = \frac{4}{10 \times 10^{-9}} = 4 \times 10^8$$


$$= 0.4 \times 10^9$$

$$= 4 \times 10^8$$

$$(g) \text{ TRAN RESISTANCE} = \frac{V_{out}}{I_{in}} = \frac{4}{1 \times 10^{-6}} = 4 \times 10^6 \Omega = 4M\Omega$$
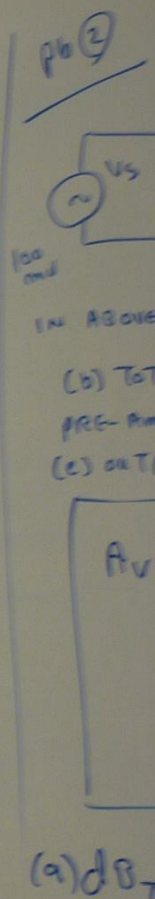
$$(h) \text{ TRAN CONDUCTANCE} = \frac{I_{out}}{V_{in}} = \frac{1}{10 \text{ mV}} = \frac{1}{10 \times 10^{-3}} = \frac{10^3}{10} = 100 \Omega$$



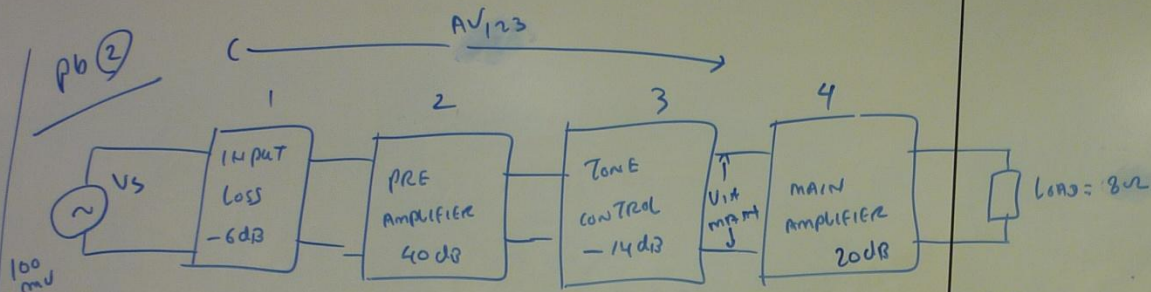

IN ABOVE CIRCUIT . FIND (a) TOTAL VOLTAGE GAIN IN dB
 (b) TOTAL VOLTAGE GAIN IN DIRECT RATIO (c) INPUT VOLTAGE OF PRE-AMPLIFIER (d) INPUT VOLTAGE OF MAIN AMPLIFIER
 (e) OUTPUT VOLTAGE OF AMPLIFIER

$$A_V(dB) = 20 \log_{10} \frac{V_2}{V_1}$$

$$\frac{V_2}{V_1} = 10^{\frac{A_V(dB)}{20}}$$

$$A_V = 10^{\frac{A_V(dB)}{20}}$$

$$dB_T = dB_1 + dB_2 + dB_3$$

$$A_{VT} = A_1 \times A_2 \times A_3$$

$$(a) dB_T = dB_1 + dB_2 + dB_3 + dB_4$$

$$= (-6) + (40) + (-14) + 20 = 40$$

$$(b) A_{VT} = A_{V1} \times A_{V2} \times A_{V3} \times A_{V4}$$

$$= 10^{\frac{A_{V1}(dB)}{20}} \times 10^{\frac{A_{V2}(dB)}{20}} \times 10^{\frac{A_{V3}(dB)}{20}} \times 10^{\frac{A_{V4}(dB)}{20}}$$

$$= 10^{\frac{-6}{20}} \times 10^{\frac{40}{20}} \times 10^{\frac{-14}{20}} \times 10^{\frac{20}{20}}$$

$$= 10^{-0.3} \times 10^2 \times 10^{-0.7} \times 10^1$$


$$= 10^{(-0.3) + 2 + (-0.7) + 1}$$

$$= 10^2 = 100$$

$$(1) A_{V123} = 10^{\frac{A_{V1}(dB)}{20}} \times 10^{\frac{A_{V2}(dB)}{20}} \times 10^{\frac{A_{V3}(dB)}{20}}$$

$$= 10^{-0.3} \times 10^2 \times 10^{-0.7}$$
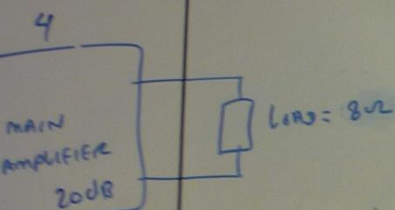
$$= 10^{(-0.3) + 2 + (-0.7)} = 10^1 = 10$$



dB
STAGE OF
FEED

dB₃

AV₃

$$(b) A_{VT} = A_{V1} \times A_{V2} \times A_{V3} \times A_{V4}$$

$$= 10^{\frac{AV_1(dB)}{20}} \times 10^{\frac{AV_2(dB)}{20}} \times 10^{\frac{AV_3(dB)}{20}} \times 10^{\frac{AV_4(dB)}{20}}$$

$$= 10^{\frac{-6}{20}} \times 10^{\frac{40}{20}} \times 10^{\frac{-14}{20}} \times 10^{\frac{20}{20}}$$

$$= 10^{-0.3} \times 10^2 \times 10^{-0.7} \times 10^1$$

$$= 10^{(-0.3+2+(-0.7)+1)}$$

$$= 10^2 = 100$$

$$(c) A_{V_{123}} = 10^{\frac{AV_1(dB)}{20}} \times 10^{\frac{AV_2(dB)}{20}} \times 10^{\frac{AV_3(dB)}{20}}$$

$$= 10^{-0.3} \times 10^2 \times 10^{-0.7}$$

$$= 10^{(-0.3+2+(-0.7))} = 10^1 = 10$$

$$(d) V_{IN(MAIN)} = V_S \times A_{V_{123}}$$

$$= (100 \times 10^{-3}) \times 10$$

$$= 100 \times 10^{-3} \times 10$$

$$= 1V$$

$$(e) V_{OUT} = V_{IN(MAIN)} \times A_{V4}$$


$$= 1 \times 10^{\frac{AV_4(dB)}{20}}$$

$$= 1 \times 10^{\frac{20}{20}}$$



$$= 1 \times 10^1$$

$$= 10V$$

Pb(3)
FOR THE

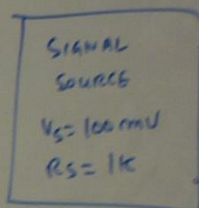

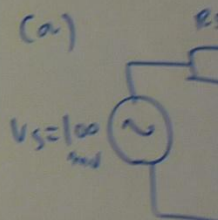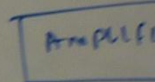- (a) DRAW THE EQ
(b) DETERMINE
(c) DETERMINE
(d) DETERMINE
TO ACHIEVE




$$\begin{aligned}
 (d) V_{IN(MAIN)} &= V_S \times A_{V_{123}} \\
 &= (100 \times 10^{-3}) \times 10 \\
 &= 100 \times 10^{-3} \times 10 \\
 &= 1V
 \end{aligned}$$


$$\begin{aligned}
 (e) V_{OUT} &= V_{IN(MAIN)} \times A_{V4} \\
 &= 1 \times 10^{\frac{20}{20}} \\
 &= 1 \times 10^1 \\
 &= 10V
 \end{aligned}$$

pb(3)

FOR THE AMPLIFIER CONNECTION BELOW

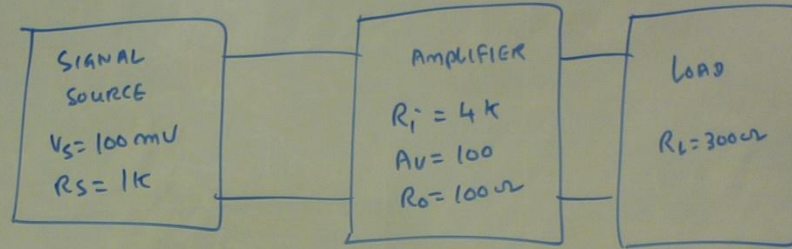

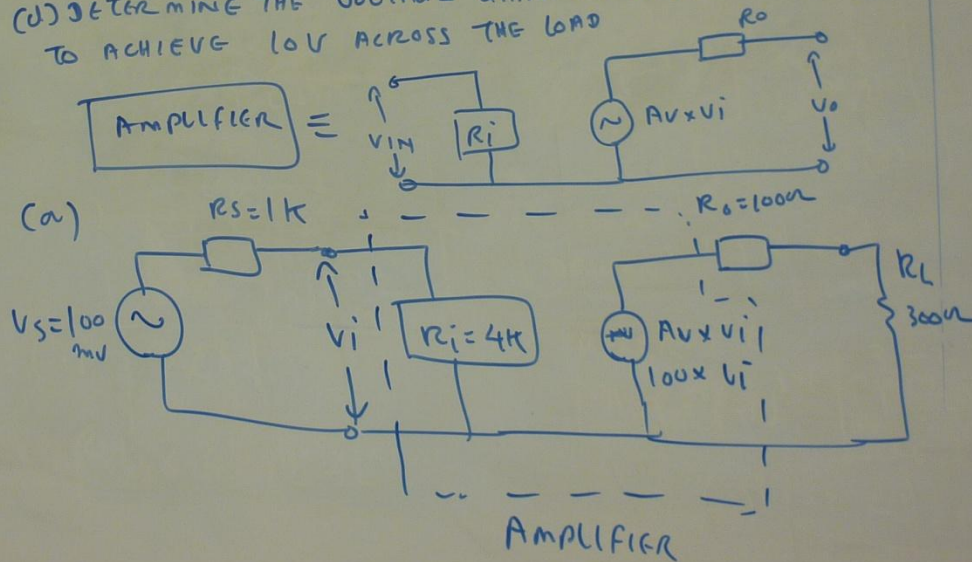- (a) DRAW THE EQUIVALENT CIRCUIT
 (b) DETERMINE THE INPUT VOLTAGE OF AMPLIFIER
 (c) DETERMINE THE OUTPUT VOLTAGE OF AMPLIFIER
 (d) DETERMINE THE VOLTAGE GAIN OF AMPLIFIER TO ACHIEVE 10V ACROSS THE LOAD



$$(b) V_i = V_S \times \frac{R_i}{R_S + R_i}$$

$$(c) V_{OUT} = A_V \times V_i$$


$$(d) V_{OUT} = 10V$$

$$V_{IN} = 80mV$$



$$A_V = \frac{V_{OUT}}{V_{IN}}$$

Pb(3)

FOR THE AMPLIFIER CONNECTION BELOW

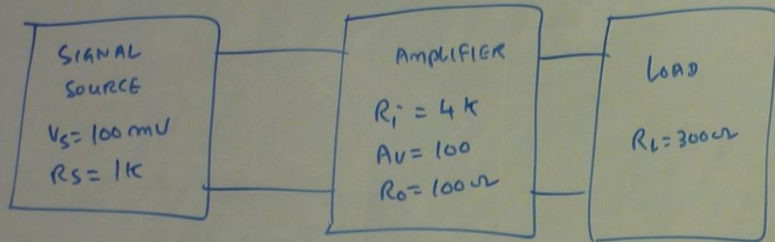

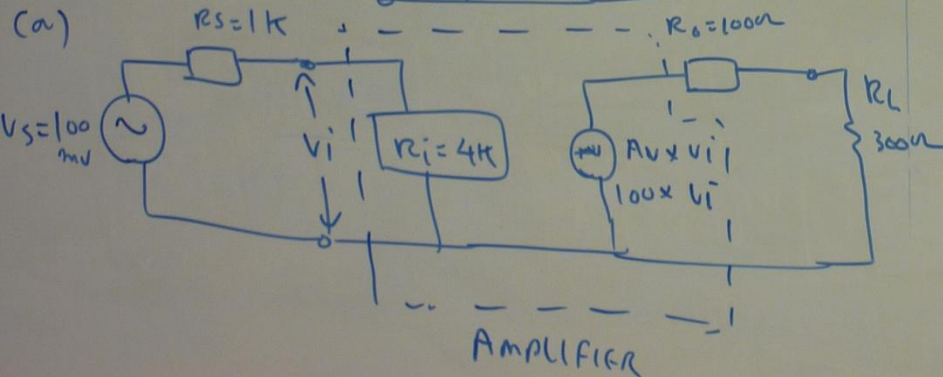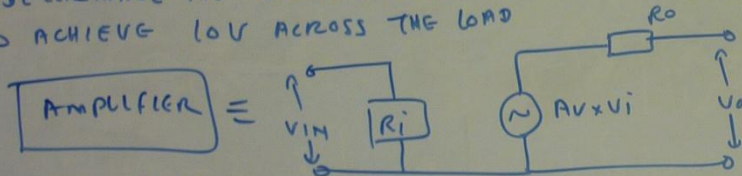- (a) DRAW THE EQUIVALENT CIRCUIT
 (b) DETERMINE THE INPUT VOLTAGE OF AMPLIFIER
 (c) DETERMINE THE OUTPUT VOLTAGE OF AMPLIFIER
 (d) DETERMINE THE VOLTAGE GAIN OF AMPLIFIER
 TO ACHIEVE 10V ACROSS THE LOAD



$$(b) V_i = V_s \times \frac{R_i}{R_s + R_i} = 100 \times \frac{4}{1+4} = \frac{100 \times 4}{5} = 80 \text{ mV}$$


$$(c) V_{out} = A_v \times V_i = 100 \times 80 \text{ mV} = 100 \times 80 \times 10^{-3} = 8 \text{ V}$$

$$(d) V_{out} = 10 \text{ V}$$

$$V_{in} = 80 \text{ mV}$$


$$A_v = \frac{V_{out}}{V_{in}} = \frac{10}{80 \times 10^{-3}} = \frac{1000}{80} = 12.5$$

6. AMPLIFIER CONNECTION BELOW

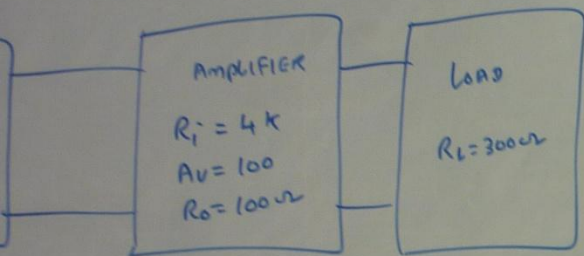

EQUIVALENT CIRCUIT

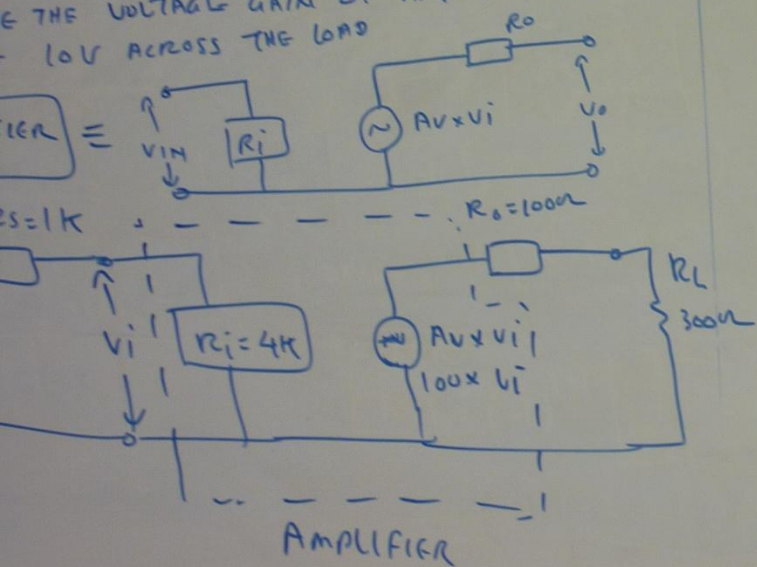THE INPUT VOLTAGE OF AMPLIFIER
 THE OUTPUT VOLTAGE OF AMPLIFIER
 THE VOLTAGE GAIN OF AMPLIFIER
 10V ACROSS THE LOAD



$$(b) V_i = V_s \times \frac{R_i}{R_s + R_i} = 100 \times \frac{4}{1 + 4} = \frac{100 \times 4}{5} = 80 \text{ mV}$$


$$(c) V_{out} = A_v \times V_i = 100 \times 80 \text{ mV} = 100 \times 80 \times 10^{-3} = 8 \text{ V}$$

$$(d) V_{out} = 10 \text{ V}$$

$$V_{in} = 80 \text{ mV}$$


$$A_v = \frac{V_{out}}{V_{in}} = \frac{10}{80 \times 10^{-3}} = \frac{1000}{80} = 12.5$$

Pb 4

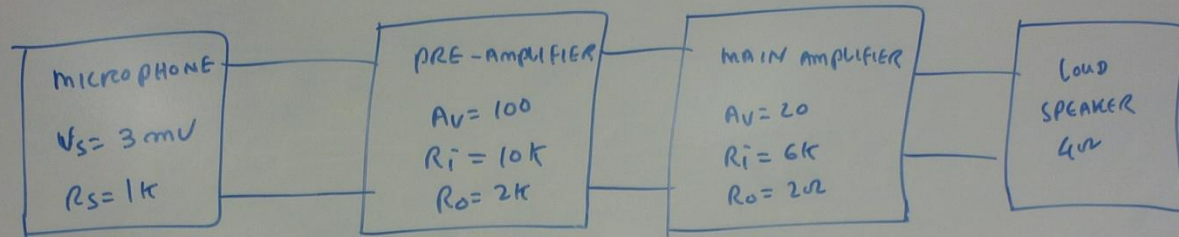

THE ABOVE DIAGRAM IS A MULTI STAGE AMPLIFIER

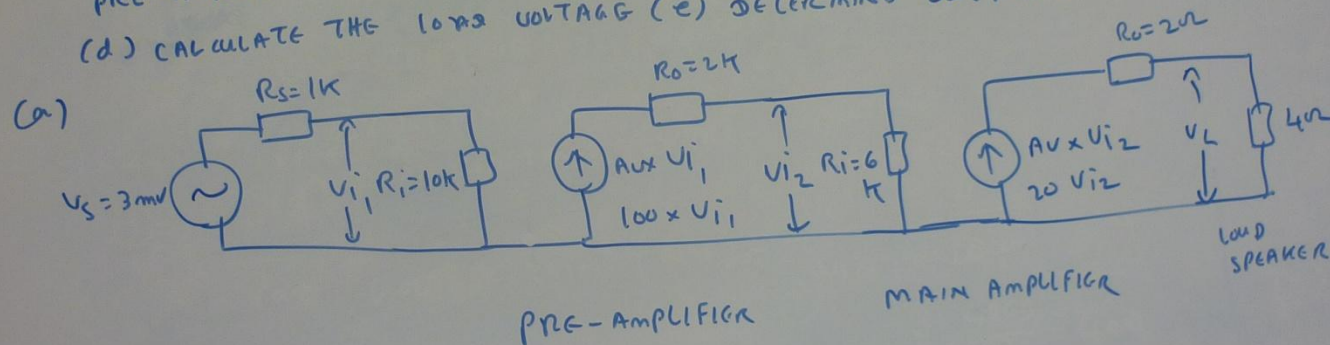- (a) DRAW AN EQUIVALENT CIRCUIT (b) CALCULATE THE INPUT VOLTAGE OF PRE-AMPLIFIER (c) CALCULATE THE INPUT VOLTAGE OF MAIN AMPLIFIER (d) CALCULATE THE LOAD VOLTAGE (e) DETERMINE OUTPUT POWER.




(b) $V_{i1} = ?$

$$V_{i1} = V_s \times \frac{R_i}{R_s + R_i} = 3 \text{ mV} \times \frac{10 \text{ k}}{(1 + 10) \text{ k}} = 2.72 \text{ mV}$$

(c) $A_v \times V_{i1} = 2.72 \times 100 = 272 \text{ mV}$

LOAD
SPEAKER
4Ω

OF
R
2Ω

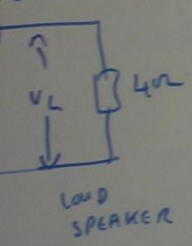

0.72 mV

$$V_{i2} = A_V \times V_{i1} \times \frac{R_i}{R_i + R_o}$$

$$= 272 \times \frac{6}{6+2}$$

$$= 204 \text{ mV}$$

$$(d) A_V \times V_{i2} = 20 \times 204 \text{ mV}$$

$$= 20 \times 0.204$$

$$= 4.08 \text{ V}$$

$$V_L = (A_V \times V_{i2}) \times \frac{R_L}{R_o + R_L}$$

$$= 4.08 \times \frac{4}{4+2}$$

$$= \frac{4.08 \times 4}{6} = \frac{16.32}{6}$$

$$= 2.7 \text{ V}$$

$$P_{out} = \frac{V_{out}^2}{R_L}$$

$$= \frac{(2.7)^2}{4}$$

$$= \frac{2.7 \times 2.7}{4}$$

$$= 1.8225 \text{ W}$$

MID BAND

pb 5

PLOT THE FREQUENCY RESPONSE FROM AN AMPLIFIER AND INDICATE

$$\text{VOLTAGE GAIN } A_V = \frac{V_o}{V_i}$$

$$\text{POWER AT LOAD} = \frac{V_o^2}{R}$$

FREQUENCY (Hz)	V_i (mV)	V_o (V)	VOLTAGE
10	100	1	$\frac{100 \times 10^{-3}}{100 \times 10^{-3}} = 1$
20	100	1.96	$\frac{1.96}{100 \times 10^{-3}} = 19.6$
40	100	3.71	$\frac{3.71}{100 \times 10^{-3}} = 37.1$
100	100	7.07	$\frac{7.07}{100 \times 10^{-3}} = 70.7$
200	100	8.94	$\frac{8.94}{100 \times 10^{-3}} = 89.4$
400	100	9.28	$\frac{9.28}{100 \times 10^{-3}} = 92.8$
1k	100	9.95	$\frac{9.95}{100 \times 10^{-3}} = 99.5$
2k	100	10	$\frac{10}{100 \times 10^{-3}} = 100$
4k	100	10	$\frac{10}{100 \times 10^{-3}} = 100$
10k	100	9.95	$\frac{9.95}{100 \times 10^{-3}} = 99.5$
20k	100	9.81	$\frac{9.81}{100 \times 10^{-3}} = 98.1$

$$P_T = \frac{V_{out}^2}{R_L}$$

$$= \frac{(2.7)^2}{4}$$

$$= \frac{2.7 \times 2.7}{4}$$

$$= 1.8225 \text{ W}$$

pb 5 Plot the frequency response of the following data obtained from an amplifier and indicate mid band and half power points.

$$\text{VOLTAGE GAIN } A_V = \frac{V_o}{V_i}$$

$$\text{VOLTAGE GAIN (dB)} = 20 \log_{10} \frac{V_o}{V_i}$$

$$\text{POWER AT LOAD} = \frac{V_o^2}{R}$$

$$\text{POWER GAIN (dB)} = 10 \log \frac{\text{POWER AT LOAD}}{\text{BASE POWER}}$$

FREQUENCY (Hz)	V _i (mV)	V _o (V)	VOLTAGE GAIN	VOLTAGE GAIN (dB)	LOAD POWER (mW)	POWER GAIN (dB)
					10mW	(mW = 0dB)
10	100	1	$\frac{1}{100 \times 10^{-3}} = 10$	$20 \log_{10} \frac{1}{100 \times 10^{-3}} = 20$	$\frac{1^2}{10} = 0.1 \text{ W}$	$10 \log \frac{0.1}{1 \times 10^{-3}} = 10$
20	100	1.96	$\frac{1.96}{100 \times 10^{-3}} = 19.6$	$20 \log_{10} \frac{1.96}{100 \times 10^{-3}} = 25.8$	$\frac{1.96^2}{10} = 0.384 \text{ W}$	$10 \log \frac{0.384}{1 \times 10^{-3}} = 15.3$
40	100	3.71	37.1	31.3	1.376	31.3
100	100	7.07	70.7	36.9	4.99	36.9
200	100	8.94	89.4	39	7.94	39.02
400	100	9.28	92.8	39.3	8.61	39.35
1k	100	9.95	99.5	39.5	9.9	39.45
2k	100	10	100	40	10	40
4k	100	10	100	40	10	40
10k	100	9.95	99.5	39.5	9.9	39.45
20k	100	9.81	98.1	39.8	9.62	39.83

MID BAND

HALF

MID

$$\frac{V_{out}^2}{R_L}$$

$$\frac{(2.7)^2}{4}$$

$$\frac{2.7 \times 2.7}{4}$$

$$1.8225 W$$

pb 5

PLOT THE FREQUENCY RESPONSE OF THE FOLLOWING DATA OBTAINED FROM AN AMPLIFIER AND INDICATE MID BAND AND HALF POWER POINT.

$$VOLTAGE GAIN A_V = \frac{V_o}{V_i}$$

$$VOLTAGE GAIN (dB) = 20 \log \frac{V_o}{V_i}$$

$$POWER AT LOAD = \frac{V_o^2}{R}$$

$$POWER GAIN (dB) = 10 \log \frac{POWER AT LOAD}{BASE POWER}$$

FREQUENCY (Hz)	V _i (mV)	V _o (V)	VOLTAGE GAIN	VOLTAGE GAIN (dB)	LOAD POWER	POWER GAIN (dB)
10	100	1	$\frac{1}{100 \times 10^{-3}} = 10$	$20 \log \frac{1}{100 \times 10^{-3}} = 20$	$\frac{12}{10} = 0.1 W$	$10 \log \frac{0.1}{1 \times 10^{-3}} = 10$
20	100	1.96	$\frac{1.96}{100 \times 10^{-3}} = 19.6$	$20 \log \frac{1.96}{100 \times 10^{-3}} = 25.8$	$\frac{1.96^2}{10} = 0.384 W$	$10 \log \frac{0.384}{1 \times 10^{-3}} = 15.3$
40	100	3.71	37.1	31.3	1.376	31.3
100	100	7.07	70.7	36.9	4.99	36.9
200	100	8.94	89.4	39	7.94	39.02
400	100	9.28	92.8	39.3	8.61	39.35
1k	100	9.95	99.5	39.5	9.9	39.95
2k	100	10	100	40	10	40
4k	100	10	100	40	10	40
10k	100	9.95	99.5	39.9	9.9	39.95
20k	100	9.81	98.1	39.8	9.62	39.85

MID BAND

HALF POWER POINT

MID BAND

FREQUENCY

40k

100k

200k

400k

1M

$\text{GAIN (dB)} = 20 \log \left(\frac{V_o}{V_i} \right)$
 $\text{mW} = 0.43$
 $\frac{0.1}{1 \times 10^3} = 10$
 $\frac{0.384}{1 \times 10^3} = 15.3$

31.3
 36.9
 39.02
 39.35
 39.95
 40
 40
 39.95
 39.83

FREQUENCY (Hz)	V_i (mV)	V_o (V)	VOLTAGE GAIN	VOLTAGE GAIN (dB)	LOAD POWER	POWER GAIN (dB)
40k	100	9.28	92.8	39.8	8.61	39.35
100k	100	7.07	70.7	36.9	4.99	36.9
200k	100	4.47	44.7	33	1.99	32.9
400k	100	2.43	24.3	27.7	0.59	27.7
1M	100	1	10	20	0.1	10


HALF POWER
 POINT (2)

pb 6

AN
 AN
 Em
 FR

HALF POWER
 POINT (1)

MID BAND

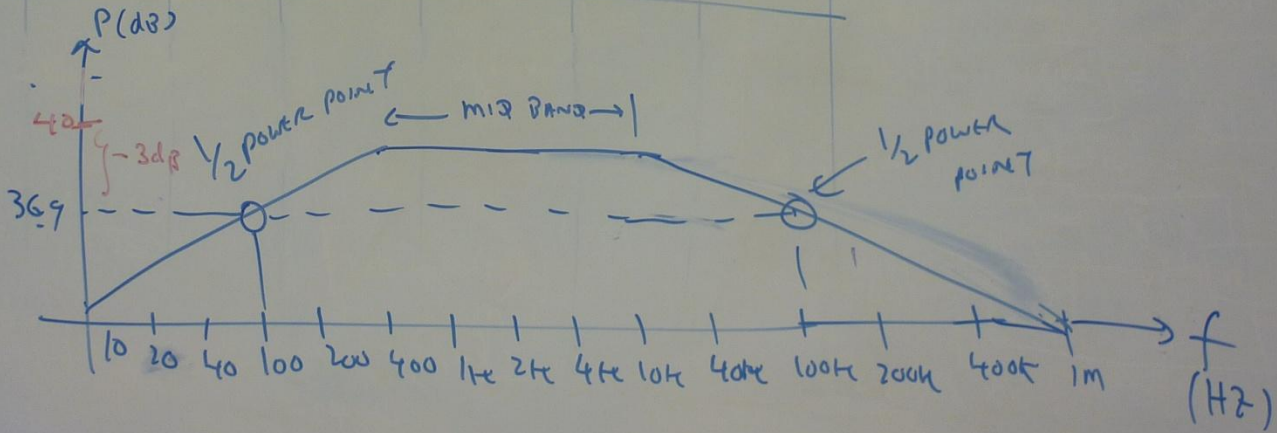

pn 7

pb ⑥

AN AUDIO SIGNAL GENERATOR WHOSE SOURCE RESISTANCE IS $600\ \Omega$ IS CONNECTED TO AN AMPLIFIER WHICH HAS A $3\ \text{k}\Omega$ INPUT RESISTANCE. A $1\ \mu\text{F}$ COUPLING CAPACITOR IS EMPLOYED THE SIGNAL SOURCE AND THE AMPLIFIER. DETERMINE THE LOWER HALF POWER FREQUENCY.

$$f_{L-3dB} = \frac{1}{2\pi (R_S + R_i) C}$$

(frequency)

R_S = SOURCE RESISTANCE, R_i = INPUT RESISTANCE OF AMPLIFIER, C = COUPLING CAPACITOR

$$f_{L-3dB} = \frac{1}{2 \times 3.1416 \times (600 + 3 \times 10^3) \times 1 \times 10^{-6}} = 44.2\ \text{Hz}$$

pb ⑦

AN AMPLIFIER HAS AN INPUT IMPEDANCE $10\ \text{k}\Omega$. CALCULATE THE VALUE OF COUPLING CAPACITOR REQUIRES FOR $40\ \text{Hz}$ LOWER -3dB FREQUENCY. SOURCE RESISTANCE = $600\ \Omega$

$$40 = \frac{1}{2 \times 3.1416 (600 + 1000) C}$$

$$C = \frac{1}{2 \times 3.1416 \times 40 \times 1600} = 2.486\ \mu\text{F}$$

f
(Hz)