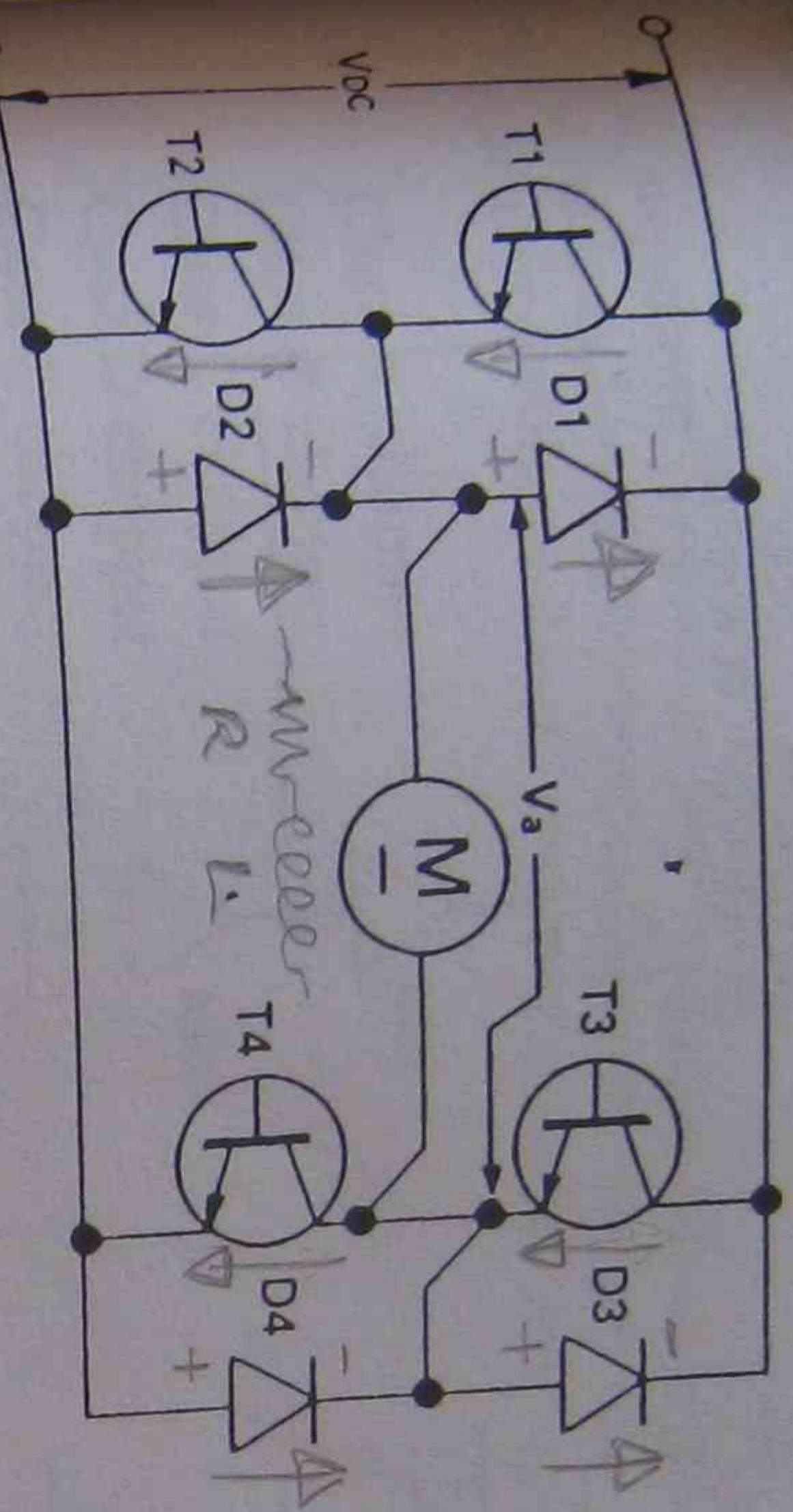




A.C. Motor Control.

Topic -



4 quadrant
operation
Forward &
Reverse
- Motoring &
- Braking.

Forward Motoring

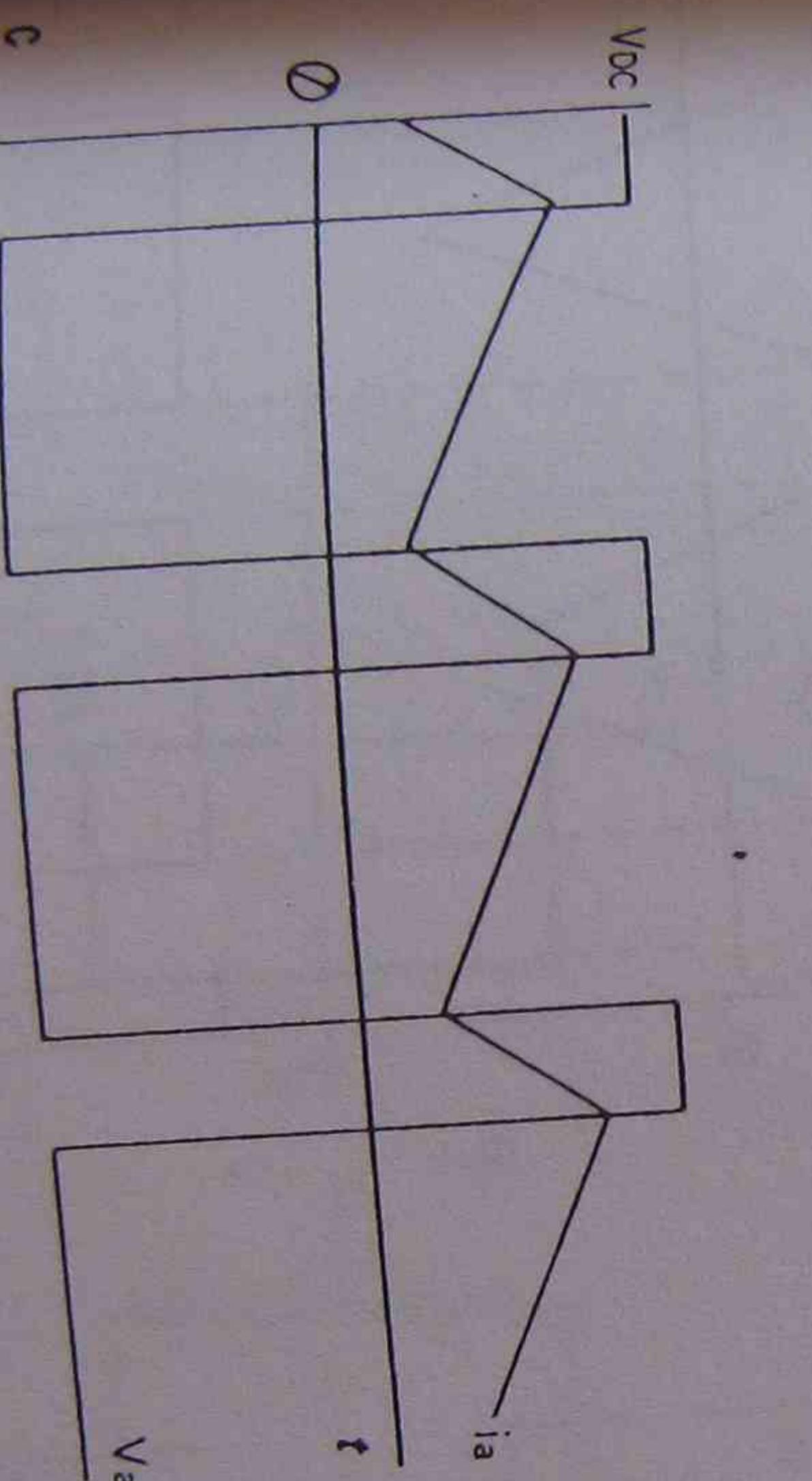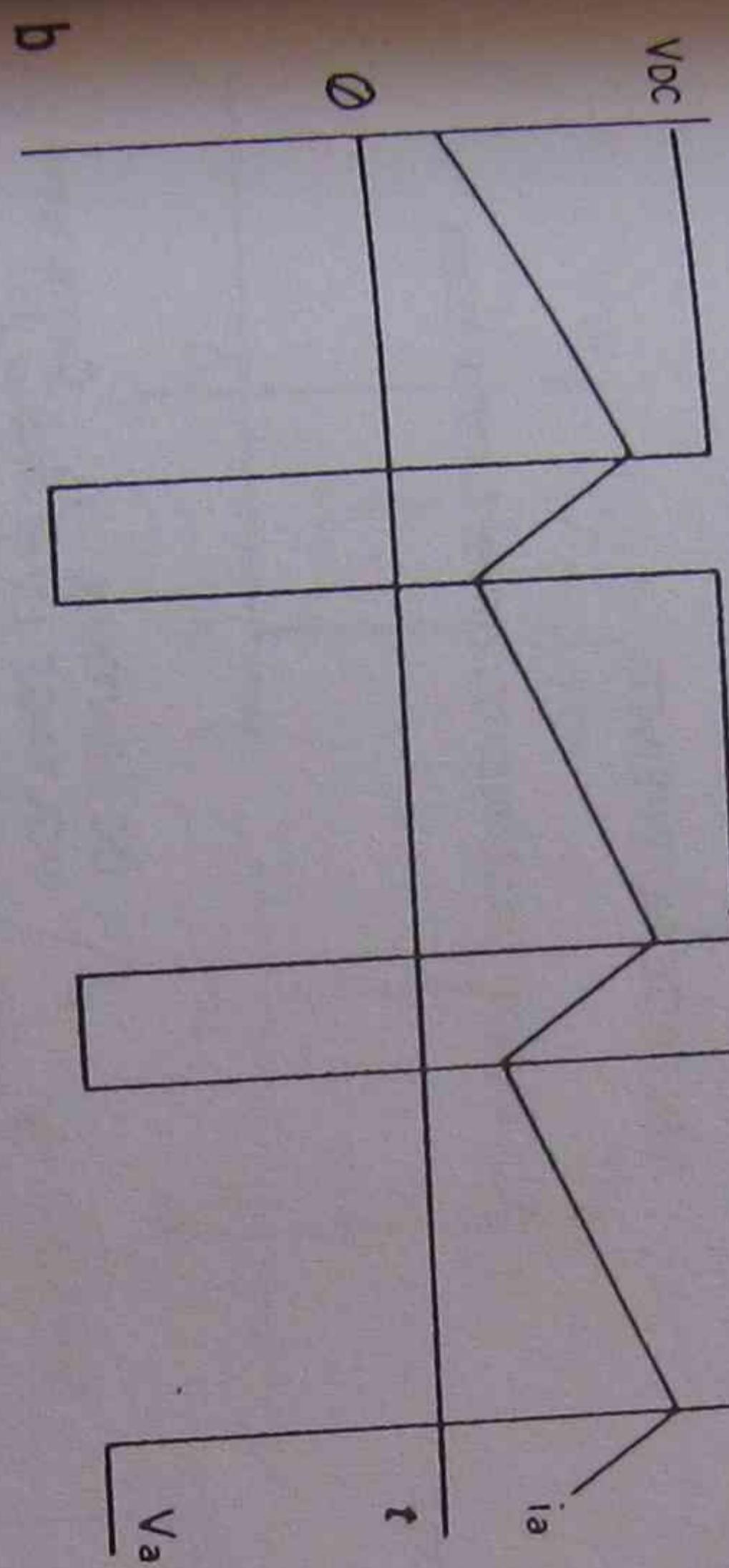

- 4 quadrant dc-dc converter:
a circuit; **b** forward
motoring; **c** reverse braking.

Reverse Braking

1
2
3 Rev
4 Fwd
speed & v
load.

Sydney Institute of Technology

School of Electrotechnology

Learners Theory

Work Book

NET6

Module

A.C. Motor Control

Area

Topic

Session No.

3.1

For further information on this module, or this subject

contact Jim Hafford, (02) 217 3620, Bld K, Ultimo, S.I.T.

A.C. Motor Control.

Topic -

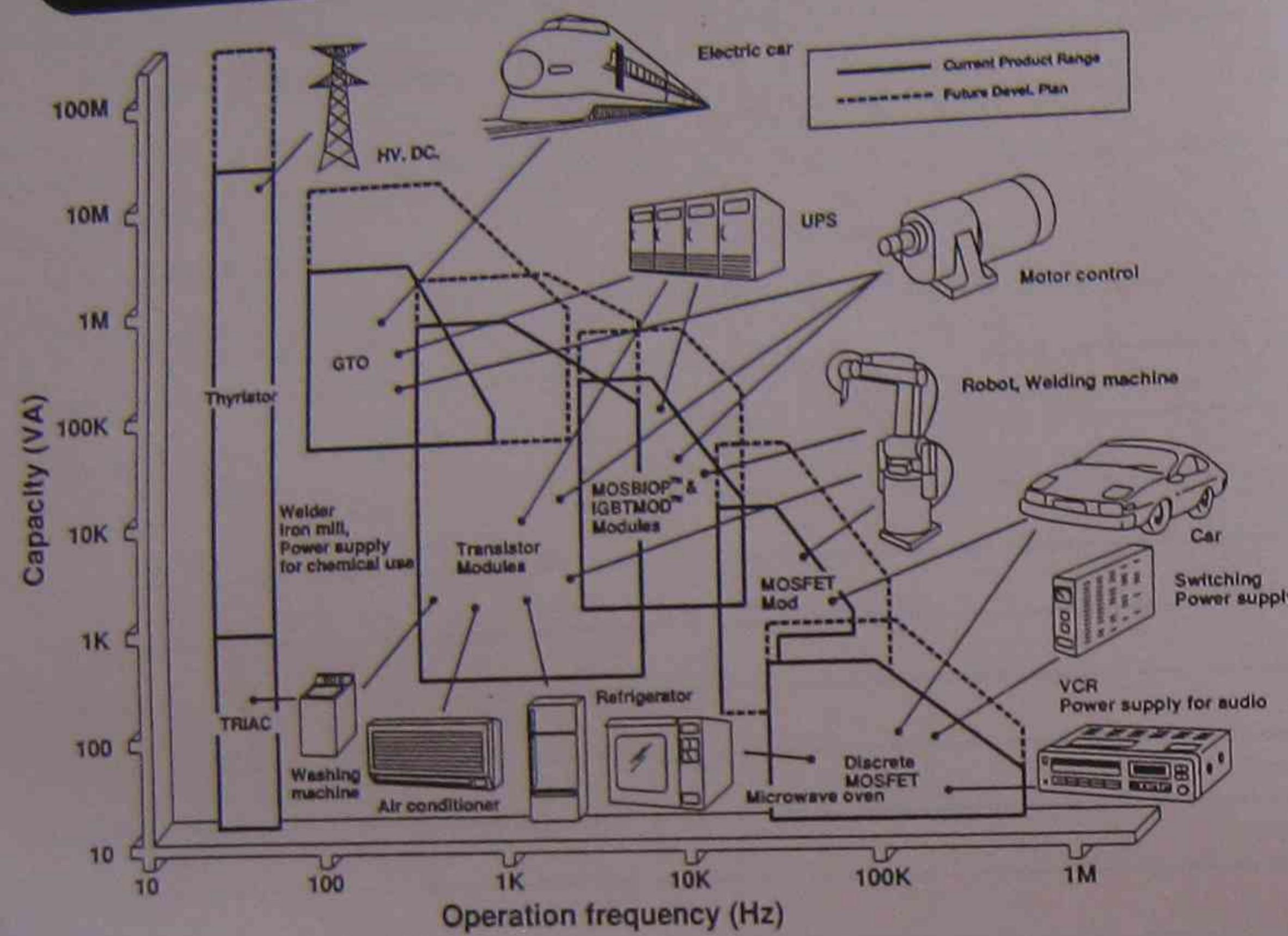


Figure 1-6 Applications of power devices. (Courtesy of Powerex, Inc.)

TABLE 1.2 RATINGS OF POWER SEMICONDUCTOR DEVICES

Type	Voltage/current rating	Upper frequency (Hz)	Switching time (μ s)	On-state resistance (Ω)
Diodes	General purpose	5000 V/5000 A	1k	100
	High speed	3000 V/1000 A	10k	2-5
	Schottky	40 V/60 A	20k	0.23
Forced-turned-off thyristors	Reverse blocking	5000 V/5000 A	1k	200
	High speed	1200 V/1500 A	10k	20
	Reverse blocking	2500 V/400 A	5k	40
	Reverse conducting	2500 V/1000 A	5k	40
GATT	1200 V/400 A	20k	8	2.24m
	Light triggered	6000 V/1500 A	400	0.53m
	1200 V/300 A	400	200-400	3.57m
TRIACs				
Self-turned-off thyristors	GTO	4500 V/3000 A	10k	15
	SITH	4000 V/2200 A	20k	6.5
Power transistors	Single	400 V/250 A	20k	9
		400 V/40 A	20k	6
		630 V/50 A	25k	31m
SITs	Darlington	1200 V/400 A	10k	1.7
	Power MOSFETS	1200 V/300 A	100k	30
	Single	500 V/8.6 A	100k	0.55
		1000 V/4.7 A	100k	0.7
		500 V/50 A	100k	0.9
IGBTs	Single	1200 V/400 A	0.6	2
MCTs	Single	600 V/60 A	20k	0.4m
	Single	1200 V/400 A	20k	2.3
	Single	600 V/60 A	20k	2.2

A.C. Motor Control.

Topic -

TABLE 1.3 CHARACTERISTICS AND SYMBOLS OF SOME POWER DEVICES

Devices	Symbols	Characteristics
Diode		
Thyristor		
SITH		
GTO		
MCT		
TRIAC		
LASCR		
NPN BJT		
IGBT		
N-Channel MOSFET		
SIT		


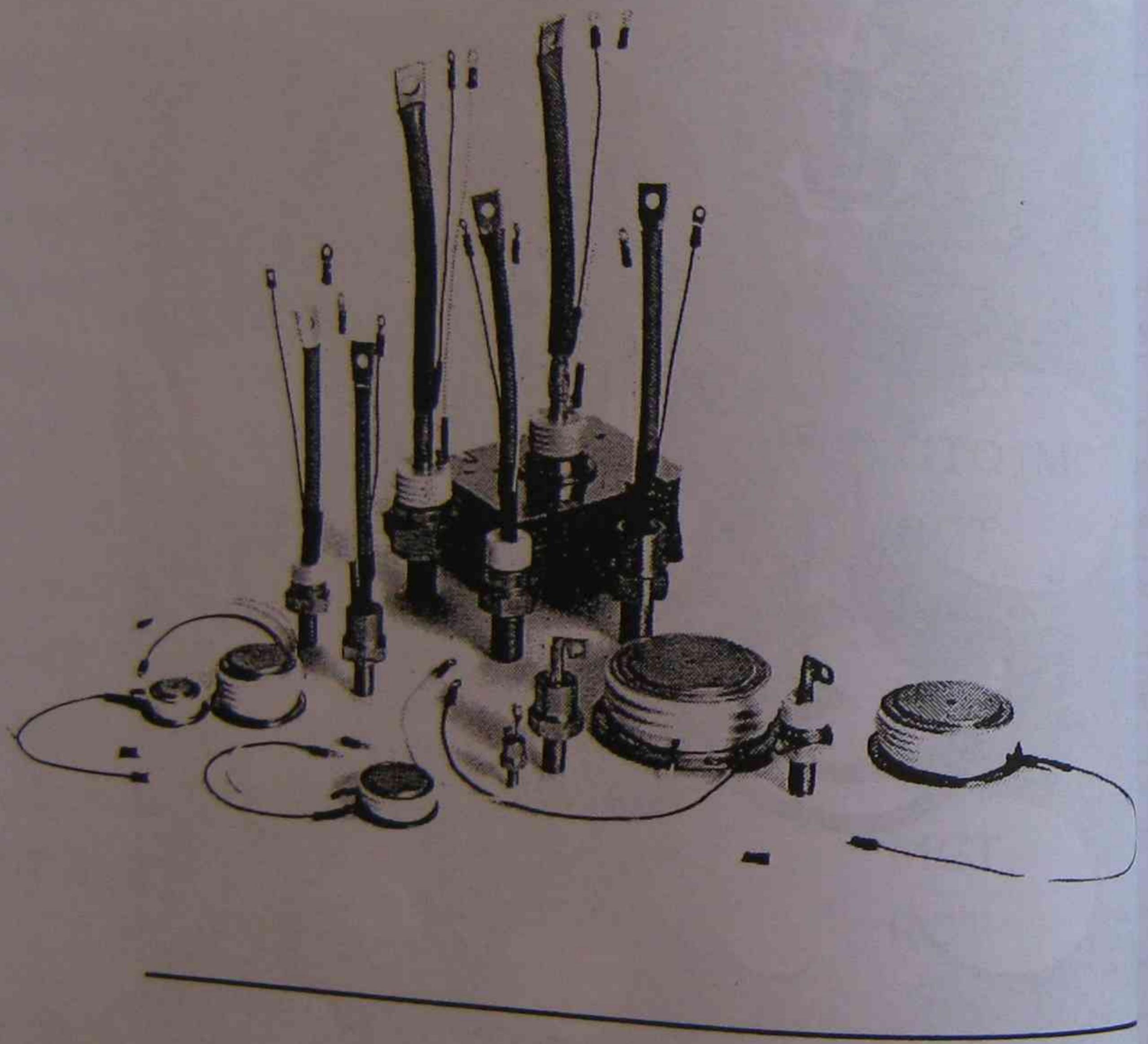


Figure 1-3 Various general-purpose diode configurations.
(Courtesy of Powerex, Inc.)

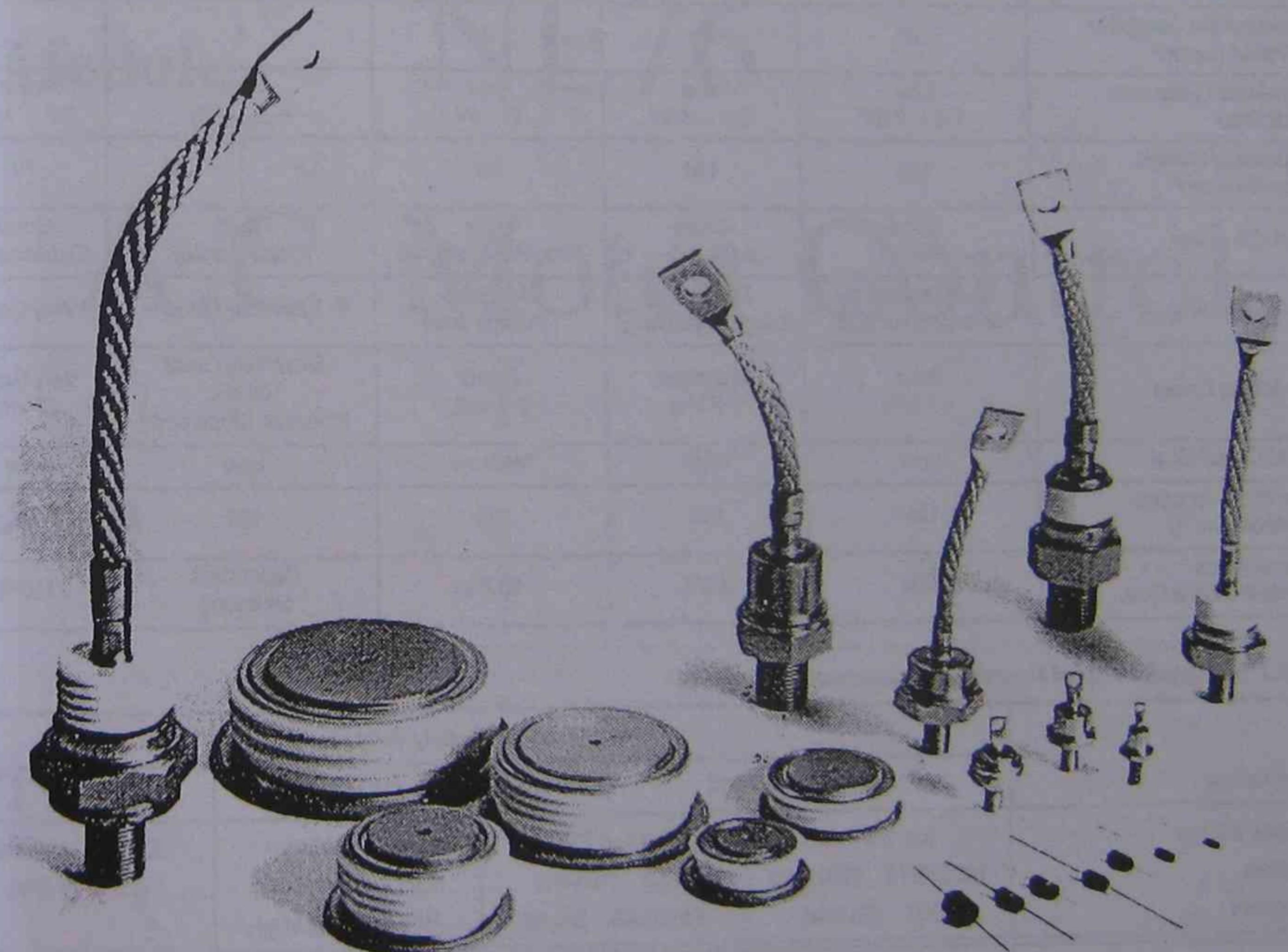

Sydney Institute of Technology

School of Electrotechnology

Learners Theory

Work Book

NET/6

Module

A.C. Motor Control

Area

Topic

Session No.

3.2

The devices in the following converters are used to illustrate the basic principles only. The switching action of a converter can be performed by more than one device. The choice of a particular device will depend on the voltage, current, and speed requirements of the converter.

Rectifiers. A diode rectifier circuit converts ac voltage into a fixed dc voltage and is shown in Fig. 1-8. The input voltage to the rectifier could be either single-phase or three-phase.


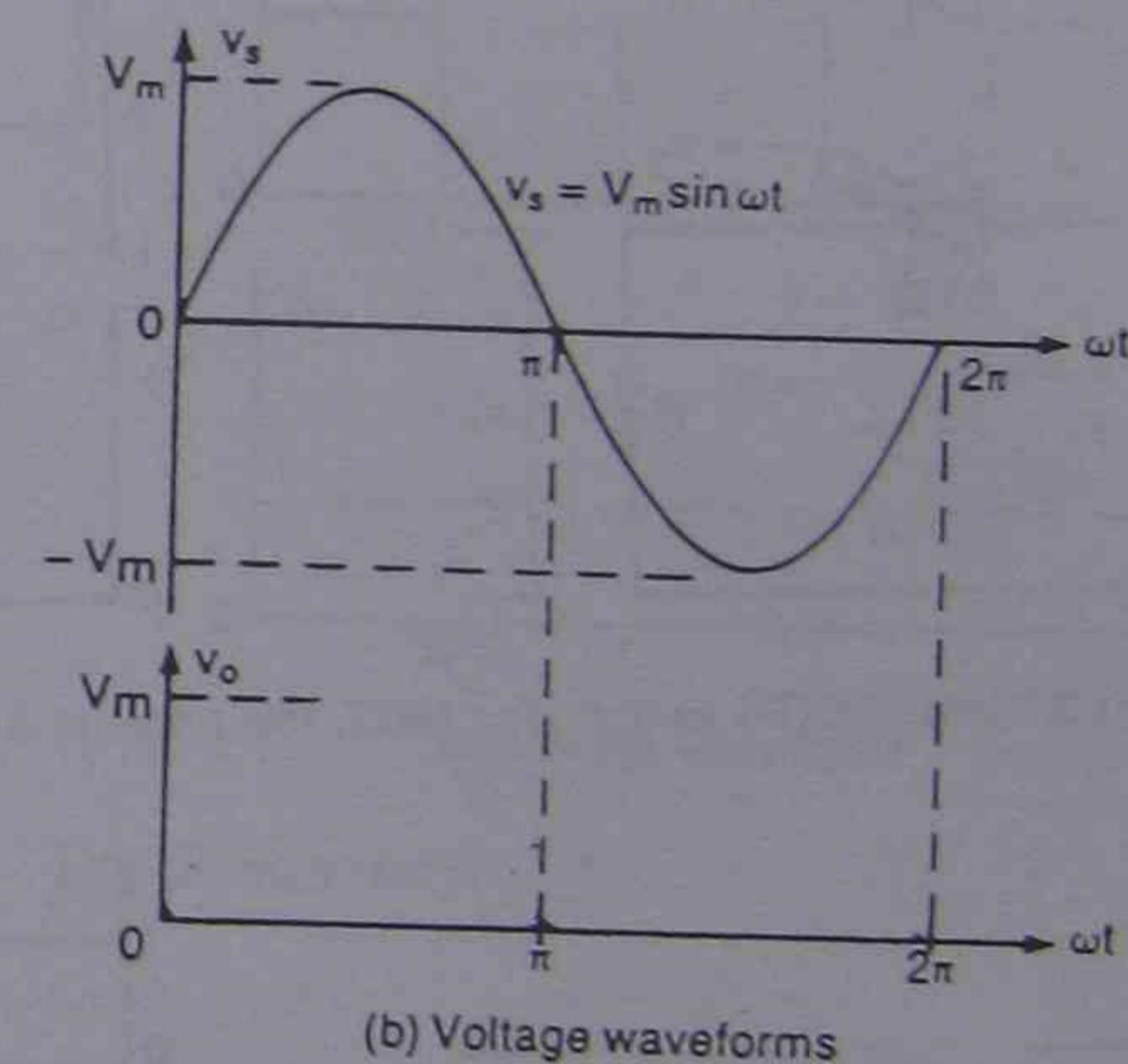
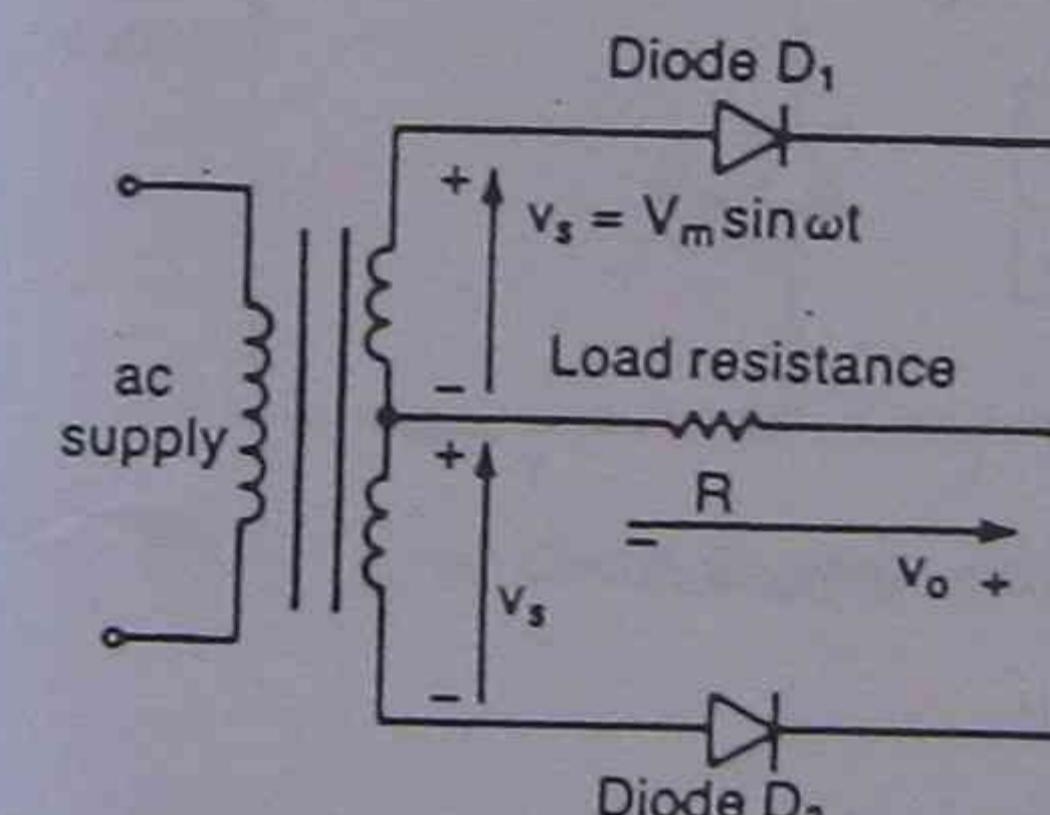


Figure 1-8 Single-phase rectifier circuit.

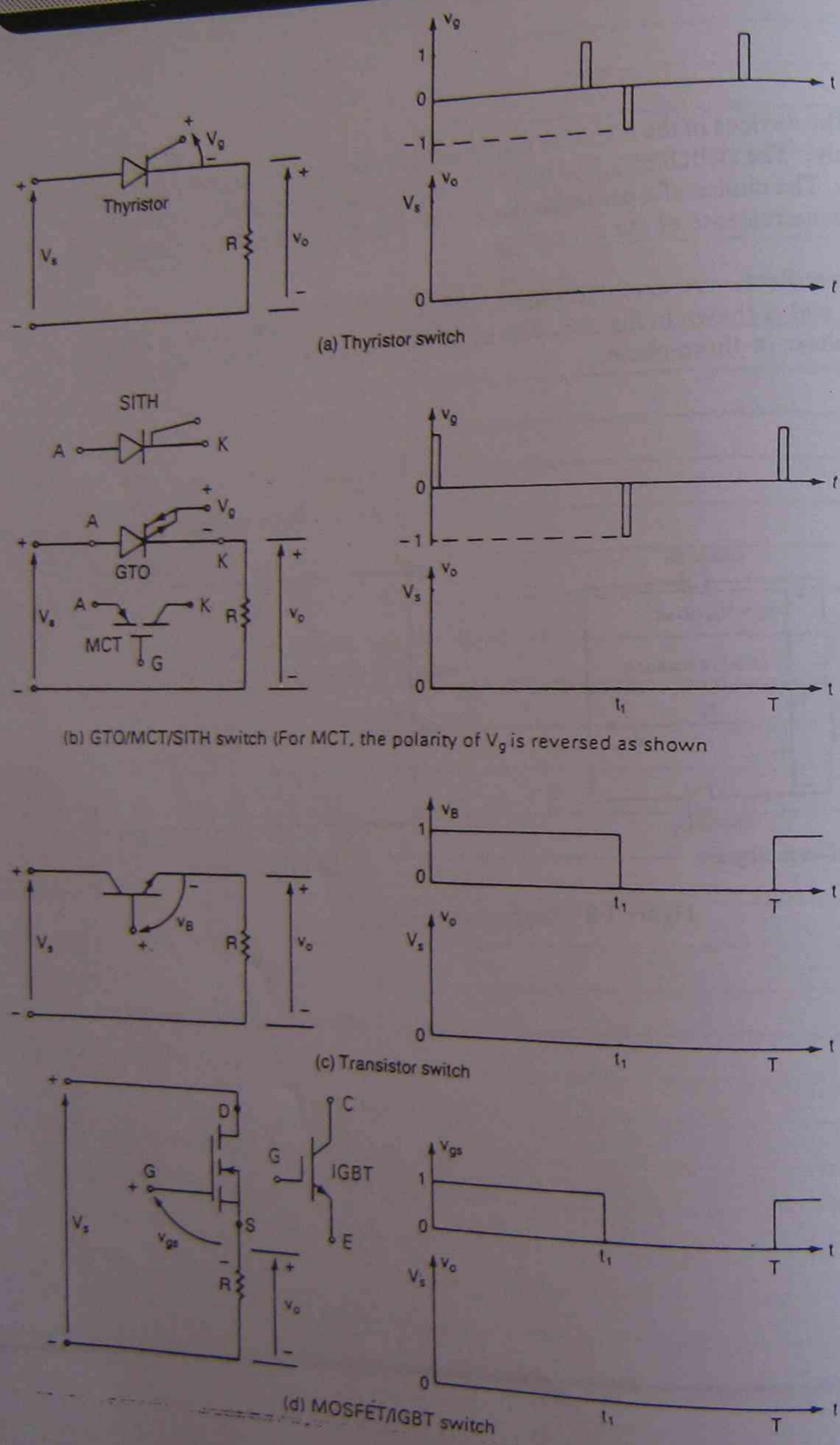

Dc-dc converters. A dc-dc converter is also known as a *chopper* or *switching regulator* and a transistor chopper is shown in Fig. 1-11. The average output voltage is controlled by varying the conduction time t_1 of transistor Q_1 . If T is the chopping period; then $t_1 = \delta T$. δ is called as the *duty cycle* of the chopper.

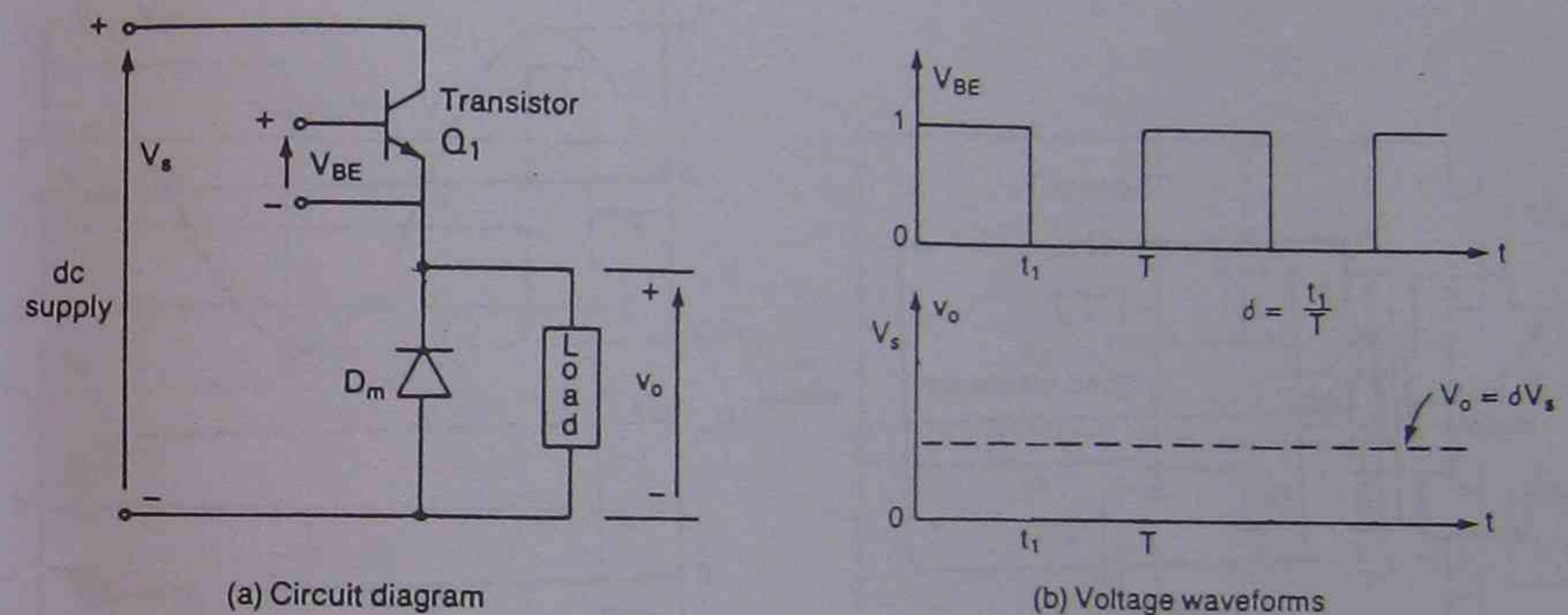


Figure 1-11 Dc-dc converter.

Topic -

Ac-dc converters. A single-phase converter with two natural commutated thyristors is shown in Fig. 1-9. The average value of the output voltage can be controlled by varying the conduction time of thyristors or firing delay angle, α . The input could be a single or three-phase source. These converters are also known as *controlled rectifiers*.

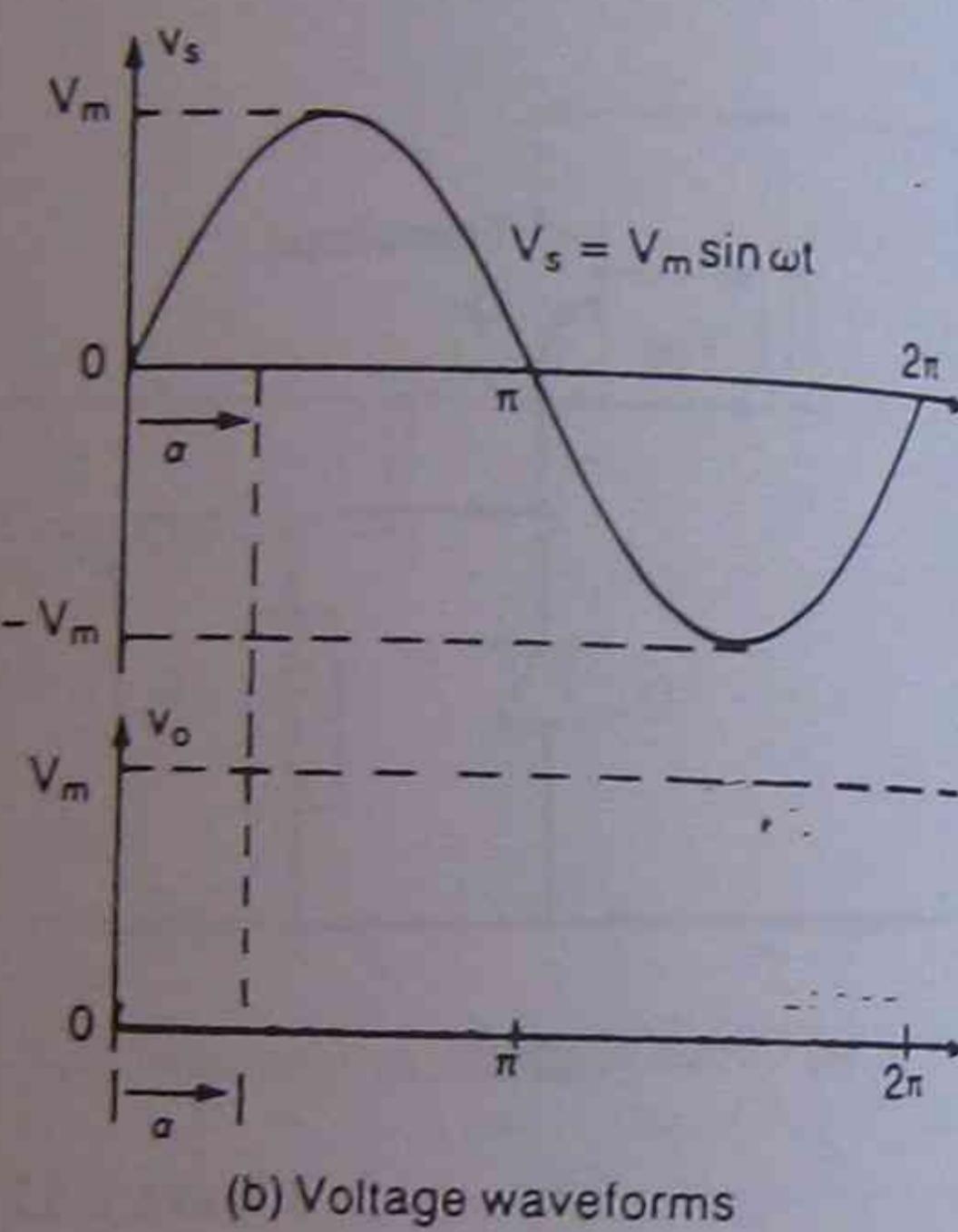
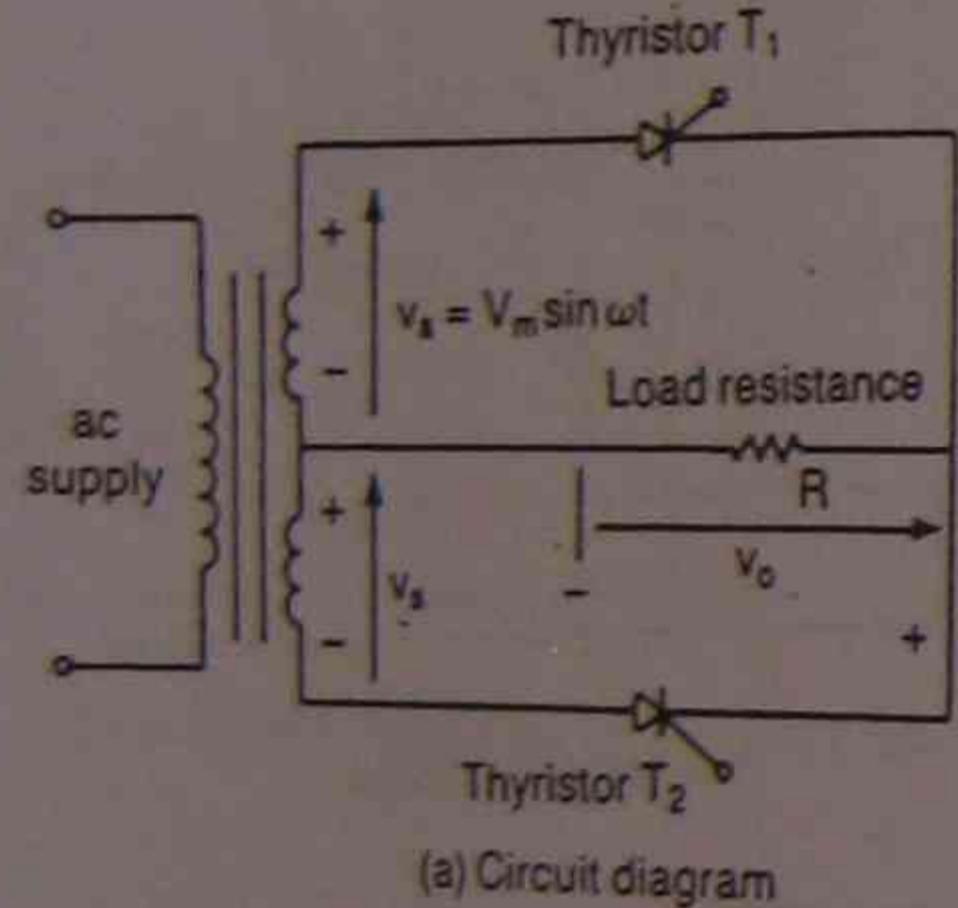


Figure 1-9 Single-phase ac-dc converter.

Topic -

Dc-ac converters. A dc-ac converter is also known as an *inverter*. A single-phase transistor inverter is shown in Fig. 1-12. If transistors M_1 and M_2 conduct for one-half period and M_3 and M_4 conduct for the other half, the output voltage is of alternating form. The output voltage can be controlled by varying the conduction time of transistors.

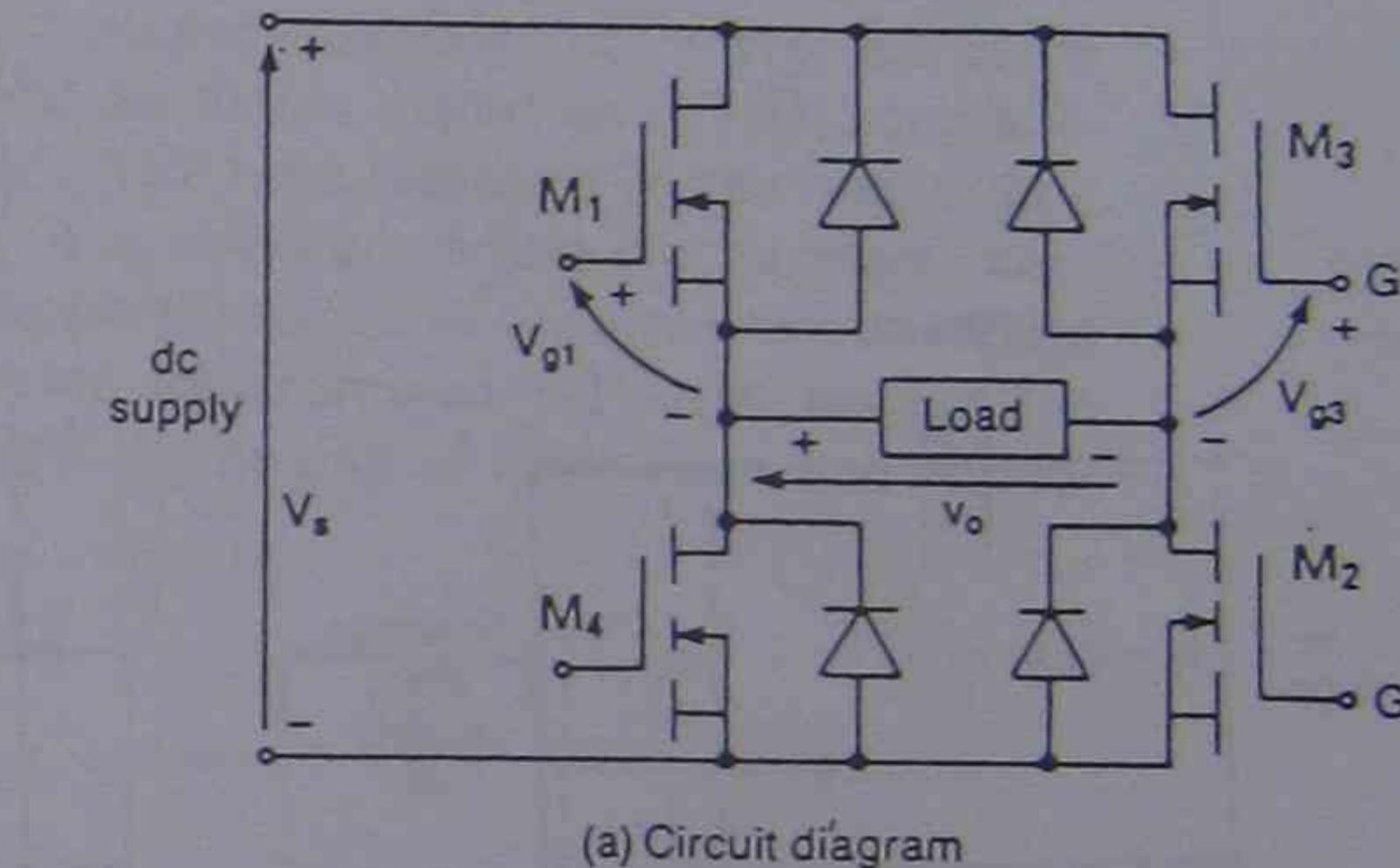
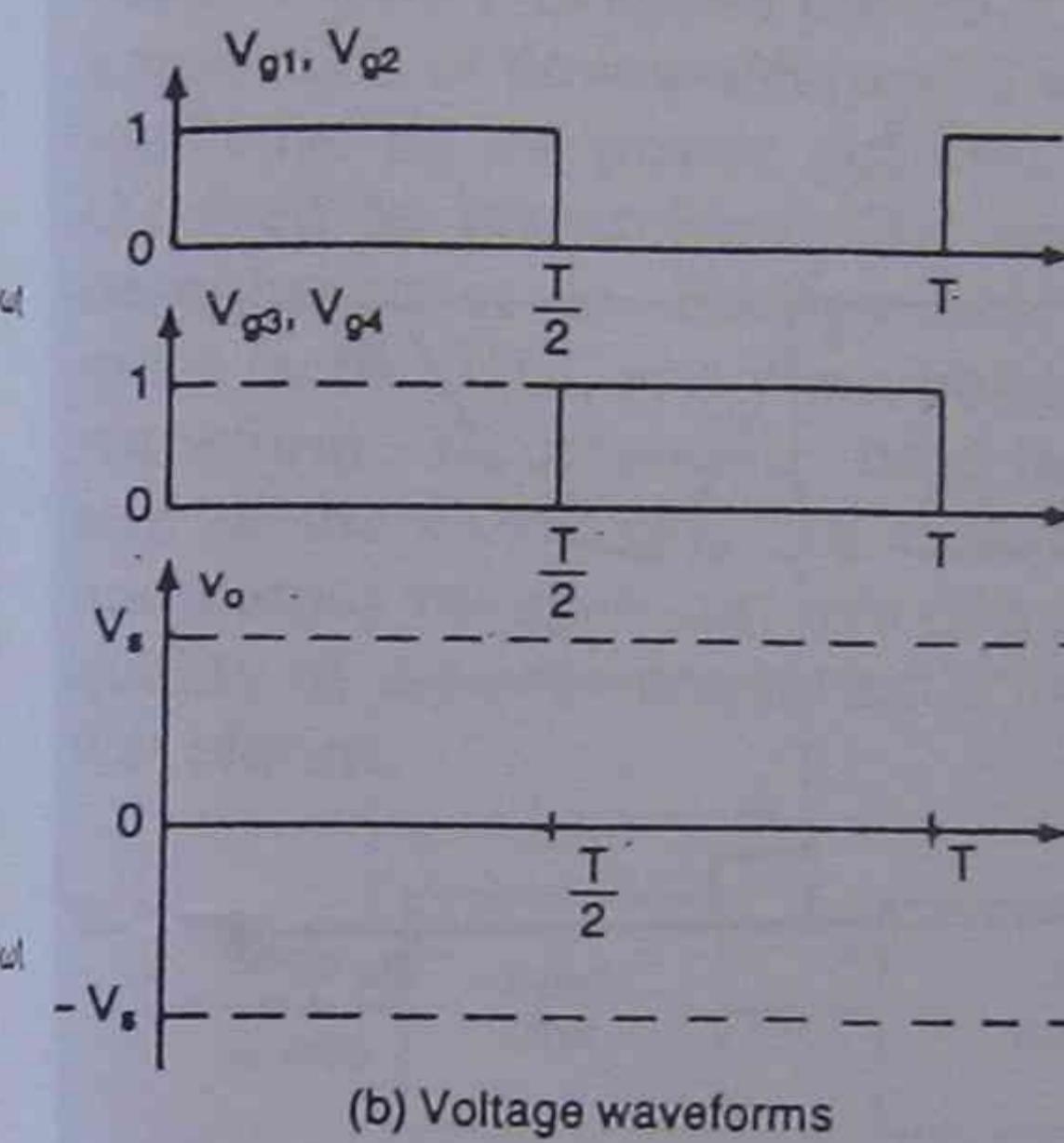


Figure 1-12 Single-phase dc-ac converter.

Topic -

Ac-ac converters. These converters are used to obtain a variable ac output voltage from a fixed ac source and a single-phase converter with a TRIAC is shown in Fig. 1-10. The output voltage is controlled by varying the conduction time of a TRIAC or firing delay angle, α . These types of converters are also known as *ac voltage controllers*.

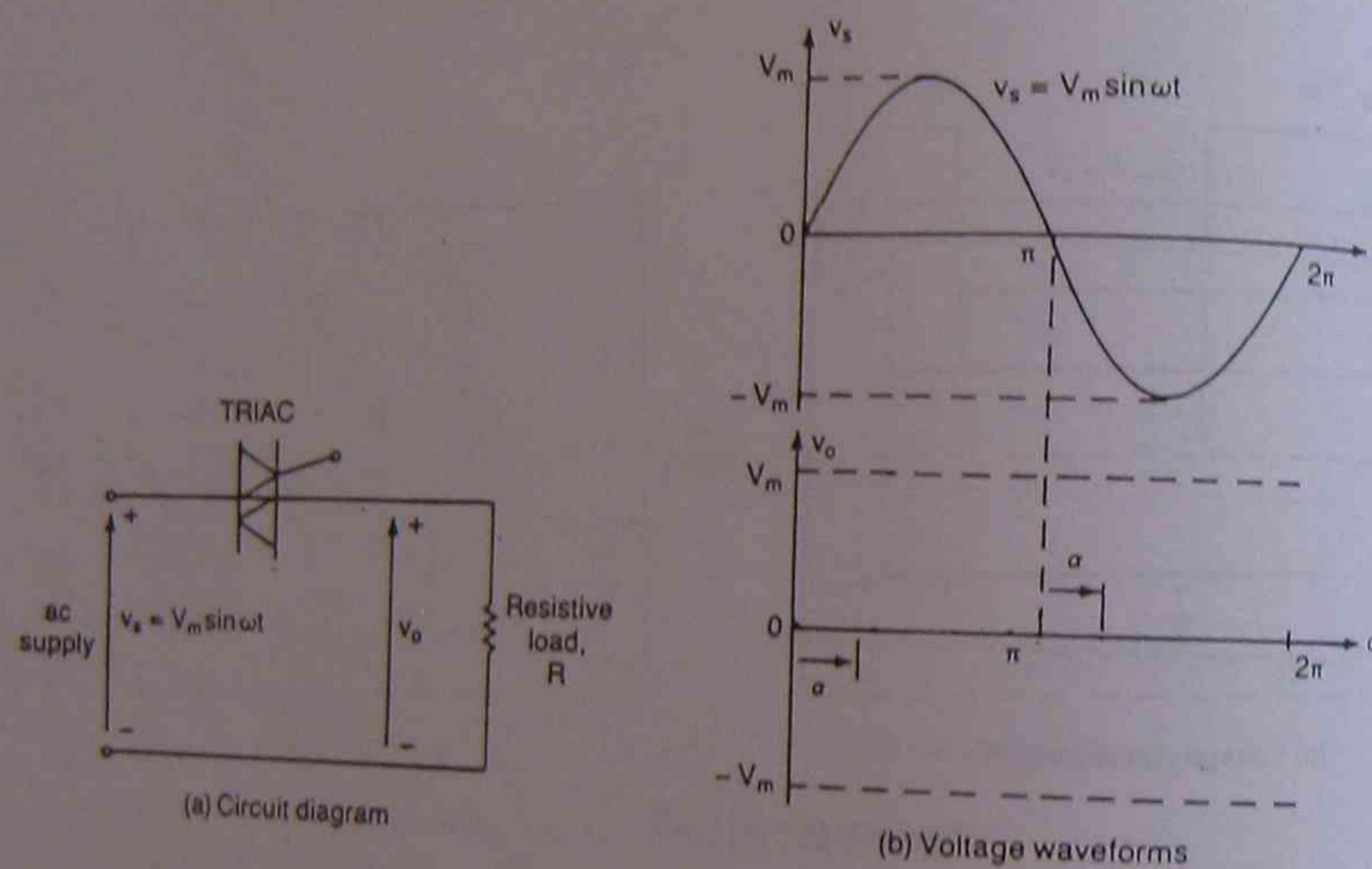


Figure 1-10 Single-phase ac-ac converter.

Topic -

The operations of the power converters are based mainly on the switching of power semiconductor devices; and as a result the converters introduce current and voltage harmonics into the supply system and on the output of the converters. These can cause problems of distortion of the output voltage, harmonic generation into the supply system, and interference with the communication and signaling circuits. It is normally necessary to introduce filters on the input and output of a converter system to reduce the harmonic level to an acceptable magnitude. Figure 1-13 shows the block diagram of a generalized power converter. The application of power electronics to supply the sensitive electronic loads poses a challenge on the power quality issues and raises problems and concerns to be resolved by researchers. The input and output quantities of converters could be either ac or dc. Factors such as total harmonic distortion (THD), displacement factor (HF), and input power factor (IPF) are measures of the quality of a waveform. To determine these factors, it is required to find the harmonic content of the waveforms. To evaluate the performance of a converter, the input and output voltages/currents of a converter are expressed in Fourier series. The quality of a power converter is judged by the quality of its voltage and current waveforms.

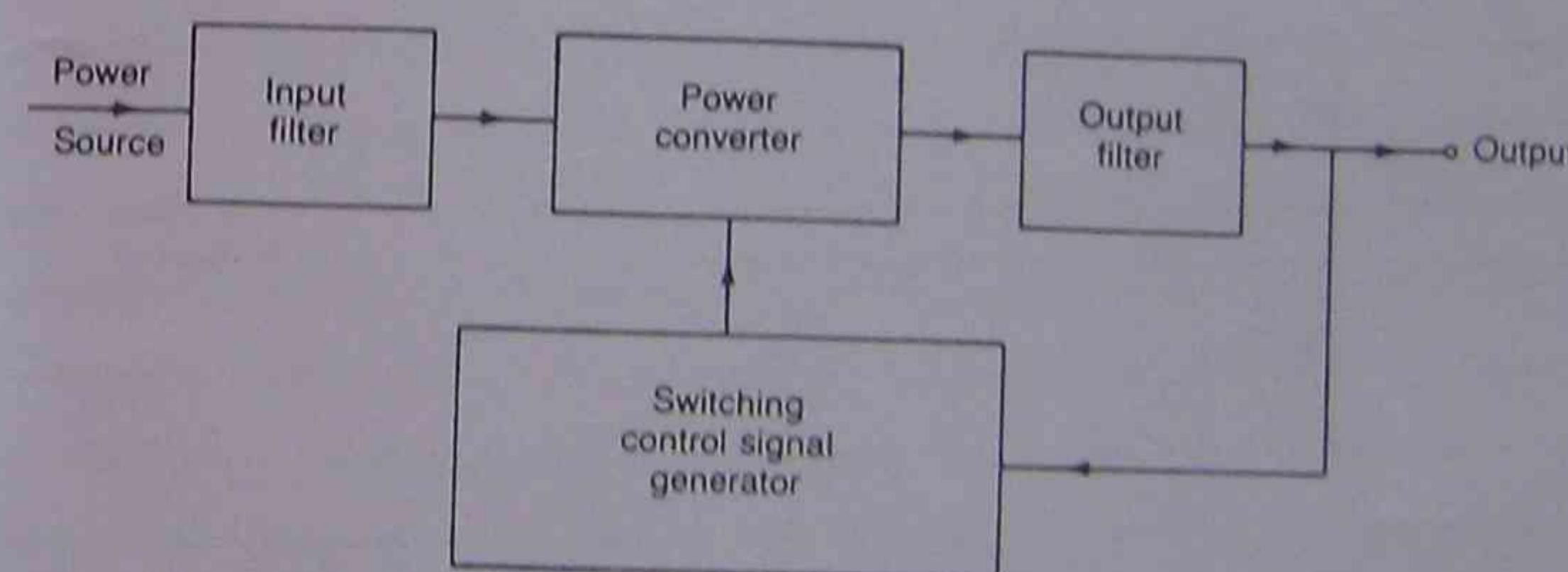


Figure 1-13 Generalized power converter system.

The control strategy for the power converters plays an important part on the harmonic generation and output waveform distortion, and can be aimed to minimize or reduce these problems. The power converters can cause radio-frequency interference due to electromagnetic radiation and the gating circuits may generate erroneous signals. This interference can be avoided by *grounded shielding*.

Learners Theory

Work Book



Module

NET6

A.C. Motor Control

Area

Topic

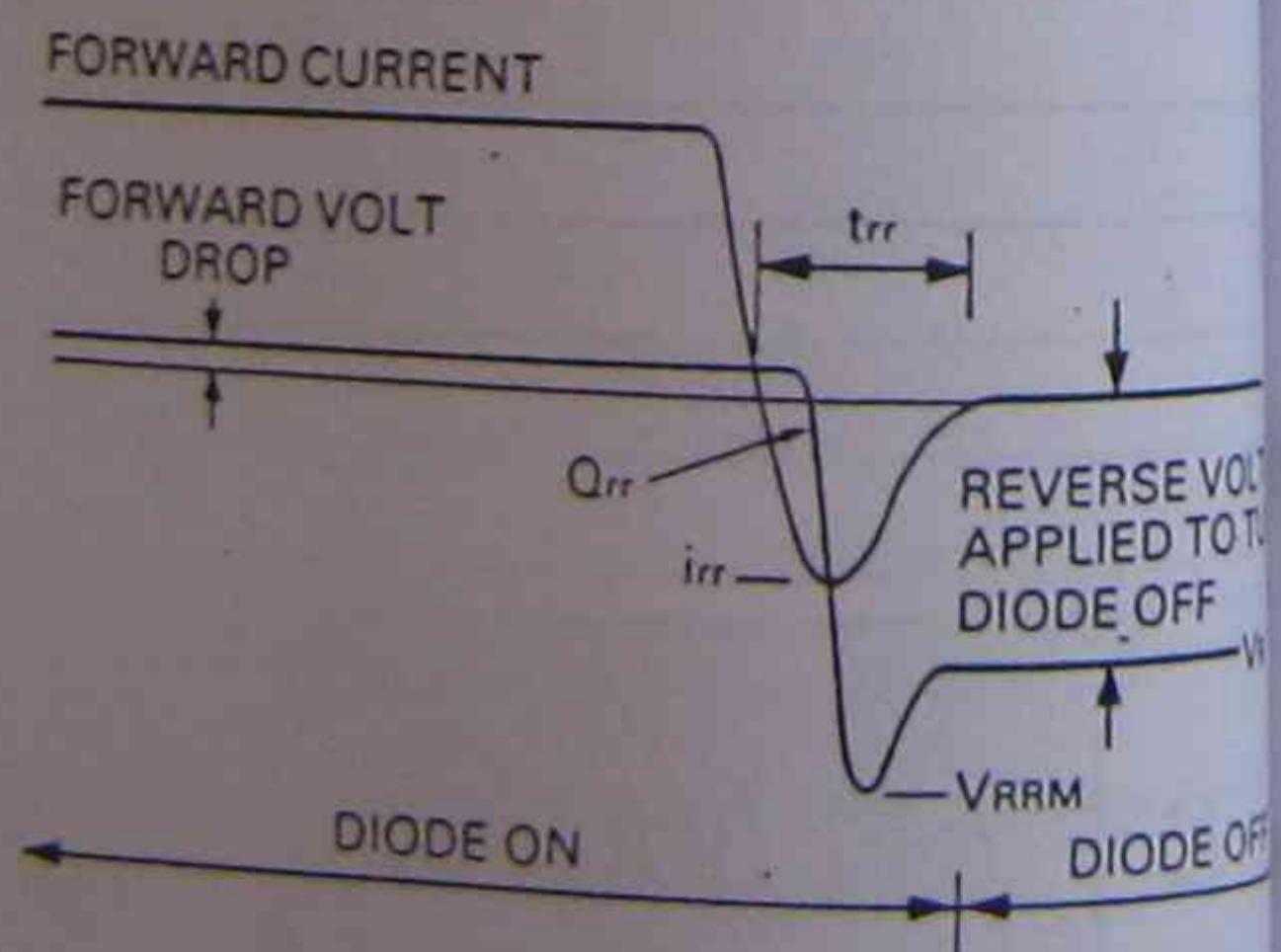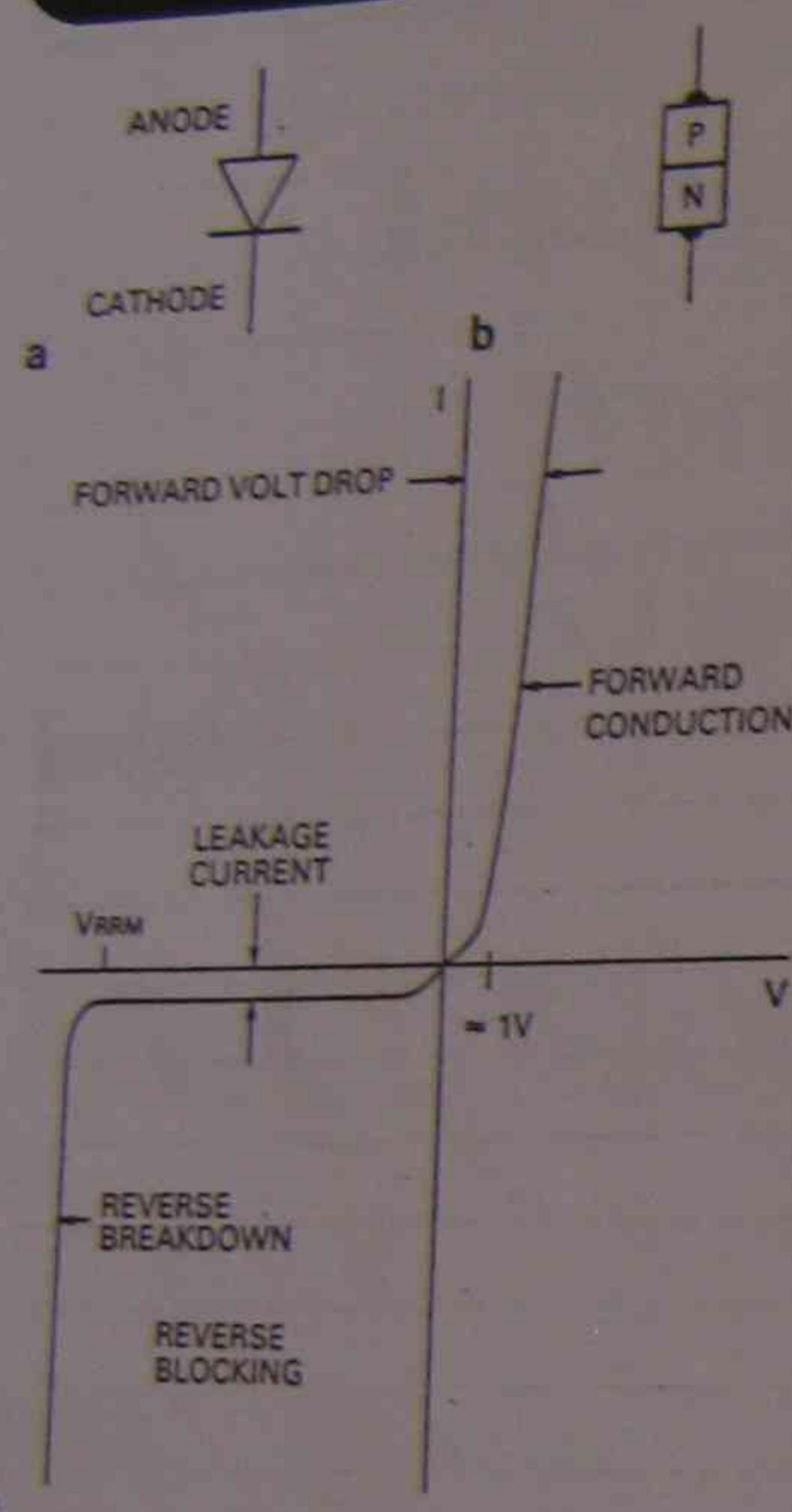

20.4 POWER DIODES

There are a number of diodes designed specifically to handle the high-power and high-temperature demands of some applications. The most frequent use of power diodes occurs in the rectification process, in which ac signals (having zero average value) are converted to ones having an average or dc level. As noted in Chapter 2, when used in this capacity, diodes are normally referred to as *rectifiers*.

The majority of the power diodes are constructed using silicon because of its higher current, temperature, and PIV ratings. The higher current demands require that the junction area be larger, to ensure that there is a low forward diode resistance. If the forward resistance were too large, the I^2R losses would be excessive. The current capability of power diodes can be increased by placing two or more in parallel and the PIV rating can be increased by stacking the diodes in series.

Various types of power diodes and their current rating have been provided in Fig. 20.12a. The high temperatures resulting from the heavy current require, in many cases, that heat sinks be used to draw the heat away from the element. A few of the various types of heat sinks available are shown in Fig. 20.12b. If heat sinks are not employed, stud diodes are designed to be attached directly to the chassis, which in turn will act as the heat sink.


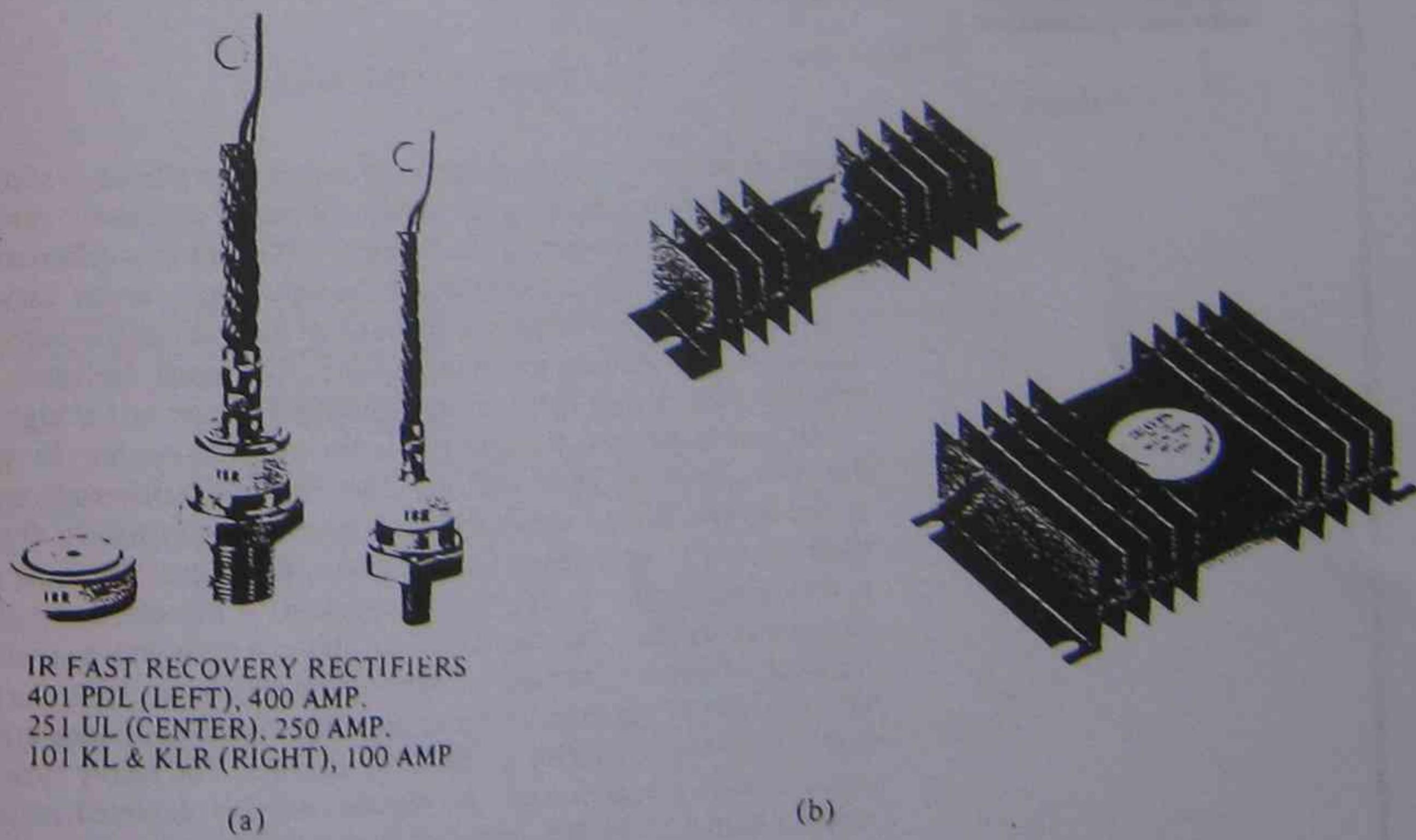



Figure 20.12 Power diodes and heat sinks. (Courtesy International Rectifier Corporation.)

A.C. Motor Control.

Topic -

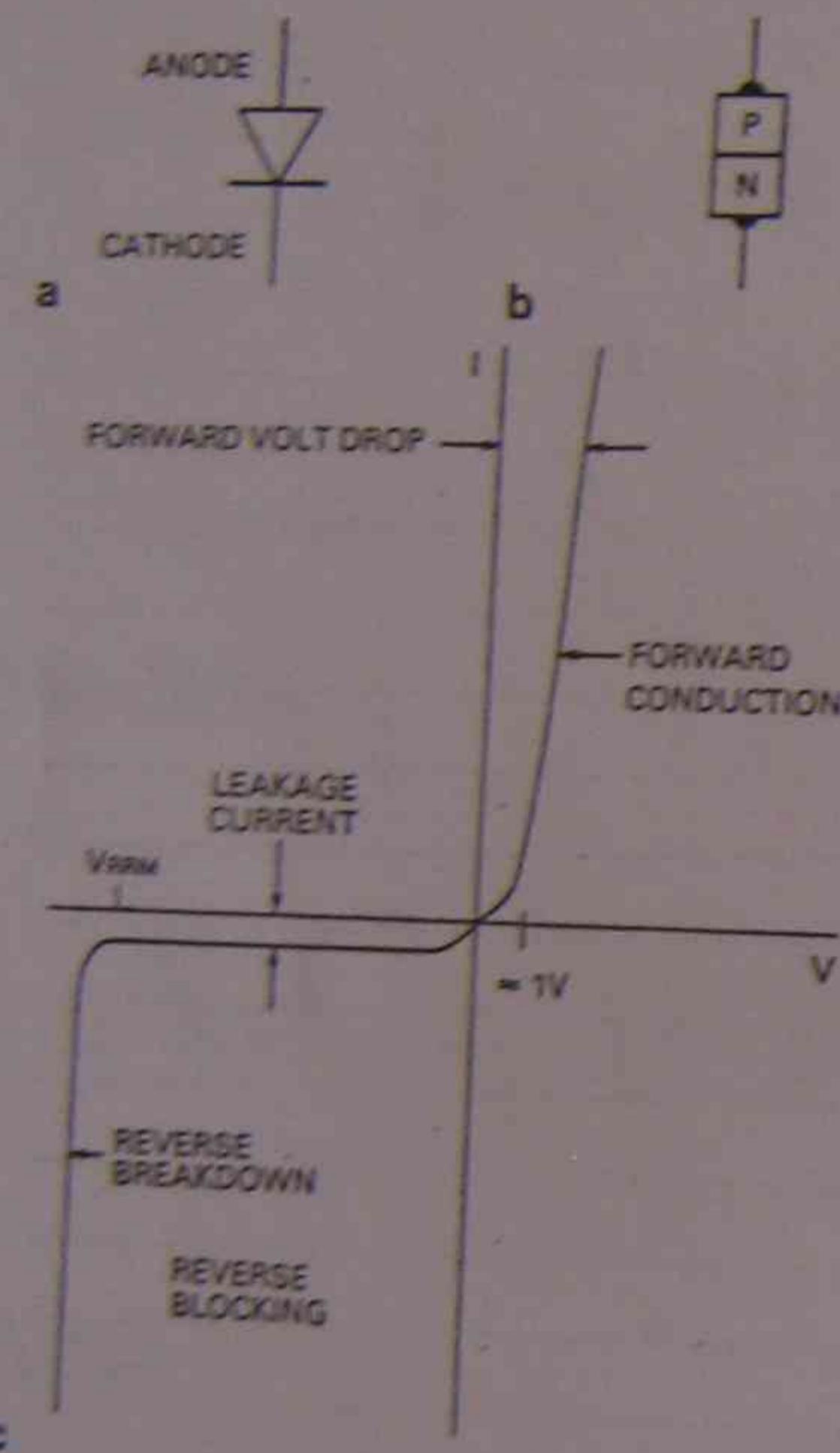

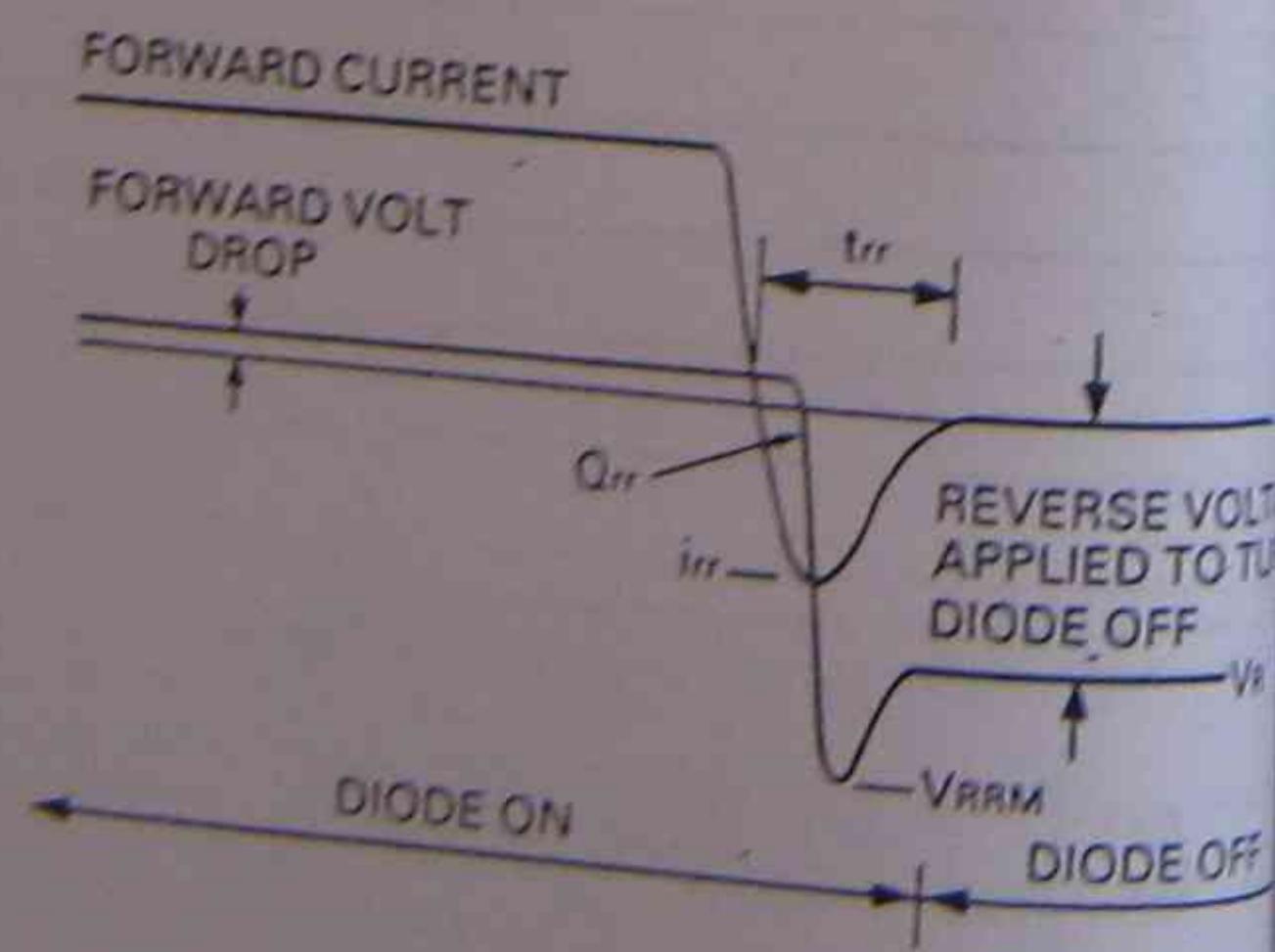1 Diode: a circuit symbol; b structure; c characteristic.



2 Switching characteristics of a diode

A.C. Motor Control.

Topic -

2

20.4 POWER DIODES

There are a number of diodes designed specifically to handle the high-power and high-temperature demands of some applications. The most frequent use of power diodes occurs in the rectification process, in which ac signals (having zero average value) are converted to ones having an average or dc level. As noted in Chapter 2, when used in this capacity, diodes are normally referred to as *rectifiers*.

The majority of the power diodes are constructed using silicon because of its higher current, temperature, and PIV ratings. The higher current demands require that the junction area be larger, to ensure that there is a low forward diode resistance. If the forward resistance were too large, the I^2R losses would be excessive. The current capability of power diodes can be increased by placing two or more in parallel and the PIV rating can be increased by stacking the diodes in series.

Various types of power diodes and their current rating have been provided in Fig. 20.12a. The high temperatures resulting from the heavy current require, in many cases, that heat sinks be used to draw the heat away from the element. A few of the various types of heat sinks available are shown in Fig. 20.12b. If heat sinks are not employed, stud diodes are designed to be attached directly to the chassis, which in turn will act as the heat sink.

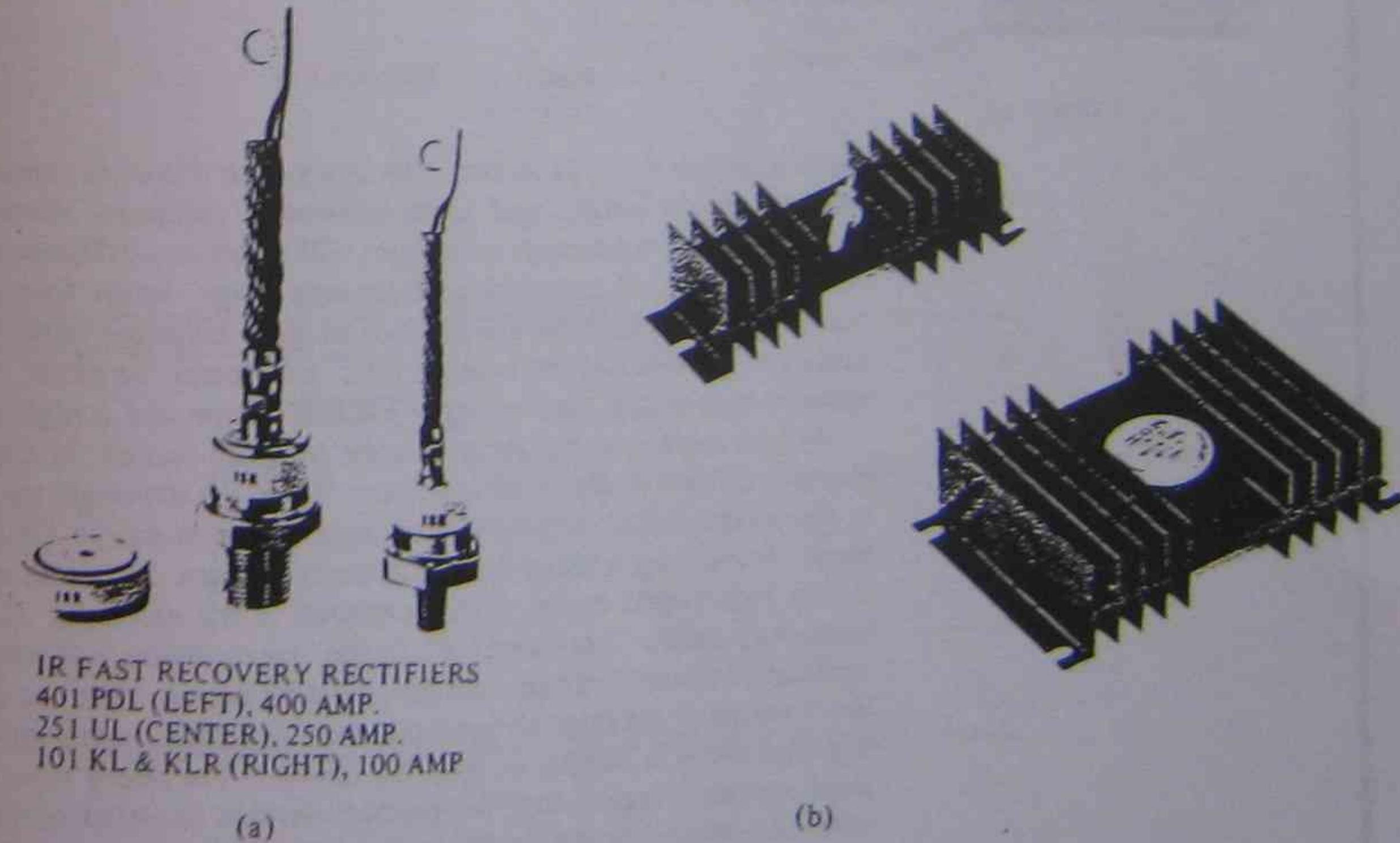


Figure 20.12 Power diodes and heat sinks. (Courtesy International Rectifier Corporation.)

20.2 SCHOTTKY BARRIER (HOT-CARRIER) DIODES

In recent years there has been increasing interest in a two-terminal device referred to as a *Schottky-barrier*, *surface-barrier*, or *hot-carrier* diode. Its areas of application were first limited to the very high frequency range due to its quick response time (especially important at high frequencies) and a lower noise figure (a quantity of real importance in high-frequency applications). In recent years, however, it is appearing more and more in low-voltage/high-current power supplies and ac-to-dc converters. Other areas of application of the device include radar systems, Schottky TTL logic for computers, mixers and detectors in communication equipment, instrumentation, and analog-to-digital converters.

Its construction is quite different from the conventional *p-n* junction in that a metal-semiconductor junction is created such as shown in Fig. 20.1. The semicon-

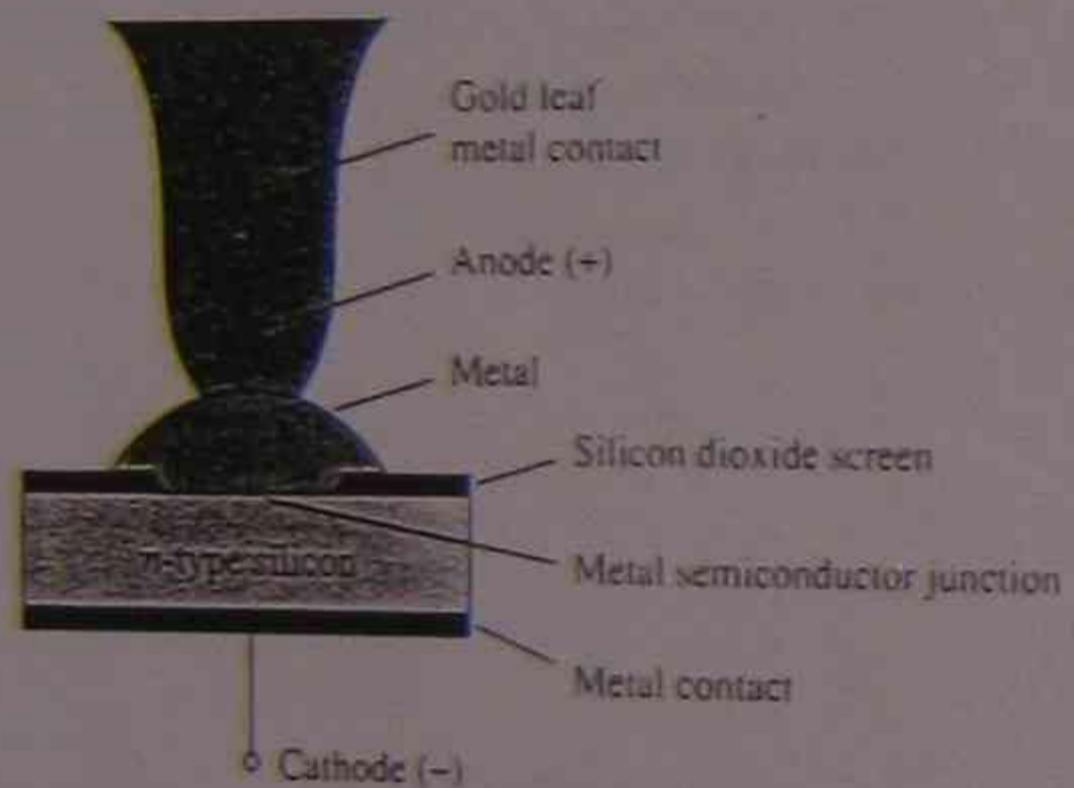


Figure 20.1 Passivated hot-carrier diode.

ductor is normally *n*-type silicon (although *p*-type silicon is sometimes used), while host of different metals, such as molybdenum, platinum, chrome, or tungsten, are used. Different construction techniques will result in a different set of characteristics for the device, such as increased frequency range, lower forward bias, and so on. Priorities do not permit an examination of each technique here, but information can usually be provided by the manufacturer. In general, however, Schottky diode construction results in a more uniform junction region and a high level of ruggedness.

In both materials, the electron is the majority carrier. In the metal, the level of minority carriers (holes) is insignificant. When the materials are joined the electrons in the *n*-type silicon semiconductor material immediately flow into the adjoining metal, establishing a heavy flow of majority carriers. Since the injected carriers have a very high kinetic energy level compared to the electrons of the metal, they are commonly called "hot carriers." In the conventional *p-n* junction there was no injection of minority carriers into the adjoining region. Here the electrons are injected into a region of the same electron plurality. Schottky diodes are therefore unique in that conduction is entirely by majority carriers. The heavy flow of electrons into the metal creates a region near the junction surface depleted of carriers in the silicon material—much like the depletion region in the *p-n* junction diode. The additional carriers in the metal establish a "negative wall" in the metal at the boundary between the two materials. The net result is a "surface barrier" between the two materials, preventing any further current. That is, any electrons (negatively charged) in the silicon material face a carrier-free region and a "negative wall" at the surface of the metal.

The application of a forward bias as shown in the first quadrant of Fig. 20.2 will reduce the strength of the negative barrier through the attraction of the applied positive potential for electrons from this region. The result is a return to the heavy flow of electrons across the boundary, the magnitude of which is controlled by the level of the applied bias potential. The barrier at the junction for a Schottky diode is less than that of the *p-n* junction device in both the forward- and reverse-bias regions. The result is therefore a higher current at the same applied bias in the forward- and reverse-bias regions. This is a desirable effect in the forward-bias region but highly undesirable in the reverse-bias region.

The exponential rise in current with forward bias is described by Eq. (1.4) but with η dependent on the construction technique (1.05 for the metal whisker type of

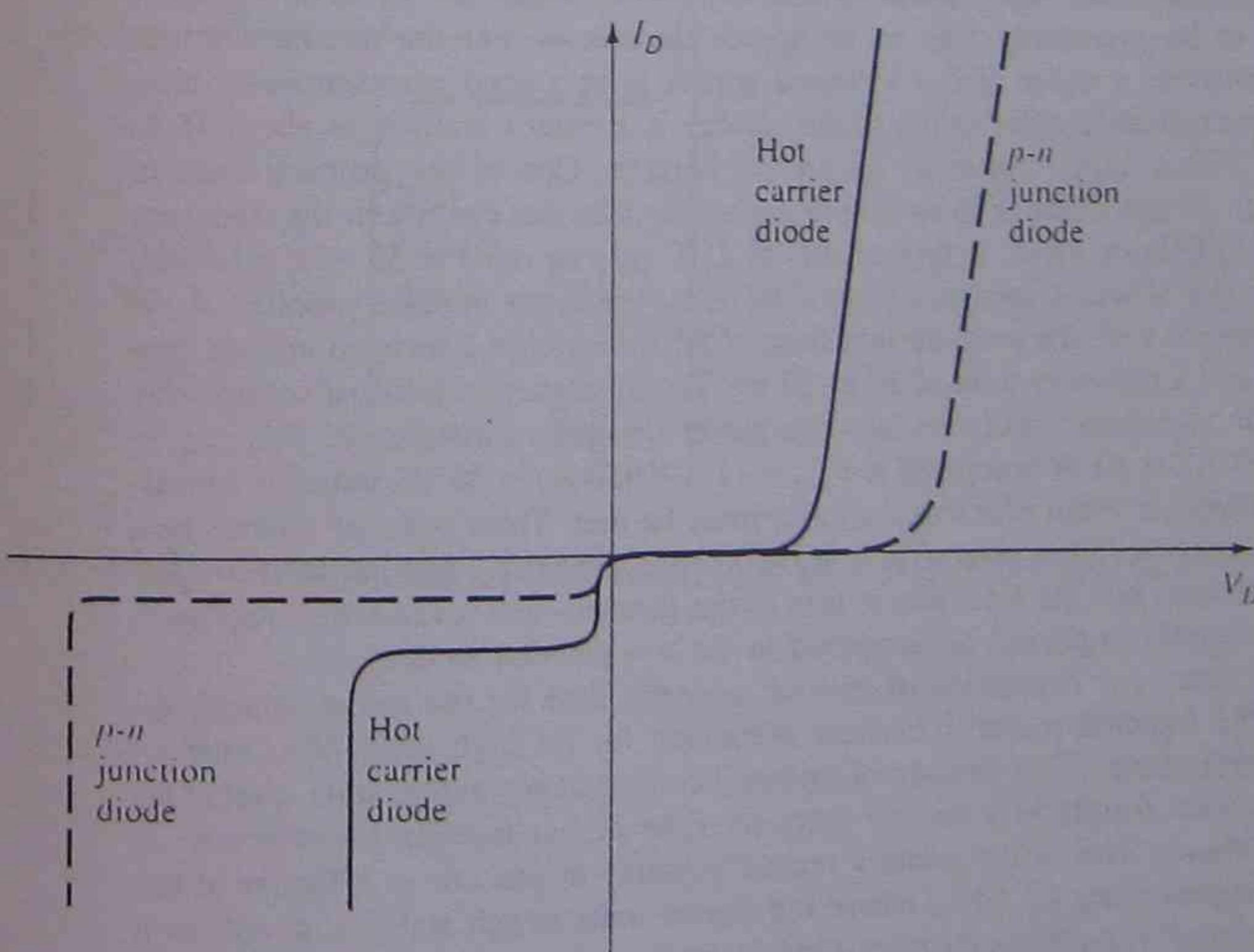


Figure 20.2 Comparison of characteristics of hot-carrier and *p-n* junction diodes.

A.C. Motor Control.

Topic -

A.C. Motor Control.

Topic -

construction, which is somewhat similar to the germanium diode). In the reverse-bias region the current I_s is due primarily to those electrons in the metal passing into the semiconductor material. One of the areas of continuing research on the Schottky diode centers on reducing the high leakage currents that result with temperatures over 100°C. Through design, improvement units are now becoming available that have a temperature range from -65 to +150°C. At room temperature, I_s is typically in the microampere range for low-power units and milliamperes range for high-power devices, although it is typically larger than that encountered using conventional p-n junction devices with the same current limits. In addition, the PIV of Schottky diodes is usually significantly less than that of a comparable p-n junction unit. Typically, for a 50-A unit, the PIV of the Schottky diode would be about 50 V as compared to 150 V for the p-n junction variety. Recent advances, however, have resulted in Schottky diodes with PIVs greater than 100 V at this current level. It is obvious from the characteristics of Fig. 20.2 that the Schottky diode is closer to the ideal set of characteristics than the point contact and has levels of V_T less than the typical silicon semiconductor p-n junction. The level of V_T for the "hot-carrier" diode is controlled to a large measure by the metal employed. There exists a required trade-off between temperature range and level of V_T . An increase in one appears to correspond to a resulting increase in the other. In addition, the lower the range of allowable current levels, the lower the value of V_T . For some low-level units, the value of V_T can be assumed to be essentially zero on an approximate basis. For the middle and high range, however, a value of 0.2 V would appear to be a good representative value.

The maximum current rating of the device is presently limited to about 75 A, although 100-A units appear to be on the horizon. One of the primary areas of application of this diode is in switching power supplies that operate in the frequency range of 20 kHz or more. A typical unit at 25°C may be rated at 50 A at a forward voltage of 0.6 V with a recovery time of 10 ns for use in one of these supplies. A p-n junction device with the same current limit of 50 A may have a forward voltage drop of 1.1 V and a recovery time of 30 to 50 ns. The difference in forward voltage may not appear significant, but consider the power dissipation difference: $P_{\text{hot carrier}} = (0.6 \text{ V})(50 \text{ A}) = 30 \text{ W}$ compared to $P_{\text{p-n}} = (1.1 \text{ V})(50 \text{ A}) = 55 \text{ W}$, which is a measurable difference when efficiency criteria must be met. There will, of course, be a higher dissipation in the reverse-bias region for the Schottky diode due to the higher leakage current, but the total power loss in the forward- and reverse-bias regions is still significantly improved as compared to the p-n junction device.

Recall from our discussion of reverse recovery time for the semiconductor diode that the injected minority carriers accounted for the high level of t_{rr} (the reverse recovery time). The absence of minority carriers at any appreciable level in the Schottky diode results in a reverse recovery time of significantly lower levels, as indicated above. This is the primary reason Schottky diodes are so effective at frequencies approaching 20 GHz, where the device must switch states at a very high rate. For higher frequencies the point-contact diode, with its very small junction area, is still employed.

The equivalent circuit for the device (with typical values) and a commonly used symbol appear in Fig. 20.3. A number of manufacturers prefer to use the standard diode symbol for the device, since its function is essentially the same. The inductance L_p and capacitance C_p are package values, and r_s is the series resistance, which includes the contact and bulk resistance. The resistance r_d and capacitance C_d are values defined by equations introduced in earlier sections. For many applications, an excellent approximate equivalent circuit simply includes an ideal diode in parallel with the junction capacitance as shown in Fig. 20.4.

A number of hot-carrier rectifiers manufactured by Motorola Semiconductor Products, Inc., appear in Fig. 20.5 with their specifications and terminal identifica-

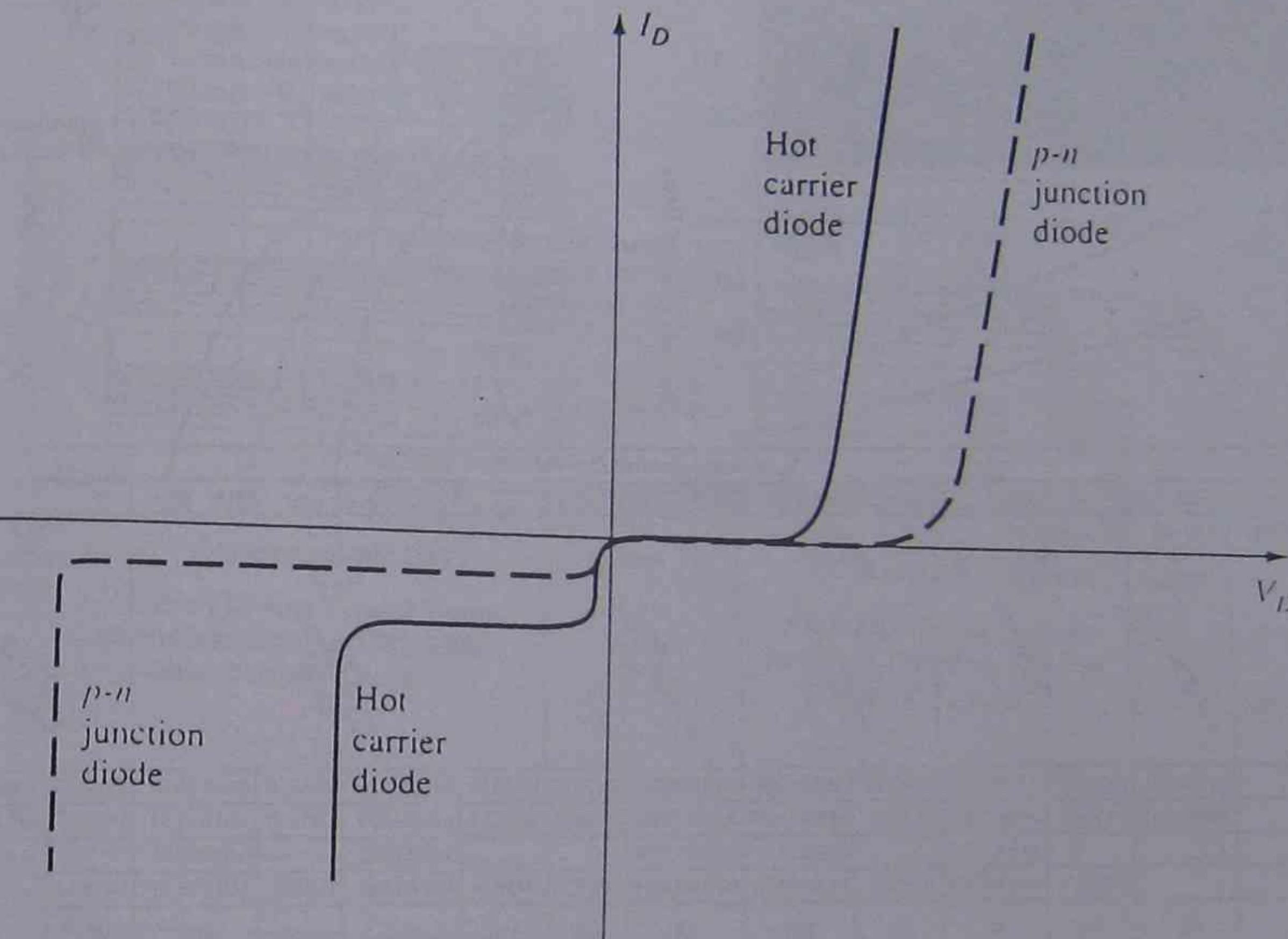


Figure 20.2 Comparison of characteristics of hot-carrier and p-n junction diodes.

A.C. Motor Control.

Topic -

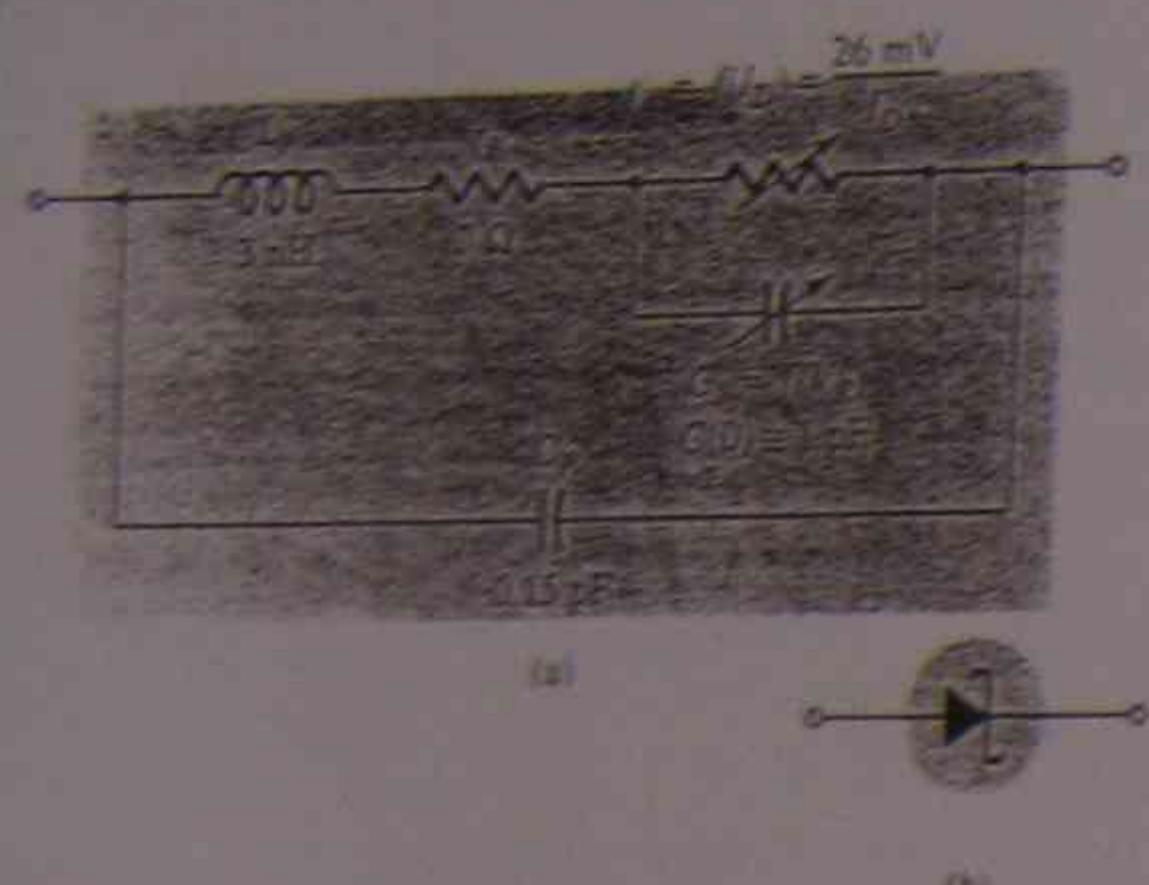


Figure 20.3 Schottky (hot-carrier) diode: (a) equivalent circuit, (b) symbol.

		I ₀ : Average rectified forward current (amperes)							
	Case	0.5 A	1.0 A	3.0 A	3.0 A	5.0 A	15 A	25 A	40 A
1	51-02 (DO-7) Glass	29-04 Plastic	267 Plastic	60 Metal	257 (DO-4) Metal	257 (DO-5) Metal			
20	MBR020	IN5817	MBR120P	IN5830	MBR320P	IN5823	IN5826	MBR1520	IN5829
30	MBR030	IN5818	MBR130P	IN5831	MBR330M	IN5824	IN5827	MBR1530	IN5830
35			MBR135P		MBR335P			MBR2530	IN5833
40			2N5819	MBR140P	IN5822	MBR340M	IN5825	IN5828	MBR40
I ₀ (Amps)	0.5	1.0	3.0	3.0	5.0	15	25	40	
V _F @ I ₀ = I ₀ /2 (Volts)	0.50	0.60	0.60	0.60	0.45 V@5A	0.38 V	0.50 V	0.55 V	
T _J Max (°C)	125°C	125°C	125°C	125°C	125°C	125°C	125°C	125°C	
Max I _R @ I ₀ = I ₀ /2 (V)	0.50 V	0.60 V	0.60 V	0.60 V	0.45 V@5A	0.38 V	0.50 V	0.55 V	

Schottky barrier devices, ideal for use in low-voltage, high-frequency power supplies and as free-wheeling diodes. These units feature very low forward voltages and switching times estimated at less than 10 ns. They are affected by current ratings of 0.5 to 5.0 amperes and in voltages to 40.

Peak reverse peak voltage
Peak reverse current, surge peak
Peak reverse current, maximum

Figure 20.5 Motorola Schottky barrier devices. (Courtesy: Motorola Semiconductor Products Incorporated.)

Note: Note that the maximum forward voltage drop V_F does not exceed 0.65 V for any of the devices, while this was essentially V_F for a silicon diode.

Three sets of curves for the Hewlett-Packard 5082-2300 series of general-purpose Schottky barrier diodes are provided in Fig. 20.6. Note at $T = 100^\circ\text{C}$ in Fig. 20.6a that V_F is only 0.1 V at a current of 0.01 mA. Note also that the reverse current has been limited to nanoamperes in Fig. 20.6b and the capacitance to 1 pF in Fig. 20.6c to ensure a high switching rate.

A.C. Motor Control.

Topic -



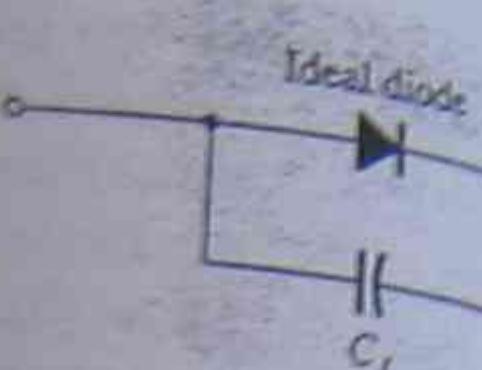


Figure 20.4 Approximate equivalent circuit for the Schottky diode.

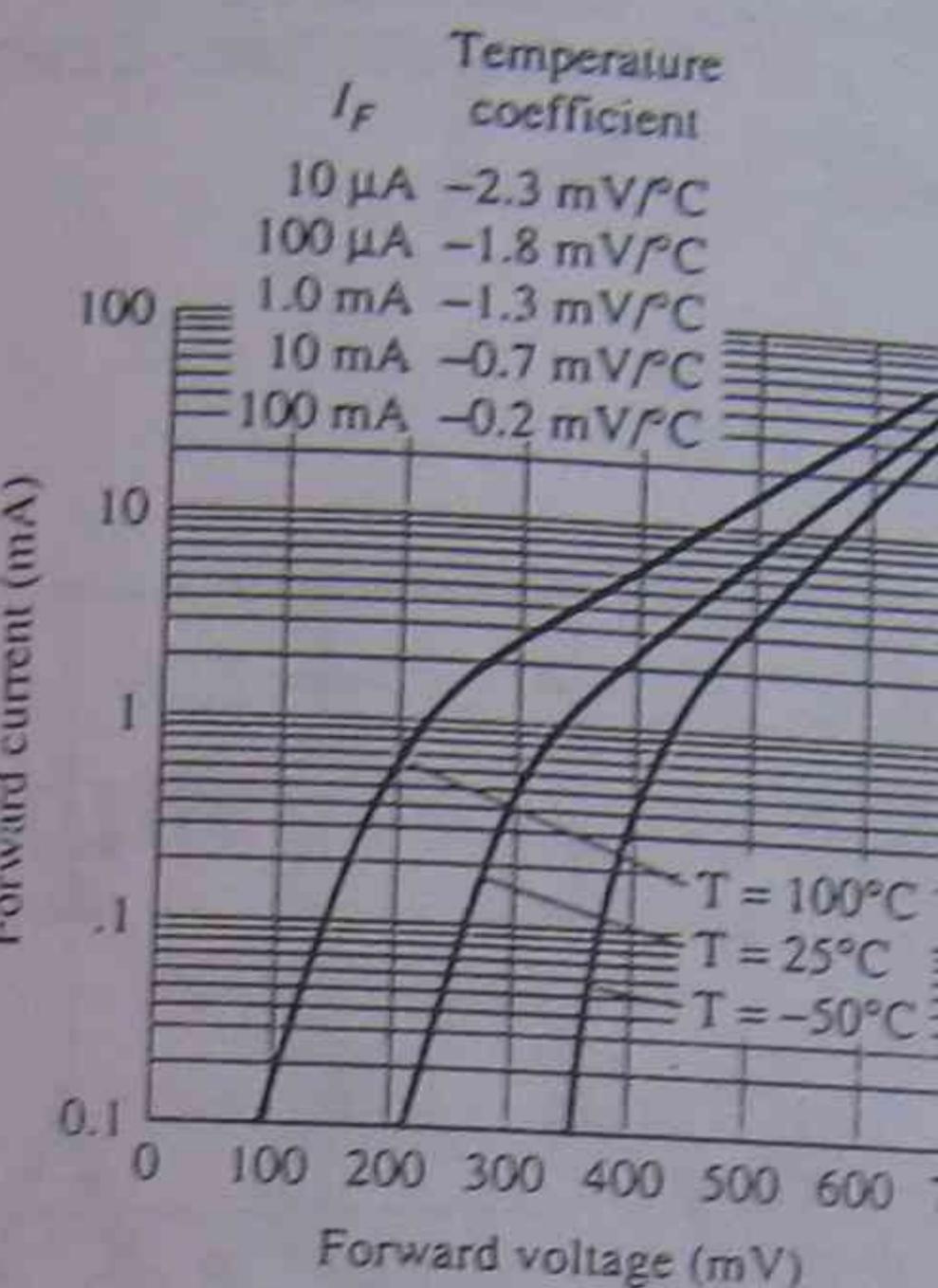


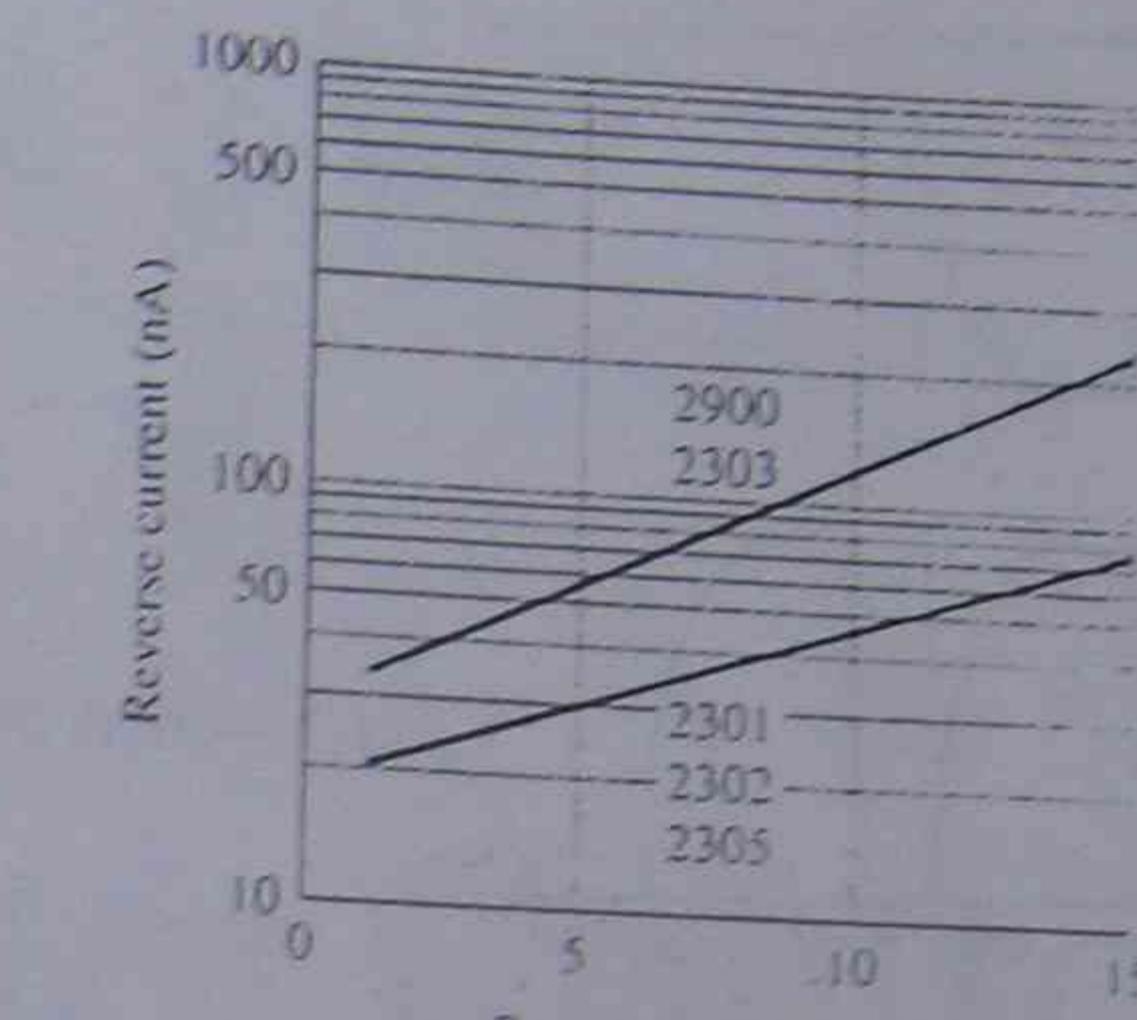I-V Curve Showing Typical Temperature Variation for 5082-2300 Series Schottky Diodes.



5082-2300 Series Typical Reverse Current vs. Reverse Voltage at $T_A = 25^\circ\text{C}$.

(a)

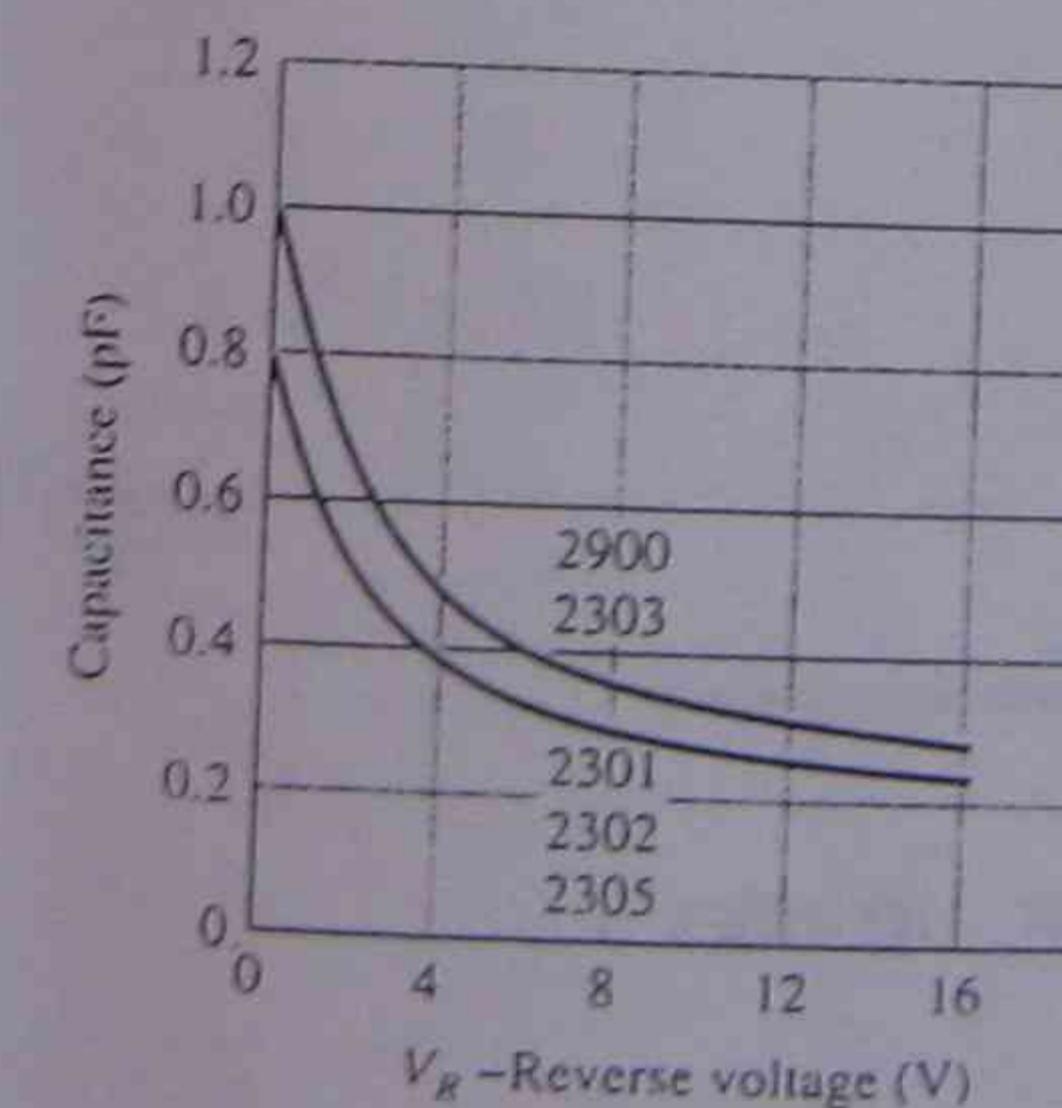


5082-2300 Series Typical Capacitance vs. Reverse Voltage at $T_A = 25^\circ\text{C}$.

(c)

Figure 20.6: Characteristic curves for Hewlett-Packard 5082-2300 series of general-purpose Schottky barrier diodes. (Courtesy: Hewlett-Packard Corporation.)

A.C. Motor Control.



Topic -

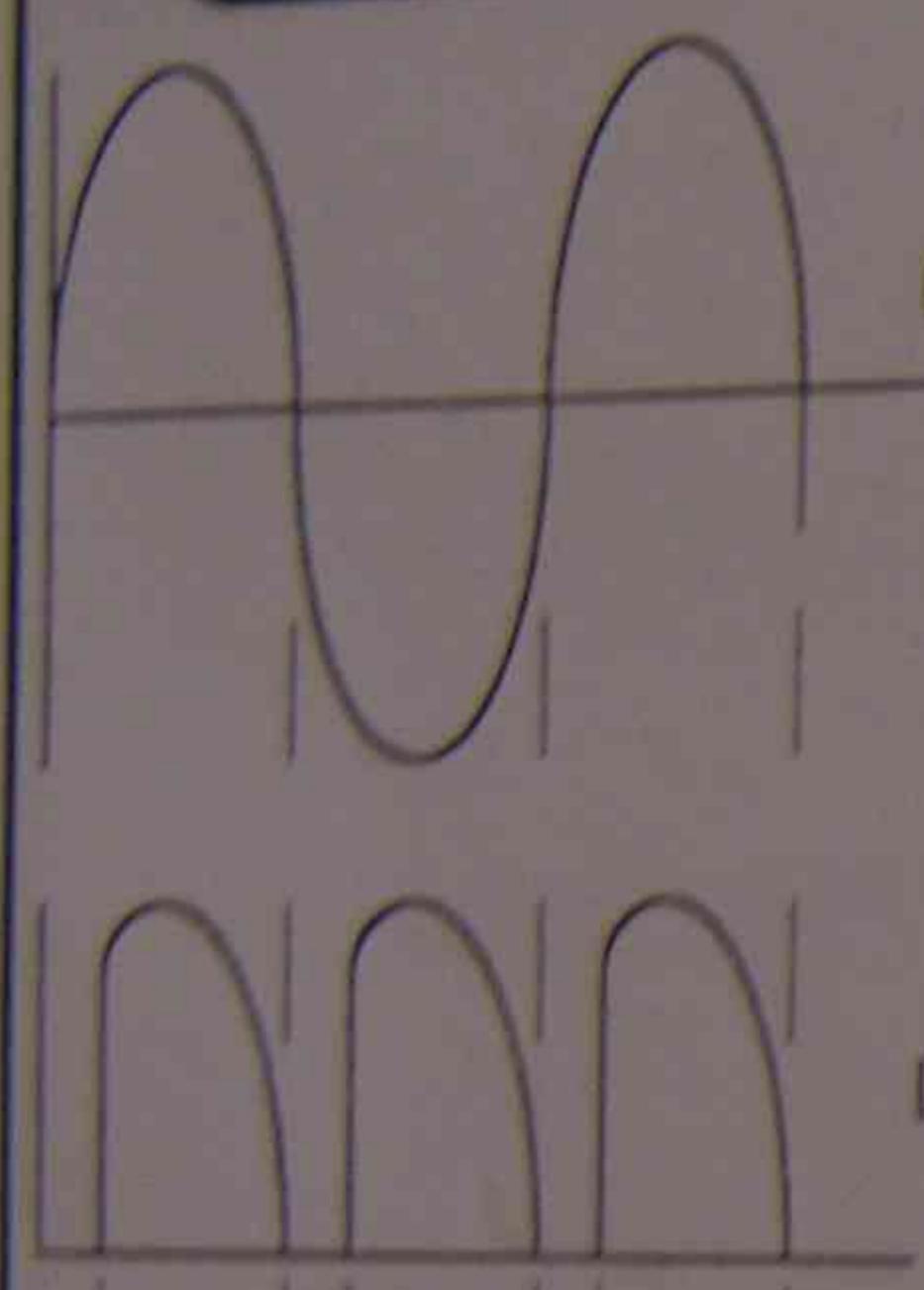

SINGLE PHASE, HALF CONTROLLED,
BRIDGE RECTIFIER CIRCUIT

Line Voltage
(Vac)

Load Voltage

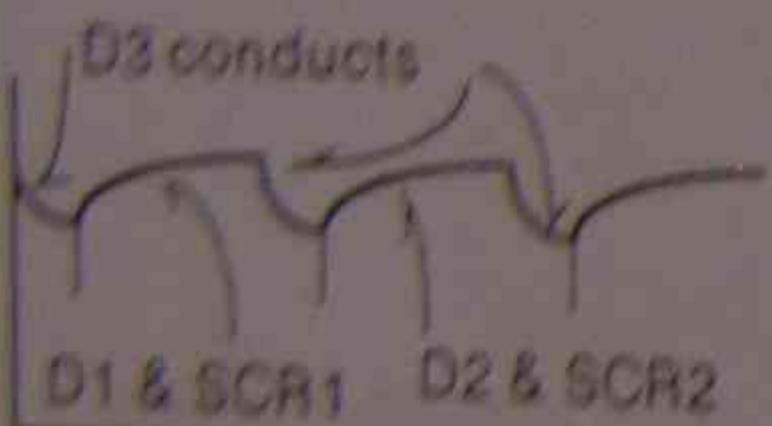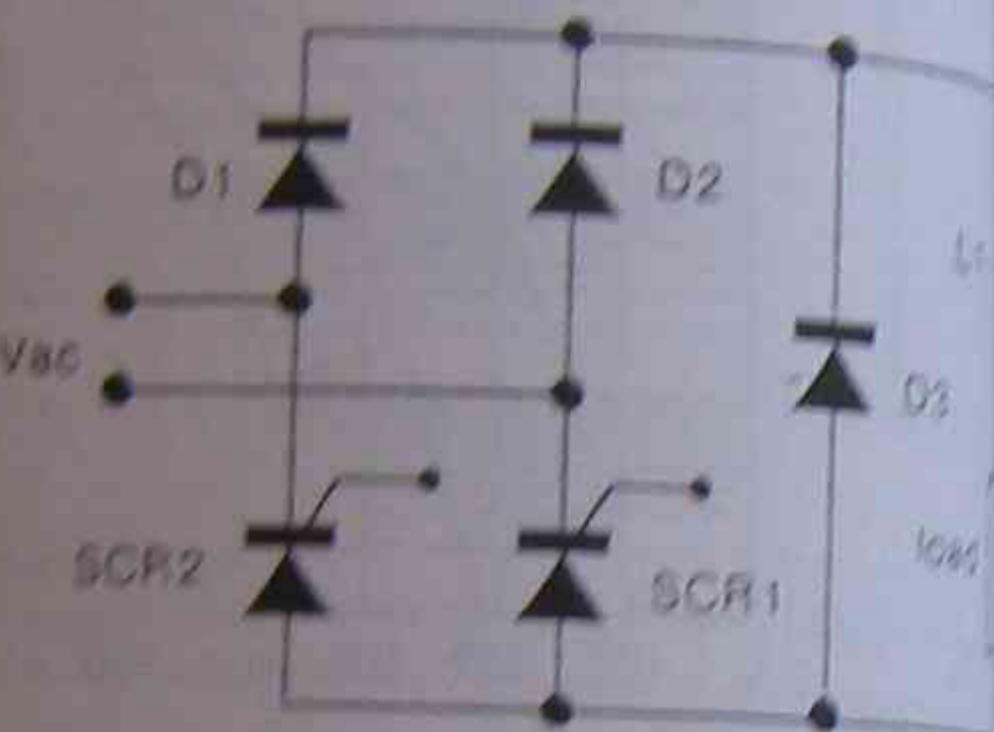

Load Current

Trigger pulses

Fig.10 Single-phase, half controlled bridge with flywheel diode (D3)

SUITABLE FOR SEVERAL KW SUPPLIES,
USE IN A 3 PHASE CONFIGURATION FOR HIGHER
POWERS.
EXHIBITS A HIGH POWER FACTOR.
FOR INDUCTIVE LOADS D3, FREE WHEELING DIODE,
MUST BE USED.
ALSO FOR INDUCTIVE LOADS TO MITIGATE di/dt THE
SATURABLE REACTOR, L1, IS INCORPORATED.

Sydney Institute of Technology

School of Electrotechnology

Learners Theory

Work Book

Module

NE76

A.C. Motor Control

Area

Topic


Session No.

3-4

For further information on this module, or this subject
contact Jim Hafford, (02) 217 3620, Bld. K, Ultimo, S.I.T.

A.C. Motor Control.


Topic -

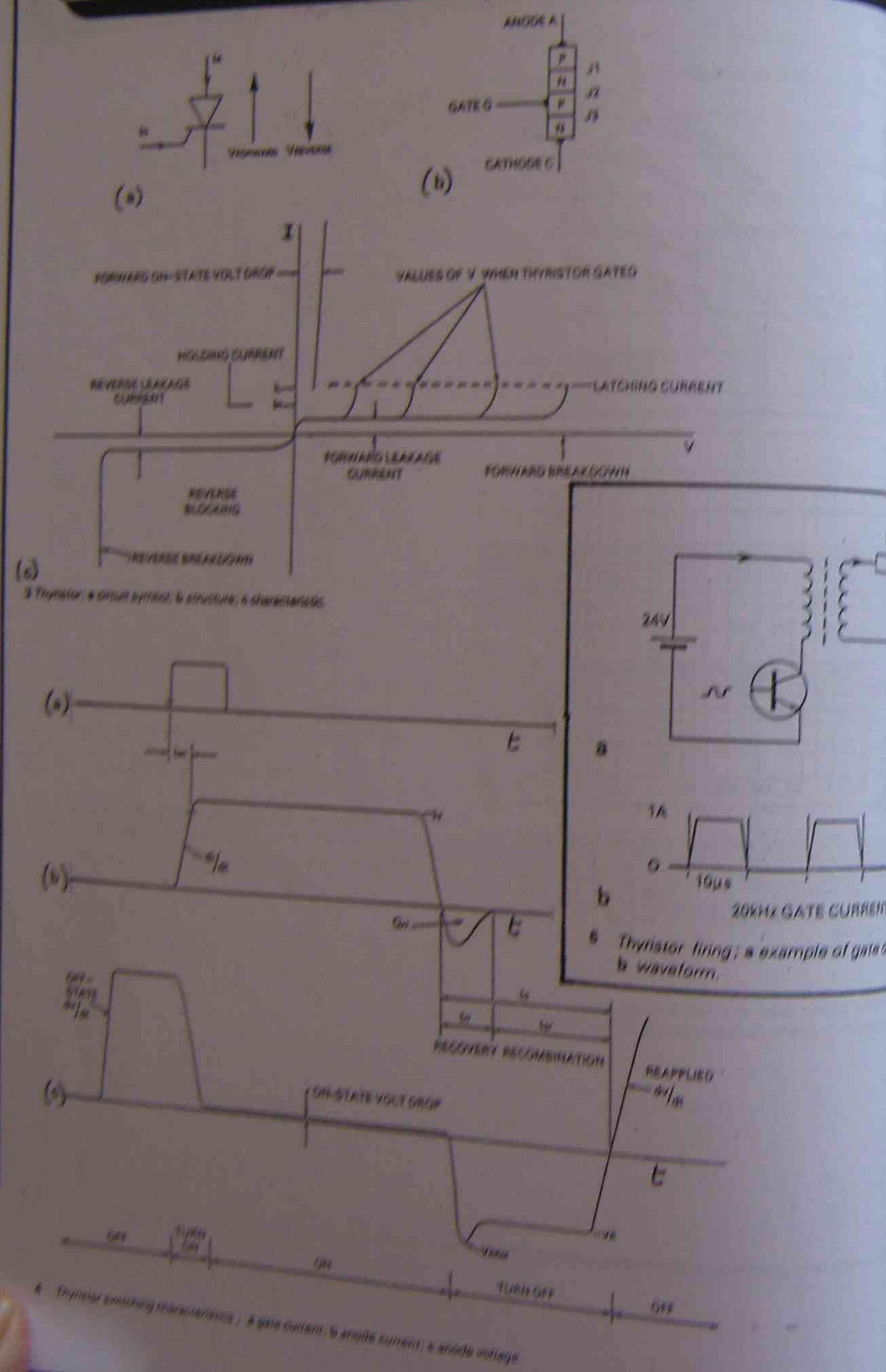

A.C. Motor Control.

Topic -

FIG 3 (b) & (c),
VOLTAGE AND CURRENT WAVEFORMS FOR AN INDUCTIVE
LOAD WITH SMALL CONDUCTION ANGLE.

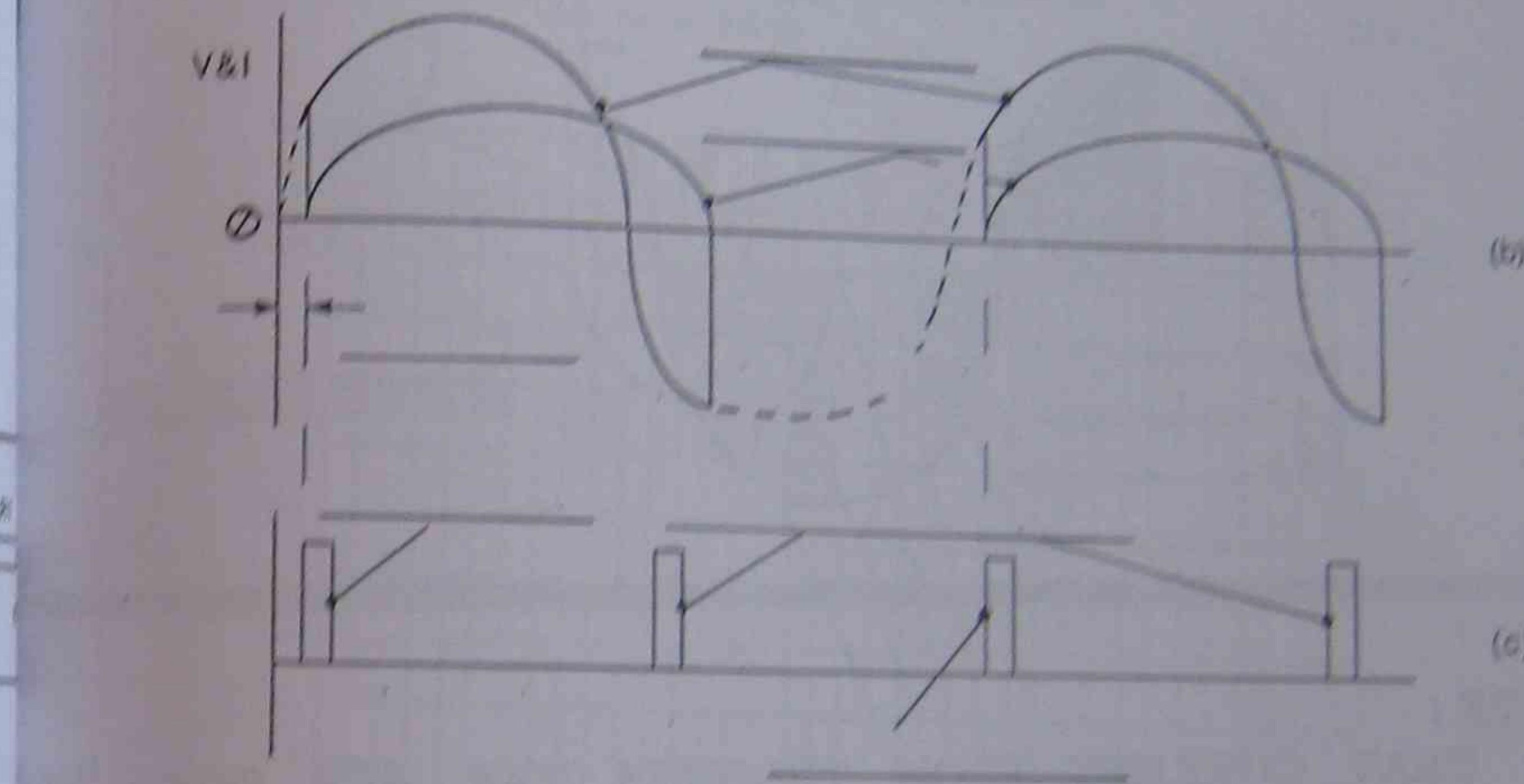


THE SITUATION SHOWN IN (a) LEADS TO PROBLEMS
WHEN THE FIRING ANGLE IS SMALL.

AFTER INITIAL FIRING OF SCR1 THE CONDUCTION OF
SCR2 IS PREVENTED BECAUSE OF SCR1 STILL
CONDUCTING AND REVERSE BIASING IT.

THIS SITUATION IS THE CASE WITH A SIMPLE
SINGLE PULSE FIRING SYSTEM.

WITH THE USE OF AN EXTENDED PULSE OR A PULSE
TRAIN OF SUITABLE DURATION, SCR WILL FIRE AS
SOON AS CONDITIONS ALLOW.

FIG 3(a),
VOLTAGE AND CURRENT WAVEFORMS FOR AN INDUCED
LOAD.

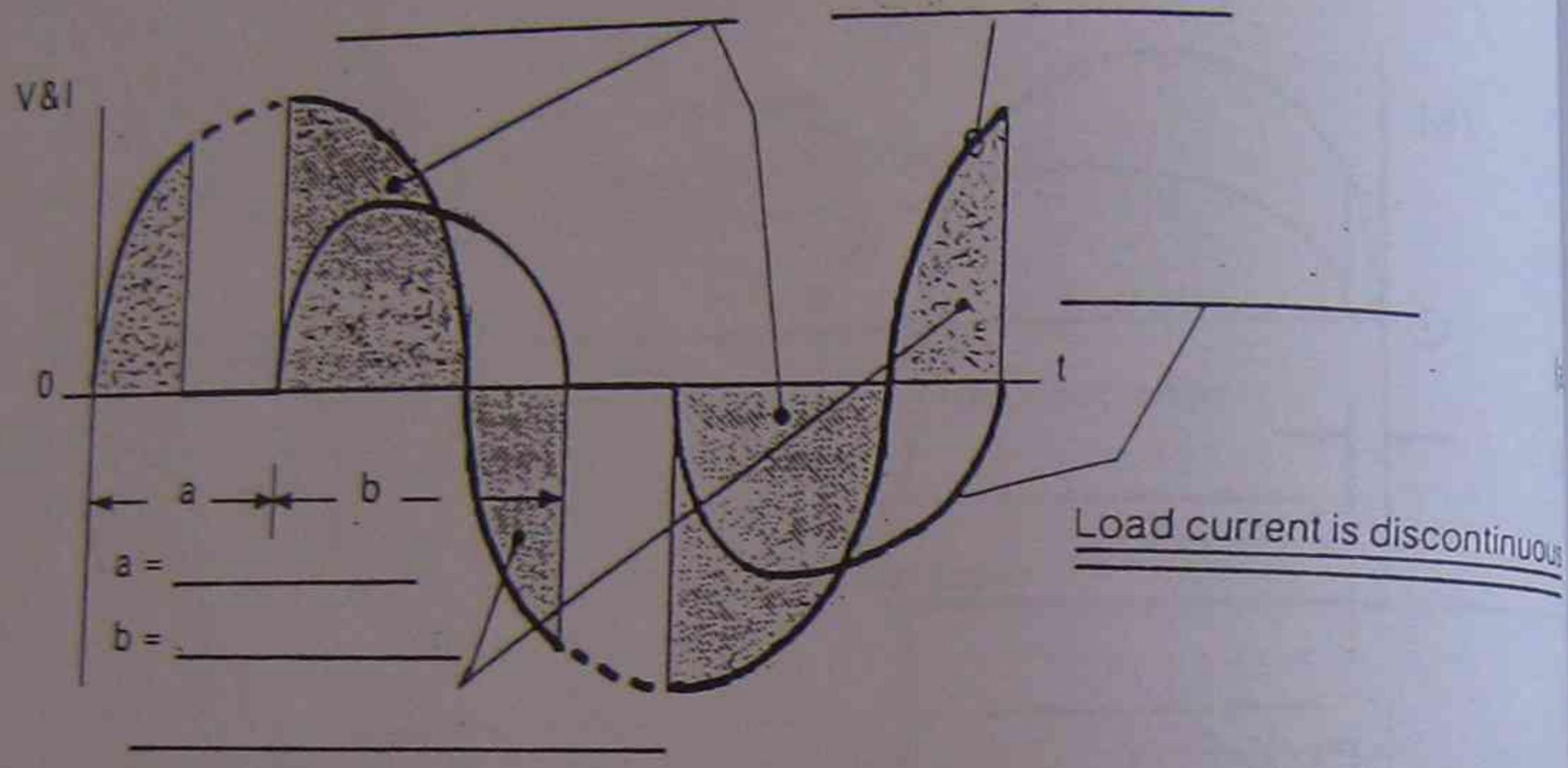**NOTE:**

- THAT CURRENT FLOW THROUGH THE SCR DOES NOT STOP UNTIL THE END OF PERIOD b, THEREFORE NATURAL COMMUTATION IS BEING USED SO IT WOULD NOT TURN OFF UNTIL THIS POINT.
- THERE IS TWO WAY FLOW OF ENERGY, BOTH FROM THE SUPPLY AND BEING RETURNED TO THE SUPPLY.

LOAD CURVES OF RMS SUPPLY TO RMS LOAD VOLTAGE FOR LOAD POWER FACTORS OF 1.0 (PURE RESISTIVE) TO 0 (PURE INDUCTIVE).

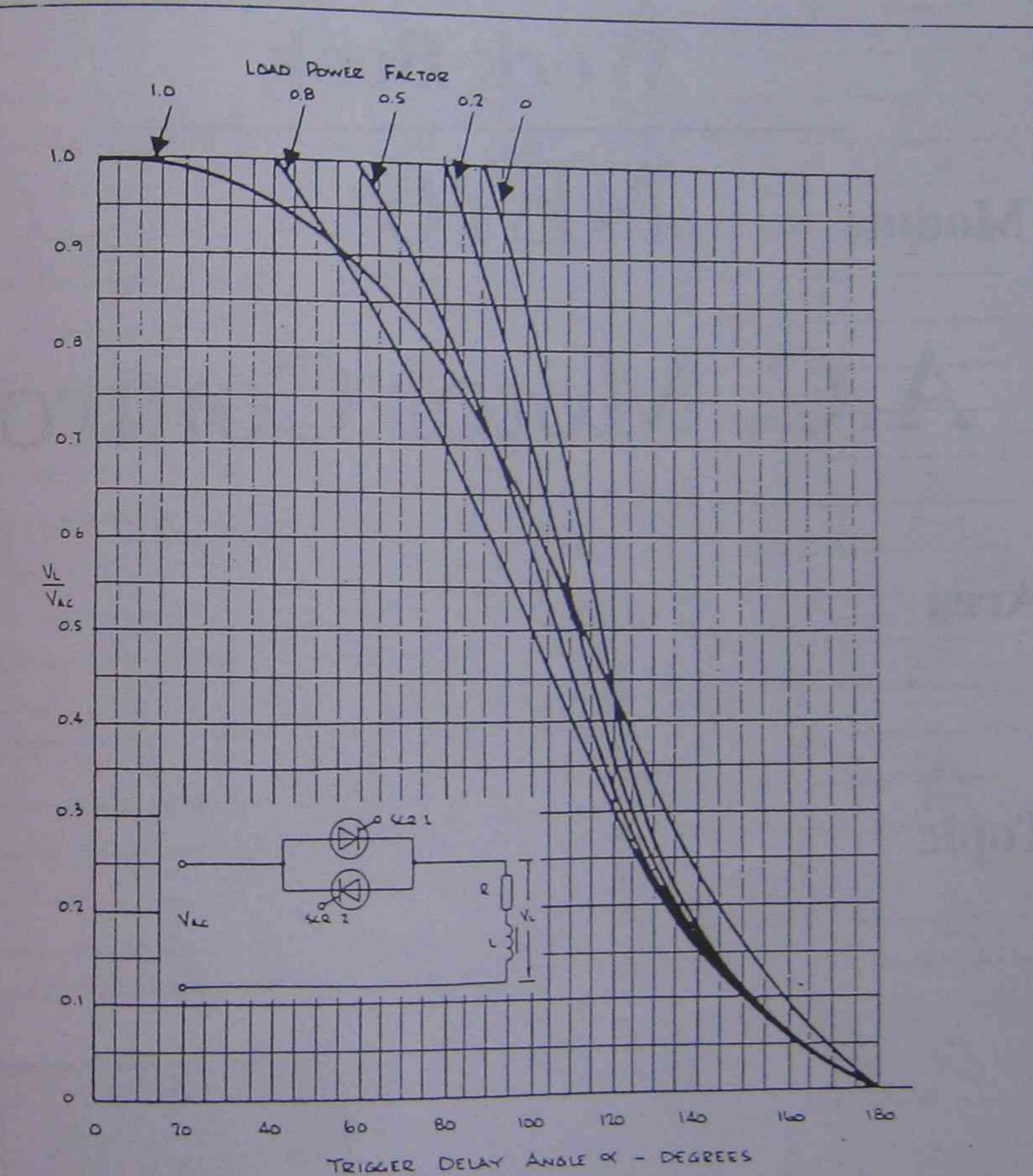


Fig. 2 Curves showing the ratio of load to supply voltage for various load power factors and trigger angles

Sydney Institute of Technology

School of Electrotechnology

Learners Theory

A.C. Work Book

Module

NET6

A.C. Motor Control


Area

Topic

Session No.

3

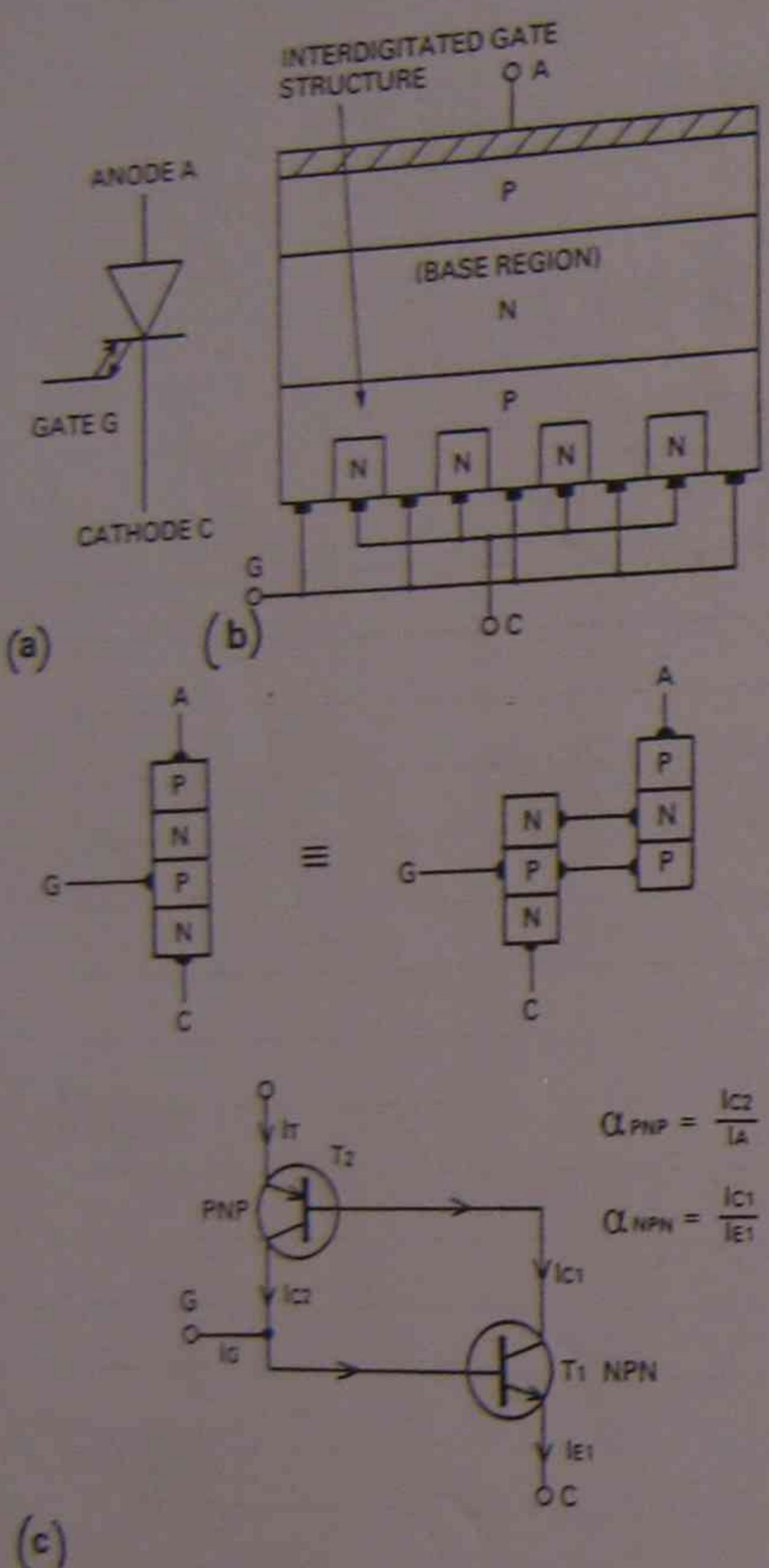For further information on this module, or this subject
contact Jim Hafford (02) 217 ~



8 GTO : a circuit symbol; b structure; c two-transistor model of thyristor.

Topic


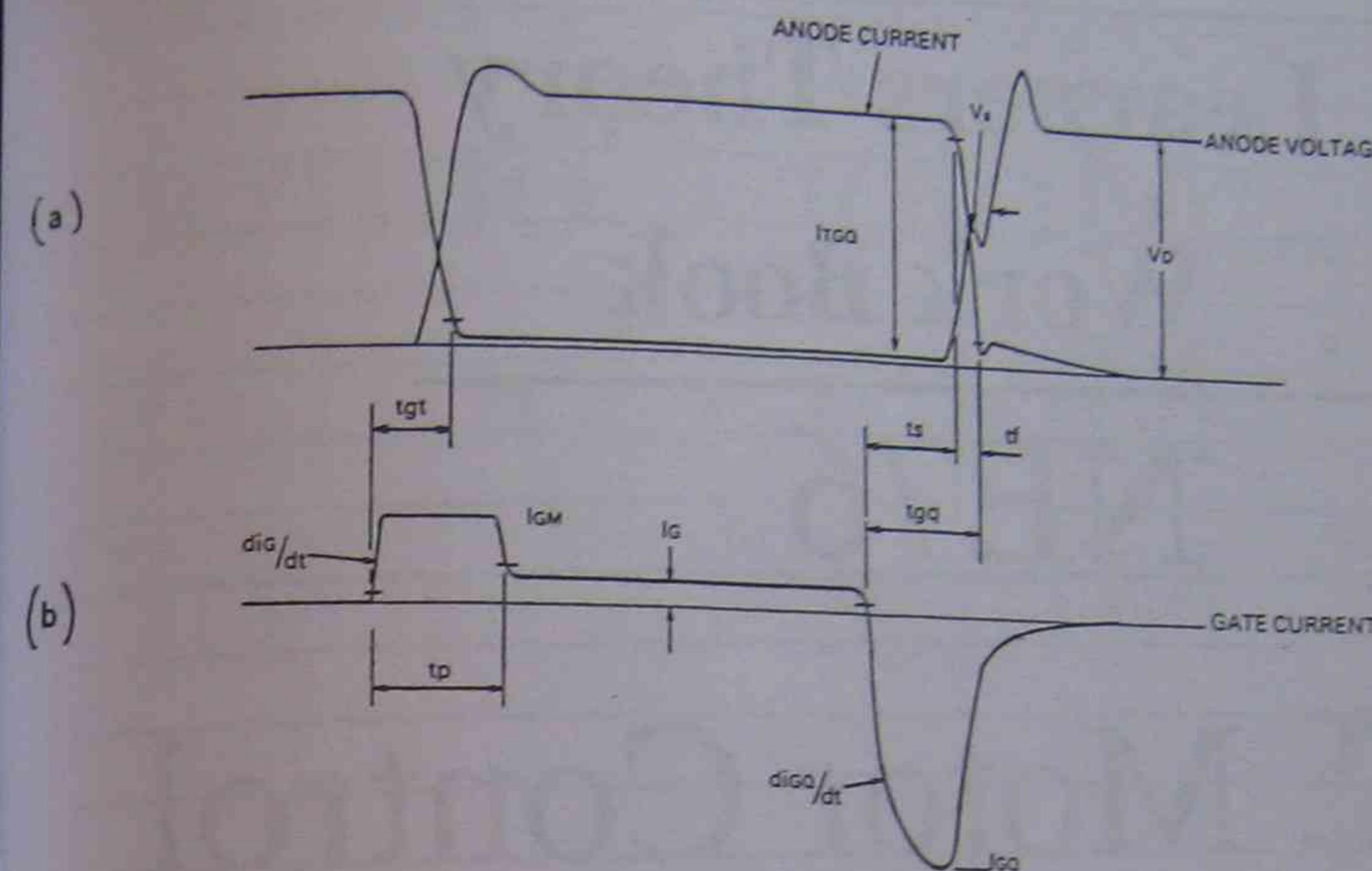


TABLE 1 Recommended Gate Drive for IR 160 PF

I_{GM}	\geq	10A	RESISTIVE SWITCHING PERFORMANCE	
I_G	\geq	2A	$V_D = 600V$	$I_{TGO} = 600A \text{ max}$
I_{GO}	\geq	120A	Snubber = $2\mu F$	
t_w	\geq	$10\mu s$	$t_{g1} = 5\mu s$ (turn-on time)	
dI_G/dt	=	$5A/\mu s$	$t_{g2} = 8\mu s$ (turn-off time)	
			$t_s = 0.8\mu s$	

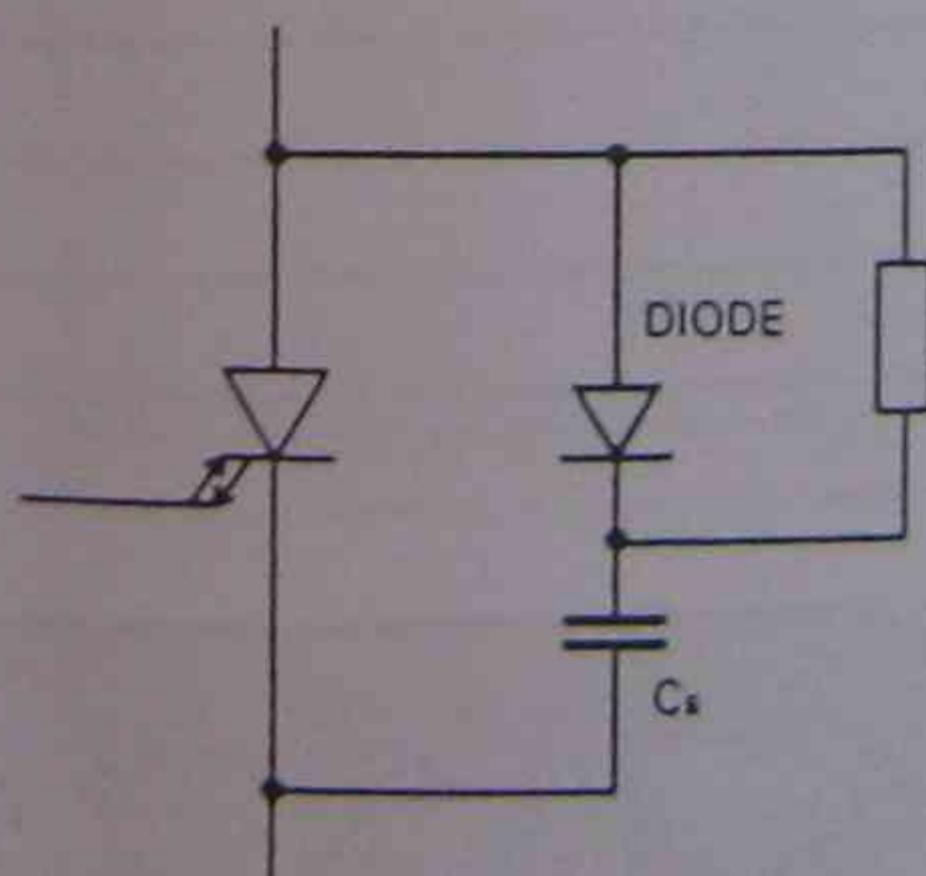9 GTO switching performance; a anode current and voltage; b gate current



10 Typical snubber circuit required for GI

Sydney Institute of Technology

School of Electrotechnology

Learners Theory

Work Book

Module

NET6

A.C. Motor Control

Area

Topic


Session No.

3

For further information on this module, or this subject
contact Jim Hafford, (02) 217 3620, Bld K Ultimo, S.I.T.

A.C. Motor Control.


Topic -

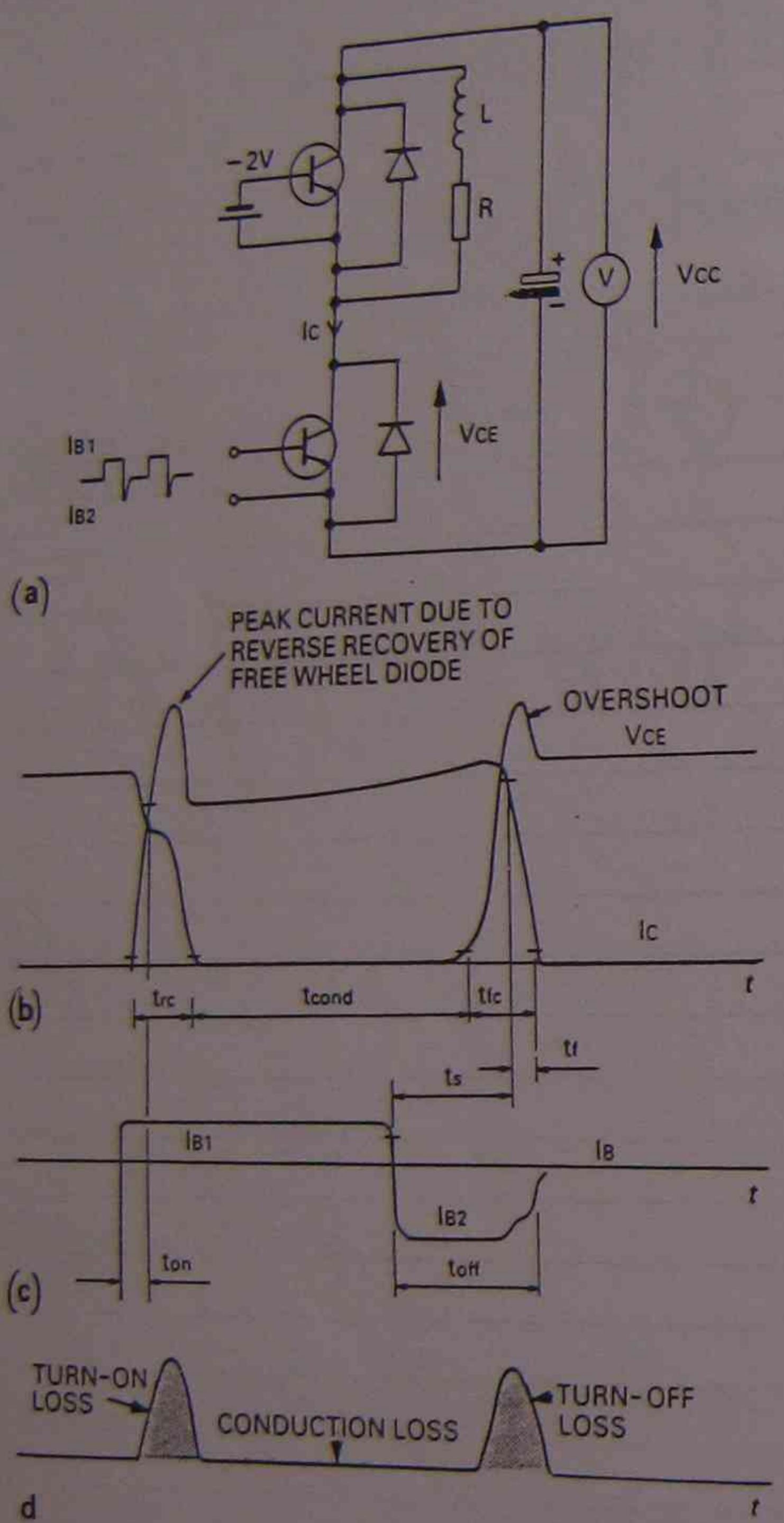


15 Bipolar transistor switching an inductive load: a test circuit; b collector current and voltage waveforms; c base drive; d power loss over one switching cycle.

A.C. Motor Control.


Topic -

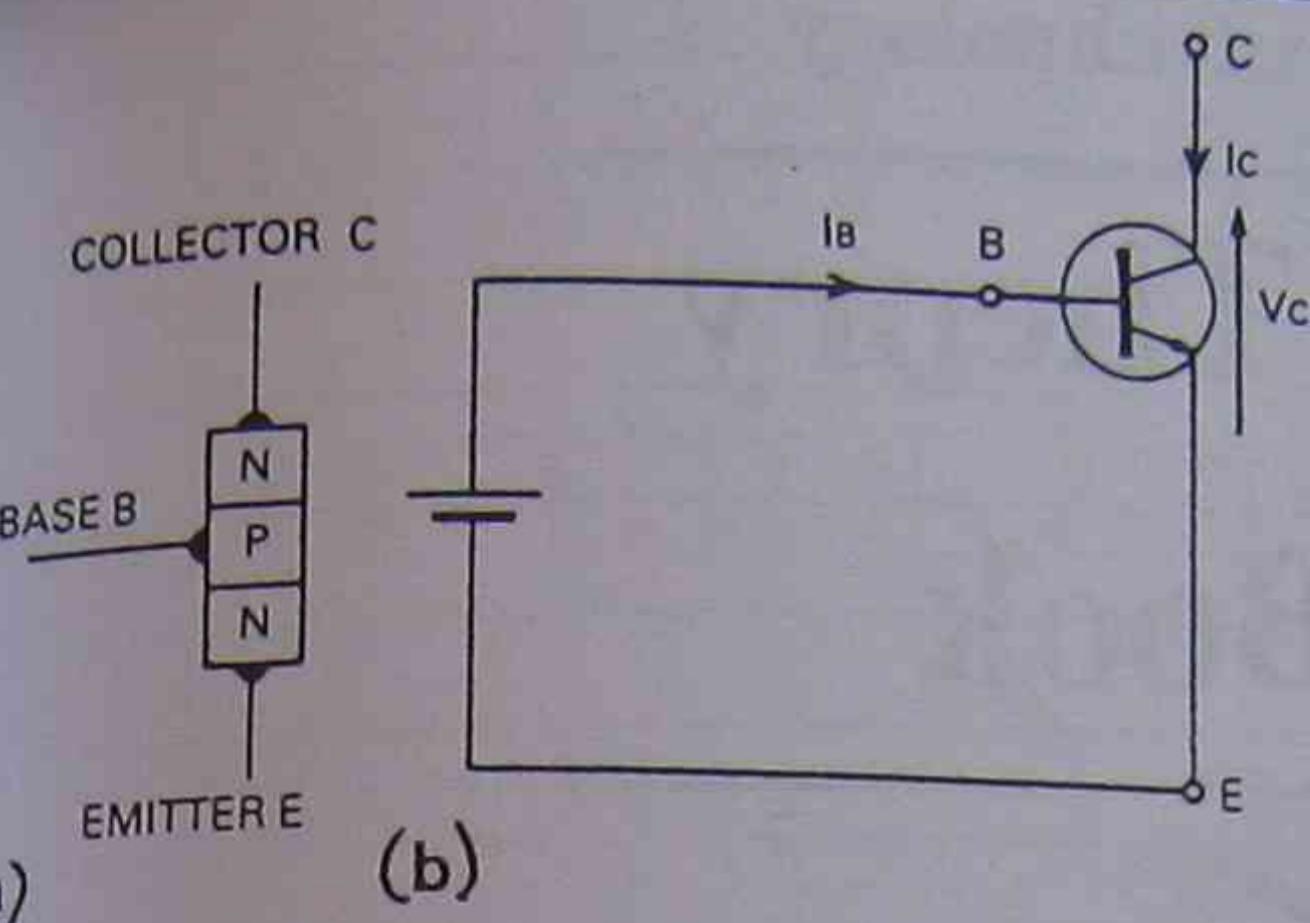

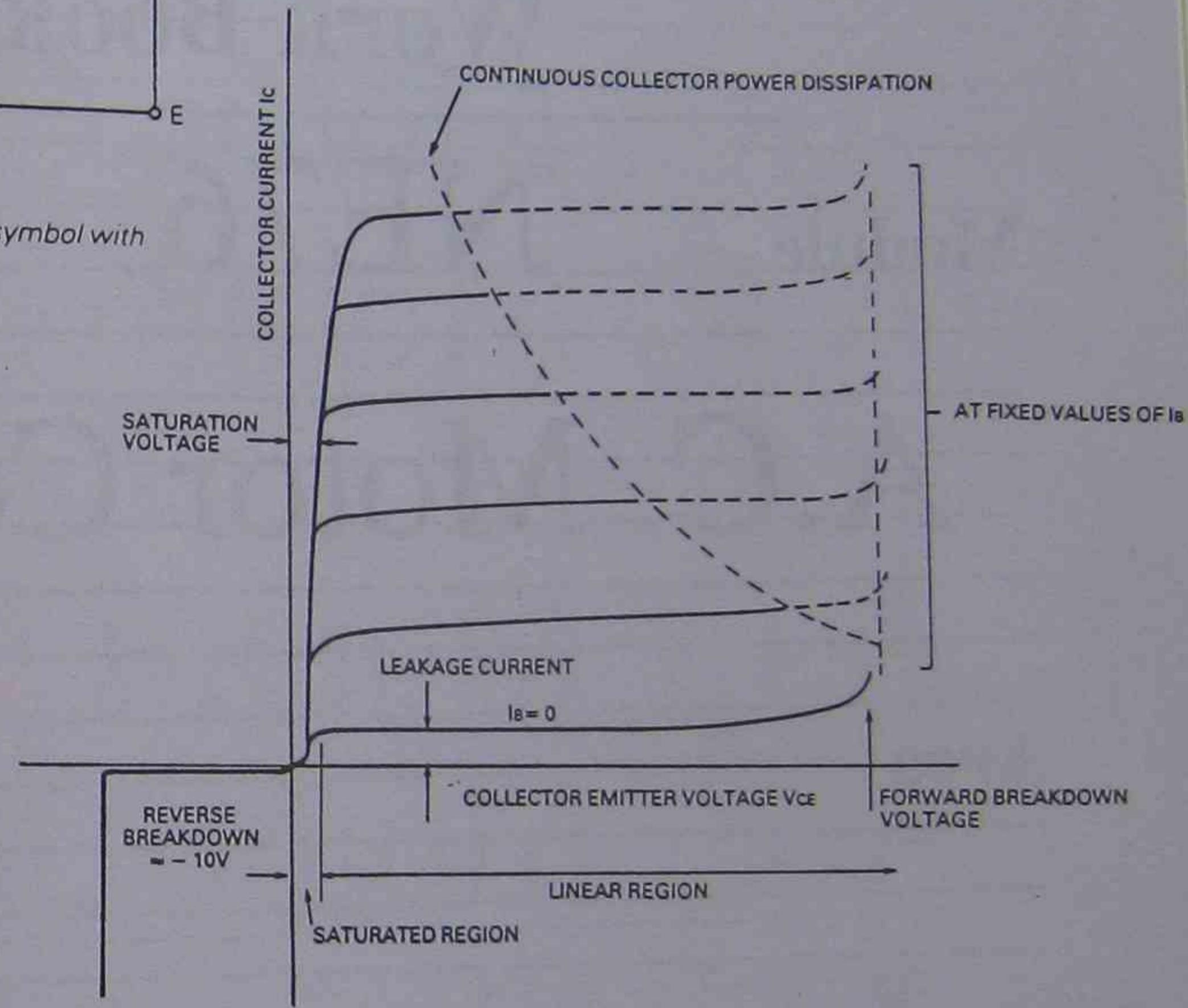11 NPN transistor; a structure; b circuit symbol with current directions.



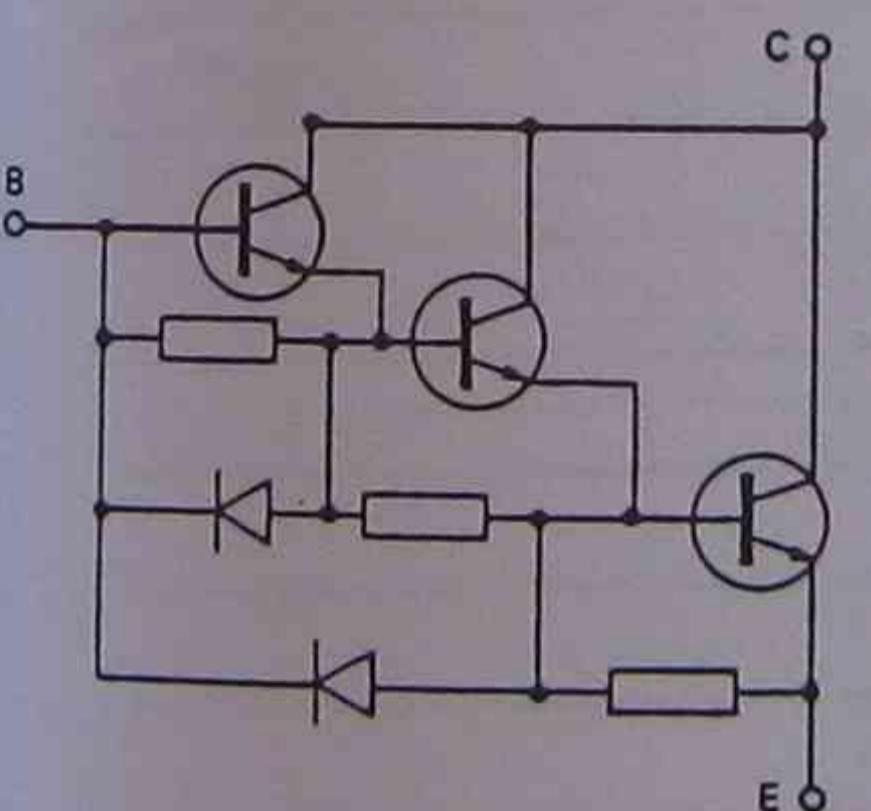12 Output characteristic (common emitter) for NPN transistor



13 Three-stage Darlington arrangement of power transistor.

TABLE 2 Calculation of Switching and Conduction Losses for a Bipolar Transistor

Energy dissipated during turn-on	$W_{on} = \frac{1}{2}t_{rc} \times V_{CC} \times I_C$
Energy dissipated during turn-off	$W_{off} = \frac{1}{2}t_{lc} \times V_{CC} \times I_C$
Energy dissipated during conduction period	$W_{cond} = V_{CESat} \times I_C \times t_{cond}$
Switching loss (watts)	$f(W_{on} + W_{off})$
Conduction loss (watts)	$f \times W_{cond}$
TOTAL AVERAGE POWER LOSS	Switching loss + Conduction loss

Sydney Institute of Technology

School of Electrotechnology

Learners Theory

Work Book

Module

NET6

A.C. Motor Control

Area

Topic

Session No.

4

For further information on this module, or this subject

Tim Hafford, (02) 217 3620, Bld K, Ultimo, S.I.T.

A.C. Motor Control.

Topic -

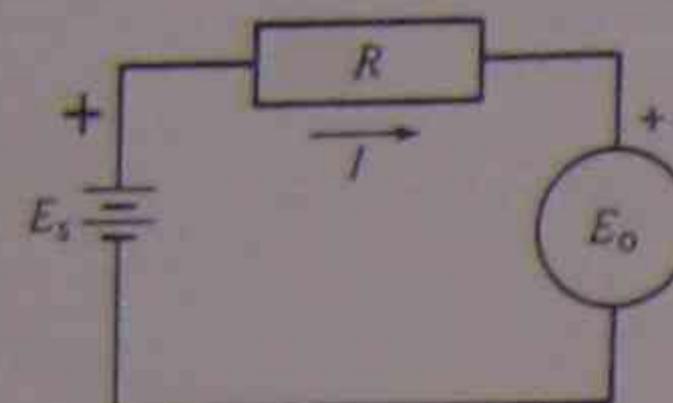


Figure 21-38
Inefficient power transfer.

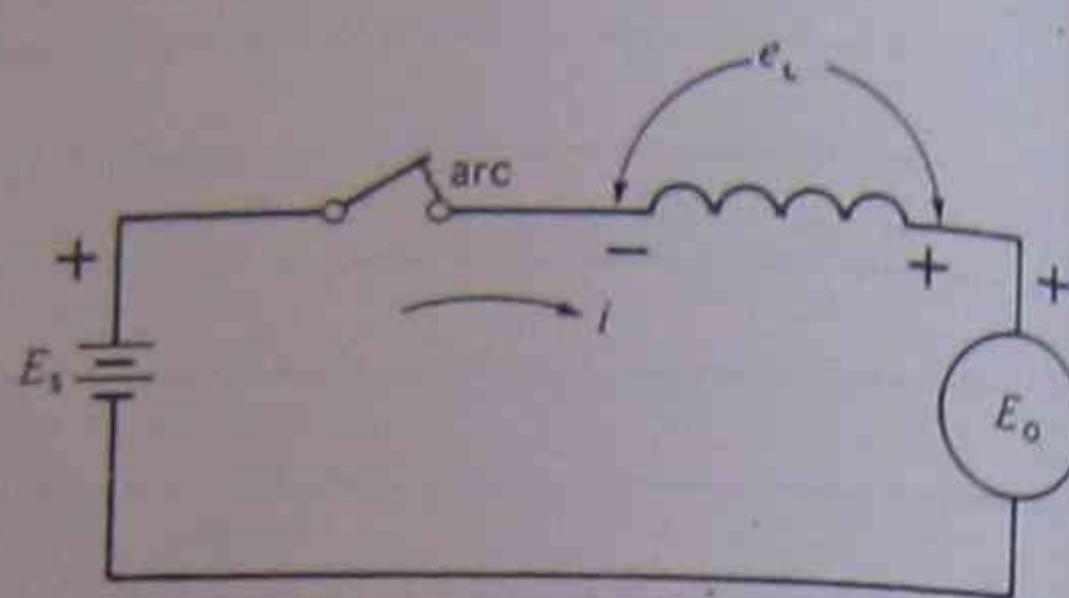


Figure 21-41
Energy is dissipated in the arc. Note the polarity of e_L .

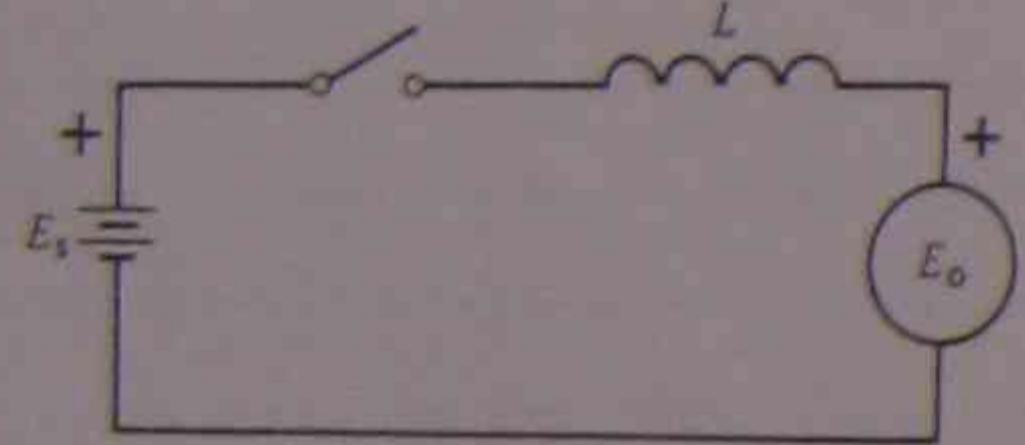


Figure 21-39
Energy transfer using an inductor.

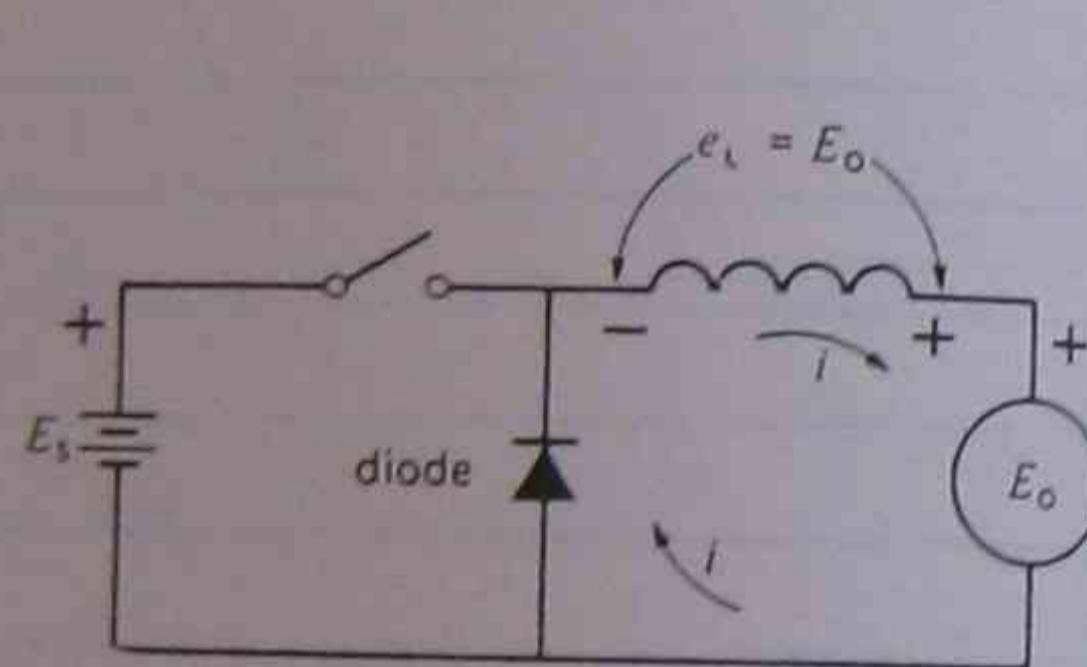


Figure 21-42
Energy transferred without loss.

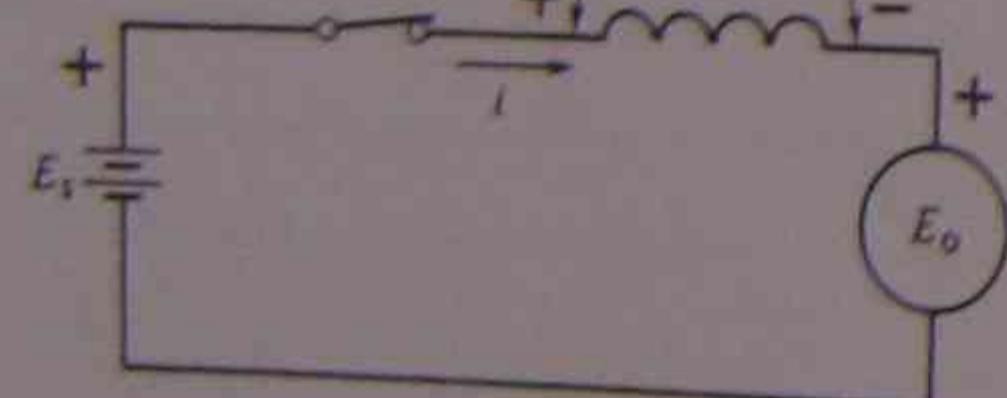


Figure 21-40
Energy is stored in the inductor.

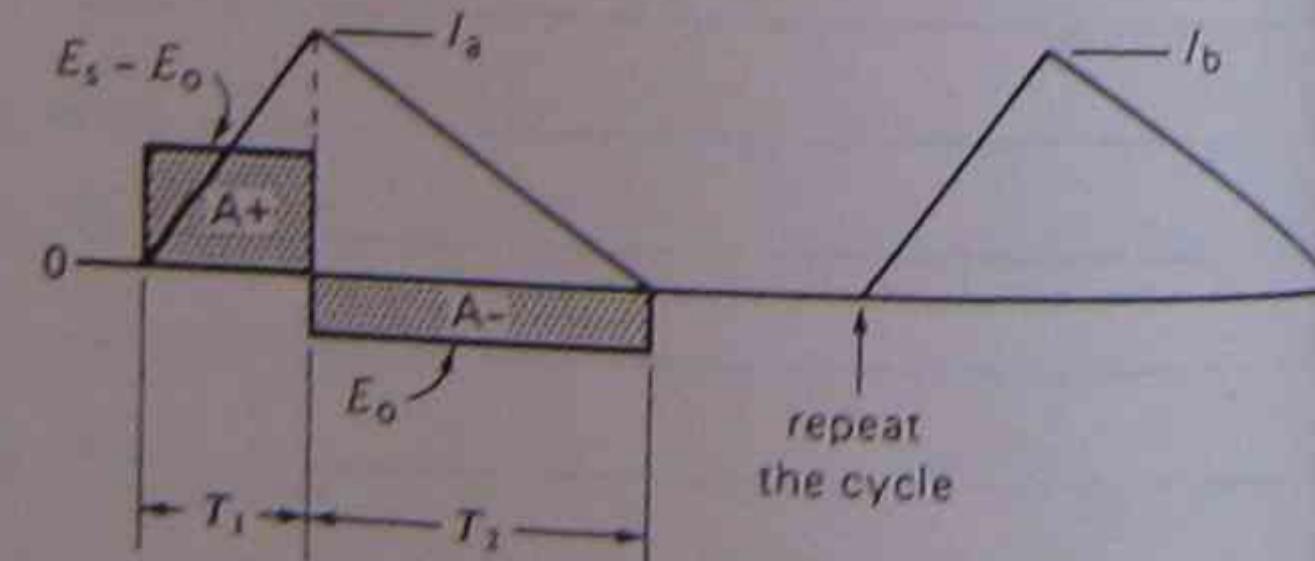


Figure 21-43
 E and I in the inductor of Fig. 21-42.

$$\text{at } T_1 \quad I_a = A + \frac{E_o}{L} = (E_s - E_o) \frac{T_1}{L}$$

Energy stored in L

$$W = \frac{1}{2} L I_a^2$$


$$(E_s - E_o) T_1 = E_o T_2 -$$

A.C. Motor Control.


Topic -

When the chopper is turned on, the energy is transferred from the source V_s to inductor L . If the chopper is then turned off, a magnitude of the energy stored in the inductor is forced to battery E .

Note. Without the chopping action, v_s must be greater than E for transferring power from V_s to E .

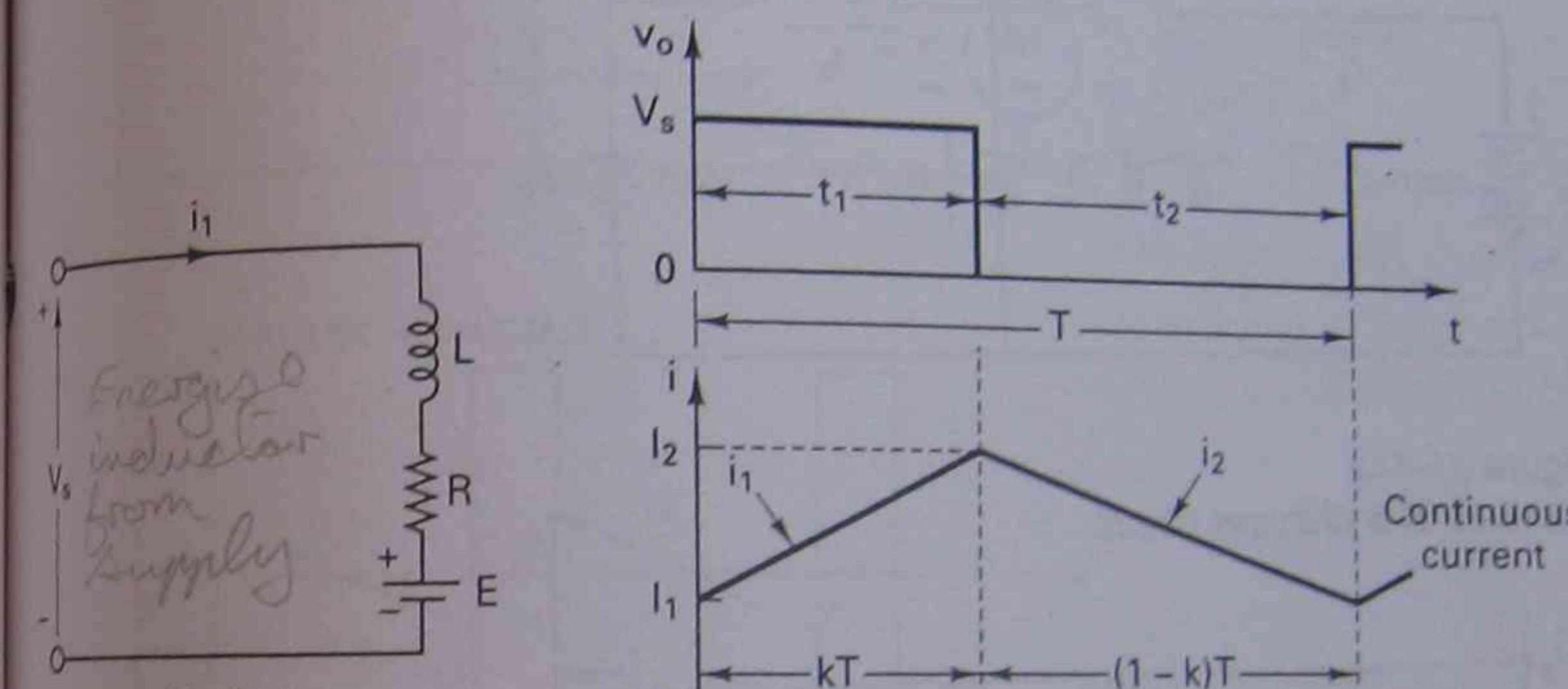

Mode 1

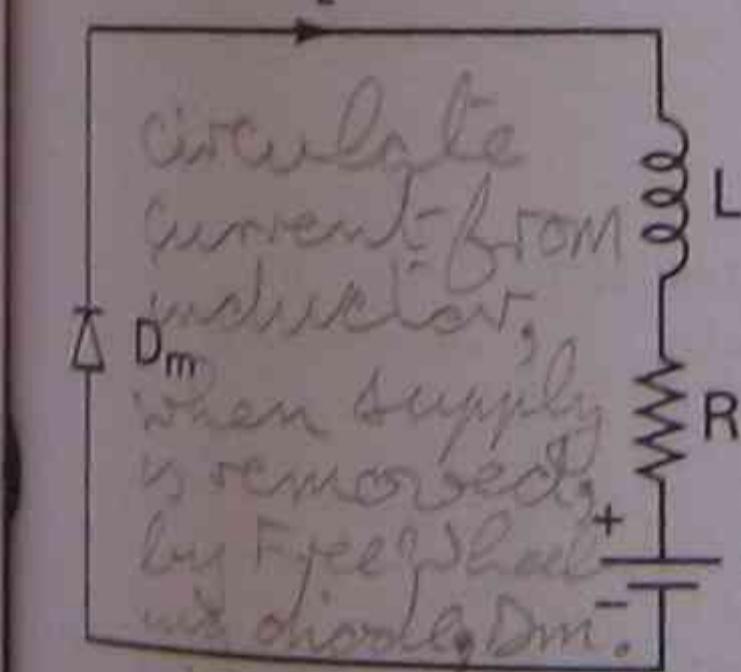

Mode 2

(a) Equivalent circuits

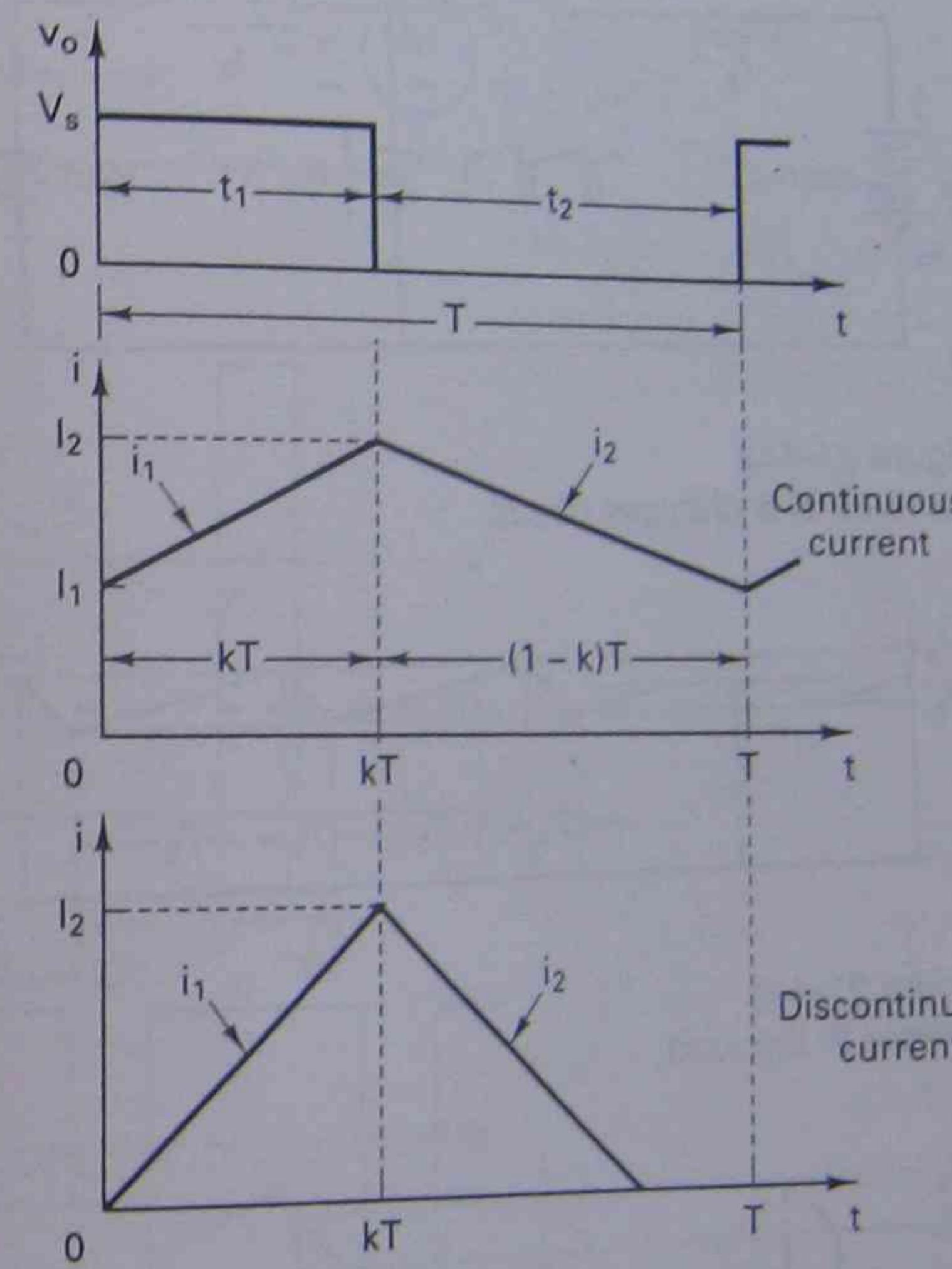


Figure 9-3 Equivalent circuits and waveforms for RL loads.

The power semiconductor devices require a minimum time to turn on and turn off. Therefore, the duty cycle k can only be controlled between a minimum value k_{\min} and a maximum value k_{\max} , thereby limiting the minimum and maximum value of output voltage. The switching frequency of the chopper is also limited. It can be noticed from Eq. (9-20) that the load ripple current depends inversely on the chopping frequency f . The frequency should be as high as possible to reduce the load ripple current and to minimize the size of any additional series inductor in the load circuit.

$$\text{Eq (9-20)} \quad \Delta I_{\text{RIPPLE}} = \frac{\sqrt{s}}{4fL}$$

A.C. Motor Control.

Topic -

3

A.
C.
T
o
p
i
c
-

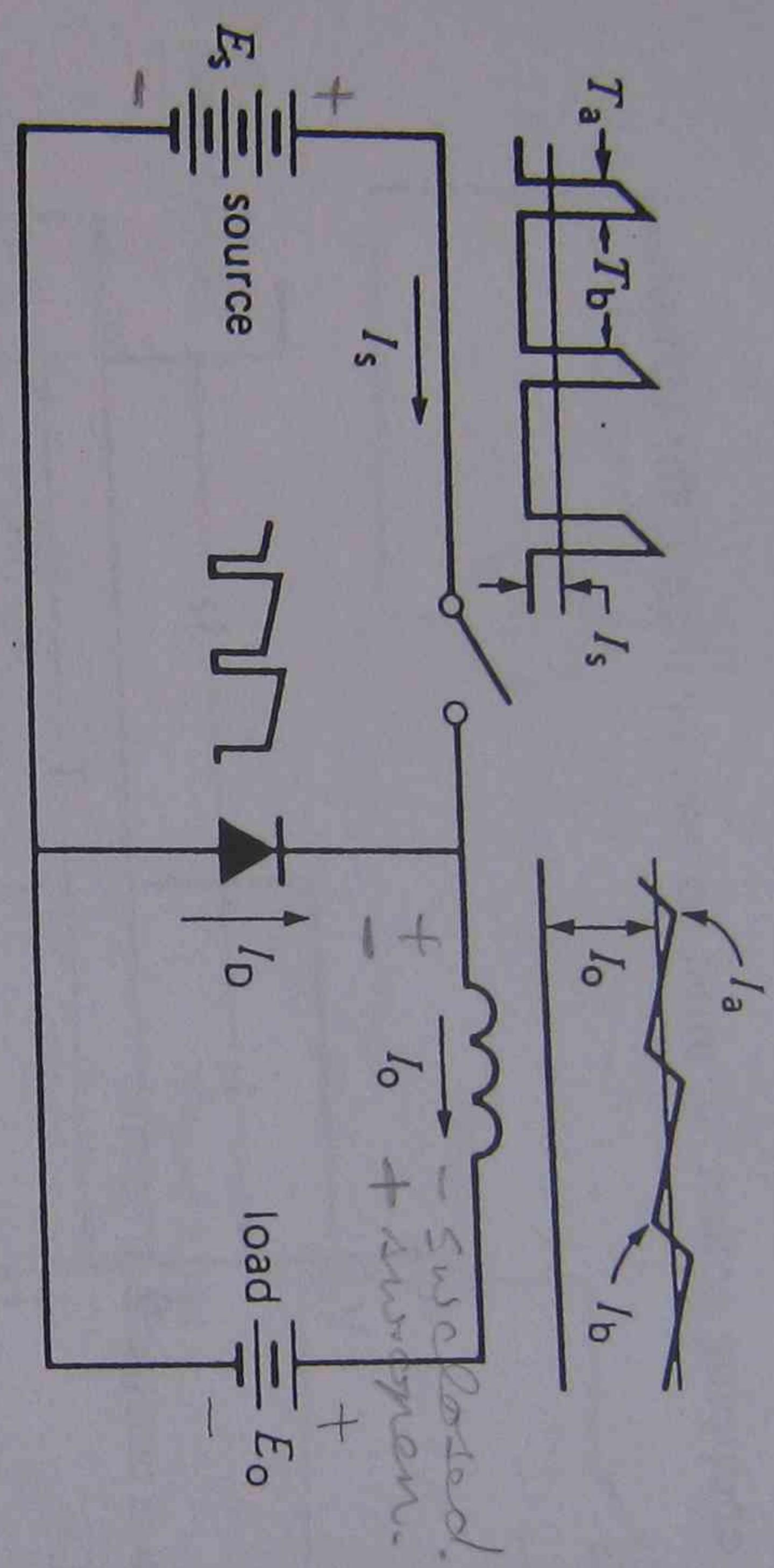


Figure 21-44a
Currents in a chopper circuit.

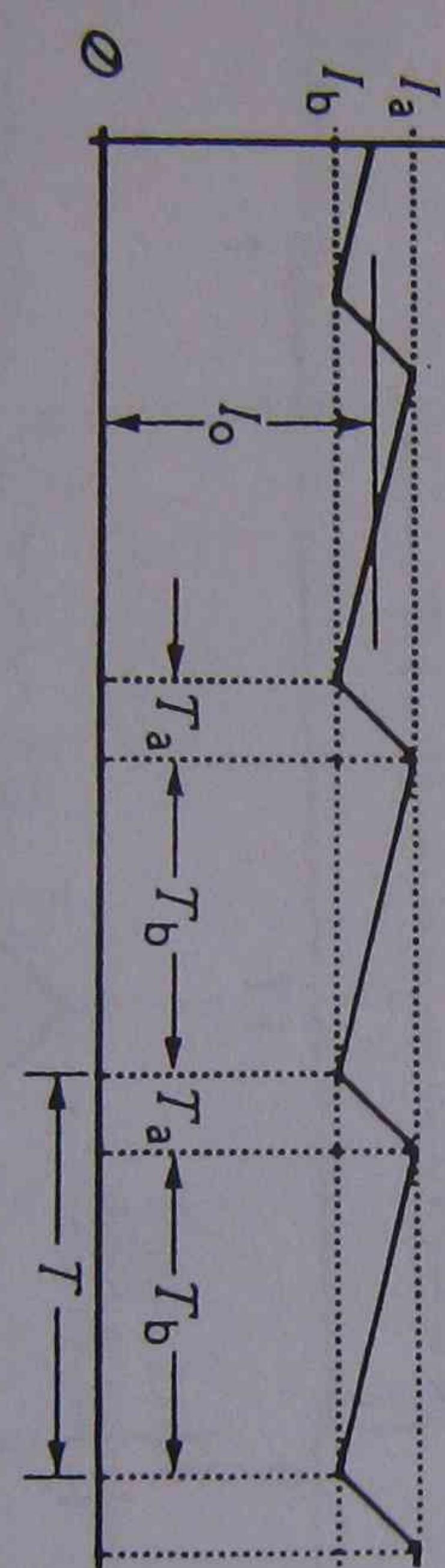


Figure 21-44b
Current in the load.


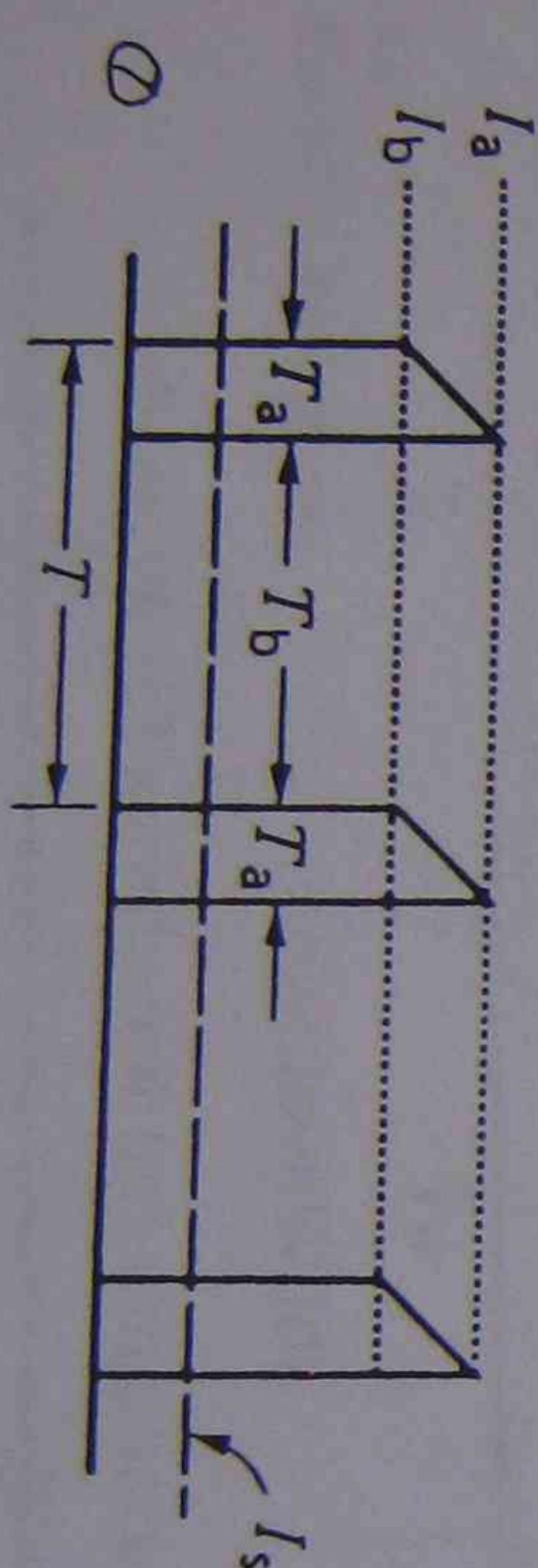


Figure 21-44c
Current drawn from the source.


A.C. Motor Control.

Topic -


4

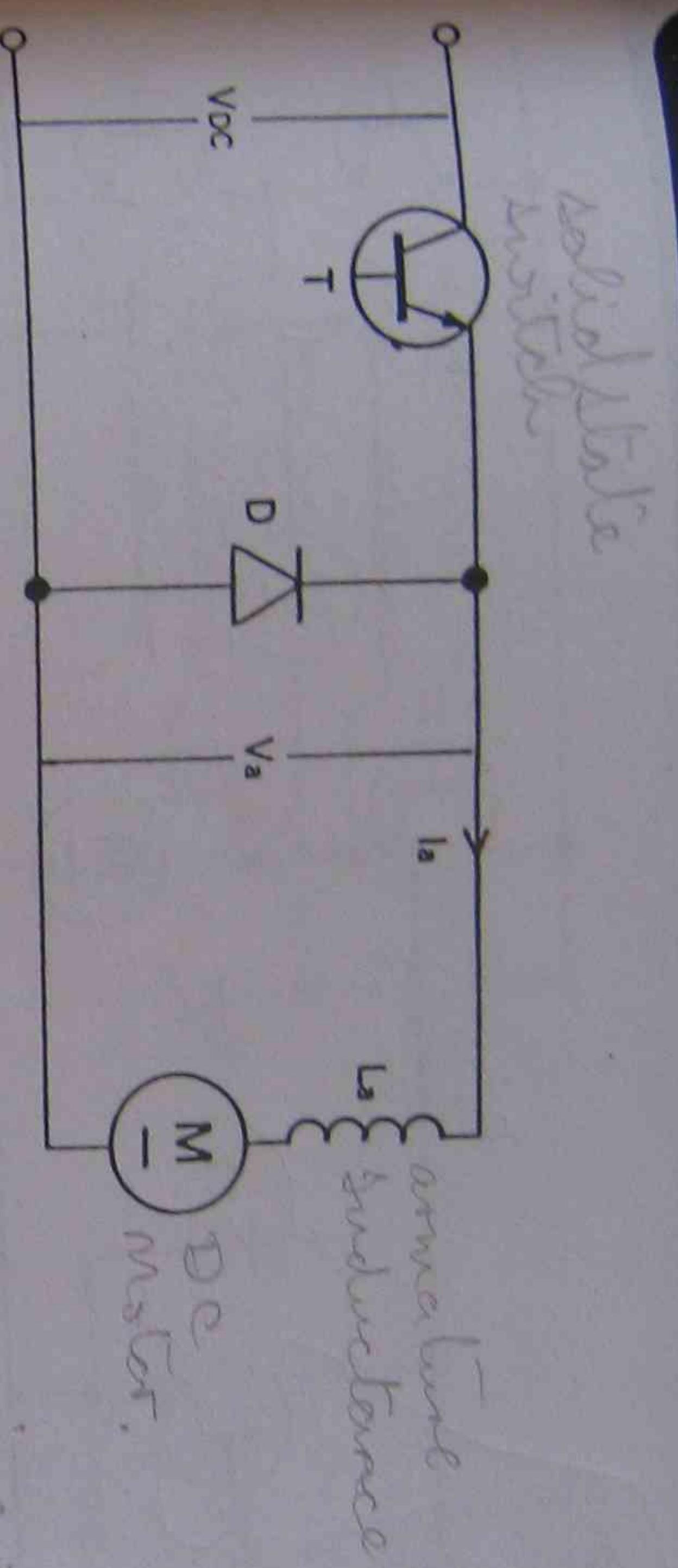

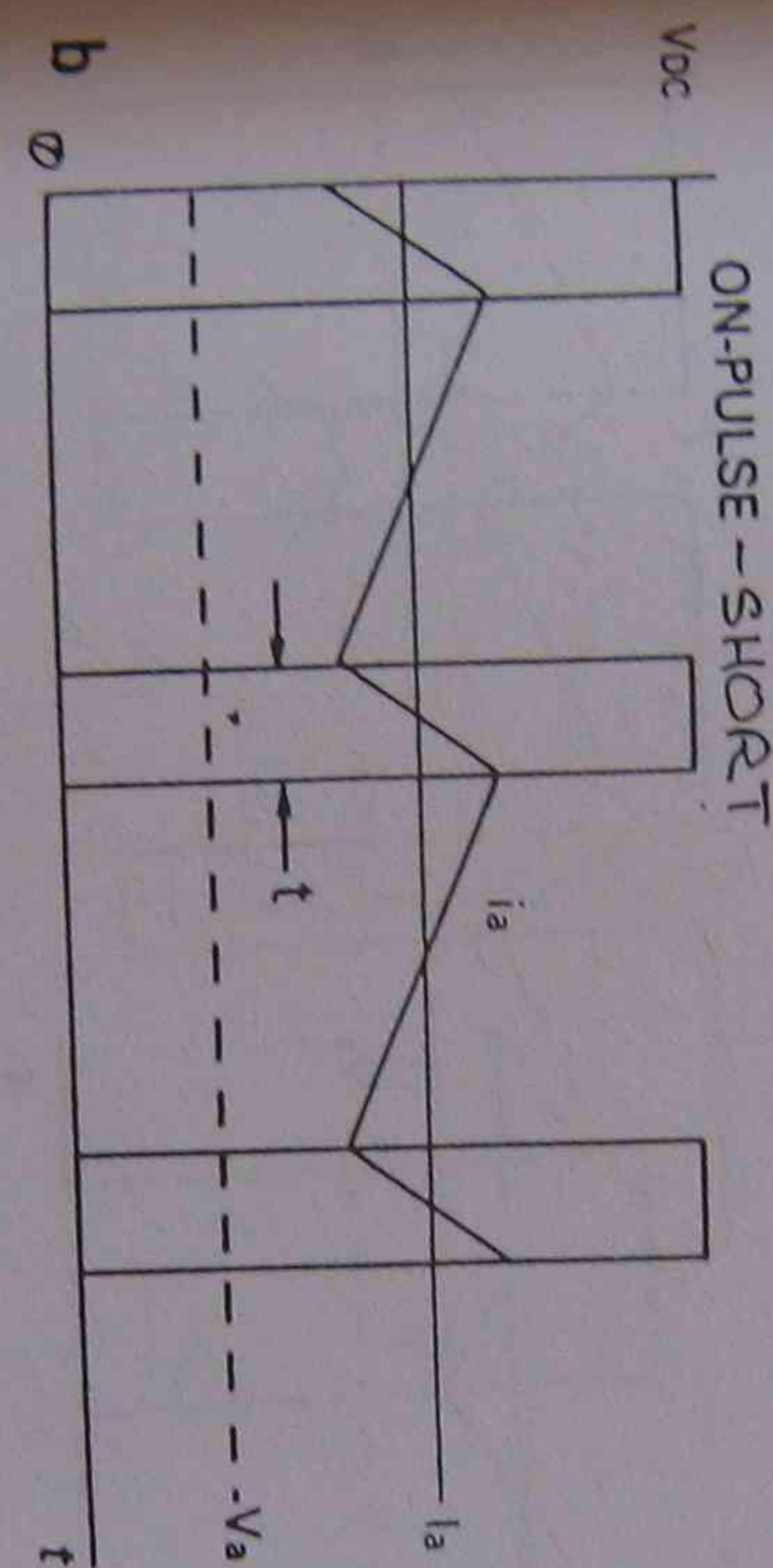*Varying applied
voltage by varying
the pulse width*



ON-PULSE - LONG

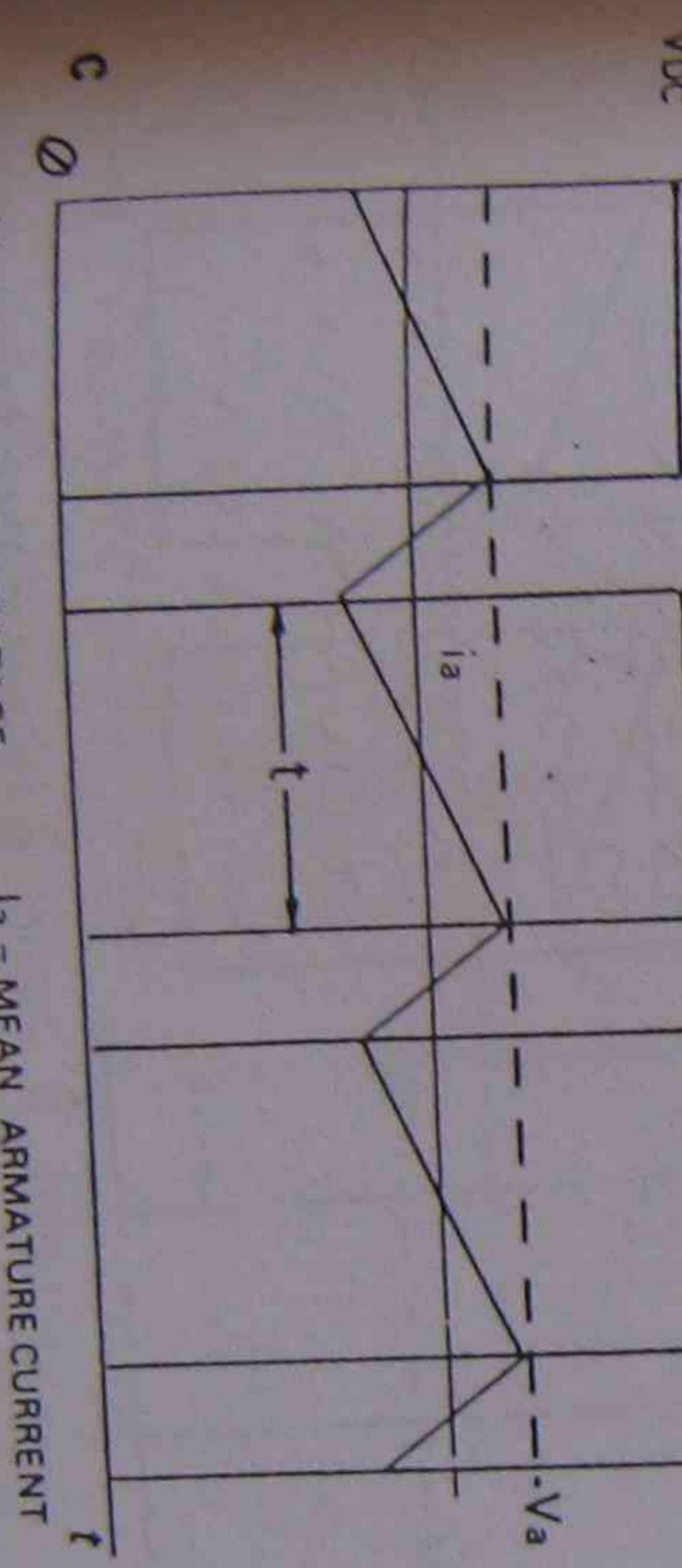

V_{DC}

V_a

i_a

t

C

O

V_{DC} = DC SUPPLY VOLTAGE
 V_a = DC ARMATURE VOLTAGE
 L_a = ARMATURE INDUCTANCE

i_a = MEAN ARMATURE CURRENT
 i_a = INSTANTANEOUS ARMATURE CURRENT


- 2 Basic dc dc converter, or chopper: **a** circuit;
- b** low output voltage; **c** high output voltage.

A.C. Motor Control.


Topic -

5

A.C.
TOP

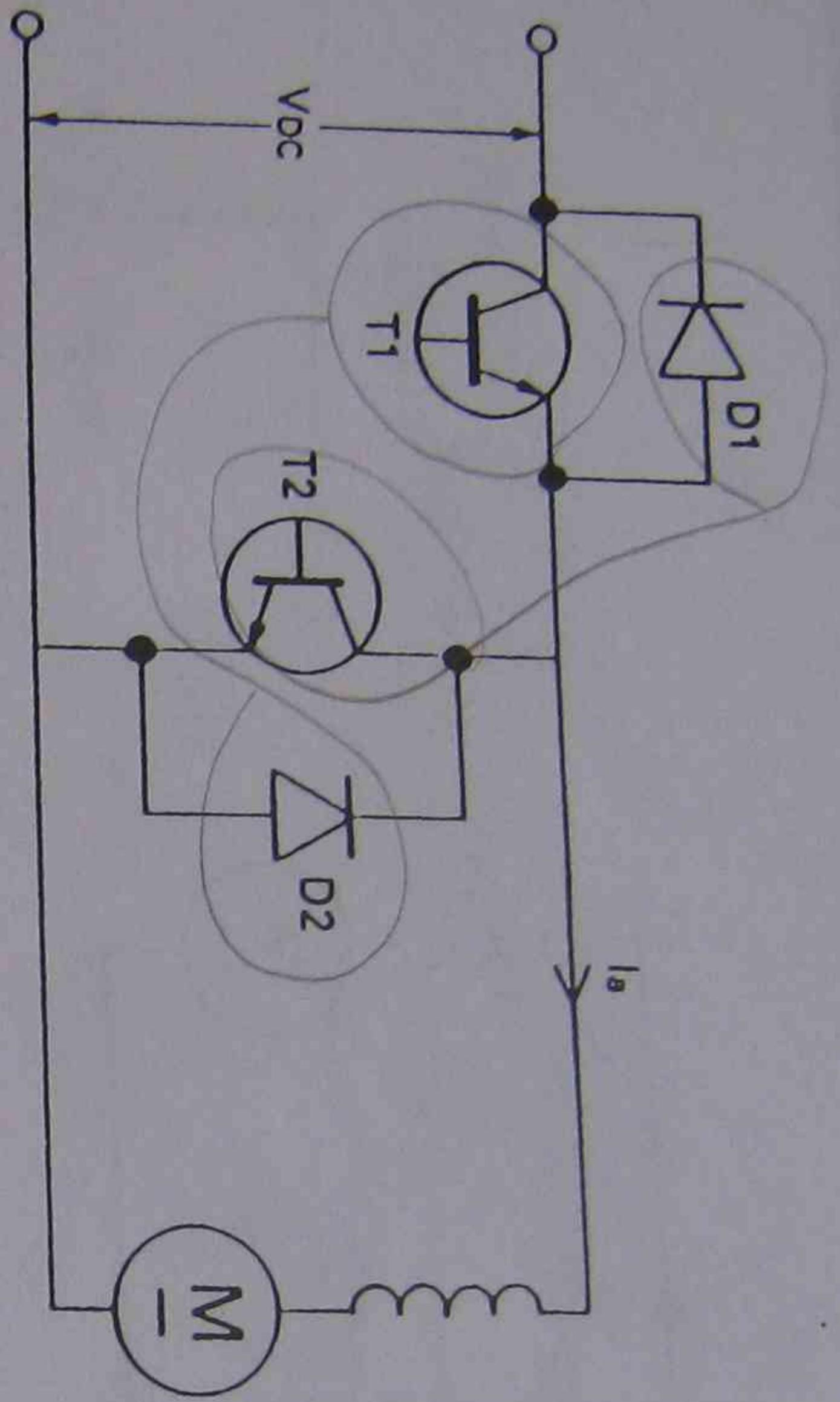


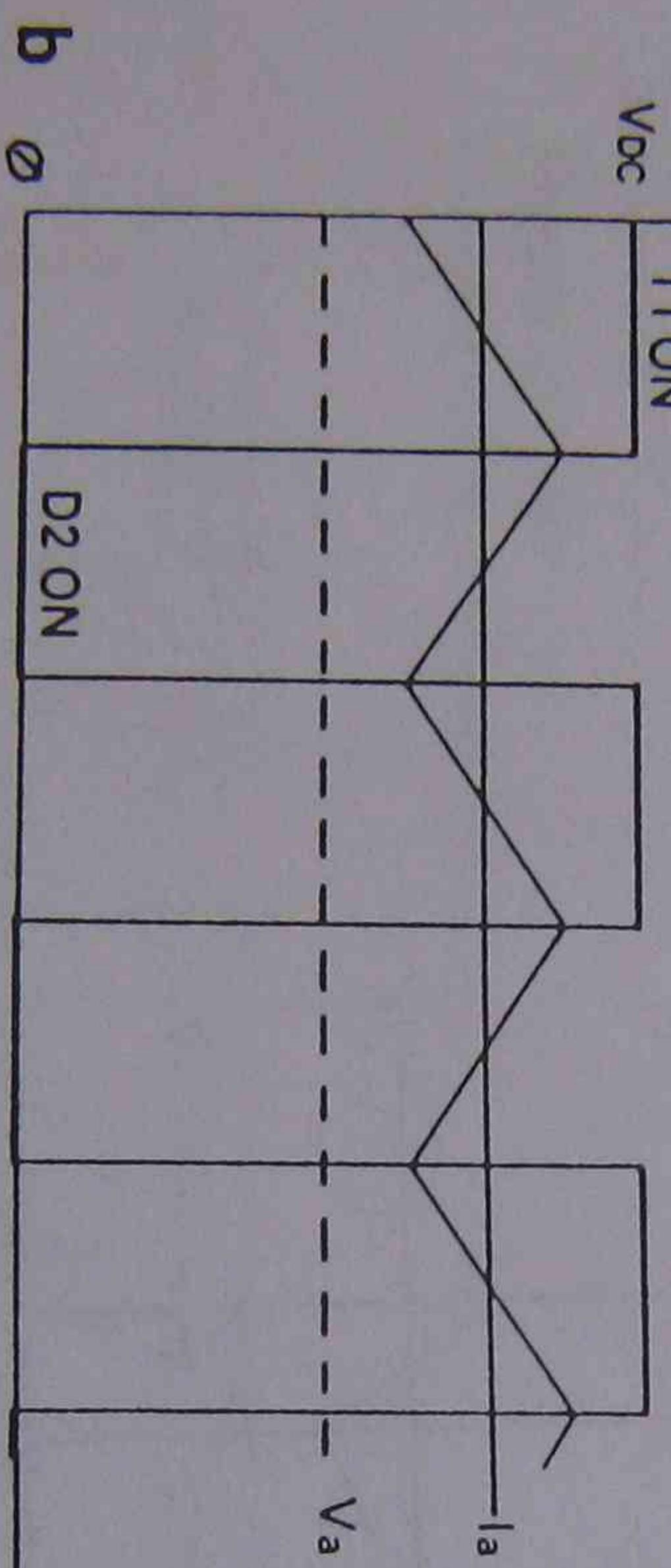- Quadrant 1 operation
- Motor driving
- Energy transferred from supply to motor
- Braking.



T_1 & D_2 control

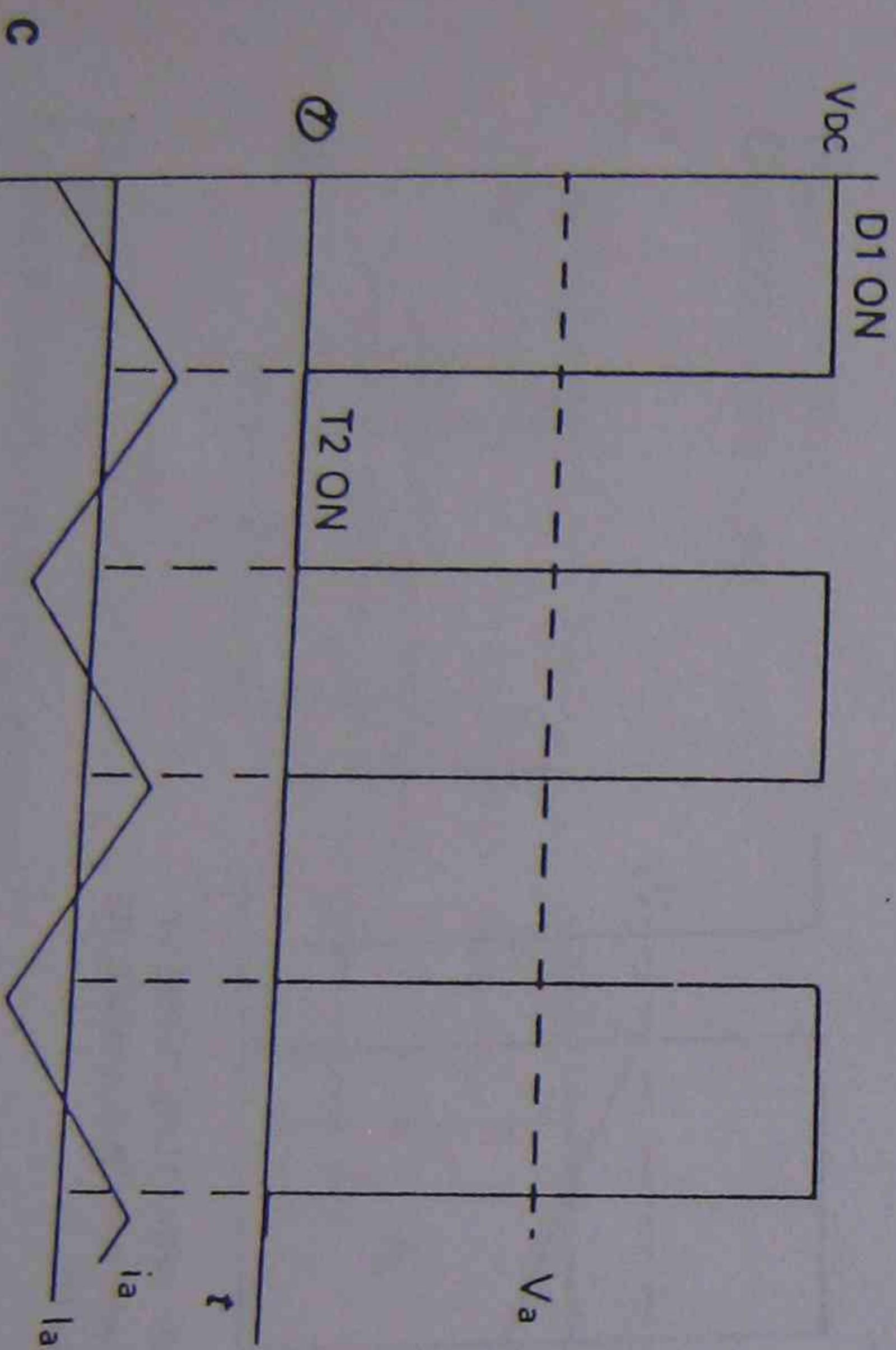- Quadrant 2
- Braking
- Energy transferred back from motor to the supply i.e. the motor is a generator with the supply as the load



- Two-quadrant dc-dc converter;
- a circuit;
- b forward
- motoring;
- c forward braking.