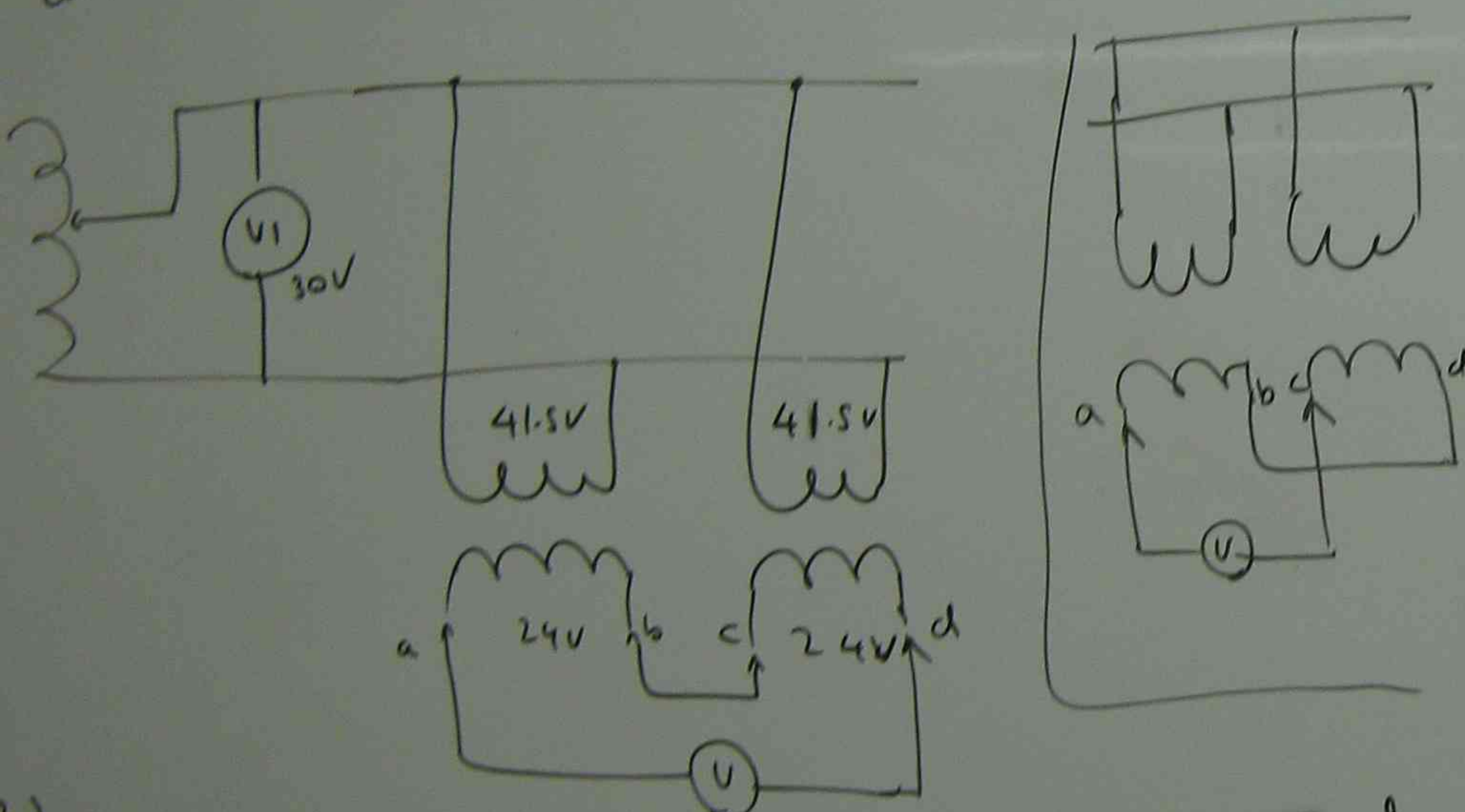


LAB (1) POWER TRANSFORMER POLARITY TEST

CONNECT THE GIVEN CIRCUIT



2) CONNECT b-c & MEASURE VOLTAGE ACROSS a-d

3) CONNECT b-d & MEASURE VOLTAGE ACROSS a-c

4) DETERMINE CORRECT SECONDARY CONNECTION FOR PARALLEL OPERATION

LAB (2)


TRANSFORMER CONNECTION

(1) REFER POWER TRANSFORMER VECTOR GROUPING

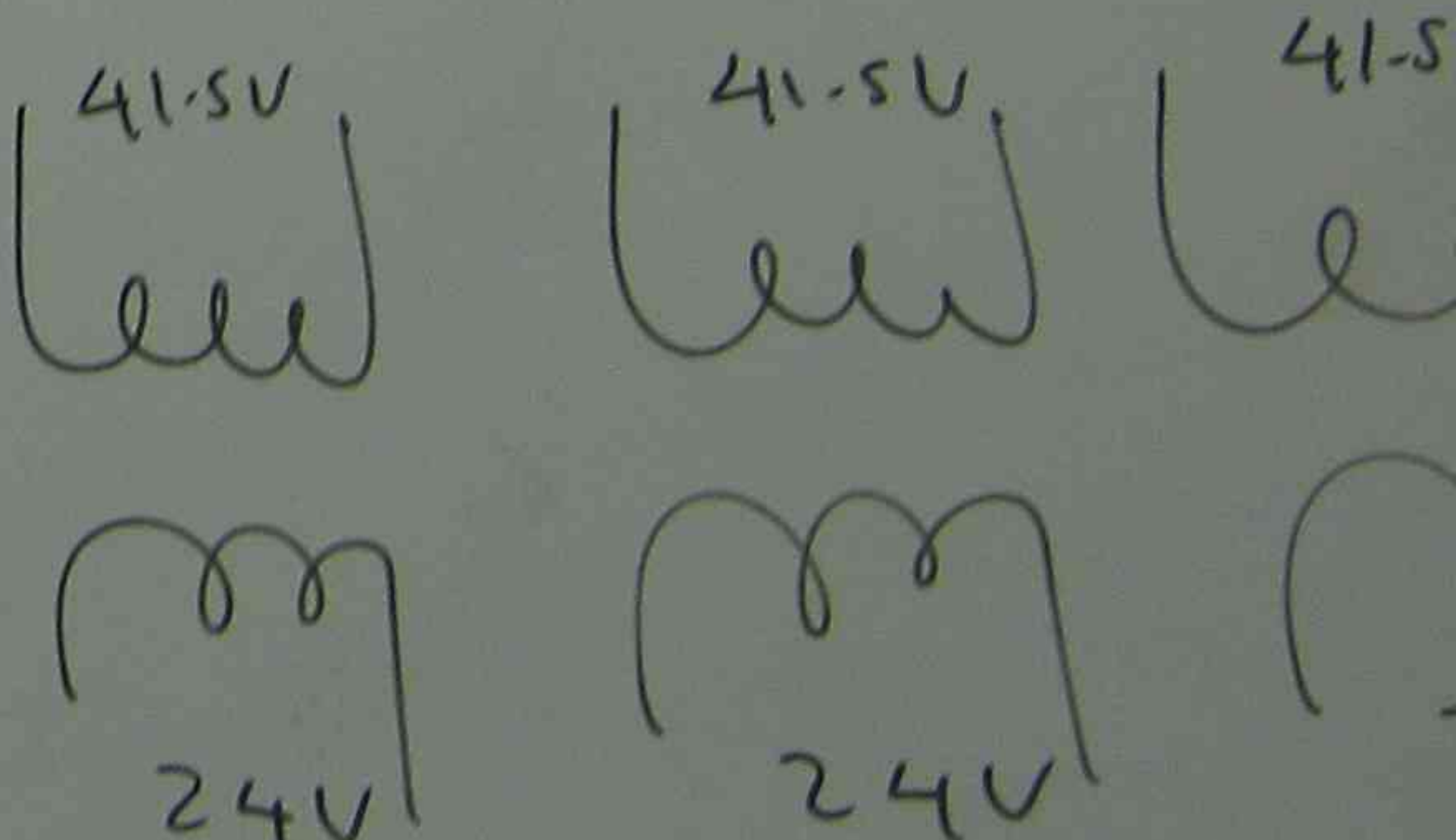(2) CONNECT Yy0, Dd6 AND

Yd11 CONNECTIONS FOR GIVEN TRANSFORMERS


(THREE SINGLE PHASE TRANS FOR 3φ CONNECTION



TEACHER
20 desks
20 chairs 3 Cap.

LAB (1) POWER TRANSFORMER POLARITY TEST

(1) CONNECT THE GIVEN CIRCUIT

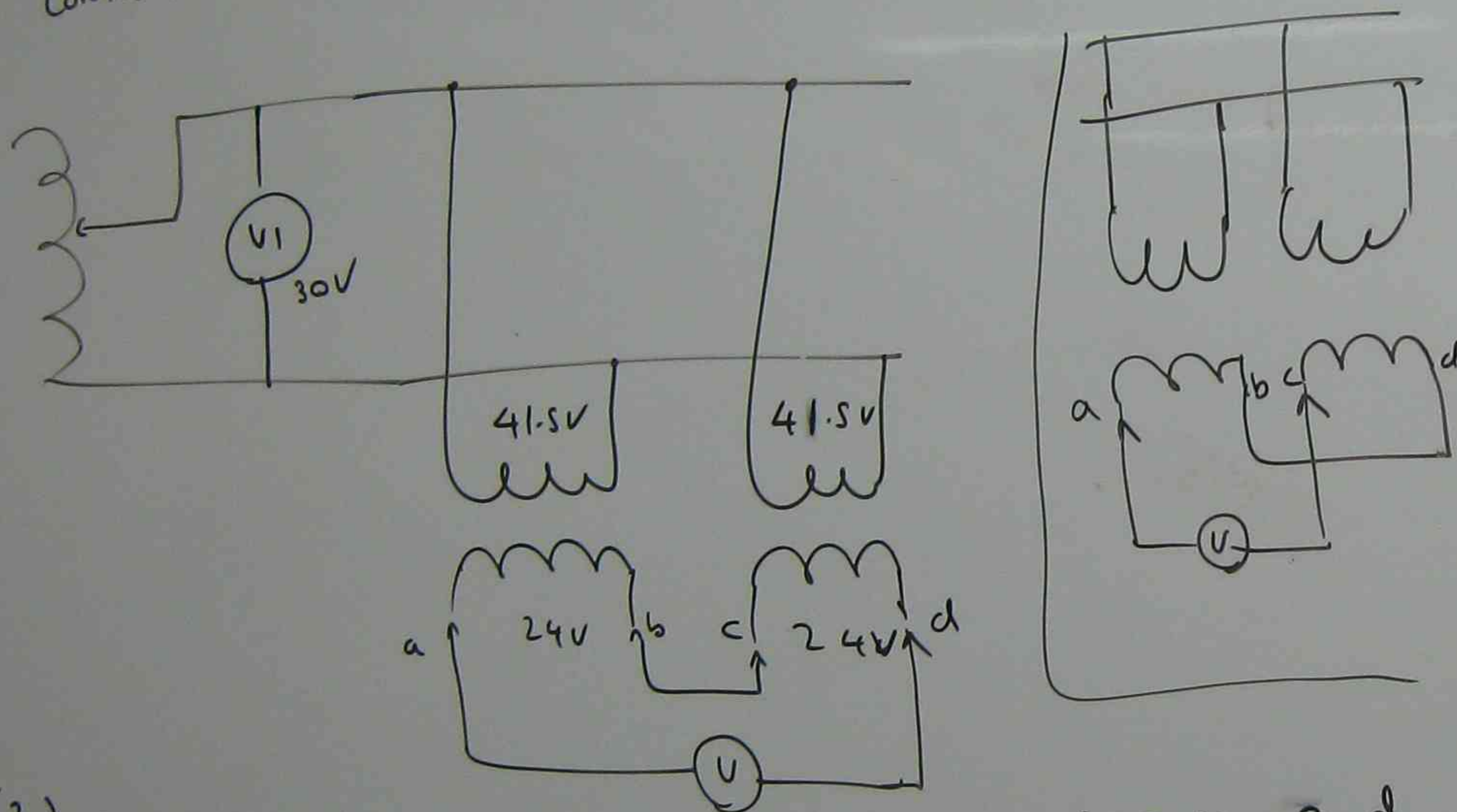

(2) CONNECT b-c & MEASURE VOLTAGE ACROSS a-d

(3) CONNECT b-d & MEASURE VOLTAGE ACROSS a-c

(4) DETERMINE CORRECT SECONDARY CONNECTION FOR PARALLEL OPERATION


LAB (2)

TRANSFORMER CONNECTION

(1) REFER POWER TRANSFORMER VECTOR GROUP

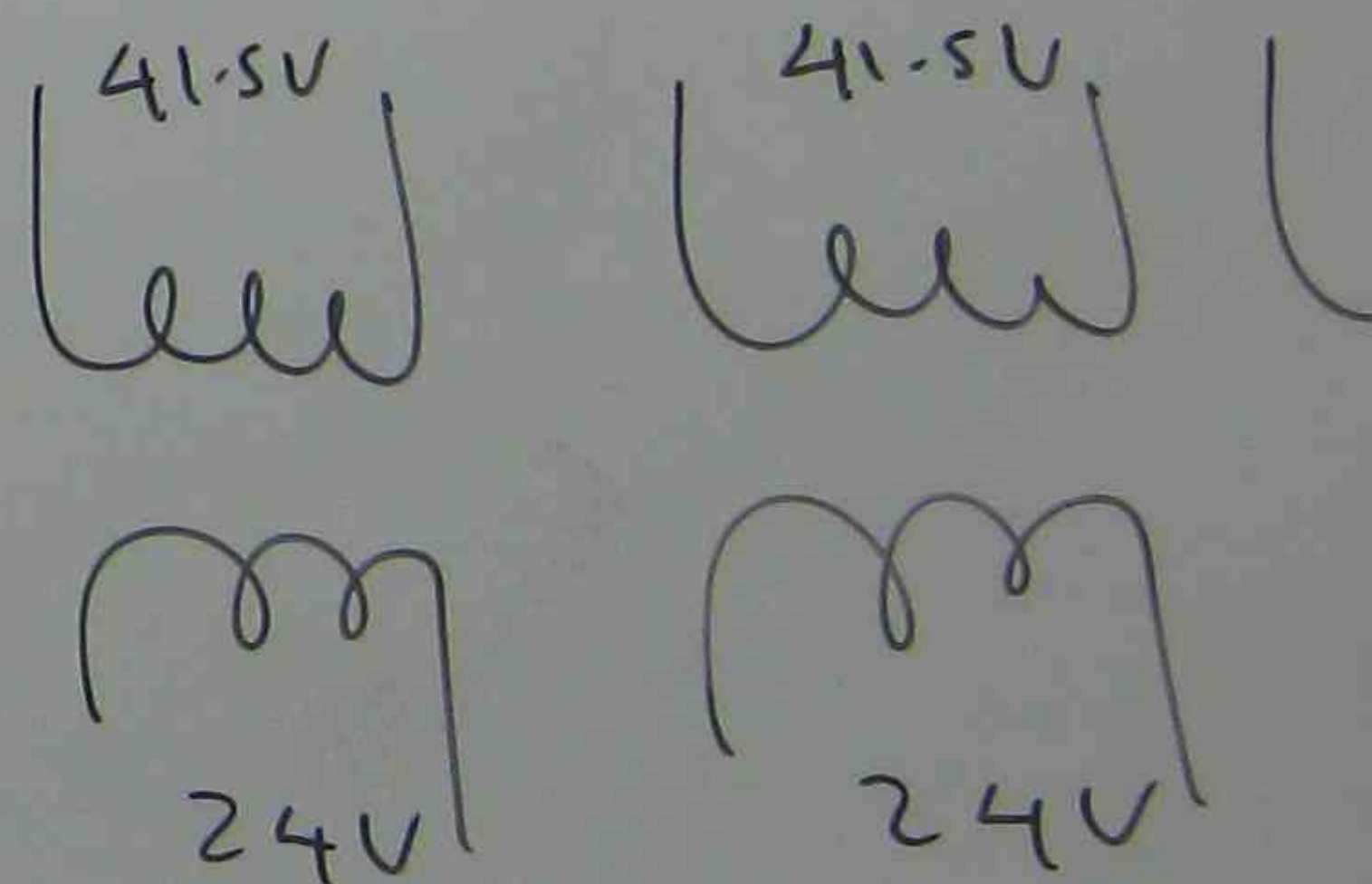(2) CONNECT Y_{y0} , $Dd6$ AND


$Yd11$ CONNECTIONS
GIVEN TRANSFORMERS
(THREE SINGLE PHASE -
FOR 3 ϕ CONNECTION



(3)

TRANSFORMER OPEN CIRCUIT | SHORT CIRCUIT TEST

CONNECT THE GIVEN CIRCUIT

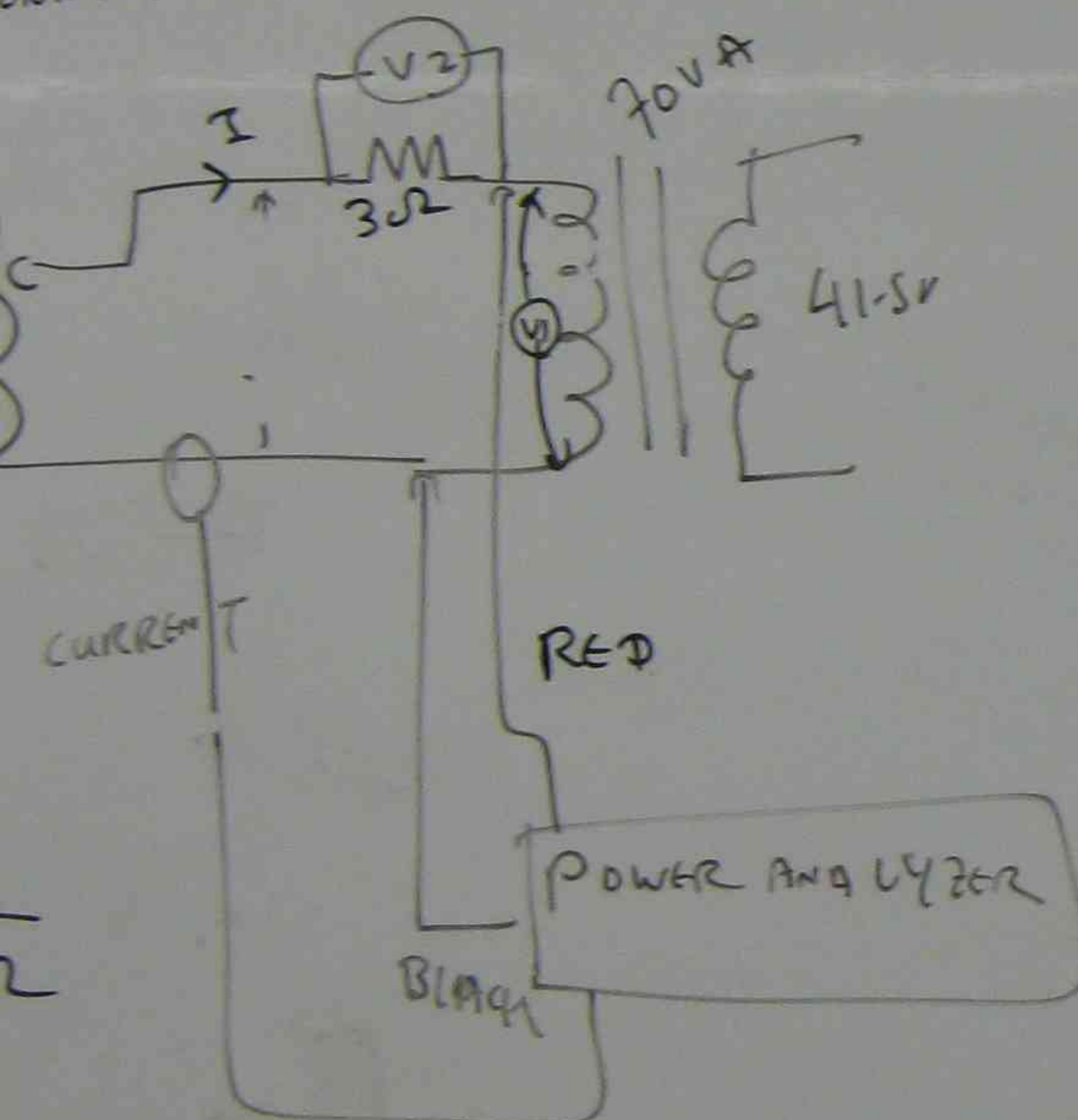

MEASURE $V_1, V_2,$


TAKE VOLTAGE, P.F. READING
OF POWER ANALYZER

$$\text{Power} = U \times I \times \text{P.F.} \\ = U_1 \times \frac{V_2}{30\Omega} \times \cos\phi$$

$$\frac{V^2}{R_{htc}} = \text{power} \quad R_{htc} =$$

$$\frac{V^2}{X_m} = \text{power} \times \tan\phi \quad X_m =$$

CONNECT THE GIVEN CIRCUIT

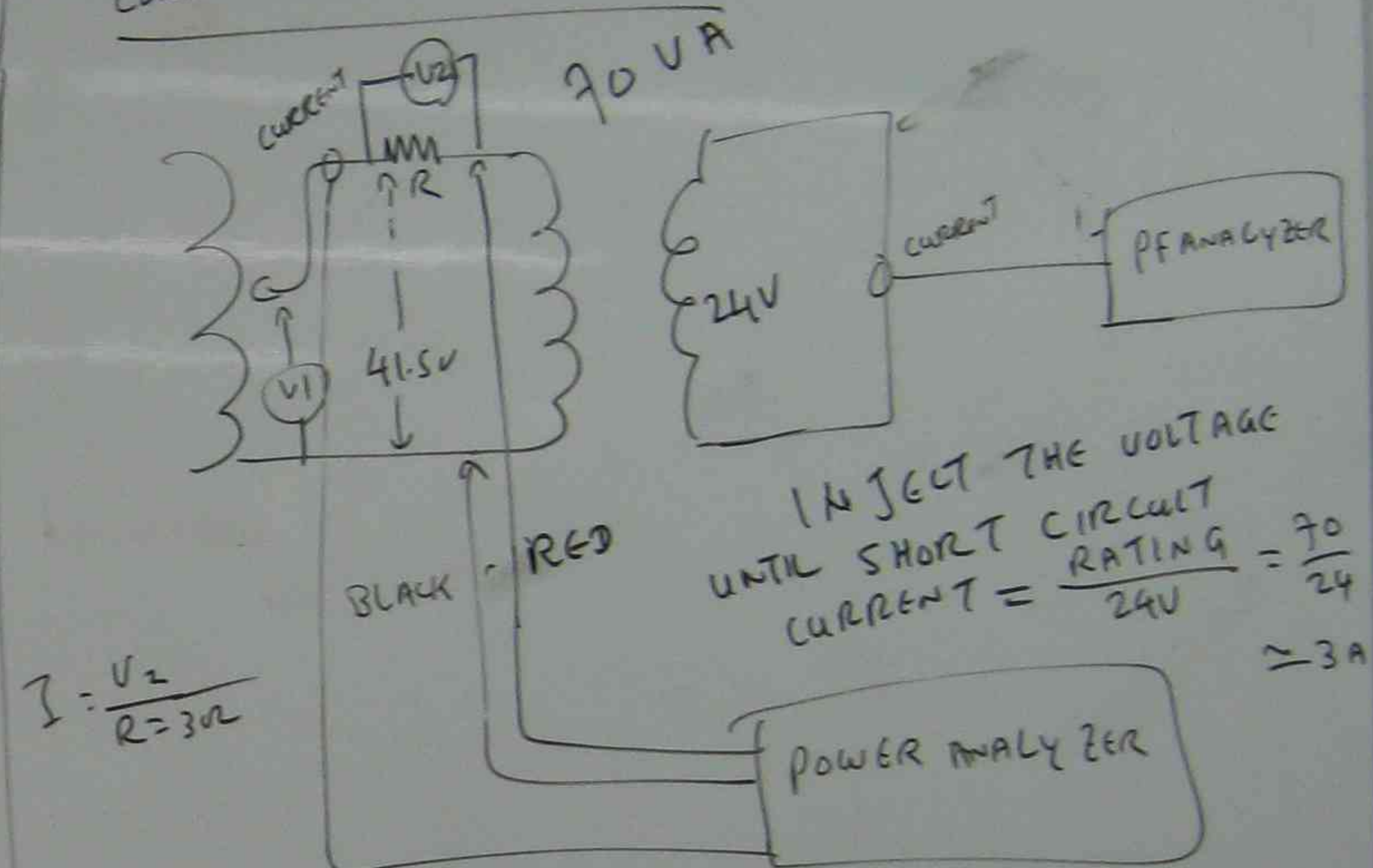

$$I = \frac{V_2}{R = 30\Omega}$$

$$I^2 R_e'' = \text{power} \quad R_e'' = \frac{V}{I}$$

$$X_e'' = \sqrt{(Z_e'')^2 - (R_e'')^2} =$$

