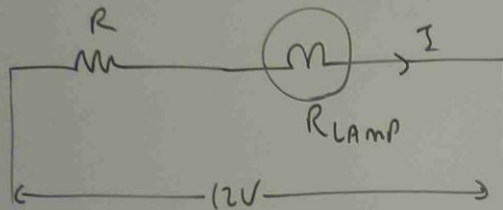


LAMPS AND RESISTOR CIRCUITS

- ① AN INDICATOR LAMP RATED AT 6V, 0.6W IS REQUIRED TO SHOW WHEN A 12V SUPPLY IS SWITCHED ON. CALCULATE THE RESISTANCE AND POWER RATING OF A SUITABLE DROPPER RESISTOR.

LAMP 6V, 0.6W



$$I (\text{PASSING THROUGH LAMP}) = \frac{P}{V} = \frac{0.6 \text{ W}}{6 \text{ V}} = 0.1 \text{ Amp}$$


$$R_T = \frac{V_t}{I_t} = \frac{12}{0.1} = 120 \Omega$$

$$P = \frac{V^2}{R_{\text{LAMP}}} \rightarrow R_{\text{LAMP}} = \frac{V^2}{P} = \frac{6^2}{0.6} = \frac{36}{0.6} = 60 \Omega$$

$$\begin{aligned} R &= R_T - R_{\text{LAMP}} \\ &= 120 - 60 \\ &= 60 \Omega \end{aligned}$$

LAMPS IN SERIES AND PARALLEL

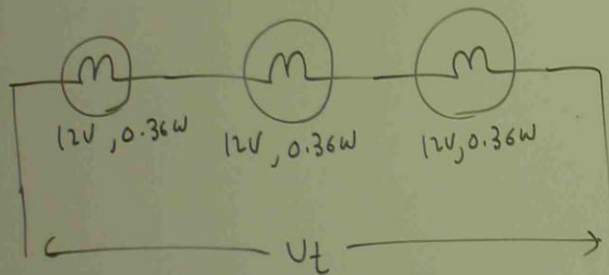- ② THREE FILAMENT LAMP INDICATORS ARE EACH RATED AT 12V, 0.36W. IF THEY ARE CONNECTED IN SERIES, WHAT SUPPLY VOLTAGE SHOULD BE USED?, WHAT CIRCUIT CURRENT WILL FLOW AND WHAT TOTAL POWER WILL THE CIRCUIT DISSIPATE?




$$P_T = 0.36 + 0.36 + 0.36 = 1.08 \text{ W}$$

$$V_t = 12 + 12 + 12 = 36 \text{ V}$$

$$I_t = \frac{P_T}{V_T} = \frac{1.08}{36} = 0.03 \text{ A (OR) } 30 \text{ mA}$$

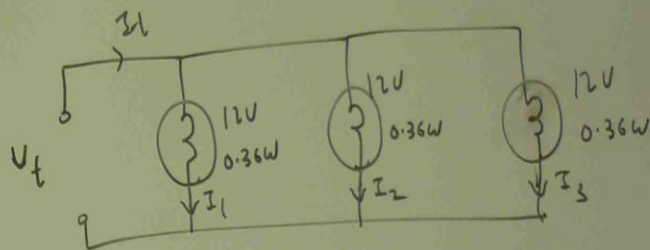- ③ THE SAME THREE 12V, 0.36W LAMPS ARE CONNECTED IN PARALLEL. AGAIN FIND THE SUPPLY VOLTAGE TO BE USED. THE CIRCUIT CURRENT AND TOTAL POWER DISSIPATED.



$$V_t = 12 \text{ V}$$

$$I_1 = I_2 = I_3 = \frac{P}{V} = \frac{0.36}{12} = 0.03 \text{ A}$$

$$I_t = I_1 + I_2 + I_3 = 0.03 + 0.03 + 0.03 = 0.09 \text{ A}$$


$$P_t = V_t \times I_t = 12 \times 0.09 = 1.08 \text{ W}$$

EXERCISE

- ① A 24V, 1.2W INDICATOR LAMP IS TO BE USED FROM A 115V SUPPLY AS SHOWN IN FIGURE.


A SUITABLE BALLAST RESISTOR VALUE IS

- (a) 2300Ω (b) 480Ω (c) 91Ω (d) 1820Ω

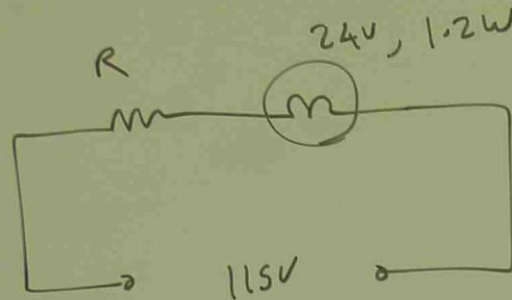

- ② A SUITABLE POWER RATING FOR THE ABOVE PROBLEM IS
- (a) 5W (b) 10W (c) 2W (d) 7.27W


THE POTENTIAL DIVIDER

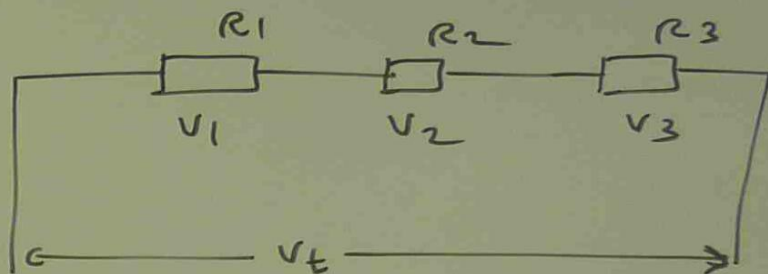

$$V_1 = V_t \times \frac{R_1}{R_1 + R_2 + R_3}$$


$$V_2 = V_t \times \frac{R_2}{R_1 + R_2 + R_3}$$
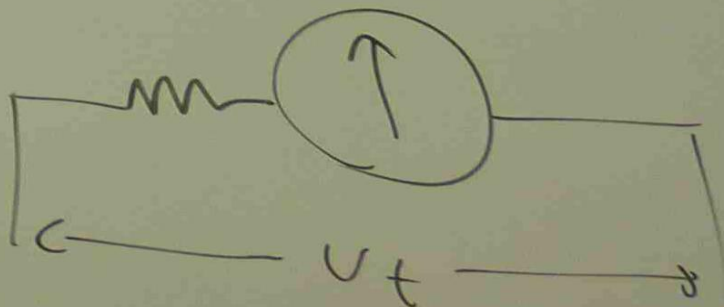
$$V_3 = V_t \times \frac{R_3}{R_1 + R_2 + R_3}$$



pb ①

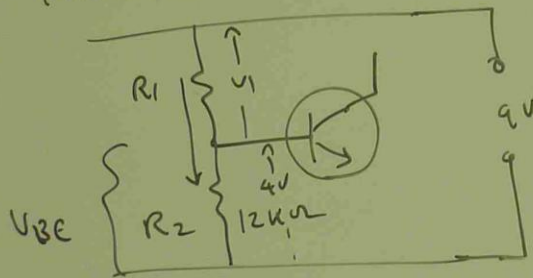A CIRCUIT IS FED WITH A 9V SUPPLY. BUT A 4V POTENTIAL TO GROUND IS REQUIRED AT THE BASE OF A PARTICULAR TRANSISTOR. IF THIS VOLTAGE IS TO BE DERIVED FROM THE SUPPLY WITH A 12 KΩ RESISTOR CONNECTED TO GROUND, CALCULATE THE VALUE OF THE SECOND RESISTOR FORMING THE NECESSARY POTENTIAL DIVIDER





$$V_{R_1} + V_{R_2} = V_T = 9V$$

$$V_{R_1} = V_T - V_{R_2}$$

$$= 9 - 4 = 5V$$

$$R_1 = \frac{V_{R_1}}{I_{R_1}}$$

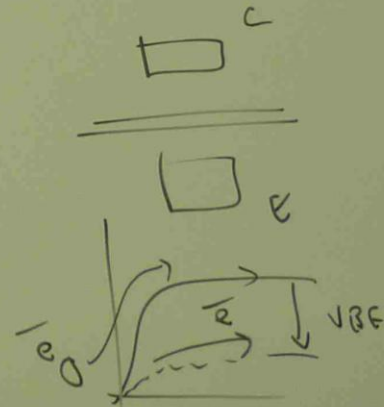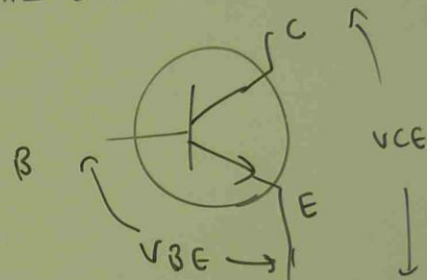


$$\begin{aligned}
 I_{R_2} &= \frac{V_2}{R_2} \\
 &= \frac{4}{12 \text{ k}\Omega} \\
 &= 0.333 \text{ mA}
 \end{aligned}$$

$$I_{R_2} = I_{R_1} = 0.333 \text{ mA}$$


$$\begin{aligned}
 R_1 &= \frac{V_{R_1}}{I_{R_1}} \\
 &= \frac{5}{0.333 \times 10^{-3}}
 \end{aligned}$$

$$= 15 \times 10^3 \Omega$$


$$= 15 \text{ k}\Omega$$

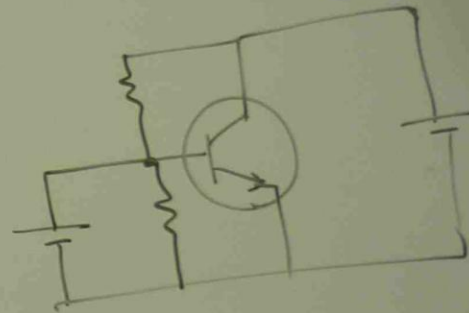


VARIBLE RESISTORS

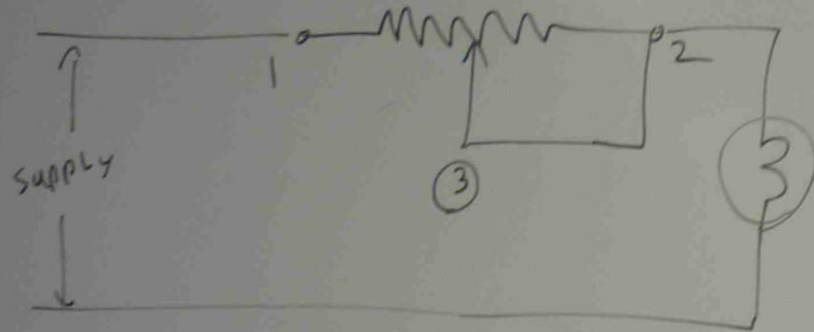


ELECTRONIC POTENTIOMETER

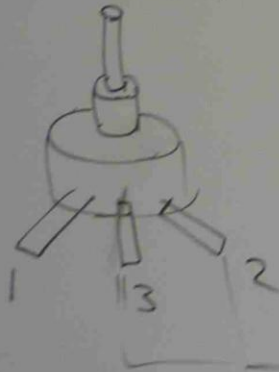

RHEOSTAT

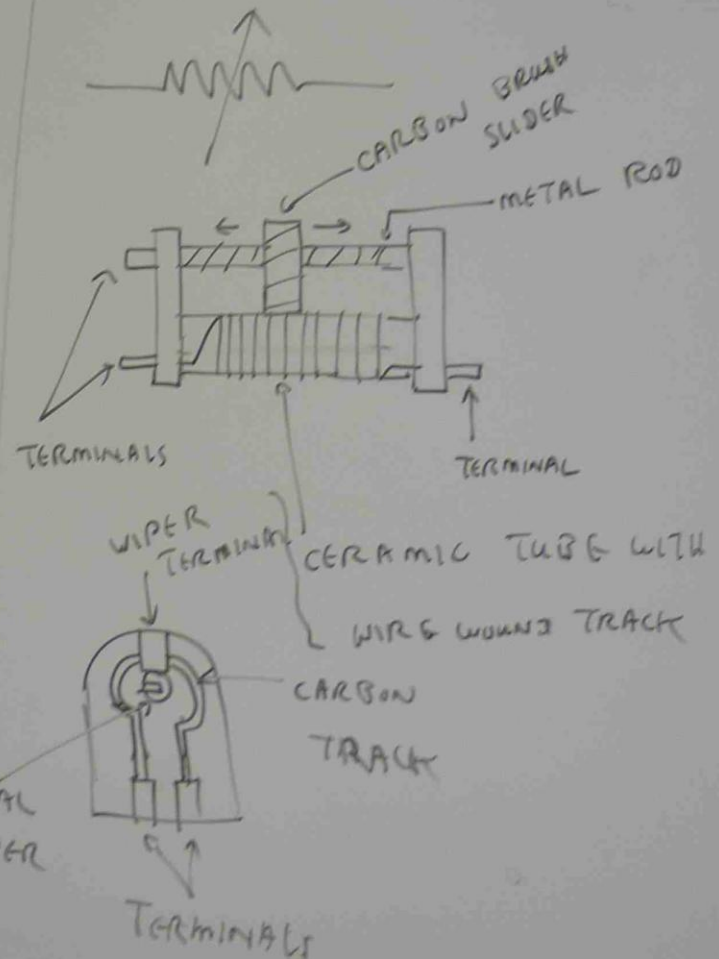

NON LINEAR POTENTIAL METER

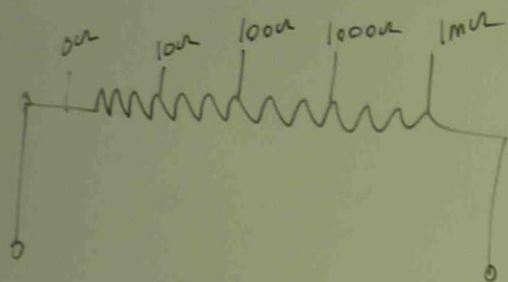


Pb

A LINEAR POTENTIAL DIVIDER

POT HAS A TOTAL RESISTANCE $45k\Omega$ AND IS CONNECTED ACROSS A $6V$ SUPPLY. IF A VOLTAGE OF $2V$ IS REQUIRED WITH ONE END CONNECTED TO THE POSITIVE SIDE OF THE SUPPLY, WHAT WILL BE THE RESISTANCE VALUES ON EITHER SIDE OF THE TAPPING AND

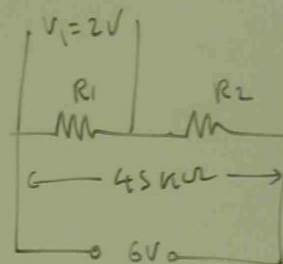THROUGH WHAT FRACTION OF ITS TOTAL POSSIBLE MOVEMENT FROM THE POSITIVE END WILL THE SLIDER HAVE TO BE MOVED?



$$V_1 = V_t \times \frac{R_1}{R_1 + R_2}$$

$$2 = 6 \times \frac{R_1}{45k}$$

$$R_1 = \frac{45 \times 2}{6} = 15k\Omega$$

$$R_2 = R_t - R_1 = 45 - 15 = 30k\Omega$$

EXERCISE

- ① Two resistors both of $56\text{ k}\Omega$ are connected across a 9 V supply. The voltage across one resistor will be
(a) 3 V (b) 18 V (c) 6 V (d) 4.5 V
- ② A $22\text{ k}\Omega$ and a $68\text{ k}\Omega$ resistor form a potential divider across a 15 V supply. The voltage across the $22\text{ k}\Omega$ resistor will be
(a) 3.67 V (b) 36.7 V (c) 11.3 V (d) 4.71 V
- ③ A potential divider consists of $120\text{ k}\Omega$ and $180\text{ k}\Omega$ resistors. If the voltage across $120\text{ k}\Omega$ resistor is 3 V , the supply voltage is (a) 5 V (b) 7.5 V (c) 6 V (d) 12 V
- ④ The maximum permissible current drain on a 12 V supply is $120\text{ }\mu\text{A}$, an output of 2.16 V is required, a suitable divider could be made of resistors with values of
(a) $18\text{ k}\Omega$ & $47\text{ k}\Omega$ (b) $82\text{ k}\Omega$ & $12\text{ k}\Omega$ (c) $33\text{ k}\Omega$ & $120\text{ k}\Omega$ (d) $82\text{ k}\Omega$ & $18\text{ k}\Omega$