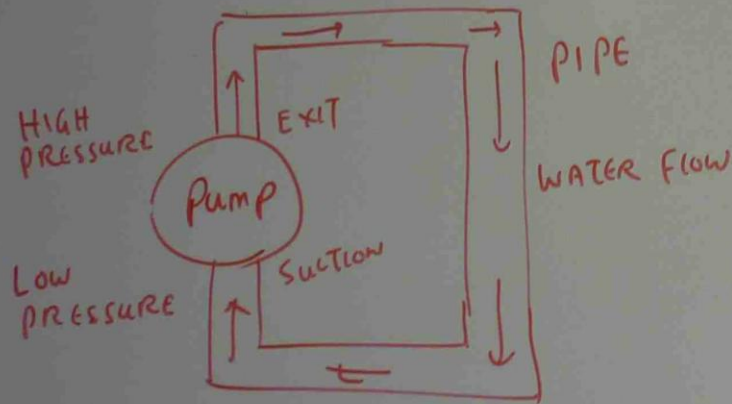



DC CIRCUITS

(E003 + E004)

1:30 → 3:30 THEORY (DC CIRCUIT E003 + E004)
3:30 → 5:00 - PRACTICAL



HYDRAULIC SYSTEM

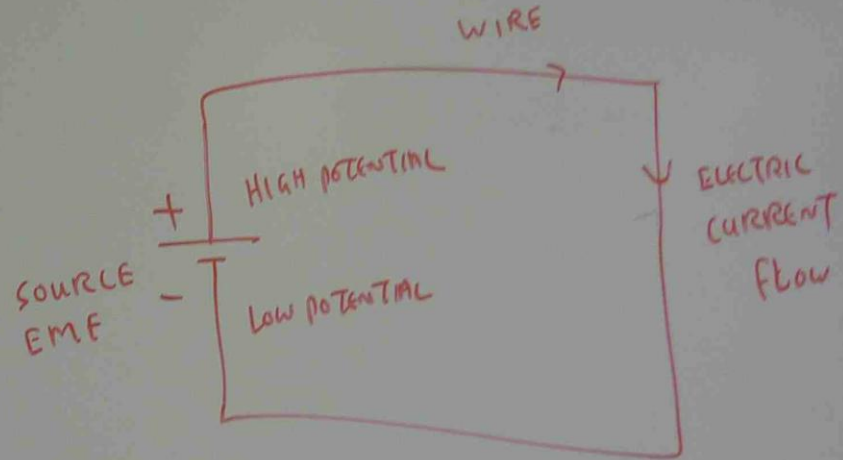


ELECTRIC SYSTEM

OHM'S LAW

$$I = \frac{V}{R}$$

I = CURRENT
 V = VOLTAGE
 R = RESISTANCE

DC SERIES CIRCUITS

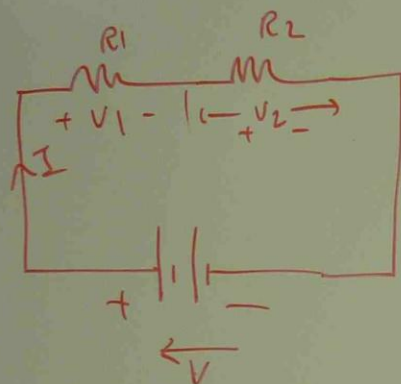

$$V = V_1 + V_2$$


$$R_T = R_1 + R_2$$

$$I = \frac{V_1}{R_1} = \frac{V_2}{R_2}$$

pb ①

RESISTORS OF 5Ω AND 7Ω ARE CONNECTED IN SERIES TO $12V$ SUPPLY. CALCULATE

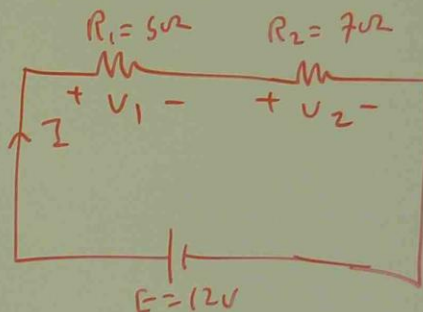- TOTAL RESISTANCE OF THE CIRCUIT
- CIRCUIT CURRENT
- POTENTIAL DIFFERENCE ACROSS EACH RESISTOR.




$$(a) \text{ TOTAL RESISTANCE} = R_1 + R_2 = 5 + 7 = 12\Omega$$

$$(b) I = \frac{E}{R_T} = \frac{12}{12} = 1 \text{ Amp}$$

$$(c) V_1 = I R_1 = 1 \times 5 = 5V, V_2 = I R_2 = 1 \times 7 = 7V$$

pb ②

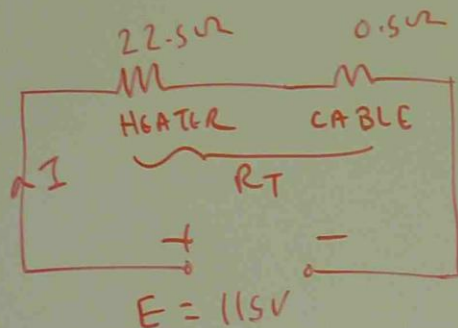AN ELECTRIC HEATER OF RESISTANCE 22.5Ω IS CONNECTED TO A $115V$ SUPPLY THROUGH A CABLE OF TOTAL RESISTANCE 0.5Ω .
CALCULATE THE CIRCUIT CURRENT AND THE POTENTIAL DIFFERENCE ACROSS THE HEATER.




$$R_T = 22.5 + 0.5 = 23\Omega$$

$$I = \frac{E}{R_T} = \frac{115}{23} = 5A$$

$$\begin{aligned}\text{VOLTAGE ACROSS HEATER} &= I R \\ &= 5 \times 22.5 \\ &= 112.5V\end{aligned}$$

Prob 3

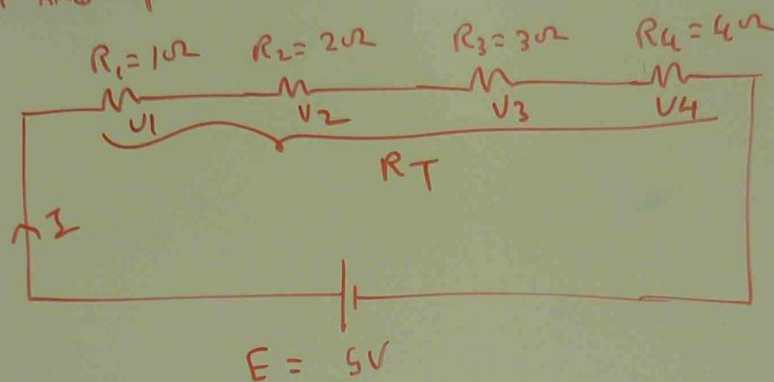FOUR RESISTORS OF VALUES 1Ω , 2Ω , 3Ω AND 4Ω ARE CONNECTED IN SERIES TO $5V$ SUPPLY. CALCULATE THE CIRCUIT CURRENT AND POTENTIAL DIFFERENCE ACROSS EACH RESISTOR.



$$R_T = R_1 + R_2 + R_3 + R_4 = 1 + 2 + 3 + 4 = 10\Omega$$

$$I = \frac{E}{R_T} = \frac{5}{10} = 0.5A$$

$$V_1 = I R_1 = 0.5 \times 1 = 0.5V$$

$$V_2 = I R_2 = 0.5 \times 2 = 1V$$

$$V_3 = I R_3 = 0.5 \times 3 = 1.5V$$

$$V_4 = I R_4 = 0.5 \times 4 = 2V$$

CURRENT

$$1 \text{ kA} = 1000 \text{ A} = 10^3 \text{ A}$$

$$1 \text{ mA} = \frac{1}{1000} \text{ A} = 10^{-3} \text{ A}$$

$$1 \text{ }\mu\text{A} = \frac{1}{1,000,000} \text{ A} = 10^{-6} \text{ A}$$

RESISTANCE

$$1 \text{ }\Omega$$

$$1 \text{ k}\Omega = 1000 \Omega = 10^3 \Omega$$

$$1 \text{ M}\Omega = 1,000,000 \Omega = 10^6 \Omega$$

VOLTAGE


$$1 \text{ V}$$

$$1 \text{ mV} = 10^{-3} \text{ V}$$

$$1 \text{ kV} = 1000 \text{ V}$$

$$1 \text{ }\mu\text{V} = 10^{-6} \text{ V}$$

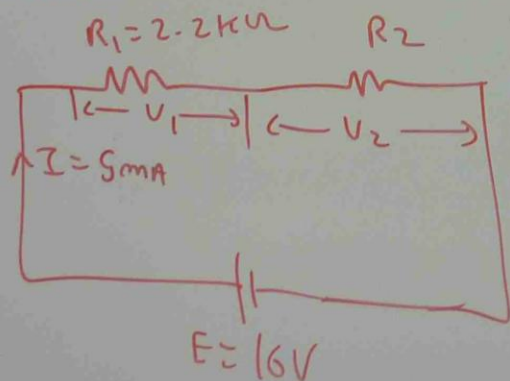PB 4 A $2.2 \text{ k}\Omega$ RESISTOR IS CONNECTED IN SERIES WITH A RESISTOR OF UNKNOWN VALUE ACROSS A 16 V SUPPLY. IF THE CIRCUIT CURRENT FLOW IS 5 mA , CALCULATE THE VALUE OF THE UNKNOWN RESISTOR.



$$V_1 = I R_1 = 5 \times 10^{-3} \times 2.2 \times 10^3 = 11 \text{ V}$$

$$V_1 + V_2 = E$$

$$11 + V_2 = 16$$

$$V_2 = 16 - 11 = 5 \text{ V}$$

$$R_2 = \frac{V_2}{I}$$


$$= \frac{5}{5 \times 10^{-3}}$$

$$= 10^3 \Omega$$

$$= 1 \text{ k}\Omega$$

pb 5

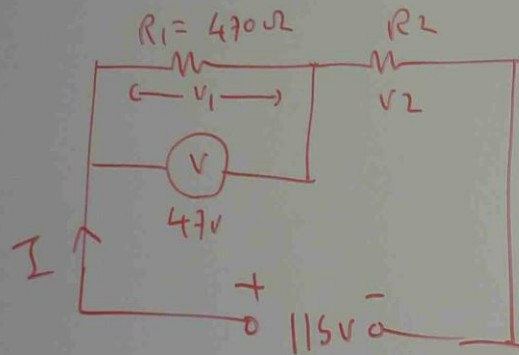TWO RESISTORS ARE CONNECTED IN SERIES TO A 115 V SUPPLY.
ONE IS KNOWN TO HAVE A RESISTANCE OF 470Ω AND A VOLTMETER
CONNECTED ACROSS IT SHOWS A READING OF 47V.
CALCULATE (a) THE VALUE OF SECOND RESISTOR
(b) THE CIRCUIT CURRENT



$$V_1 + V_2 = V_T = 115 \text{ V}$$

$$47 + V_2 = 115 \text{ V}$$

$$V_2 = 115 - 47 = 68 \text{ V}$$

$$I = I_1 = \frac{V}{R_1} = \frac{47}{470} = 0.1 \text{ A}$$


$$I = I_2 = 0.1 \text{ A}$$

$$R_2 = \frac{V_2}{I_2} = \frac{68}{0.1} = 680\Omega$$

EXERCISE


- ① THE EFFECTIVE RESISTANCE OF A NUMBER OF RESISTORS CONNECTED IN SERIES IS
- (a) THE SUM OF THE INDIVIDUAL RESISTANCE VALUES
 - (b) EQUAL TO THE RESISTANCE OF THE HIGHEST VALUE RESISTOR
 - (c) SMALLER THAN THE LOWEST INDIVIDUAL RESISTOR VALUE
- ② INDICATE WHICH OF THE FOLLOWING STATEMENTS DOES NOT APPLY TO RESISTORS CONNECTED IN SERIES
- (a) THEY ALL CARRY THE SAME CURRENT
 - (b) THE TOTAL CIRCUIT RESISTANCE IS EQUAL TO THE SUM OF THE INDIVIDUAL RESISTOR VALUES
 - (c) THE SUPPLY VOLTAGE IS EQUAL TO THE SUM OF THE INDIVIDUAL RESISTOR VOLTAGE DROPS
 - (d) THE CURRENT IN EACH RESISTOR IS DIFFERENT
- ③ THE POTENTIAL DIFFERENCE ACROSS A RESISTOR WHICH IS CONNECTED IN SERIES OF OTHERS IS
- (a) EQUAL TO SUPPLY VOLTAGE
 - (b) NEGLIGIBLE
 - (c) MUST BE LESS THAN THE SUPPLY VOLTAGE
 - (d) HIGHER THAN SUPPLY VOLTAGE.

- (4) THE CURRENT FLOWING IN A RESISTOR CONNECTED IN SERIES WITH ANOTHER WILL BE
- (a) THE SAME AS THAT IN THE OTHER RESISTOR
 - (b) DEPENDENT ONLY ON THE SUPPLY VOLTAGE AND ITS RESISTANCE VALUE
 - (c) UNRELATED TO THAT IN THE OTHER RESISTOR
 - (d) THE SMALLER OF THE TWO CURRENTS

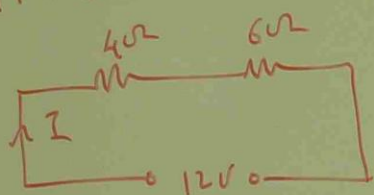
- (5) THE CURRENT IN THE FIGURE WILL BE
- 
- (a) 1.2A (b) 3A (c) 0.2A (d) 2A

- (6) THE POTENTIAL DIFFERENCE ACROSS 6Ω RESISTOR IN ABOVE FIGURE WILL BE
- (a) 12V (b) 6V (c) 4.8V (d) 7.2V

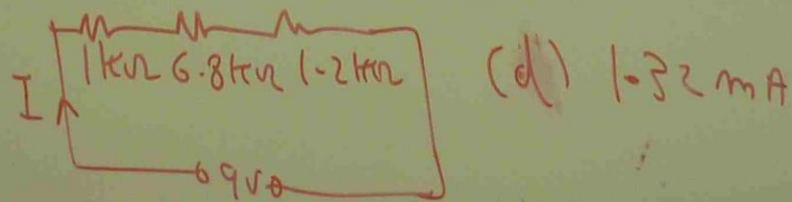- (7) THE CURRENT FLOWING IN THE CIRCUIT OF FIGURE BELOW WILL BE
- (a) 1A (b) 1mA (c) 9mA




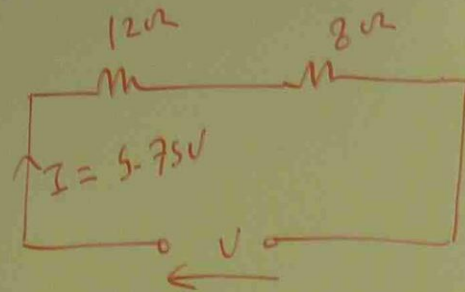(8) THE SUPPLY VOLTAGE OF THE FIGURE BELOW WILL BE



- (a) 69V (b) 20V (c) 115V
(d) 46V

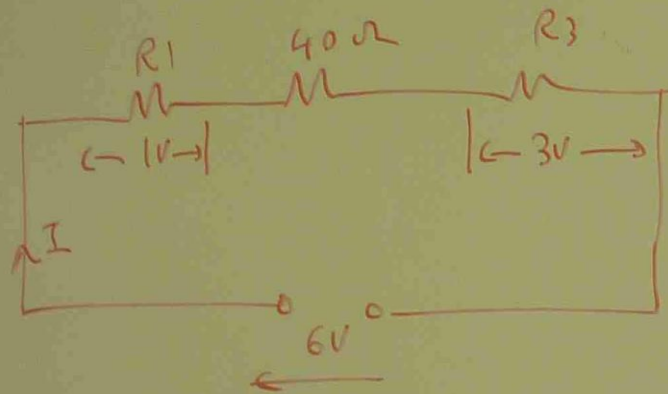
(9) THE CURRENT FLOWING IN THE CIRCUIT BELOW WILL BE



- (a) 50mA (b) 6.7 A (c) 3mA (d) 150mA

DC PARALLEL CIRCUITS

PARALLEL CONNECTION OF RESISTORS

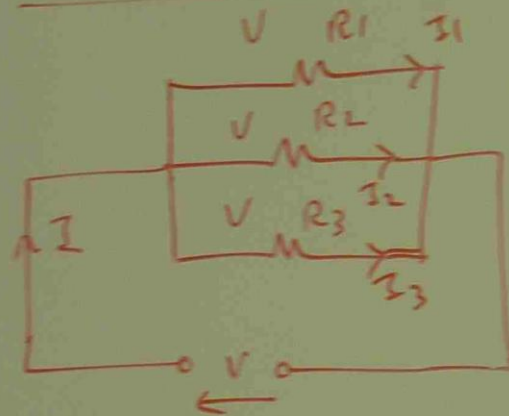


$$I_1 = \frac{V}{R_1}, \quad I_2 = \frac{V}{R_2}, \quad I_3 = \frac{V}{R_3}$$

$$I = I_1 + I_2 + I_3$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Pb ①

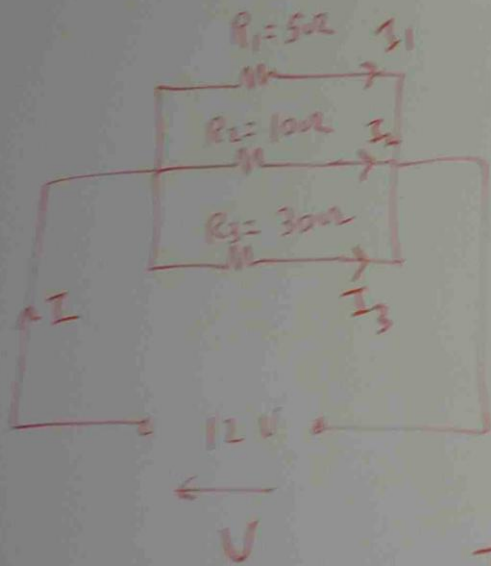RESISTORS OF 5Ω , 10Ω AND 30Ω ARE CONNECTED IN PARALLEL TO A $12V$ SUPPLY. CALCULATE THE SUPPLY CURRENT



$$I_1 = \frac{V}{R_1} = \frac{12}{5} = 2.4 \text{ A}$$

$$I_2 = \frac{V}{R_2} = \frac{12}{10} = 1.2 \text{ A}$$

$$I_3 = \frac{V}{R_3} = \frac{12}{30} = 0.4 \text{ A}$$

$$I = I_1 + I_2 + I_3$$

$$= 2.4 + 1.2 + 0.4$$

$$= 4 \text{ A}$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_T} = \frac{R_2 R_3 + R_1 R_3 + R_1 R_2}{R_1 R_2 R_3}$$

3 RESISTORS
||

$$R_T = \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

4 RESISTORS
||

$$R_T = \frac{R_1 R_2 R_3 R_4}{R_1 R_2 R_3 + R_2 R_3 R_4 + R_3 R_4 R_1 + R_4 R_1 R_2}$$


Pb(2) RESISTORS OF $33\text{ k}\Omega$ AND $68\text{ k}\Omega$ ARE CONNECTED IN

PARALLEL TO A 50V SUPPLY. CALCULATE

(a) TOTAL CIRCUIT RESISTANCE

(b) TOTAL CIRCUIT CURRENT

(c) INDIVIDUAL BRANCH CURRENTS.

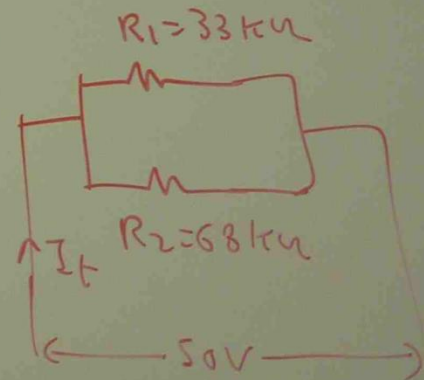

$$(a) \quad \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

$$= \frac{33 \times 68}{33 + 68}$$

$$= \frac{33 \times 68}{101}$$

$$= 22.2 \text{ k}\Omega$$

$$(c) \quad I_1 = \frac{V}{R_1} = \frac{50}{33 \times 10^3} = 1.5 \text{ mA}$$


$$I_2 = \frac{V}{R_2} = \frac{50}{68 \times 10^3} = 0.74 \text{ mA}$$

$$(b) \quad I_T = I_1 + I_2 = 1.5 + 0.74$$

$$= 2.24 \text{ mA}$$

pb 3

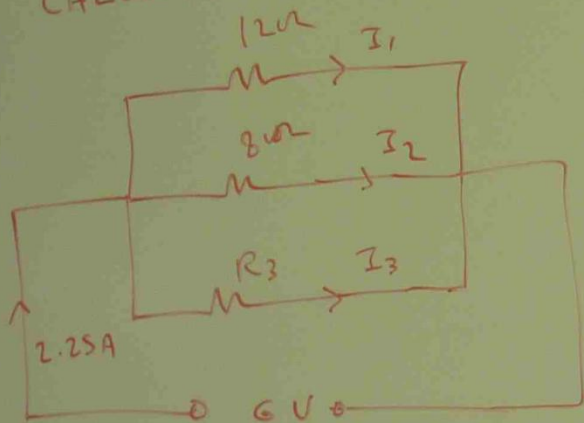RESISTORS OF VALUES 12Ω AND 8Ω ARE CONNECTED IN PARALLEL WITH A RESISTOR R_3 OF UNKNOWN VALUE ACROSS A $6V$ SUPPLY. WHEN THE CURRENT FROM THE SUPPLY IS FOUND TO BE $2.25A$, CALCULATE (a) THE VALUE OF R_3 AND (b) THE CURRENT FLOWING IN R_3



$$I_3 = 2.25 - (0.5 + 0.75) \\ = 2.25 - 1.25 = 1A$$

$$R_3 = \frac{V}{I_3} = \frac{6}{1} = 6\Omega$$

$$I_1 = \frac{V}{R_1} = \frac{6}{12} = 0.5A$$


$$I_2 = \frac{V}{R_2} = \frac{6}{8} = 0.75A$$

$$I_1 + I_2 + I_3 = I_T = 2.25$$

$$0.5 + 0.75 + I_3 = 2.25$$

Pb (4)

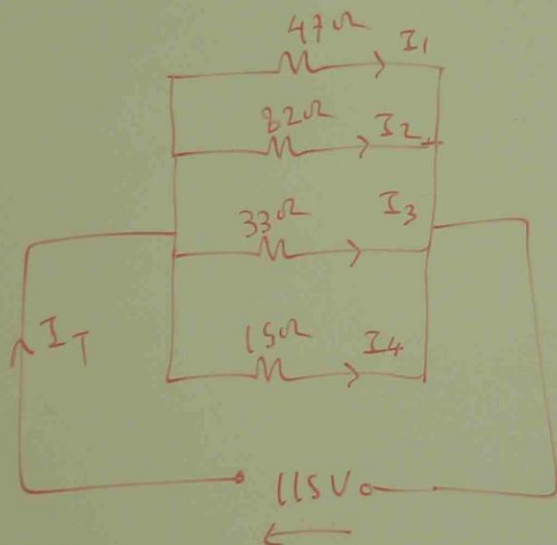FOUR RESISTORS OF INDIVIDUAL VALUES 47Ω , 82Ω , 33Ω AND 15Ω ARE CONNECTED IN PARALLEL WITH EACH OTHER AND CONNECTED TO A $115V$ SUPPLY. CALCULATE THE CURRENT PROVIDED TO THEM BY THE SUPPLY.



$$I_4 = \frac{V}{R_4} = \frac{115}{15} = 7.67 \text{ A}$$

$$I_T = I_1 + I_2 + I_3 + I_4$$

$$= 2.45 + 1.4 + 3.48 + 7.67$$

$$= 15 \text{ A}$$

$$I_1 = \frac{V}{R_1} = \frac{115}{47} = 2.45 \text{ A}$$


$$I_2 = \frac{V}{R_2} = \frac{115}{82} = 1.4 \text{ A}$$

$$I_3 = \frac{V}{R_3} = \frac{115}{33} = 3.48 \text{ A}$$

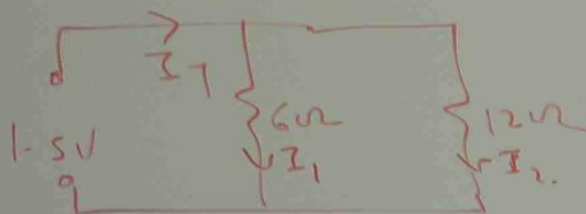EXERCISE

- ① WHEN THE RESISTORS ARE CONNECTED IN PARALLEL
- (a) THEY EACH HAVE THE SUPPLY VOLTAGE CONNECTED DIRECTLY ACROSS THEM
 - (b) THE SUM OF THE VOLTAGE ACROSS EACH RESISTOR WILL SUM TO THE SUPPLY VOLTAGE
 - (c) THERE WILL BE NO VOLTAGE ACROSS THEM

- ② THE EFFECTIVE RESISTANCE OF THE GROUP OF PARALLEL RESISTORS IN GIVEN FIGURE IS




- (a) 18Ω (b) 3Ω
- (c) 4Ω (d) 0.25Ω

- ③ IN ABOVE FIGURE THE CORRECT CURRENTS ARE


- | | | |
|-------------------|----------------|----------------|
| (a) $I_1 = 0.25A$ | $I_2 = 0.125A$ | $I_T = 0.375A$ |
| (b) $I_1 = 0.25A$ | $I_2 = 0.8A$ | $I_T = 0.75A$ |
| (c) $I_1 = 0.25A$ | $I_2 = 0.125A$ | $I_T = 0.125A$ |
| (d) $I_1 = 2.5A$ | $I_2 = 1.25A$ | $I_T = 3.75A$ |

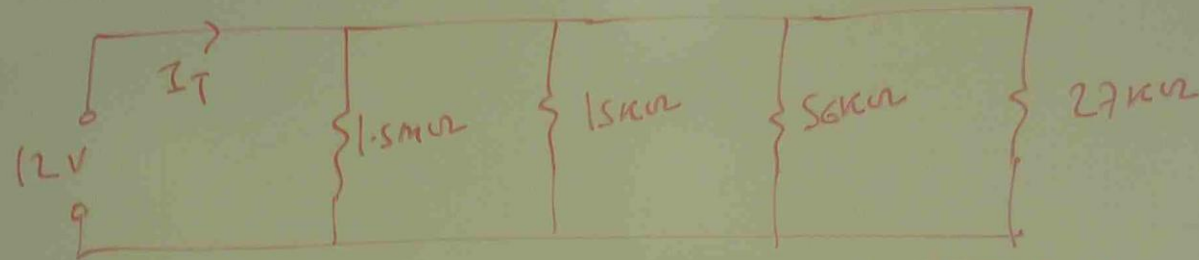- ④ THE SUPPLY CURRENT IN THE FOUR BRANCH RESISTIVE CIRCUIT OF THE DIAGRAM BELOW IS



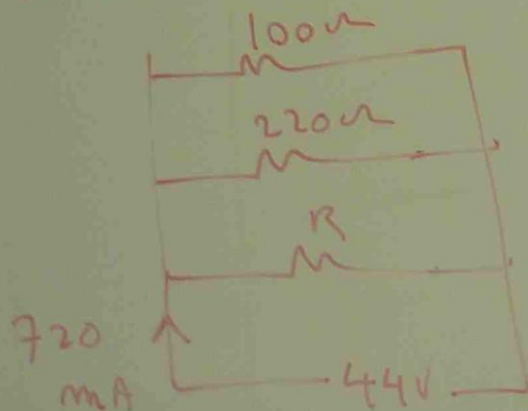- (a) $800\mu A$ (b) $0.8mA$ (c) $14.7mA$ (d) $1.47mA$

- ⑤ THE VALUE OF THE UNKNOWN RESISTOR IN FIGURE BELOW IS



- (a) 320Ω
 (b) 550Ω
 (c) 68.7Ω
 (d) 61.1Ω