
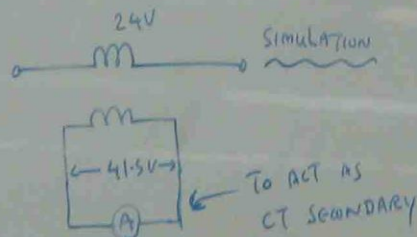


POWER SYSTEM PROTECTION PRACTICAL (2)


CURRENT TRANSFORMER RATIO

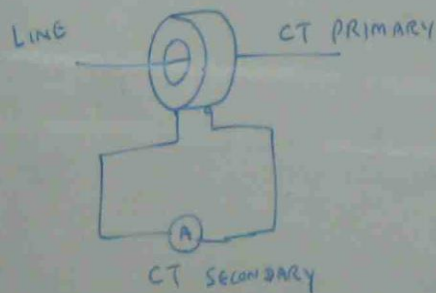

TAKE THE READINGS & FILL IN THE TABLE

		CT RATIO	
V_1	V_2	$I_1 = \frac{V_2}{10\Omega}$	$\frac{I_1}{I_2} = a$
4V			$a_1 =$
5V			$a_2 =$
6V			$a_3 =$
7V			$a_4 =$

CONNECT THE GIVEN CIRCUIT

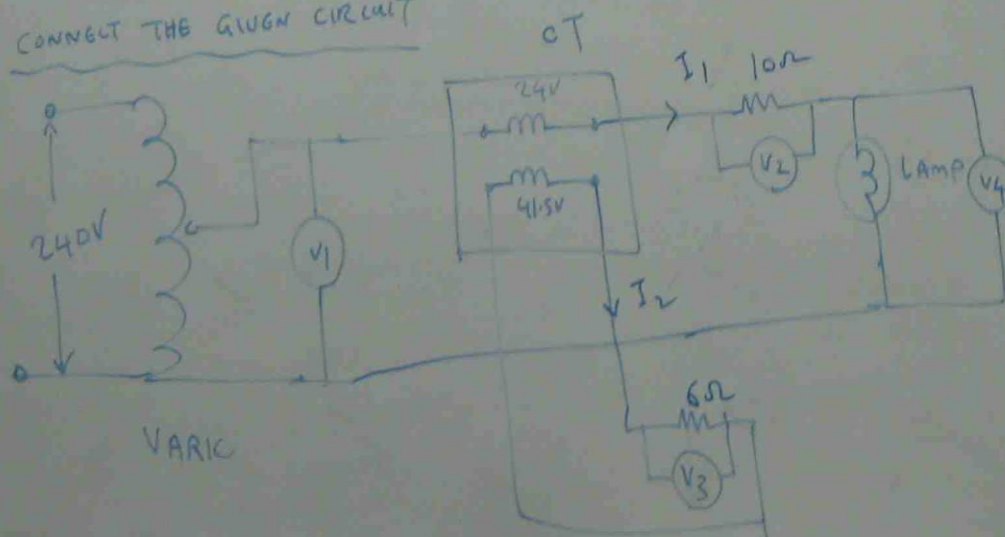

$$\text{AVERAGE CT RATIO} = \frac{a_1 + a_2 + a_3 + a_4}{4}$$

CT RATIO

$$\frac{I_1}{I_2} = a$$

$$a_1 =$$

$$a_2 =$$

$$a_3 =$$

$$a_4 =$$



THEN ADJUST

$$V_3 = 0.3 \text{ V (OR)} I_2 = \frac{0.3}{6} = 0.05 \text{ A}$$

USE CT RATIO AND CALCULATE

PRIMARY CURRENT I_1


$$I_1 = \text{AVERAGE CT RATIO} \times 0.5 \text{ AMP}$$

=

THEN MEASURE V_2 AND FIND

$$I_1 = \frac{V_2}{10 \Omega}$$

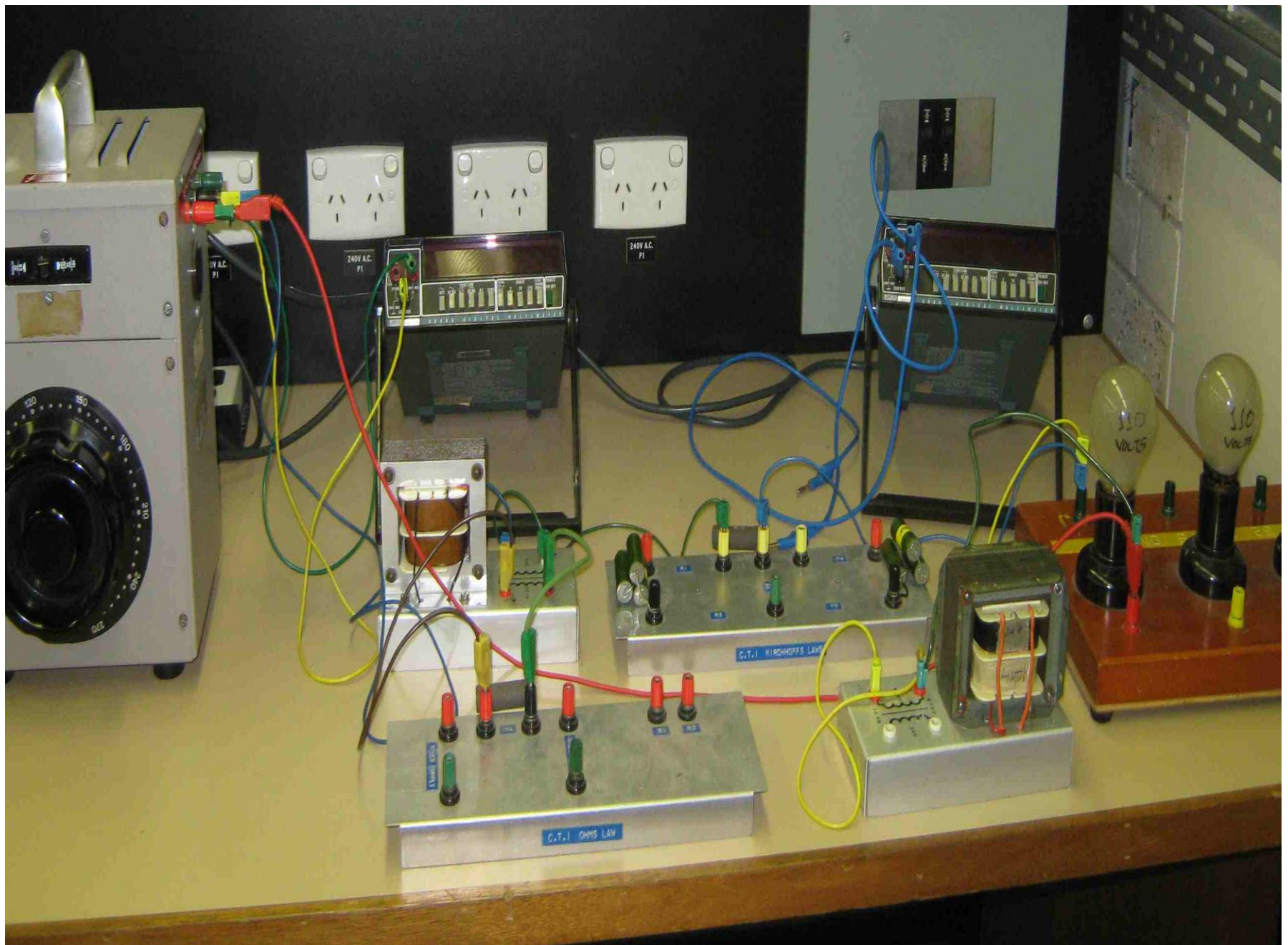COMPARE CALCULATED RESULT AND MEASURED RESULT.





PROTECTIVE TRANSFORMERS

CT - CURRENT TRANSFORMER } PROTECTIVE TRANSFORMER
PT - POTENTIAL TRANSFORMER }



PROTECTIVE TRANSFORMERS ARE UTILIZED TO REDUCE THE SYSTEM
LEVEL HIGH VOLTAGE AND CURRENT TO RELAY LEVEL / INSTRUMENT
LEVEL LOW VOLTAGE AND CURRENT.

CONNECTION (PT)

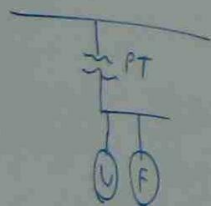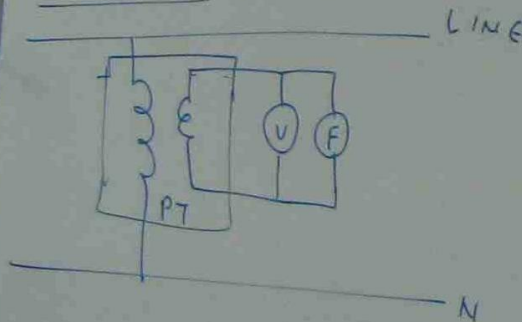



PT REDUCES HIGH
VOLTAGE TO LOW VOLTAGE

LT CONNECTION

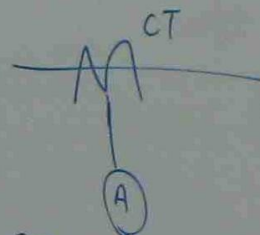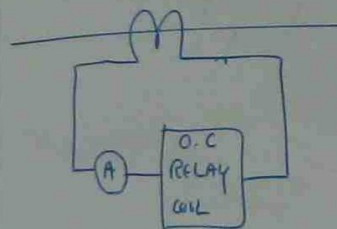

CT - REDUCES HIGH CURRENT
TO LOW CURRENT

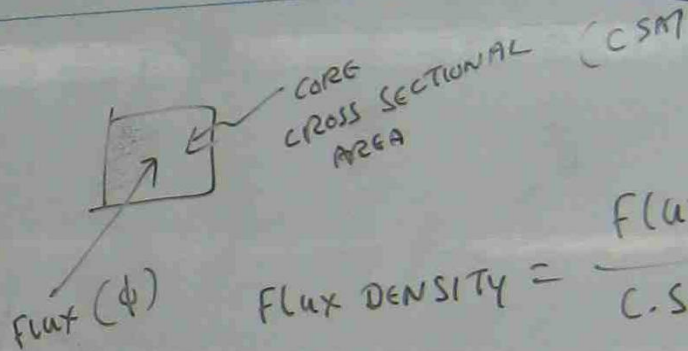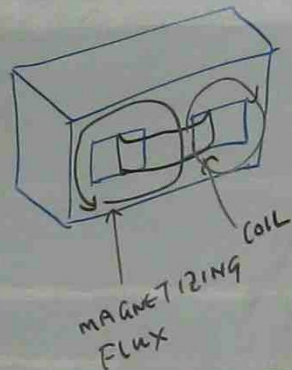DIFFERENCE BETWEEN POWER TRANSFORMER & INSTRUMENT TRANSFORMER



$$\text{FLUX DENSITY} = \frac{\text{FLUX}}{\text{C.S.A}} \quad (\text{wb})$$

IN POWER TRANSFORMER, CORE FLUX DENSITY IS CONSTANT REGARDLESS OF THE LOAD.

BUT IN CURRENT TRANSFORMER, CORE FLUX DENSITY DEPENDS ON

- (1) MAGNITUDE OF PRIMARY CURRENT
- (2) IMPEDANCE OF SECONDARY CIRCUIT.

$$\frac{V_1}{V_2} = \frac{I_2}{I_1} = \frac{N_1}{N_2}$$