

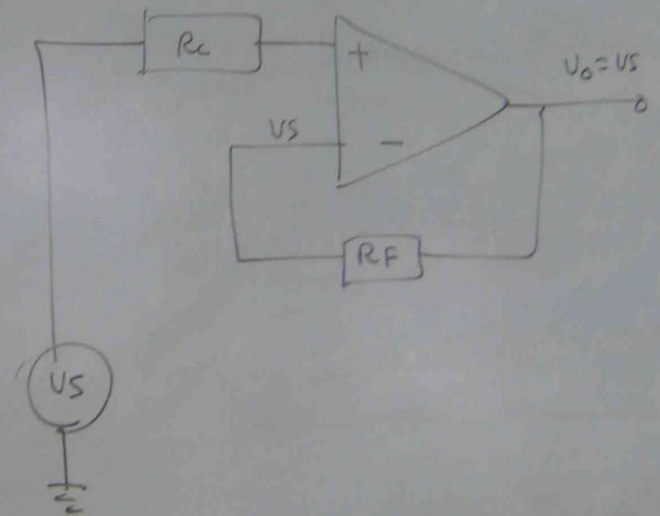
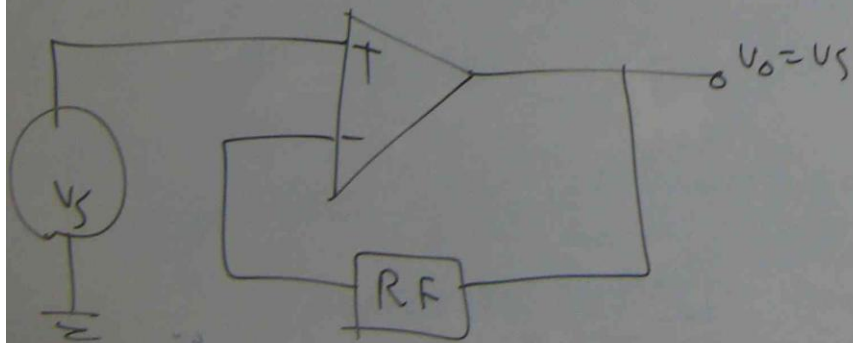


ANALOGUE AMPLIFIER CONFIGURATION


VOLTAGE FOLLOWER

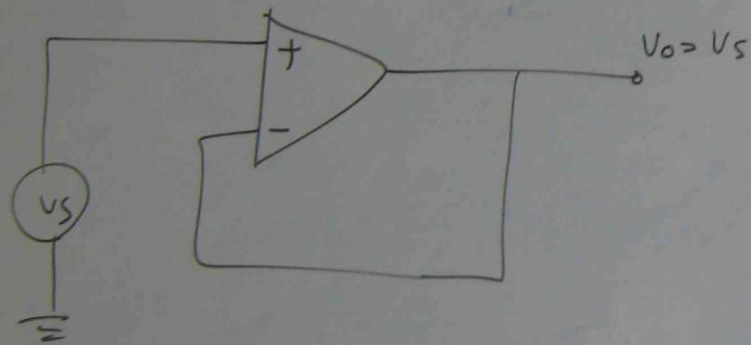

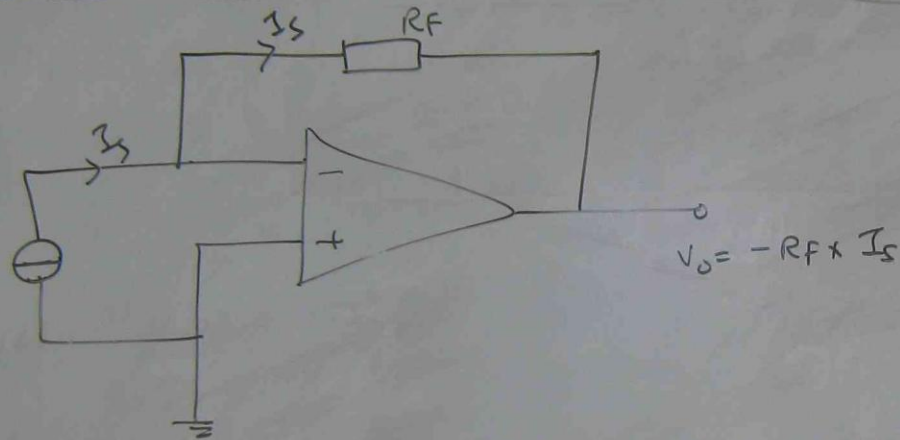CURRENT TO VOLTAGE CONVERTER (TRANSIMPEDANCE AMPLIFIER)




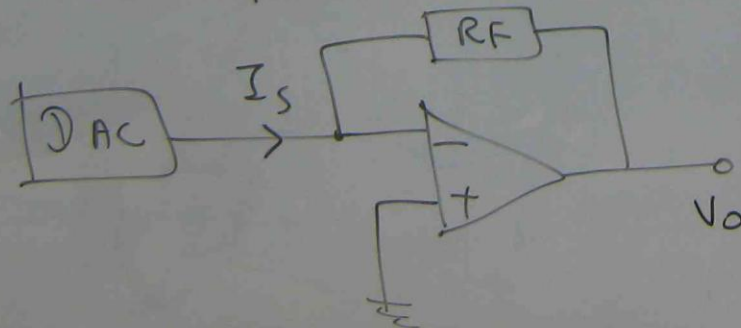Pb IN THE FOLLOWING CIRCUIT, THE D TO A CONVERTER GIVES AN OUT PUT CURRENT IN THE RANGE 0 TO 1.992 mA. SELECT R_F TO GIVE OUT PUT VOLTAGE RANGE 0 TO 5V



$$R_F = \frac{V_o}{I_s} = \frac{5}{1.992 \times 10^{-3}} = 2.51 \text{ k}\Omega$$

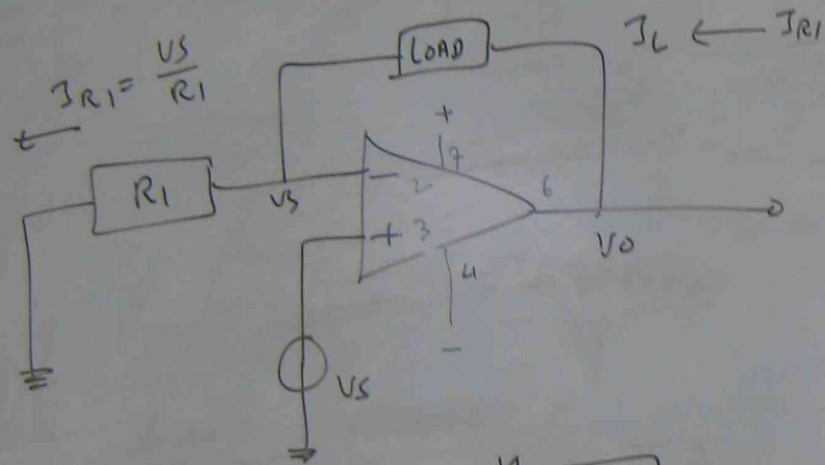
VOLTAGE TO CURRENT CONVERTER (TRANS CONDUCTANCE AMPLIFIER)



(a) DIODE IS FORWARD BIASED

(b) DIODE CURRENT = $\frac{5V}{470\Omega} = 10.63 \text{ mA}$

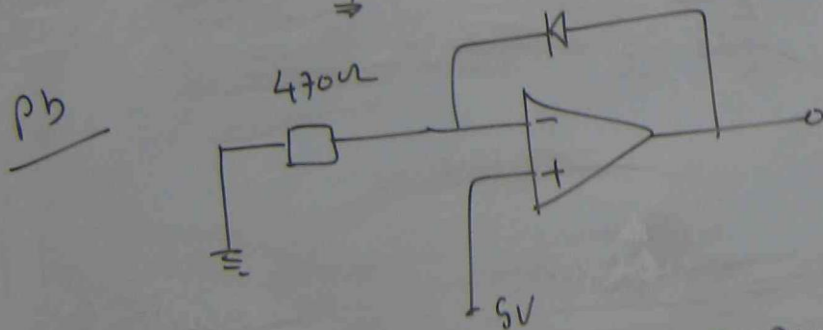(c) OUTPUT VOLTAGE = $5V + \text{DIODE DROP}$
 $= 5 + 650 \times 10^{-3}$
 $= 5.65 V$





(a) IS THE DIODE FORWARD BIAS OR REVERSE BIASED

(b) CALCULATE DIODE CURRENT

(c) CALCULATE OUTPUT VOLTAGE IF DIODE DROP IS 650mV

POWER SUPPLY CONNECTION FOR OP AMPS

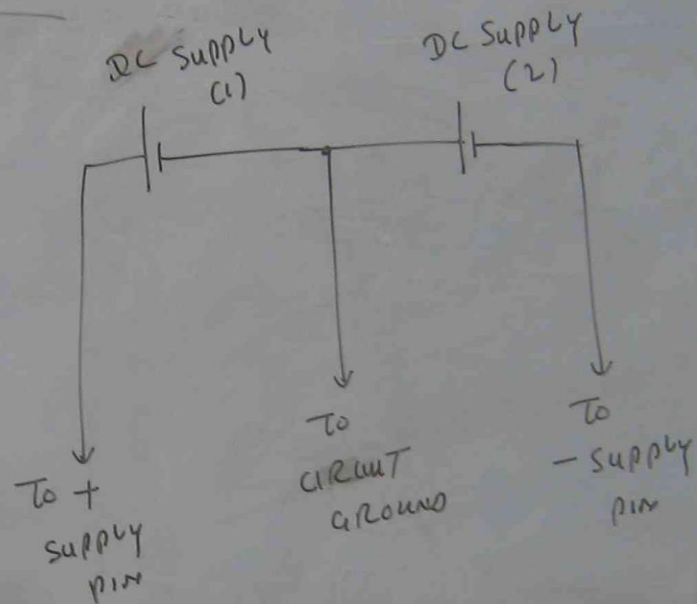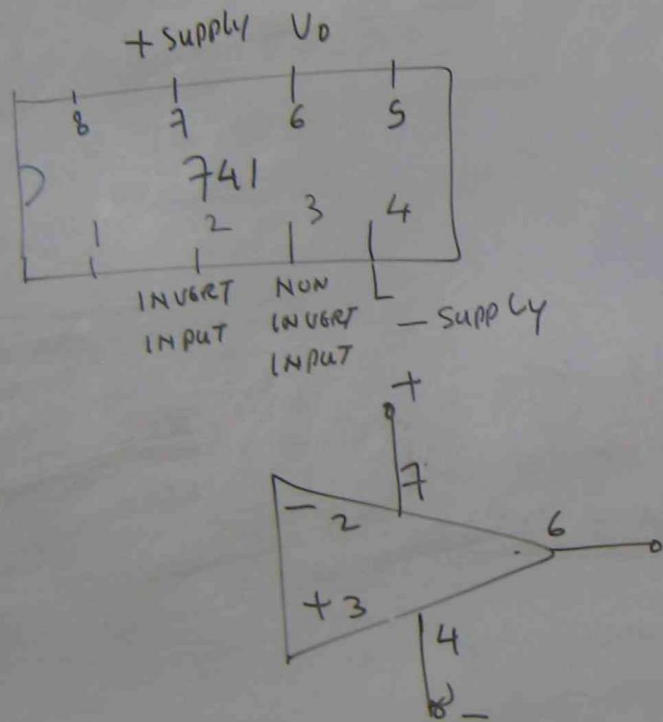

SUMMARY

THE IDEAL OP-AMP HAS INFINITE GAIN, INFINITE INPUT RESISTANCE AND ZERO OUTPUT RESISTANCE.


IN INVERTING AMPLIFIER, THE INPUT SIGNAL IS CONNECTED TO - INPUT.

IN VOLTAGE FOLLOWER, THE SIGNAL IS CONNECTED TO + INPUT.

INPUT OFFSET VOLTAGE

INPUT OFFSET VOLTAGE (V_{io})

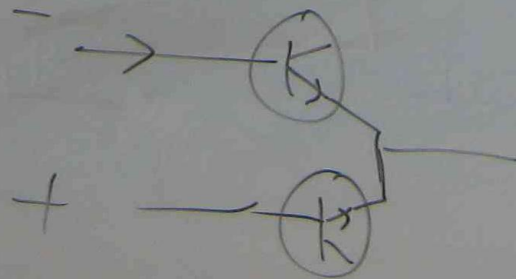IF WE CONNECT AN OP-AMP AS A VOLTAGE FOLLOWER AND GROUND THE INPUT, WE WOULD EXPECT ZERO OUTPUT VOLTAGE. BUT PRACTICALLY THERE WOULD BE A SMALL DC OUTPUT VOLTAGE. THIS IS CALLED INPUT OFFSET VOLTAGE.




THE DC OUTPUT VOLTAGE
DUE TO INPUT OFFSET
VOLTAGE

$$= V_{io} \left(1 + \frac{R_F}{R_1} \right)$$

V_{io} = INPUT OFFSET VOLTAGE


R_F = NEGATIVE FEED BACK
RESISTOR

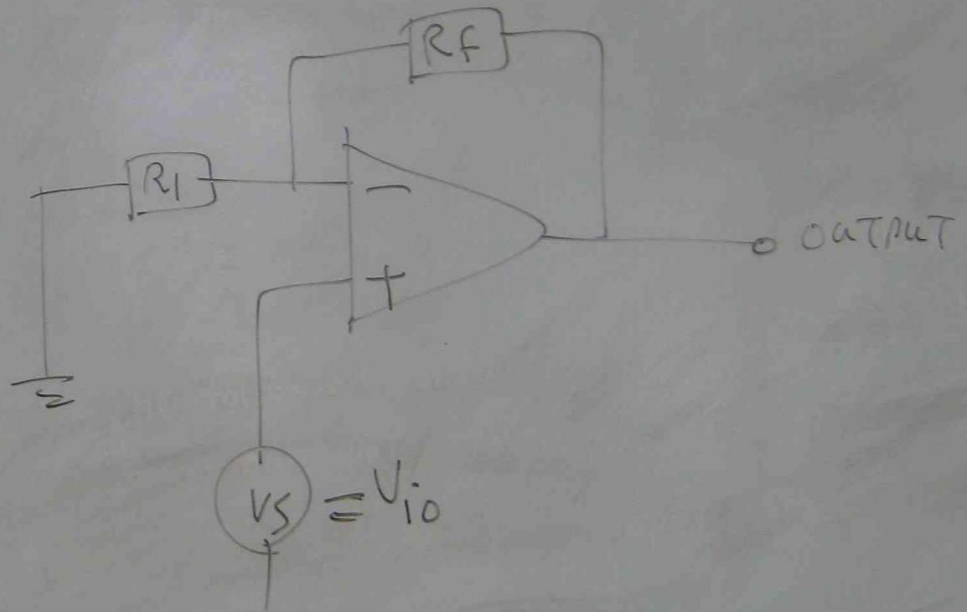
R_1 = TOTAL RESISTANCE
FROM INVERTING INPUT
TO GROUND.



REDUCING THE EFFECT OF INPUT OFF SET VOLTAGE

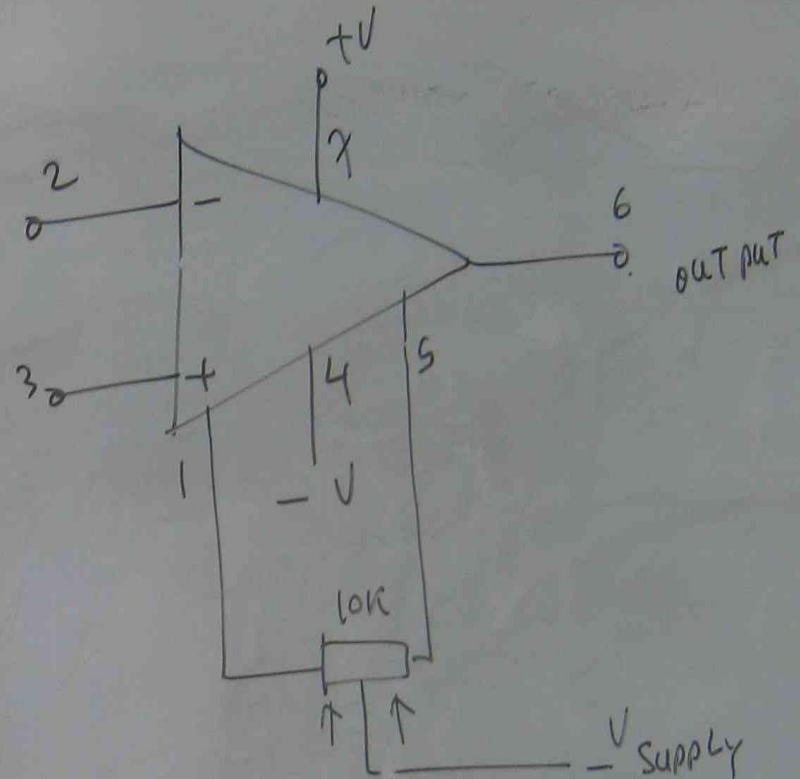- CHOOSE HIGH QUALITY
O-P-AMP WITH LOW V_{io}
- WORK WITH AC SIGNAL
RATHER THAN DC
- USE OFFSET NULLING
CIRCUIT.



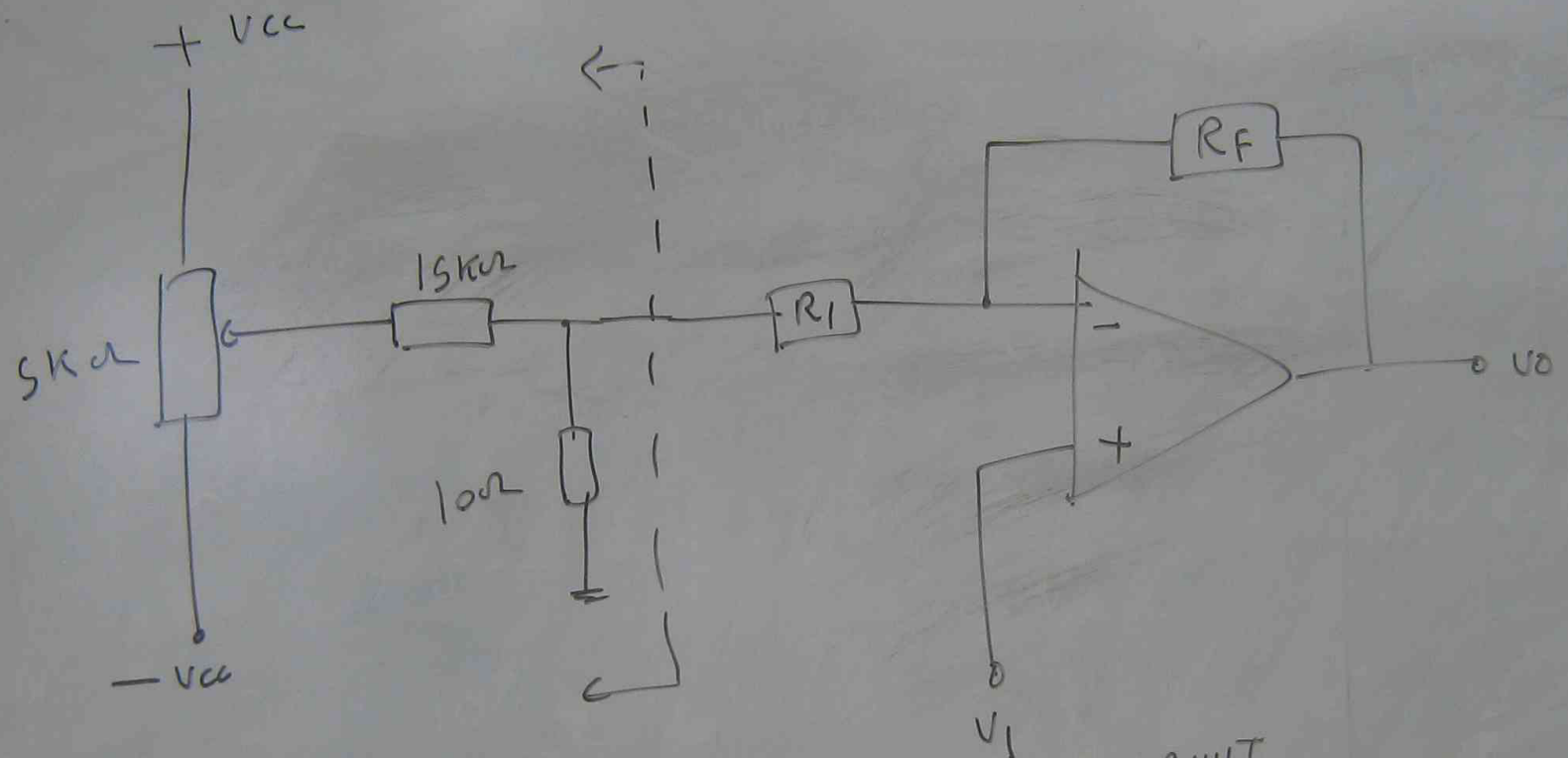

UNIVERSAL OFFSET NULLING CIRCUIT

BIAS CURRENT COMPENSATION

