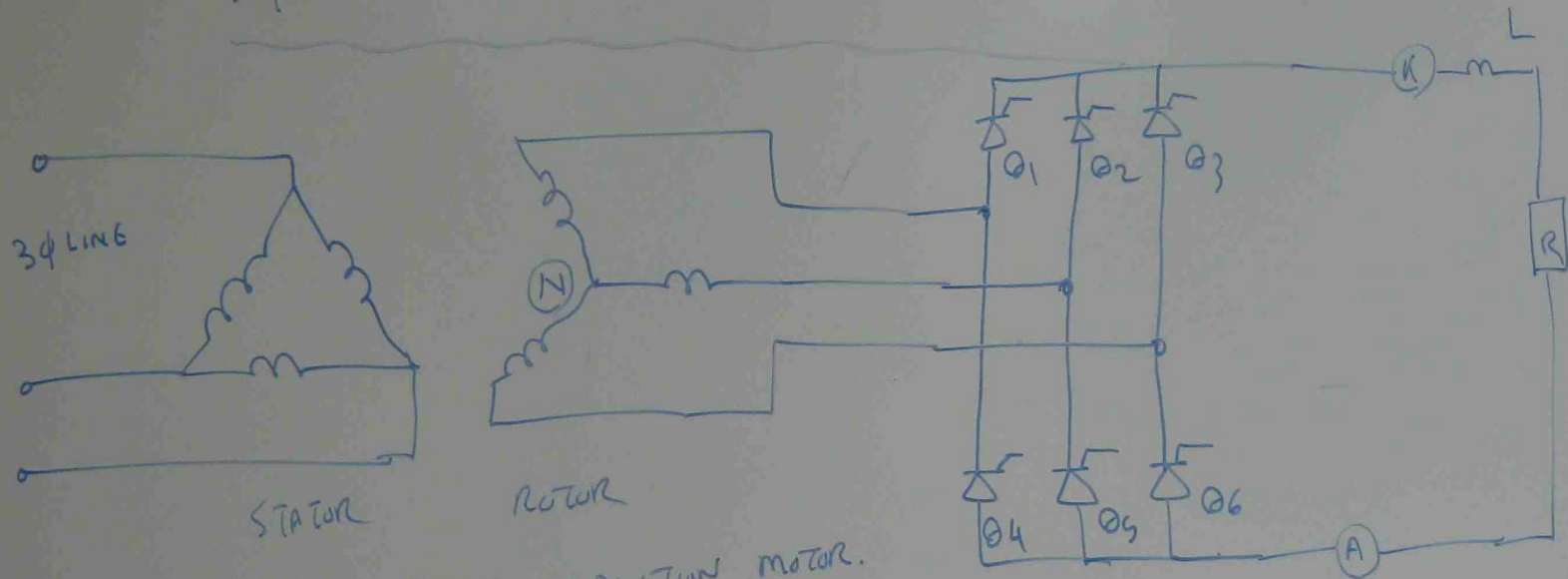


3 ϕ SCR CONNECTION FOR VARIABLE DRIVE SYSTEM



3 ϕ wound rotor induction motor.

By adjusting the thyristor firing angle, the rotor current & flux can be changed and motor speed can be changed.

(3 ϕ 6 pulse converter)

$$E_d = 1.35 E \cos \alpha$$

E_d = DC VOLTAGE PRODUCED BY 3 ϕ 6 PULSE CONVERTER

E = EFFECTIVE VALUE OF AC LINE TO LINE VOLTAGE (V)

α = FIRING ANGLE

$$P_i = 1.35 V_{rms} I_D \cos \phi$$

$$S_i = \sqrt{3} V_{rms} \times 0.78 I_D$$


$$I_{rms} = \frac{\sqrt{3} \times \sqrt{2} I_D}{\pi}$$

$$= 0.78 I_D$$

$$1.35 V_{rms} I_D$$

I_D = DC CURRENT.

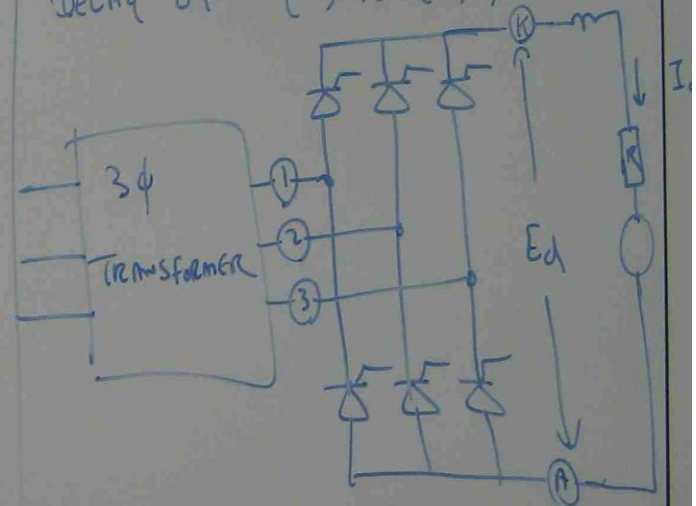ph THE following 3 ϕ CONVERTER IS CONNECTED TO 3 ϕ 480V 60HZ SOURCE. THE LOAD CONSISTS OF A 500V DC SOURCE HAVING AN INTERNAL RESISTANCE 2 Ω . CALCULATE THE POWER SUPPLIED TO THE LOAD FOR TRIGGERING DELAY OF (a) 15 (b) 75



$$E_d = 1.35 E \cos \alpha$$

$$\alpha = 15^\circ, E = 480$$

$$\begin{aligned} E_d &= 1.35 \times 480 \cos 15 \\ &= 1.35 \times 480 \times 0.9659 \\ &= 625.9 \text{ V} \end{aligned}$$

$$I_D = \frac{E_d}{R} = \frac{625.9}{2} = 312.95 \text{ Amp.}$$

$$\begin{aligned} S_1 &= \sqrt{3} V_{\text{rms}} \times 0.78 I_D \\ &= 1.7321 \times 480 \times 0.78 \times 312.95 \\ &= 202947 \text{ VA} \\ &= 202.947 \text{ KVA} \end{aligned}$$

$$\alpha = 75^\circ$$

$$\begin{aligned} E_d &= 1.35 \times 480 \times \cos 75 \\ &= 167.71 \text{ V} \end{aligned}$$


$$I_D = \frac{E_d}{R} = \frac{167.71}{2} = 83.85 \text{ Amp}$$

$$\begin{aligned} S_1 &= \sqrt{3} V_{\text{rms}} \times 0.78 I_D \\ &= 1.7321 \times 480 \times 0.78 \times 83.85 \\ &= 54381 \text{ VA} \\ &= 54.38 \text{ KVA} \end{aligned}$$


$$W = \frac{2\pi TN}{60} \Rightarrow N = \frac{W \times 60}{2\pi T}$$

$$N = \text{speed}, T = \text{torque}, W = \text{power}$$

CONCEPTS OF DELAYED FIRING ANGLE

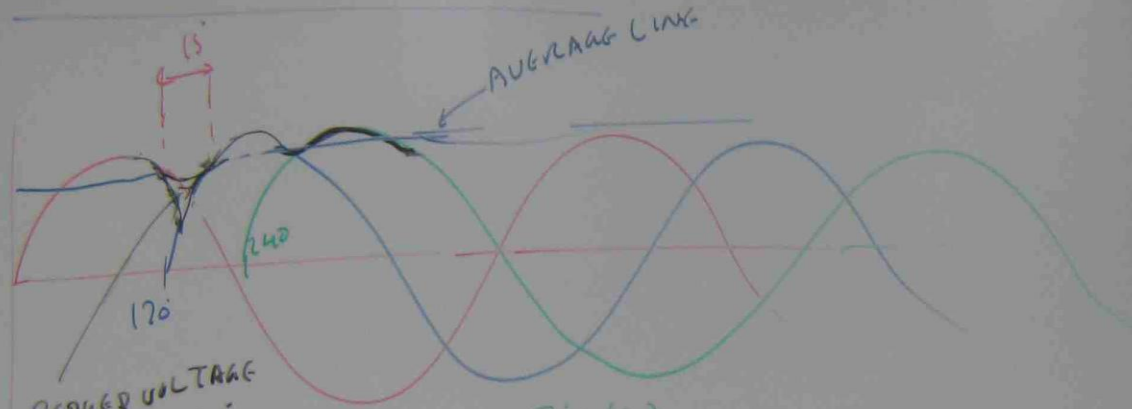

Fig(a)

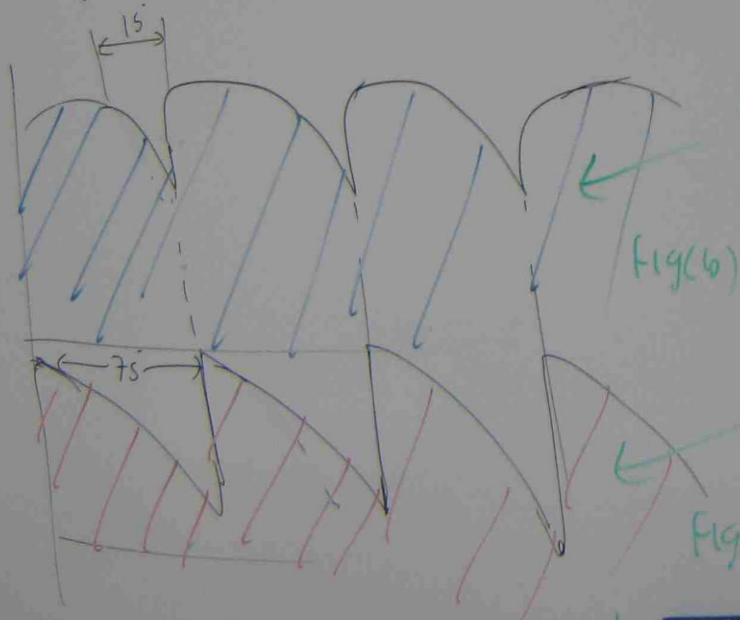

TOTAL POWER TRANSFER AT $\alpha = 15^\circ$

Fig(b)

TOTAL POWER TRANSFER AT

Fig(c) $\alpha 75^\circ$

IN THE DIAGRAM, WHEN FIRING ANGLE IS ZERO, THE OUT PUT VOLTAGE IS THE VOLTAGE PRODUCED BY 3 ϕ RECTIFIER BRIDGE.

WHEN FIRING ANGLE IS 15° , THE OUT PUT VOLTAGE IS IN FIG(b)

WHEN THE FIRING ANGLE IS 75° , THE OUT PUT VOLTAGE IS IN FIG(c)

BY INCREASING THE VALUE OF FIRING ANGLE, THE OUT PUT VOLTAGE AND POWER CAN BE VARIED.

TRIACER INA MODE

DELAY TRIACER INA MODE

TRIACERINA RANGE


1S \longrightarrow 1GS

CONVERTER

1S \longrightarrow 90

INVERTER


90 \longrightarrow 1GS

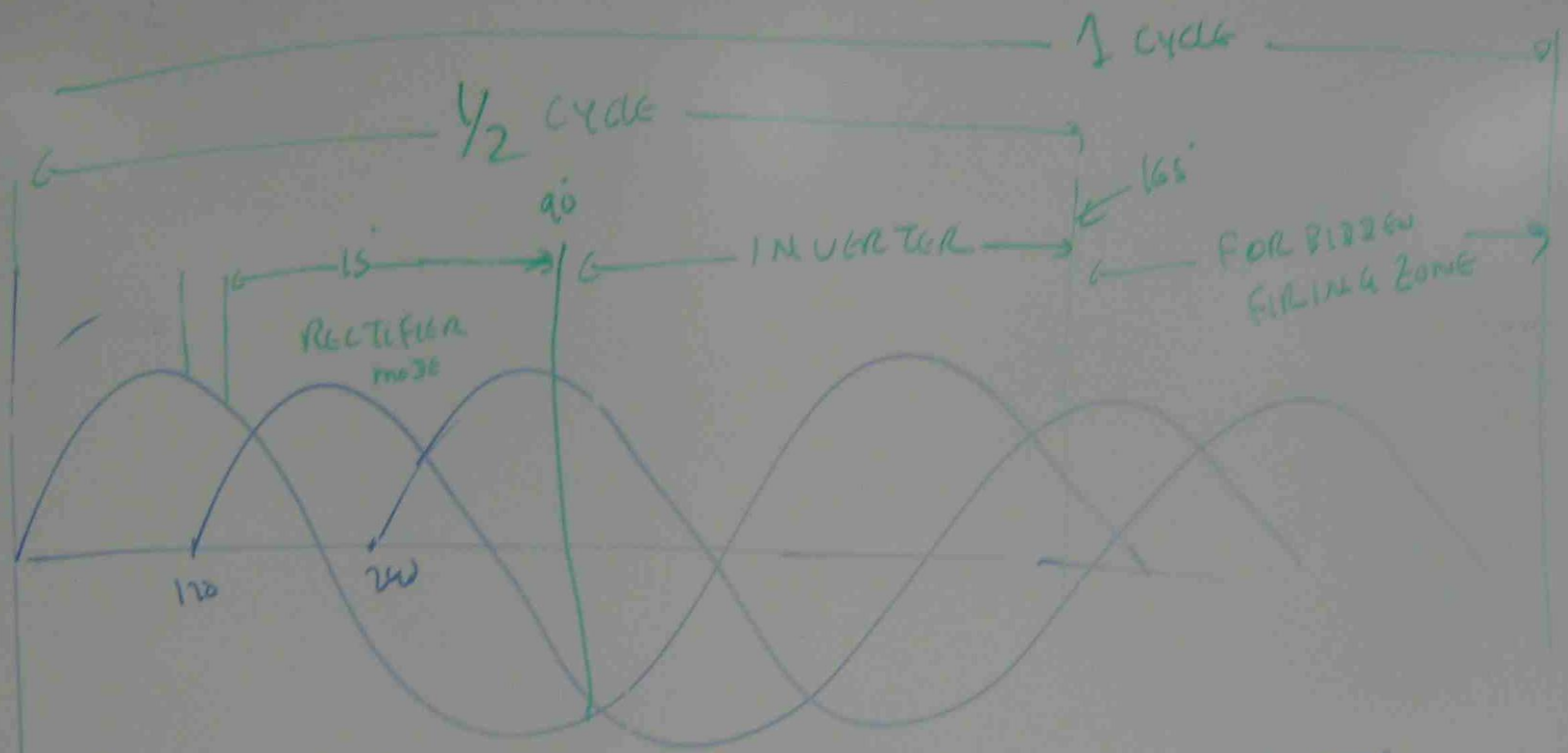

IF THE TRIGGERING IS DELAYED BY MORE THAN α_0 , THE VOLTAGE DEVELOPED BY CONVERTER BECOMES NEGATIVE.

AND THE SYSTEM OPERATES AS INVERTER MODE CHANGING DC POWER TO AC.

COMMUTATION OVER LAP

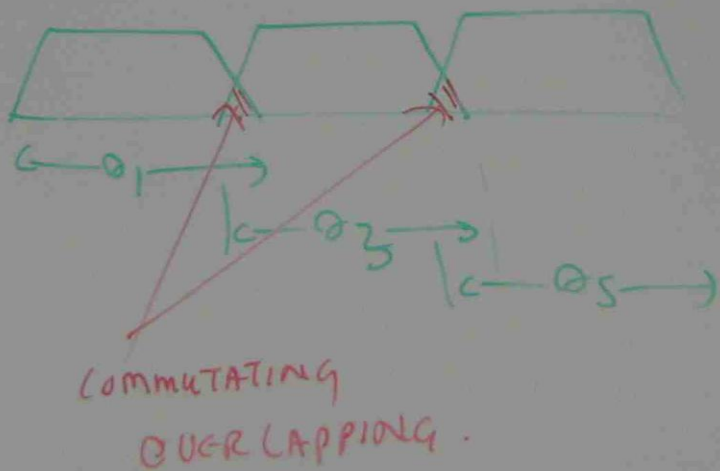

EXTINCTION ANGLE

ADVANCED ANGLE $\rightarrow \beta = 180 - \alpha$

EXTINCTION ANGLE $\gamma = \beta - \mu$


CONSTANT
 $\gamma = 15 \rightarrow 20^\circ$

PROPERTIES OF SOME RECTIFIER CONVERTERS RESISTIVE LOAD

ITEM	CONVERTER (A)	CONVERTER (B)	CONVERTER (C)
	3 ϕ 6 PULSE	3 ϕ 6 PULSE + FREE WHEEL DIODE	HALF BRIDGE
FIRING ANGLE LIMIT (α)	$0 \rightarrow 90$	$60 \rightarrow 120$	$60 \rightarrow 180$
DC OUTPUT VOLTAGE	$1.35 E \cos \alpha$	$1.35 E (1 - \cos(120 - \alpha))$	$0.695 E (1 + \cos \alpha)$
DISPLACEMENT ANGLE ϕ_d	α	$30 + \frac{\alpha}{2}$	$\frac{\alpha}{2}$
POWER FACTOR	$\cos \alpha$	$\cos(30 + \frac{\alpha}{2})$	$\cos \frac{\alpha}{2}$
EFFECTIVE LINE CURRENT	$0.816 I_d$	$I_d \sqrt{(120 - \alpha)/90}$	$I_d \sqrt{(180 - \alpha)/180}$
TOTAL APPARENT POWER	$E I \sqrt{3}$	$E I \sqrt{3}$	$E I \sqrt{3}$

	CONVERTER (A)	CONVERTER (B)	CONVERTER (C)
ITCM	3PH 6 pulse	3 ϕ 6 pulse + FREE WHEEL DIODE	HALF BRIDGE
TOTAL ACTIVE POWER	$E_d I_d$	$E_d I_d$	$E_d I_d$
TOTAL REACTIVE POWER	$P \tan \phi_d$	$P \tan \phi_d$	$P \tan \phi_d$
PF (TOTAL)	P/S	P/S	P/S
PF (DISTORTION)	$\frac{P}{S} \cos \phi_d$	$\frac{P}{S} \cos \phi_d$	$\frac{P}{S} \cos \phi_d$

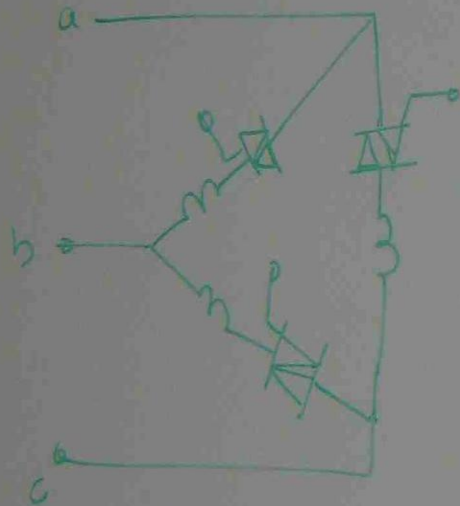
VARIABLE VOLTAGE - SPEED CONTROL OF SCHEIBERLE CAGE INDUCTION MOTOR




METHOD (1)




METHOD (2)

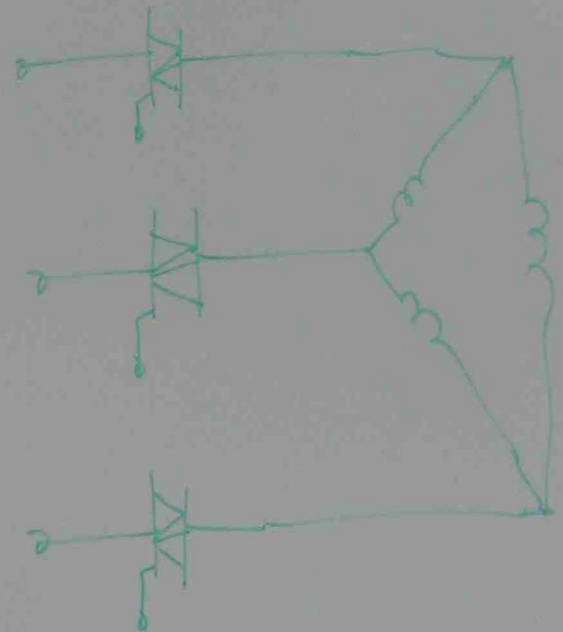


METHOD (3)

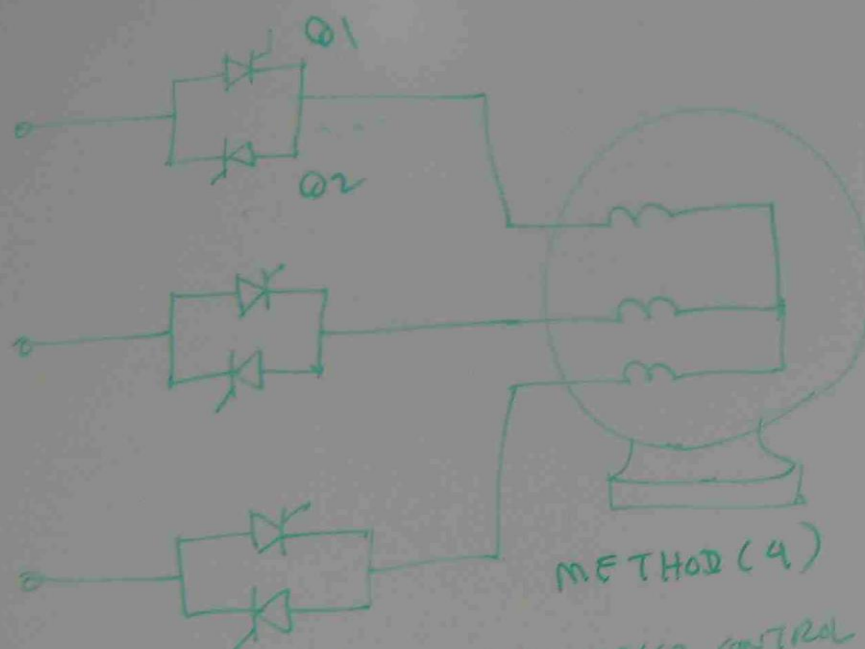

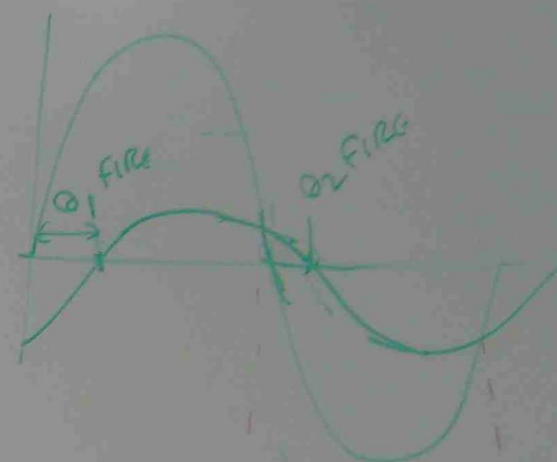VARIABLE VOLTAGE SPEED CONTROL OF
A SQUIRREL CAGE INDUCTION MOTOR.



WAVE SHAPES
OF FIRED VALUE

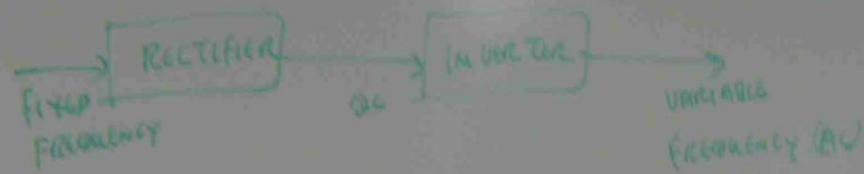

VVI - VARIABLE VOLTAGE INVERTER

VVI TAKES INPUT POWER IN THE FORM OF ADJUSTABLE DC SOURCE. THE SOURCE PROVIDES THE INPUT DC VOLTAGE TO PROVIDE THE REQUIRED OUTPUT VOLTAGE AMPLITUDE.

CSI - CURRENT SOURCE INVERTER

CSI TAKES INPUT POWER FOR ADJUSTABLE CURRENT SOURCE.

PWM - PULSE WIDTH MODULATED INVERTER TAKES THE VOLTAGE FROM

FIXED VOLTAGE SOURCE. THE OUTPUT VOLTAGE WAVE-FORM IS CONTROLLED BY CHANGING WIDTH OF VOLTAGE INTERVALS.