
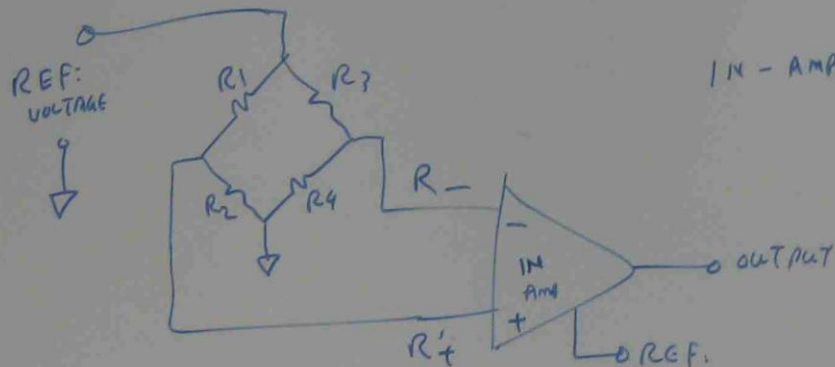


INSTRUMENTATION AMPLIFIER

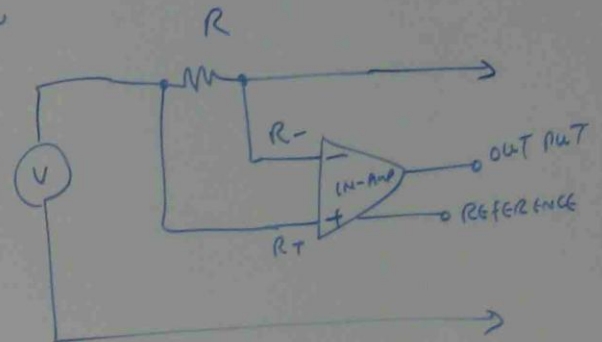


IN-AMP = INSTRUMENTATION AMPLIFIER

IN LINE CURRENT MEASUREMENT



AN INSTRUMENTATION AMPLIFIER IS A CLOSED LOOP GAIN BLOCK THAT HAS A DIFFERENTIAL INPUT THAT IS SINGLE ENDED WITH RESPECT TO REFERENCE TERMINAL.

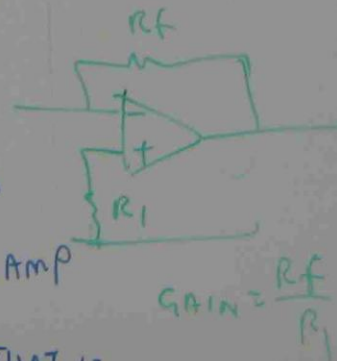UNLIKE AN OP-AMP WHICH HAS IT'S CLOSED LOOP GAIN DETERMINED BY EXTERNAL RESISTORS, AN IN-AMP EMPLOYS AN INTERNAL FEEDBACK RESISTOR NETWORK THAT IS ISOLATED FROM SIGNAL INPUT TERMINAL.



$$\text{GAIN} = \frac{R_f}{R_1}$$

PROPERTIES OF INSTRUMENTATION AMPLIFIER


- HIGH AC AND DC COMMON MODE REJECTION RATIO
- LOW OFFSET VOLTAGE AND OFFSET VOLTAGE DRIFT $1 \mu V/C \rightarrow 10 \mu V/C$
- A MATCHED HIGH INPUT IMPEDANCE $10^9 \Omega \rightarrow 10^{12} \Omega$
- LOW INPUT BIAS AND OFFSET CURRENT ERRORS $\left\{ \begin{array}{l} \text{BI-POLAR} \\ \text{FET} \end{array} \right. \quad \begin{array}{l} 1 \text{ mA} \rightarrow 50 \text{ nA} \\ 1 \text{ pA} \rightarrow 50 \text{ pA} \end{array}$
- LOW NOISE $10 \text{ mV}/\sqrt{\text{Hz}} @ 1 \text{ kHz}$
- LOW NON LINEARITY
- SIMPLE GAIN SELECTION
- ADEQUATE BAND WIDTH $500 \text{ kHz} \rightarrow 4 \text{ MHz}$

APPLICATION

MEDICAL INSTRUMENTATION
MONITOR AND CONTROL ELECTRONICS
SOFTWARE PROGRAMMABLE APPLICATIONS
AUDIO APPLICATIONS.
HIGH SPEED SIGNAL CONDITIONING


VIDEO APPLICATIONS
POWER CONTROL APPLICATIONS.

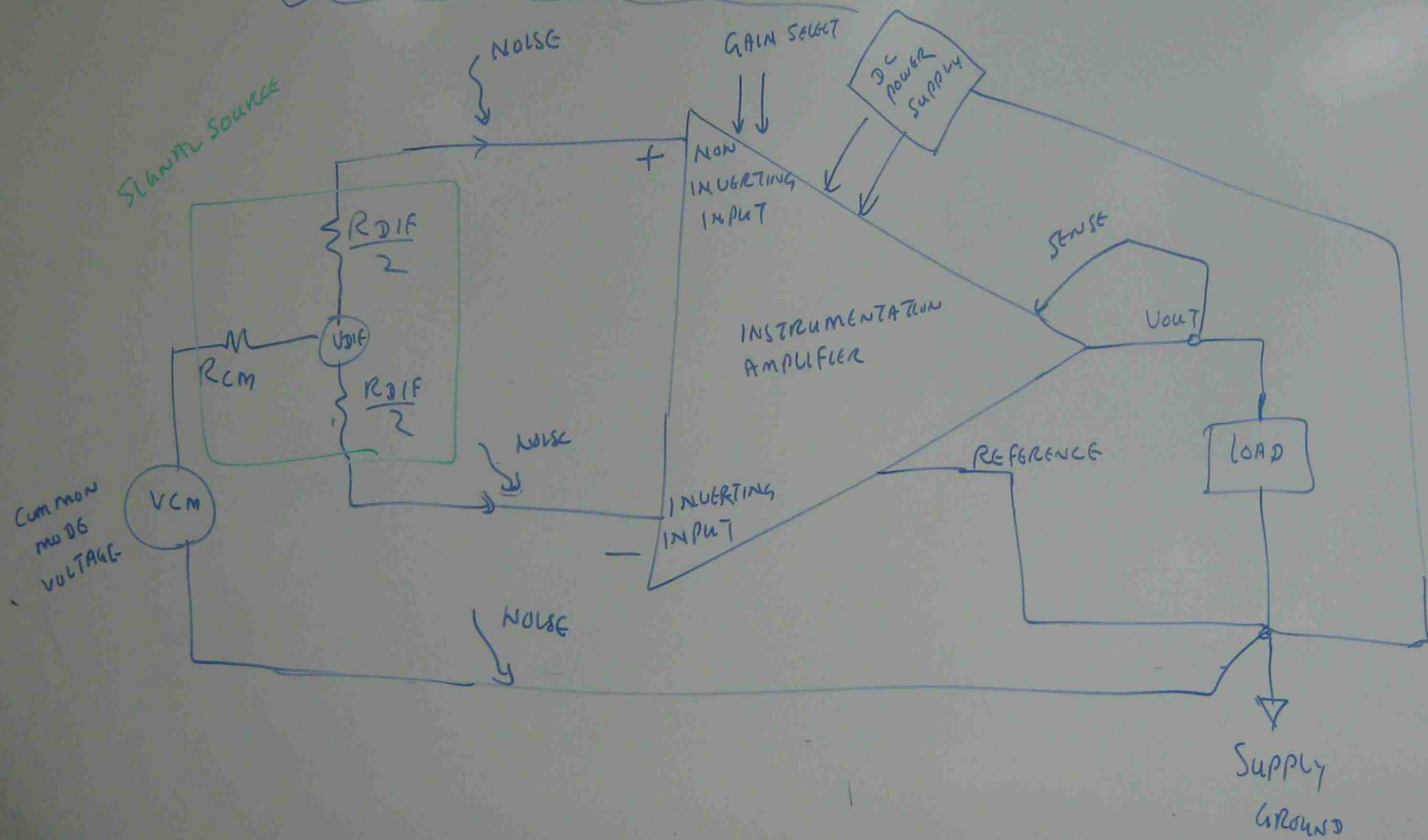EXTERNAL VIEW OF INSTRUMENTATION AMPLIFIER





INSIDE VIEW OF INSTRUMENTATION AMPLIFIER

$A_1 = \text{AD705, OP97}$

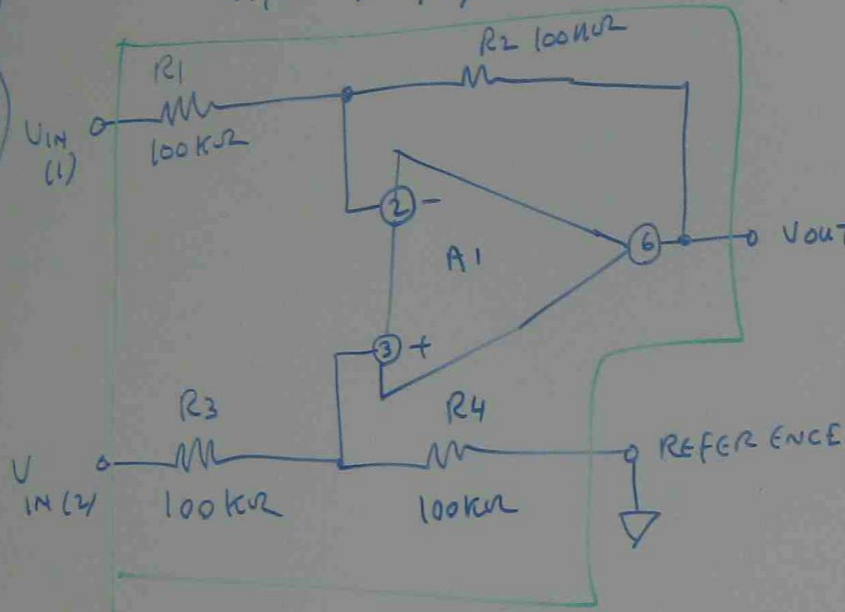
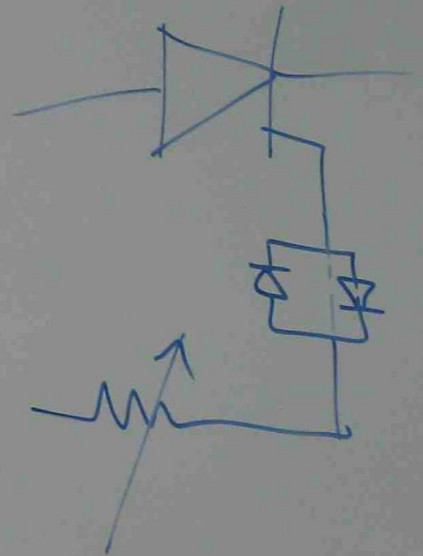
$$V_{OUT} = (V_{IN2} - V_{IN1}) \times \frac{R_2}{R_1}$$



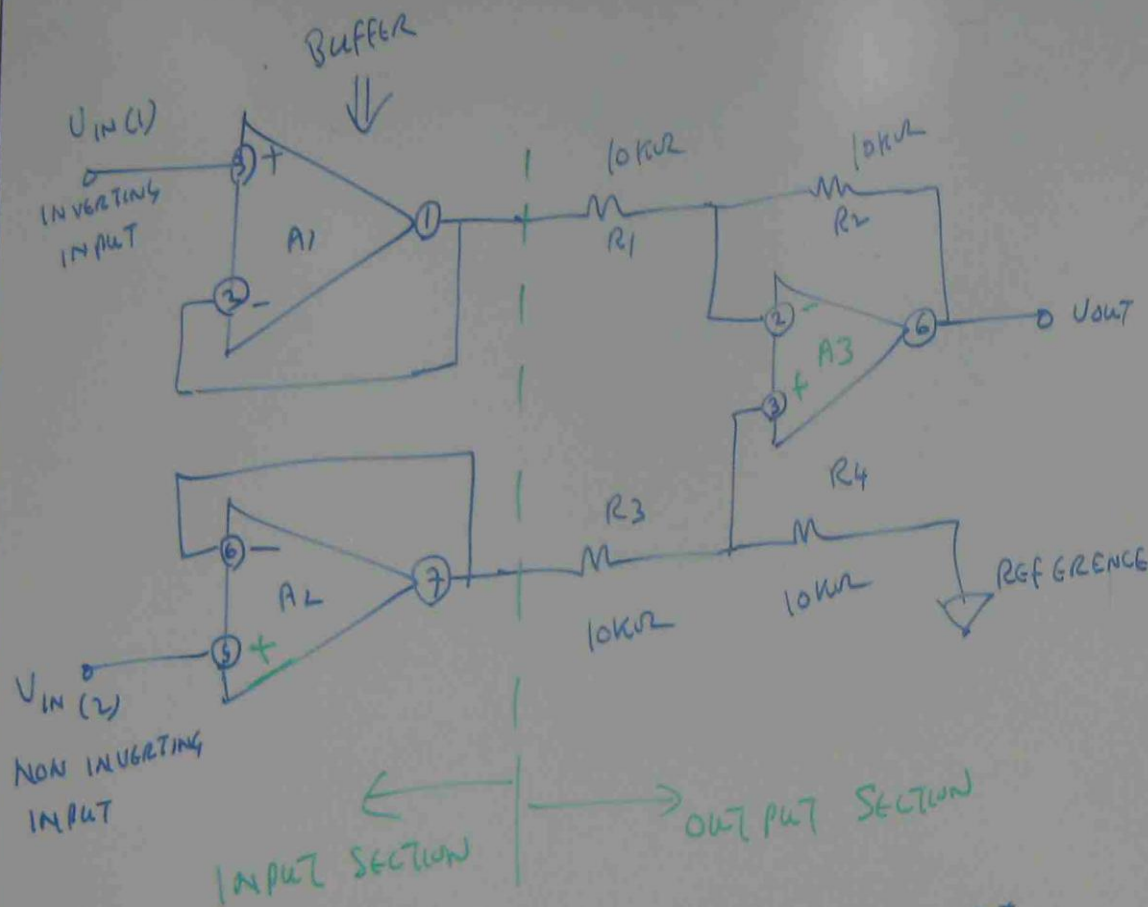

$$V_{OUT} = (V_{IN(1)} - V_{IN(2)}) \frac{R_2}{R_1}$$

for $R_1 = R_3$
 $R_2 = R_4$


A_1 & $A_2 \rightarrow$ AD706, OP247

$A_3 \rightarrow$ AD709, OP97

SUBTRACTOR CIRCUIT WITH INPUT
 BUFFERING



$$\begin{array}{l} V_1 - V_2 \\ V_1 - 10V_2 \quad \dots \quad 10V_3 - 5V_2 \\ 10V_1 - V_2 \end{array}$$

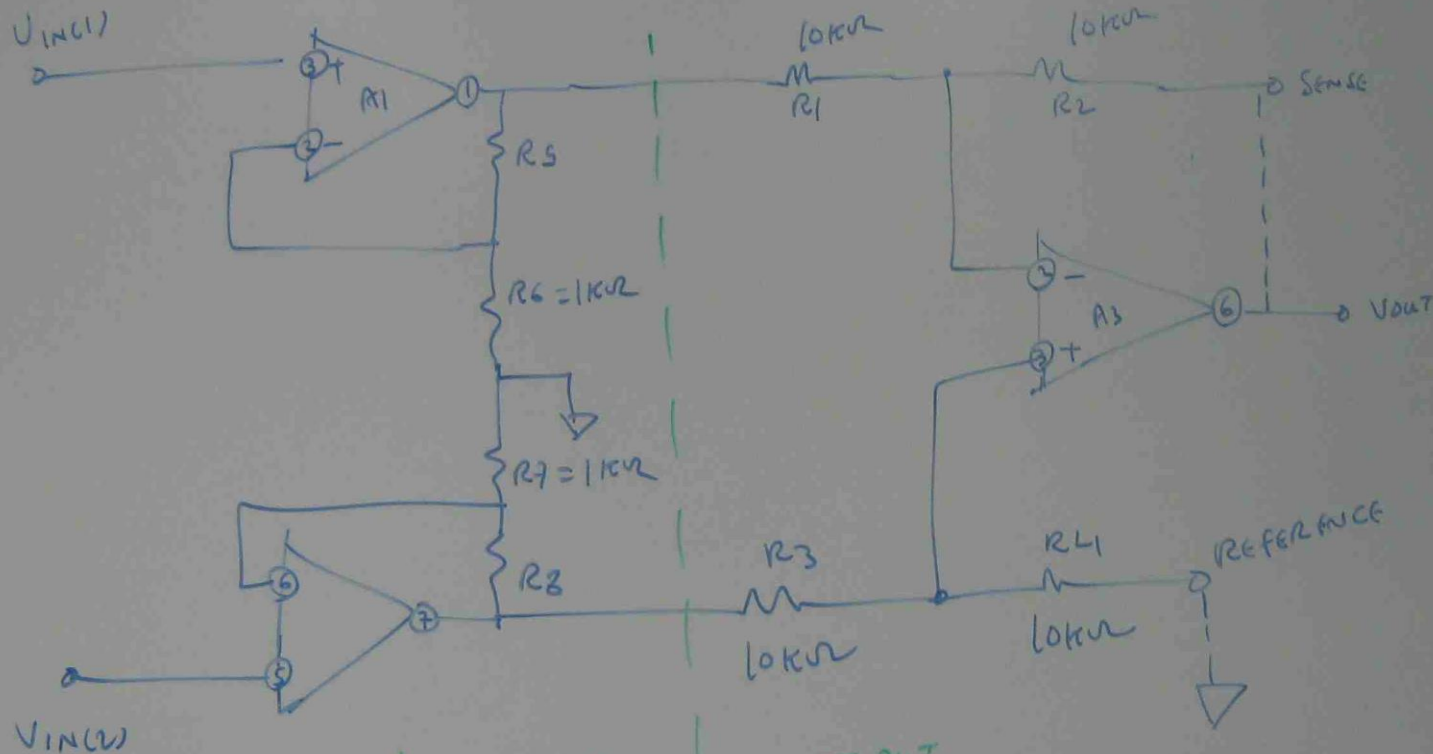A BUFFERED SUBTRACTOR WITH BUFFER AMPLIFIERS OPERATING WITH GAIN



REDUCED CMV

COMMON MODE VOLTAGE

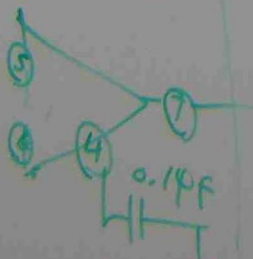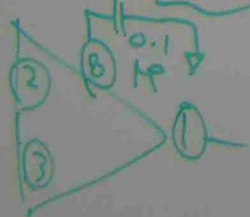

INPUT SECTION → OUTPUT SECTION

$$V_{OUT} = (V_{IN(2)} - V_{IN(1)}) \left(1 + \frac{2R_2}{R_6} \right) \left(\frac{R_2}{R_1} \right)$$

FOR $R_1 = R_3$, $R_2 = R_4$, $R_5 = R_6$

