
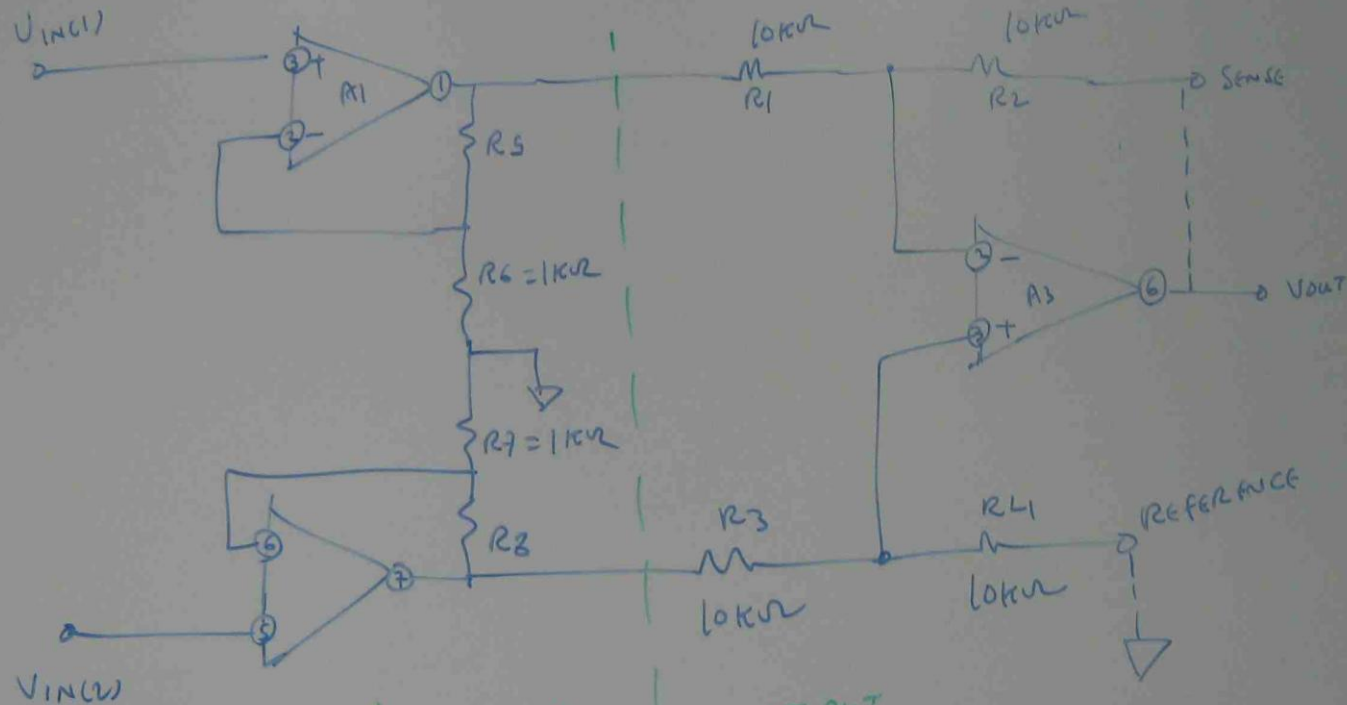

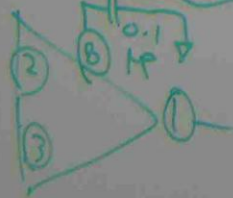
# A BUFFERED SUBTRACTOR WITH BUFFER AMPLIFIERS OPERATING WITH GAIN



REDUCED CMV

COMMON MODE VOLTAGE




INPUT SECTION

OUTPUT SECTION

$$V_{OUT} = (V_{IN(2)} - V_{IN(1)}) \left( 1 + \frac{2R_2}{R_6} \right) \left( \frac{R_2}{R_1} \right)$$

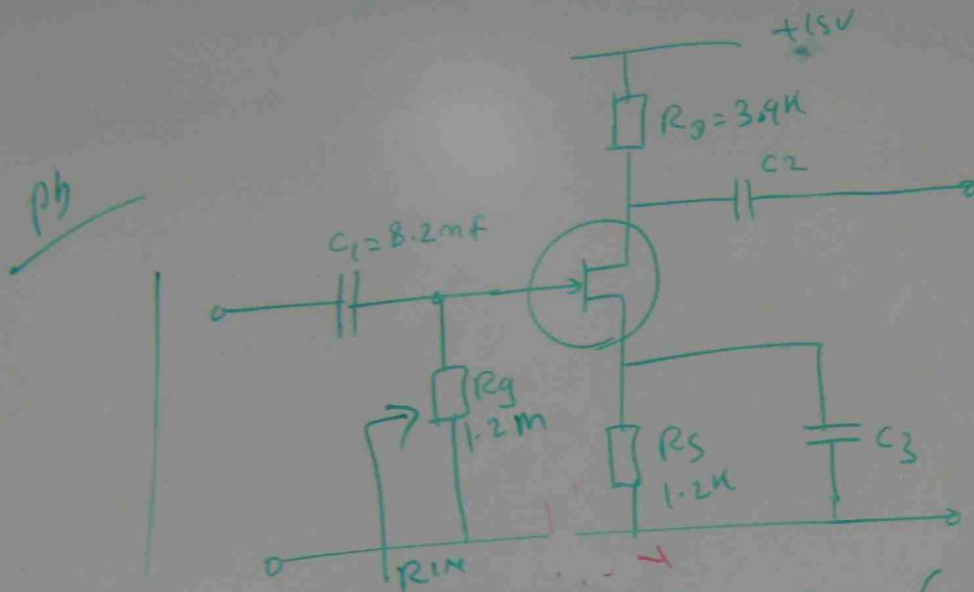FOR  $R_1 = R_3$ ,  $R_2 = R_4$ ,  $R_5 = R_6$



CALCULATE THE CUT OFF FREQUENCY  $f_1$  OF GIVEN CIRCUIT

$$f_1 = \frac{1}{2\pi R_{IN} C_C}$$

$$C_C = C_1 = 8.2 \text{ nF}$$


$$R_{IN} = R_S = 1.2 \text{ M}\Omega$$

$$f_1 = \frac{1}{2 \times 3.1416 \times 1.2 \times 10^6 \times 8.2 \times 10^{-9}}$$

$$= \frac{1}{6.28 \times 1.2 \times 8.2 \times 10^{-3}}$$


$$= \frac{1000}{6.28 \times 1.2 \times 8.2} = 16.2 \text{ Hz}$$
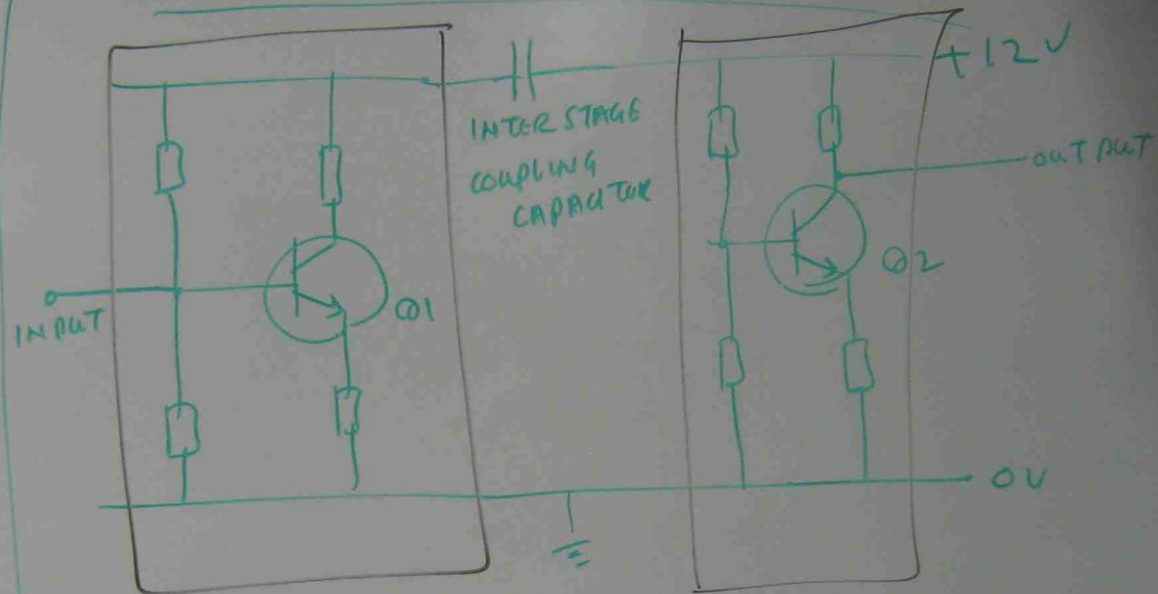
# CAPACITIVELY COUPLED MULTI STAGE AMPLIFIERS



STAGE (1)


STAGE (2)

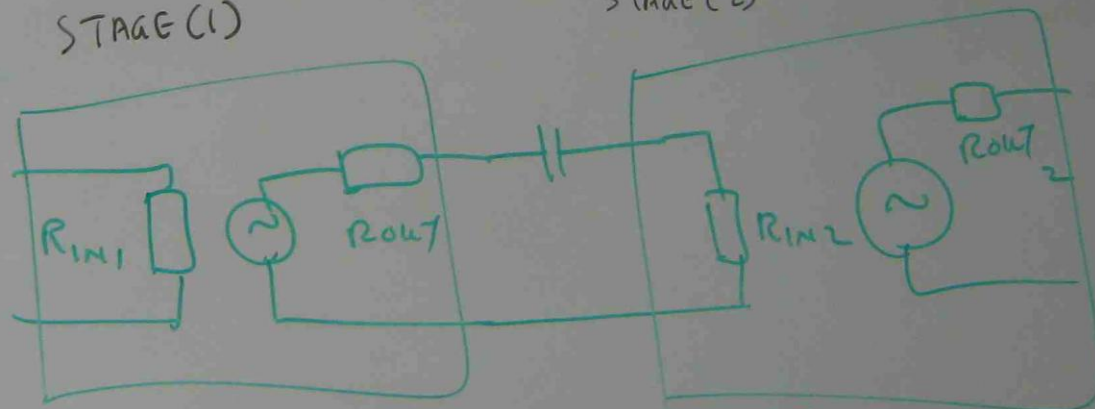

STAGE (1)

STAGE (2)

Pb

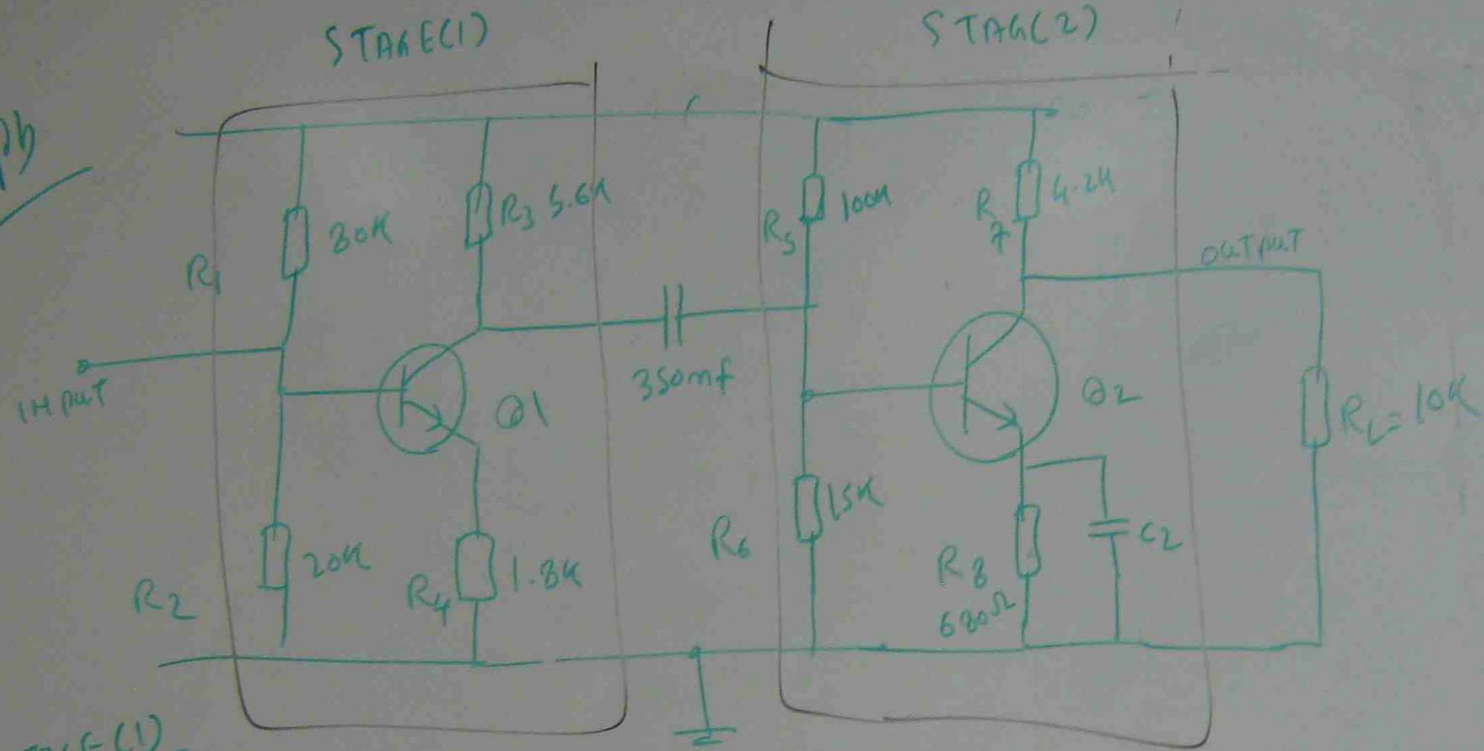

STAGE (1)

$$r_e = 26\Omega$$

$$\beta_1 = 300$$

STAGE (2)

$$r_e = 18.3\Omega, \beta_2 = 400$$

FIND  $R_{IN1}$ ,  $R_{OUT1}$ ,  $R_{IN2}$ ,  $R_{OUT2}$ ,  $A_{V1}$ ,  $A_{V2}$ ,  $A_{V_{TOTAL}}$



STAGE (1)

$$R_{in(1)} = R_1 \parallel R_2 \parallel \beta(R_4 + r_{e1})$$


$R_1 \parallel R_2$

$$= 80k \parallel 20k \parallel 300(1.8k + \frac{26}{1000})$$

$$\rightarrow \frac{80 \times 20 \times 300(1.8 + \frac{26}{1000})}{80 \times 20 + 20 \times 300(1.8 + \frac{26}{1000}) + 80(1.8 + \frac{26}{1000})}$$

$$= 15.5k\Omega$$

$$R_{out(1)} = R_3 = 5.6k\Omega$$

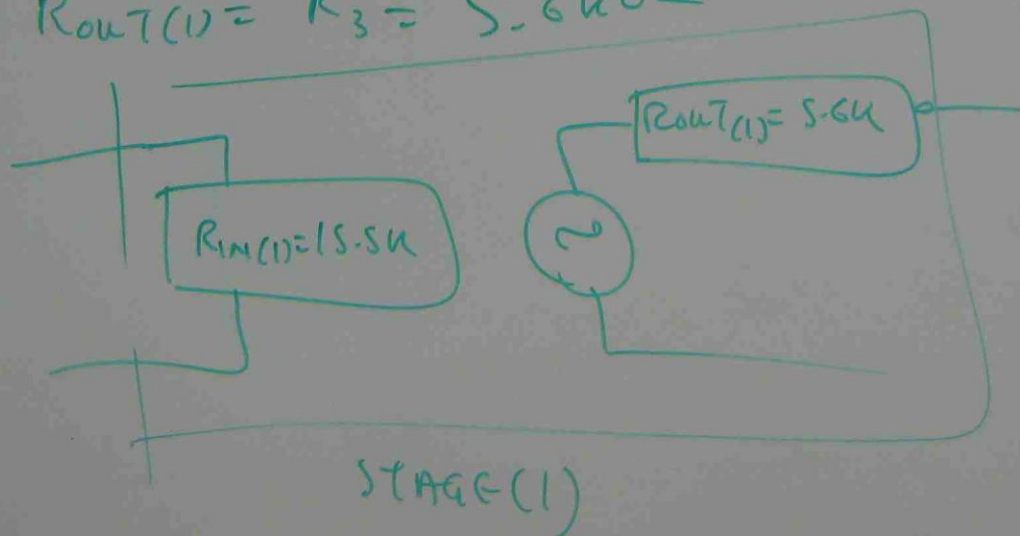

$$R_1 \parallel R_2 \parallel R_3 \rightarrow R_T = \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_3 R_1}$$

STAGE (2)

$$R_{IN2} = R_S \parallel R_G \parallel \beta \times r_{e2}$$

$$= 100k \parallel 15k \parallel \frac{400 \times 18.3}{1000}$$

$$= \frac{100 \times 15 \times \frac{400 \times 18.3}{1000}}{100 \times 15 + 15 \times \frac{400 \times 18.3}{1000} + \frac{100 \times 400 \times 18.3}{1000}}$$

$$= 4.69k\Omega$$

$$R_{OUT(2)} = 4.2k$$

$$A_{V1} = \frac{R_3 \parallel R_{IN2}}{R_4 + r_{e1}} = \frac{\frac{5.6 \times 4.69}{5.6 + 4.69}}{1.8 + \frac{26}{1000}} = 1.4$$

$$A_{V2} = \frac{R_7 \parallel R_L}{r_{e2}}$$

$$= \frac{4.2k \parallel 10k}{\frac{18.3}{1000}}$$

$$= \frac{\frac{4.2 \times 10}{4.2 + 10}}{\frac{18.3}{1000}}$$

$$= 162$$

$$A_{VT} = A_{V1} \times A_{V2}$$

$$= 1.4 \times 162$$

$$= 227$$

CUT OFF FREQUENCY

$$f_1 = \frac{1}{2\pi R_T C_C}$$

$$R_T = R_{out1} + R_{in2}$$

$$= 5.6 + 4.69 = 10.29$$

$$A_{VT} = A_{V1} \times A_{V2}$$

$$= 1.4 \times 162$$

$$= 227$$

CUT OFF FREQUENCY

$$f_1 = \frac{1}{2\pi R_T C_C}$$

$$R_T = R_{OUT1} + R_{IN2}$$


$$= 5.6 + 4.69 = 10.29$$

$$f_1 = \frac{1}{2 \times 3.1416 \times 10.29 \times 10^3 \times 350 \times 10^{-9}}$$

$$= 44.19 \text{ Hz} \quad \times$$




## TRANSFORMER COUPLED AMPLIFIERS

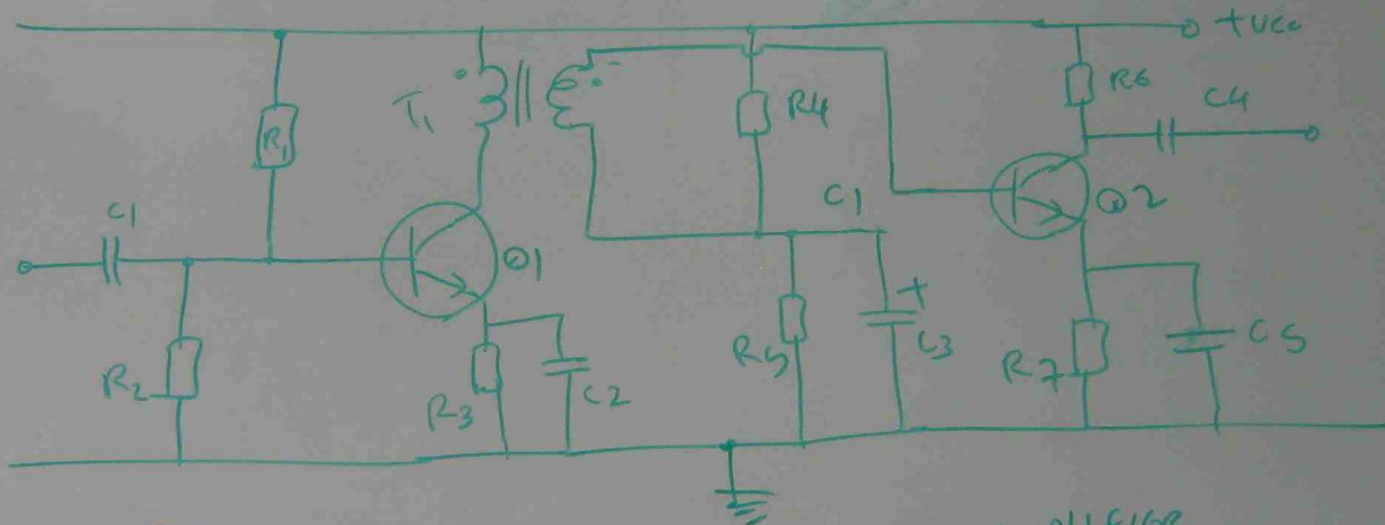

MORE EFFICIENT THAN RC COUPLED AMPLIFIER

BUT MORE DISTORTION AND POOR FREQUENCY RESPONSE

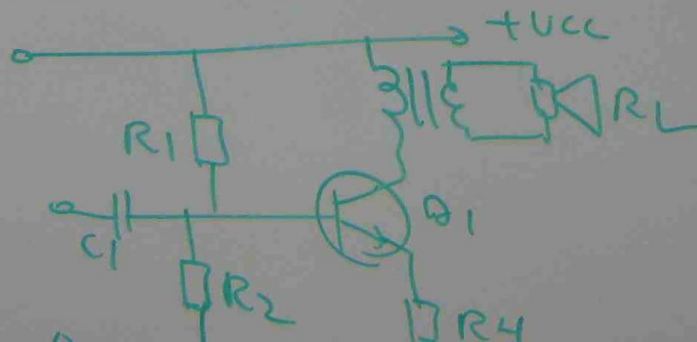
POWER AMPLIFIER (OUTPUT STAGE TRANSFORMER COUPLED)



AUDIO AMPLIFIER

## DIRECT COUPLING AND INTRODUCTION TO THE DIFFERENTIAL AMPLIFIER

DIRECT MODE - NO COUPLING CAPACITORS

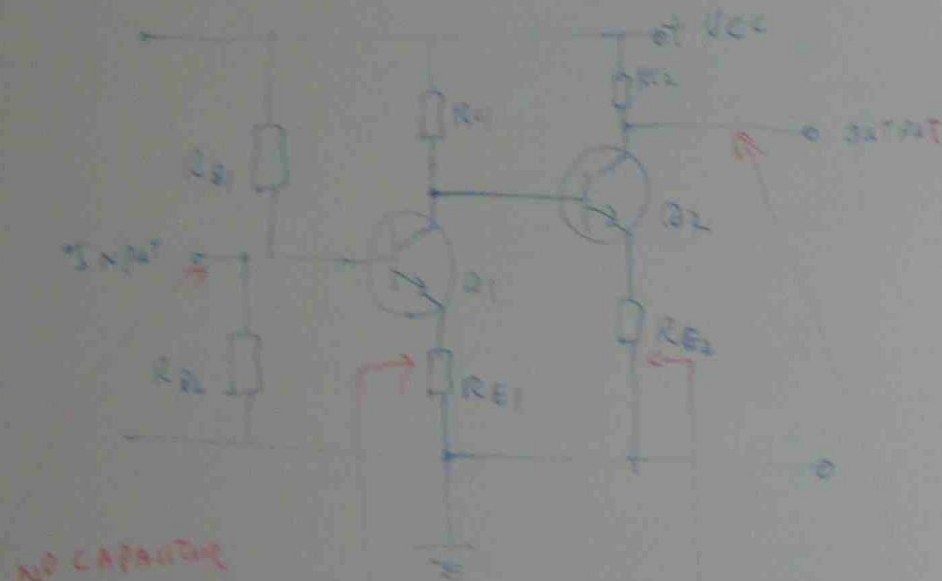


NO CAPACITORS

NO CAPACITORS

Reason

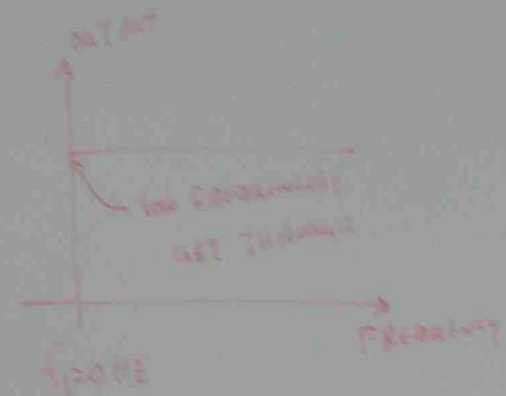
NO LIMITATION ON THE  
LOW FREQUENCY RESPONSE



DISADVANTAGES

- NO DC STABILITY
- DRIFT DUE TO TEMPERATURE VARIATION

NO CAPACITORS

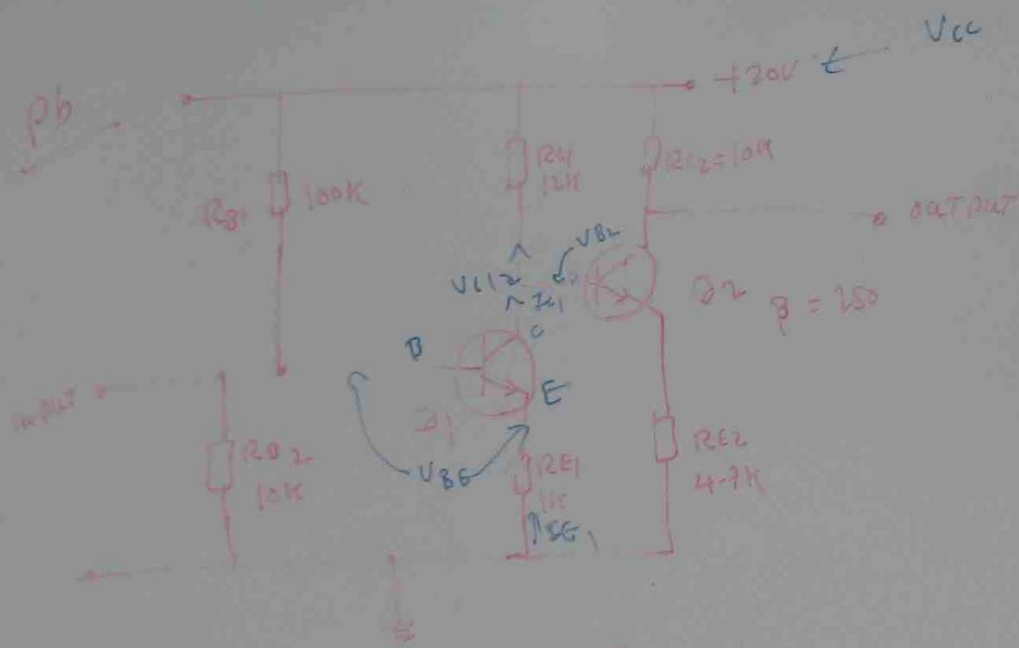

CALCULATE  
 $V_{B1}$ ,  $V_{E1}$ ,  $I_{C1}$   
 $V_{B2}$ ,  $V_{E2}$ ,  $I_{C2}$   
 $I_{E2}$   
 DC GAIN,  $R_{in2}$   
 $A_{V1}$ ,  $A_{V\text{TOTAL}}$

$$V_{B1} = V_{CC} \times \frac{R_{B2}}{R_{B1} + R_{B2}}$$

$$= 20 \times \frac{10k}{100k + 10k}$$

$$= 1.82V$$

$$V_{E1} = V_{B1} - V_{BE}$$

$$= 1.82 - 0.6 = 1.22V$$

$V_{BE} = 0.6V$  Silicon  
 $V_{BE} = 0.2V$  Ge

$$I_{C1} \approx I_{E1} = \frac{V_{E1}}{R_{E1}} = \frac{1.22V}{1k} = 1.22 \text{ mA}$$

$$V_{C1} = V_{CC} - I_{C1} R_{C1} = 20 - 1.22 \times 10^{-3} \times 12 \times 10^3$$

$$V_{C1} = V_{B2} = V_{CE1} = 5.36V$$

DIRECT COUPLED

$$V_{E2} = V_{B2} - V_{BE} = 5.36 - 0.6 = 4.76 \text{ V}$$

$$I_{C2} = I_{E2} = \frac{V_{E2}}{R_{E2}} = \frac{4.76 \text{ V}}{4.7 \times 10^3} = 1.01 \text{ mA}$$

$$V_{C2} = V_{CC} - (I_{C2} \times R_{C2})$$

$$= 20 - 1.0 \times 10^{-3} \times 10 \times 10^3$$

$$= 9.9 \text{ V}$$

$$A_{V2} = \frac{R_{C2}}{R_{E2}} = \frac{10 \text{ K}}{4.7 \text{ K}} = 2.13$$

$$R_{in2} = \beta \times R_{E2} = 250 \times 4.7 \text{ K} = 1.18 \text{ M}\Omega$$

$$A_{V1} = \frac{R_{C1}}{R_{E1}} = \frac{12 \text{ K}}{1 \text{ K}} = 12$$

$$A_{VT} = A_{V1} \times A_{V2}$$

$$= 12 \times 2.13$$

$$= 25.6$$



$$I_o = - \frac{A_{VNL} E_i}{R_L + R_o}$$

$$E_i = I_i R_i$$

$$I_o = - \frac{A_{VNL} (I_i R_i)}{R_L + R_o}$$

$$A_I = \frac{I_o}{I_i} = - A_{VNL} \times \frac{R_i}{R_L + R_o}$$