
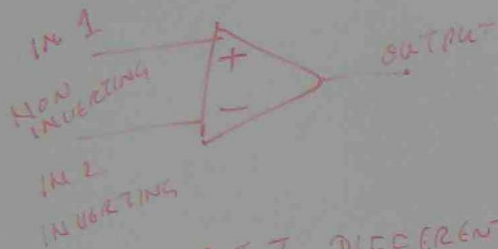


## DIFFERENTIAL AMPLIFIER

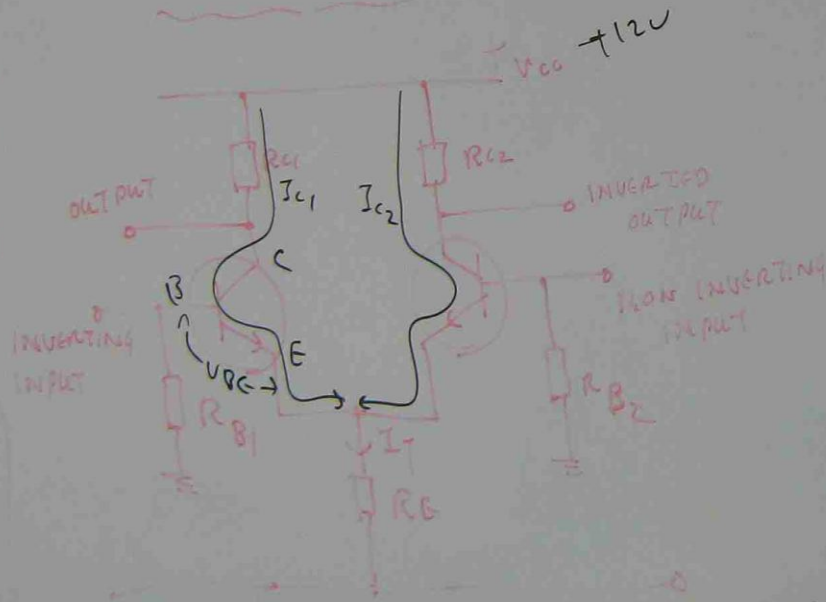

## BJT DIFFERENTIAL AMPLIFIER



Pb. IN ABOVE CIRCUIT IF

$$R_{C1} = 2.2 \text{ k}\Omega, \quad R_{C2} = 2.2 \text{ k}\Omega$$

$$R_{B1} = 33 \text{ k}\Omega, \quad R_{B2} = 33 \text{ k}\Omega$$

$$R_E = 2.7 \text{ k}\Omega$$

$$V_{CC} = +12 \text{ V}, \quad V_{BE} = -12 \text{ V} \quad \text{ALREADY}$$

(a)  $V_{B1}, V_{B2}$  (b)  $V_{E1}, V_{E2}$

(c)  $I_T$  (d)  $I_{C1}, I_{C2}$  (e)  $V_{C1}, V_{C2}$

(a)

$$V_{B1} = V_{B2} = 0$$

(b)  $V_{E1} = V_{E2} = V_{BE} = 0.6 \text{ V}$

(c)  $I_T = \frac{V_{E1} - V_{EE}}{R_E} = \frac{-0.6 - (-12)}{2.7 \times 10^3} = 4.22 \text{ mA}$

(d)  $I_{C1} = I_{C2} = \frac{I_T}{2} = \frac{4.22}{2} = 2.11 \text{ mA}$

(e)  $V_{C1} = V_{C2} = V_{CC} - I_{C1} \times R_{C1} = 12 - 2.11 \times 10^{-3} \times 2.2 \times 10^3 = 7.38 \text{ V}$

Coupling Method

CHARACTERISTICS

CAPACITIVE

PROVIDE AC COUPLING  
BLOCK DC & LOW  
FREQUENCIES

TRANSFORMER

PROVIDE AC COUPLING  
IMPEDANCE MATCHING  
BLOCK DC

REDUCE LOW FREQ:  
DISTORTION  
BULKY


DIRECT

PROVIDE DC / AC COUPLING


GOOD LOW FREQUENCY  
RESPONSE

DC STABILITY  
PROBLEM


## DIFFERENTIAL AMPLIFIER

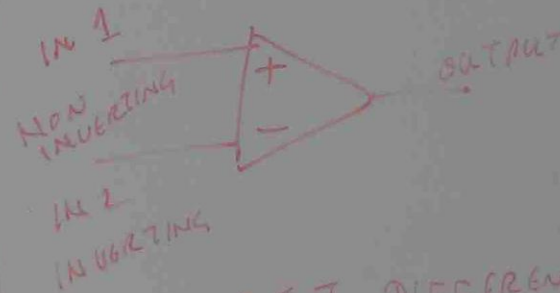

## BJT DIFFERENTIAL AMPLIFIER

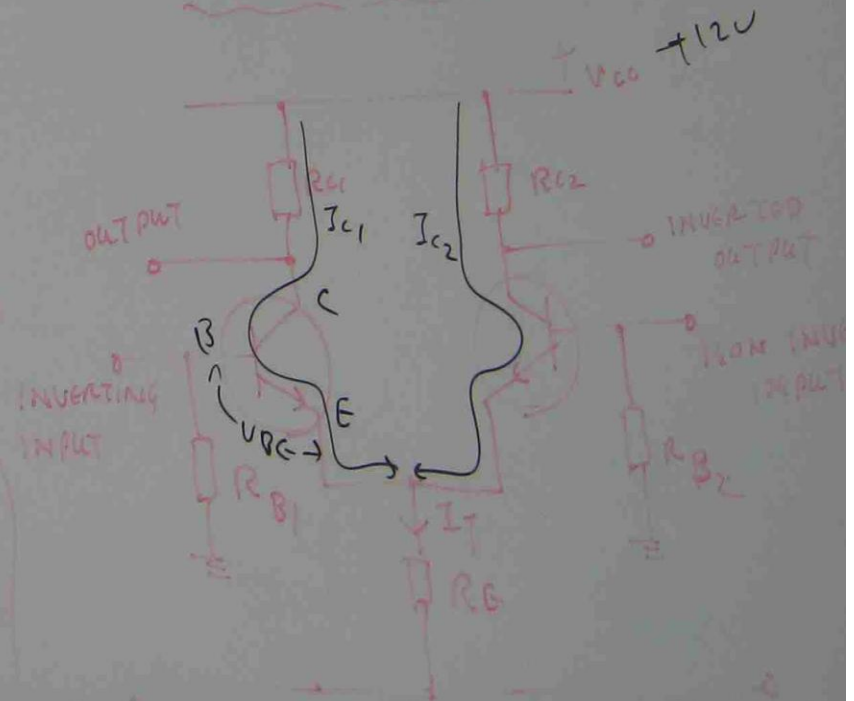
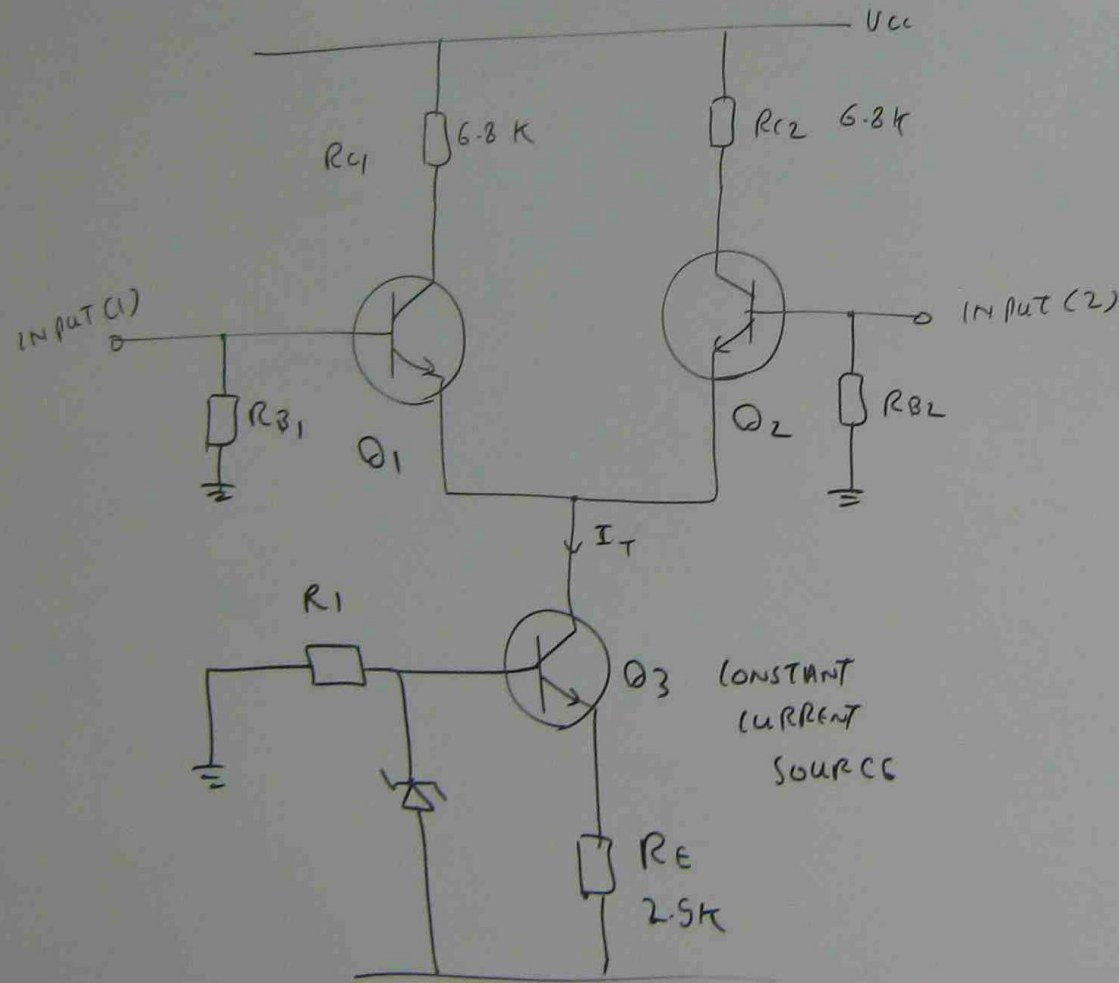
## DISCRETE DIFFERENTIAL AMPLIFIER WITH CONSTANT CURRENT SOURCE



By PROVIDING  
CONSTANT CURRENT  
SOURCE  
CMRR (Common mode  
REJECTION RATIO)  
IS IMPROVED

