
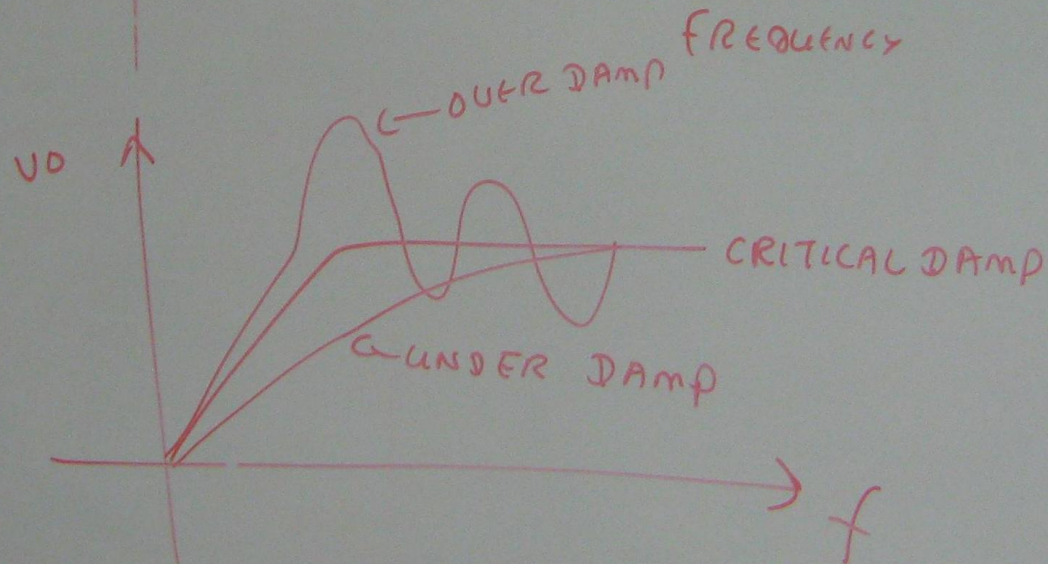


FREQUENCY COMPENSATION

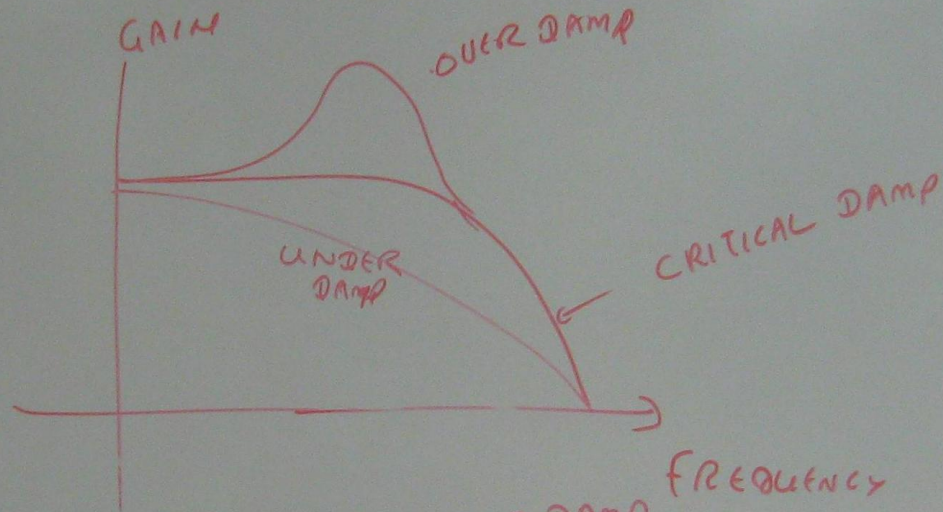

FREQUENTLY COMPENSATION IS TO BE APPLIED FOR OVER DAMP AND UNDER DAMP CIRCUITS TO ATTAIN THE CRITICAL DAMP FUNCTION

CAUSE OF DAMPING

PHASE MARGIN $45^\circ \rightarrow$ CRITICAL DAMPING

PHASE MARGIN $> 45^\circ \rightarrow$ OVER DAMPING


PHASE MARGIN $< 45^\circ \rightarrow$ UNDER DAMPING

INTERNAL AND EXTERNAL COMPENSATION

IC 741, LF351, 714 \leftarrow INTERNALLY COMPENSATED

LM301, NE5534 \leftarrow EXTERNALLY COMPENSATED

CONNECTION OF COMPENSATION CAPACITOR

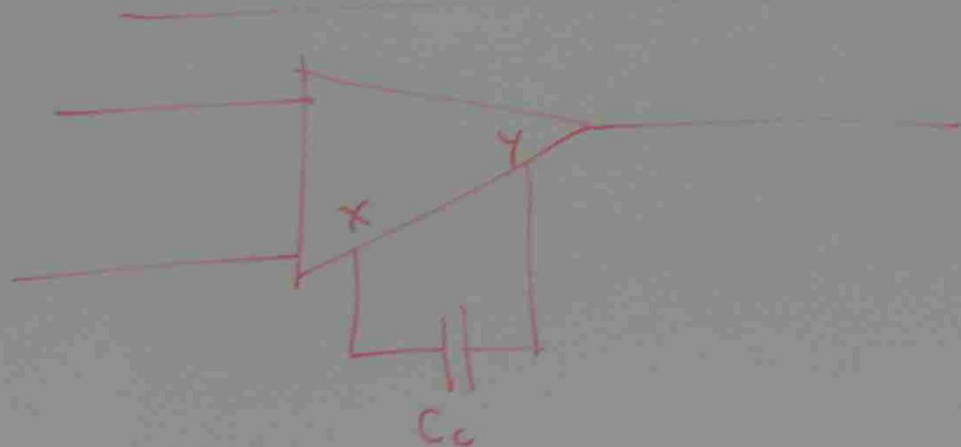

SELECTION OF CAPACITOR

$$C_c = \text{REQUIRED COMPENSATION CAPACITOR}$$

REQUIRED COMPENSATION
CAPACITOR

C_c

$$= \frac{1}{A C_L (\text{CLOSED LOOP GAIN})}$$

$$\text{OPTIMAL } C_c = \frac{\text{REQUIRED } C_c}{A_{CL}}$$

BANDWIDTH AND SLEW RATE ARE EFFECTED BY OPTIMAL CAPACITOR VALUE

$$B W (\text{BANDWIDTH}) = \text{GAIN BANDWIDTH PRODUCT (GBWP)} \times \frac{\text{REQUIRED } C_c}{\text{ACTUAL } C_c} \times \frac{1}{A_{CL}}$$

$$B W = G B W P \times \frac{R E Q C_c}{A C T C_c} \times \frac{1}{A_{CL}}$$

$$\text{NEW SLEW RATE} = \text{GIVEN SLEW RATE} \times \frac{C_c}{\text{ACTUAL } C_c}$$

Q1) THE LM301 OP-AMP REQUIRES A 30 PF COMPENSATION CAPACITOR FOR USE AS VOLTAGE FOLLOWER. ITS SLEW RATE IS $0.5 \text{ V}/\mu\text{s}$ AND GAIN BANDWIDTH PRODUCT IS 1 MHz . THIS OP-AMP IS USED TO MAKE A NFB [NEGATIVE FEEDBACK] AMPLIFIER WITH $A_{CL} = 10$.

(a) WHAT IS THE OPTIMAL VALUE OF C_c ?

(b) IF C_c OF 10 PF IS ACTUALLY USED, WHAT IS THE BAND WIDTH OF THE CIRCUIT AND SLEW RATE

$$(a) \text{ OPTIMAL } C_c = \frac{\text{REQUIRED } C_c}{A_{CL}} = \frac{30 \text{ PF}}{10} = 3 \text{ PF}$$


$$(b) \text{ BW} = \text{GBWP} \times \frac{\text{REQD. } C_c}{\text{ACT. } C_c} \times \frac{1}{A_{CL}}$$

$$= 1 \text{ MHz} \times \frac{30 \text{ PF}}{10 \text{ PF}} \times \frac{1}{10} = \frac{1000 \text{ kHz} \times 3}{10} = 300 \text{ kHz}$$

$$\text{NEW SLEW RATE} = \text{GIVEN SLEW RATE} \times \frac{C_c}{\text{ACT. } C_c} = 0.5 \times \frac{30}{10} = 1.5 \text{ V}/\mu\text{s}$$

CONNECTION METHODS OF COMPENSATION

(1) Two CAPACITOR COMPENSATION

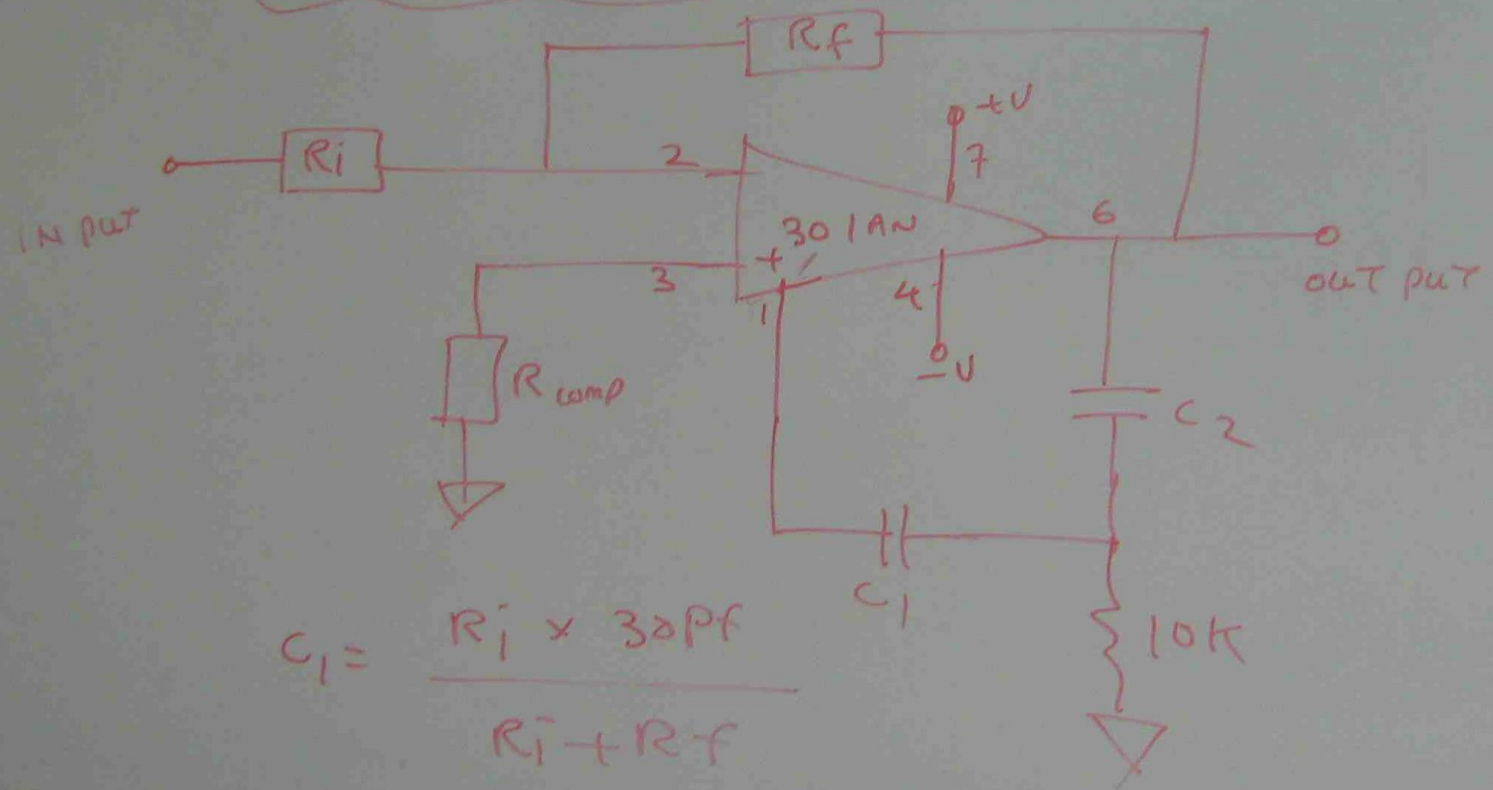



$$C_1 = \frac{R_i \times 30pF}{R_i + R_f}$$

$$C_2 = 10 C_1$$

CHARACTERISTICS

- REDUCTION IN HIGH FREQUENCY GAIN WHICH IS NEEDED FOR STABILITY
- HIGHER SLEW RATE FOR A GIVEN GAIN BANDWIDTH PRODUCT

FEED FORWARD COMPENSATION

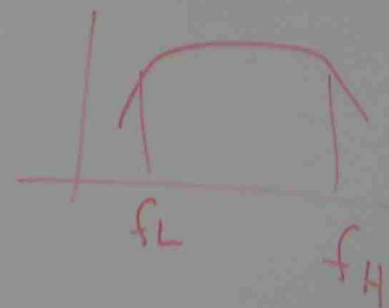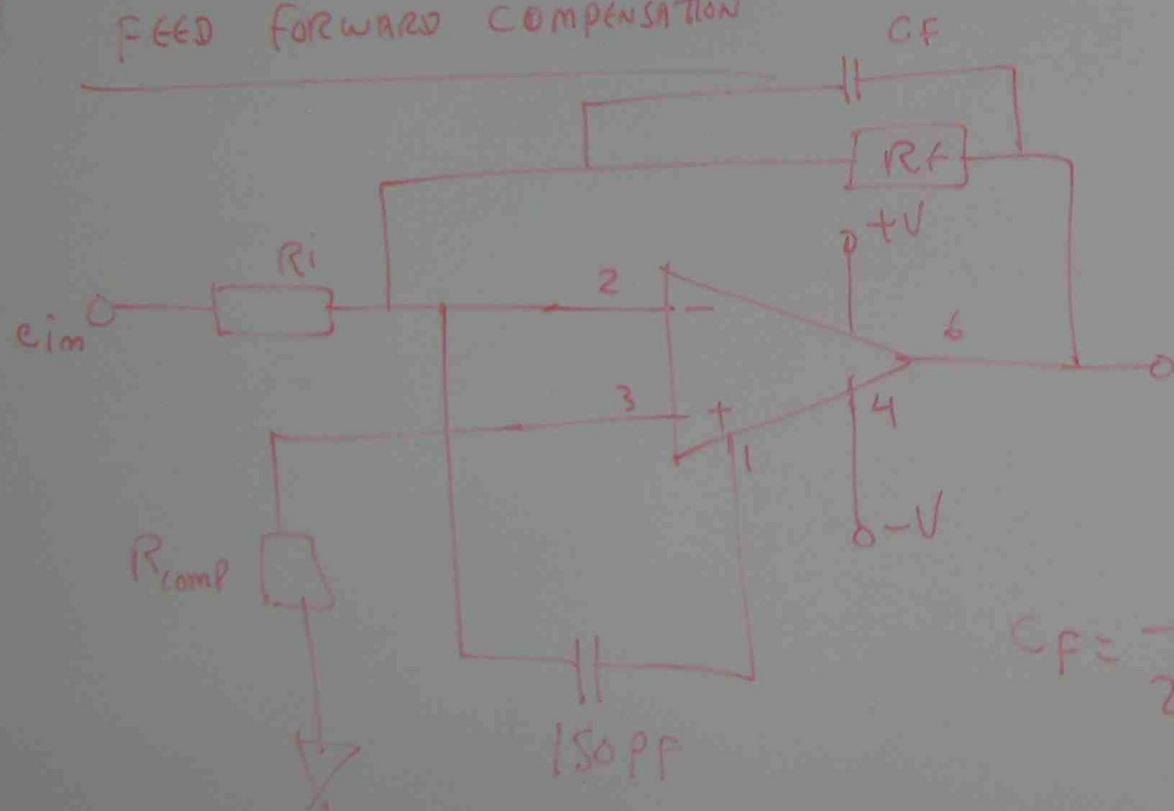

$$C_F = \frac{1}{2\pi f_H R_F}$$

IN MANY OP-AMP, THE INVERTING SIGNAL HAS TO PASS THROUGH SOME SLOW BIASING TRANSISTORS WHICH INTRODUCE LARGE NEGATIVE PHASE SHIFT.

IN FEED FORWARD COMPENSATION, THE PHASE SHIFTING TRANSISTORS ARE BY PASSED BY A CAPACITOR.

C_F WORKS ONLY FOR INVERTING AMPLIFIER.
IT CAN PROVIDE HIGH SLEW RATE.