

INPUT OFFSET VOLTAGE

THE OP-AMP OUTPUT VOLTAGE MAY NOT BE ZERO WHEN THE VOLTAGE ACROSS INPUT IS ZERO.

INPUT OFFSET CURRENT

OFFSET CURRENT MAY BE REQUIRED ACROSS THE INPUT TO MAKE OUTPUT VOLTAGE TO BECOME ZERO.

INPUT BIAS CURRENT


THE AVERAGE OF THE TWO INPUT CURRENTS REQUIRED TO DRIVE THE OUTPUT VOLTAGE TO ZERO.

SLEW RATE

IF A VOLTAGE IS SUDDENLY APPLIED TO THE INPUT OF AN OP-AMP, THE OUTPUT WILL SATURATE TO THE MAXIMUM. THE SLEW RATE IS THE RATE AT WHICH THE OUTPUT VOLTAGE CHANGES TO THE SATURATION VALUE

UNITY GAIN FREQUENCY BANDWIDTH

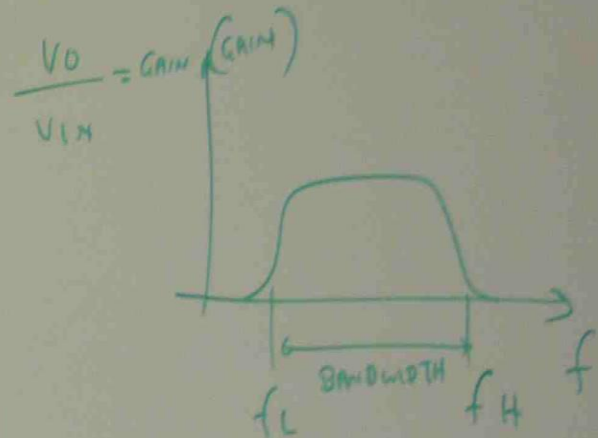THE FREQUENCY RESPONSE OF AN OP-AMP IS TYPICALLY DEFINED BY A GRAPH OF OPEN LOOP VOLTAGE GAIN VERSUS FREQUENCY.




$$BW = f_H - f_L$$

UNITY GAIN FREQUENCY BANDWIDTH


THE FREQUENCY RESPONSE OF AN OP-AMP IS
TYPICALLY DEFINED BY A GRAPH OF OPEN
LOOP VOLTAGE GAIN VERSUS FREQUENCY.
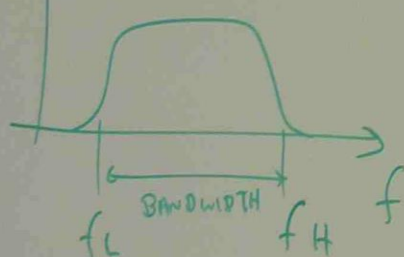
$$\frac{V_O}{V_{IN}} = \text{GAIN (GAIN)}$$




$$BW = f_H - f_L$$

VOLTAGE FOLLOWER

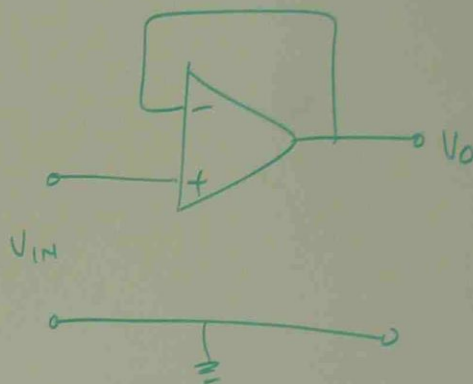

SUMMING AMPLIFIER

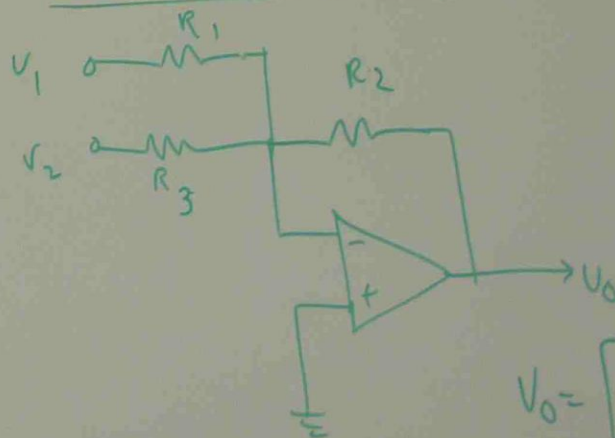

$$V_O = \left[\frac{R_2}{R_1} V_1 + \frac{R_2}{R_3} V_2 \right]$$

pb

DEVELOP AN OP
PROVIDE AN CO
RELATED TO

$$V_{OUT} =$$

$$V_{IN} = \frac{V}{I}$$

5

3


pb

DEVELOP AN OP-AMP CIRCUIT THAT CAN
PROVIDE AN OUTPUT VOLTAGE THAT IS
RELATED TO THE INPUT VOLTAGE BY

$$V_{out} = 3.4 V_{in} + 5 \quad \leftarrow \text{comparator}$$

$$V_o = \left[\frac{R_2}{R_1} V_1 + \frac{R_2}{R_3} V_3 \right]$$

\downarrow \uparrow
 V_{in} $5V$

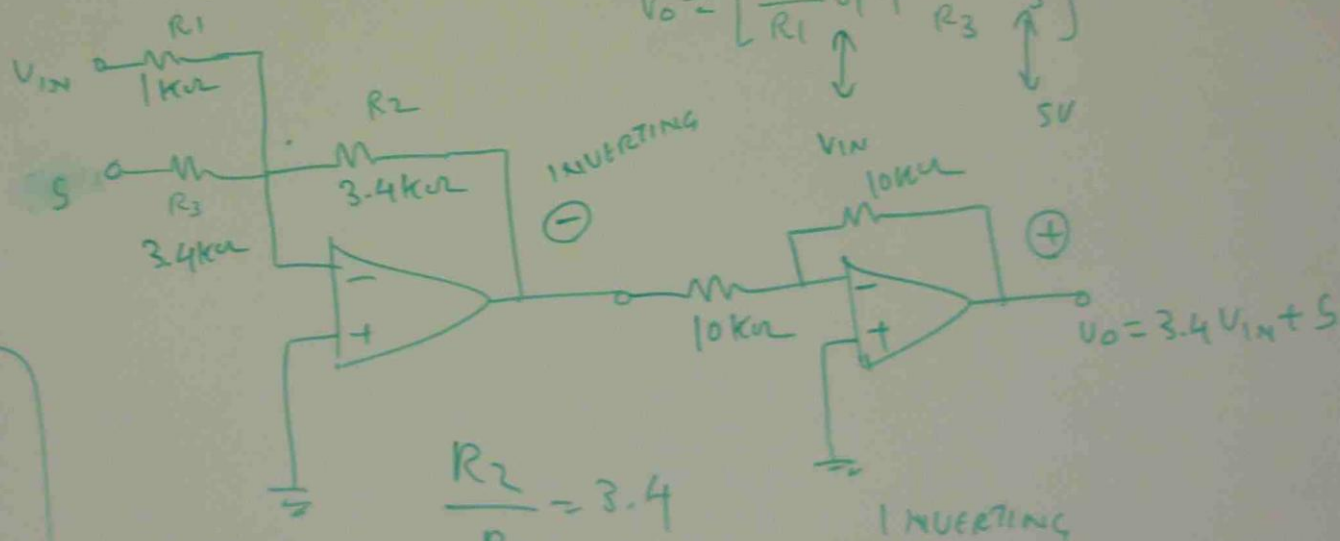


$$\frac{R_2}{R_1} = 3.4$$

$$\frac{R_2}{R_3} = 1$$

$$V_o = \left[\frac{R_2}{R_1} V_1 + \frac{R_2}{R_3} V_2 \right]$$

NON INVERTING AMPLIFIER

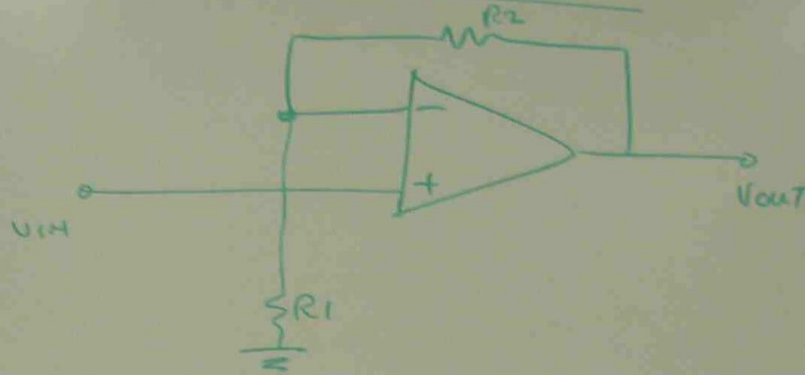

$$V_{OUT} = \left[1 + \frac{R_2}{R_1} \right] V_{IN}$$

pb


DESIGN A HIGH IMPEDANCE AMPLIFIER
WITH A VOLTAGE GAIN OF 42.

$$V_{OUT} = \left[1 + \frac{R_2}{R_1} \right] V_{IN}$$


$$\frac{V_{OUT}}{V_{IN}} = 1 + \frac{R_2}{R_1}$$

$$42 = 1 + \frac{R_2}{R_1}$$

$$\frac{R_2}{R_1} = 41$$

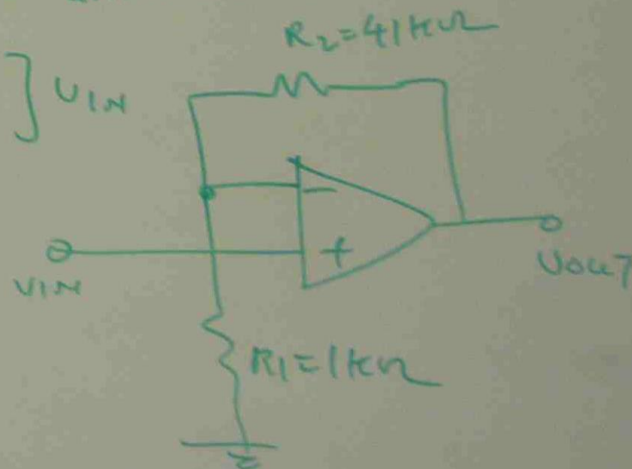

DIFFERENTIAL AMPLIFIER

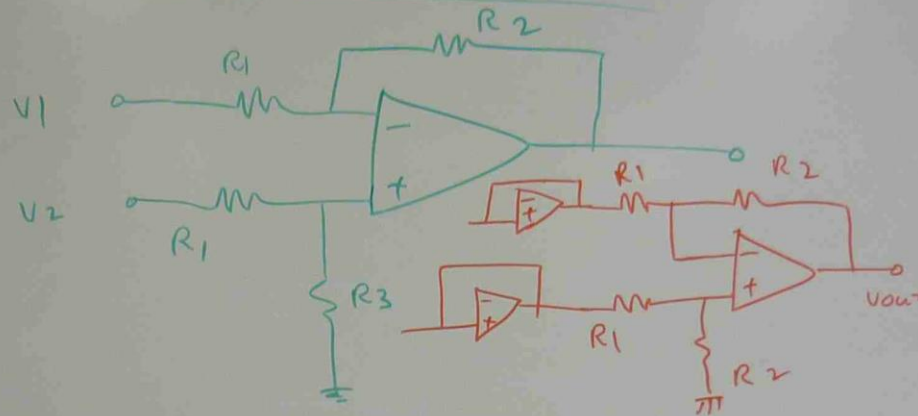

$$V_{out} = \frac{R_2}{R_1} (\underline{V_2} - \underline{V_1})$$

pb A SENSOR OUTPUTS A RANGE OF 20 TO 250 mV AS A VARIABLE VARIES OVER ITS RANGE. DEVELOP SIGNAL CONDITIONING SO THAT THIS BECOMES 0 TO 5 V.

$$V_{out} = m V_{IN1} + V_{IN2}$$

$$0 = m \times 0.02 + V_{IN2} \quad \text{--- (1)}$$

$$5 = m \times 0.25 + V_{IN2} \quad \text{--- (2)}$$

$$(2) - (1) \Rightarrow 5 = 0.23 m$$

$$m = \frac{5}{0.23} = 21.7 = \frac{R_2}{R_1}$$


$$5 = 0.25 \times 21.7 + V_{IN2}$$

$$V_{IN2} = 5 - 0.25 \times 21.7 = -0.434$$

$$V_{out} = m V_{IN1} + V_{IN2}$$

$$= 21.7 V_{IN1} + (-0.434)$$

$$V_{out} = 21.7 V_{IN1} - 0.434$$

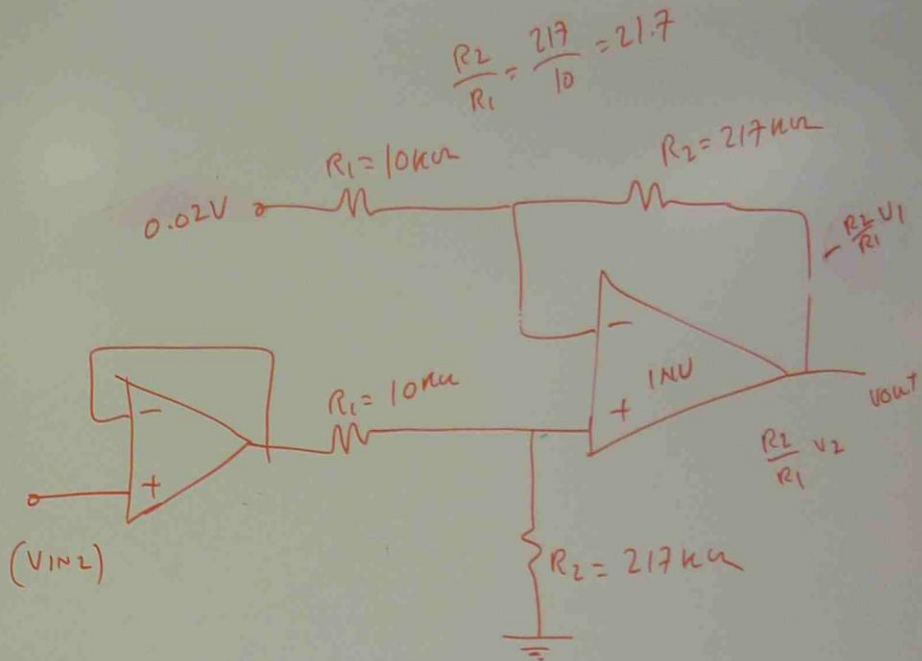

$V_{SAT} = \text{OP-AMP SATURATION VOLTAGE}$

$I_m = \text{MAXIMUM CURRENT}$

2

N2 — (1)

N2 — (2)

$$21.7 = \frac{R_L}{R_1} (V_{INL})$$


$$= (-) 0.434$$

2

$$0.434)$$

4

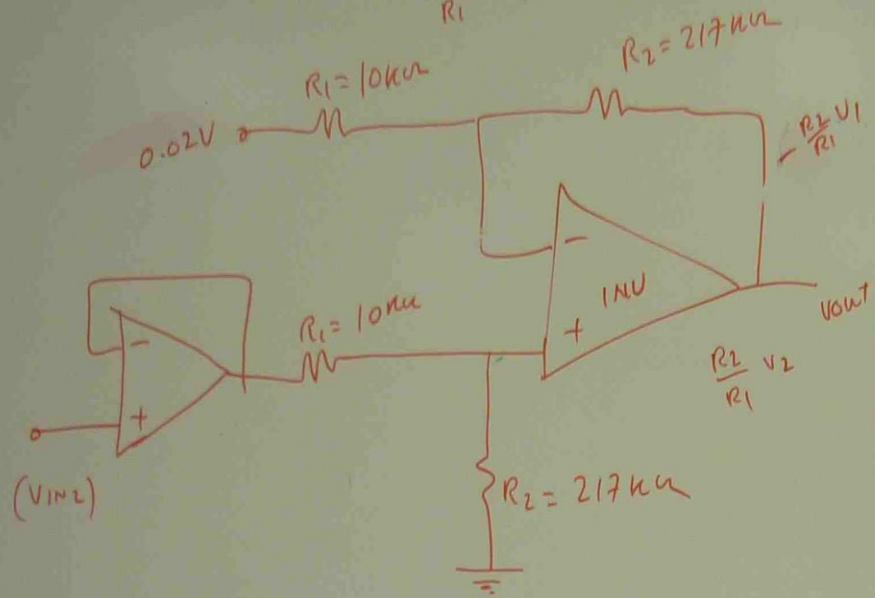
$$\frac{R_2}{R_1} = \frac{217}{10} = 21.7$$



V_{SAT} = OP-AMP
SATURATION
VOLTAGE

I_m = MAXIMUM
CURRENT

VOLTAGE TO CURRENT CONVERTER

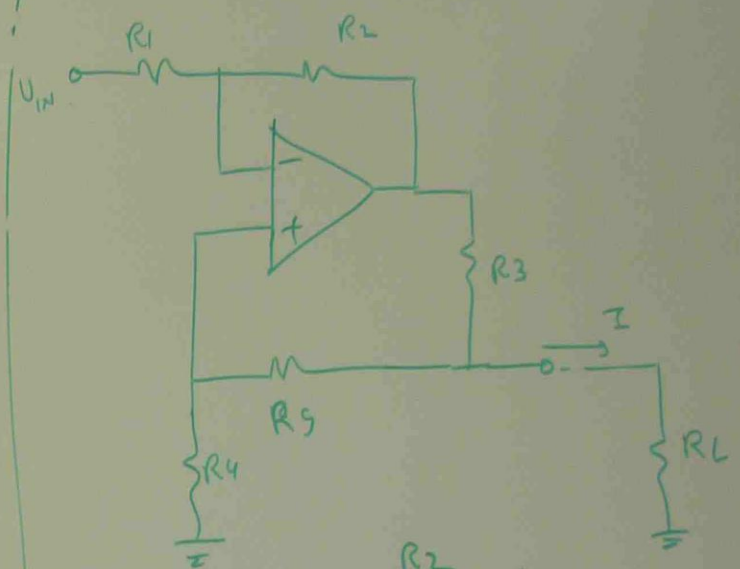


$$I = \frac{R_2}{R_1 R_3} V_{IN}$$

R_{mL} = MAXIMUM LOAD RESISTANCE


$$R_{mL} = \frac{(R_4 + R_5) \left[\frac{V_{SAT}}{I_m} - R_3 \right]}{R_3 + R_4 + R_5}$$

21.7

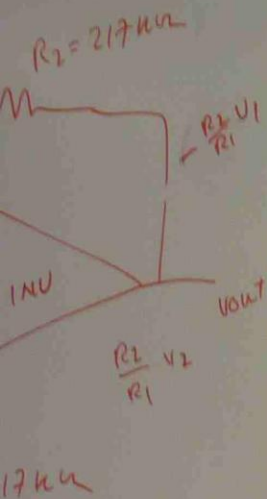

$V_{SAT} = \text{OP-AMP SATURATION VOLTAGE}$
 $I_m = \text{MAXIMUM CURRENT}$

VOLTAGE TO CURRENT CONVERTER

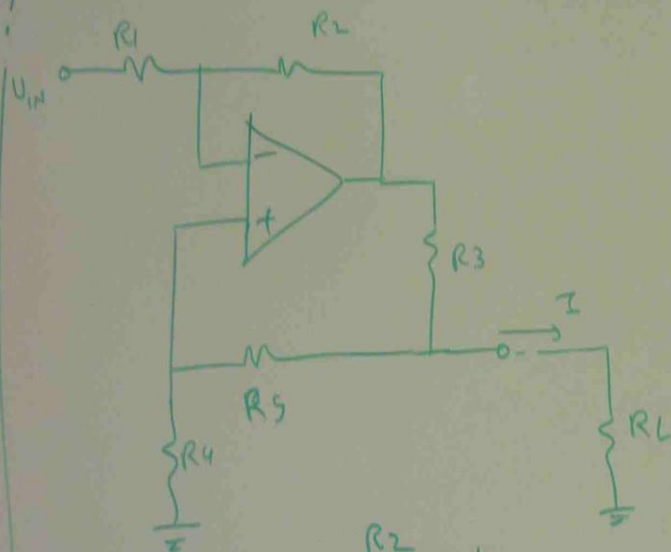


$$I = \frac{R_2}{R_1 R_3} V_{IN}$$

$R_{mL} = \text{MAXIMUM LOAD RESISTANCE}$

$$R_{mL} = \frac{(R_4 + R_5) \left[\frac{V_{SAT}}{I_m} - R_3 \right]}{R_3 + R_4 + R_5}$$

pb

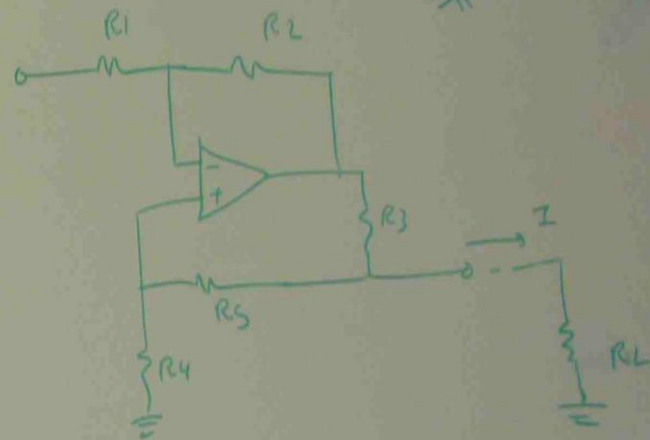A SENSOR OUTPUTS 0 TO 1 VOLT. DEVELOP A VOLTAGE TO CURRENT CONVERTER SO THAT THIS BECOMES 0 TO 10 mA. SPECIFY THE CURRENT IF THE OP-AMP SATURATES AT 10V.




$$I = \frac{R_2}{R_1 R_3} V_{IN}$$

IN PRACTICAL DESIGN, SET $R_1 = R_2$ (ANY VALUE)

$$I = \frac{V_{IN}}{R_3}$$

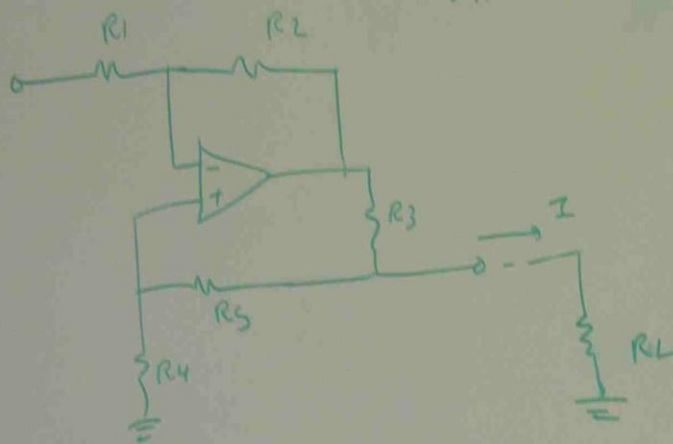pb A SENSOR OUTPUTS 0 TO 1 VOLT. DEVELOP A VOLTAGE TO CURRENT CONVERTER SO THAT THIS BECOMES 0 TO 10 mA. SPECIFY THE MAXIMUM LOAD RESISTANCE IF THE OP-AMP SATURATES AT 10V.



$$I = \frac{R_2}{R_1 R_3} V_{IN}$$

IN PRACTICAL DESIGN, SET $R_1 = R_2$ (ANY VALUE)

$$I = \frac{V_{IN}}{R_3}$$

$$I = 10 \text{ mA}, V_{IN} = 1 \text{ V}, R_3 = ?$$

$$10 \times 10^{-3} = \frac{1}{R_3}$$

$$R_3 = \frac{1}{10^{-2}} = 10^2 = 100 \Omega$$

IN PRACTICAL DESIGN

$$\text{SET } R_3 = R_4$$

$$\therefore R_3 = R_4 = 100 \Omega$$

IN PRACTICAL $R_5 \approx 0$

$$R_{mL} = \frac{(R_4 + R_5) \left[\frac{V_{SAT}}{I_m} - R_3 \right]}{R_3 + R_4 + R_5}$$

$$R_{mL} =$$

CUR

I a


$$R_{ml} = \frac{(100 + 0) \left[\frac{10}{10 \times 10^{-3}} - 100 \right]}{100 + 100 + 0}$$

$$= \frac{100 \times [1000 - 100]}{200}$$


$$= \frac{900}{2}$$

$$= 450 \Omega$$

CURRENT TO VOLTAGE CONVERTER

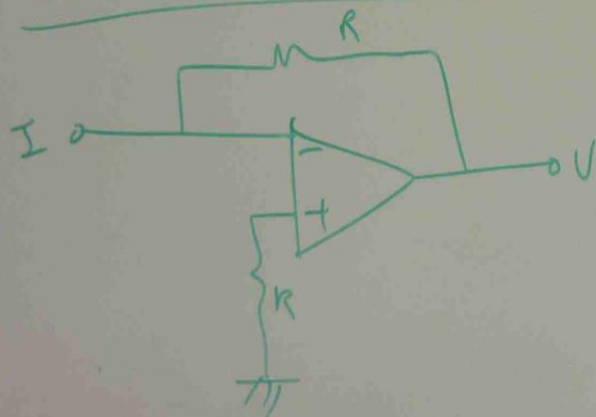

INTEGRATOR

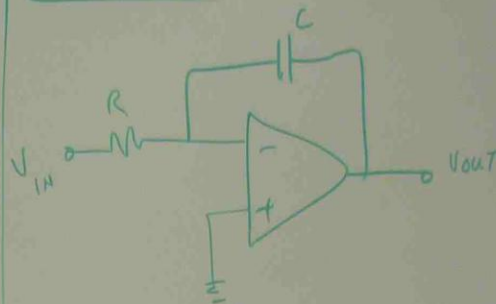

$$V_{out} = -\frac{1}{R_C} \int V_{in} dt$$

$$V_{out} = \frac{K}{R_C} t$$

$$\text{IF } V_{in} = K$$

pn
USE AN INTEGRATOR TO PRODUCE
LINEAR RAMP VOLTAGE RISING AT
10 V PER CMS.

$$V_{out} = \frac{V_{in}}{R_C} t$$

$$10 = \frac{V_{in}}{R_C} \times 10^{-3}$$

$$\frac{10}{10^{-3}} = \frac{V_{in}}{R_C}$$

$$10^4 = \frac{V_{in}}{R_C}$$

$$\text{IF } V_{in} = 1V$$

$$R_C = ? \quad \left| \quad R_C = \frac{1}{10^4} = 10^{-4} \Omega$$

$$C = ?$$

$$\left[\frac{10}{10 \times 10^{-3}} - 100 \right]$$

$$100 + 0$$


$$\times \left[1000 - 100 \right]$$

$$200$$


$$0$$

$$0$$

VOLTAGE CONVERTER

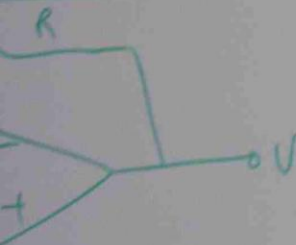

INTEGRATOR

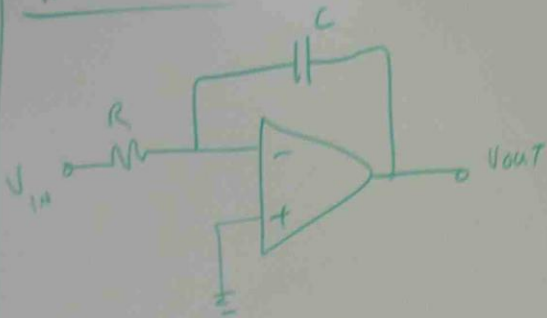

$$V_{OUT} = -\frac{1}{RC} \int V_{IN} dt$$

$$V_{OUT} = \frac{K}{RC} t$$

$$\text{IF } V_{IN} = K$$

PRO USE AN INTEGRATOR TO PRODUCE A LINEAR RAMP VOLTAGE RISING AT 10 V PER CMS.

$$V_{OUT} = \frac{V_{IN}}{RC} t$$

$$10 = \frac{V_{IN}}{RC} \times 10^{-3}$$

ANY COMBINATION

SAY

$$\text{IF } R = 100k$$

$$\text{THEN } C = 1\mu F$$

$$\frac{10}{10^{-3}} = \frac{V_{IN}}{RC}$$

$$10^4 = \frac{V_{IN}}{RC}$$



$$\text{IF } V_{IN} = 1V$$

$$R = ?$$

$$C = ?$$

$$RC = \frac{1}{10^4} = 10^{-4}$$

LINEARIZATION

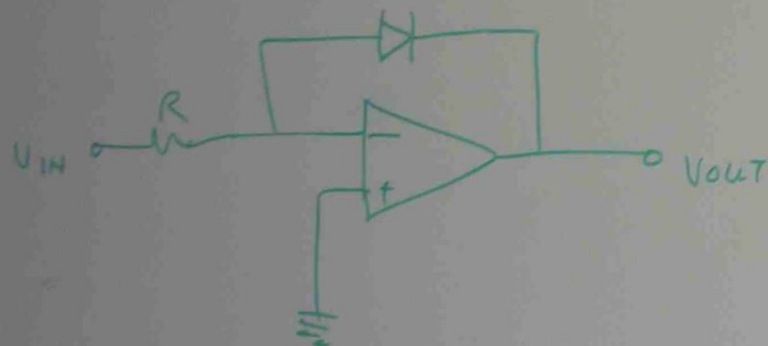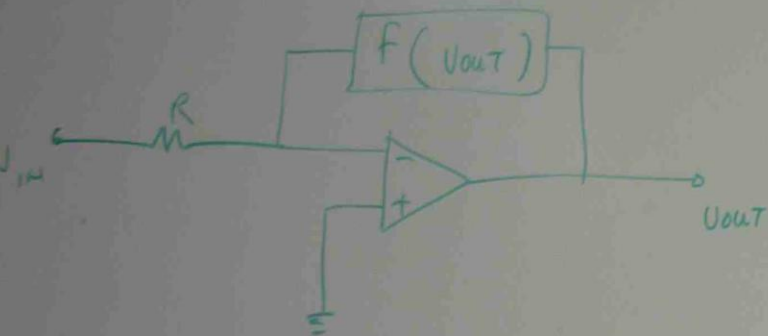

$$F(V_{OUT}) = f_0 e^{\alpha V_{OUT}}$$

f_0 = AMPLITUDE CONSTANT

α = EXPONENTIAL CONSTANT

$$V_{OUT} = \frac{1}{\alpha} \log_e V_{IN} - \frac{1}{\alpha} \log_e (f_0 R)$$

LOGARITHMIC AMPLIFIER CIRCUIT

SPECIAL INTEGRATED CIRCUITS (ICs)

- ① HIGH GAIN DIFFERENTIAL INSTRUMENTATION AMPLIFIERS
- ② CURRENT TO VOLTAGE CONVERTERS
- ③ MODULATOR / DEMODULATORS
- ④ BRIDGE AND NULL DETECTORS
- ⑤ PHASE SENSITIVE DETECTORS

$\log_e (FoR)$

CIRCUIT

S (ICs)

INSTRUMENTATION

ALTERS



ATORS

TECTORS


ECTORS

INDUSTRIAL ELECTRONICS

SILICON CONTROLLED RECTIFIERS

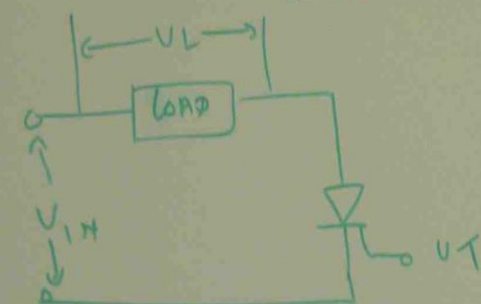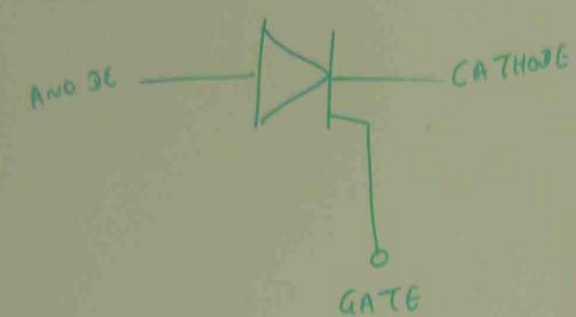


$V_T = \text{TRIGGERED VOLTAGE}$

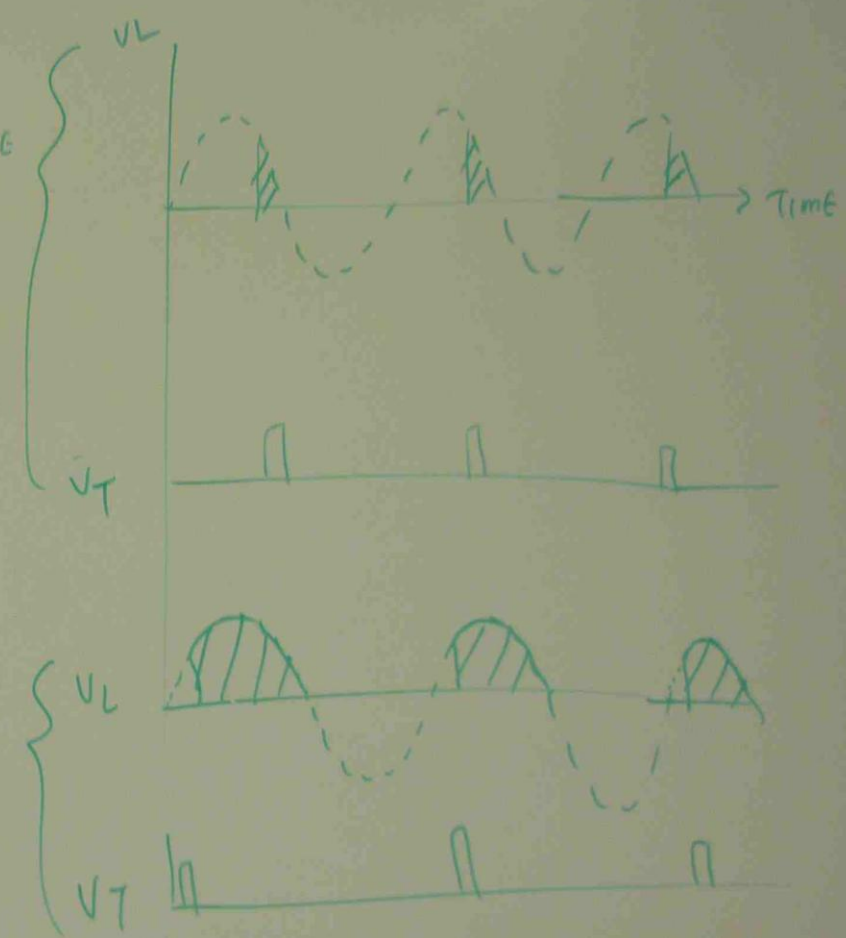

PRACTICAL (1)

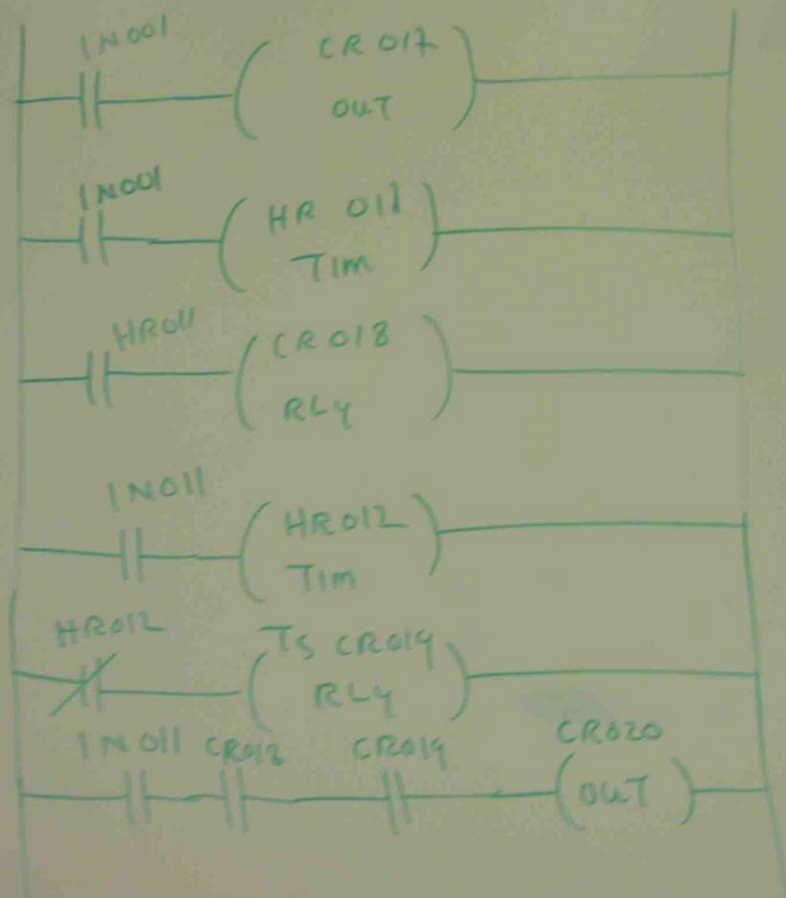USE YOUR COMPUTER AND DESIGN THE FOLLOWING CONTROL SYSTEM
BY USING TL31 PLC PROGRAM



INPUT
IN001

OUTPUT
CR020
CR017

RELAY
CR018
CR019

TIMER
HR011 87 sec
HR012 16 sec

PLC CONTROL SYSTEM

INPUT

I001

OUTPUT

Q020

Q017

RELAY

C018

C014

TIMER

T011

87 sec

T012

16 sec

pb

A NORMALLY CLOSED LIMIT SWITCH IS CONNECTED TO INPUT X1. OUTPUT Y2 MUST TURN ON WHEN THE LIMIT SWITCH OPENS WHEN THE OBJECT IS PRESENT




INPUT X1

OUTPUT Y2

pb

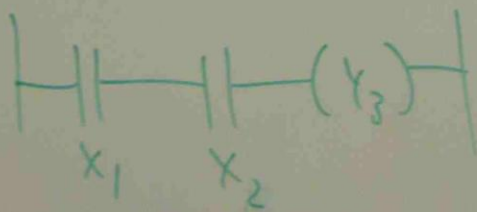A NORMALLY OPEN PROXIMITY SWITCH IS CONNECTED TO INPUT X1 AND A SECOND NORMALLY OPEN PROXIMITY SWITCH IS CONNECTED TO INPUT X2. OUTPUT Y3 MUST OPERATE WHEN BOTH SWITCHES ARE ACTIVATED.




INPUT X1, X2


OUTPUT Y3

pb

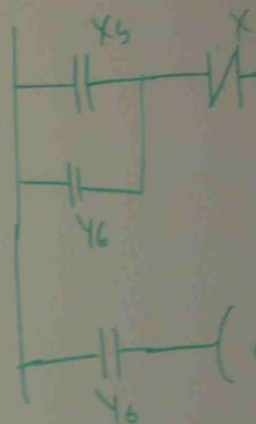A NORMALLY CLOSED SWITCH IS CONNECTED TO INPUT X4 AND A NORMALLY OPEN SWITCH IS CONNECTED TO INPUT X5. OUTPUT Y7 MUST OPERATE WHEN BOTH SWITCHES ARE TO BE ACTIVATED.




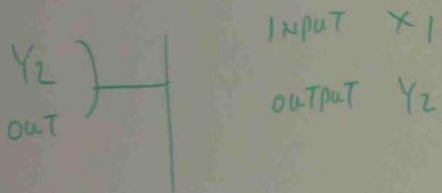SECOND LIMIT SWITCH IS CONNECTED TO
 PUT Y₂ MUST TURN ON WHEN
 OPENS WHEN THE OBJECT IS PRESENT




INPUT X₁
 OUTPUT Y₂

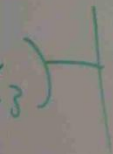A PROXIMITY SWITCH IS
 PUT X₁ AND A SECOND NORMALLY
 SWITCH IS CONNECTED TO INPUT X₂.
 OPERATE WHEN BOTH SWITCHES




INPUT X₁, X₂
 OUTPUT Y₃

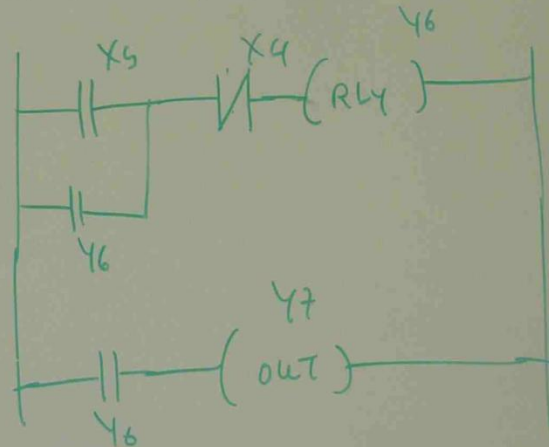Pb) A NORMALLY CLOSED PUSH BUTTON SWITCH IS CONNECTED TO
 INPUT X₄ AND A NORMALLY OPEN PUSH BUTTON SWITCH IS
 CONNECTED TO INPUT X₅. THESE TWO PUSH BUTTON
 SWITCHES ARE TO BE USED TO CONTROL THE OPERATION
 OF OUTPUT Y₇.



MOTOR STARTER
 CIRCUIT

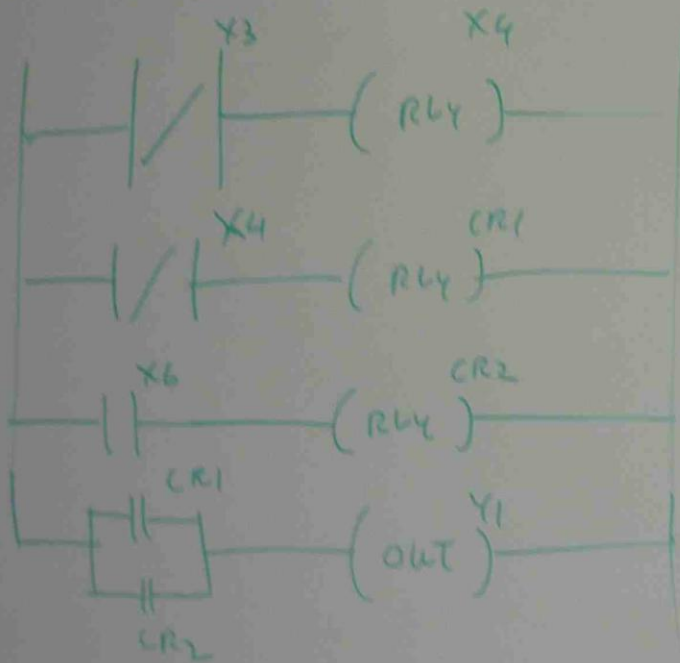Prob A NORMALLY CLOSED LIMIT SWITCH IS CONNECTED TO INPUT X_3 AND A NORMALLY OPEN LIMIT SWITCH IS CONNECTED TO INPUT X_6 . OUTPUT Y_1 OPERATES ONLY WHEN EITHER LIMIT SWITCH DETECTS AN OBJECT.



INPUT
 X_3, X_6

OUTPUT
 Y_1


RELAY
 X_4, CR_1, CR_2

SIMULATION

| IN | OUT |
|--------------------|---------|
| $X_3=0$ $X_6=0$ | $Y_1=0$ |
| $X_3=1$ $X_6=0$ | $Y_1=1$ |
| $X_3=0$ $X_6=1$ | $Y_1=1$ |
| $X_3=1$ $X_6=1$ | $Y_1=1$ |

TIME DELAY LADDER

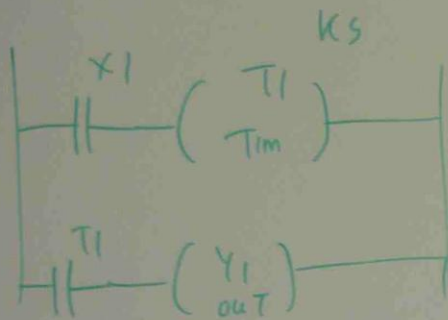pb) OUTPUT Y_1 OPERATES 0.5 SEC AFTER THE EXTERNAL SWITCH CONNECTED TO INPUT X_1 IS CLOSED.




INPUT X_1

OUTPUT Y_1

| IN | OUT |
|---------|---------|
| $X_1=0$ | $Y=0$ |
| $X_1=1$ | $Y_1=1$ |

SIMULATION

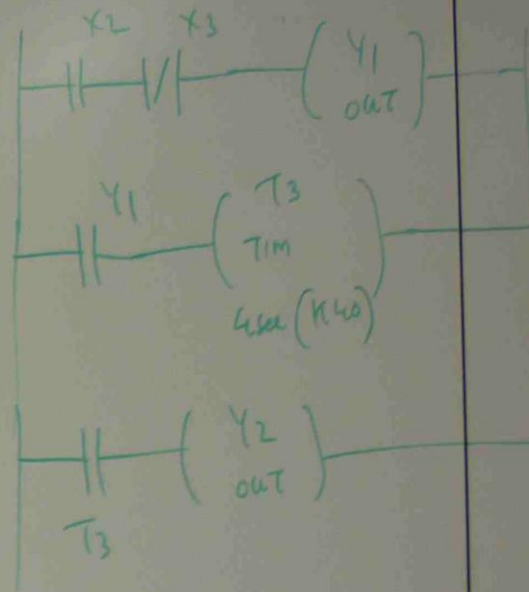pb) OUTPUT Y_1 OPERATES VIA A START BUTTON CONNECTED TO INPUT X_2 AND TURN OFF BY A STOP BUTTON CONNECTED TO INPUT X_3 . Y_2 SHOULD OPERATE VIA TIMER T_3 , 4 SEC AFTER Y_1 IS ENERGIZED. THE STOP BUTTON SHOULD TURN ALL OUTPUTS OFF.



INPUT X_2

X_3

OUTPUT Y_1

Y_2

TIMER T_3 4sec

