

I006 - PROCESS CONTROL

TRANSDUCERS, FLOW, PRESSURE, TEMPERATURE MEASUREMENT

SIGNAL CONDITIONING (ANALOG + DIGITAL)

SENSORS, PROCESS CONTROL SYSTEM, ELECTRONICS SIGNAL
AND SYSTEM, PROCESS CONTROLLERS,

PLC SYSTEM.

www.Power semester 4- zoom share.com

Analog Digital Signal Conditioning

Hobs_I006 Note 1 Sensor 1

— 2 Sensor 2

— 3 Sensor 3

Hobs_I006 Note 4 Control concept +
Note 5 — 2

Hobs_I006 Note 6 Electronic Signal

Note 8 Process control 1

— 9 Process control 2

PLC

PLC Textbook 1

PLC Textbook 2

PLC Textbook 3

PLC 6487 E. 21P

PLC REFERENCE

TRILOGIC PLC

USER MANUAL

SETUP TL6 Edu

INSTALLATION INSTRUCTION

I001 - INSTALL SETUP TRANSDUCERS AND SENSING DEVICES

I002 - SOLVE THE PROBLEMS IN PRESSURE MEASUREMENT

I004 - SOLVE THE PROBLEMS IN FLOW MEASUREMENT

I005 - SOLVE THE PROBLEMS IN TEMPERATURE
MEASUREMENT.

I002 + I004

I002 I004 PRESSURE Flow PNEUMATIC REFERENCE .zip

I005
I005 TEMPERATURE MEASUREMENT .zip

FIRST PART - TEMPERATURE
LIGHT


LATER PART - FLOW

PRINCIPLE OF ANALOG SIGNAL CONDITIONING

A SENSOR MEASURES A VARIABLE SIGNAL BY CONVERTING THE INFORMATION ABOUT THAT VARIABLE INTO A DEPENDENT SIGNAL OF EITHER ELECTRICAL (OR) PNEUMATIC NATURE.

ANALOG SIGNAL CONDITIONING PROVIDES THE OPERATION NECESSARY TO TRANSFORM A SENSOR OUTPUT INTO A FORM NECESSARY TO INTERFACE WITH OTHER ELEMENTS OF THE PROCESS CONTROL LOOP.

CONTROL

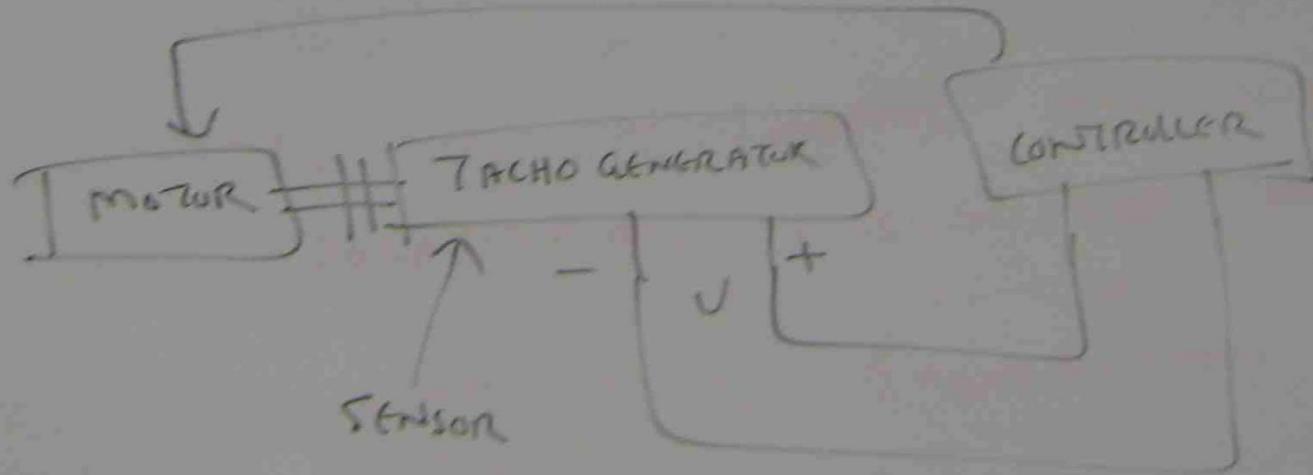

y = 2

CONTROL SIGNAL

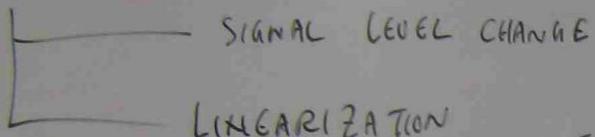


PHOTO CELL
LIGHT → VOLTAGE


$$V_i = V_0 e^{-\alpha I}$$

V_i = output voltage at intensity I

V_0 = zero intensity voltage

α = exponential constant

I = light intensity

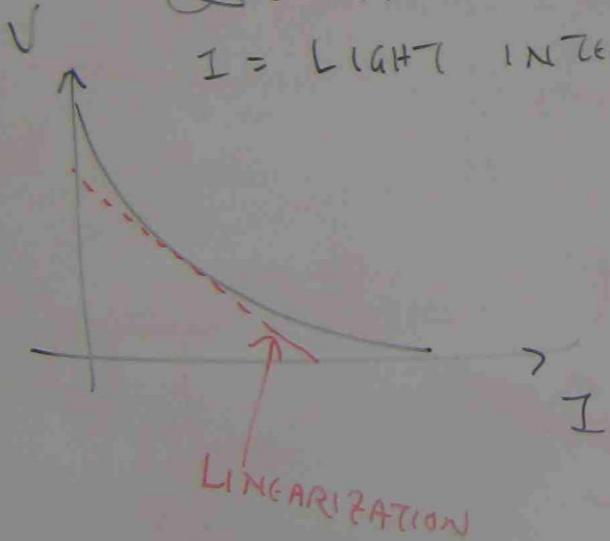

SIGNAL CONVERSION

LIGHT → PHOTOCELL → VOLTAGE

GAS → COMPRESSOR → PRESSURE
FORCE

MOTION → TACHO GENERATOR → VOLTAGE
ROTATIONAL
FORCE

HEAT → THERMOCOUPLE → MECHANICAL
TEMPERATURE

SIGNAL TRANSMISSION

THE SIGNAL IS TRANSMITTED OVER
ELECTRICAL WIRE, DATA BUSES
AND FED TO CONTROLLER.

SIGNAL CONVERSION

LIGHT \rightarrow PHOTOCELL \rightarrow VOLTAGE

Gas \rightarrow COMPRESSOR \rightarrow PRESSURE FORCE

MOTION ROTATIONAL \rightarrow TACHO GENERATOR \rightarrow VOLTAGE
FORCE

HEAT \rightarrow THERMO COUPLE \rightarrow MECHANICAL
TEMPERATURE movement

SIGNAL TRANSMISSION



THE SIGNAL IS TRANSMITTED OVER
ELECTRICAL WIRE, DATA BUSES
AND FED TO CONTROLLER.

DIGITAL INTERFACE

THE USE OF COMPUTER IN PROCESS CONTROL
REQUIRES CONVERSION OF ANALOG SIGNAL
IN TO DIGITAL FORMAT BY INTEGRATED
DEVICES CALLED ANALOG TO DIGITAL CONVERTER

PASSIVE CIRCUIT

BRIDGE AND DIVIDERS.

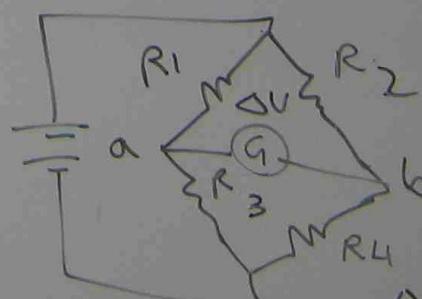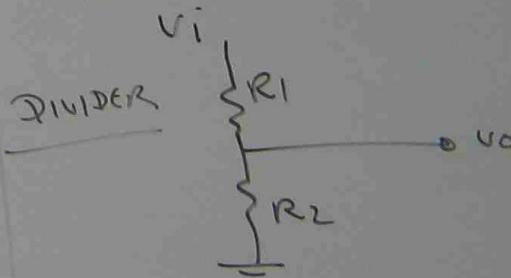

$$V_a = \frac{V R_3}{R_1 + R_3}$$

$$V_b = \frac{V R_4}{R_2 + R_4}$$

$$\Delta V = V_a - V_b$$

CONTROL SIGNAL



SIGNAL LEVEL CHANGE

LINEARIZATION

PHOTO CELL

LIGHT \rightarrow VOLTAGE


$$V_I = V_0 e^{-\alpha I}$$

V_I = OUT PUT VOLTAGE AT INTENSITY I

V_0 = ZERO INTENSITY VOLTAGE

α = EXPONENTIAL CONSTANT

I = LIGHT INTENSITY

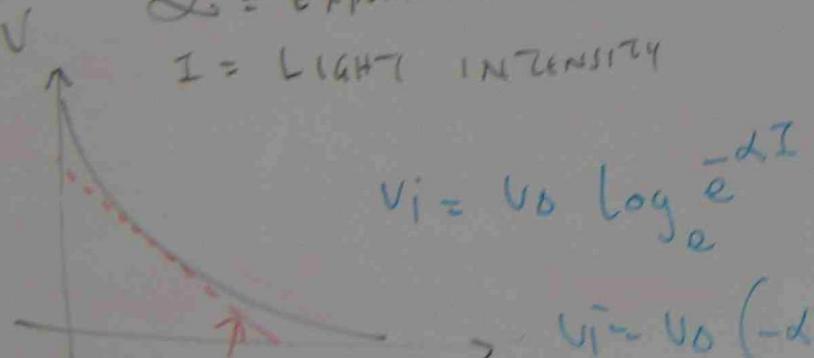

$$V_I = V_0 \log_e^{-\alpha I}$$

I

$$V_I \approx V_0 (-\alpha I)$$

LINEARIZATION

$$dB = 20 \log \frac{V_I}{V_0}$$

SIGNAL CONVERSION

LIGHT \rightarrow PHOTO CELL \rightarrow VOLTAGE

GAS \rightarrow COMPRESSOR \rightarrow PRESSURE
FORCE

MOTION \rightarrow TACHO GENERATOR \rightarrow VOLTAGE
ROTATIONAL
FORCE

HEAT \rightarrow THERMO COUPLE \rightarrow MECHANICAL
MOVEMENT
TEMPERATURE

SIGNAL TRANSMISSION

THE SIGNAL IS TRANSMITTED OVER
ELECTRICAL WIRE, DATA BUSES
AND FED TO CONTROLLER.

SIGNAL CONVERSION

LIGHT \rightarrow PHOTO CELL \rightarrow VOLTAGE

AIRS \rightarrow COMPRESSOR \rightarrow PRESSURE FORCE

MOTION \rightarrow TACHO GENERATOR \rightarrow VOLTAGE
ROTATIONAL FORCE

HEAT \rightarrow THERMO COUPLE \rightarrow MECHANICAL MOVEMENT
TEMPERATURE

SIGNAL TRANSMISSION


THE SIGNAL IS TRANSMITTED OVER
ELECTRICAL WIRE, DATA BUSES
AND FED TO CONTROLLER.

DIGITAL INTERFACE


THE USE OF COMPUTER IN PROCESS CONTROL
REQUIRES CONVERSION OF ANALOG SIGNAL
IN TO DIGITAL FORMAT BY INTEGRATED
DEVICES CALLED ANALOG TO DIGITAL CONVERTER.

PASSIVE CIRCUIT

BRIDGE AND DIVIDERS.

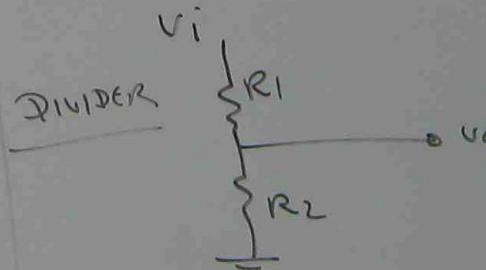
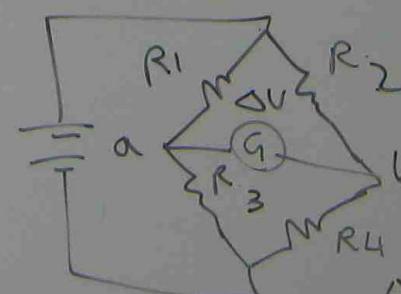
$$V_o = V_i \times \frac{R_2}{R_1 + R_2}$$




$$V_a = \frac{V R_3}{R_1 + R_3}$$

$$V_b = \frac{V R_4}{R_2 + R_4}$$

$$\Delta V = V_a - V_b$$

Pb

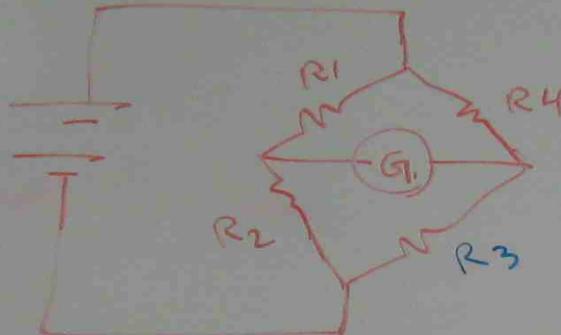

IN GIVEN WHEAT STONE BRIDGE, IF $R_1 = 1000\Omega$

$R_2 = 842\Omega$, $R_3 = 500\Omega$, FIND R_4

BALANCE

$$R_1 \times R_3 = R_2 \times R_4$$

$$1000 \times 500 = 842 \times R_4$$

$$R_4 = \frac{1000 \times 500}{842} =$$

GALVANOMETER DETECTOR

$$V_{th} = \sqrt{\frac{R_3 R_2 - R_1 R_4}{(R_1 + R_3)(R_2 + R_4)}}$$

$$R_{th} = \frac{R_1 R_3}{R_1 + R_3} + \frac{R_2 R_4}{R_2 + R_4}$$

$$\rightarrow I_A = \frac{V_{th}}{R_{th} + R_A}$$

OFFSET CURRENT

ph


A BRIDGE CIRCUIT HAS $R_1 = R_2 = R_3 = 2 \text{ k}\Omega$ RESISTANCES, $R_4 = 2.03 \text{ k}\Omega$ 5V SUPPLY. THE BRIDGE IS NULL. IF A GALVANOMETER WITH $50 \text{ }\mu\text{A}$ INTERNAL RESISTANCE IS USED FIND THE OFFSET CURRENT.

$$V_{Th} = \frac{R_3 R_2 - R_1 R_4}{(R_1 + R_3)(R_2 + R_4)}$$
$$= 5 \frac{(2 \times 2) - (2 \times 2.03)}{(2+2)(2+2.03)}$$
$$= -30.9 \text{ mV}$$

$$R_{Th} = \frac{R_1 R_3}{R_1 + R_3} + \frac{R_2 R_4}{R_2 + R_4}$$
$$= \frac{2 \times 2}{2+2} + \frac{2 \times 2.03}{2+2.03}$$
$$= 2.01 \text{ k}\Omega$$

$$I_g = \frac{V_{Th}}{R_{Th} + R_g}$$
$$= \frac{-30.9 \text{ mV}}{2.01 \text{ k}\Omega + 0.05 \text{ k}\Omega}$$
$$= -15 \mu\text{A}$$

TRIGGER CONTROL

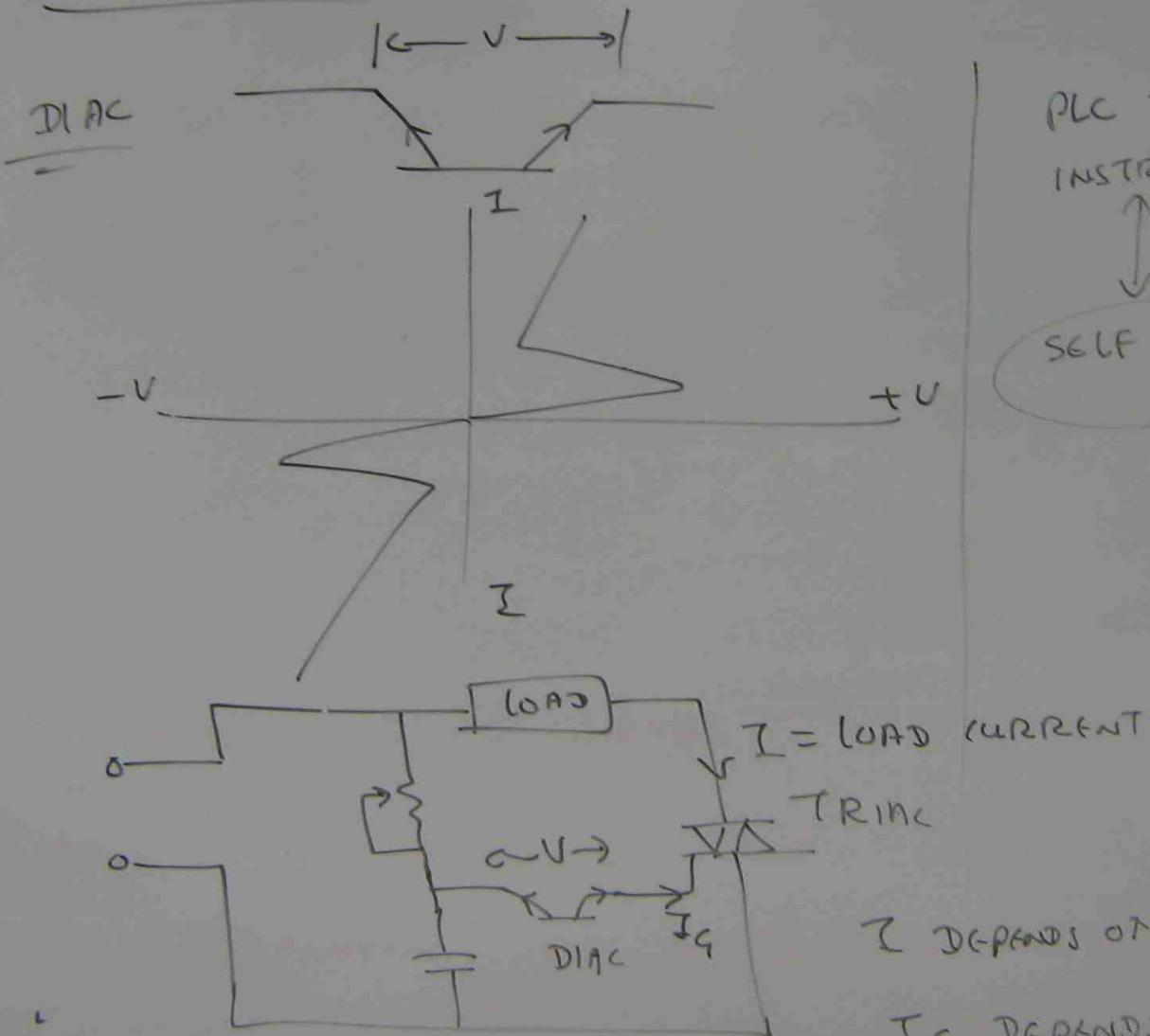

PLC TL31 U3

INSTRUCTION

SELF STUDY

WEEK

1, 2, 3

4, 5,

6, 7, 8

9, 10

9, 10

WEEK	PERIOD		TOPIC
	1 1→3	2 3→4:30	
1, 2, 3	✓	✓	ANALOG SIGNAL CONDITIONING + TEMPERATURE PRESSURE MEASUREMENT
4, 5,	✓	✓	DIGITAL (2)
6, 7, 8	✓	✓	DIGITAL SIGNAL PROCESSING
9, 10	✓		ELECTRONICS SIGNAL
9, 10		✓	PROCESS CONTROL

PLC TL31 V3

INSTRUCTION



SELF STUDY

+U

= LOAD CURRENT

TRIAC

2 DEPENDS ON Ig

Ig DEPENDS ON V

Em

B

GUIDELINES FOR ANALOG SIGNAL CONDITIONING DESIGN

(1) DEFINE THE MEASUREMENT OBJECTIVES

(a) PARAMETER

WHAT IS THE NATURE OF MEASURED VARIABLE:

PRESSURE, TEMPERATURE, FLOW, LEVEL, VOLTAGE,
CURRENT, RESISTANCE ETC?

(b) RANGE

WHAT IS THE RANGE OF THE MEASUREMENT?

(c) ACCURACY


WHAT IS THE REQUIRED ACCURACY?

(d) LINEARITY


MUST THE MEASUREMENT OUT PUT BE LINEAR?

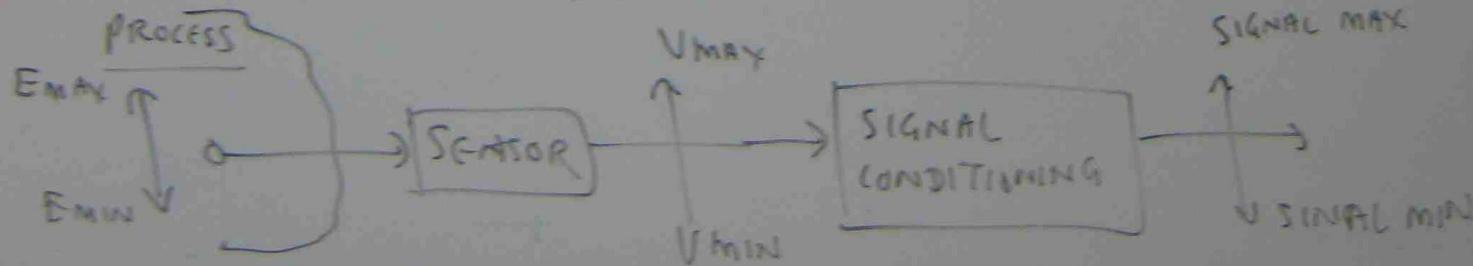(e) NOISE


WHAT IS THE NOISE LEVEL AND FREQUENCY SPECTRUM
OF THE MEASUREMENT ENVIRONMENT?



AC BRIDGES

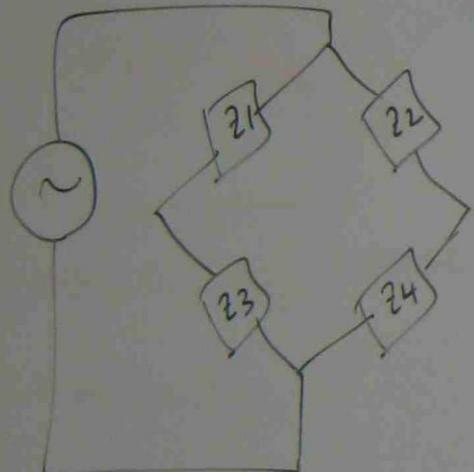

$$Z_1 Z_4 = Z_3 Z_2$$

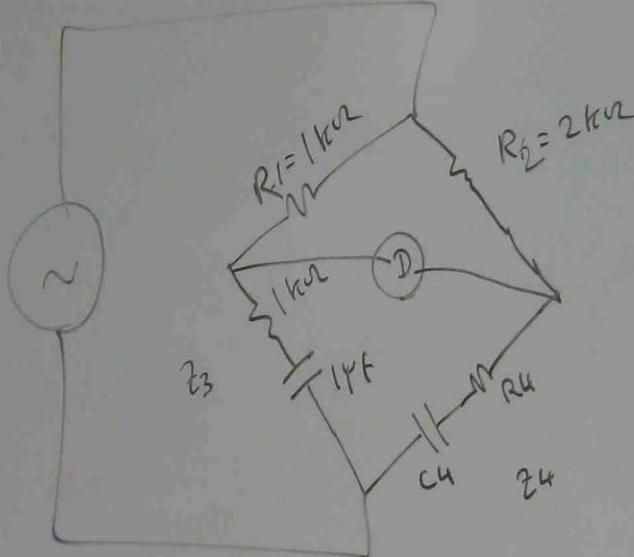

CALCULATE R_4 & C_4

$$Z_1 Z_4 = Z_3 Z_2$$

$$R_1 \left(R_4 - j \frac{1}{\omega C_4} \right) = R_2 \left(R_3 - j \frac{1}{\omega C_3} \right)$$

$$R_1 R_4 - j \frac{R_1}{\omega C_4} = R_2 R_3 - j \frac{R_2}{\omega C_3}$$

$$R_1 R_4 = R_2 R_3$$

$$(1 \text{ k}\Omega)(R_4) = (2 \text{ k}\Omega)(1 \text{ k}\Omega)$$

$$R_4 = \frac{2 \times 1}{1} = 2 \text{ k}\Omega$$

$$-\int \frac{R_1}{\omega C_4} = -\int \frac{R_2}{\omega C_3}$$

$$\frac{R_1}{\omega C_4} = \frac{R_2}{\omega C_3}$$


$$\frac{R_1}{C_4} = \frac{R_2}{C_3}$$

$$\frac{1 \text{ k}\Omega}{C_4} = \frac{2 \text{ k}\Omega}{1 \mu F}$$

$$C_4 = \frac{1 \text{ k}\Omega \times 1 \mu F}{2 \text{ k}\Omega}$$

$$= \frac{1 \mu F}{2}$$
$$= 0.5 \mu F$$


HIGH PASS RC FILTER

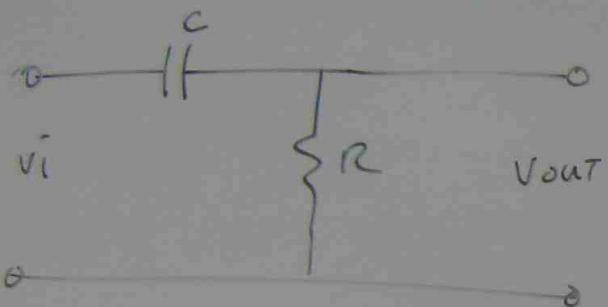

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{f/f_c}{1 + \left(\frac{f}{f_c}\right)^2}$$

f = ANY FREQUENCY

f_c = CUT OFF FREQUENCY

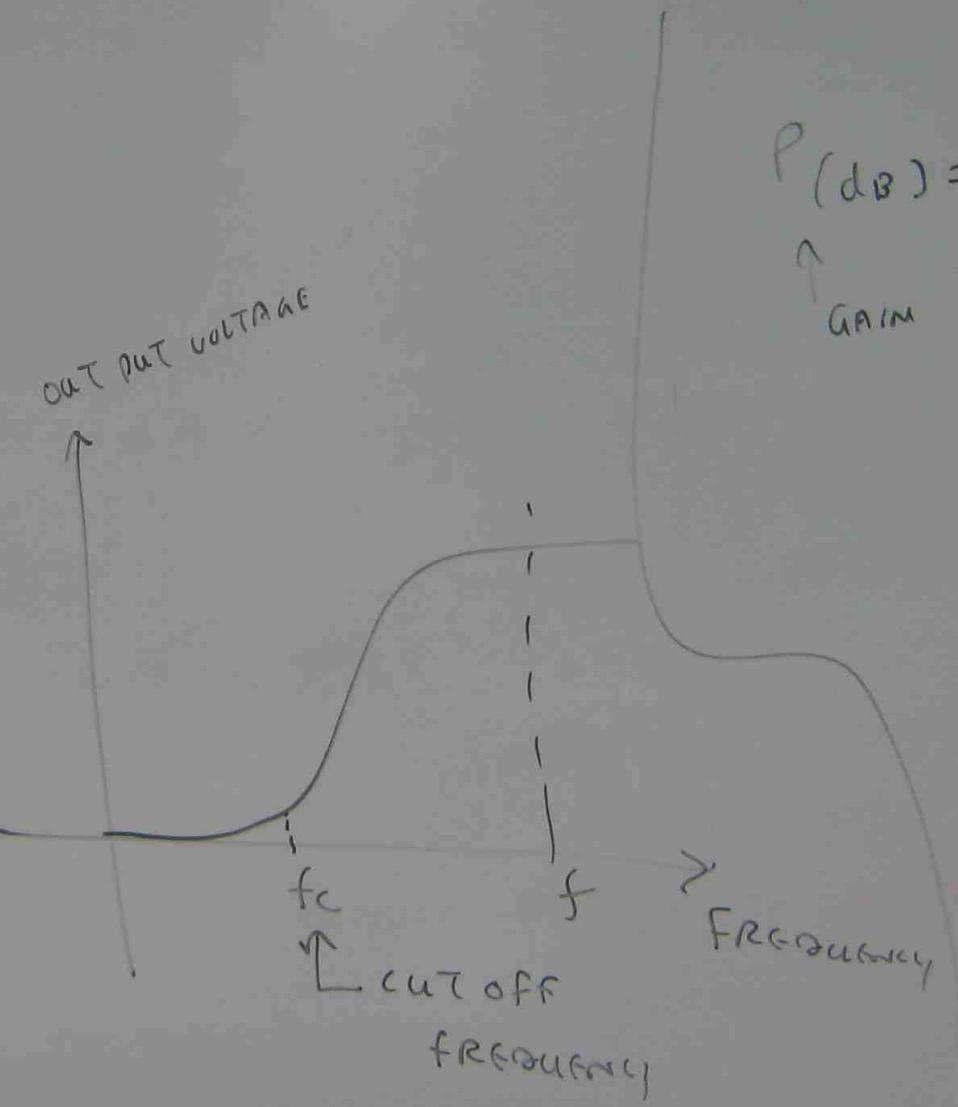

$$P_{dB} = 20 \log \frac{V_{out}}{V_{in}}$$

↑
GAIN IN DECIBEL UNIT (dB)

Pb PULSES FOR STEPPING MOTOR
 ARE BEING TRANSMITTED AT 2000Hz
 DESIGN A FILTER TO REDUCE 60Hz
 NOISE, BUT REDUCE THE PULSES BY
 NO MORE THAN 3dB

2 Frequency

$$P_{dB} = 20 \log \frac{V_{out}}{V_{in}}$$

$$-3dB = 20 \log \frac{V_{out}}{10V_{in}}$$

$$-\frac{3}{20} = \log \frac{V_{out}}{10V_{in}}$$

$$-0.15 = \log \frac{V_{out}}{10V_{in}}$$

$$\frac{V_{out}}{V_{in}} = 10^{-0.15}$$

$$\frac{V_{out}}{V_{in}} = 0.707$$

$$\frac{V_{out}}{V_{in}} = \frac{f/f_c}{\sqrt{1 + \left(\frac{f}{f_c}\right)^2}}$$

$$\frac{V_{out}}{V_{in}} = \frac{60/2000}{\sqrt{1 + \left(\frac{60}{2000}\right)^2}}$$

$$= 0.03$$

ONLY 3% OF 60Hz NOISE REMAIN

IF INPUT VOLTAGE IS REDUCED TO
70.7%, NOISE WILL BE 3dB

IF INPUT VOLTAGE IS REDUCED TO 3%.
NOISE CAN BE ELIMINATED.

OPERATION PROCEDURE for PLC

TL 31 V3 SOFTWARE

PLC 6487 E - ZIP

DOWNLOAD ZIP FILE & EXTRACT THE FILES.

DIRECTORY

TL 31 ← (ENTER)

YOU CAN ACCESS THE
PLC PROGRAM
MAIN PAGE


PRESS ANY KEY

TO START THE PROGRAM

FILE - LOAD - PC3 - SELECT PC3 <ENTER>


YOU CAN REACH MAIN PROGRAM PAGE

TO DRAW LADDER DIAGRAM

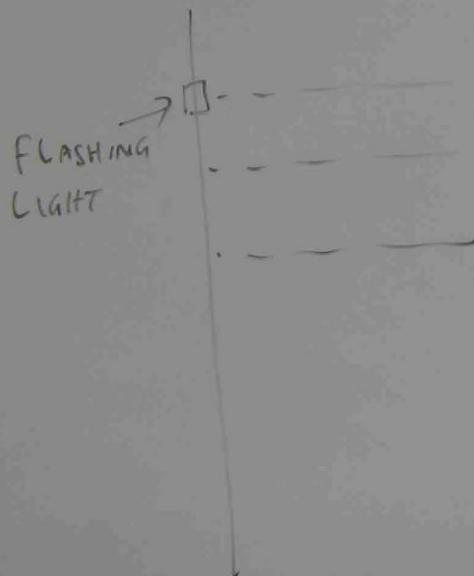

To DRAW PLC CONTROL PROGRAM

IT IS REQUIRED TO ALLOCATE INPUT, OUTPUT, RELAY, TIMER AND COUNTER.

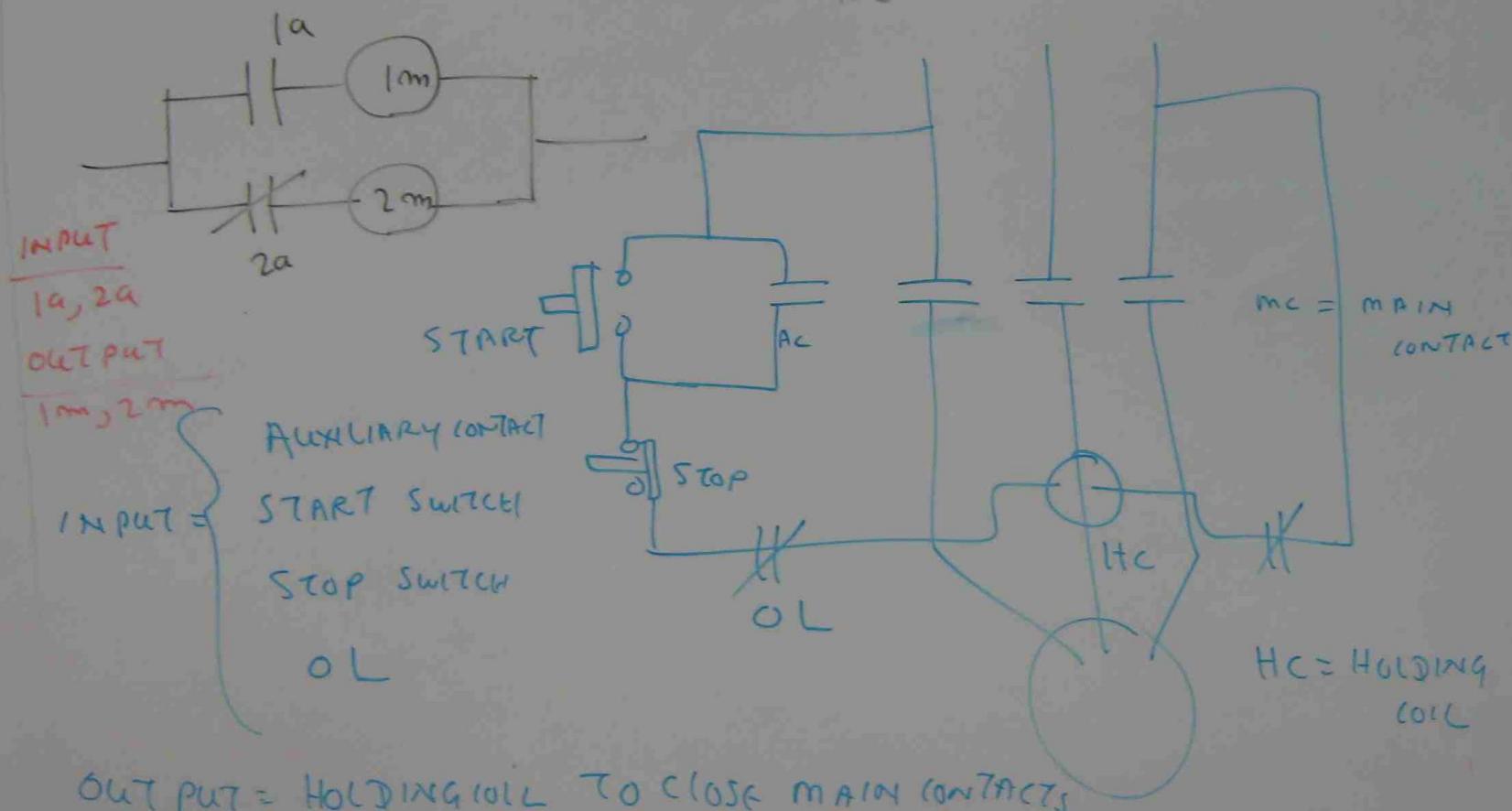

TL 31

INPUT — PRESS f2 →

OUTPUT — PRESS f3 →

RELAY — PRESS f4 →

TIMER — PRESS f5 →

COUNTER — PRESS f6 →

INPUT NUMBER	LABEL	CH BIT
--------------	-------	--------

OUTPUT NUMBER	LABEL	CH BIT
---------------	-------	--------

RELAY NUMBER	LABEL	CH. BIT
--------------	-------	---------

TIMER NUMBER	LABEL	CH. BIT
--------------	-------	---------

COUNTER NUMBER	LABEL	CH. BIT
----------------	-------	---------

STEP

H BIT


H BIT

CH. BIT

CH. BIT

CH. BIT


EXAMPLE

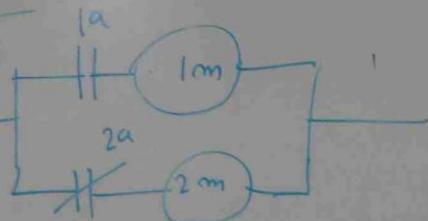

CLOSE 1a, 1m ENERGIZED

THEN 1m OPENS 2a

THEN 2m IS BE ENERGIZED.

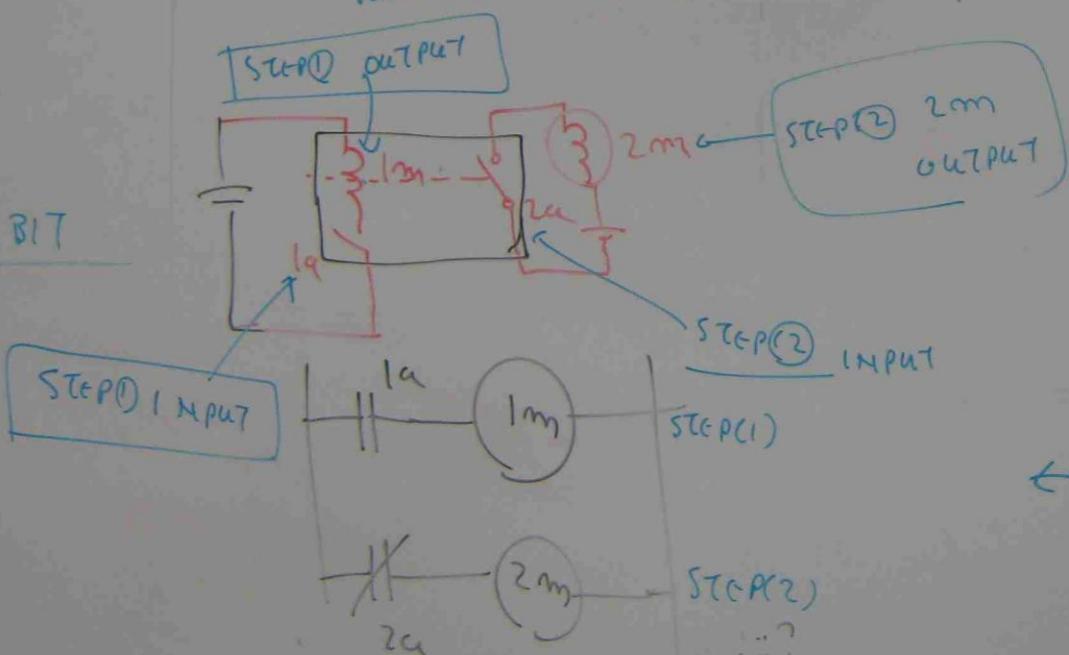

INPUT
1a, 2a

OUTPUT
1m, 2m

PROGRAM IN

PRESS F2

TYPE 1a

TYPE 2a


ES


PROGRAM OUT

PRESS F3

TYPE

TYPE

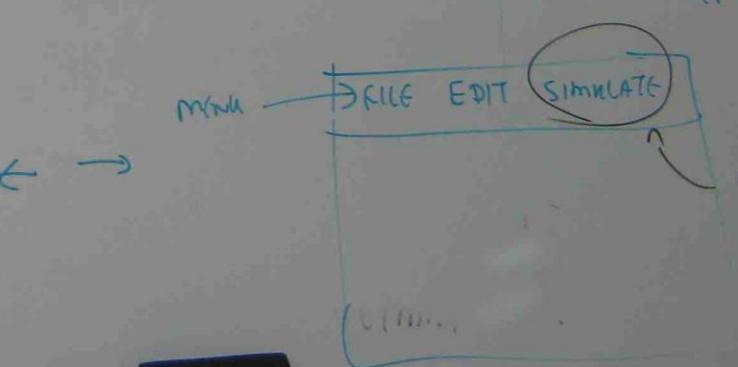


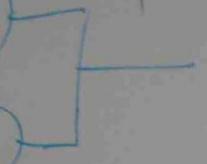

1 ENERGIZED

2 ENS 2a

3 DE ENERGIZED.

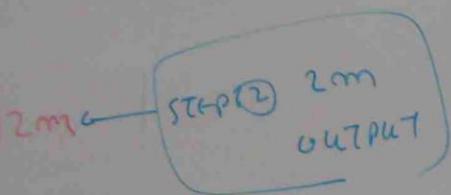

STEP(2) INPUT

STEP(1)

STEP(2)



PROGRAM INPUT		LABEL	CH. BIT
PRESS F2	INPUT NUMBER		
TYPE 1a <ENTER>			
TYPE 2a <ENTER>			
ESC			

PROGRAM OUTPUT

PROGRAM OUTPUT		LABEL	CH. BIT
PRESS F3	OUTPUT NUMBER		
TYPE 1m <ENTER>			
TYPE 2m <ENTER>			

ESC

ENTER → You will see

CIRCUIT PERFORMANCE.

TL 31

INPUT — PRESS f2 →
 OUTPUT — PRESS f3 →
 RELAY — PRESS f4 →
 TIMER — PRESS f5 →
 COUNTER — PRESS f6 →

INPUT NUMBER	LABEL	CH. BIT
--------------	-------	---------


OUTPUT NUMBER	LABEL	CH. BIT
---------------	-------	---------

RELAY NUMBER	LABEL	CH. BIT
--------------	-------	---------

TIMER NUMBER	LABEL	CH. BIT
--------------	-------	---------

COUNTER NUMBER	LABEL	CH. BIT
----------------	-------	---------


Example

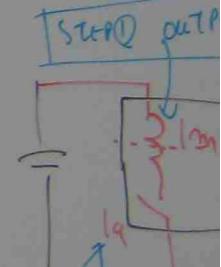

STEP0 INPUT

1a
2a
3a
4a


EXAMPLE

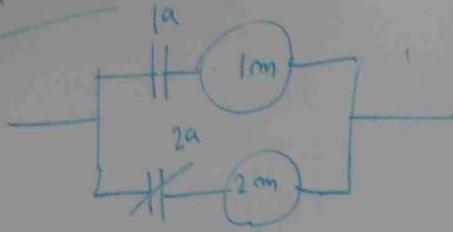

CLOSE 1a, 1m ENERGIZED

THEN 1m OPENS 2a

THEN 2m IS @ E ENERGIZED

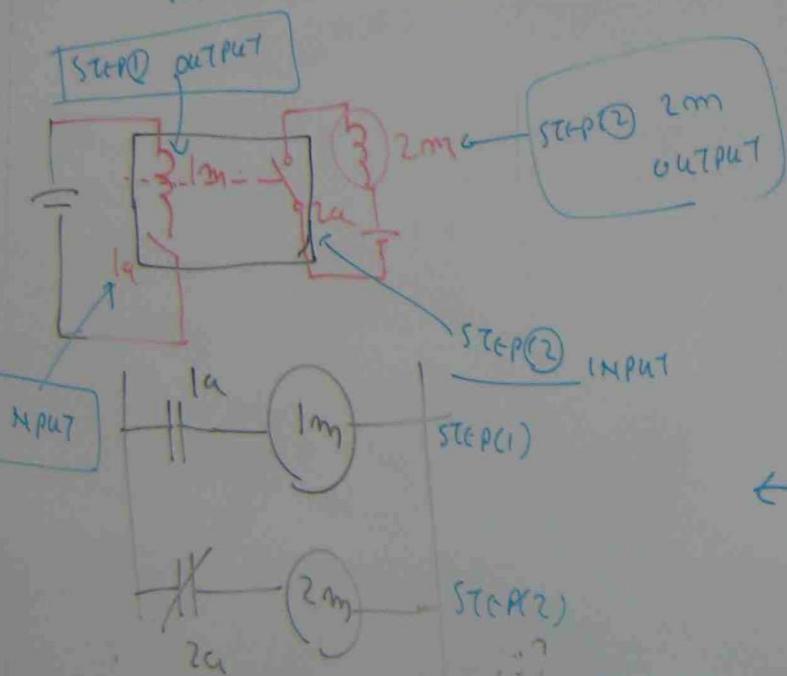

INPUT
1a, 2a

OUTPUT
1m, 2m

PROGRAM INPUT

PRESS F2

INPUT NUMBER

LABEL

CH. 017

TYPE 1a <ENTER>

TYPE 2a <ENTER>

ESC

PROGRAM OUTPUT

PRESS F3

OUTPUT NUMBER


LABEL

CH. 017

TYPE 1m <ENTER>

TYPE 2m <ENTER>


ESC

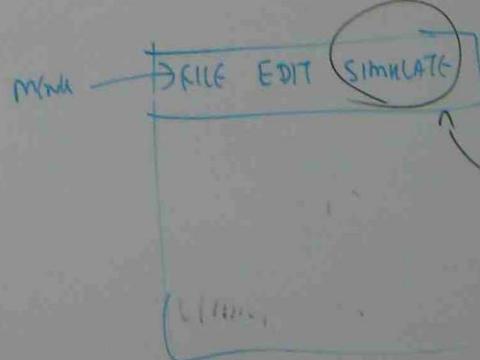

ENTER → YOU WILL SEE
CIRCUIT PERFORMANCE

LADDER DIAGRAM

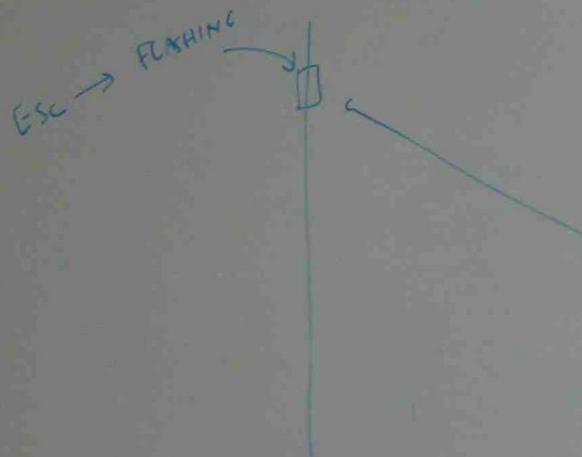PRESS ESC UNTIL FLASHING occurs ON VERTICAL
MARGIN LINE FOR DRAWING



WHEN FLASHING HAPPENS, PRESS SPACE BAR

TO INSERT COMPONENTS FOR DRAWING

VERTICAL
LINE




PRESS 1



PRESS 2



PRESS 3

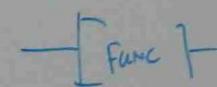

[func]



PRESS 4



PRESS 5




PRESS 6



()

PRESS 7

- FLASHING OCCURS ON VERTICAL
DRAWING

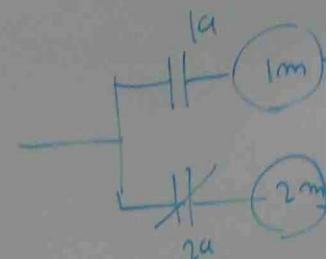

ESC - FLASHING

WHEN FLASHING HAPPENS, PRESS SPACE BAR

TO INSERT COMPONENTS FOR DRAWING



PRESS 1




PRESS 2



PRESS 3



PRESS 9

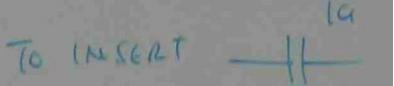

TO INSERT



PRESS 4




PRESS 5



PRESS 6




PRESS 7

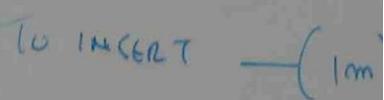

TO INSERT

(1m)

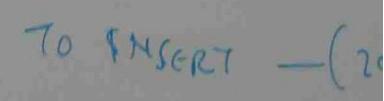


TO INSERT

(2m)

To SIMULATE - Esc

To CLOSE THE FILE

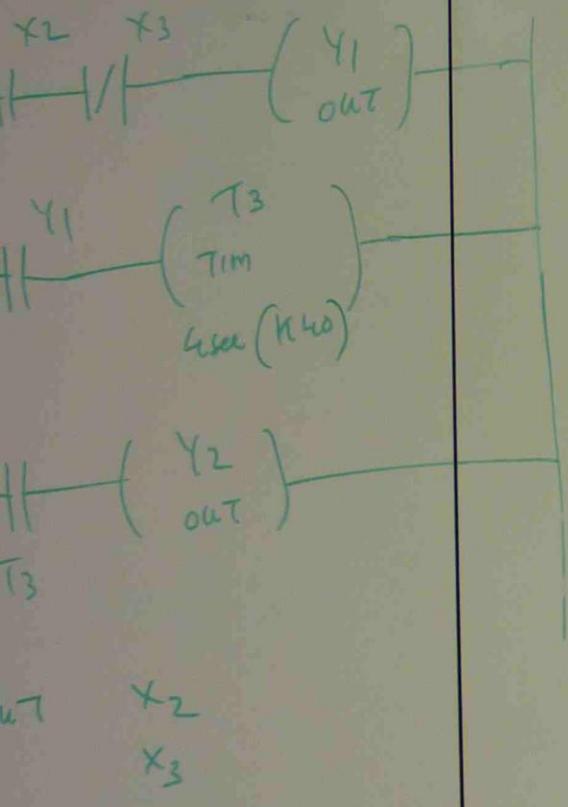

x_1
 x_2
 x_3
 7pu τ
 y_1
 y_2
 mfr T_3 4sec

SIMULATION

	$x_2 = 0$	$y_1 = 0$
I	$x_3 = 0$	$y_2 = 0$
	$x_2 = 1$	$y_1 = 1$
II	$x_3 = 0$	THEN 4sec $y_2 = 1$
	$x_2 = 1$	$y_1 = 0$
III	$x_3 = 1$	$y_2 = 0$