

## ENCODERS AND DECODER

### SERIAL DATA

A DATA TRANSFER METHOD IN WHICH EACH BIT IS FED SEQUENTIALLY OVER A SINGLE TRANSMISSION LINE

### PARALLEL DATA

A DATA TRANSFER METHOD WHERE DATA IS TRANSFERRED OVER A NUMBER OF LINES.


### ASCII CODE (AMERICAN STANDARD CODE FOR INFORMATION INTERCHANGE)

- 7 BIT CODE FOR ALL ALPHA NUMERIC CHARACTERS ON TYPE WRITER.
- USED FOR SENDING TEXT BETWEEN COMPUTERS, PRINTERS, WORD PROCESSORS ETC.

CHARACTER	ASCII CODE	
	BINARY	HEX
A	100 0001	41
B	100 0010	42
a	110 0001	61
0	011 0001	30
9	011 1001	39
SPACE	010 0000	20
 
## MULTIPLEXERS

A SPECIAL USE OF DECODER / ENCODER ICs IS MULTIPLEXING WHICH, IN AN ELECTRICAL SENSE, MEANS USING ONE DATA LINE TO TRANSMIT SEVERAL SIGNALS; APPARENTLY SIMULTANEOUSLY.




(4 POLES SINGLE WAY SWITCH)

MULTIPLEXING IS OFTEN USED IN COMPUTERS TO TRANSMIT DATA OVER A SINGLE LINE. (Eg. PRINTED CIRCUIT BOARD TRACK)

# MULTIPLIER (DATA SELECTOR)

- A FORM OF ENCODER

 


LOGIC DIAGRAM OF  
4 INPUTS  
MULTIPLIER.

# MULTIPLIER IC

TYPE	DEVICE	OUTPUT
QUAD 2 INPUT	74LS157	TRUE OUTPUT
QUAD 2 INPUT	74LS158	INVERTED
QUAD 2 INPUT	74LS257	TRUE
QUAD 2 INPUT	74LS258	INVERTED
QUAD 2 INPUT	74LS298	LATCHED
DUAL 4 INPUT	74LS153	TRUE
DUAL 4 INPUT	74LS253	TRUE
DUAL 4 INPUT	74LS352	INVERT
DUAL 4 INPUT	74LS353	INVERT
8 INPUT	74LS151	INVERT + TRUE
8 INPUT	74LS251	INVERT + TRUE
8 INPUT	74LS152	INVERT
16 INPUT	74150	INVERT

 TRANSFERRING DIGITAL DATA ALONG A  
COMMON DATA LINE  $\rightarrow$  USE MULTIPLEXER




A	B	C	Z
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

# FLIP FLOP

COMBINATIONAL LOGIC - MULTIPLEXER/DE-MULTIPLEXER (NO MEMORY)  
 OUTPUT REMAINS STEADY AS LONG AS INPUT CONDITIONS REMAIN CONSTANT


SEQUENTIAL LOGIC - UTILIZE MEMORY DEVICE  
 SEQUENTIAL DIGITAL SYSTEM.

 FUNDAMENTAL ELEMENT OF SEQUENTIAL LOGIC IS FLIP FLOP




TRUTH TABLE


INPUTS		OUTPUT		RESULT
S	R	Q	$\bar{Q}$	
INACTIVE	INACTIVE	X	X	NO CHANGE
ACTIVE	INACTIVE	1	0	SET
INACTIVE	ACTIVE	0	1	RESET
ACTIVE	ACTIVE	UNDEFINED	INVALID	

 

## NOR GATE SR FLIP FLOP

 


## NAND GATE SR FLIP FLOP

 

 
# NAND RS FLIP FLOP TO DEBOUNCE SWITCH

SINGLE POLE DOUBLE THROW TYPE (SPDT)

PULL UP RESISTORS  $\longrightarrow$  OPEN CIRCUIT INPUT IS LOGIC 1



DEBOUNCING SWITCH WITH NAND GATE

 


DEBOUNCING SWITCH WITH NOR GATE
 
## GATED SR LATCH $\rightarrow$ CLOCKED RS FLIP FLOP

THE BASIC SR FLIP FLOP RESPONDS TO ITS INPUTS DIRECTLY WHICH IN MANY INSTANCES CAUSE TIMING PROBLEMS.

TO OVERCOME THIS IS A CLOCKED SR FLIP FLOP USED TO STORE THE DATA. (STATE OF THE SET (OR) RESET TERMINALS) ONLY WHEN THE FLIP FLOP IS ENABLED BY ANOTHER SIGNAL CALLED CLOCK SIGNAL.




THE SR DATA IS PASSED ONTO FLIP FLOP ONLY WHEN THE GATE (OR) ENABLE SIGNAL IS A LOGIC 1. THE FLIPFLOP WILL STORE THE RS DATA EXISTING AT THE INSTANT THE ENABLE SIGNAL IS REMOVED.

## DEVELOPMENT OF FLIP FLOP

SR FLIP FLOP IS NOT A COMMONLY USED DEVICE BECAUSE IT HAS INVALID STATE.

D, T, K FLIP FLOPS ARE DEVELOPED TO OVERCOME THE PROBLEM


### D FLIP FLOP

 

### D FLIP FLOP TRUTH TABLE

	D	Q	Q <sub>next</sub>	
1	0	0	0	} RESET
2	0	1	0	
3	1	0	1	} SET
4	1	1	1	

### TOGGLE (T) FLIP FLOP

 

## J-K FLIP FLOP


THE J-K FLIP FLOP OVERCOMES THE PROBLEM OF THE POSSIBLE INVALID OUTPUT CONDITION IN S-R FLIP FLOP WHILE STILL RETAINING TWO INPUTS.

THE SET INPUT IS NOW J INPUT. THE RESET INPUT IS NOW THE K INPUT.


IF BOTH THE J AND K INPUTS ARE HELD AT A LOGIC 1, THE OUTPUTS WILL TOGGLE RATHER THAN BECOME INDETERMINATE

JK FLIP FLOP TRUTH TABLE

	J	K	Q	Q <sub>next</sub>	
1	0	0	0	0	} NO CHANGE
2	0	0	1	1	
3	0	1	0	0	} RESET
4	0	1	1	0	
5	1	0	0	1	} SET
6	1	0	1	1	
7	1	1	0	1	} TOGGLE
8	1	1	1	0	

 


JK FLIP FLOP  
(NEGATIVE EDGE TRIGGERED)

 

T FLIP FLOP  
FROM  
JK FLIP FLOP


## MASTER-SLAVE FLIP FLOP

 

CONNECTING CONVENTIONAL J-K FLIP FLOP  
CAN GIVE THE PROBLEMS DUE TO TIME DELAY

THE PROBLEMS CAN ARISE FROM THE FACT THAT

 ALTHOUGH THE FLIP FLOP CHANGES ON THE EDGE OF IT'S  
CLOCK SIGNAL, THERE IS A SMALL TIME INTERVAL  
BEFORE AND AFTER THE CLOCK EDGE DURING WHICH  
THE INPUT DATA MUST BE HELD STABLE. THESE TIMES  
ARE CALLED SETUP & HOLD TIMES RESPECTIVELY.



WHEN THE CLOCK IS HIGH

MASTER IS ENABLED, SLAVE IS DISABLED

MASTER OUTPUT WILL BE SET ACCORDING TO DATA

PRESENTS AT MASTER'S INPUT, SLAVE FLIP FLOP  
REMAINS UNCHANGED

WHEN THE CLOCK SIGNAL RETURNS TO ZERO

SLAVE FLIP FLOP WILL RESPOND TO THE OUTPUT OF MASTER.

TRUTH DIAGRAMS OF EDGE TRIGGERED  
FLIP FLOP AND MASTER SLAVE FLIP FLOP


INPUT			OUTPUT	
CLK	J	K	Q	$\bar{Q}$
↓	L	L	Q <sub>0</sub>	$\bar{Q}$ <sub>0</sub>
↓	H	L	H	L
↓	L	H	L	H
↓	H	H	TOGGLE	

EDGE TRIGGERED FLIP-FLOP

INPUT			OUTPUT	
CLK	J	K	Q	$\bar{Q}$
	L	L	Q <sub>0</sub>	$\bar{Q}$ <sub>0</sub>
	H	L	H	L
	L	H	L	H
	H	H	TOGGLE	

MASTER-SLAVE FLIP FLOP
 
# JK FLIP FLOP WITH ASYNCHRONOUS PRESET AND CLEAR



PR - PRESET  
CL - CLEAR

INPUTS					OUTPUTS	
PR	CL	CLK	J	K	Q	$\bar{Q}$
L	H	X	X	X	H	L
H	L	X	X	X	L	H
L	L	X	X	X	$H^*$	$H^*$
H	H	↓	L	L	$Q_0$	$\bar{Q}_0$
H	H	↓	H	L	H	L
H	H	↓	L	H	L	H
H	H	↓	H	H	TOGGLE	
H	H	H	X	X	$Q_0$	$\bar{Q}_0$

## SHIFT REGISTERS AND DATA LATCHES


FLIP FLOPS ARE USED IN A VARIETY OF APPLICATIONS INCLUDING THE LATCH AND SHIFT REGISTER FUNCTIONS.

FLIP FLOP → STORE 1 BIT OF DATA


LATCH → INTER CONNECTION OF FLIP FLOPS → CAN STORE SEVERAL BITS OF DATA

4 BIT LATCH → 4 FLIP FLOP - STORE 4 BIT DATA

2 BIT LATCH - STORE 2 BIT DATA

 



74 LS 75 4 BIT LATCH

 


74 LS 374 OCTAL D TYPE LATCH
  
## SHIFT REGISTER


MANY DIGITAL APPLICATIONS REQUIRE THAT BINARY DATA BE SHIFTED EITHER TO LEFT (OR) RIGHT



## 4 BIT SHIFT REGISTER - SHIFT RIGHT

 

## 4 BIT SHIFT REGISTER - SHIFT LEFT

 

COMMERCIAL SHIFT REGISTER ICs

TTL 74LS194, CMOS 4194 } 16 pin 4 REGISTERS

## COUNTERS

- COUNTERS CAN BE USED TO COUNT THE NUMBER OF ITEMS ON A CONVEYOR (OR) IF USED TO COUNT THE NUMBER OF PULSES FROM A SHAFT ENCODER CAN INDICATE THE ROTARY POSITION OF A SHAFT (OR) X-Y POSITION OF MACHINING BEDS
- FLIP FLOPS ARE CONNECTED AS COUNTERS
- COUNTER PRODUCES A SERIES OF BINARY NUMBERS STARTING AT A PRESET VALUE (OFTEN 0) CYCLING AT A RATE DETERMINED BY THE INPUT CLOCK.


DECIMAL	C	B	A
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

(LSB - LEAST SIGNIFICANT BIT)

3 BITS BINARY  
COUNTER


UP COUNTER

0 1 2 3

 


COMBINING ODD  
NUMBER OF NEGATIVE  
FUNCTION

(OR)

 


DOWN COUNTER

3 2 1 0

 

(COMBINING EVEN NUMBER  
OF NEGATIVE FUNCTION)


(OR)

 
 
## MODULUS OF A COUNTER

THE MODULUS OF A COUNTER REFERS TO THE NUMBER OF THE STATES THAT THE COUNTER CAN OUTPUT


0  $\rightarrow$  15 COUNTER HAS 16 STATES. IT IS MODULO 16 COUNTER



COUNTER ICs



TYPE	MODULUS	CLOCK FREQUENCY
74LS90	2x5	32 MHz
74LS92	2x6	32 MHz
74LS93	2x8	32 MHz
74LS390	2x5	40 MHz
4020	16384	10 MHz
4024	128	12 MHz

7 SEGMENT DISPLAY

 


# 7 SEGMENT DISPLAY

LCD DISPLAY

  


# MULTIPLEXED LCD DISPLAY

 


MULTIPLEXING 7 SEGMENT LCD DISPLAY.
 
## 4 BIT SHIFT REGISTER - SHIFT RIGHT PARALLEL OUT



## 4 BIT SHIFT REGISTER - SHIFT LEFT

 

COMMERCIAL SHIFT REGISTER ICs

TTL 74LS194, CMOS 4194 (16 pins 4 REGISTERS)

## COUNTERS


- COUNTERS CAN BE USED TO COUNT THE NUMBER OF ITEMS ON A CONVEYOR (OR) IF USED TO COUNT THE NUMBER OF PULSES FROM A SHAFT ENCODER CAN INDICATE THE ROTARY POSITION OF A SHAFT (OR) X-Y POSITION OF MACHINING BEDS
- FLIP FLOPS ARE CONNECTED AS COUNTERS
- COUNTER PRODUCES A SERIES OF BINARY NUMBERS STARTING AT A PRESET VALUE (OFTEN 0) CYCLING AT A RATE DETERMINED BY THE INPUT CLOCK.

DECIMAL	C	B	A
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1


(LSB - LEAST SIGNIFICANT BIT)

3 BITS BINARY COUNTER


UP COUNTER      0 1 2 3

 

 (COMBINING ODD  
NUMBER OF NEGATIVE  
FUNCTION)



DOWN COUNTER      3 2 1 0

 

(COMBINING EVEN NUMBER  
OF NEGATIVE FUNCTION)

