

Single & Three Phase Rotating Machines Test**PHILIPS Final Test (Combined Test 1 & 2) Time****allowed – 90 minutes****19 Pages in this Question Booklet****Student Feedback****TOTAL MARKS AVAILABLE**

				SECTION	Possible Marks	Actual Marks
The results of my performance have been discussed and explained to me.				A	30	
Student:		Date:		B	30	
If you would like to request a review of your results or if you have any concerns about your results, contact your teacher or head teacher.				C	31	
				D	27	
Teacher:		Date:		TOTAL	118	

Aids to be supplied by College: None**Instructions to Students:****Electronic devices are to be turned off and removed from your person.**

You cannot access an electronic device during this examination.

- All questions are to be answered in the space provided in this Question Booklet.
Answers to Section A – Multi-choice Questions, are to be recorded on the Answer Sheet attached to this Question Booklet.
- You are not to use any reference book in this examination.
 - The whole of this Question Booklet is to be handed to the Supervisor upon completion.

Aids permitted where indicated:

Standard Dictionaries	Bilingual Dictionaries	Technical Dictionaries	Programmable Calculators	Non-programmable Calculators	Mobile Phones	MP3 Players
No	Yes	No	No	Yes	No	No

SECTION A MULTIPLE CHOICE (30 Marks)

In the following statements one of the suggested answers is the most correct. Place the letter corresponding to this answer in the space provided on the answer sheet.

1. As load on an induction motor increases, the power factor of the stator supply usually:
 - A. remains unchanged
 - B. increases the rotor power factor
 - C. increases
 - D. Decrease

2. The resistance of the insulation between windings and motor core should be:
 - A. Greater than $1M\Omega$
 - B. Less than $1M\Omega$
 - C. Greater than 1Ω
 - D. Less than 1Ω

3. The speed of a squirrel cage induction motor:
 - A. decreases with load
 - B. increases with load
 - C. is constant irrespective of load
 - D. is inversely proportional to the frequency of the supply

4. Slots on a stator or rotor of an induction motor may be skewed to:
 - A. provide a smoother starting torque
 - B. reduce starting current
 - C. increase the speed
 - D. increase the starting torque

5. Rotor currents in an induction motor operating at normal speed are:
 - A. low frequency
 - B. high frequency
 - C. supply frequency
 - D. stator frequency

6. Service & Installation rules NSW sets limitations on maximum starting currents for motors to prevent;
 - A. excessive demand during peak times
 - B. excessive strain on distribution transformers
 - C. fluctuations on supply voltages
 - D. non compliance with environmental & sustainability policy

7. The frequency produced by an alternator depends upon the :
 - A. value of field current
 - B. speed of rotation
 - C. value of stator current
 - D. value of terminal voltage

8. When resistance is added to the rotor circuit of a slip ring induction motor driving a constant load, the speed will:
 - A. remain the same and supply more torque
 - B. remain the same and draws more current
 - C. be reduced
 - D. be increased

9. Failure of one phase of a 3phase supply while a motor is running will cause it to;
 - A. run normally
 - B. over speed
 - C. overheat
 - D. increase the supply voltage

10. The setting on a thermal overload is adjusted to:
 - A. the full load current of the motor
 - B. 150% of the motor full load current
 - C. 200% of the motor full load current
 - D. anywhere within the adjustment range

11. The maximum efficiency of an induction motor usually occurs:
 - A. when the stator losses equal the rotor losses
 - B. at starting
 - C. at almost full load
 - D. when slip is 50%

12. The rotor field of a three phase induction motor is due to:
- A. DC excitation
 - B. electromagnetic induction
 - C. rotor reactance
 - D. rotor resistance
13. The rotating magnetic field of an induction motor has:
- A. constant speed but strength decreases with more load
 - B. a speed loss and a loss in strength with increased load
 - C. constant strength and speed
 - D. constant strength but speed decreases with greater load
14. If the setting on a thermal overload is set to the maximum possible adjustment, the overload will:
- A. operate correctly
 - B. not provide effective protection
 - C. only protect on low currents
 - D. protect for short circuits as well
15. The frequency of the rotor currents in an induction motor:
- A. increases when the speed increases
 - B. decreases when the slip increases
 - C. increases when the slip increases
 - D. decreases when the load increases
16. If a three phase 415 volt 50 hertz induction motor is connected to a 415 volt 100 hertz supply the:
- A. speed of the rotating magnetic field will double
 - B. speed of the rotating magnetic field will not be affected
 - C. speed of the rotating magnetic field will be halved
 - D. synchronous speed will be less than the actual speed
17. Alternators are designed to generate a sinusoidal voltage waveform because:
- A. it allows the use of cylindrical rotors
 - B. it allows alternators to be paralleled
 - C. this wave form can be transformed without distortion
 - D. greater voltages can be generated

18. A common method of starting modern synchronous motors is by:
- A. providing a commutator
 - B. induction motor principles
 - C. the help of a compensator
 - D. star/delta method
19. The maximum torque produced by an induction motor occurs when the:
- A. rotor resistance is greater than rotor reactance
 - B. rotor reactance is maximum
 - C. rotor resistance is minimum
 - D. rotor reactance equals rotor resistance
20. The most suitable test instrument used to measure the insulation between the “U” winding and the “W” winding of a three phase motor with all connections removed would be:
- A. an insulation resistance tester set to 1000 volts
 - B. an insulation resistance tester set to 500 volts
 - C. a digital multimeter set on $M\Omega$
 - D. an analogue multimeter set on ohms
21. The operating power factor of a synchronous motor can be varied by changing the:
- A. rotor speed
 - B. phase sequence
 - C. field polarity
 - D. field excitation
22. The armature current of a series universal motor is:
- A. less than the stator current
 - B. the same as the stator current
 - C. greater than the stator current
 - D. independent of the stator current
23. If the following single phase motors had identical power ratings, which one would produce the lower value of starting torque?
- A. split phase
 - B. shaded pole
 - C. capacitor start
 - D. Universal

24. The speed at which a synchronous motor rotates is governed by the:
- A. pony motor
 - B. field winding
 - C. exciter
 - D. supply frequency
25. A higher starting torque can be obtained with a split phase induction motor by:
- A. placing extra induction in series with each motor winding
 - B. connecting a capacitor in parallel with the motor
 - C. disconnecting the centrifugal switch
 - D. connecting a capacitor in series with the start winding
26. A shaded pole induction motor would be the most suitable motor for use in a:
- A. vacuum cleaner
 - B. desk fan
 - C. electric clock
 - D. washing machine
27. The single phase motor which is most suitable for driving a domestic vacuum cleaner would be a:
- A. series motor
 - B. capacitor start/capacitor run motor
 - C. shaded pole motor
 - D. resistance start motor
28. The single phase motor that has two similar windings with a capacitor in series with one, is the:
- A. split phase motor
 - B. capacitor start/capacitor run motor
 - C. permanently split capacitor motor
 - D. capacitor start motor
29. The advantages of a shaded pole motor are:
- A. good power factor and reasonable starting torque
 - B. low cost and simple construction
 - C. good efficiency and good power factor
 - D. low cost and good power factor
30. The single phase motor that has two dissimilar windings displaced 90 electrical degrees is the:
- A. series motor
 - B. permanently split capacitor motor
 - C. shaded pole motor
 - D. capacitor start motor

SECTION B – SHORT ANSWER (Marks 30)

1. What is the minimum number of phases required to produce a rotating magnetic field in the stator of a three phase induction motor?

2. Name the **2** factors that govern the speed of rotation of the rotating magnetic field produced by a three phase induction motor.

3. Name two types of overload protection relays?

4. State the two reasons why ‘Amortisseur windings’ or ‘Damping bars’ are fitted to the rotor of a synchronous motor.

5. Name the **2** fields that interact to provide torque.

6. How is the output voltage of a 3ph alternator altered?

7. Name the **2** metals commonly used for the rotor bars of squirrel cage rotors.

8. How can the direction of a three phase motor be reversed?

9. State the approximate angle of phase displacement between the start and run winding currents of a single phase split phase induction motor?

10. Describe the differences in resistance between the start and run winding of a split phase motor.

11. State the **2** methods used to isolate the start winding from the supply when a split phase motor reaches approx, 75% of running speed.

12. Describe how to reverse the rotation of a series universal motor.

13. What type of single phase motor is best suited to drive a reversible ceiling fan?

14. What type of single phase motor uses a commutator?

15. What will be the likely outcome if the centrifugal switch fails to open as a split phase motor accelerates?

SECTION C- DRAWINGS & DIAGRAMS - 3ph Machines (18 Marks)

1. Inspect the graph in figure 1 and determine

- a. Approximately at what percentage does the motor reach maximum torque? _____ (2 Marks)
- b. Does the graph show a variable or constant torque machine? _____ (1 Mark)
- c. What type of squirrel cage motor does the graph represent? _____ (2 Marks)

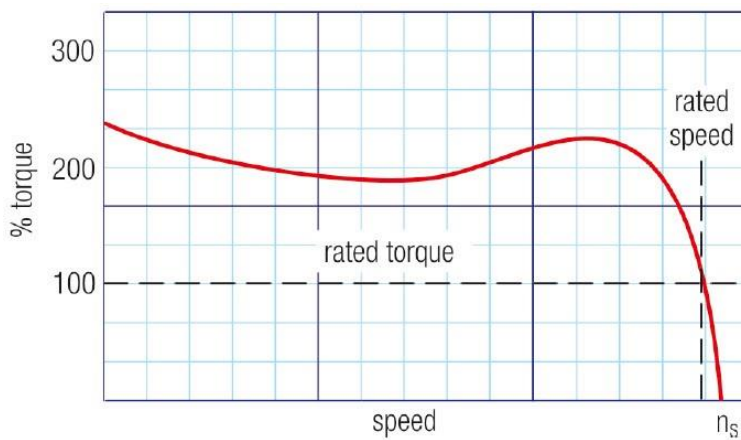


Figure 1

2. Inspect the graph in figure 2 and determine

- a. Explain why the torque is remaining constant at each stage? _____ (2Marks)
- b. What type of motor does the graph represent? _____ (2 Marks)


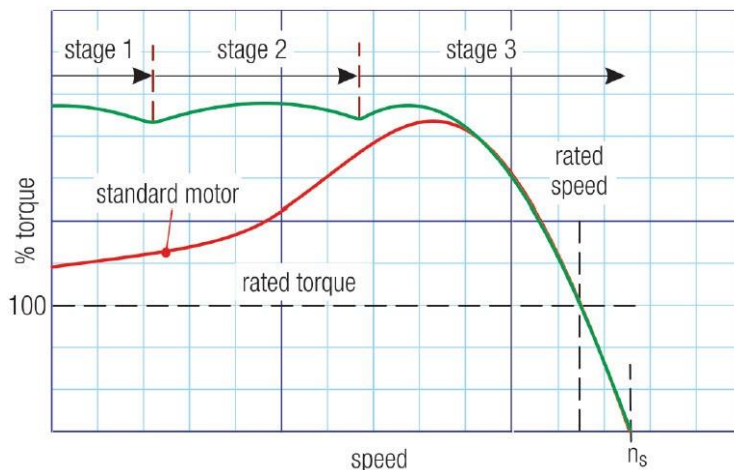


Figure 2

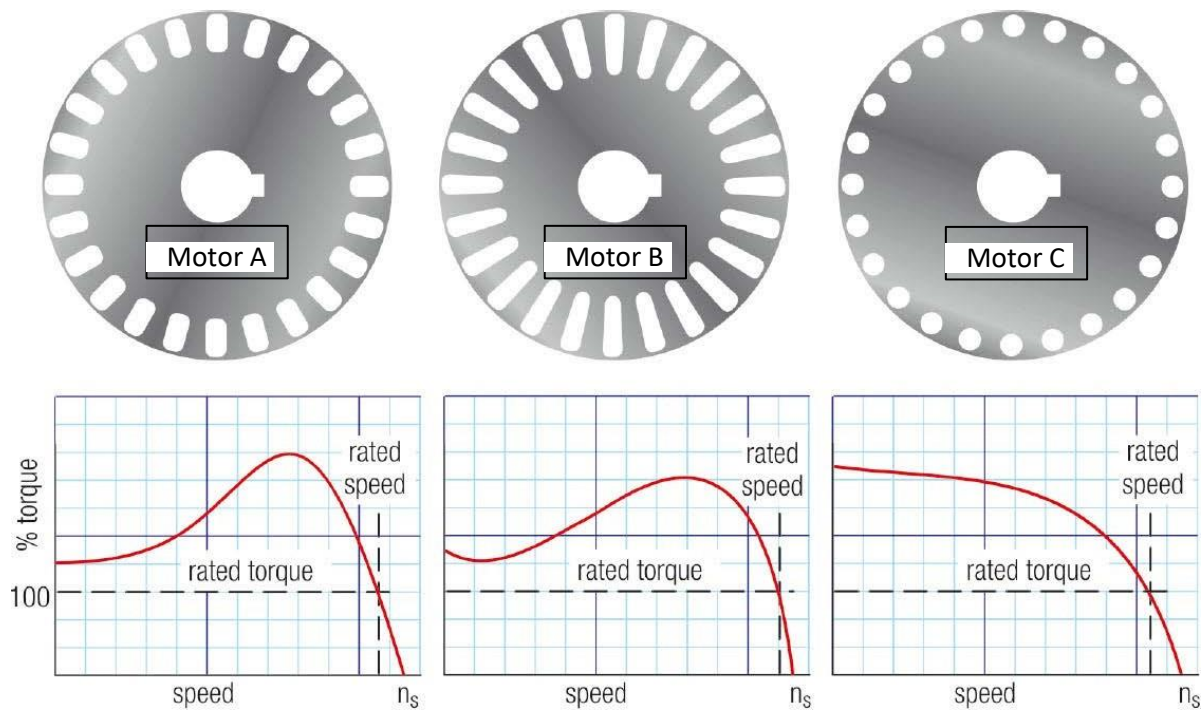3. Inspect the figure 3 below and match the design characteristics with the appropriate description.




- Which motor has the highest inductive reactance _____ (2)
- Which motor has the highest resistance _____ (2)
- Which motor has both low reactance and resistance _____ (1)

4. Name the following components




a. _____ (2 Marks)

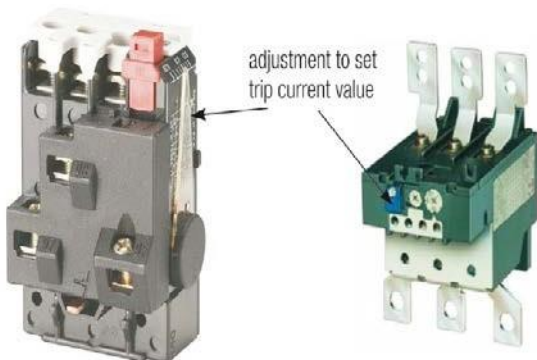

b. _____
 _____ (2 Mark)

SECTION C- DRAWINGS & DIAGRAMS - Single Machines (13 Marks)

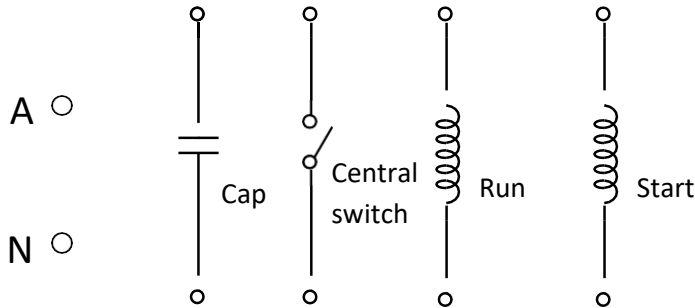1. Parts A, B, and C relate to the following diagram which represents the components of a single phase 'capacitor start' induction motor.




- (A) **On the diagram**, connect the components to the single phase terminals to give correct motor operation. (3marks)

- (B) What characteristic of this motor make it suitable for use in a refrigerator? (1mark)


- (C) How could the direction of rotation of this motor be reversed? (1mark)

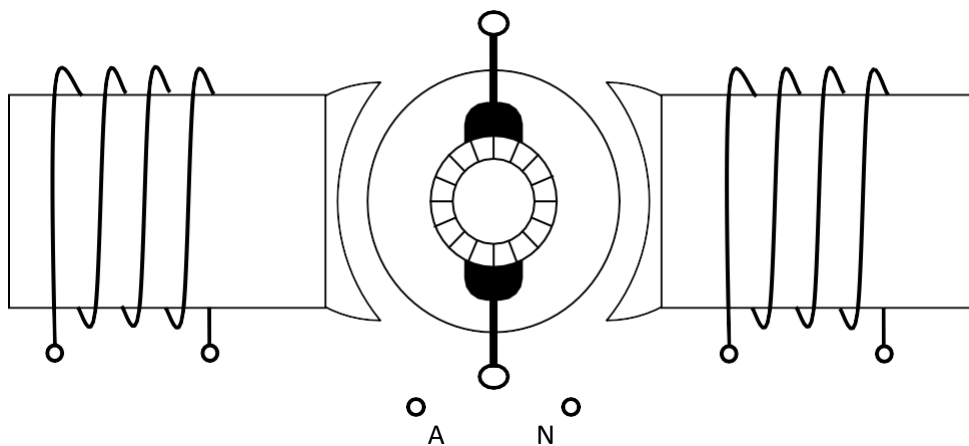2. On the diagram below draw the connections required for the correct operation of the series universal motor (3marks)




3. Name the two motors represented below

(2 Marks)

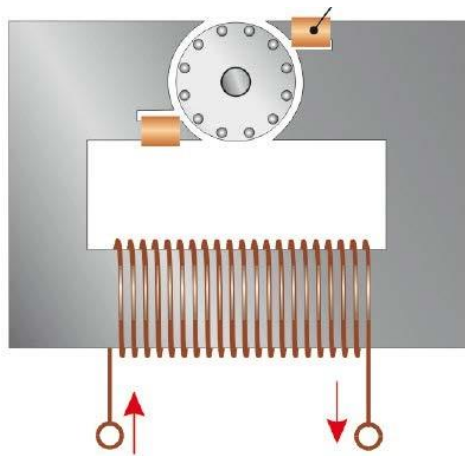


(A) _____

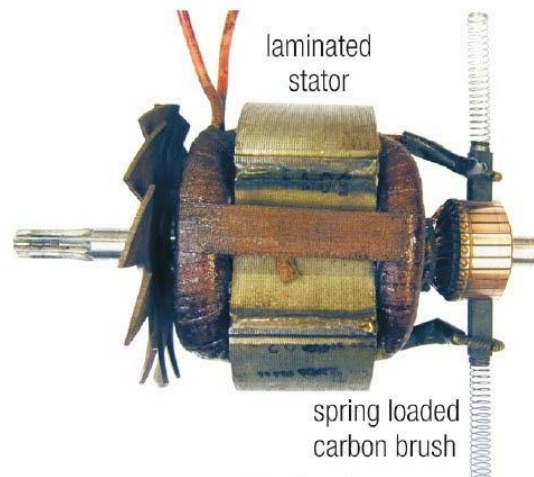


B _____

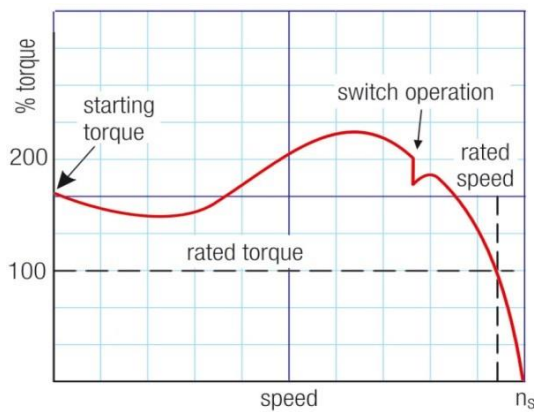6. Study the torque curves below and answer the following questions



Graph A

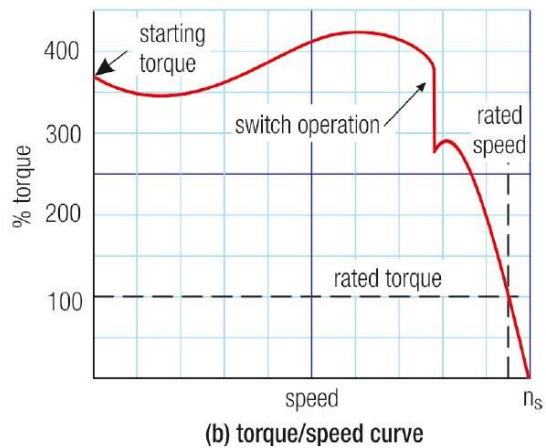

Graph B

a. Which graph represents a single phase motor which can be reversed while running

_____ (1 Mark)

b. What motor design characteristics produces the torque curve represented by graph B

_____ (2Marks)

SECTION D- CALCULATIONS (27 Marks)

All working must be shown as marks are allocated for correct working.

1. Calculate the number of poles required to if the synchronous speed of a 50Hz induction motor is 750rpm.

Answer: _____

(3 Marks)

2. If a six pole, 50 Hz induction motor has a full load slip of 5%, what is the full load rotor speed?

Answer: _____

(4 Marks)

3. An induction motor has a synchronous speed of 1500rpm and a rotor speed of 1420rpm, calculate the %slip.

Answer: _____

(3 Marks)

4. If a 50 Hz induction motor operates with a slip % of 6%, calculate the frequency of the rotor current.

Answer: _____

(3 Marks)

5. Three phase induction motor on full voltage develops a starting torque at 180Nm
Determine the torque developed if the supply voltage is 65% of the rated value.

Answer: _____

(3 marks)

6. A 50Hz, induction motor is operating at 1475rpm driving a compressor. If the driving torque is 50Nm determine:

(a) Output power

(b) Efficiency if the input power is 8.2kW.

(4 marks)

7. At full load a three phase 11kV alternator supplies a current of 1335 amps. Determine the rated output of the alternator.

Answer: _____

(2 marks)

8. Determine the output current of a three phase 250kVA, 415V alternator which is supplying a load with a power factor of 0.75 lagging.

Answer: _____

(3 marks)

8. Calculate the kW output of a three phase 500kVA alternator when supplying a load with a power factor of 0.95.

Answer: _____

(2 marks)

Note: The symbols used on this sheet follow AS1046 pt 1. There are alternate recognised symbols in use. The list does not contain every equation used in the course. Transposition of equations will be necessary to solve problems

$$Q = It$$

$$v = \frac{s}{t}$$

$$a = \frac{\Delta v}{t}$$

$$F = ma$$

$$W = Fs$$

$$W = mgh$$

$$W = Pt$$

$$\eta\% = \frac{\text{output}}{\text{input}} \times \frac{100}{1}$$

$$I = \frac{V}{R}$$

$$P = VI$$

$$P = I^2 R$$

$$P = \frac{V^2}{R}$$

$$R_2 = \frac{R_1 A_1 l_2}{A_2 l_1}$$

$$R_h = R_c (1 + \alpha \Delta t)$$

$$R = \frac{\rho l}{A}$$

$$R_T = R_1 + R_2 + R_3$$

$$V_T = V_1 + V_2 + V_3$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$I_T = I_1 + I_2 + I_3$$

$$V_2 = V_T \frac{R_2}{R_1 + R_2}$$

$$I_2 = I_T \frac{R_1}{R_1 + R_2}$$

$$R_x = \frac{R_A R}{R_B}$$

$$C = \frac{Q}{V}$$

$$\tau = RC$$

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$C_T = C_1 + C_2 + C_3$$

$$C = \frac{A \epsilon_o \epsilon_r}{d}$$

$$F_m = IN$$

$$H = \frac{F_m}{l}$$

$$B = \frac{\Phi}{A}$$

$$\Phi = \frac{F_m}{S}$$

$$S = \frac{l}{\mu_o \mu_r A}$$

$$V = N \frac{\Delta \Phi}{\Delta t}$$

$$e = Blv$$

$$L = \frac{\mu_o \mu_r AN^2}{l}$$

$$L = N \frac{\Delta \Phi}{\Delta I}$$

$$V = L \frac{\Delta I}{\Delta t}$$

$$\tau = \frac{L}{R}$$

$$F = Bil$$

$$T = Fr$$

$$E_g = \frac{\Phi Z n P}{60 a}$$

$$P = \frac{2 \pi T}{60}$$

$$t = \frac{1}{f}$$

$$f = \frac{n p}{120}$$

$$V = 0.707 V_{\max}$$

$$I = 0.707 I_{\max}$$

$$V_{\text{ave}} = 0.637 V_{\max}$$

$$I_{\text{ave}} = 0.637 I_{\max}$$

$$v = V_{\max} \sin \phi$$

$$i = I_{\max} \sin \phi$$

$$I = \frac{V}{Z}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$X_L = 2 \pi f L$$

$$X_C = \frac{1}{2 \pi f C}$$

$$\cos \phi = \frac{P}{S}$$

$$S = VI$$

$$f_o = \frac{1}{2\pi\sqrt{LC}}$$

$$S = \sqrt{3}V_L I_L$$

$$\tan \phi = \sqrt{3} \left(\frac{W_2 - W_1}{W_2 + W_1} \right)$$

$$V' = 4.44\Phi f N$$

$$N_{syn} = \frac{120f}{P}$$

$$V_{reg} \% = \frac{(V_{NL} - V_{FL})}{V_{FL}} \times \frac{100}{1}$$

$$I_{ST} = \frac{1}{3} \times I_{DOL}$$

$$T_{ST} = \left(\frac{V_{ST}}{V} \right)^2 \times T_{DOL}$$

$$E = \frac{\Phi_v}{A}$$

$$V_L = 0.45V_{ac}$$

$$V_L = 1.35V_{line}$$

$$PRV = 2.45V_{ac}$$

$$V_{ripple} = 0.1895V_{line}$$

$$\cos \phi = \frac{R}{Z}$$

$$P = VI \cos \phi$$

$$V_L = \sqrt{3}V_P$$

$$P = \sqrt{3}V_L I_L \cos \phi$$

$$Q = mC\Delta t$$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$s\% = \frac{(n_{syn} - n)}{n_{syn}} \times \frac{100}{1}$$

$$V_{reg} \% = \frac{(V_{NL} - V_{FL})}{V_{NL}} \times \frac{100}{1}$$

$$T_{ST} = \frac{1}{3} \times T_{DOL}$$

$$I_{motor\ st} = \frac{\%TAP}{100} \times I_{DOL}$$

$$E = \frac{I}{d^2}$$

$$V_L = 0.9V_{ac}$$

$$PRV = \sqrt{2}V_{ac}$$

$$V_{ripple} = \sqrt{2}V_{ac}$$

$$S = \sqrt{P^2 + Q^2}$$

$$Q = VI \sin \phi$$

$$I_L = \sqrt{3}I_P$$

$$Q = \sqrt{3}V_L I_L \sin \phi$$

$$\frac{I_2}{I_1} = \frac{N_1}{N_2}$$

$$f_r = \frac{s\% \times f}{100}$$

$$T = \frac{\Phi ZIP}{2\pi a}$$

$$I_{ST} = \frac{V_{ST}}{V} \times I_{DOL}$$

$$I_{line\ st} = \left(\frac{\%TAP}{100} \right)^2 \times I_{DOL}$$

$$\eta_v = \frac{\Phi_v}{P}$$

$$V_L = 1.17V_{phase}$$

$$PRV = 2\sqrt{2}V_{ac}$$

$$V_{ripple} = 0.707V_{phase}$$

Student Name: _____

Class : _____

Date : _____

ANSWER SHEET

Section A (Multi-choice Questions)

Instructions:

Enter your personal details in the top right hand corner of this sheet.

Place an **X** in box of your choice. If you make a mistake, circle your answer ⊗ and choose again.

Question	A.	B.	C.	D.
1				
2				
3				
4				
5				
6				
7				
8				
9				
10				
11				
12				
13				
14				
15				
Totals				

Question	A.	B.	C.	D.
16				
17				
18				
19				
20				
21				
22				
23				
24				
25				
26				
27				
28				
29				
30				
Totals				