

[Dashboard](#) / [My courses](#) / [Electrical Fundamentals](#) / [TUTORIALS](#) / [Week 2 Quiz](#) / [Preview](#)

Started on Monday, 4 March 2024, 6:03 PM

State Finished

Completed on Monday, 4 March 2024, 6:03 PM

Time taken 12 secs

Marks 0.00/28.00

Grade 0.00 out of 10.00 (0%)

Question **1**

Not answered

Marked out of 1.00

In a parallel circuit the supply current is equal to the:

- a. total power multiplied by the supply voltage
- b. supply voltage divided by the resistance of any one branch
- c. sum of the branch currents
- d. ratio of the branch currents

Your answer is incorrect.

The correct answer is:

sum of the branch currents

Question **2**

Not answered

Marked out of 1.00

Connecting resistors in parallel produces the same general effect as:

- a. increasing the cross-sectional area of a conductor
- b. increasing the temperature of a metallic conductor
- c. increasing the length of a conductor
- d. decreasing the conductance of a conductor.

Your answer is incorrect.

The correct answer is:

decreasing the conductance of a conductor.

Question **3**

Not answered

Marked out of 1.00

When three 10Ω resistors are connected in parallel to each other, the voltage drop across each is:

- a. one third of the supply voltage
- b. supply voltage divided by 10
- c. supply voltage divided by 30.
- d. equal to the supply voltage

Your answer is incorrect.

The correct answer is:

equal to the supply voltage

Question **4**

Not answered

Marked out of 1.00

The lowest value of resistance in any parallel combination of resistors is always:

- a. (b) less than the equivalent resistance of the combination.
- b. (d) greater than the equivalent resistance of the combination
- c. (a) equal to the equivalent resistance of the combination.
- d. (c) dependent on voltage and current for its resistance.

Your answer is incorrect.

The correct answer is:

(d) greater than the equivalent resistance of the combination

Question **5**

Not answered

Marked out of 1.00

1. Twenty five resistors each with a resistance of $100\ \Omega$ are connected in parallel with each other. The equivalent resistance of the combination is:

- a. (d) $25\ \Omega$
- b. (a) $100\ \Omega$
- c. (c) $4\ \Omega$
- d. (b) $2500\ \Omega$

Your answer is incorrect.

The correct answer is:

(c) $4\ \Omega$

Question **6**

Not answered

Marked out of 1.00

1. A parallel circuit is defined as a circuit with:

- a. (c) only one current path
- b. (b) more than one current path
- c. (a) more than one resistor
- d. (d) more than one supply voltage

Your answer is incorrect.

The correct answer is:

(b) more than one current path

Question **7**

Not answered

Marked out of 1.00

1. If an extra parallel connected resistor is added to a circuit, the equivalent resistance of the circuit will:

(

- a. (a) increase
- b. (b) remain unchanged
- c. (c) decrease
- d. (d) cause the applied voltage to increase.

Your answer is incorrect.

The correct answer is:

(c) decrease

Question 8

Not answered

Marked out of 1.00

1. The voltage in a parallel circuit:

- a. (a) is the same in all parts of the circuit
- b. (d) increases with increase resistance.
- c. (b) decreases through the circuit from resistor to resistor
- d. (c) greater than the supply voltage

Your answer is incorrect.

The correct answer is:

(a) is the same in all parts of the circuit

Question 9

Not answered

Marked out of 1.00

1. The voltages in the parallel section of a series-parallel circuit:

- a. (d) decrease through the circuit from component to component
- b. (a) are affected by the circuit equivalent resistance
- c. (c) are the same across the parallel components
- d. (b) are difficult to determine

Your answer is incorrect.

The correct answer is:

(c) are the same across the parallel components

Question **10**

Not answered

Marked out of 1.00

1. If one resistor in the parallel section of a series-parallel circuit goes open circuit, the circuit power dissipation will:

- a. (b) decrease.
- b. (d) decrease to zero.
- c. (a) remain constant.
- d. (c) increase.

Your answer is incorrect.

The correct answer is:

(b) decrease.

Question **11**

Not answered

Marked out of 1.00

1. The power dissipation of any circuit:

- a. (b) equal to the product of the power dissipation of each resistor.
- b. (a) equal to the sum of the power dissipation of each resistor.
- c. (c) equal to the supply voltage squared times the circuit equivalent resistance.
- d. (d) depends on the circuit arrangement.

Your answer is incorrect.

The correct answer is:

(a) equal to the sum of the power dissipation of each resistor.


Question **12**

Not answered

Marked out of 1.00

In the circuit of figure 12, the supply current is equal to the:

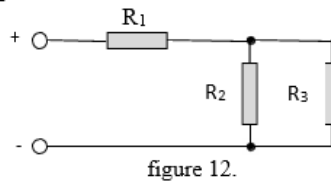- (a) value of branch currents.
- (b) product of the branch currents.
- (c) sum of the currents in each resistor.
- (d) sum of the branch currents.



+

-

- a. (d) sum of the branch currents.
- b. (a) value of branch currents.
- c. (c) sum of the currents in each resistor.
- d. (b) product of the branch currents.

Your answer is incorrect.

The correct answer is:

- (d) sum of the branch currents.


Question **13**

Not answered

Marked out of 1.00

For the circuit of figure 14, determine the -

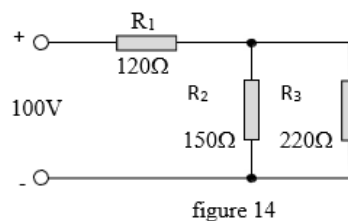- (a) equivalent circuit resistance
- (b) circuit current
- (c) voltage drop across resistor R₁
- (d) voltage drop across R₂ and R₃
- (e) currents in resistors R₂ and R₃
- (f) total power dissipated



- a. 209.19 Ohm / 0.478A/ 57.36V / 42.63V/ 0.284A, 0.193A/47.8W
- b. 109.19 Ohm / 1.478A/ 87.36V / 52.63V/ 1.284A, 0.193A/87.8W

Your answer is incorrect.

The correct answer is:

- 209.19 Ohm / 0.478A/ 57.36V / 42.63V/ 0.284A, 0.193A/47.8W


Question **14**

Not answered

Marked out of 1.00

For the circuit of figure 15, determine the –

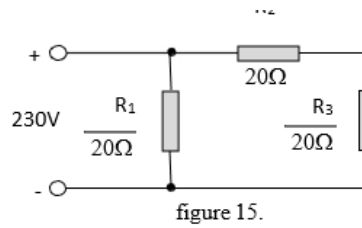- (a) equivalent resistance
- (b) current in each branch
- (c) supply current



- d power dissipated by each component (4408W, 863.3W, 647.47W)
- e total power dissipation

- a. 13.33 Ohm, 11.5A, 5.75A. 17.25A/ 2645W,661.25W,661.25W, 3967.5W
- b. 13.33 Ohm, 15A, 5A. 20A/ 2645W,661.25W,661.25W, 3967.5W

Your answer is incorrect.

The correct answer is:

13.33 Ohm, 11.5A, 5.75A. 17.25A/ 2645W,661.25W,661.25W, 3967.5W

Question **15**

Not answered

Marked out of 1.00

1. The resistance of a conductor is said to be:

- a. (c) proportional to its cross-sectional area.
- b. (b) inversely proportional to its length.
- c. (d) inversely proportional to its resistivity.
- d. (a) proportional to its length.

Your answer is incorrect.

The correct answer is:

(a) proportional to its length.

Question **16**

Not answered

Marked out of 1.00

1. If all other factors remain constant while the length of a conductor is halved, the resistance of the conductor is:

- a. (d) quartered
- b. (c) halved
- c. (b) squared
- d. (a) doubled.

Your answer is incorrect.

The correct answer is:

(c) halved

Question **17**

Not answered

Marked out of 1.00

2. The voltmeter sensitivity or the resistance of a voltmeter is given in terms of:

- a. (d) ampere per volt.
- b. (c) volts per ampere
- c. (a) volts per ohm
- d. (b) ohms per volt

Your answer is incorrect.

The correct answer is:

(b) ohms per volt

Question **18**

Not answered

Marked out of 1.00

2. An AVO-7 multimeter has a sensitivity of 500 ohms/volt. Determine the resistance of the meter when used on the:

- (a) 25 V range
 (b) 1000 V range.
- a. 22500 ohm, 5Mega Ohm
 b. 12500 ohm, 0.5Mega Ohm
 c. 32500 ohm, 1.5Mega Ohm

Your answer is incorrect.

The correct answer is:

12500 ohm, 0.5Mega Ohm

Question **19**

Not answered

Marked out of 1.00

Determine

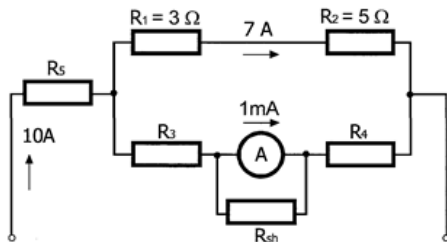


figure 19

- (a) the value of the current through Rsh.
 (b) the voltage drop across R2
 (c) the power rating of R1

- a. 2.99 A, 35V, 147W
 b. 3A,40V, 150W
 c. 7A, 30V, 147W

Your answer is incorrect.

The correct answer is:

2.99 A, 35V, 147W

Question **20**

Not answered

Marked out of 1.00

1. Which of the following cannot be used as a dielectric:

- a. (b) paper
- b. (c) carbon
- c. (d) polyester
- d. (a) air

Your answer is incorrect.

The correct answer is:

(c) carbon

Question **21**

Not answered

Marked out of 1.00

1. Decreasing the plate area of a capacitor:

- a. (c) decreases its capacitance
- b. (b) does not effect its capacitance
- c. (a) increases its capacitance
- d. (d) increases its dielectric strength

Your answer is incorrect.

The correct answer is:

(c) decreases its capacitance

Question **22**

Not answered

Marked out of 1.00

1. The practical unit of capacitance is the:

- a. (a) micro-coulomb
- b. (c) micro-farad
- c. (d) farad.
- d. (b) milli-farad

Your answer is incorrect.

The correct answer is:

(c) micro-farad

Question **23**

Not answered

Marked out of 1.00

1. An R-C circuit consists of a resistance of $120\text{k}\Omega$ and a capacitance of $36\mu\text{F}$. Determine the -

- (a) time constant of the circuit
- (b) time taken for the capacitor to fully charge.

- a. (5.32 seconds) (30 seconds)
- b. (4.32 seconds) (21.6 seconds)
- c. (3.32 seconds) (20.6 seconds)

Your answer is incorrect.

The correct answer is:

(4.32 seconds) (21.6 seconds)

Question **24**

Not answered

Marked out of 1.00

1. An R-C circuit has an applied voltage of 24V. What is the voltage across the capacitor after one time constant.

- a. 15.17V
- b. 12V
- c. 10V

Your answer is incorrect.

The correct answer is:

15.17V

Question **25**

Not answered

Marked out of 1.00

Two, $2\mu\text{F}$ capacitors connected in parallel will have a total capacitance of:

- a. 1
- b. 4
- c. 2
- d. 0.5

Your answer is incorrect.

The correct answer is:

4

Question **26**

Not answered

Marked out of 1.00

Two, $4\mu\text{F}$ capacitors connected in series will have a total capacitance of:

- a. 4
- b. 0.5
- c. 2
- d. 1

Your answer is incorrect.

The correct answer is:

2

Question **27**

Not answered

Marked out of 1.00

Three capacitors having capacitances of 4, 6 and $12\mu\text{F}$ are connected in series across a 120V supply. Calculate the –

- (a) equivalent capacitance
- (b) total charge stored
- (c) charge stored on each capacitor

- a. ($1\mu\text{F}$)(0.00048C) (0.00048C)
- b. ($2\mu\text{F}$)(0.00024C) (0.00024C)

Your answer is incorrect.

The correct answer is:

($2\mu\text{F}$)(0.00024C) (0.00024C)

Question **28**

Not answered

Marked out of 1.00

Three capacitors are connected in series have an equivalent capacitance of $10\mu\text{F}$. If two of them have capacitances of 30 and $60\mu\text{F}$, determine the capacitance of the third capacitor.

- a. 5
- b. 20
- c. 15
- d. 10

Your answer is incorrect.

The correct answer is:

20

[◀ Week 1 Quiz](#)

Jump to...