

[Dashboard](#) / [My courses](#) / [Electrical Fundamentals](#) / [TUTORIALS](#) / [Week 3 Quiz](#) / [Preview](#)

**Started on** Monday, 4 March 2024, 7:17 PM

**State** Finished

**Completed on** Monday, 4 March 2024, 7:17 PM

**Time taken** 14 secs

**Marks** 0.00/20.00

**Grade** 0.00 out of 10.00 (0%)

Question **1**

Not answered

Marked out of 1.00

1. The value of AC voltage shown on the name plate of an appliance is the:

- a. (d) r.m.s. value
- b. (a) average value
- c. (b) peak value
- d. (c) instantaneous value

Your answer is incorrect.

The correct answer is:

(d) r.m.s. value

Question **2**

Not answered

Marked out of 1.00

1. The value of AC voltage that has the same heating effect as the equivalent value of DC voltage is the:

- a. (a) rms value.
- b. (d) peak to peak value.
- c. (b) peak value.
- d. (c) average value.

Your answer is incorrect.

The correct answer is:

(a) rms value.

Question **3**

Not answered

Marked out of 1.00

1. For one complete cycle of an AC supply, the current flow:

- a. (c) will flow in one direction then reverses direction.
- b. (d) reaches a maximum in one direction then falls to zero.
- c. (a) will remain constant in magnitude.
- d. (b) will flow in one direction only.

Your answer is incorrect.

The correct answer is:

(c) will flow in one direction then reverses direction.

Question **4**

Not answered

Marked out of 1.00

1. The standard unit of frequency is the:

- a. (c) period (T)
- b. (a) Hertz (Hz)
- c. (d) cycle per second (CPS)
- d. (b) Volt (V)

Your answer is incorrect.

The correct answer is:

(a) Hertz (Hz)

Question **5**

Not answered

Marked out of 1.00

1. A sinusoidal wave has a maximum value of 340 volts. Determine the instantaneous value of voltage at angles of:

(a)  $45^\circ$

(A sinusoidal wave has a frequency of 400 Hz.. Determine the period for this frequency.

- a. (120V) (5mS)
- b. (240V) (2.5mS)
- c. (200V) (3mS)

Your answer is incorrect.

The correct answer is:

(240V) (2.5mS)

Question **6**

Not answered

Marked out of 1.00

1. When measuring the phase difference with a CRO., the CRO.

- a. (a) must be able to show two waveforms.
- b. (c) time base must be re-calibrated.
- c. (d) must be set to DC input.
- d. (b) needs to have a high sensitivity.

Your answer is incorrect.

The correct answer is:

(a) must be able to show two waveforms.

Question **7**

Not answered

Marked out of 1.00

Phasors are quantities which vary in:

- a. (b) magnitude and direction only
- b. (c) magnitude, direction and time
- c. (a) magnitude and time only
- d. (d)  
(a) direction only

(d) direction only

Your answer is incorrect.

The correct answer is:

(b) magnitude and direction only

Question 8

Not answered

Marked out of 1.00

Two sinusoidal waves with a frequency of 50 Hz are displayed on a CRO. If the horizontal displacement between the waveforms is measured to be 3.5mS, determine the phase angle between the two waveshapes

- a. 30 degree
- b. 90 degree
- c. 63 degree
- d. 45 degree

Your answer is incorrect.

The correct answer is:

63 degree

Question 9

Not answered

Marked out of 1.00

1. The resultant of two or more voltages differing in phase angle may be determined by:

- a. (d) numerical addition
- b. (b) averaging the voltage values
- c. (c) phasor addition
- d. (a) algebraic addition

Your answer is incorrect.

The correct answer is:

(c) phasor addition

Question **10**

Not answered

Marked out of 1.00

240 volt, 50Hz single phase motor draws 18A from the supply at a lagging phase angle of  $40^\circ$ . A capacitor connected across the motor draws 7A at a leading phase angle of  $90^\circ$ , determine the current drawn from the supply

- a. 25A
- b. 14.5A
- c. 20A
- d. 10A

Your answer is incorrect.

The correct answer is:

14.5A

Question **11**

Not answered

Marked out of 1.00

1. The opposition to current flow in a purely capacitive circuit is known as\_\_\_\_\_and is measured in

---

- a. (b) resistance, ohms
- b. (c) capacitive reactance, farads
- c. (d) impedance, farads
- d. (a) capacitive reactance, ohms

Your answer is incorrect.

The correct answer is:

(a) capacitive reactance, ohms

Question **12**

Not answered

Marked out of 1.00

The phase angle (f) between voltage and current in a purely capacitive circuit is:

- a. (a) 180 electrical degrees.
- b. 1.  
(d) 0 electrical degrees.
- (c) 45 electrical degrees.
- (c) 0 electrical degree
- c. (b) 90 electrical degrees.

Your answer is incorrect.

The correct answer is:

(b) 90 electrical degrees.

Question **13**

Not answered

Marked out of 1.00

Adding extra capacitance to a purely capacitive circuit will cause the phase angle (f) between voltage and current to:

- a. (b) decrease.
- b. (d) become maximum.
- c. (a) increase.
- d. (c) remain unchanged.

Your answer is incorrect.

The correct answer is:

(a) increase.

Question **14**

Not answered

Marked out of 1.00

Determine the current taken by a 390mF capacitor when connected to a 240V, 50Hz supply.

- a. (39.4A)
- b. (29.4A)
- c. (49.4A)

Your answer is incorrect.

The correct answer is:

(29.4A)

Question **15**

Not answered

Marked out of 1.00

In a parallel resonant circuit, circuit impedance is a\_\_\_\_\_, and circuit current is a\_\_\_\_\_.

- a. (b) minimum, minimum
- b. (d) minimum, maximum
- c. (a) maximum, maximum
  
- d. (c) maximum, minimum

Your answer is incorrect.

The correct answer is:

(c) maximum, minimum



Question **16**

Not answered

Marked out of 1.00

1. Adding extra capacitance to a leading R.L.C. parallel circuit will cause the phase angle ( $\phi$ ) between voltage and current to:

- a. (c) become maximum.
- b. (b) increase.
- c. (a) remain unchanged.
- d. (d) decrease.

Your answer is incorrect.

The correct answer is:

(b) increase.

Question **17**

Not answered

Marked out of 1.00

In a parallel L.C. circuit, the component with the largest \_\_\_\_\_ will determine the phase angle for the circuit.

- a. (b) voltage
- b. (d) resistance
- c. (a) current
- d. (c) reactance

Your answer is incorrect.

The correct answer is:

(c) reactance

Question **18**

Not answered

Marked out of 1.00

1. An L.C. parallel circuit is connected to a single phase 240V, 50Hz supply. If the current through the capacitor 12A, and the current through the inductor is 16A at a phase angle of  $60^\circ$  lagging, determine the:

- (a) impedance of the inductor;
- (b) resistance of the inductor;
- (c) impedance of the capacitor;
- (d) current drawn from the supply; )
- (e) circuit impedance;

- a. (25 ohm) (8.5 ohm) (20 ohm) (8.2A) (30.3 ohm)
- b. (35 ohm) (17.5 ohm) (50 ohm) (8.2A) (29.3 ohm)
- c. (15 ohm) (7.5 ohm) (20 ohm) (8.2A) (29.3 ohm)

Your answer is incorrect.

The correct answer is:

(15 ohm) (7.5 ohm) (20 ohm) (8.2A) (29.3 ohm)

Question **19**

Not answered

Marked out of 1.00

An 80 ohm resistor connected in parallel with a 33mF capacitor is connected to a 250V, 50Hz supply. Determine by phasor diagram the current drawn from the supply and the circuit phase angle using a scale of 1mm = 0.05A.

- a. 6 A, 20 degree
- b. 4A, 40 Degree
- c. 2A 40 Degree

Your answer is incorrect.

The correct answer is:

4A, 40 Degree

Question **20**

Not answered

Marked out of 1.00

1. The opposition to current flow in any ac circuit containing\_\_\_\_\_and reactive components is known as\_\_\_\_\_and is measured in ohms.

- a. (c) resistive, impedance
- b. (a) capacitive , reactance
- c. (d) inductive, impedance
- d. (b) inductive reactance

Your answer is incorrect.

The correct answer is:

(c) resistive, impedance

[◀ Week 2 Quiz](#)

Jump to...