

1. The value of AC voltage shown on the name plate of an appliance is the:
    - (a) average value
    - (b) peak value
    - (c) instantaneous value
    - (d) r.m.s. value
  
  2. The value of AC voltage that has the same heating effect as the equivalent value of DC voltage is the:
    - (a) rms value.
    - (b) peak value.
    - (c) average value.
    - (d) peak to peak value.
  
  3. For one complete cycle of an AC supply, the current flow:
    - (a) will remain constant in magnitude.
    - (b) will flow in one direction only.
    - (c) will flow in one direction then reverses direction.
    - (d) reaches a maximum in one direction then falls to zero.
  
  4. The standard unit of frequency is the:
    - (a) Hertz (Hz)
    - (b) Volt (V)
    - (c) period (T)
    - (d) cycle per second (CPS)
-

5. A sinusoidal wave has a maximum value of 340 volts. Determine the instantaneous value of voltage at angles of:
- (a)  $45^\circ$  (240V)
- (A sinusoidal wave has a frequency of 400 Hz.. Determine the period for this frequency. (2.5mS)

1. When measuring the phase difference with a CRO., the CRO.
    - (a) must be able to show two waveforms.
    - (b) needs to have a high sensitivity.
    - (c) time base must be re-calibrated.
    - (d) must be set to DC input.
  2. Phasors are quantities which vary in:
    - (a) magnitude and time only
    - (b) magnitude and direction only
    - (c) magnitude, direction and time
    - (d) direction only
  3. Two sinusoidal waves with a frequency of 50 Hz are displayed on a CRO. If the horizontal displacement between the waveforms is measured to be 3.5mS, determine the phase angle between the two waveshapes ( $63^\circ$ )
- 
1. Current phasors are represented by an arrow with a/an\_\_head, whilst voltage phasors are represented by an arrow with a/an\_\_head.
    - (a) closed, open
    - (b) open, open
    - (c) open, closed
    - (d) closed, closed
  2. The resultant of two or more voltages differing in phase angle may be determined by:
    - (a) algebraic addition
    - (b) averaging the voltage values
    - (c) phasor addition
    - (d) numerical addition
  3. A 240 volt, 50Hz single phase motor draws 18A from the supply at a lagging phase angle of  $40^\circ$ . A capacitor connected across the motor

dra  
 ws  
 7A  
 at a  
 lead  
 ing  
 pha  
 se  
 angl  
 e of  
 $90^\circ$ .  
 Usi  
 ng a  
 scal  
 e of  
 1m  
 m =  
 0.2  
 A,  
 dete  
 rmin  
 e  
 the  
 curr  
 ent  
 dra  
 wn  
 fro  
 m  
 the  
 sup  
 ply,  
 and  
 the  
 resu  
 ltant  
 circ  
 uit  
 pha  
 se  
 angl

e. [14.5A @ 18.5° lag]

and \_\_\_\_\_

1. The opposition to current flow in a purely capacitive circuit is known as\_\_and is measured in \_\_\_\_
  - (a) capacitive reactance, ohms
  - (b) resistance, ohms
  - (c) capacitive reactance, farads
  - (d) impedance, farads
  
2. The phase angle ( $\phi$ ) between voltage and current in a purely capacitive circuit is:
  - (a) 180 electrical degrees.
  - (b) 90 electrical degrees.
  - (c) 45 electrical degrees.
  - (d) 0 electrical degrees.

3. Adding extra capacitance to a purely capacitive circuit will cause the phase angle ( $\phi$ ) between voltage and current to:
    - (a) increase.
    - (b) decrease.
    - (c) remain unchanged.
    - (d) become maximum.
  
  4. Determine the capacitive reactance of a  $47\mu\text{F}$  capacitor when connected to a 32V, 50Hz supply. ( $67.7\Omega$ )
  5. Determine the current taken by a  $390\mu\text{F}$  capacitor when connected to a 240V, 50Hz supply. (29.4A)
  6. A capacitor takes 3A when connected to a 240V, 50Hz supply. Determine:
    - (a) the capacitive reactance of the capacitor; ( $80\Omega$ )
    - (b) the capacitance of the capacitor. ( $39.8\mu\text{F}$ )
  
  1. Adding extra inductance to an R.L. series circuit will cause the phase angle ( $\phi$ ) between voltage and current to:
    - (a) remain unchanged.
    - (b) increase.
    - (c) become maximum.
    - (d) decrease.
  2. The opposition to current flow in any ac circuit containing \_\_\_ and reactive components is known as \_\_\_ and is measured in ohms.
    - (a) capacitive , reactance
    - (b) inductive reactance
    - (c) resistive, impedance
    - (d) inductive, impedance
  
  1. In a parallel resonant circuit, circuit impedance is a \_\_\_, and circuit current is a \_\_\_\_\_.
    - (a) maximum, maximum
    - (b) minimum, minimum
    - (c) maximum, minimum
    - (d) minimum, maximum
  2. Adding extra capacitance to a leading R.L.C. parallel circuit will cause the phase angle ( $\phi$ ) between voltage and current to:
    - (a) remain unchanged.
    - (b) increase.
    - (c) become maximum.
    - (d) decrease.
-

3. In a parallel L.C. circuit, the component with the largest\_\_\_will determine the phase anglefor the circuit.
  - (a) current
  - (b) voltage
  - (c) reactance
  - (d) resistance
  
4. An L.C. parallel circuit is connected to a single phase 240V, 50Hz supply. If the current through the capacitor 12A, and the current through the inductor is 16A at a phase angle of  $60^{\circ}$  lagging, determine the:
  - (a) impedance of the inductor; ( $15\Omega$ )
  - (b) resistance of the inductor; ( $7.5\Omega$ )
  - (c) impedance of the capacitor; ( $20\Omega$ )
  - (d) current drawn from the supply; ( $8.2A$ ) ( $1mm = 0.2A$ )
  - (e) circuit phase angle. ( $13.1^{\circ}$  lag)
  - (f) circuit impedance; ( $29.3\Omega$ )
  
5. An  $80\Omega$  resistor connected in parallel with a  $33\mu F$  capacitor is connected to a 250V, 50Hz supply. Determine by phasor diagram the current drawn from the supply and the circuit phase angle using a scale of  $1mm = 0.05A$ . ( $4A$ ;  $\phi = 40^{\circ}$  lead)

1. 240 volt, 50Hz single phase motor draws 18A from the supply at a lagging phase angle of  $40^{\circ}$ . A capacitor connected across the motor draws 7A at a leading phase angle of  $90^{\circ}$ . Using a scale of  $1mm = 0.2A$ , determine the current drawn from the supply, and the resultant circuit phase angle.
 

[ $14.5A @ 18.5^{\circ}$  lag]