

[Dashboard](#) / [My courses](#) / [Electrical Fundamentals](#) / [TUTORIALS](#) / [Week 4 Quiz](#) / [Preview](#)

**Started on** Monday, 4 March 2024, 8:01 PM

**State** Finished

**Completed on** Monday, 4 March 2024, 8:01 PM

**Time taken** 12 secs

**Marks** 0.00/16.00

**Grade** 0.00 out of 10.00 (0%)

Question **1**

Not answered

Marked out of 1.00

1. True power is measured in \_\_\_\_\_ and is a measure of the \_\_\_\_\_.

- a. (b) volt-amps ; power consumed
- b. (c) watts; power consumed
- c. (a) volt-amps; power supplied
- d. (d) watts; power supplied

Your answer is incorrect.

The correct answer is:

(c) watts; power consumed

Question **2**

Not answered

Marked out of 1.00

1. In a purely resistive circuit there is no:

- a. (a) apparent power
- b. (b) true power
- c. (c) average power
- d. (d) reactive power

Your answer is incorrect.

The correct answer is:

(d) reactive power

Question **3**

Not answered

Marked out of 1.00

1. In a power triangle, apparent power is represented by the:

- a. (a) side adjacent the phase angle
- b. (b) hypotenuse
- c. (c) side opposite the phase angle
- d. (d) cosine of the phase angle

Your answer is incorrect.

The correct answer is:

(b) hypotenuse

Question **4**

Not answered

Marked out of 1.00

1. Power factor is a ratio of:

- a. 1. Power factor is a ratio of:
- (b) true power to reactive power
- b. (a) reactive power to apparent
- c. (c) apparent power to true power
- d. (d) true power to apparent power

Your answer is incorrect.

The correct answer is:

(d) true power to apparent power

Question **5**

Not answered

Marked out of 1.00

1. The power consumed in a circuit is determined by:

- a. (d) true power plus the power factor
- b. (c) reactive power times the power factor
- c. (b) apparent power divided by the power factor
- d. (a) apparent power times the power factor

Your answer is incorrect.

The correct answer is:

(a) apparent power times the power factor

Question **6**

Not answered

Marked out of 1.00

1. A heating element connected to a 240V, 50Hz supply draws 10A. Determine the:

- (a) the circuit phase angle.
- (b) apparent power of the circuit;
- (c) true power consumed by the circuit.

- a. ( $0^\circ$ ) (2400VA) (2400W)
- b. ( $0^\circ$ ) (4800VA) (4800W)
- c. ( $0^\circ$ ) (1200VA) (1200W)

Your answer is incorrect.

The correct answer is:

( $0^\circ$ ) (2400VA) (2400W)

Question **7**

Not answered

Marked out of 1.00

1. A single phase load draws 2.5A from a 32V, 50Hz supply. If the power consumed by the circuit is 60W, determine the:

- (a) the circuit impedance;
- (b) apparent power of the circuit;
- (c) circuit power factor;
- (d) circuit phase angle;
- (e) reactive power of the circuit; (

- a. (12.8ohm) (80VA) (0.75) ( $41.4^\circ$ ) 52.9VAr
- b. (32.8ohm) (8VA) (0.85) ( $41.4^\circ$ ) 52.9VAr
- c. 212.8ohm) (100VA) (0.75) ( $41.4^\circ$ ) 52.9VAr

Your answer is incorrect.

The correct answer is:

(12.8ohm) (80VA) (0.75) ( $41.4^\circ$ ) 52.9VAr

Question **8**

Not answered

Marked out of 1.00

1. Positive phase sequence is represented by:

- a. (a) B-A-C
- b. (d) A-C-B
- c. (b) C-B-A
- d. (c) A-B-C

Your answer is incorrect.

The correct answer is:

(c) A-B-C

Question **9**

Not answered

Marked out of 1.00

1. Single phase loads can be connected to a three phase distribution system that is:

- a. (a) delta connected with three wires
- b. (b) delta connected with four wires
- c. (c) star connected with three wires
- d. (d) star connected with four wires

Your answer is incorrect.

The correct answer is:

(d) star connected with four wires

Question **10**

Not answered

Marked out of 1.00

1. In a star connected system, the phase angle between the line voltage and phase voltage is:

- a.  $90^\circ$
- b.  $0^\circ$
- c.  $120^\circ$
- d.  $30^\circ$

Your answer is incorrect.

The correct answer is:

$120^\circ$

Question **11**

Not answered

Marked out of 1.00

1. The minimum number of fixed wattmeters required to measure the power consumed by a three phase, four wire unbalanced system is:

- a. three
- b. two
- c. one
- d. four

Your answer is incorrect.

The correct answer is:

two

Question **12**

Not answered

Marked out of 1.00

1. The total power in a three phase system can be measured using a single wattmeter provided the:

- a. () load is unbalanced
- b. () load is balanced
- c. () load is star connected
- d. () neutral is not connected

Your answer is incorrect.

The correct answer is:

load is balanced

Question **13**

Not answered

Marked out of 1.00

An indication that harmonics are present in a three phase supply system would be:

- a. (c) low neutral currents
- b. (b) low transformer currents
- c.  
r
- (d) lower power consumption
- d. (a) erratic motor behaviour

Your answer is incorrect.

The correct answer is:

low neutral currents

Question **14**

Not answered

Marked out of 1.00

1. A 415V uses the two wattmeter method to measure its total power consumption. If  $W_1$  indicates -750W and  $W_2$  indicates 2 kW, determine:

- the Total power supplied to the load;
- the Power factor for the load;
- the Line current for the load;

the Impedance of each phase of the load if the load is star connected.

- a. (1250W) (0.254 lead) (6.85A) (35.2 ohm)
- b. (2750W) (0.254 lead) (6.85A) (35.2 ohm)
- c. (1250W) (0.8 lead) (6.85A) (35.2 ohm)

Your answer is incorrect.

The correct answer is:

(1250W) (0.254 lead) (6.85A) (35.2 ohm)


Question **15**

Not answered

Marked out of 1.00

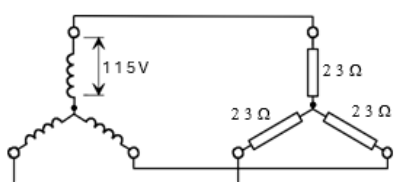1. For the circuit of figure 3, determine the:

- line voltage output of the transformer secondary;
- phase voltage of the heating load;
- line current from the transformer to the load;
- power used by the load, assuming the power factor is unity



Transformer  
Secondary

3 Phase  
Heater

Figure 3

- a. (400V) (115V) (5A) (1.732kW)
- b. (200V) (115V) (5A) (1.732kW)
- c. (4000V) (2305V) (5A) (1.732kW)

Your answer is incorrect.

The correct answer is:

(200V) (115V) (5A) (1.732kW)



Question **16**

Not answered

Marked out of 1.00

1. A delta connected transformer secondary supplies a star connected inductive load. The power consumption of the load is measured at 15kW at a power factor of 0.695. If the phase current of the load is 30A, determine the:

- (a) line voltage output of the transformer;
- (a) phase voltage of the load;
- (b) phase angle for the load;
- (c) current in the transformer windings.

- a. (415V) (240V) ( $46^\circ$  lag) (17.32A)
- b. (230V) (115V) ( $46^\circ$  lag) (17.32A)
- c. (230V) (115V) ( $30^\circ$  lag) (17.32A)

Your answer is incorrect.

The correct answer is:

(415V) (240V) ( $46^\circ$  lag) (17.32A)

[◀ Week 3 Quiz](#)

Jump to...