

①

TO 3.1 calculate the touch voltage for a single phase final sub circuit having 4mm^2 active conductor having a percent impedance of 1.0% and 2.5mm^2 earthing conductor having a percent impedance of 2.4% where the operating voltage of installation is 230V .

$$V_t = \frac{V_o \times Z_{PE}}{(Z_A + Z_{PE})} =$$

$V_t =$ Touch voltage

$V_o =$ operating voltage

$Z_A =$ Impedance of active conductor

$Z_{PE} =$ Protective earthing conductor (percent impedance)


$$Z_A = 1\%, \quad Z_{PE} = 2.4\%, \quad V_o = 230\text{V}$$

$$\therefore V_t = \frac{230 \times 2.4}{(1 + 2.4)} = \frac{230 \times 2.4}{3.4} = \quad \checkmark$$


TO 3.2 List 4 methods to protect against direct contact

TO 3.11 For the loop shown below

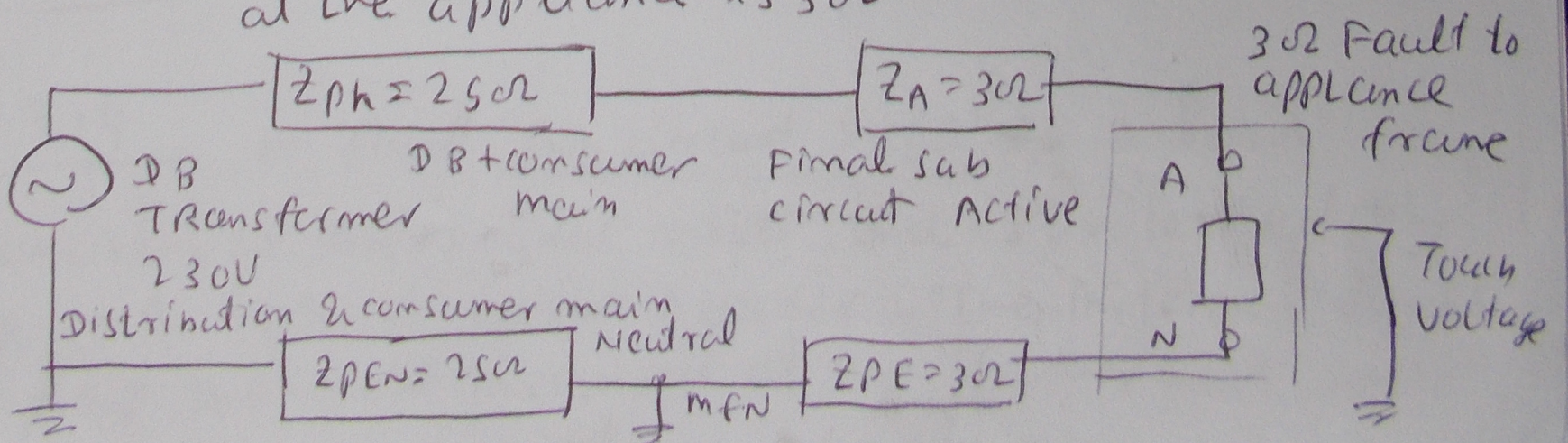- calculate the fault loop impedance
- The maximum fault current that will flow in the circuit
- The fault current if the fault resistance at the appliance is 3Ω



(2)

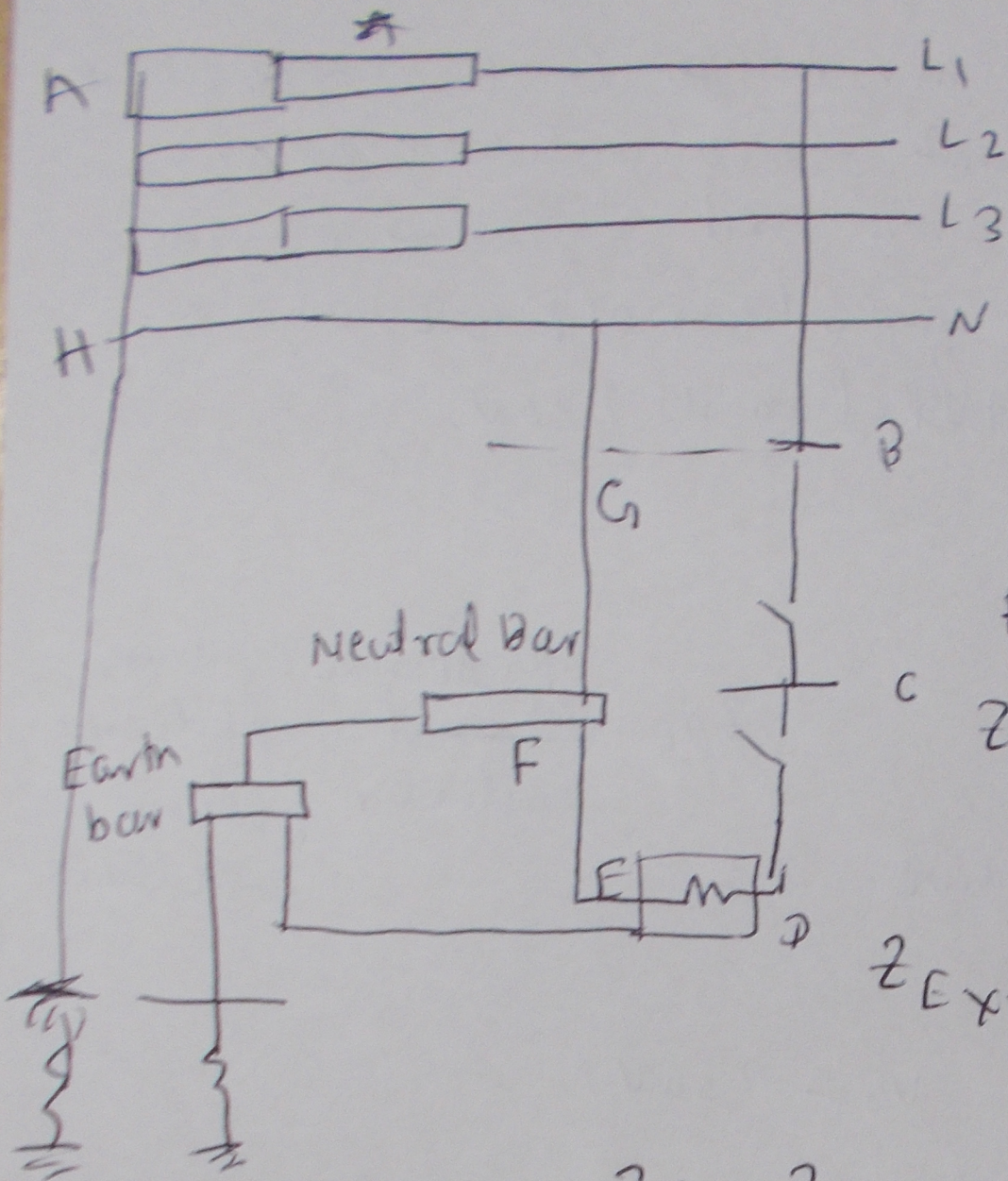

Point of supply

Fault loop Impedance

$$Z_s = 2Z_{AB} + 2Z_C + Z_{CD} + Z_{EF} + Z_{GH} + Z_{HA}$$

$$Z_{Ext} = 2Z_{AB} + 2Z_C + Z_{CD} + Z_{FG} + Z_{GH} + Z_{HA}$$

$$Z_s = Z_{int} + Z_{Ext}$$

$$Z_{\text{fault loop}} = 0.25\Omega + 3\Omega + 0\Omega + 3\Omega + 0.25\Omega = 9.5\Omega$$

$$I_{\text{fault}} = \frac{230}{9.5} \approx 35.3\text{A}$$

If fault resistance at appliance is 3Ω

$$I_{\text{fault}} = \frac{230}{9.5} = 24.2\text{A}$$

(3)

For TO 3.12

Find cable resistance by referring the table on

page 15.

$$\text{Source} = 0.028 \Omega$$

$$25 \text{mm}^2 - 90 \text{m} \rightarrow 0.0330 \Omega$$

$$6 \text{mm}^2 - 25 \text{m} \rightarrow 0.0755 \Omega$$

$$4 \text{mm}^2 - 25 \text{m} \rightarrow 0.1130 \Omega$$

$$3.5 \text{mm}^2 - 50 \text{m} \rightarrow 0.0257 \Omega$$

$$\begin{aligned} Z_{\text{fault loop}} &= 0.0330 + 0.0755 + 0.1130 + 0.0257 \\ &\quad + 0.028 \\ &= 0.2472 \Omega + 0.028 \\ &= 0.2752 \Omega \end{aligned}$$

$$I_{\text{fault}} = \frac{230 \text{V}}{0.2752 \Omega} = 835 \text{A}$$

$$\text{Fault resistance } 3 \Omega \rightarrow \frac{230}{3.2752} = 70.22 \text{A}$$

TO 3.13 A final sub circuit supplies a load consisting of 10A socket outlet and is protected by a 20A type C circuit breaker. Determine the maximum fault loop impedance of the final sub circuit based on 230V, when supply is unavailable.

Table 8.1 page 10 $20\text{A-CB} \rightarrow \text{Type(C)} \quad 1.93 \Omega$

TO 3.14 A final sub circuit supplies a load consisting of 10A socket outlet and is protected by a 16A type C circuit breaker. The internal fault loop impedance measured at the furthestmost socket

(4)

outlet is 1.2Ω . Determine whether this value of internal fault loop impedance based on 230V satisfies the requirements of AS/NZS 3000:

Table 8.1 page 10

16A, Type C, 230V $Z_{\text{fault loop}} = 1.92\Omega$

Now 1.2Ω is lower than 1.92Ω

It satisfies AS 3000.

TO 3.15, TO 3.16 Do it yourself

TO 3.17 HRC fuse

A final subcircuit supplies a load consisting of 15 A socket outlet and is protected by a 2 SA HRC Fuse. Determine the maximum internal fault loop impedance of the final subcircuit based on 230V when supply is unavailable.

Table 8.1 page 10

2 SA HRC fuse $\rightarrow 1.64\Omega$

TO 3.18 Determine the maximum route length of a circuit in accordance with AS/NZS 3000:2007 for a single phase circuit that has an active conductor size of 6mm^2 and a 2.5mm^2 earthing conductor if the circuit is protected by a 40A circuit breaker with a type D curve

(5)

$$L_{max} = \frac{0.8 U_0 S_{pn} S_{pe}}{I_a \rho (S_{pn} + S_{pe})}$$

L_{max} = maximum ~~the~~ route length in metre

U_0 = Nominal phase voltage (230V)

ρ = Resistivity $\Omega\text{-mm}^2/\text{m}$ \rightarrow 22×10^{-3} (Copper)
 36×10^{-3} (Aluminium)

I_a = Trip current setting

S_{pn} = cross sectional Area of active conductor

S_{pe} = cross sectional area of protective earthing conductor.

Table B 1 page 460 / of AS/NZS 3000
2016

Active / Neutral conductor	Earth conductor	C_B	C-curve	2-5% volt drop
6mm^2	2.5mm^2	40A	60mm	14 31mm

Type D

Time \uparrow
current \rightarrow

0.4602 Table B.1

To 3.19, To 3.20 do it yourself

(6)

T03-29 Given a 11kV/400V (Delta/star) 600 kVA transformer has an impedance of 4%, determine the
 (a) rated current (b) fault current at the transformer secondary terminals (c) fault level at transformer secondary terminals (d) transformer impedance in ohms

$$\text{Rated current} = \frac{\text{kVA}}{\sqrt{3} \times E} = \frac{600 \times 10^3}{1.7321 \times 11 \times 10^3} = 31.49 \text{ A}$$

$$\text{Secondary current} = \frac{\text{kVA}}{\sqrt{3} \times E} = \frac{600 \times 10^3}{1.7321 \times 400} = 866 \text{ A}$$

$$\text{Fault current } - I_{sn} = \frac{I_{fl}}{\%Z} \times 100 = \frac{866}{4} \times 100 = 21650 \text{ A}$$

$$\text{Fault level} = \text{MVA}_{sn} = \frac{\text{MVA}_{fl}}{\%Z} \times 100 = \frac{600}{4} \times 100 = 15 \text{ MVA}$$

$$\%Z = \frac{I_{fl} \times Z_{pn}}{E_{pn}} \times 100$$

$$\Delta = 11 \text{ kV} = E_{pn}$$

$$4 = \frac{31.49 \times Z_{pn}}{11 \times 10^3} \times 100 \Rightarrow Z_{pn} = \frac{4 \times 11000}{31.44 \times 100} = 13.99 \Omega$$

T03-30 A 11kV, (Δ/\star), 500 kVA transformer has a

nominated fault level of 10 MVA, determine
 - prospective fault current at the transformer
 - transformer impedance in ohms.

$$I_{sn} = \frac{\text{MVA}_{sn}}{\sqrt{3} E} = \frac{10 \times 10^6}{1.7321 \times 11 \times 10^3} = 524.8 \text{ A}$$

$$I_{fl} = \frac{500 \times 10^3}{\sqrt{3} \times 11 \times 10^3} = 26.24 \text{ A}$$

$$I_{sn} = \frac{I_{fl}}{\%Z_{pn}} \times 100 \rightarrow 524.8 = \frac{26.24}{\%Z_{pn}} \times 100$$

$$\%Z_{pn} = \frac{26.24}{5.248} = 5.0$$

$$\%Z = \frac{524.2}{15.15 \times 100} = 0.346\%$$

$$\%Z = \frac{I_{FL} \times Z_{pn} \times 100}{E_{pn}}$$

$$0.346 = \frac{15.15 \times Z_{pn} \times 100}{11 \times 10^3}$$

$$Z_{pn} = \frac{0.346 \times 11 \times 10^3}{15.15 \times 100} = 2.51 \Omega$$

To 3.31, do it yourself

To 3.32 for the installation shown below determine the prospective fault current at each relevant point within the installation.

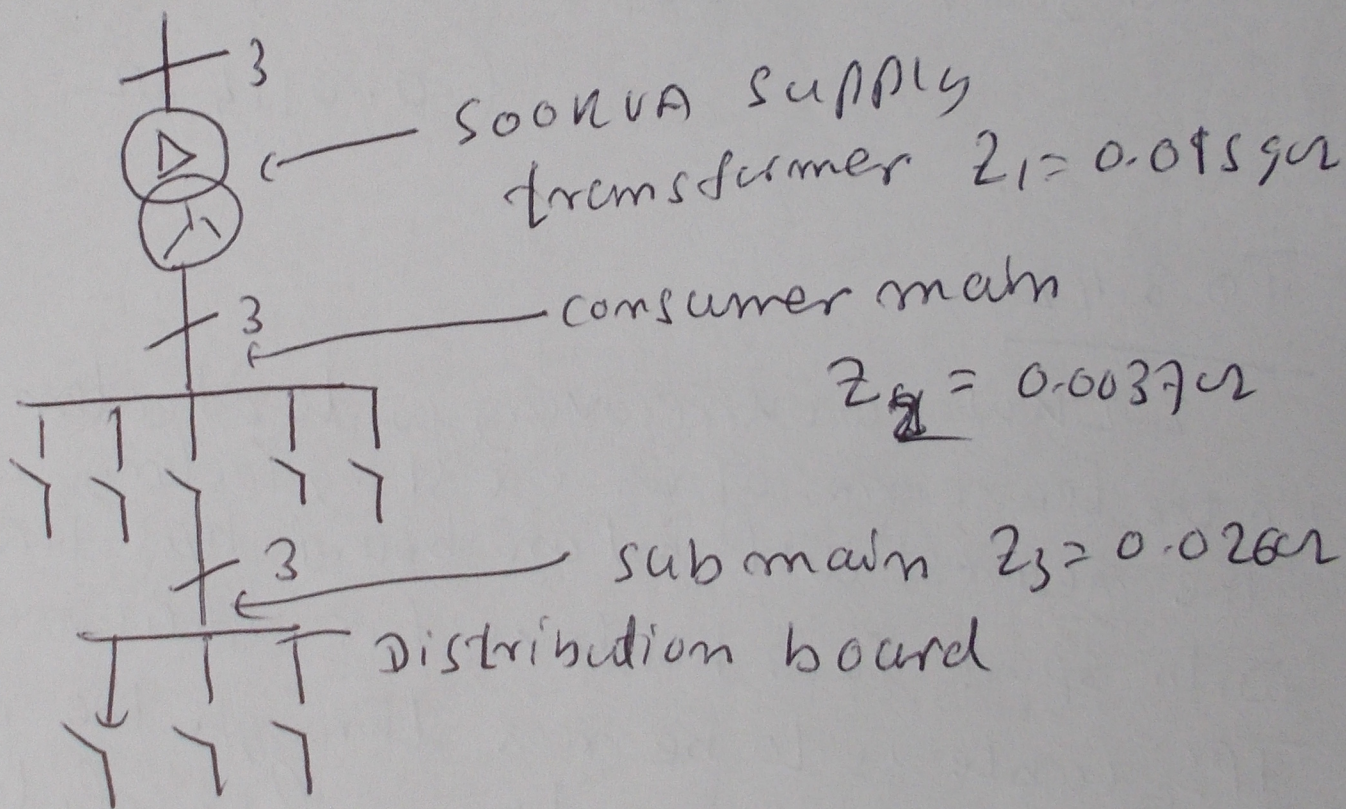


Fig 3.3.3

$$Z_1 = 0.0159 \Omega \rightarrow 3 \text{ kA}$$

$$Z_2 = 0.0037 \Omega \quad 5 \text{ kA}$$

$$Z_3 = 0.028 \Omega = 5 \text{ kA}$$

(8)

To 3.33

A 3 phase 400/230V service supplies the main switchboard to a block of factory units

The supply authority advises that the fault level at the consumer's terminals is 18 kA. The

consumer's mains consist of 50 mm² active conductors and a 35 mm² neutral conductor having a length of 30 meters. Determine the theoretical fault current at the main switchboard. Use the table from Fig 3.3.4 to determine cable impedance.

Active 50 mm² Neutral 35 mm², 30m
(0.0114 Ω)

To 3.42

2.2 kW quick recovery water heater is to be installed in the tea room of an existing factory.

The nearest distribution board has MRC fuses fitted with spare fuse holders for additional circuits. The TPS cable is to be run through the roof space of the tea room which has terminal insulation installed.

- determine maximum demand current
- select a fuse to protect the circuit
- current carrying capacity of cable, assume cable is partially surrounded
- do the values of current comply with $I_B < I_n < I_2$?
- does the arrangement comply with $I_2 < 1.45 I_n$?
- what is required to ensure the circuit will comply?
- Assuming 1.5 mm² cable is used, will the arrangement provide